


EE 230

Lecture 7

Amplifiers

Quiz 6

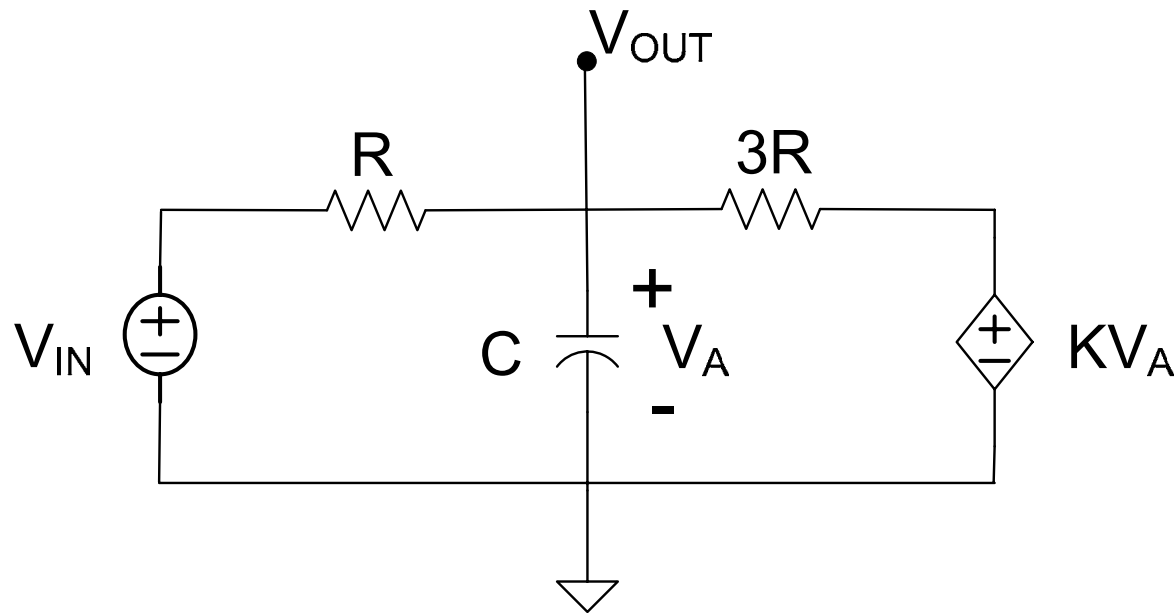Determine the maximum value of the controlling parameter, K , of the dependent source that can be used if the circuit shown is to be stable..



And the number is ?

1

3

8

5

4

2

6

9

7

And the number is ?

1

3

8

5

4

2

6


9

4

7

Quiz 6

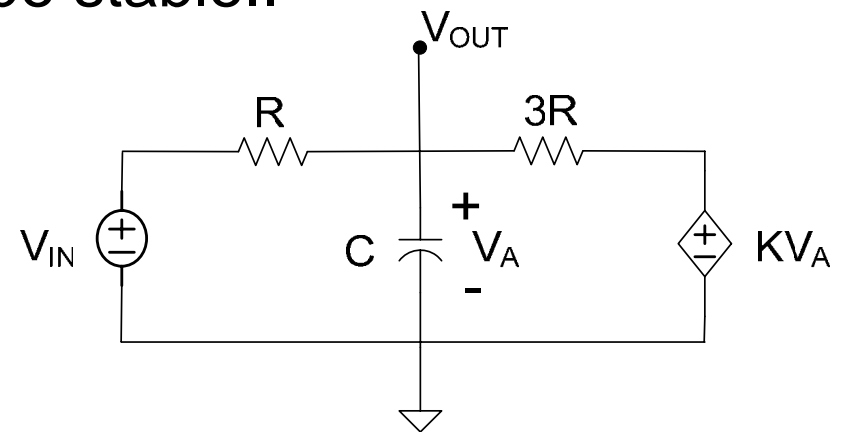Determine the maximum value of the controlling parameter, K , of the dependent source that can be used if the circuit shown is to be stable..



Solution:

Will find the poles of the circuit to determine stability criterion

For convenience define $G = \frac{1}{R}$

$$\left. \begin{aligned} V_{\text{OUT}} \left(G + \frac{G}{3} + sC \right) &= V_{\text{IN}} G + KV_A \frac{G}{3} \\ V_A &= V_{\text{OUT}} \end{aligned} \right\}$$

Quiz 6

Determine the maximum value of the controlling parameter, K , of the dependent source that can be used if the circuit shown is to be stable..

Solution:

For convenience define $G = \frac{1}{R}$

$$\left. \begin{aligned} V_{\text{OUT}} \left(G + \frac{G}{3} + sC \right) &= V_{\text{IN}} G + K V_A \frac{G}{3} \\ V_A &= V_{\text{OUT}} \end{aligned} \right\}$$

Solving we obtain the transfer function

$$T(s) = \frac{G}{sC + G \left(\frac{4-K}{3} \right)}$$

For stability, pole must be in LHP

$$p = \frac{G(K-4)}{3C} < 0 \quad \longrightarrow \quad K < 4$$

Review from Last Time

Stability

A system is stable iff all poles lie in the LHP

A system is stable if any bounded input causes a bounded output

Stability can be a desirable or an undesirable property depending upon the application

Instability is the compliment of stability

Review from Last Time

Systematic strategy for solving electronic circuits

Write a complete set of equations before attempting to solve the equations


(This separates the problem into an engineering part and a mathematics part of the problem)

Nodal analysis often most convenient for solving practical electronic circuits


Short-Hand Strategy for Writing Nodal Equations

$$V_h \sum_k Y_{hk} = \sum_k Y_{hk} V_{hk}$$

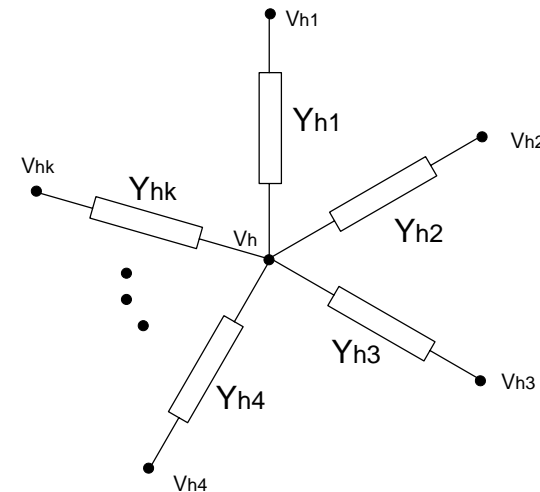where Y_{hk} are conductances adjacent to node h



Amplifiers

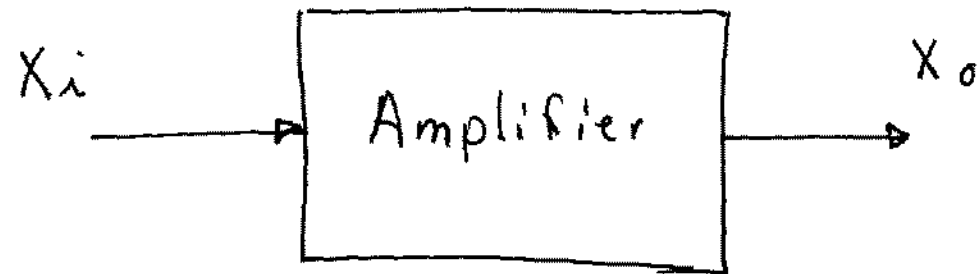

An ideal amplifier is linear and has a frequency independent transfer function that does not change with source or load impedance.

Ideally: $X_o = K X_i$

K is termed amplifier gain

$K = T(s)$. Often $K > 1$

Types of Amplifiers

(variables of interest $\{v, i\}$)


Input	Output	Type	Dimensions
V	V	Voltage	Dimensionless
I	I	Current	"
V	I	Transconductance	A/V
I	V	Transresistance	Ω

Amplifiers are generally not ideal
(but can be nearly ideal)


- Gain can be frequency dependent

$$\frac{X_o}{X_i} = K \quad \rightarrow \quad \frac{X_o}{X_i} = A(s)$$

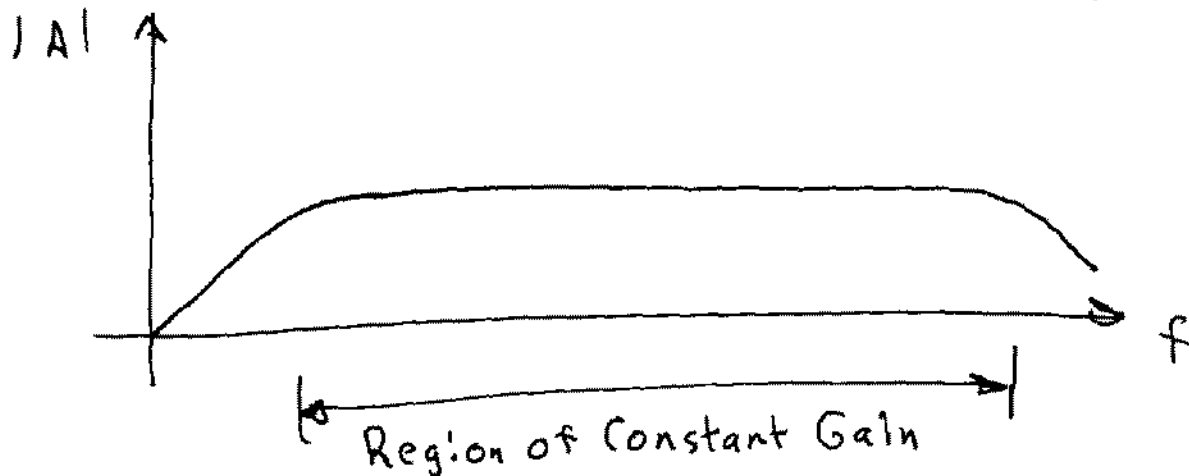- for good practical amplifiers,
 $A(s)$ will be nearly constant over
a wide frequency range



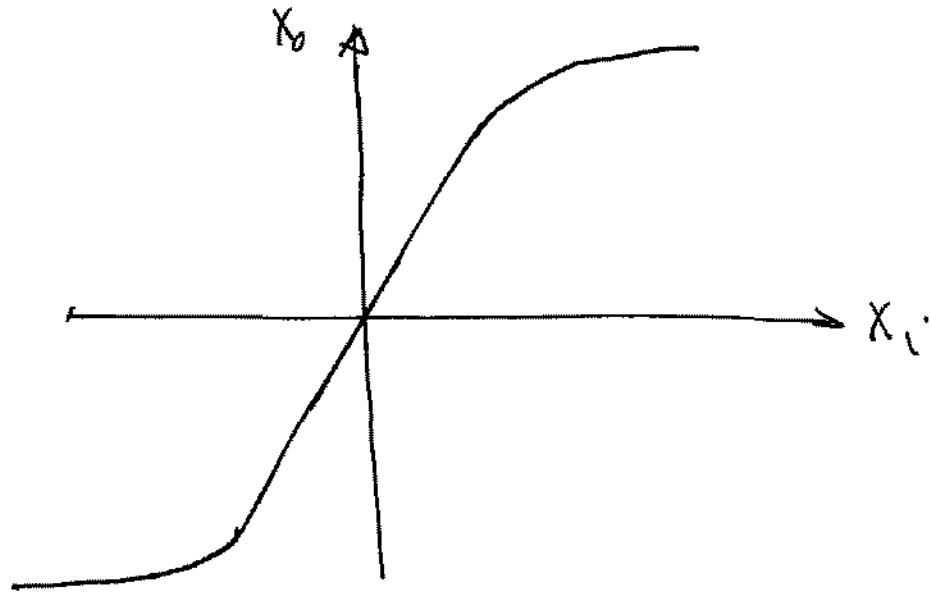
- The amplifier will display some nonlinearity



For a practical amplifier, the output range over which the amplifier is linear or nearly linear can be quite large


- The input and output impedances may not be ideal

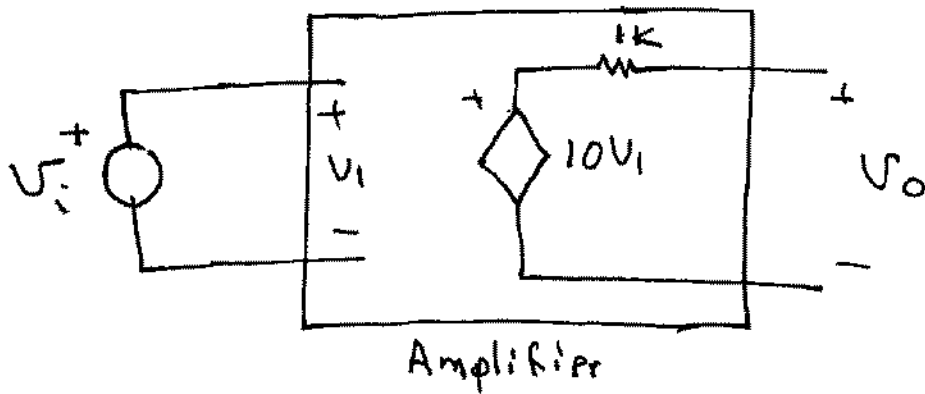Example: Voltage Amplifier, ideally $V_o = KV_i$



$$V_o = 10V_i \quad \text{😊}$$

$$\text{Gain} = 10$$

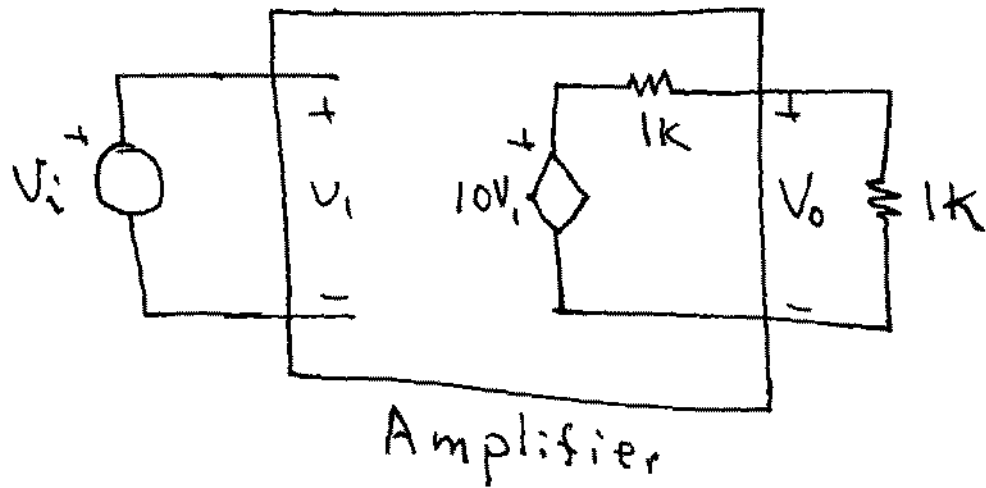



$$V_o = \left(\frac{1k}{1k+1k} \right) 10V_i$$

$$V_o = 5V_i$$

Gain dependent
upon Load



Amplifiers are Two-Port Networks

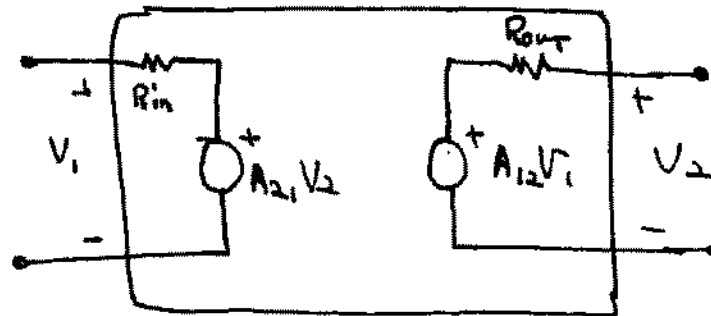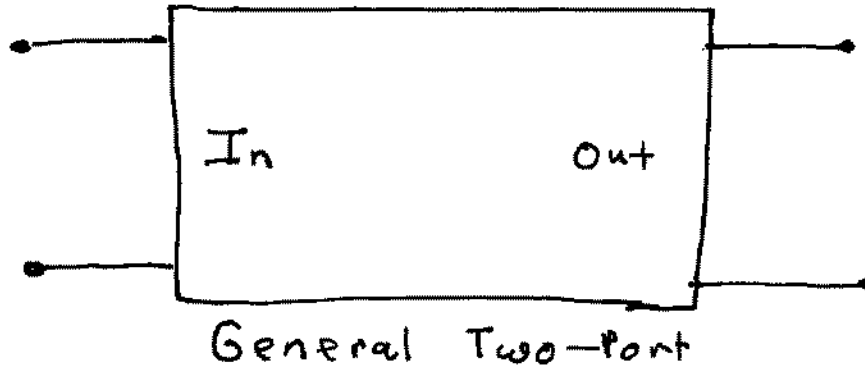


Linear Two-Port
Model

R_{in} : input impedance

R_{out} : output impedance


Amplifiers Ideally Unilateral

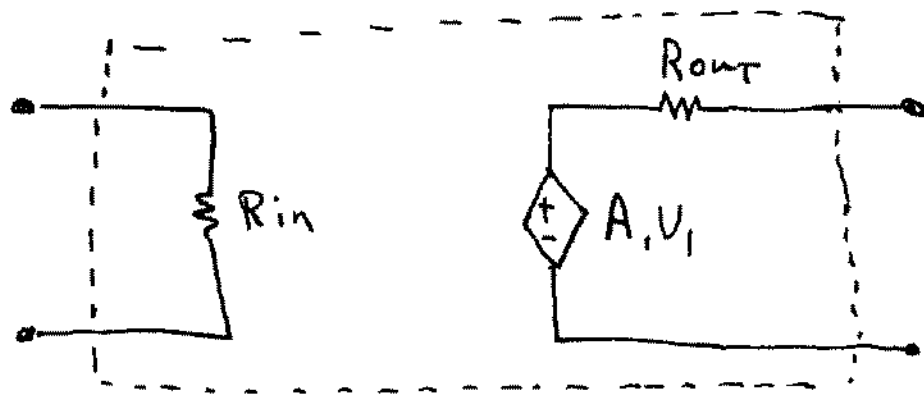- Signals propagate in only one direction




- Dependent sources discussed in EE 201 were actually two-ports but this terminology may not have been used.
- Dependent sources used in SPICE are two-ports
- Dependent sources are amplifiers.

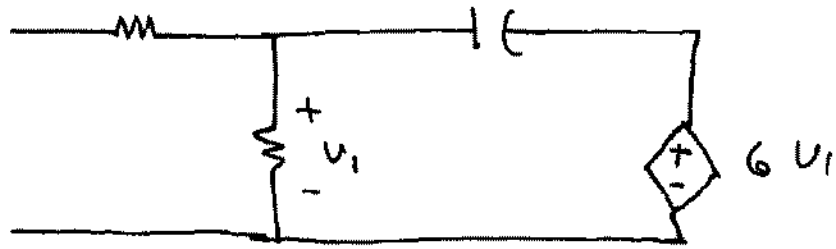Dependent Source Representation from EE 201



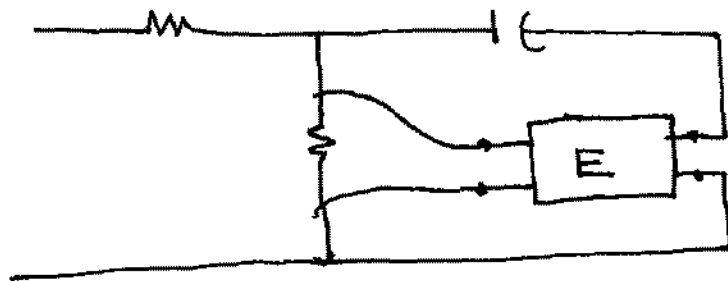Two-port Representation of Dependent Source




Consider 4 basic Amplifiers

- 1) Voltage
- 2) Current
- 3) Transconductance
- 4) Transresistance


- Why so many different amplifier types?
 - because we can have them?
 - some transducers have output variables different than what is needed
 - sometimes perf. can be optimized by using a particular amplifier type
- If the amplifiers are not ideal, they are all functionally the same

Voltage Amplifier


Ideal

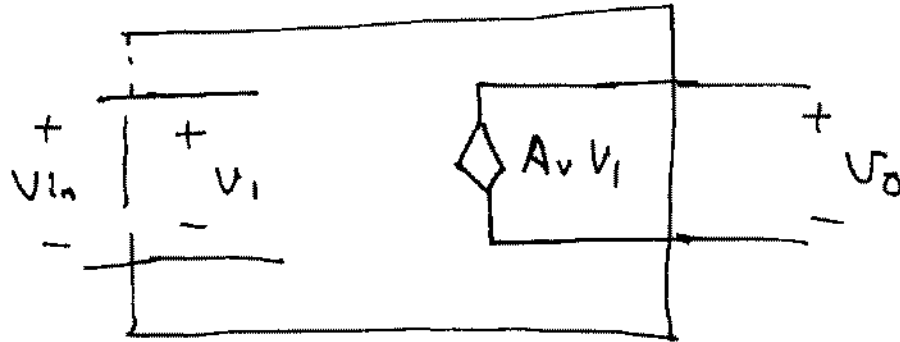

- Note this is a two-port

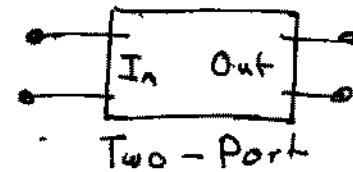

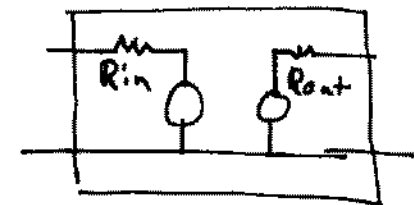- Both ports can be represented as a Thevenin equivalent circuit




$R_{in} \stackrel{\text{defn}}{=} \text{Thevenin impedance at input port}$

$R_{out} \stackrel{\text{defn}}{=} \text{Thevenin impedance at output port}$

For ideal voltage amplifier



$$R_{in} = \infty, \quad R_{out} = 0$$

Practical Voltage Amplifier

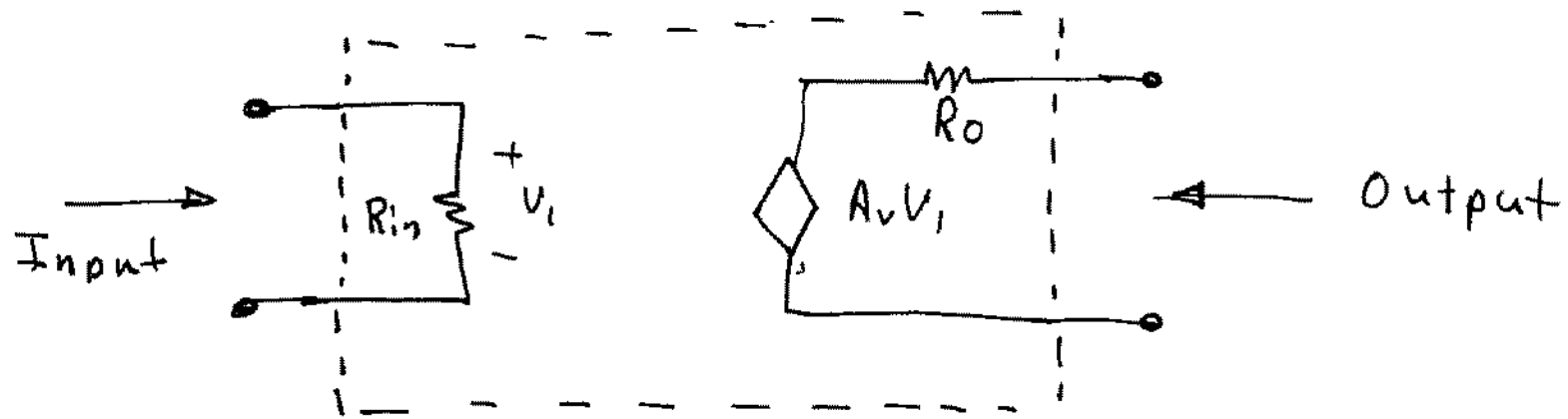

Current Amplifier

Ideal

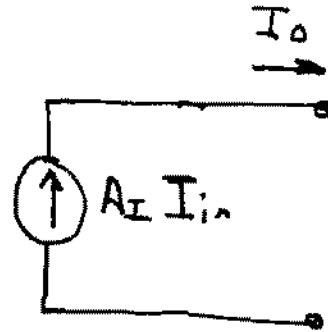
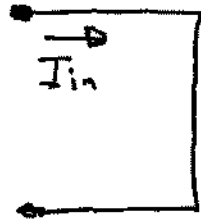


$$R_{in} = 0$$

$$R_{out} = \infty$$

$$\frac{I_o}{I_{in}} = A_I$$


Practical

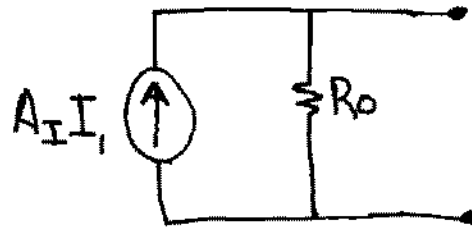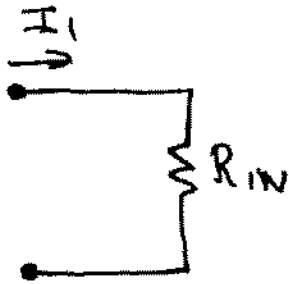

Note: Norton equivalent shown on output port


Transconductance Amplifier

Ideal

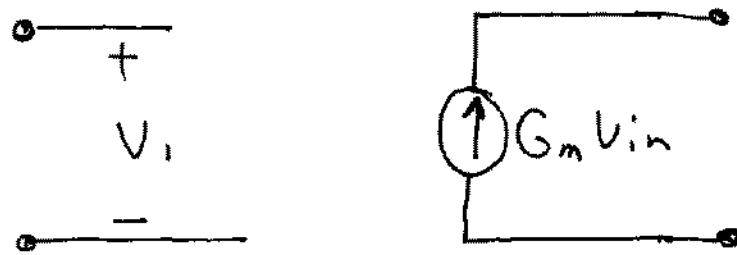


$$R_{in} = \infty, R_{out} = \infty$$

Practical

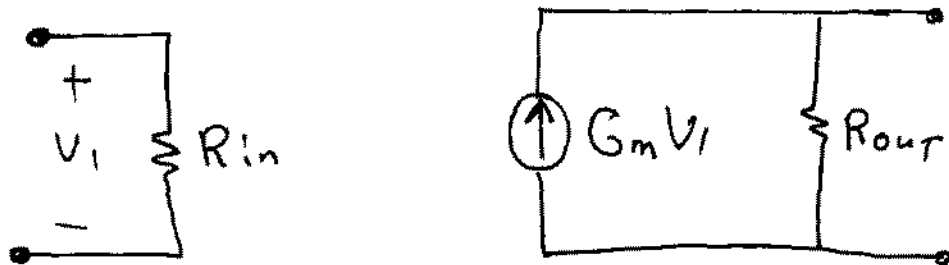


Transresistance Amplifier

Ideal

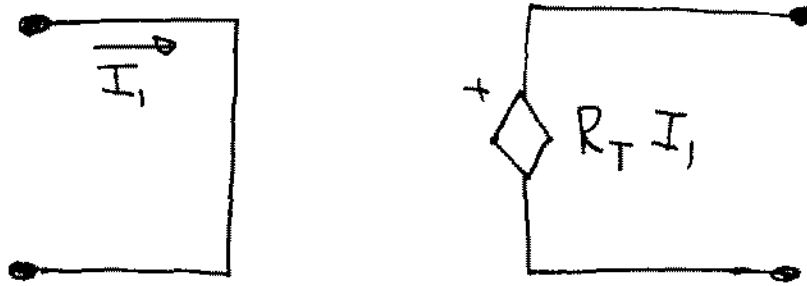

$$R_{IN} = 0 \quad R_{OUT} = 0$$

Practical

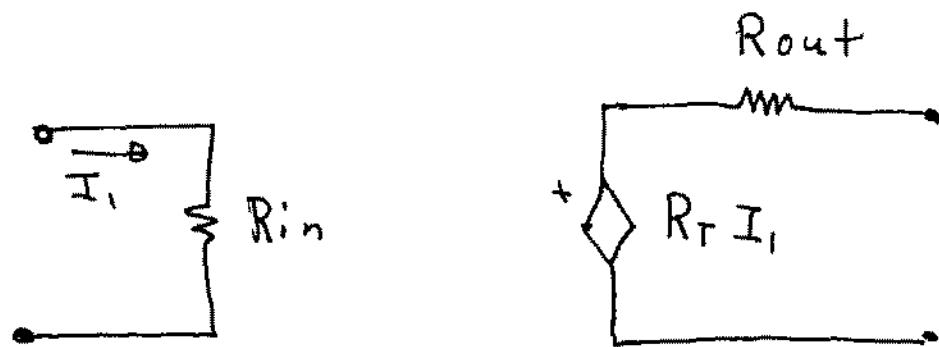


Ideal Port Impedances

		R_{IN}	
		0	∞
R_{OUT}	0	R_T	A_V
	∞	A_I	G_m



End of Lecture 7

Frequency Response of Amplifiers

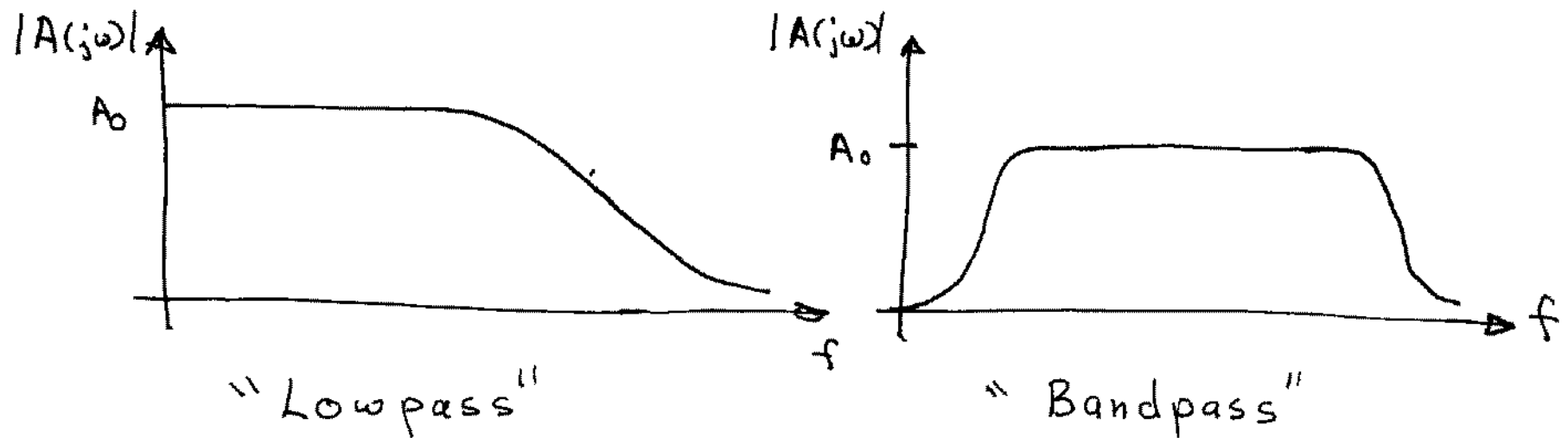
- In a region of interest, amplifiers behave linearly and can be modeled by a transfer function $A(s)$
- All amplifiers exhibit a roll-off in gain at high frequencies and some also a roll-off at low frequencies



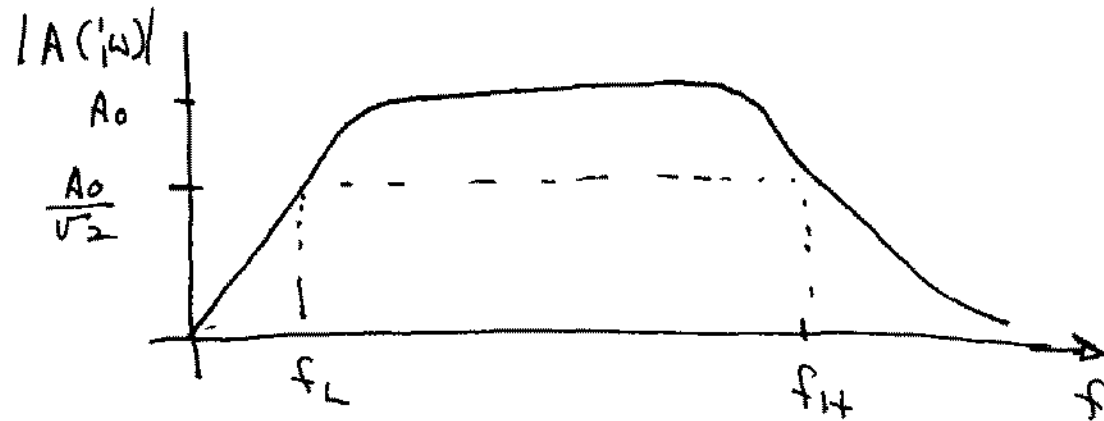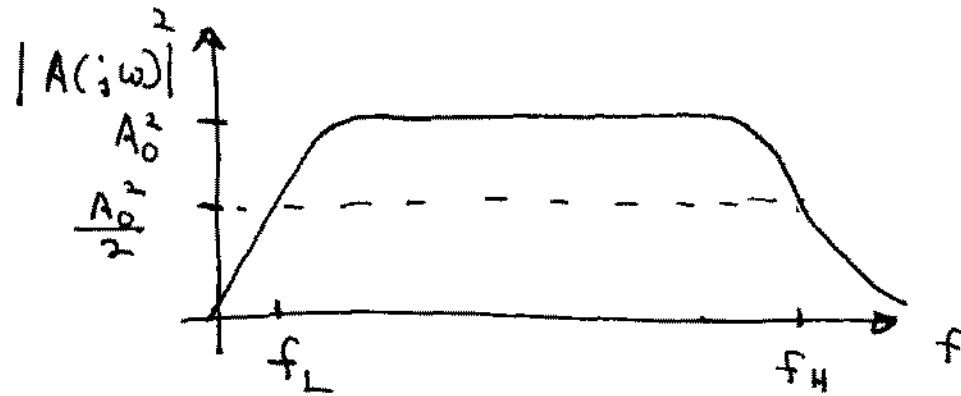Half-power frequency is frequency where output power drops to $\frac{1}{2}$ of the peak output power.



3-dB frequency notation

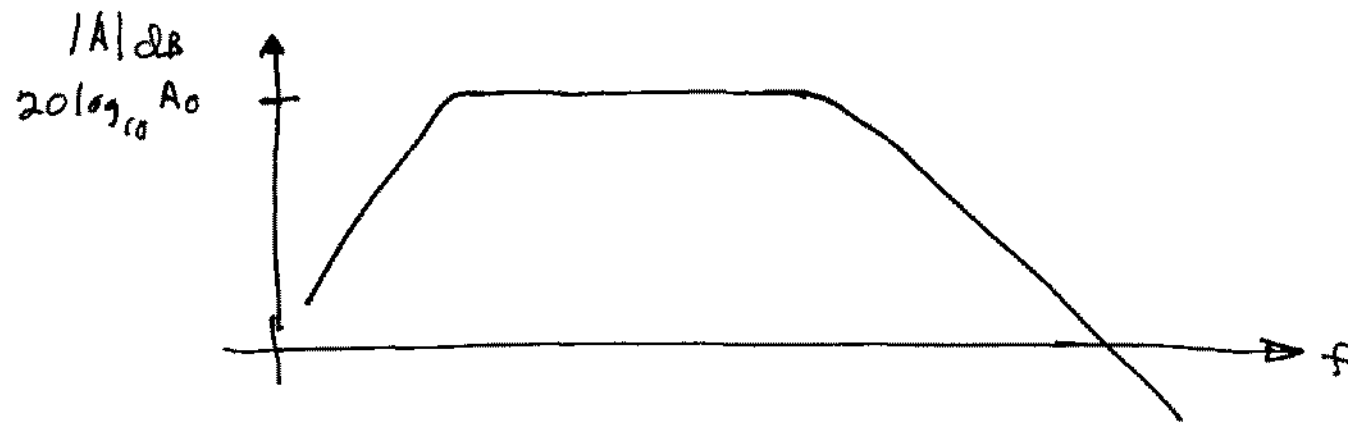


$$\begin{aligned} 20 \log_{10} A_0 - 20 \log_{10} \left(\frac{A_0}{\sqrt{2}} \right) &= 20 \log_{10} A_0 - 20 \log_{10} A_0 + 20 \log_{10} \sqrt{2} \\ &= 20 \log_{10} \sqrt{2} \\ &= 3.01 \text{ dB} \end{aligned}$$

Half-power frequency often termed "3dB frequency" since it is close to a 3dB drop in magnitude

Typical $A(s)$

1) Lowpass

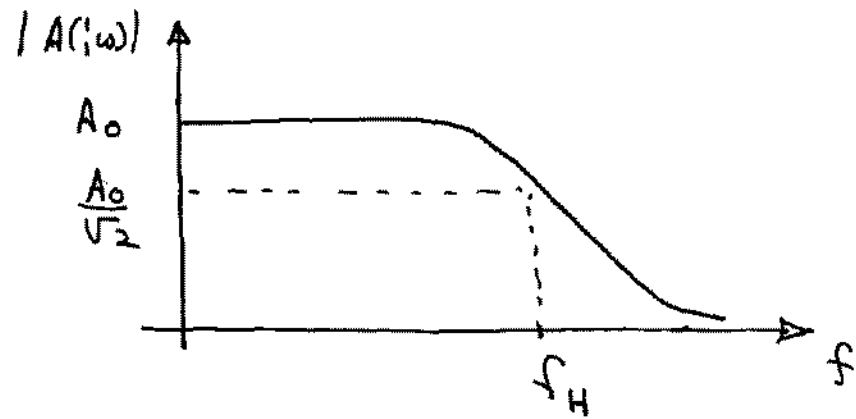

$$\omega_H = 2\pi f_H$$

$$A(s) \approx \frac{A_0}{\frac{s}{p} + 1}$$

$$|A(j\omega)| = \frac{A_0}{\sqrt{1 + \frac{\omega^2}{p^2}}}$$


$$|A(j\omega_H)| = \frac{A_0}{\sqrt{2}} = \frac{A_0}{\sqrt{1 + \frac{\omega_H^2}{p^2}}}$$

solving, obtain $\omega_H = p$

$$|A(j\omega)|_{dB} = 20 \log_{10} \left(\frac{A_0}{\sqrt{1 + \frac{\omega^2}{P^2}}} \right)$$

at high f $|A(j\omega)| \approx \frac{A_0}{\omega/P} = \frac{A_0 P}{\omega} = \frac{GB}{\omega}$

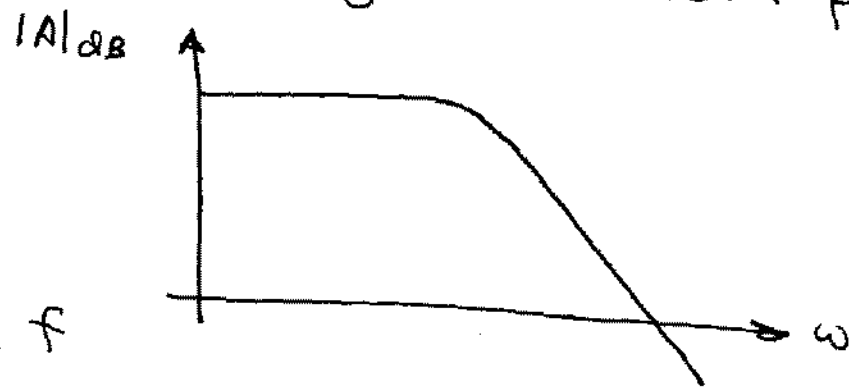where GB is the product of gain and bandwidth
 - termed gain-bandwidth product



At high f

$$20 \log_{10} |A(j\omega)| \approx 20 \log_{10} \left(\frac{GB}{\omega} \right)$$

in 1 decade, $\Delta |A| = 20 \log_{10} \frac{GB}{\omega} - 20 \log_{10} \frac{GB}{10\omega} = -20 \text{ dB}$


\therefore roll-off is 20 dB/decade

or

6.02 dB/octave

Typical $A(s)$

2) Bandpass

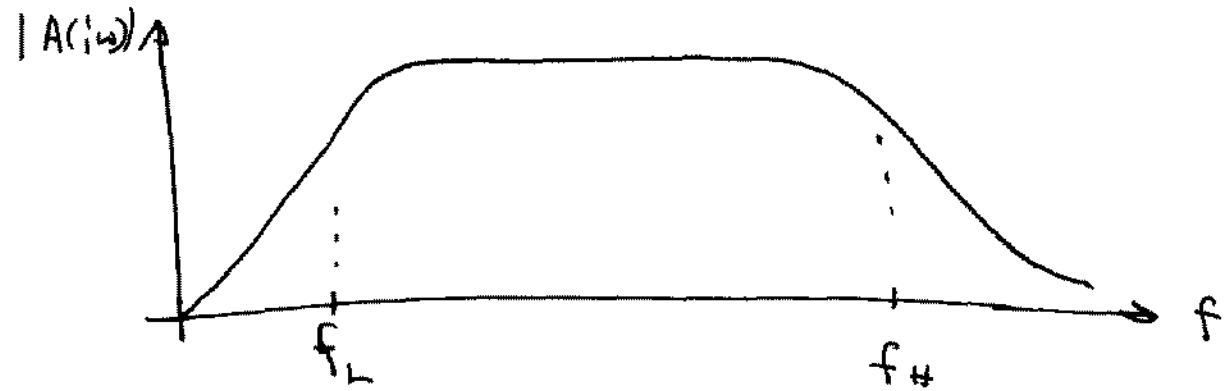

$$\omega_L = 2\pi f_L$$
$$\omega_H = 2\pi f_H$$

Typical $A(s)$

$$A(s) = \frac{A_0 \cdot s}{(s + P_1) \left(\frac{s}{P_2} + 1 \right)}$$

$$\approx \begin{cases} \frac{A_0 s}{s + P_1} \approx \frac{A_0 s}{P_1} & f < f_L \\ A_0 & f_L < f < f_H \\ \frac{A_0}{\left(\frac{s}{P_2} + 1 \right)} \approx \frac{A_0 P_2}{s} & f > f_H \end{cases}$$

$$\omega_L \approx P_1$$

$$\omega_H \approx P_2$$

To find ω_L

$$A(s) = \frac{A_0 s}{s + P_1}$$

$$|A(j\omega_L)| = \frac{A_0}{\sqrt{2}}$$

$$|A(j\omega)| \approx \frac{A_0 \omega}{\sqrt{\omega^2 + P_1^2}}$$



$$\therefore \frac{A_0 \omega_L}{\sqrt{\omega_L^2 + P_1^2}} = \frac{A_0}{\sqrt{2}}$$

$$\frac{\omega_L^2}{\omega_L^2 + P_1^2} = \frac{1}{2}$$


$$2\omega_L^2 = \omega_L^2 + P_1^2$$

$$\omega_L = P_1$$

Linear vs Log Axis

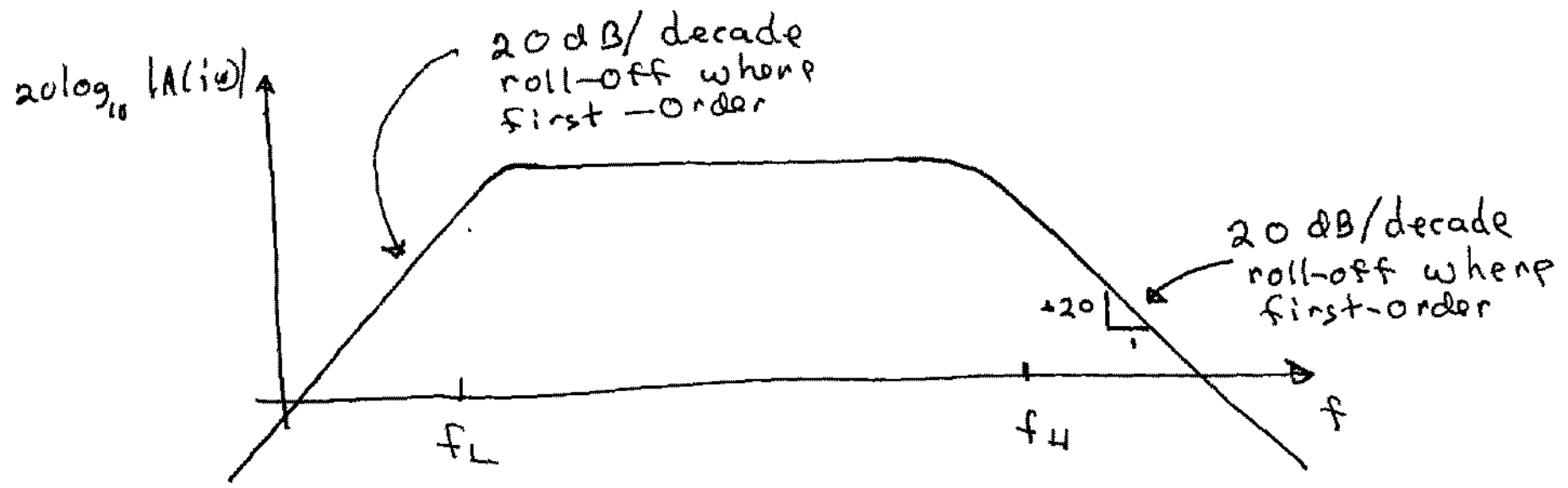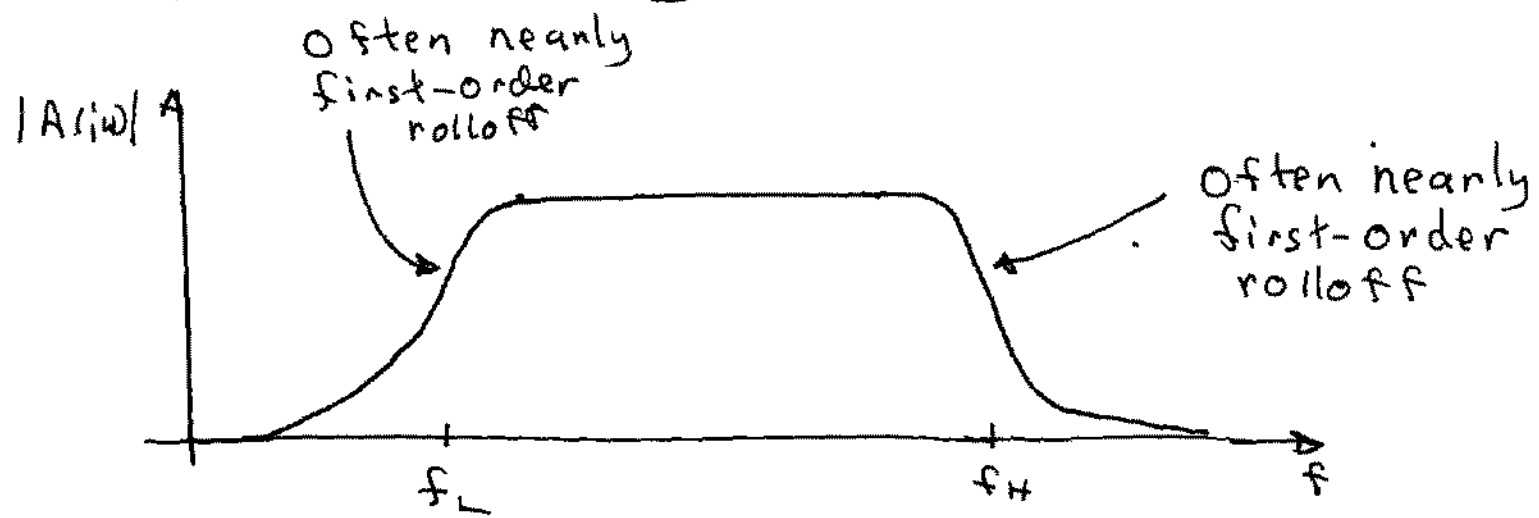

Equivalence of Amplifier Structure

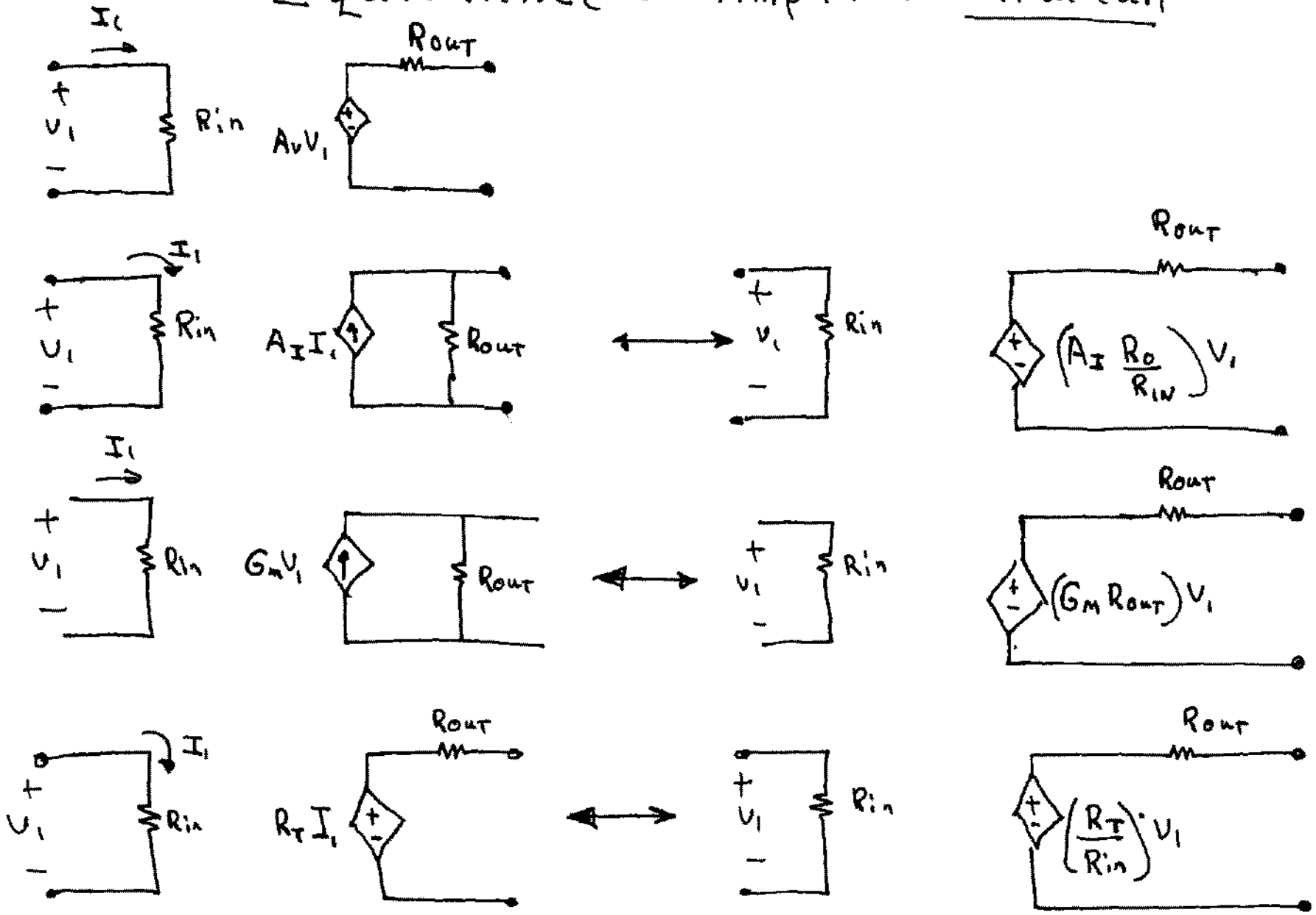

Relative magnitudes of R_{IN} , R_{OUT} , R_T & G_m determine which type is most ideal