

EE303 — Energy Systems and Power Electronics

Lecture 8. Three-phase circuit analysis

Prof. Dionysios Aliprantis

Electrical & Computer Engineering

Sep. 17, 2008

Today's objectives

- **DESCRIBE** power factor correction and **COMPREHEND** why it is necessary

Power factor correction example (a)

Problem

A symmetric three-phase 2400-V source is connected to a symmetric Δ -connected load via a transmission line. The line's impedance is $Z_L = 0.5 + j3 \Omega/\phi$, and the load's impedance is $Z_{\Delta} = 24 + j12 \Omega$.

Compute:

- 1 The load voltage (phasor)
- 2 The line current (phasor)
- 3 The real and reactive power consumed by the load, and the power factor
- 4 The power from the source, and the power factor
- 5 The power loss on the transmission line as a percentage of the load's active power

Power factor correction example (b)

Problem

In order to improve the load's power factor (from previous problem), and make it equal to 1, we connect a Y-connected capacitor bank in parallel to the load. Compute:

- 1 *The susceptance B_C of each capacitor*
- 2 *The load voltage (phasor)*
- 3 *The line current (phasor)*
- 4 *The real and reactive power consumed by the load, and the power factor*
- 5 *The reactive power produced by the capacitor bank*
- 6 *The power loss on the transmission line as a percentage of the load's active power*

Reading material

The material we covered today corresponds to:

- Chapters 7.7.6–7.7.7, pp. 167–174 of textbook