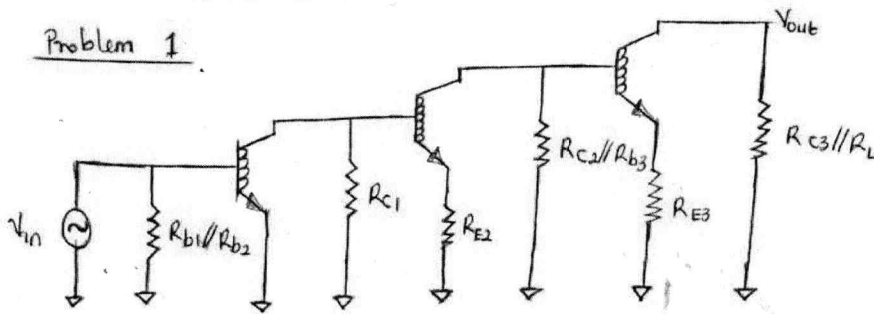


EE 330 HW 10 Solutions Spring 2024


EE 330 HW10

Problem 1



Problem 2

(9)

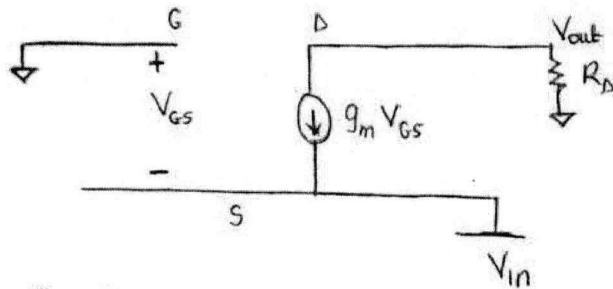

Solving for $\frac{V_{out}}{V_{in}}$,

$$\Rightarrow \frac{V_{out}}{R_D} + g_m(-V_{in}) = 0 \Rightarrow \frac{V_{out}}{R_D} = V_{in} g_m$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = g_m R_D$$

(b) In terms of the quiescent operating point of the transistor,

$$g_m = \frac{2I_{DQ}}{V_{GSQ} - V_T}$$

therefore,
$$\frac{V_{out}}{V_{in}} = \frac{2I_{DQ}}{V_{GSQ} - V_T} R_D$$

Problem 3 For the p-channel device operating in saturation


$$I_D = -\mu_p C_{OX} \frac{W}{2L} (V_{GS} - V_{THP})^2 (1 - \lambda_p V_{DS})$$

Note $\lambda_p > 0$ when expressed in this form. It thus follows that


$$g_{mp} = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{Q-pt} = -2\mu_p C_{OX} \frac{W}{2L} (V_{GS} - V_{THP}) (1 - \lambda_p V_{DS}) \Big|_{Q-pt} \approx -2\mu_p C_{OX} \frac{W}{2L} (V_{GSQ} - V_{THP})$$

$$g_{op} = \left. \frac{\partial I_D}{\partial V_{DS}} \right|_{Q-pt} = -\mu_p C_{OX} \frac{W}{2L} (V_{GS} - V_{THP})^2 (-\lambda_p) \Big|_{Q-pt} \approx \mu_p C_{OX} \frac{W}{2L} (V_{GSQ} - V_{THP})^2 \lambda_p \approx -\lambda_p I_{DQ}$$

A small-signal equivalent circuit is shown below.

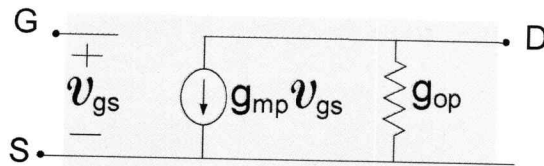


Problem 4

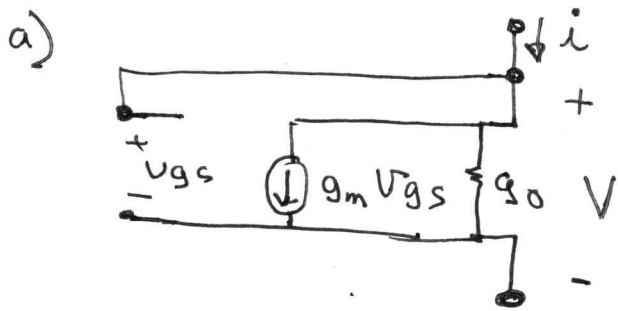

$$\left. \begin{aligned} i &= g_m V_{gs} + g_o V \\ V_{gs} &= V \end{aligned} \right\}$$

$$\therefore \frac{V}{i} = \frac{1}{g_m + g_o} \approx \frac{1}{g_m}$$

$$\text{Impedance} = \frac{1}{g_m}$$

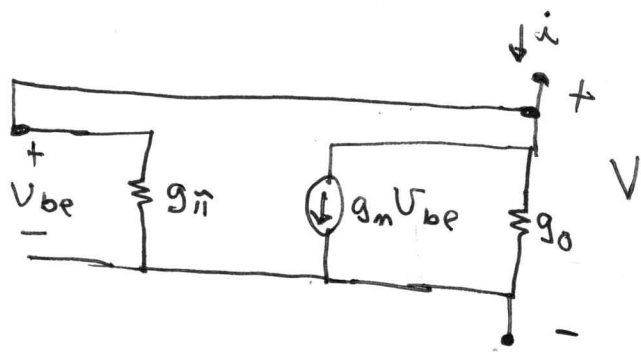

$$\left. \begin{aligned} i &= g_m V_{be} + V g_o + g_{\pi} V_{be} \\ V &= V_{be} \end{aligned} \right\}$$

$$\therefore \frac{V}{i} = \frac{1}{g_m + g_{\pi} + g_o} \approx \frac{1}{g_m}$$

$$\text{Impedance} = \frac{1}{g_m}$$

b) Small signal for both are resistors of value $\frac{1}{g_m}$

$$\begin{aligned} c) \quad R_{eq} &= \frac{1}{\sqrt{\mu_{os} \omega} \sqrt{2 I_{DQ}}} \\ &= \frac{1}{\sqrt{(10^{-4}) (2 \times 10^{-3})}} = 2.2 \text{ k}\Omega \end{aligned}$$

$$R_{eq} = \frac{1}{I_{DQ} / V_t} = \frac{25 \text{ mV}}{1 \text{ mA}} = 25 \Omega$$

Problem 5

a) Must have $V_{DS} > V_{GS} - V_{TH}$

$$I_D = \frac{\mu C_{ox} W}{2L} (V_{GS} - V_{TH})^2$$

$$= \frac{(10^{-4}) 18}{2 \times 2} (2 - 0.75)^2$$

$$= 0.703 \text{ mA}$$

$$\therefore 4V - I_D R_1 > (2V - 0.75V)$$

$$\Rightarrow R_1 < \frac{4V - 1.25V}{I_D} = 3.9 \text{ k}\Omega$$


b) $A_v = -g_m R_{INEW}$ where $R_{INEW} = \frac{3.9 \text{ k}}{3} = 1.3 \text{ k}$

$$A_v = -\frac{2 I_{DQ}}{V_{GS} - V_{TH}} (1.3 \text{ k}) = \frac{(-2)(0.703 \text{ mA})}{(1.25 \text{ V})} \times 1.3 \text{ k} = -1.46$$

c) $V_o = 4 - I_{DQ} R_{INEW} + A_v (0.001 \sin(5000t + 75^\circ))$

$$V_o = 3.09 - 0.00146 \sin(5000t + 75^\circ)$$

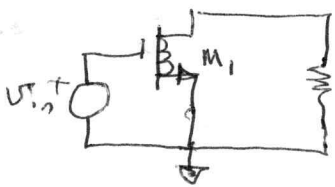Problem 6 From Problem 4, diode connected transistor M_2 is a small signal resistor of value $R_{EQ} = \frac{1}{g_{m2} + g_{o2}} \approx \frac{1}{g_{m2}}$



so $A_v \approx -g_{m1} R_{EQ} = -\frac{g_{m1}}{g_{m2}}$


$$\therefore V_o = \left(\frac{g_{m1}}{g_{m2}}\right) V_m \cos(\omega t + \theta)$$

Problem 7 will present one solution

Assume $V_{DD} = 4V$, C large

To keep M_1 in sat, set $V_{DQ} = 1V$
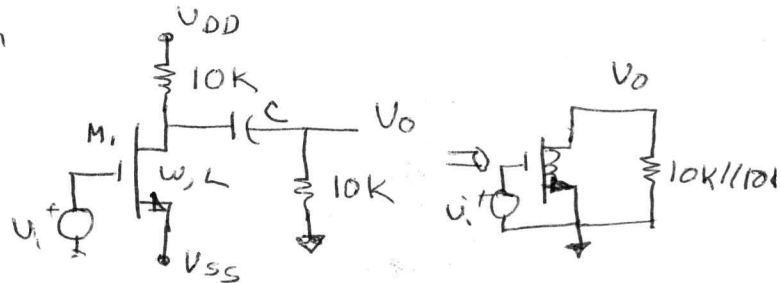
$$\therefore I_{DQ} = \frac{4V - 1V}{10 \text{ k}} = 0.3 \text{ mA}$$



$$A_v = (-g_{m1})(5 \text{ k}) = -10 \text{ so } g_{m1} = 2 \text{ E-3}$$

$$\therefore \frac{2 I_{DQ}}{V_{EB}} = 2 \text{ E-3} \Rightarrow V_{EB} = \frac{I_{DQ}}{1 \text{ E-3}} = 0.3 \text{ V}$$

so pick $V_{SS} = -0.75 - 0.3$

Now obtain W/L $0.3 \text{ mA} = \frac{\mu C_{ox} W}{2L} (V_{EB})^2 \Rightarrow \frac{W}{L} = \frac{(0.3 \text{ mA})(2)}{(10^{-4})(0.3 \text{ V})^2} = 67$


so let $L = 1 \mu$, $W = 67 \mu$

Problem 8

a)

Below is a matrix of the derived small signal parameters

$y_{11} = \frac{\partial I_1}{\partial V_1} = V_{2Q}^2$	$y_{12} = \frac{\partial I_1}{\partial V_2} = 2V_{1Q}V_{2Q}$
$y_{21} = \frac{\partial I_2}{\partial V_1} = 0.04V_{1Q}V_{2Q}e^{0.2V_{1Q}^2V_{2Q}}$	$y_{22} = \frac{\partial I_2}{\partial V_2} = 0.02V_{1Q}^2e^{0.2V_{1Q}^2V_{2Q}}$

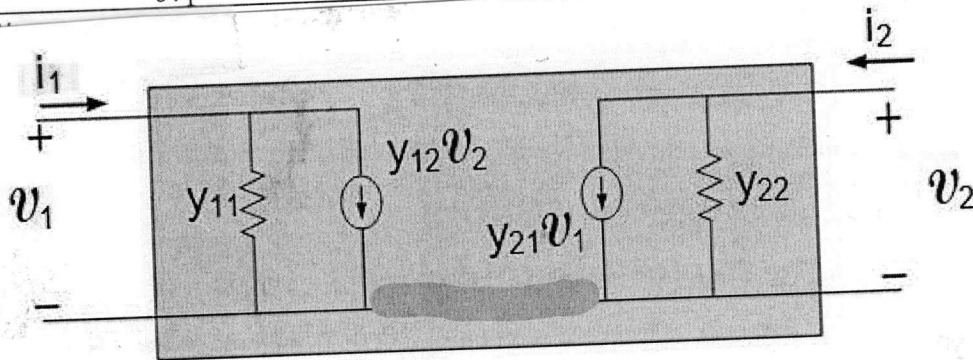

b) Using the equations derived in the previous step, we can find numerical values for the small-signal parameters

$y_{11} = \frac{\partial I_1}{\partial V_1} = V_{2Q}^2 = \frac{1}{\Omega}$	$y_{12} = \frac{\partial I_1}{\partial V_2} = 2V_{1Q}V_{2Q} = \frac{10}{\Omega}$
$y_{21} = \frac{\partial I_2}{\partial V_1} = 0.04V_{1Q}V_{2Q}e^{0.2V_{1Q}^2V_{2Q}} = \frac{0.2e^5}{\Omega}$	$y_{22} = \frac{\partial I_2}{\partial V_2} = 0.02V_{1Q}^2e^{0.2V_{1Q}^2V_{2Q}} = \frac{0.5e^5}{\Omega}$

c) $I_{1Q} = V_{1Q}V_{2Q}^2 = (5V)(1V)^2 = 25A$

$I_{2Q} = (0.1)e^{(0.2)V_{1Q}^2V_{2Q}} = (0.1)e^{(0.2)(25)(1)} = 14.8A$

d) $i_1 = y_{11}v_1 + y_{12}v_2 = (1)(1E-3) + (10)(2E-3) = 21mA$

$i_2 = y_{21}v_1 + y_{22}v_2 = (0.2e^5)(1E-3) + (0.5e^5)(2E-3) = 178mA$


Problems 9 & 10

```
1  `timescale 1ns/1ps //nice timescale for simulation
2  module dff(in, out, clk, rst, en); //instantiate module
3      input in, clk, rst, en; //instantiate inputs
4      output reg out; //instantiate output
5      always @ (posedge clk or posedge rst) begin //any time clk or reset goes high execute following code
6          if (en == 1) begin //if device is disabled
7              out = 0; //hold output low
8          end
9          else begin //if device is enabled
10             if (rst == 1) begin //if device is being reset
11                 out = 0; //change output to low
12             end
13             else begin //if receiving a clock pulse
14                 out <= in; //assign input to output
15             end
16         end
17     end
18 endmodule
```

D flip-flop code

```
1  `timescale 1ns/1ps //nice timescale for simulation
2  module dff_tb(); //instantiate testbench
3      reg in, clk, rst, en; //instantiate input registers
4      wire out; //instantiate output wires
5      dff DUT(.in(in), .clk(clk), .rst(rst), .en(en), .out(out)); //instantiate DUT
6      initial clk = 0; //set initial values for inputs
7      initial rst = 0;
8      initial en = 0;
9      initial in = 0;
10     always #5 in <= ~in; //toggle in every five time units
11     always #2 clk <= ~clk; //toggle clk every two time units
12     initial begin //used to force certain values
13         #27;rst = 1;#1;rst = 0; //force rst at time 27, high for one time unit
14         #6;en=1;#6;en=0; //force en at time 34, high for six time units
15     end
16 endmodule
```

D flip-flop testbench code

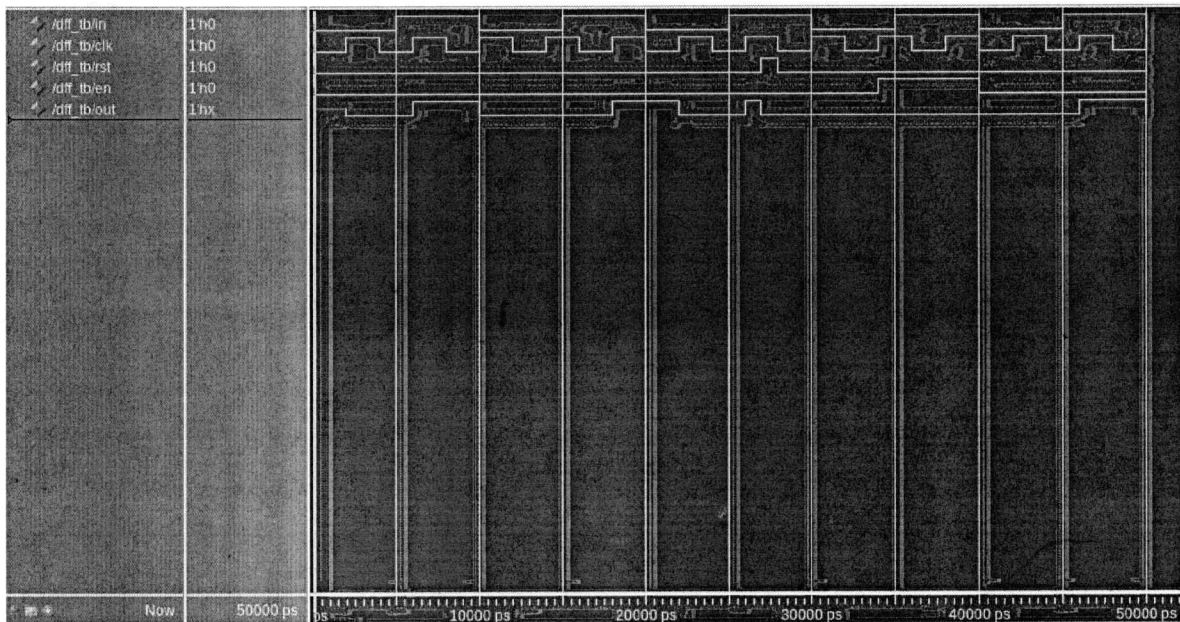

D flip-flop testbench results. Proves functionality by

- Capturing value at input on rising edge of clock when en=0 (active low enable)
- Driving output low with asynchronous reset signal
- Output stays low on rising edge of clock when en = 1 (active low enable)