

# EE 330 Homework 12 Spring 2024 Solutions

## Problem 1

$$I_{D2} = \frac{W_2}{L_2} \frac{L_1}{W_1} I_{D1}$$

$$I_{out} = I_{D4} = \frac{W_4}{L_4} \frac{L_3}{W_3} I_{D3}$$

$$I_{D3} = -I_{D2}$$

$$I_{D1} = -250 \mu A$$


$$\Rightarrow I_{out} = \frac{W_4}{L_4} \frac{L_3}{W_3} \frac{W_2}{L_2} \frac{L_1}{W_1} \cdot 250 \mu A$$

$$= \left(\frac{5}{1}\right) \left(\frac{6}{20}\right) \left(\frac{4}{2}\right) \left(\frac{1}{5}\right) \cdot 250 \mu A$$

$$= 150 \mu A$$

## Problem 2

a) One solution

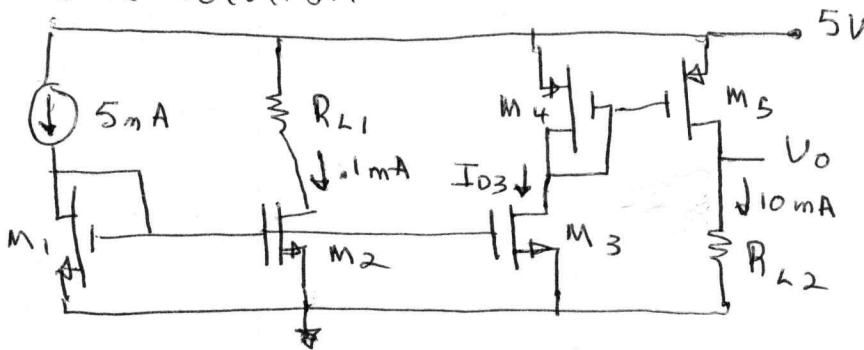

$$\left(\frac{W_2}{L_2}\right) \left(\frac{L_1}{W_1}\right) (5 \text{ mA}) = 1 \text{ mA}$$

$$\text{Let } W_2 = 50 \mu, L_1 = 1 \mu$$

$$\text{If } L_2 = 1 \mu, W_2 = 1 \mu$$

$$\text{Let } W_3 = W_1$$

$$L_3 = L_1$$

$$\therefore I_{D3} = 5 \text{ mA}$$

$$\left(\frac{W_5}{L_5}\right) \left(\frac{L_4}{W_4}\right) (5 \text{ mA}) = 10 \text{ mA}$$

$$\text{Let } W_4 = 40 \mu, L_4 = 1 \mu$$

$$\text{If } L_5 = 1 \mu, W_5 = 80 \mu$$

b) To keep M5 in saturation

$$|V_{DS5}| > |V_{GS5} - V_{TH5}|$$

$$V_{DD} - V_o > |V_{EB5}|$$

but


$$I_{D5} = \frac{\mu_p \text{ Cox } W_5}{2L_5} (V_{GS5} - V_{TH5})^2$$

$$\therefore |V_{GS5} - V_{TH5}| = \sqrt{\frac{10 \text{ mA}}{0.33 \times 10^{-4} \cdot 80}}$$

$$|V_{EB5}| = 2.75 \text{ V}$$

$$\therefore V_o < V_{DD} - |V_{EB5}| = 5 - 2.75 = 2.25 \text{ V}$$

# Problem 3 One solution

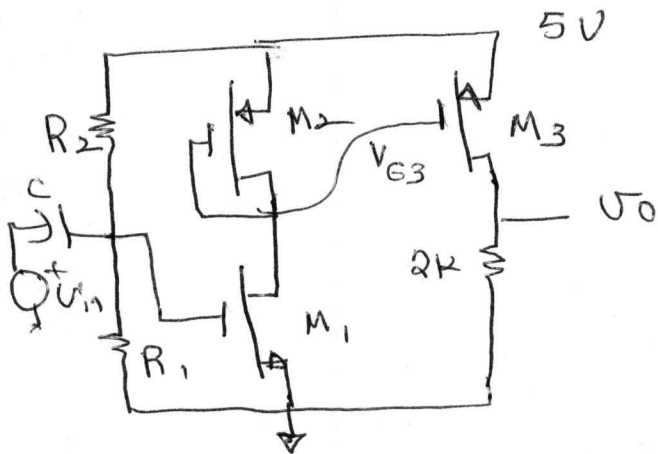

$$A_v = (-g_{m3})(2k) \times -\frac{g_{m1}}{g_{m2}}$$

$$A_v = (g_{m3})(2k) \left( \frac{g_{m1}}{g_{m2}} \right)$$

$$\text{Let's set } (g_{m3})(2k) = 1$$

$$\frac{g_{m1}}{g_{m2}} = 5$$

- Assume C is large
- Consider second stage

$$g_{m3} = \frac{2I_{DQ3}}{V_{EB3}} \quad \text{so} \quad \frac{2I_{DQ3}}{V_{EB3}} \cdot 2k = 1$$

$$\text{Set } V_{EB3} = 2V \Rightarrow I_{DQ3} = 0.5 \text{ mA}, V_{OQ} = 1V$$

$$\therefore 0.5 \text{ mA} = \frac{\mu_p C_{ox} W_3}{2L_3} V_{EB3}^2 \quad \text{so if } L_3 = 1\mu, W_3 = 7.5\mu$$

$$\text{and } V_{G3} = 5V - (V_{EB3} + 1V_{TH3}) = 5 - (2 + 0.75) = 2.25V$$

- Consider first stage

$$\frac{g_{m1}}{g_{m2}} = 5 \Rightarrow \frac{\mu_n C_{ox} W_1}{L_1} V_{EB1} = \left( \frac{\mu_p C_{ox} W_2}{L_2} V_{EB2} \right) 5$$

$$\text{but } V_{EB2} = V_{EB3} = 2V \quad \text{so } V_{EB1} = V_{EB2} \frac{\mu_p}{\mu_n} \frac{W_2}{L_2} \frac{L_1}{W_1} \cdot 5$$

$$\text{Set } V_{EB1} = 1V \Rightarrow \frac{W_2}{L_2} \frac{L_1}{W_1} = \left( \frac{1}{2} \right) \left( \frac{3}{5} \right) = \frac{3}{10}$$

$$\text{so let } W_1 = 10\mu, L_1 = L_2 = 1\mu \Rightarrow W_2 = 3\mu$$

- now obtain  $R_1$  &  $R_2$

$$V_{G1} = V_{THn} + V_{EB1} = 0.75V + 1V = 1.75V$$

$$\left( \frac{R_1}{R_1 + R_2} \right) (5V) = 1.75V$$

$$\text{select } R_1 = 100k$$

$$\text{solving find } R_2 = 186k$$

$$\text{check } R_{in} = R_1 // R_2 = 65k$$

$$\text{summary: } W_1 = 10\mu \quad W_2 = 3\mu \quad W_3 = 7.5\mu \quad R_1 = 100k$$

$$L_1 = 1\mu \quad L_2 = 1\mu \quad L_3 = 1\mu \quad R_2 = 186k$$

$$\text{Problem 4 a) } \left. \begin{aligned} I_{B1} + I_{B4} &= \frac{10 - 0.6}{R_1} \\ I_{C1} &= \beta I_{B1} \\ I_{C4} &= \beta I_{B4} \end{aligned} \right\} \Rightarrow I_{C1} + I_{C4} = \beta \cdot \frac{9.4V}{R_1} \quad (1)$$

$$\left. \begin{aligned} I_{C1} &= J_S A_{E1} e^{\frac{V_{BE1}}{V_T}} \\ I_{C4} &= J_S A_{E4} e^{\frac{V_{BE4}}{V_T}} \end{aligned} \right\} \Rightarrow \begin{aligned} &\text{since } V_{BE1} = V_{BE4} \\ &I_{C1} = I_{C4} \frac{A_{E1}}{A_{E4}} \end{aligned} \quad (2)$$

$$\therefore \text{ from (1) and (2) } I_{C4} = \frac{\beta(9.4V)}{R_1 \left(1 + \frac{A_{E1}}{A_{E4}}\right)}$$

$$\text{and } I_{C1} = \frac{\beta(9.4V)}{R_1 \left(1 + \frac{A_{E4}}{A_{E1}}\right)}$$

From the  $Q_2:Q_3$  current mirror

$$V_{O1} = I_{C1} \frac{A_{E3}}{A_{E2}} R_2 = \frac{\beta(9.4V)}{R_1 \left(1 + \frac{A_{E4}}{A_{E1}}\right)} \frac{A_{E3}}{A_{E2}} R_2$$

From the  $M_5:M_6$  current mirror

$$V_{O2} = (I_{C4}) \frac{W_6}{L_6} \frac{L_5}{W_5} R_3 = \frac{\beta(9.4V)}{R_1 \left(1 + \frac{A_{E1}}{A_{E4}}\right)} \frac{W_6}{L_6} \frac{W_5}{L_5} R_3$$

b) From expressions for  $V_{O1}$  &  $V_{O2}$  from part a)

$$R_2 = 6.1 \text{ k}\Omega$$

$$R_3 = 64 \Omega$$

# Problem 5

a)

$$\frac{V_o}{V_{in}} = \frac{V_o}{V_2} \cdot \frac{V_2}{V_1} \cdot \frac{V_1}{V_{in}}$$

$$\frac{V_o}{V_2} = -\frac{g_{m5}}{g_{m6}}$$

$$\frac{V_2}{V_1} = -\frac{g_{m4}}{g_{m3}}$$

$$\frac{V_1}{V_{in}} = -\frac{g_{m1}}{g_{m2}}$$

$$\therefore A_v = -\frac{g_{m1}}{g_{m2}} \cdot \frac{g_{m4}}{g_{m3}} \cdot \frac{g_{m5}}{g_{m6}}$$

b)

$$\frac{g_{m1}}{g_{m2}} = \frac{2 I_{DQ1}}{V_{EB1}} \quad \text{but } I_{DQ1} = I_{DQ2} \Rightarrow \frac{g_{m1}}{g_{m2}} = \frac{V_{EB2}}{V_{EB1}}$$

$$\text{but } V_{EB1} = 2 - 1 - |V_{TH1}| = .5V$$

$$V_{EB2} = (V_{GS2}) - |V_{TH2}| = 1 - .5 = .5V$$

$$\therefore \frac{g_{m1}}{g_{m2}} = \frac{.5V}{.5V} = 1$$

$$\frac{g_{m4}}{g_{m3}} = \frac{2 I_{DQ3}}{V_{EB4}} \quad \text{but } I_{DQ3} = I_1 + I_{DQ4} = 2 I_{DQ4}$$

$$\text{so } \frac{g_{m4}}{g_{m3}} = \frac{V_{EB3}}{2 V_{EB4}} \quad \text{but } V_{EB3} = V_{DD} - V_{GS} - |V_{TP}| = 2 - 1.3 - .5 = .2V$$


$$V_{EB4} = V_{GS4} - V_{TN} = 1V - .5V = .5V$$

$$\therefore \frac{g_{m4}}{g_{m3}} = \frac{.2V}{(2)(.5)V} = 0.2$$

$$\frac{g_{m5}}{g_{m6}} = \frac{2 I_{DQ5}}{V_{EB5}} \quad \text{but } I_{DQ5} = I_{DQ6} \Rightarrow \frac{g_{m5}}{g_{m6}} = \frac{V_{EB6}}{V_{EB5}}$$


$$\text{but } V_{EB5} = V_{GS5} - V_{TN} = 1.3 - .7 - .5 = .1V$$

$$V_{EB6} = V_{GS}$$

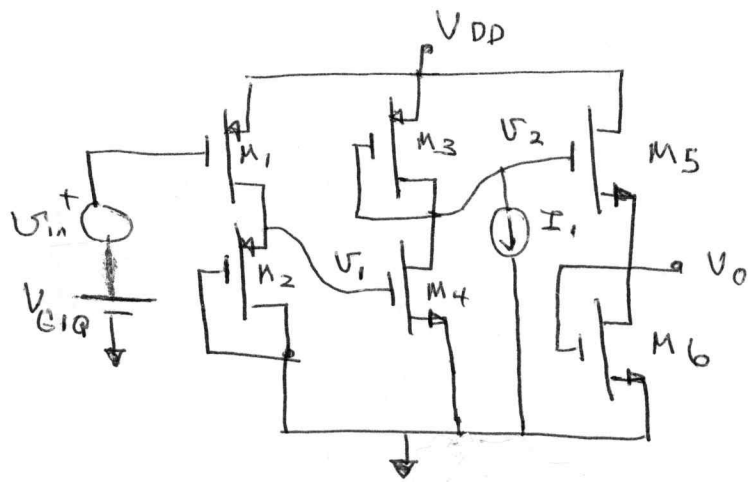



Problem 8

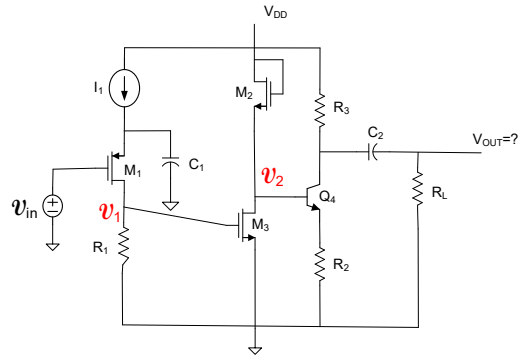

$$A_V = \frac{v_{OUT}}{v_{IN}} = \frac{v_{OUT}}{v_2} \cdot \frac{v_2}{v_1} \cdot \frac{v_1}{v_{IN}}$$

The last stage is a CE with RE stage. The middle stage is a CS stage and the first stage is a CS stage. Thus from the last stage

$$\frac{v_{OUT}}{v_2} = -\frac{R_3 // R_L}{R_2}$$

$$R_{IN3} \approx \beta R_2$$

From the middle stage

$$\frac{v_2}{v_1} = -g_{m3} \cdot \left( \frac{1}{g_{m2}} // R_{IN3} \right)$$

And from the first stage

$$\frac{v_1}{v_{IN}} = -g_{m1} R_1$$

Thus the overall gain is


$$A_V = -\frac{R_3 // R_L}{R_2} - g_{m3} \cdot \left( \frac{1}{g_{m2}} // \beta R_2 \right) \cdot g_{m1} R_1$$

# Problem 9 One solution

3-stage structure. Stage 1: CC to get large input impedance

Stage 2: Inverting Gain Stage

Stage 3: Inverting gain stage

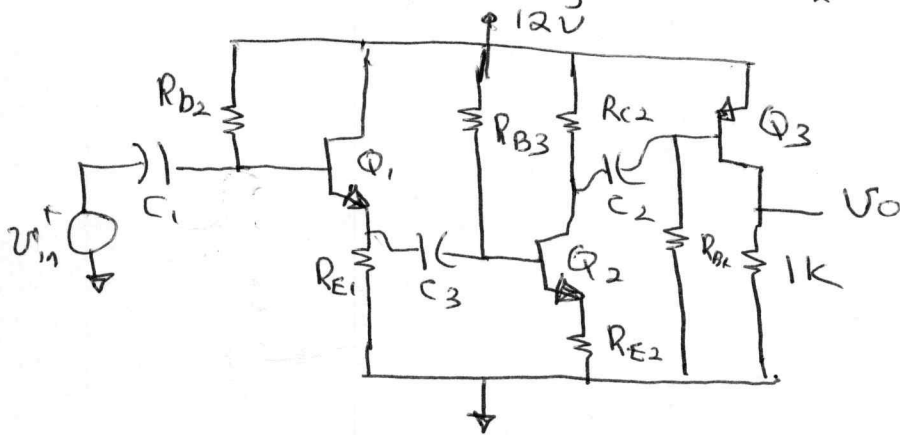

$$A_v = 1 \cdot (-g_{m3}) (1K) \left( \frac{-R_{C2} \parallel R_{B4} \parallel R_{E3}}{R_{E2}} \right)$$

$$R_{in} = R_{B2} \parallel \beta [R_{E1} \parallel \beta R_{E2}]$$

Assume  $C_1, C_2, C_3$  large

• Set  $g_{m3} \cdot 1K = 60 \Rightarrow \frac{I_{C3}}{V_t} \cdot 1K = 60 \Rightarrow I_{C3} = 1.5mA$

$\therefore I_{B3} = \frac{I_{C3}}{100} = 15\mu A \Rightarrow \frac{12 - 0.6}{R_{B4}} = 15\mu A \Rightarrow R_{B4} = 626K$

• Set  $(R_{C2} \parallel R_{B4} \parallel r_{\pi3}) / R_{E2} = 1$

Observe  $R_{in3} = R_{B4} \parallel r_{\pi3} = 626K \parallel \frac{V_t}{I_{B3}} \approx 1.66K$

Pick  $R_{C2} = 2K \Rightarrow \frac{2K \parallel 1.66K}{R_{E2}} = 1 \Rightarrow R_{E2} = 907\Omega$

Pick  $I_{C2} = 2mA \Rightarrow V_{B2} = 0.6 + (2mA)(907\Omega) = 2.4V$

$\therefore \frac{12 - 2.4}{R_{B3}} = \frac{I_{C2}}{\beta} \Rightarrow R_{B3} = \frac{(9.6)\beta}{2mA} = 480K\Omega$



• Pick  $R_{E1} = 5K, I_{E1} = 1mA$

$\therefore V_{B1} = R_{E1} \cdot I_{E1} + 0.6V = 5.6V$

$I_{B1} = \frac{I_{E1}}{\beta} = \frac{12 - 5.6}{R_{B2}} \Rightarrow R_{B2} = 640K$

check  $R_{in} = R_{B2} \parallel \beta (R_{E1} \parallel \beta R_{E2}) = 640K \parallel (100 \cdot [5K \parallel 90.7K])$   
 $R_{in} = 272K\Omega$

# Problem 10

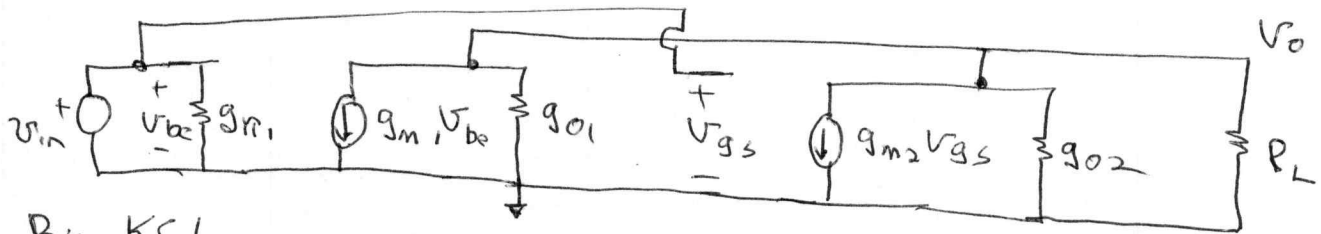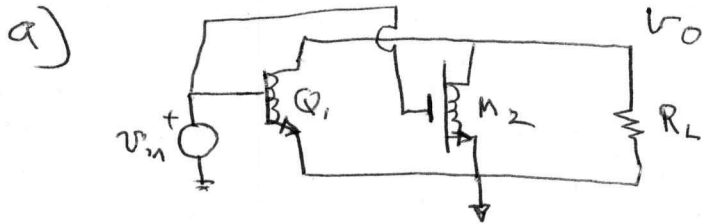

By KCL

$$V_o (g_L + g_{o1} + g_{o2}) + g_{m1} V_{in} + g_{m2} V_{in} = 0$$

$$\therefore \frac{V_o}{V_{in}} = - \frac{(g_{m1} + g_{m2})}{g_L + g_{o1} + g_{o2}} \approx - (g_{m1} + g_{m2}) R_L$$

b) Observe  $I_{CQ} = |I_{DQ}|$

$$I_{CQ} = \beta \frac{(0 - (-5 + 0.6))}{R_B} = \beta \cdot \frac{4.4V}{200K} = 2.2mA$$

$$g_{m1} = \frac{I_{CQ}}{V_t} = \frac{2.2mA}{25mV} = 8.8E-2$$

$$g_{m2} = \frac{2|I_{DQ}|}{|V_{EB2}|} = \frac{4.4mA}{1.8 - |V_{THP}|} = \frac{4.4mA}{1.05} = 4.2E-3$$

$$\therefore A_v = - (8.8E-2 + 4.2E-3)(1K) = -92.2$$

$$\text{so } V_o(t) = (-92.2)(0.01 \sin 1000t) = -0.92 \sin(1000t)$$