

If parameters of semiconductor processes are needed beyond what is given in a specific problem or question, assume a CMOS process is available with the following key process parameters;


$\mu_n C_{OX} = 100 \mu A/V^2$, $\mu_p C_{OX} = \mu_n C_{OX}/3$, $V_{TNO} = 0.75V$, $V_{TPO} = -0.75V$, $C_{OX} = 4fF/\mu^2$, $\lambda = 0$. Correspondingly, assume all npn BJT transistors have model parameters $J_S = 10^{-14} A/\mu^2$ and $\beta = 100$ and all pnp BJT transistors have model parameters $J_S = 10^{-14} A/\mu^2$ and $\beta = 25$. If the emitter area of a transistor is not given, assume it is $100 \mu^2$. Parasitic capacitance parameters for a sample 0.5u CMOS process appear in the Appendix.

Problem 1

The small-signal equivalent circuit of the standard common-source amplifier biased to operate in the saturation region is shown below where a **small** capacitor, C_L , has been placed on the amplifier output.

Express the small-signal gain of the amplifier, $A_V(s) = \frac{v_{OUT}(s)}{v_{IN}(s)}$, in terms of the small-signal model


parameters.

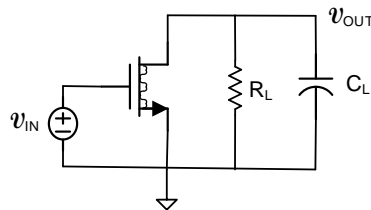

Problem 2


Consider the following amplifier where the input is a small-signal current source i_{IN} . Assume the coupling capacitor C_C is very large. Assume the transistor is in a process with $\mu_n C_{OX} = 100 \mu A/V^2$, $C_{OX} = 4fF/\mu^2$, $V_{THn} = 0.75V$, and $\lambda = 0$. Assume all parasitic capacitances in the transistor are negligible in this circuit except for C_{GS} .

- Draw the small-signal equivalent circuit
- Determine the dc small-signal current gain $A_I = \frac{i_{OUT}}{i_{IN}}$
- Determine the frequency where the magnitude of the current gain drops to one.

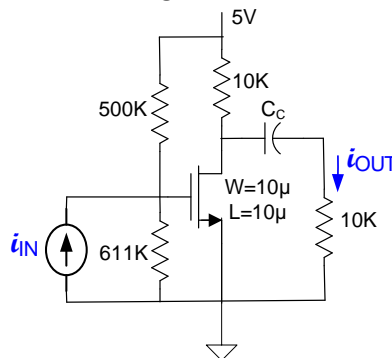


Problem 3

Find V_{OUT} for the circuit below.

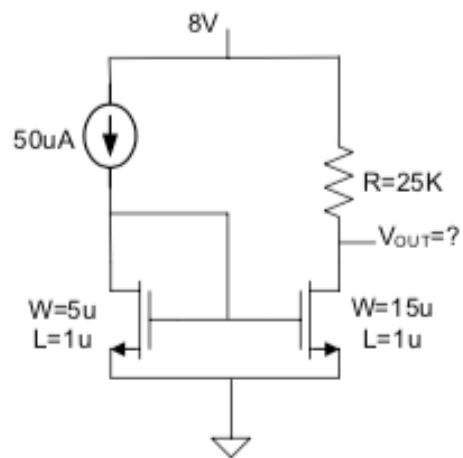

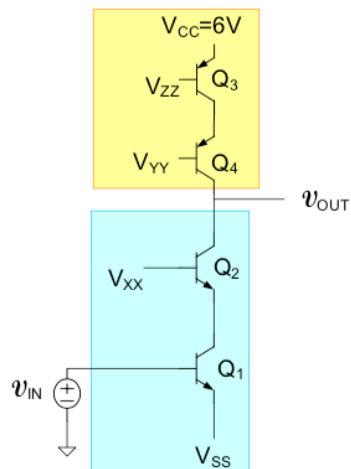
Problem 4

Assume the biasing voltages have been selected so that the quiescent output voltage is 2V and that all transistors are operating in the forward active region. Determine the small-signal voltage gain if $A_{E1} = A_{E2} = 40\mu^2$ and $A_{E3} = A_{E4} = 60\mu^2$. Assume the transistors all have parameters $\beta = 100$ and $V_{AF} = 100V$.



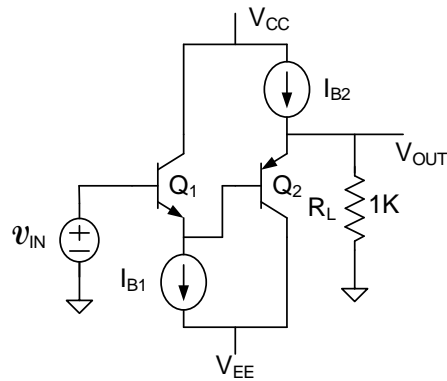
Problem 5 Assume $A_{E1}=A_{E2}=5\mu^2$, $I_{B1}=I_{B2}=1\text{mA}$ and $\beta_1=\beta_2=100$. The supply voltages are +5V and -5V.

- Determine the small signal voltage gain.
- Determine the quiescent output voltage
- Determine the small-signal input impedance
- Determine the maximum output swing.




Problem 6 Consider the two amplifier circuit shown below where $V_{DD}=5\text{V}$, $I_{B1}=5\mu\text{A}$, $I_{B2}=10\mu\text{A}$, and $R_L=5\text{K}$. Assume the transistors are identically sized with $W=10\mu$ and $L=2\mu$.

- Give the small-signal voltage gain of the two amplifiers in terms of the small-signal model parameters
- Numerically determine the small-signal voltage gain for the two amplifiers if $V_{INQ}=1\text{V}$.
- Determine the quiescent output voltage and the difference between the quiescent output voltages of the two amplifiers if $V_{INQ}=1\text{V}$.
- Repeat part c) if $V_{INQ}=4\text{V}$.

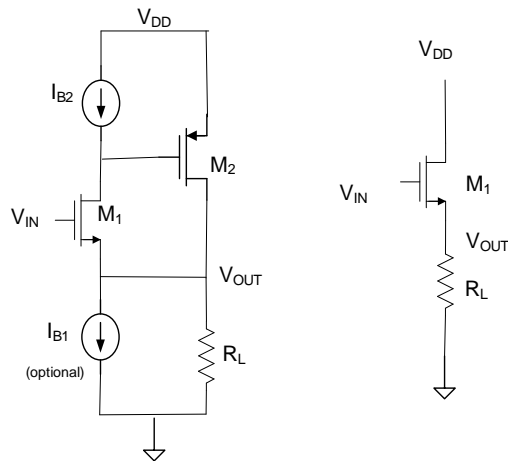

Problem 7


Assume the quiescent output is 2V and all transistors are in the forward active region of operation. Find the small signal voltage gain if $A_{E1}=A_{E2}=55\mu^2$ and $A_{E3}=75\mu^2$. Assume the transistors all have parameters $\beta = 100$ and $V_{AF}= 100V$.

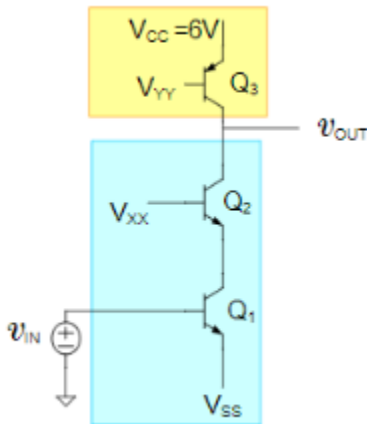

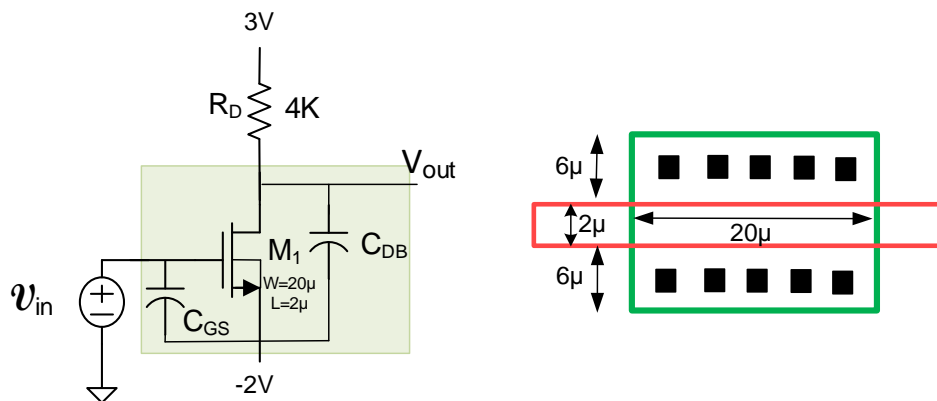Problem 8

Consider the following amplifier. Assume the dominant parasitic capacitances in the transistor are C_{GS} and C_{DB} . They are depicted in the green shaded region that comprises the transistor M_1 . The layout of the transistor, not to scale, is also shown below.

- Draw the small-signal equivalent circuit that can be used to determine the high-frequency response
- Obtain an expression for the small-signal voltage gain in terms of the small-signal model parameters
- Determine the 3dB bandwidth (in Hz) for this amplifier.



Problem 9 Design a sinking current source that can sink a current of 3mA from a 1K resistor with one terminal connected to a 5V dc voltage source. You have available for this design any number of MOS transistor, the 5V source, and the 1K resistor.

