

EE 330 HW 15 Solutions Spring 2024

Problem 1 Assume $C_{REF} = 4fF$.

$$t_{PROP} = t_{REF} \sum_{i=1}^3 \frac{F_{i+1}}{OD_i} \quad F_{I_2} = 3 \cdot \frac{3+k}{4} \Big|_{k=3} = \frac{9}{2} \quad F_{I_3} = \frac{1+3k}{4} \Big|_{k=2} = \frac{7}{4} \quad F_{I_4} = \frac{10fF}{4fF} \Big|_{k=2} = \frac{5}{2} \quad OD_1=1 \quad OD_2=3 \quad OD_3=1$$

$$t_{PROP} = t_{REF} \left(\frac{9}{2} + \frac{1}{3} \cdot \frac{7}{4} + \frac{5}{2} \right) = 7.6 t_{REF}$$

2. Assume ref inverter has $L_{min} = 0.6\mu$, $W_{min} = 0.9\mu$

a) For 3-input NAND $W_n = n \cdot OD \cdot W_{min} = 3 \cdot 4 \cdot W_{min} = 10.8\mu$
 $W_p = 3 \cdot OD \cdot W_{min} = 3 \cdot 4 \cdot W_{min} = 10.8\mu$

2-input NOR $W_n = OD \cdot W_{min} = 6W_{min} = 5.4\mu$
 $W_p = 3 \cdot n \cdot OD \cdot W_{min} = 3 \cdot 2 \cdot 6W_{min} = 32.4\mu$

b) with this sizing

$$t_{PROP(B-K)} = t_{REF} \sum_{k=1}^3 \frac{F_i(k+1)}{OD_k} = t_{PROP} \left(\frac{6+1+6 \cdot \frac{7}{4}}{4} + \frac{3}{6} + \frac{20}{3} \right) = 6.54 t_{REF}$$

with minimum sizing

$$t_{PROP(B-K)} = \frac{t_{REF}}{2} \sum_{k=1}^3 F_i(k+1) \left(\frac{1}{OD_{NLK}} + \frac{1}{OD_{PLK}} \right) = \frac{t_{REF}}{2} \left(\frac{3}{2} \left[\frac{1}{1/3} + \frac{1}{1/3} \right] + \frac{1}{2} \left[\frac{1}{1} + \frac{1}{1/6} \right] + \frac{20}{4} \left[\frac{1}{1} + \frac{1}{1/3} \right] \right) = \frac{t_{REF}}{2} (9 + 7/2 + 20) = 16.25 t_{REF}$$

3 a) $t_{PROP(A-F)} = t_{REF} \sum_{k=1}^3 \frac{F_i(k+1)}{OD_k} = t_{REF} \left(\frac{[1 + \frac{5}{4} + 3 \cdot \frac{13}{4}]}{1} + \frac{[7 + 4 \cdot \frac{6}{4}]}{3} + \frac{[7 + \frac{5}{4} + 2 \cdot \frac{10}{4}]}{1} \right) = t_{REF} (12 + 2.58 + 13.25) = 27.8 t_{REF}$


b) Since inverter changes only on HL transitions $f_{TOGGLE} = \frac{400MHz}{2} = 200MHz$

$$P_{DYNAMIC} = f_{TOGGLE} C_L V_{DD}^2 = (200E6) \left(3 \cdot \frac{5}{4} \cdot 4fF \right) (4V)^2 = 48\mu W$$

c) $t_{PROP(A-F)} = \frac{t_{REF}}{2} \sum_{k=1}^3 F_i(k+1) \left(\frac{1}{OD_{HLK}} + \frac{1}{OD_{PLK}} \right) = \frac{t_{REF}}{2} \left(\frac{3}{2} \left[\frac{1}{1} + \frac{1}{1/6} \right] + 2 \left[\frac{1}{1} + \frac{1}{1/12} \right] + \frac{3}{2} \left[\frac{1}{1} + \frac{1}{1/6} \right] \right) = \frac{t_{REF}}{2} \left(\frac{21}{2} + 26 + \frac{21}{2} \right) = 23.5 t_{REF}$

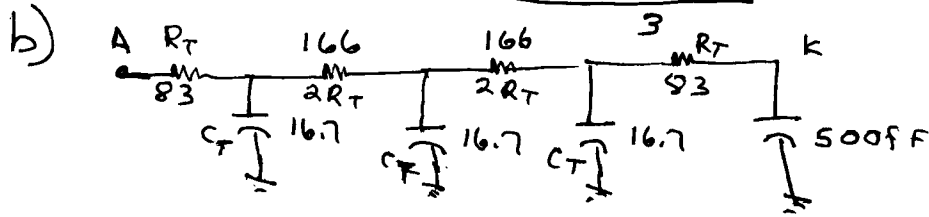4) a) $R_T = R_{\square} \frac{L}{w} \left(\frac{1}{2n} \right) = (20) \left(\frac{50}{2} \right) \left(\frac{1}{6} \right) = 83.3 \Omega$


$C_T = \frac{C_d}{n} \frac{w \cdot L}{\mu^2} = \frac{.5 \text{ fF}}{6} \frac{100 \mu^2}{\mu^2} = 16.7 \text{ fF}$



$t_{\text{delay}} = R_T C_T + 3R_T C_T + 5R_T C_T + 6R_T (500 \text{ fF})$
 $= 9R_T C_T + 6R_T (500 \text{ fF})$
 $= (83.3)(9 \cdot 16.7 \text{ fF} + 3 \text{ pF}) = 262 \text{ psec}$

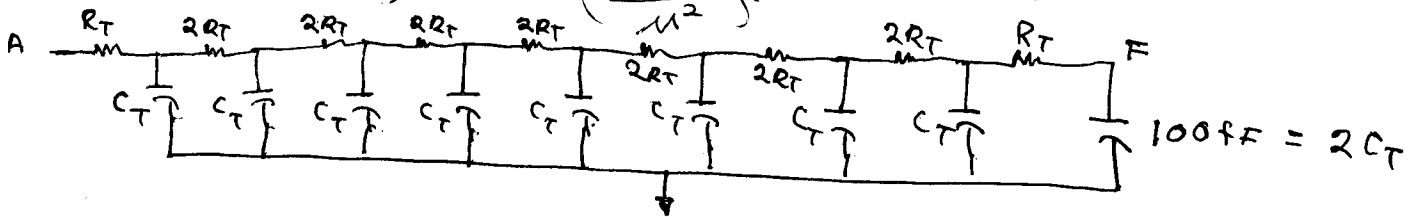
5) $R_T = R_{\square} \left(\frac{50}{2} \right) \left(\frac{1}{2} \right) = (20) \left(\frac{50}{4} \right) \Omega = 250 \Omega$

$C_T = (C_d) (2.50) = \left(\frac{.5 \text{ fF}}{\mu^2} \right) (100 \mu^2) = 50 \text{ fF}$



$t_{\text{delay}} = R_T C_T + 3R_T C_T + 5R_T C_T + 7R_T C_T + 9R_T C_T + 11R_T C_T + 13R_T C_T$
 $+ 15R_T C_T + 16R_T (100 \text{ fF})$
 $= R_T (1+3+5+7+9+11+13+15+16) C_T$
 $= 96 R_T C_T = 1.2 \text{ nsec}$

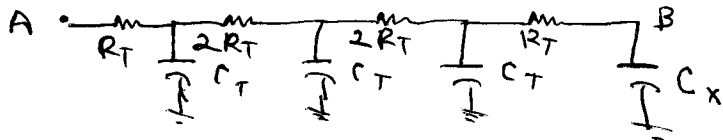b) a) Consider poly interconnect, use 3-seg model, Assume $C_{REF} = 4 \text{ fF}$



$R_T = R_{\square} \cdot \frac{L}{w} \cdot \frac{1}{2n} = \frac{50 \cdot 400}{6} = 3.3 \text{ K}\Omega$

$C_T = \left(800 \frac{\text{af}}{\mu^2} \right) \left(\frac{400 \mu^2}{3} \right) = \frac{107}{3} \text{ fF}$

$C_X = C_{REF} \cdot \frac{7}{4} = 7 \text{ fF}$

$\therefore t_{AB} = R_T C_T + 3R_T C_T + 5R_T C_T + 6R_T C_X$
 $= R_T (9C_T + 6C_X) = 3.3 \text{ nsec}$


$t_{EF} = \frac{t_{REF}}{2} \sum_{k=1}^2 F_k (k+1) = (10 \text{ psec}) \left(1 + \frac{7}{4} \right) = 27.5 \text{ psec}$
 $t_{REF} = 20 \text{ psec}$

Thus, the F input will rise first.

b) $t_{\text{prop}} = t_{REF} \sum_{k=1}^3 F_k (k+1) = t_{REF} \left(1 + \frac{7}{4} + 4 \right) = 6.75 t_{REF} = 135 \text{ psec}$

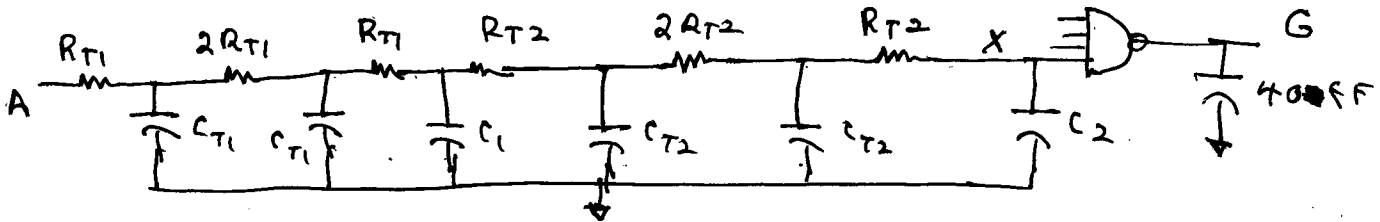7) will use 2-segment delay model for each resistor segment

Note: Propagation delay in interconnect is double t_{HL} of interconnect



$$C_1 = (6) \left(\frac{3k+1}{4} \right) \Big|_{k=2} = \frac{42}{4} C_{REF} = 42 \text{ fF}$$

$$C_2 = \frac{3+k}{4} \Big|_{k=4} = \frac{7}{4} C_{REF} = 7 \text{ fF}$$

$$R_{T1} = (20 \frac{\Omega}{\mu}) \left(\frac{20}{2} \right) \left(\frac{1}{4} \right) = 50 \Omega$$

$$R_{T2} = (40 \frac{\Omega}{\mu}) \left(\frac{20}{2} \right) \left(\frac{1}{4} \right) = 100 \Omega$$

$$C_{T1} = \left(\frac{800 \text{ aF}}{\mu^2} \right) \left(\frac{40 \mu^2}{2} \right) = 16 \text{ fF} = C_{T2}$$

(assume $C_d = 800 \text{ aF}/\mu^2$ for both poly layers!)

$$t_{PROP(A \rightarrow X)} = 2 \left[R_{T1} C_{T1} + 3R_{T1} C_{T1} + 4R_{T1} C_1 + (4R_{T1} + R_{T2}) C_{T2} \right. \\ \left. + (4R_{T1} + 3R_{T2}) C_{T2} + (4R_{T1} + 4R_{T2}) C_2 \right]$$


$$= 57.2 \text{ psec}$$

$$t_{PROP(A \rightarrow G)} = t_{PROP(A \rightarrow X)} + t_{REF} \cdot FI_G$$

$$= 57.2 \text{ psec} + (20 \text{ psec})(10)$$

$$= 257 \text{ psec}$$

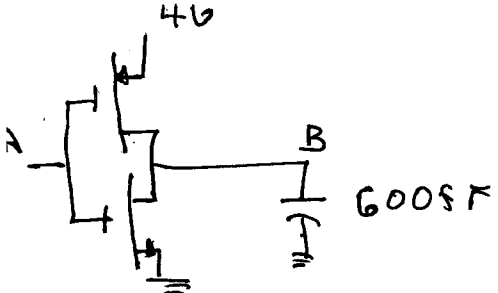8) Assume $.5\mu$ process with $W_{min} = .9\mu$, $L_{min} = .6\mu$, $C_{REF} = 4fF$



$$OD_{HL} = \frac{10}{.9} = 11.1$$

$$OD_{LH} = \frac{40}{(3)(.9)} = 14.8$$

a) $P_{dynamic} = f_{CLK} C_L V_{DD}^2 = (10^4)(600fF)(4V)^2 = 96nW$

b) same as part a) since load unchanged

c) $t_{PROP} = \frac{t_{REF}}{2} \left[\frac{1}{OD_{HL}} + \frac{1}{OD_{LH}} \right] FI$
 $= \frac{t_{REF}}{2} \left[\frac{1}{11.1} + \frac{1}{14.8} \right] \left(\frac{600}{4} \right)$
 $= 11.9 t_{REF}$

t_{CLK} must exceed t_{PROP}

$$\therefore t_{CLK} > 11.9 t_{REF}$$

or $f_{CLK} < \frac{1}{11.9 t_{REF}} = \frac{1}{(11.9)(20ps)}$

$$f_{CLK} < 4.2E9 = 4.2GHz$$

9) The FI for a minimum sized inverter is 4fF
 Total energy dissipated for charging and discharging a 4fF load is $E = CV^2 = (4fF)(16V^2) = 64fJ$

If all gates have $FI = 1/2$ and half transition on each clock cycle, dynamic power dissipated on a clock cycle would be $(500,000)(64fJ) = 32nJ$. If the clock frequency is 1.5GHz $P = (32nJ)(1.5GHz) = 48W$

10) Dynamic power is independent of driver sizing
 $P_{dynamic} = f_{CLK} C_L V_{DD}^2 = (300MHz)(25pF)(4V)^2 = 120mW$

11) $P_{dynamic} = \left(\frac{f_{CLK}}{2} \right) (C_L) V_{DD}^2 \cdot 32 = \left(\frac{800M}{2} \right) (4pF) (4V)^2 (32) = 820mW$