

Problem 1

1) b) $Y = \overline{(AB + C)} \cdot D$

Compound gate approach

Pull down n/w


$$\bar{Y} = (AB + C) \cdot D$$

Pull up n/w

$$\begin{aligned} \bar{\bar{Y}} &= \overline{(AB + C) \cdot D} \\ &= \overline{(AB + C)} + \bar{D} \\ &= (\bar{A}\bar{B} \cdot \bar{C}) + \bar{D} \\ &= ((\bar{A} + \bar{B}) \cdot \bar{C}) + \bar{D} \end{aligned}$$


Total no of transistors = 8

Number of logic gates = 1 level of logic

 

Static CMOS Gate


 
$$\begin{aligned} Y &= \overline{(AB + C)} \cdot D = \overline{(AB + C)} + \bar{D} \\ &= (\bar{A}\bar{B} \cdot \bar{C}) + \bar{D} \end{aligned}$$




Total no of transistors = 20


Number of logic gates = 5 level of logic

Problem 2

  


transistor level logic.

 

 

$$t_{HL} = R_{sw} \cdot C$$



$$R_{sw} =$$

 



$$= 10^3 \Omega$$

$$t_{HL} = 10^3 \times 50 \times 10^{-15} = 5 \times 10^{-12} \text{ s}$$

Problem 4

  


Problem 5

  


We can see that the figure of 1.31b) has 2 not gates and 2 T-gates.

Problem 6

 

 Problem 7

For this stick diagram there are 3 errors:



1. No need of contact poly to n-active.
2. Contact needed for Metal 1 to n-active.
3. Contact needed for Metal 1 to p-active.

Problem 8

Assuming ON 0.18 μ m process, $C_{IN} = 1.5fF$, $R_{SWP} = 6k\Omega$, and $R_{SWN} = 2k\Omega$

Total C_{IN} of 6 driven inverters = $C_{IN} * 6 \text{ inverters} * 2 \text{ transistors/inverter} = 18fF = C_L$

If input steps from 2V to 0V, the transition at output will be from 0V to 2V, so we will be calculating t_{LH}

From lecture, $t_{LH} = C_L * R_{SWP} = 18fF * 6k\Omega = 108 \text{ picoseconds}$

Problem 9

For this problem, there are three concepts to keep in mind

- Any interconnect will act as a resistor
- Conductivity is the inverse of resistivity
- Interconnect area = $5\mu m * 0.2\mu m = 1\mu m^2$

a) Resistivity of aluminum = $\frac{1 \text{ ohm}}{38 \mu m}$

$$\text{Resistance} = \frac{\rho L}{A}$$

$$\text{Resistance of first segment} = \frac{1/38 * (180+40)}{1} = \frac{220}{38} = 5.7895 \text{ ohms}$$

$$\text{Resistance of second segment} = \frac{1/38 * (80)}{1} = \frac{80}{38} = 2.1053 \text{ ohms}$$

$$\text{The voltage across the resistor} = 2V * \frac{50 \text{ ohms}}{(50+5.7895+2.1053)\text{ohms}} = 1.727V$$

b) Resistivity of copper = $\frac{1 \text{ ohm}}{58 \mu m}$

$$\text{Resistance} = \frac{\rho L}{A}$$

$$\text{Resistance of first segment} = \frac{1/58 * (180+40)}{1} = \frac{220}{58} = 3.7931 \text{ ohms}$$

$$\text{Resistance of second segment} = \frac{1/58 * (80)}{1} = \frac{80}{58} = 1.3793 \text{ ohms}$$

$$\text{The voltage across the resistor} = 2V * \frac{50 \text{ ohms}}{(50+3.7931+1.3793)\text{ohms}} = 1.813V$$

Problem 10

```
/*structural implementation of  $f = (!a \cdot b \cdot c) + (a \cdot b \cdot !c)$ 
EE330 - Integrated Electronics/

`timescale 1ns/1ps //set timescale to something nice for simulation
module hw3q10(A, B, C, F); //define module and IO
    input A, B, C; //define A, B, and C as inputs
    output F; //define F as an output
    wire and1, and2; //define intermediary wires to be used
    and(and1, ~A, B, C); //and1 =  $A! \cdot B \cdot C$ 
    and(and2, A, B, ~C); //and2 =  $A \cdot B \cdot !C$ 
    or(F, and1, and2); //F = and1 + and2 =  $(A! \cdot B \cdot C) + (A \cdot B \cdot !C)$ 
endmodule //end the module

/*behavioral implementation of  $f = (!a \cdot b \cdot c) + (a \cdot b \cdot !c)$ 
EE330 - Integrated Electronics/

`timescale 1ns/1ps //set timescale to something nice for simulation
module hw3q10(A, B, C, f); //define module and IO

    input A, B, C; //define A, B, and C as inputs
    output F; //define F as an output
    reg out; //define an output register for used
    assign F = out; //assign output register to given output
    always @ (A or B or C) begin //when inputs change, execute the following
        out = (~A&B&C) + (A&B&~C); //f =  $(!A \cdot B \cdot C) + (A \cdot B \cdot !C)$ 
    end //end of preceding always block
endmodule //end the module

/*standard 3-input logic testbench
EE330 - Integrated Electronics
Nickolas Moser
February 2, 2022*/

`timescale 1ns/1ps //set timescale to something nice to simulate

module standard_tb(); //instantiate testbench module
```

```

reg a_in, b_in, c_in;                                //define input registers
wire out;                                             //define output wire
hw3q10 DUT(.A(a_in), .B(b_in), .C(c_in), .F(out)); //instantiate Device Under Test
    initial a_in = 0;                                //set initial input values
    initial b_in = 0;
    initial c_in = 0;
    always #1 a_in = ~a_in;                          //for input n, toggle every 2^n time units
    always #2 b_in = ~b_in;
    always #4 c_in = ~c_in;

endmodule                                             //end testbench module

```

