

EE 330 Fall 2024
Homework 6 Solutions

Problem 1 : Assume a resistor has a resistance of $1\text{k}\Omega$ at $T = 300^\circ\text{K}$. If the TCR of this resistor is constant of value $2000\text{ppm}/^\circ\text{C}$, what will be the resistance at $T = 350^\circ\text{K}$?

Solution

$$R(T_2) = R(T_1) \left[1 + (T_2 - T_1) \frac{\text{TCR}}{10^6} \right] =$$
$$R(350^\circ\text{K}) = R(300^\circ\text{K}) \left[1 + (350 - 300) \frac{2000}{10^6} \right]$$
$$R(350^\circ\text{K}) = 1000 \left[1 + \left(50 \times \frac{2000}{10^6} \right) \right] = 1100\Omega = 1.1\text{k}\Omega$$

2.

We got the value of resistivity based on the doping density.

$$\text{Doping density} \rightarrow 5 \times 10^{14} \text{ cm}^{-3}$$

$$\text{Resistivity} \rightarrow 9.045 \Omega\text{-cm}$$

$$R = \frac{\rho L}{WH} = \frac{9.045 \times 0.2}{0.015 \times 0.005} = 24.12\text{k}\Omega$$



Problem 3





A) Left: if $V_{in} > 0.6$ then diode on else diode off, $v_{out} = 0$

$$V_{out} = \begin{cases} 0 & V_{in} < 0.6 \\ V_{in} - 0.6 & V_{in} \geq 0.6 \end{cases}$$

Right: if v_{out} neg then I_R is up and not possible with diode, so only positive voltages are passed
 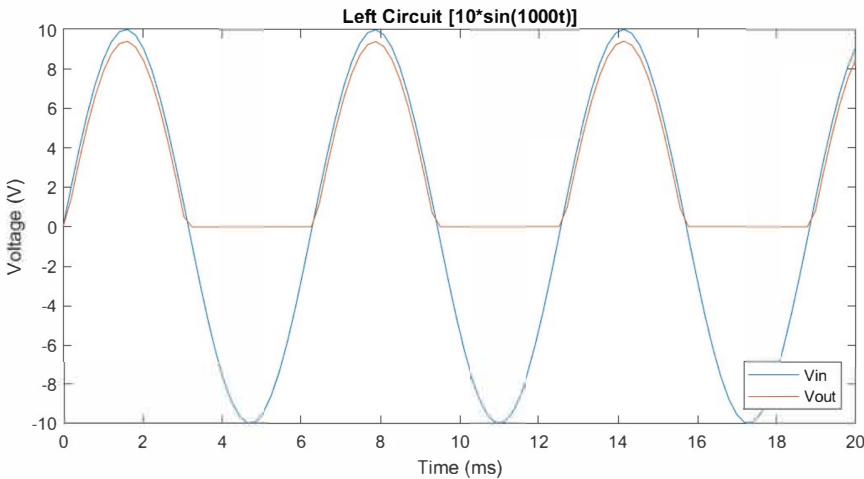
$$V_{out} = \begin{cases} 0 & V_{in} < 0 \\ V_{in} & V_{in} \geq 0 \end{cases}$$



    

Problem 4 (a)

Using voltage divider, $V_{out} = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} V_{in}$

3dB frequency = cut off frequency = $f_c = 10\text{MHz}$

$\rightarrow f_c = \frac{1}{2\pi RC}$

$\rightarrow C = \frac{1}{2\pi R f_c} = \frac{1}{2\pi \times 10 \times 10^3 \times 10 \times 10^6} = 1.592 \times 10^{-12} = 1.592\text{pF}$

\rightarrow Using $R(T_2) = R(T_1) \left[1 + (T_2 - T_1) \frac{2300}{10^6} \right]$
 $C(T_2) = C(T_1) \left[1 + (T_2 - T_1) \frac{1000}{10^6} \right]$

the temperature value pairs for each resistor can be found as

\rightarrow At 273K , $R = 10\text{k}\Omega$, $C = 1.592\text{pF}$ and the 3dB frequency = 10MHz

\rightarrow At 350K , $R = 11.771\text{k}\Omega$, $C = 1.715\text{pF}$ and 3dB frequency = 7.88MHz

so the graphs will look as shown below with the 3dB frequency or cut off frequency as calculated above.

(b)

$\% \text{ change in 3dB frequency} = \frac{10\text{MHz} - 7.88\text{MHz}}{10\text{MHz}} \times 100\%$

$= \underline{\underline{21.2\%}}$

5.

P5.) What is the range in the diode current?

$$I_D = J_s A e^{\frac{V_D}{nV_t}}$$

$$V_D = 0.5V \text{ or } 0.6$$

$$J_s = 10^{-15} \text{ A}/\mu^2$$

$$V_t = 26 \text{ mV}$$

$$A = 50 \mu^2$$

$$n = 1$$

0.5 V

$$I_D = 10^{-15} \frac{\text{A}}{\mu^2} \cdot 50 \mu^2 e^{\frac{0.5V}{26 \text{ mV}}}$$

$$I_D = 11.241 \mu\text{A}$$

0.6 V

$$I_D = 10^{-15} \frac{\text{A}}{\mu^2} \cdot 50 \mu^2 e^{\frac{0.6V}{26 \text{ mV}}}$$


$$I_D = 526.199 \mu\text{A}$$

The range in the diode current is between

$$\underline{11.241 \mu\text{A} \sim 526.199 \mu\text{A}}$$

P6.) Determine the current I_D . $V_x = 10V$ $A = 200 \mu^2$
 
$$J_s = 10^{-15} \text{ A}/\mu^2 \quad V_t = 26 \text{ mV}$$



$$V_x = I_D \cdot R + V_D$$

$$\underline{V_D = 0.6V}$$

$$\Rightarrow 10V = I_D \cdot 2k + 0.6V$$

$$I_D = \frac{10V - 0.6V}{2k} = 4.7 \text{ mA}$$

$$\underline{I_D = 4.7 \text{ mA} > 0}$$


Diode is "on"

7). Since V_x is much smaller, it can be shown that the simplified diode models will not be good enough to accurately predict I_D so must use diode equation

$$\left. \begin{aligned} 520\text{mV} &= I_D(2\text{k}) + V_D \\ I_D &= J_s A e^{\frac{V_D}{nV_t}} \end{aligned} \right\} \begin{array}{l} \text{eliminate} \\ V_D \end{array} \quad 520\text{mV} = 2\text{k}I_D + nV_t \ln\left(\frac{I_D}{J_s A}\right)$$

with $n=1$, $V_t = 25\text{mV}$ and $J_s A = 2\text{E}-14$, solving iteratively for I_D we obtain $I_D = 26.5\mu\text{A}$

 8) For circuit on left Guess D_1 and D_2 ON.



To verify guess, must show $I_{D1} > 0$ & $I_{D2} > 0$


solving, obtain $V_O = -20\text{V}$. must now verify

$$I_{D2} = \frac{20\text{V}}{4\text{k}} = 5\text{mA} \quad I_{D1} = I_A + I_{D2} = \frac{80\text{V}}{1\text{k}} + 5\text{mA} = 85\text{mA}$$

thus $I_{D1} > 0$ & $I_{D2} > 0$ so $V_O = -20\text{V}$ solution is valid

For the right circuit:

 I will start by assuming the middle diode is off, and the rightmost diode is on. This guess is made on the assumption that the location of the 10V source relative to the 4V source will cause currents to flow in the wrong directions. This allows us to treat the middle diode as an open circuit, giving us the following diagram.



As the 10V source drives an open circuit and the 10kΩ resistor ends at an open circuit, we can neglect them. Using KVL, we can find the current through the loop using the following equation:


$$4V - (i_2 * 10k\Omega) - 0.7V - (i_2 * 10k\Omega) = 0$$

This should reduce down to $i_2 = \frac{3.3V}{20k\Omega} = 165\mu A$, which gives a 1.65V drop across each resistor. Additionally, this gives a voltage of 2.35V at the anode of the rightmost diode. With the 10V source at the cathode of the middle diode, this would make the voltage across the middle 10kΩ resistor and diode -7.65V, meaning current would be flowing the wrong direction through the diode and confirming the initial assumption that it is off. This gives us the result of $i_2 = 165\mu A$.

9. a)

Case 1: $V_{in} < 0$

Assume D_2 off D_1 on

 

$$V_{OUT} = -\frac{R_2}{R_1} V_{IN} \quad (\text{inverting amplifier})$$

$V_N = 0V$ (virtual ground due to ideal op amp)

Since V_{IN} is negative, V_{OUT} is positive


So, D_2 would be reverse biased and D_1 would be forward biased.

so assumptions are correct.

current flows out through R_2 and R_3

Case 2: $V_{IN} \geq 0$

Assume D_2 off, D_1 on

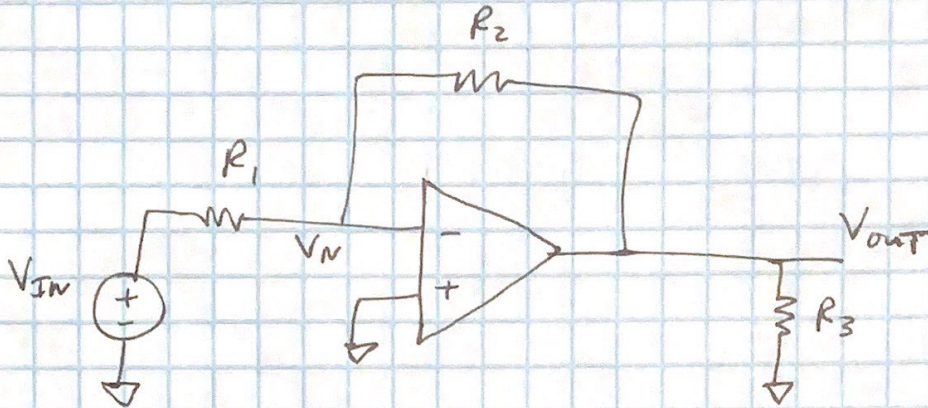


$$V_{OUT} = -\frac{R_2}{R_1} V_{IN}$$

$$V_N = 0 \quad (\text{ideal op amp})$$

So, current flows into op amp

So, assumption for D_2 is correct but D_1 assumption is wrong

Assume D_1, D_2 both off

 

op amp has no effect because it is disconnected

So,

$$V_{OUT} = \frac{R_3}{R_1 + R_2 + R_3} V_{IN}$$

Op amp equation:

$$V_o = A (V_p - V_n) \quad \left(A = \infty \text{ for ideal case} \right)$$

$$V_p = 0$$

$$V_n = \frac{R_2 + R_3}{R_1 + R_2 + R_3} V_{IN}$$

So, ~~V_o~~ $V_o = -\infty$

↳ V_o of op amp saturates at negative supply

So, $V_{O1} = V_N - \infty \rightarrow$ reverse biased

~~$V_{O2} = \dots$~~


~~$V_{O2} = -\infty - V_{OUT} = -\infty$~~ \rightarrow reverse biased

Assumptions are correct

Note, one could make $V_{IN} = 0$ a third case, but when this occurs everything in the circuit goes to 0V so it is modeled by Case 2

So,
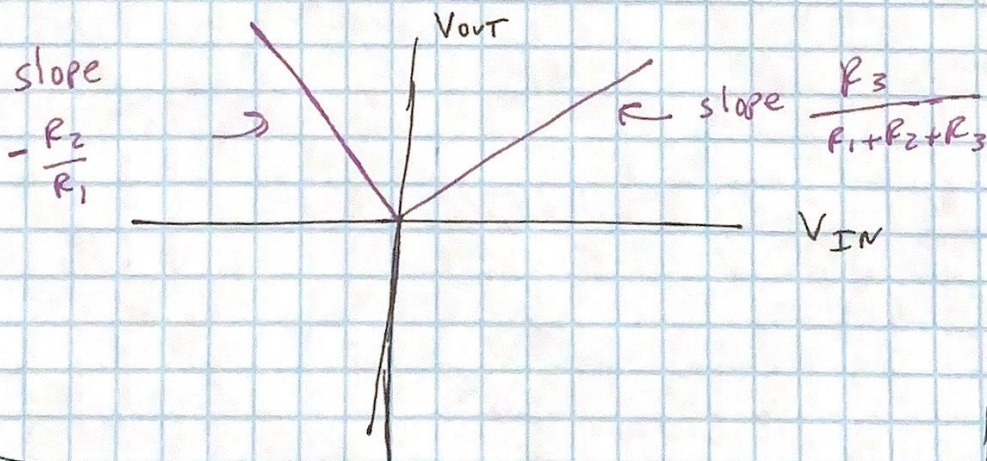
$$V_{OUT} = \begin{cases} -\frac{R_2}{R_1} V_{IN}, & V_{IN} < 0 \\ \frac{R_3}{R_1 + R_2 + R_3} V_{IN}, & V_{IN} \geq 0 \end{cases}$$



b) This circuit amplifies the absolute value of the input ~~signal~~

~~if~~ signal if $\frac{R_2}{R_1} = \frac{R_3}{R_1 + R_2 + R_3}$

Otherwise it still amplifies and rectifies the signal but not the absolute value.


```

module demux4_1(in,op0,op1,op2,op3,demux_sel,en); //initiation of module

    input in,en; //initiation of input pins
    input [1:0] demux_sel; //intitiation of select pin for demux output

    output reg op0,op1,op2,op3; //initiation of outputs

    always @(*) begin // starts for any change in values
        // active low input = 1
        if (en) begin
            op0 = 0;
            op1 = 0;
            op2 = 0;
            op3 = 0;
            end

        else begin
            case(demux_sel) //for different selections the output is
            // received at a different pin
            2'b00:begin
                op0 = in;
                op1 = 0;
                op2 = 0;
                op3 = 0;
                end
            2'b01:begin
                op0 = 0;
                op1 = in;
                op2 = 0;
                op3 = 0;
                end
            2'b10:begin
                op0 = 0;
                op1 = 0;
                op2 = in;
                op3 = 0;
                end
            2'b11:begin
                op0 = 0;
                op1 = 0;
                op2 = 0;
                op3 = in;
                end
            endcase
        end
    end
endmodule

```

```

/home/ha1207/ee465_verilog/demux_tb.v (demux_tb) - Default*
Ln#
1  `timescale 1ns/1ps
2
3  module demux_tb();
4
5      reg in, en; //inputs are initiated as registers
6      reg [1:0] demux_sel;
7
8      wire op0,op1,op2,op3; //outputs are initiated as wires
9
10     demux4_1 dut(in,op0,op1,op2,op3,demux_sel,en); //initiation of dut
11     initial in = 1;
12     initial en = 0;
13
14     initial demux_sel = 2'b00;
15
16     always #1 demux_sel[0] = ~demux_sel[0]; //toggle the bit 0 every cycle
17     always #2 demux_sel[1] = ~demux_sel[1]; //toggle the bit 1 every 2 cycles
18
19     always #4 en = ~en; //toggle the enable pin every 4 clock cycles
20
21 endmodule
22

```

