

**EE330 Spring 2024
Homework 6 Solutions**

Problem 1 : Assume a resistor has a resistance of $1\text{k}\Omega$ at $T = 300^\circ\text{K}$. If the TCR of this resistor is constant of value $2000\text{ppm}/^\circ\text{C}$, what will be the resistance at $T = 350^\circ\text{K}$?

Solution

$$R(T_2) = R(T_1) \left[1 + (T_2 - T_1) \frac{\text{TCR}}{10^6} \right] =$$
$$R(350^\circ\text{K}) = R(300^\circ\text{K}) \left[1 + (350 - 300) \frac{2000}{10^6} \right]$$
$$R(350^\circ\text{K}) = 1000 \left[1 + \left(50 \times \frac{2000}{10^6} \right) \right] = 1100\Omega = 1.1\text{k}\Omega$$

2.

We got the value of resistivity based on the doping density.

$$\text{Doping density} \rightarrow 5 \times 10^{14} \text{ cm}^{-3}$$

$$\text{Resistivity} \rightarrow 9.045 \Omega\text{-cm}$$

$$R = \frac{\rho L}{WH} = \frac{9.045 \times 0.2}{0.015 \times 0.005} = 24.12\text{k}\Omega$$

Problem 4 (a)

Using voltage divider, $V_{out} = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} V_{in}$

3dB frequency = cut off frequency = $f_c = 10\text{MHz}$

$\rightarrow f_c = \frac{1}{2\pi RC}$

$\rightarrow C = \frac{1}{2\pi R f_c} = \frac{1}{2\pi \times 10 \times 10^3 \times 10 \times 10^6} = 1.592 \times 10^{-12} = 1.592\text{pF}$

\rightarrow Using $R(T_2) = R(T_1) \left[1 + (T_2 - T_1) \frac{2300}{10^6} \right]$
 $C(T_2) = C(T_1) \left[1 + (T_2 - T_1) \frac{1000}{10^6} \right]$

the temperature value pairs for each resistor can be found as

\rightarrow At 273K , $R = 10\text{k}\Omega$, $C = 1.592\text{pF}$ and the 3dB frequency = 10MHz

\rightarrow At 350K , $R = 11.771\text{k}\Omega$, $C = 1.715\text{pF}$ and 3dB frequency = 7.88MHz

so the graphs will look as shown below with the 3dB frequency or cut off frequency as calculated above.

(b)

$\% \text{ change in 3dB frequency} = \frac{10\text{MHz} - 7.88\text{MHz}}{10\text{MHz}} \times 100\%$

$= \underline{\underline{21.2\%}}$

5.

P5.) What is the range in the diode current?

$$I_D = J_s A e^{\frac{V_D}{nV_t}}$$

$$V_D = 0.5V \text{ or } 0.6$$

$$J_s = 10^{-15} \text{ A}/\mu^2$$

$$V_t = 26 \text{ mV}$$

$$A = 50 \mu^2$$

$$n = 1$$

0.5 V

$$I_D = 10^{-15} \frac{\text{A}}{\mu^2} \cdot 50 \mu^2 e^{\frac{0.5V}{26\text{mV}}}$$

$$I_D = 11.241 \mu\text{A}$$

0.6 V

$$I_D = 10^{-15} \frac{\text{A}}{\mu^2} \cdot 50 \mu^2 e^{\frac{0.6V}{26\text{mV}}}$$


$$I_D = 526.199 \mu\text{A}$$

The range in the diode current is between

$$\underline{11.241 \mu\text{A} \sim 526.199 \mu\text{A}}$$

P6.) Determine the current I_D . $V_x = 10V$ $A = 200 \mu^2$
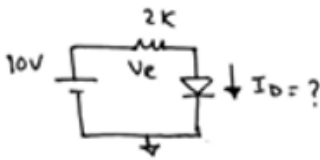
$$J_s = 10^{-15} \text{ A}/\mu^2 \quad V_t = 26 \text{ mV}$$



$$V_x = I_D \cdot R + V_D$$

$$\underline{V_D = 0.6V}$$

$$\Rightarrow 10V = I_D \cdot 2k + 0.6V$$

$$I_D = \frac{10V - 0.6V}{2k} = 4.7 \text{ mA}$$

$$\underline{I_D = 4.7 \text{ mA} > 0}$$


Diode is "on"

7). Since V_x is much smaller, it can be shown that the simplified diode models will not be good enough to accurately predict I_D so must use diode equation

$$\left. \begin{aligned} 520\text{mV} &= I_D(2\text{k}) + V_D \\ I_D &= J_s A e^{\frac{V_D}{nV_t}} \end{aligned} \right\} \text{eliminate } V_D \quad 520\text{mV} = 2\text{k}I_D + nV_t \ln\left(\frac{I_D}{J_s A}\right)$$

with $n=1$, $V_t = 25\text{mV}$ and $J_s A = 2\text{E}-14$, solving iteratively for I_D we obtain $I_D = 26.5\mu\text{A}$

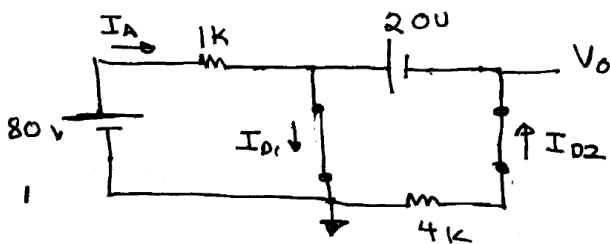8) For circuit on left Guess D_1 and D_2 ON.



To verify guess, must show $I_{D1} > 0$ & $I_{D2} > 0$


solving, obtain $V_O = -20\text{V}$. must now verify

$$I_{D2} = \frac{20\text{V}}{4\text{k}} = 5\text{mA} \quad I_{D1} = I_A + I_{D2} = \frac{80\text{V}}{1\text{k}} + 5\text{mA} = 85\text{mA}$$

thus $I_{D1} > 0$ & $I_{D2} > 0$ so $V_O = -20\text{V}$ solution is valid

For the right circuit:

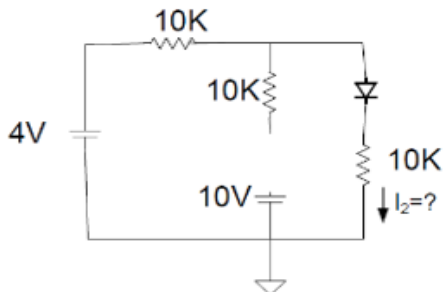I will start by assuming the middle diode is off, and the rightmost diode is on. This guess is made on the assumption that the location of the 10V source relative to the 4V source will cause currents to flow in the wrong directions. This allows us to treat the middle diode as an open circuit, giving us the following diagram.



As the 10V source drives an open circuit and the 10kΩ resistor ends at an open circuit, we can neglect them. Using KVL, we can find the current through the loop using the following equation:


$$4V - (i_2 * 10k\Omega) - 0.7V - (i_2 * 10k\Omega) = 0$$

This should reduce down to $i_2 = \frac{3.3V}{20k\Omega} = 165\mu A$, which gives a 1.65V drop across each resistor. Additionally, this gives a voltage of 2.35V at the anode of the rightmost diode. With the 10V source at the cathode of the middle diode, this would make the voltage across the middle 10kΩ resistor and diode -7.65V, meaning current would be flowing the wrong direction through the diode and confirming the initial assumption that it is off. This gives us the result of $i_2 = 165\mu A$.

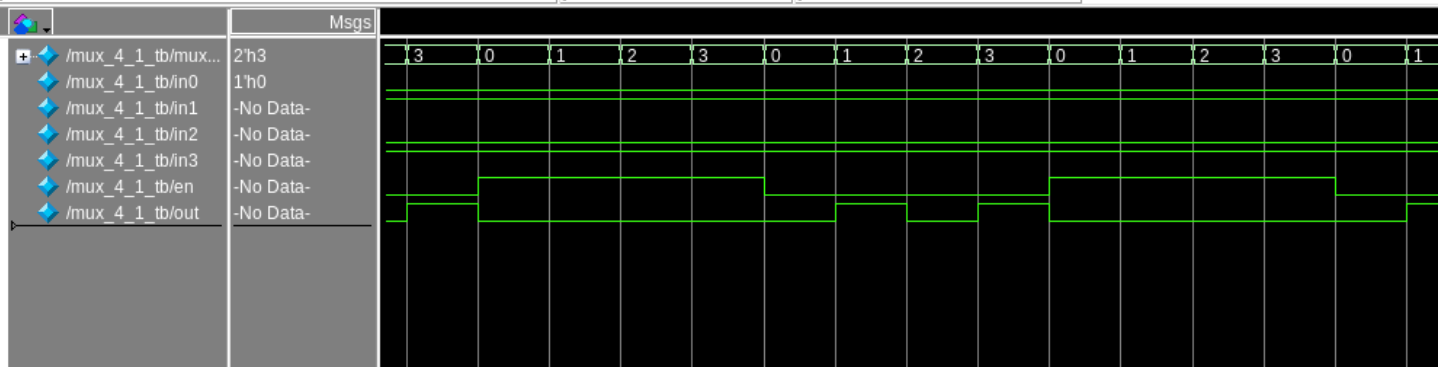Problem 10

```
Line
1 `timescale 1ns/1ps
2 module mux4_1(in0,in1,in2,in3,en,mux_sel,out); //initiation of module
3
4     input in0,in1,in2,in3,en; //initiation of input bits
5     input [1:0] mux_sel; //initiation of select pin for mux
6     output reg out; // initiation of output
7
8     always @(*)begin //starts for any change values
9         if (en) begin //active low input =1
10            out = 0; //active low output
11        end
12
13        else
14            begin // for selecting a mux pin
15                case(mux_sel) //assigning values based on select pin
16                    2'b00 : out = in0;
17                    2'b01 : out = in1;
18                    2'b10 : out = in2;
19                    2'b11 : out = in3;
20                endcase
21            end
22
23        end
24    end
25 endmodule
26
27
```

```
Ln#
1 `timescale 1ns/1ps
2 module mux_4_1_tb();
3
4     reg [1:0] mux_sel; //inputs are initiated as registers
5
6     reg in0,in1,in2,in3,en;
7
8     wire out; //outputs are initiated as wires
9
10    mux4_1 dut(in0,in1,in2,in3,en,mux_sel,out); //initiation of dut
11
12    initial in0 = 0;
13    initial in1 = 1;
14    initial in2 = 0;
15    initial in3 = 1;
16    initial en = 0;
17    initial mux_sel = 2'b00;
18
19    always #1 mux_sel[0] = ~mux_sel[0];
20    always #2 mux_sel[1] = ~mux_sel[1];
21
22    always #4 en = ~en;
23
24 endmodule
25
26
```



```

module demux4_1(in,op0,op1,op2,op3,demux_sel,en); //initiation of module

    input in,en; //initiation of input pins
    input [1:0] demux_sel; //intitiation of select pin for demux output

    output reg op0,op1,op2,op3; //initiation of outputs

    always @(*) begin // starts for any change in values
        // active low input = 1
        if (en) begin
            op0 = 0;
            op1 = 0;
            op2 = 0;
            op3 = 0;
            end

        else begin
            case(demux_sel) //for different selections the output is
            // received at a different pin
            2'b00:begin
                op0 = in;
                op1 = 0;
                op2 = 0;
                op3 = 0;
            end
            2'b01:begin
                op0 = 0;
                op1 = in;
                op2 = 0;
                op3 = 0;
            end
            2'b10:begin
                op0 = 0;
                op1 = 0;
                op2 = in;
                op3 = 0;
            end
            2'b11:begin
                op0 = 0;
                op1 = 0;
                op2 = 0;
                op3 = in;
            end

            endcase
        end
    end

endmodule

```

```

/home/ha1207/ee465_verilog/demux_tb.v (demux_tb) - Default*
Ln#
1  `timescale 1ns/1ps
2
3  module demux_tb();
4
5      reg in, en; //inputs are initiated as registers
6      reg [1:0] demux_sel;
7
8      wire op0,op1,op2,op3; //outputs are initiated as wires
9
10     demux4_1 dut(in,op0,op1,op2,op3,demux_sel,en); //initiation of dut
11     initial in = 1;
12     initial en = 0;
13
14     initial demux_sel = 2'b00;
15
16     always #1 demux_sel[0] = ~demux_sel[0]; //toggle the bit 0 every cycle
17     always #2 demux_sel[1] = ~demux_sel[1]; //toggle the bit 1 every 2 cycles
18
19     always #4 en = ~en; //toggle the enable pin every 4 clock cycles
20
21 endmodule
22

```

