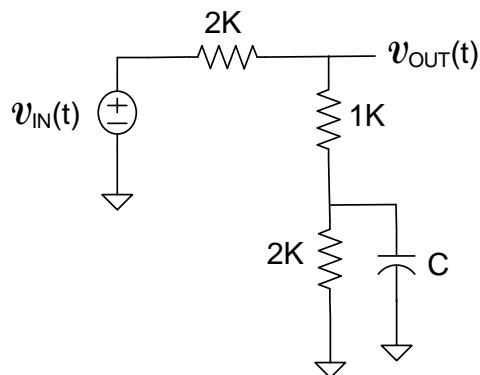


EE 330  
 Homework 9  
 Spring 2024  
 Due Friday March 22 at noon.

Unless specified to the contrary, assume all n-channel MOS transistors have model parameters  $\mu_n C_{OX} = 100 \mu\text{A}/\text{V}^2$  and  $V_{Tn} = 0.75\text{V}$ , all p-channel transistors have model parameters  $\mu_p C_{OX} = 33 \mu\text{A}/\text{V}^2$  and  $V_{Tp} = -0.75\text{V}$ . Correspondingly, assume all npn BJT transistors have model parameters  $J_S = 10^{-14} \text{A}/\mu^2$  and  $\beta = 100$  and all pnp BJT transistors have model parameters  $J_S = 10^{-14} \text{A}/\mu^2$  and  $\beta = 25$ . If the emitter area of a transistor is not given, assume it is  $100 \mu^2$ . Assume all diodes are characterized by the model parameters  $J_{SX} = 0.5 \text{A}/\mu\text{m}^2$ ,  $V_{G0} = 1.17\text{V}$ , and  $m = 2.3$ .


**Problem 1** Assume the capacitor  $C$  is very large.

- Draw the small-signal equivalent circuit
- Determine the quiescent output voltage
- Determine the small-signal voltage gain.
- Determine the output voltage if  $v_{IN}(t) = 2\sin 500t$




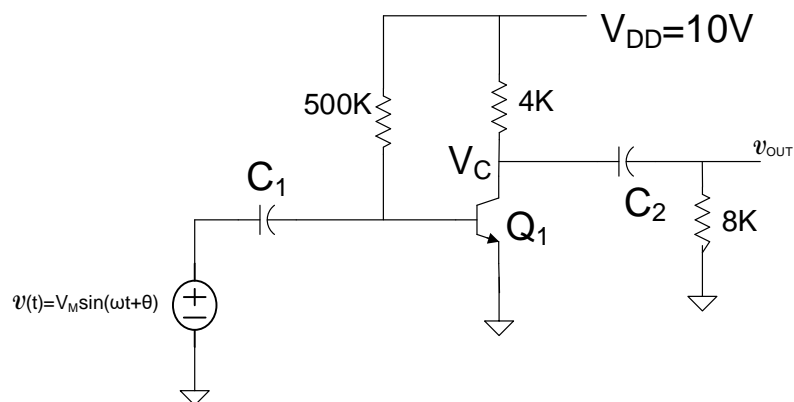**Problem 2** Assume the capacitors are very large and  $V_M$  is small.

- Draw the small signal equivalent circuit for the amplifier shown
- Determine the quiescent value of  $V_C$  and  $V_{OUT}$




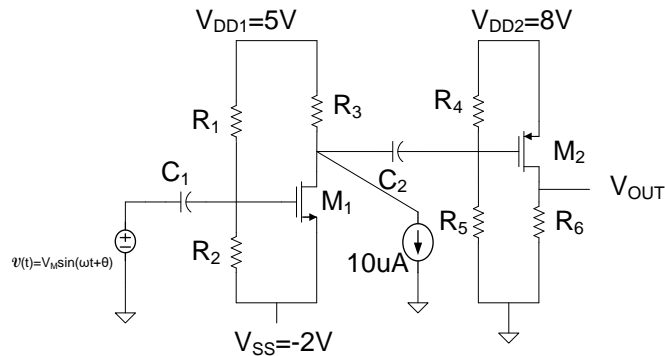**Problem 3** Obtain the small signal equivalent circuit for the following network. Assume the transistors are operating in the saturation region, all capacitors are large, and  $V_M$  is small. You need not solve the circuit.



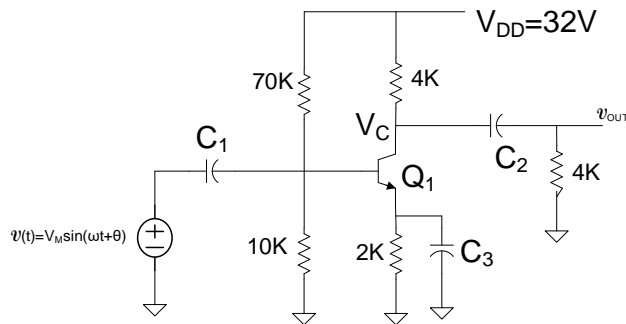
**Problem 4** Assume the capacitors are all very large and  $V_m$  is small.

- Draw the small signal equivalent circuit for the amplifier shown
- Determine the quiescent value of  $V_C$  and  $V_{OUT}$



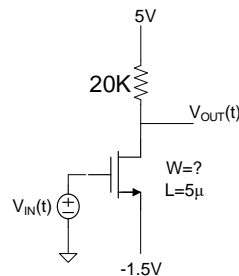
**Problem 5** Consider the following circuit

- Determine the width  $W$  so that the quiescent drain current is  $0.1\text{mA}$
- Draw the small-signal equivalent circuit
- With the drain current specified in part a), determine the small-signal voltage gain (do not use small-signal device models to solve this part of the problem)
- Determine the THD if the input is a  $1\text{KHz}$  sinusoidal signal of amplitude  $200\text{mV}$  0-p



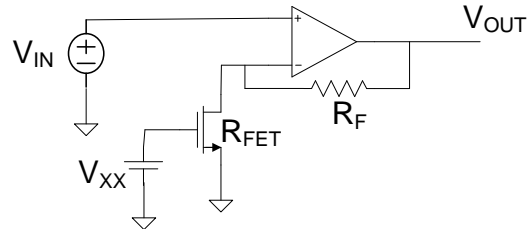
**Problem 6** Assume  $V_{IN}$  is a low frequency nearly sinusoidal waveform that is below 10mV 0-P and that  $W=12\mu\text{m}$ ,  $L=1\mu\text{m}$  for the MOSFET.

- Determine the voltage gain of this circuit if  $V_{XX}=2.5\text{V}$ .
- How does the voltage gain change if  $V_{XX}$  is swept between 1.5V and 4V?



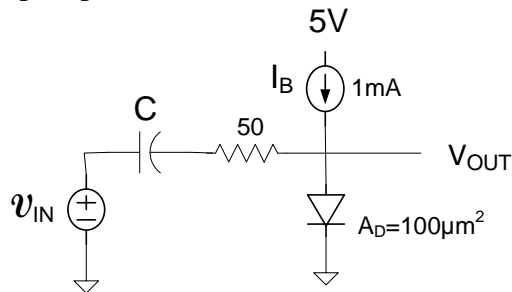**Problem 7** Consider the following circuit operating at  $T=300\text{K}$ . Assume the capacitor  $C$  is very large and the  $v_{IN}$  is a small-signal input.

- Determine the quiescent output voltage.
- Draw the small-signal equivalent circuit
- Determine the small-signal voltage gain from the input to the output.
- Repeat part c) if the current  $I_B$  is increased to 5mA



**Problem 8** Consider the following circuit operating at  $T=300\text{K}$ . Assume  $v_{IN}$  is a small-signal voltage source.

- Draw the small-signal equivalent circuit
- If the voltage  $V_{BB}$  is adjusted so that the quiescent diode current is 1mA, determine the small signal voltage gain  $A_V = \frac{v_{OUT}}{v_{IN}}$
- Repeat part b) if  $V_{BB}$  is adjusted so that the quiescent diode current is 10mA

