

EE 330

Lecture 17

MOSFET Modeling


Fall 2023 Exam Schedule

Exam 1	Friday Sept 22	
Exam 2	Friday Oct 20	
Exam 3	Friday Nov. 17	
Final	Monday Dec 11	12:00 – 2:00 p.m.


Prelab Announcement

There will be a pre-lab posted on the class WEB site for Lab 7

Limitations of Existing MOSFET Models

 

What is Y when $A=B=V_{DD}$

 


For minimum-sized devices in a 0.5u process with $V_{DD}=5V$

$$C_{GS} \cong 1.5fF$$

$$R_{sw} \cong \left. \begin{array}{l} 2K\Omega \text{ n-channel} \\ 6K\Omega \text{ p-channel} \end{array} \right\}$$

 What is R_{sw} if MOSFET is not minimum sized?




What is power dissipation if A is stuck at an intermediate voltage?

Better Model of MOSFET is Needed!

Review from last lecture

n-Channel MOSFET Operation and Model

 


$$\begin{aligned} I_D &= 0 \\ I_G &= 0 \\ I_B &= 0 \end{aligned}$$

Model in Cutoff Region

Review from last lecture

n-Channel MOSFET Operation and Model

 Critical value of V_{GS} that creates inversion layer termed threshold voltage, V_{TH}



Increase V_{GS} more

Inversion layer forms in channel

Inversion layer will support current flow from D to S

Channel behaves as thin-film resistor


$$I_D R_{CH} = V_{DS}$$

$$I_G = 0$$

$$I_B = 0$$

Review from last lecture

n-Channel MOSFET Operation and Model

 

Increase V_{DS} and $V_{GS} > V_{TH}$

$V_{GC}(x)$ changes with x for larger V_{DS}

Inversion layer thins near drain

I_D no longer linearly dependent upon V_{DS}


Still termed “ohmic” or “triode” region of operation

$$I_D = ?$$

$$I_G = 0$$

$$I_B = 0$$

Triode Region of Operation

 

For V_{DS} larger

~~$$R_{CH} = \frac{L}{W} \frac{1}{(V_{GS} - V_{TH}) \mu C_{OX}}$$~~


$$I_D = \mu C_{OX} \frac{W}{L} \left(V_{GS} - V_{TH} - \frac{V_{DS}}{2} \right) V_{DS}$$

$$I_G = I_B = 0$$

Model in Triode Region

Review from last lecture

n-Channel MOSFET Operation and Model

 

Increase V_{DS} even more (beyond $V_{GS} - V_{TH}$)


Nothing much changes !!

Termed “saturation” region of operation

$$\begin{aligned} I_D &=? \\ I_G &=0 \\ I_B &=0 \end{aligned}$$

Review from last lecture

Saturation Region of Operation

 

For V_{DS} in Saturation

$$I_D = \frac{\mu C_{OX} W}{2L} (V_{GS} - V_{TH})^2$$

$$I_G = I_B = 0$$


Model in Saturation Region

Review from last lecture

Model Summary

n-channel MOSFET

 Notation: Don't confuse V_{TH} with $V_t = kT/q$



$$I_D = \begin{cases} 0 & V_{GS} \leq V_{TH} & \text{Cutoff} \\ \mu C_{OX} \frac{W}{L} \left(V_{GS} - V_{TH} - \frac{V_{DS}}{2} \right) V_{DS} & V_{GS} \geq V_T & V_{DS} < V_{GS} - V_{TH} & \text{Triode} \\ \mu C_{OX} \frac{W}{2L} (V_{GS} - V_{TH})^2 & V_{GS} \geq V_T & V_{DS} \geq V_{GS} - V_{TH} & \text{Saturation} \end{cases}$$

$$I_G = I_B = 0$$

Model Parameters: $\{\mu, V_{TH}, C_{OX}\}$ Design Parameters : $\{W, L\}$

This is a piecewise model (not piecewise linear though)


Piecewise model is continuous at transition between regions

(Deep triode special case of triode where V_{DS} is small $R_{CH} = \frac{L}{W} \frac{1}{(V_{GS} - V_{TH}) \mu C_{OX}}$)

Note: This is the third model we have introduced for the MOSFET

Model Summary

n-channel MOSFET

 

$V_{BS} = 0$

$$I_D = \begin{cases} 0 & V_{GS} \leq V_{TH} \\ \mu C_{OX} \frac{W}{L} \left(V_{GS} - V_{TH} - \frac{V_{DS}}{2} \right) V_{DS} & V_{GS} \geq V_{TH} \quad V_{DS} < V_{GS} - V_{TH} \\ \mu C_{OX} \frac{W}{2L} (V_{GS} - V_{TH})^2 & V_{GS} \geq V_{TH} \quad V_{DS} \geq V_{GS} - V_{TH} \end{cases}$$

$$I_G = I_B = 0$$

Observations about this model (developed for $V_{BS}=0$):

$$I_D = f_1(V_{GS}, V_{DS})$$


$$I_G = f_2(V_{GS}, V_{DS})$$

$$I_B = f_3(V_{GS}, V_{DS})$$

This is a nonlinear piecewise model characterized by the functions f_1 , f_2 , and f_3 where we have assumed that the port voltages V_{GS} and V_{DS} are the independent variables and the drain currents are the dependent variables

Review from last lecture

General Nonlinear Models


 


$$I_1 = f_1(V_1, V_2)$$



$$I_2 = f_2(V_1, V_2)$$

I_1 and I_2 are 3-dimensional relationships which are often difficult to visualize

  Two-dimensional representation of 3-dimensional relationships



Graphical Representation of MOS Model



 
 


$$I_D = \begin{cases} 0 & V_{GS} \leq V_{TH} \\ \mu C_{ox} \frac{W}{L} \left(V_{GS} - V_{TH} - \frac{V_{DS}}{2} \right) V_{DS} & V_{GS} \geq V_{TH} \quad V_{DS} < V_{GS} - V_{TH} \\ \mu C_{ox} \frac{W}{2L} (V_{GS} - V_{TH})^2 & V_{GS} \geq V_{TH} \quad V_{DS} \geq V_{GS} - V_{TH} \end{cases}$$

$$I_G = I_B = 0$$


Parabola separated triode and saturation regions and corresponds to $V_{DS} = V_{GS} - V_{TH}$

PMOS and NMOS Models

    

- Functional form identical, sign changes and parameter values different
- Will give details about p-channel model later

 Example: Determine the output voltage for the following circuit using the square-law model of the MOSFET. Assume $V_{TH}=1V$ and $\mu C_{OX}=100\mu AV^{-2}$




Solution:

Since $V_{GS} > V_{TH}$, M_1 is operating in either saturation or triode region

Strategy will be to guess region of operation, solve, and then verify region

 Example: Determine the output voltage for the following circuit using the square-law model of the MOSFET. Assume $V_{TH}=1V$ and $\mu C_{OX}=100\mu AV^{-2}$



Solution:

Guess M_1 in saturation

$$5V = I_D 10K + V_{OUT}$$

$$I_D = \frac{\mu C_{OX} W}{2L} (3 - V_{TH})^2$$

Required verification: $V_{DS} > V_{GS} - V_{TH}$

Can eliminate I_D between these 2 equations to obtain V_{OUT}

Example: Determine the output voltage for the following circuit using the square-law model of the MOSFET. Assume $V_{TH}=1V$ and $\mu C_{OX}=100\mu AV^{-2}$

Guess M_1 in saturation

Required verification: $V_{DS} > V_{GS} - V_T$


$$\left. \begin{aligned} 5V &= I_D 10K + V_{OUT} \\ I_D &= \frac{\mu C_{OX} W}{2L} (3 - V_{TH})^2 \end{aligned} \right\}$$

$$V_{OUT} = 5V - 10K \left[\frac{100\mu AV^{-2} 10\mu}{2 \cdot 2\mu} (2V)^2 \right]$$

$$V_{OUT} = -5V$$

Verification: $V_{DS} = V_{OUT}$

 $-5 >? 2V - - 0$ No! So verification fails and Guess of region is invalid



Example: Determine the output voltage for the following circuit using the square-law model of the MOSFET. Assume $V_{TH}=1V$ and $\mu C_{OX}=100\mu AV^{-2}$

Guess M_1 in triode

Required verification: $V_{DS} < V_{GS} - V_T$

$$5V = I_D 10K + V_{OUT}$$

$$I_D = \frac{\mu C_{OX} W}{L} \left(3 - V_{TH} - \frac{V_{DS}}{2} \right) V_{DS}$$

$$V_{OUT} = 5V - 10K \left[\frac{100\mu AV^{-2} 10\mu}{2\mu} \left(2V - \frac{V_{OUT}}{2} \right) V_{OUT} \right]$$

$$V_{OUT} = 5V - \left[5 \left(2V - \frac{V_{OUT}}{2} \right) V_{OUT} \right]$$


Solving for V_{OUT} , obtain

$$V_{OUT} = 0.515V$$

Verification: $V_{DS} = V_{OUT}$





$0.515 <? 2V$ Yes!

 So verification succeeds and triode region is valid



$$V_{OUT} = 0.515V$$

Limitations of Existing Models

    


Switch-Level Models

Simple square-law Model



Voltage Gain
Input/Output Relationship ?

Model Extensions

 


Projections intersect $-V_{DS}$ axis at same point, termed Early Voltage


Typical values from -20V to -200V

Usually use parameter λ instead of V_A in MOS model

Model Extensions

 


Existing Model

 

Actual Device

Slope is not 0

Model Extensions

 

$$I_D = \begin{cases} 0 & V_{GS} \leq V_{TH} \\ \mu C_{OX} \frac{W}{L} \left(V_{GS} - V_{TH} - \frac{V_{DS}}{2} \right) V_{DS} & V_{GS} \geq V_{TH} \quad V_{DS} < V_{GS} - V_{TH} \\ \mu C_{OX} \frac{W}{2L} (V_{GS} - V_{TH})^2 \cdot (1 + \lambda V_{DS}) & V_{GS} \geq V_{TH} \quad V_{DS} \geq V_{GS} - V_{TH} \end{cases}$$


Note: This introduces small discontinuity in model at SAT/Triode transition

Further Model Extensions

Existing model does not depend upon the bulk voltage !



 
Observe that changing the bulk voltage will change the electric field in the channel region !



Further Model Extensions

Existing model does not depend upon the bulk voltage !

 Observe that changing the bulk voltage will change the electric field in the channel region !



Changing the bulk voltage will change the thickness of the inversion layer

Changing the bulk voltage will change the threshold voltage of the device

$$V_{TH} = V_{TH0} + \gamma \left(\sqrt{\phi - V_{BS}} - \sqrt{\phi} \right)$$


ϕ is the surface potential (some authors use symbol Φ_S)

γ is the bulk threshold

Typical Bulk Effects on Threshold Voltage for n-channel Devices

$$V_{TH} = V_{TH0} + \gamma \left(\sqrt{\phi - V_{BS}} - \sqrt{\phi} \right)$$
 
$$\gamma \cong 0.4V^{1/2} \quad \phi \cong 0.6V$$




- Bulk-Diffusion Generally Reverse Biased ($V_{BS} < 0$ or at least $V_{BS} < 0.3V$) for n-channel
- Shift in threshold voltage with bulk voltage can be substantial
- Often $V_{BS} = 0$

Typical Bulk Effects on Threshold Voltage for n-channel Devices

$$V_{TH} = V_{TH0} + \gamma \left(\sqrt{\phi - V_{BS}} - \sqrt{\phi} \right)$$
 
$$\gamma \cong 0.4V^{1/2} \quad \phi \cong 0.6V$$




$$\Delta V = V_{TH} - V_{TH0} = \gamma \left(\sqrt{\phi - V_{BS}} - \sqrt{\phi} \right)$$

$$\Delta V \cong 0.4 \left(\sqrt{0.6V - (-5V)} - \sqrt{0.6} \right) \cong 0.64V$$

Typical Bulk Effects on Threshold Voltage for p-channel Devices

$$V_{TH} = V_{TH0} - \gamma \left(\sqrt{\phi + V_{BS}} - \sqrt{\phi} \right)$$
 
$$\gamma \cong 0.4V^{1/2} \quad \phi \cong 0.6V$$




- Bulk-Diffusion Generally Reverse Biased ($V_{BS} > 0$ or at least $V_{BS} > -0.3V$) for p-channel
- Same functional form as for n-channel but $V_{TH0} < 0$
- Magnitude of threshold voltage increases with magnitude of reverse bias

Model Extension Summary

$$I_G = 0$$

$$I_B = 0$$

 


$$I_D = \begin{cases} 0 & V_{GS} \leq V_{TH} \\ \mu C_{OX} \frac{W}{L} \left(V_{GS} - V_{TH} - \frac{V_{DS}}{2} \right) V_{DS} & V_{GS} \geq V_{TH} \quad V_{DS} < V_{GS} - V_{TH} \\ \mu C_{OX} \frac{W}{2L} (V_{GS} - V_{TH})^2 \cdot (1 + \lambda V_{DS}) & V_{GS} \geq V_{TH} \quad V_{DS} \geq V_{GS} - V_{TH} \end{cases}$$


$$V_{TH} = V_{TH0} + \gamma \left(\sqrt{\phi - V_{BS}} - \sqrt{\phi} \right)$$

Model Parameters : $\{\mu, C_{OX}, V_{TH0}, \phi, \gamma, \lambda\}$

 Design Parameters : $\{W, L\}$ but only one degree of freedom W/L



Operation Regions by Applications

 

Most analog circuits operate in the saturation region

(basic VVR operates in triode and is an exception)

Most digital circuits operate in triode and cutoff regions and switch between these two with Boolean inputs

Model Extension (short devices)

$$I_D = \begin{cases} 0 & V_{GS} \leq V_{TH} \\ \mu C_{OX} \frac{W}{L} \left(V_{GS} - V_{TH} - \frac{V_{DS}}{2} \right) V_{DS} & V_{GS} \geq V_{TH} \quad V_{DS} < V_{GS} - V_{TH} \\ \mu C_{OX} \frac{W}{2L} (V_{GS} - V_{TH})^2 & V_{GS} \geq V_{TH} \quad V_{DS} \geq V_{GS} - V_{TH} \end{cases}$$

As the channel length becomes very short, velocity saturation will occur in the channel and this will occur with electric fields around $2V/u$. So, if a gate length is around $1u$, then voltages up to $2V$ can be applied without velocity saturation. But, if gate length decreases and voltages are kept high, velocity saturation will occur

$$I_D = \begin{cases} 0 & V_{GS} \leq V_{TH} \\ \frac{\theta_2}{\theta_1} \mu C_{OX} \frac{W}{L} (V_{GS} - V_{TH})^{\frac{\alpha}{2}} V_{DS} & V_{GS} \geq V_{TH} \quad V_{DS} < \theta_1 (V_{GS} - V_{TH})^{\frac{\alpha}{2}} \\ \theta_2 \mu C_{OX} \frac{W}{L} (V_{GS} - V_{TH})^{\alpha} & V_{GS} \geq V_{TH} \quad V_{DS} \geq \theta_1 (V_{GS} - V_{TH})^{\frac{\alpha}{2}} \end{cases}$$

α is the velocity saturation index, $2 \geq \alpha \geq 1$

Model Extension (short devices)

(n-channel device)

$$I_D = \begin{cases} 0 & V_{GS} \leq V_{TH} \\ \frac{\theta_2}{\theta_1} \mu C_{OX} \frac{W}{L} (V_{GS} - V_{TH})^{\frac{\alpha}{2}} V_{DS} & V_{GS} \geq V_{TH} \quad V_{DS} < \theta_1 (V_{GS} - V_{TH})^{\frac{\alpha}{2}} \\ \theta_2 \mu C_{OX} \frac{W}{L} (V_{GS} - V_{TH})^{\alpha} & V_{GS} \geq V_{TH} \quad V_{DS} \geq \theta_1 (V_{GS} - V_{TH})^{\frac{\alpha}{2}} \end{cases}$$

α is the velocity saturation index, $2 \geq \alpha \geq 1$

No longer a square-law model (some term it an α -power or α -law model)

For long devices, $\alpha=2$


Channel length modulation (λ) and bulk effects can be added to the velocity Saturation as well

Degrading of α is not an attractive limitation of the MOSFET

Be aware of existence but of little use !

(too complicated for analytical calculations, not accurate enough for simulations)

Model Errors with Different W/L Values

 

Binning models can improve model accuracy

BSIM Binning Model


- Bin on device sizes
- multiple BSIM models !

```
.MODEL CMOSN NMOS (
+VERSION = 3.1          TNOM    = 27          LEVEL   = 49
+XJ      = 1.5E-7      NCH     = 1.7E17      TOX     = 1.42E-8
+K1      = 0.8976376   K2     = -0.09255    VTH0    = 0.629035
+K3B     = -8.2369696  W0     = 1.041146E-8 K3      = 24.0984767
+DVT0W   = 0          DVT1W  = 0          NLX     = 1E-9
+DVT0    = 2.7123969  DVT1   = 0.4232931  DVT2W   = 0
+U0      = 451.2322004 UA     = 3.091785E-13 DVT2    = -0.1403765
+UC      = 1.22401E-11 VSAT   = 1.715884E5   UB      = 1.702517E-18
+AGS     = 0.130484   B0     = 2.446405E-6 A0      = 0.6580918
+KETA    = -3.043349E-3 A1     = 8.18159E-7  B1      = 5E-6
+RDSW    = 1.367055E3 PRWG   = 0.0328586  A2      = 0.3363058
+WR      = 1          WINT   = 2.443677E-7 PRWB    = 0.0104806
+XL      = 1E-7       XW     = 0          LINT    = 6.999776E-8
+DWB     = 3.676235E-8 VOFF   = -1.493503E-4 DWG     = -1.256454E-8
+CIT     = 0          CDSC   = 2.4E-4      NFACTOR = 1.0354201
+CDSCB   = 0          ETA0   = 2.342963E-3 CDSCD   = 0
+DSUB    = 0.0764123 PCLM   = 2.5941582  ETAB    = -1.5324E-4
+PDIBLC2 = 2.366707E-3 PDIBLCB = -0.0431505  PDIBLC1 = 0.8187825
+PSCBE1  = 6.611774E8 PSCBE2 = 3.238266E-4 DROUT   = 0.9919348
                                     PVAG   = 0
+PRT     = 0          UTE    = -1.5       KT1     = -0.11
+KT1L    = 0          KT2    = 0.022      UA1     = 4.31E-9
+UB1     = -7.61E-18 UC1     = -5.6E-11  AT      = 3.3E4
+WL      = 0          WLN    = 1         WW      = 0
+WWN     = 1          WWL    = 0         LL      = 0
+LLN     = 1          LW     = 0         LWN     = 1
+LWL     = 0          CAPMOD = 2         XPART   = 0.5
+CGDO    = 2.32E-10  CGSO   = 2.32E-10  CGBO    = 1E-9
+CJ      = 4.282017E-4 PB      = 0.9317787 MJ      = 0.4495867
+CJSW    = 3.034055E-10 PBSW   = 0.8       MJSW    = 0.1713852
+CJSWG   = 1.64E-10  PBSWG  = 0.8       MJSWG   = 0.1713852
+CF      = 0          PVTH0  = 0.0520855 PRDSW   = 112.8875816
+PK2     = -0.0289036 WKETA  = -0.0237483 LKETA   = 1.728324E-3
*)
*
```

With 32 bins, this model has 3040 model parameters !

Model Changes with Process Variations

(n-ch characteristics shown)

 

Corner models can improve model accuracy

BSIM Corner Models with Binning

- Often 4 corners in addition to nominal TT, FF, FS, SF, and SS

- bin on device sizes

```
.MODEL CMOSN NMOS (
+VERSION = 3.1          TNOM = 27          TOX = 1.42E-8
+XJ = 1.5E-7           NCH = 1.7E17       VTH0 = 0.629035
+K1 = 0.8976376       K2 = -0.09255      K3 = 24.0984767
+K3B = -8.2369696     W0 = 1.041146E-8    NLX = 1E-9
+DVT0W = 0            DVT1W = 0           DVT2W = 0
+DVT0 = 2.7123969     DVT1 = 0.4232931   DVT2 = -0.1403765
+U0 = 451.2322004     UA = 3.091785E-13  UB = 1.702517E-18
+UC = 1.22401E-11     VSAT = 1.715884E5  A0 = 0.6580918
+AGS = 0.130484       B0 = 2.446405E-6   B1 = 5E-6
+KETA = -3.043349E-3  A1 = 8.18159E-7    A2 = 0.3363058
+RDSW = 1.367055E3    PRWG = 0.0328586   PRWB = 0.0104806
+WR = 1               WINT = 2.443677E-7 LINT = 6.999776E-8
+XL = 1E-7            XW = 0              DWG = -1.256454E-8
+DWB = 3.676235E-8    VOFF = -1.493503E-4 NFACTOR = 1.0354201
+CIT = 0              CDSC = 2.4E-4       CDSCD = 0
+CDSCB = 0            ETA0 = 2.342963E-3 ETAB = -1.5324E-4
+DSUB = 0.0764123     PCIM = 2.5941582    PDIBLC1 = 0.8187825
+PDIBLC2 = 2.366707E-3 PDIBLCB = -0.0431505 DROUT = 0.9919348
+PSCBE1 = 6.611774E8  PSCBE2 = 3.238266E-4 PVAG = 0
+DPR.TA = 0.01        RSH = 83.5         MORMOD = 1
+PRT = 0              UTE = -1.5          KT1 = -0.11
+KT1L = 0             KT2 = 0.022         UA1 = 4.31E-9
+UB1 = -7.61E-18      UC1 = -5.6E-11     AT = 3.3E4
+WL = 0               WLN = 1             WW = 0
+WWN = 1              WWL = 0             LL = 0
+LLN = 1              LW = 0              LWN = 1
+LWL = 0              CAPMOD = 2          XPART = 0.5
+CGDO = 2.32E-10      CGSO = 2.32E-10    CGBO = 1E-9
+CJ = 4.282017E-4     PB = 0.9317787     MJ = 0.4495867
+CJSW = 3.034055E-10  PBSW = 0.8          MJSW = 0.1713852
+CJSWG = 1.64E-10     PBSWG = 0.8         MJSWG = 0.1713852
+CF = 0               PVTH0 = 0.0520855  PRDSW = 112.8875816
+PK2 = -0.0289036     WKETA = -0.0237483 LKETA = 1.728324E-3 )
*
```

With 32 size bins and 4 corners, this model has 15,200 model parameters !

How many models of the MOSFET do we have?

Switch-level model (2)

Square-law model

Square-law model (with λ and bulk additions)



α -law model (with λ and bulk additions)

BSIM model

BSIM model (with binning extensions)

BSIM model (with binning extensions and process corners)

The Modeling Challenge

  


$$I_D = f_1(V_{GS}, V_{DS})$$

$$I_G = f_2(V_{GS}, V_{DS})$$

$$I_B = f_3(V_{GS}, V_{DS})$$

Difficult to obtain analytical functions that accurately fit actual devices over bias, size, and process variations


Model Status

 

In the next few slides, the models we have developed will be listed and reviewed

- Square-law Model
- Switch-level Models
- Extended Square-law model
- Short-channel model
- BSIM Model
- BSIM Binning Model
- Corner Models

Square-Law Model


 


$$I_D = \begin{cases} 0 & V_{GS} \leq V_{TH} \\ \mu C_{OX} \frac{W}{L} \left(V_{GS} - V_{TH} - \frac{V_{DS}}{2} \right) V_{DS} & V_{GS} \geq V_{TH} \quad V_{DS} < V_{GS} - V_{TH} \\ \mu C_{OX} \frac{W}{2L} (V_{GS} - V_{TH})^2 & V_{GS} \geq V_{TH} \quad V_{DS} \geq V_{GS} - V_{TH} \end{cases}$$

Model Parameters : $\{\mu, C_{OX}, V_{TH0}\}$

Design Parameters : $\{W, L\}$ but only one degree of freedom W/L

Switch-Level Models

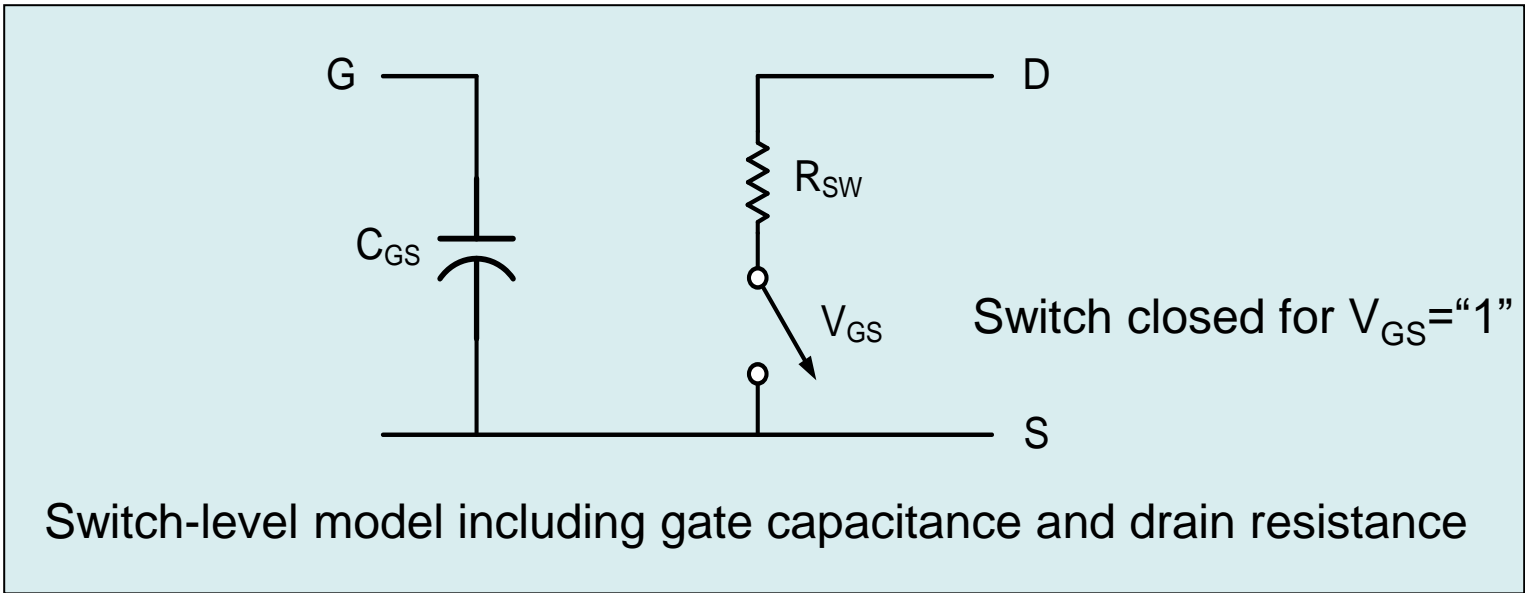 

C_{GS} and R_{SW} dependent upon device sizes and process

For minimum-sized devices in a 0.5u process

$$C_{GS} \cong 1.5\text{fF} \quad R_{sw} \cong \left. \begin{array}{l} 2\text{K}\Omega \text{ n-channel} \\ 6\text{K}\Omega \text{ p-channel} \end{array} \right\}$$


Considerable emphasis will be placed upon device sizing to manage C_{GS} and R_{SW}

Model Parameters : $\{C_{GS}, R_{SW}\}$

Extended Square-Law Model

$$I_G = 0$$

$$I_B = 0$$

 

$$I_D = \begin{cases} 0 & V_{GS} \leq V_{TH} \\ \mu C_{OX} \frac{W}{L} \left(V_{GS} - V_{TH} - \frac{V_{DS}}{2} \right) V_{DS} & V_{GS} \geq V_{TH} \quad V_{DS} < V_{GS} - V_{TH} \\ \mu C_{OX} \frac{W}{2L} (V_{GS} - V_{TH})^2 \cdot (1 + \lambda V_{DS}) & V_{GS} \geq V_{TH} \quad V_{DS} \geq V_{GS} - V_{TH} \end{cases}$$

$$V_{TH} = V_{TH0} + \gamma \left(\sqrt{\phi - V_{BS}} - \sqrt{\phi} \right)$$

Model Parameters : $\{\mu, C_{OX}, V_{TH0}, \phi, \gamma, \lambda\}$

Design Parameters : $\{W, L\}$ but only one degree of freedom W/L

Short-Channel Model

$$I_D = \begin{cases} 0 & V_{GS} \leq V_{TH} \\ \frac{\theta_2}{\theta_1} \mu C_{OX} \frac{W}{L} (V_{GS} - V_{TH})^{\frac{\alpha}{2}} V_{DS} & V_{GS} \geq V_{TH} \quad V_{DS} < \theta_1 (V_{GS} - V_{TH})^{\frac{\alpha}{2}} \\ \theta_2 \mu C_{OX} \frac{W}{L} (V_{GS} - V_{TH})^{\alpha} & V_{GS} \geq V_{TH} \quad V_{DS} \geq \theta_1 (V_{GS} - V_{TH})^{\frac{\alpha}{2}} \end{cases}$$

α is the velocity saturation index, $2 \geq \alpha \geq 1$

Channel length modulation (λ) and bulk effects can be added to the velocity Saturation as well

BSIM model

```
.MODEL CMOSN NMOS (
+VERSION = 3.1          TNOM    = 27          TOX      = 1.42E-8
+XJ      = 1.5E-7       NCH     = 1.7E17       VTH0     = 0.629035
+K1      = 0.8976376    K2     = -0.09255    K3       = 24.0984767
+K3B     = -8.2369696   W0     = 1.041146E-8 NLX      = 1E-9
+DVT0W   = 0           DVT1W  = 0           DVT2W    = 0
+DVT0    = 2.7123969   DVT1   = 0.4232931  DVT2     = -0.1403765
+U0      = 451.2322004 UA     = 3.091785E-13 UB       = 1.702517E-18
+UC      = 1.22401E-11 VSAT    = 1.715884E5  A0       = 0.6580918
+AGS     = 0.130484    B0     = 2.446405E-6 B1       = 5E-6
+KETA    = -3.043349E-3 A1     = 8.18159E-7  A2       = 0.3363058
+RDSW    = 1.367055E3  PRWG    = 0.0328586  PRWB     = 0.0104806
+WR      = 1           WINT    = 2.443677E-7 LINT     = 6.999776E-8
+XL      = 1E-7        XW      = 0           DWG      = -1.256454E-8
+DWB     = 3.676235E-8 VOFF    = -1.493503E-4 NFACTOR  = 1.0354201
+CIT      = 0          CDSC    = 2.4E-4      CDSCD    = 0
+CDSCB   = 0          ETA0    = 2.342963E-3  ETAB     = -1.5324E-4
+DSUB    = 0.0764123  PCLM    = 2.5941582  PDIBLC1  = 0.8187825
+PDIBLC2 = 2.366707E-3 PDIBLCB = -0.0431505  DROUT    = 0.9919348
+PSCBE1  = 6.611774E8 PSCBE2  = 3.238266E-4 PVAG     = 0

+PRT     = 0          UTE     = -1.5        KT1      = -0.11
+KT1L    = 0          KT2     = 0.022       UA1      = 4.31E-9
+UB1     = -7.61E-18 UC1     = -5.6E-11    AT       = 3.3E4
+WL      = 0          WLN     = 1           WW       = 0
+WWN     = 1          WWL     = 0           LL       = 0
+LLN     = 1          LW      = 0           LWN     = 1
+LWL     = 0          CAPMOD  = 2           XPART    = 0.5
+CGDO    = 2.32E-10  CGSO    = 2.32E-10  CGBO     = 1E-9
+CJ      = 4.282017E-4 PB       = 0.9317787  MJ       = 0.4495867
+CJSW    = 3.034055E-10 PBSW    = 0.8         MJSW    = 0.1713852
+CJSWG   = 1.64E-10  PBSWG   = 0.8         MJSWG   = 0.1713852
+CF      = 0          PVTH0   = 0.0520855  PRDSW    = 112.8875816
+PK2     = -0.0289036 WKETA   = -0.0237483  LKETA    = 1.728324E-3 )
*
```

Note this model has 95 model parameters !

BSIM Binning Model

- Bin on device sizes
- multiple BSIM models !

```
.MODEL CMOSN NMOS (
+VERSION = 3.1          TNOM    = 27          LEVEL   = 49
+XJ      = 1.5E-7      NCH     = 1.7E17      TOX     = 1.42E-8
+K1      = 0.8976376   K2     = -0.09255    VTH0    = 0.629035
+K3B     = -8.2369696  W0     = 1.041146E-8 K3      = 24.0984767
+DVT0W   = 0          DVT1W  = 0          NLX     = 1E-9
+DVT0    = 2.7123969  DVT1   = 0.4232931  DVT2W   = 0
+U0      = 451.2322004 UA     = 3.091785E-13 DVT2    = -0.1403765
+UC      = 1.22401E-11 VSAT   = 1.715884E5   UB      = 1.702517E-18
+AGS     = 0.130484   B0     = 2.446405E-6 A0      = 0.6580918
+KETA    = -3.043349E-3 A1     = 8.18159E-7  B1      = 5E-6
+RDSW    = 1.367055E3 PRWG   = 0.0328586  A2      = 0.3363058
+WR      = 1          WINT   = 2.443677E-7 PRWB    = 0.0104806
+XL      = 1E-7       XW     = 0          LINT    = 6.999776E-8
+DWB     = 3.676235E-8 VOFF   = -1.493503E-4 DWG     = -1.256454E-8
+CIT     = 0          CDSC   = 2.4E-4      NFACTOR = 1.0354201
+CDSCB   = 0          ETA0   = 2.342963E-3 CDSCD   = 0
+DSUB    = 0.0764123 PCLM   = 2.5941582  ETAB    = -1.5324E-4
+PDIBLC2 = 2.366707E-3 PDIBLCB = -0.0431505  PDIBLC1 = 0.8187825
+PSCBE1  = 6.611774E8 PSCBE2 = 3.238266E-4 DROUT   = 0.9919348
                                     PVAG   = 0
+PRT     = 0          UTE    = -1.5       KT1     = -0.11
+KT1L    = 0          KT2    = 0.022      UA1     = 4.31E-9
+UB1     = -7.61E-18 UC1    = -5.6E-11  AT      = 3.3E4
+WL      = 0          WLN    = 1         WW      = 0
+WWN     = 1          WWL    = 0         LL      = 0
+LLN     = 1          LW     = 0         LWN    = 1
+LWL     = 0          CAPMOD = 2         XPART   = 0.5
+CGDO    = 2.32E-10  CGSO   = 2.32E-10  CGBO    = 1E-9
+CJ      = 4.282017E-4 PB      = 0.9317787 MJ      = 0.4495867
+CJSW    = 3.034055E-10 PBSW   = 0.8       MJSW    = 0.1713852
+CJSWG   = 1.64E-10  PBSWG  = 0.8       MJSWG   = 0.1713852
+CF      = 0          PVTH0  = 0.0520855 PRDSW   = 112.8875816
+PK2     = -0.0289036 WKETA  = -0.0237483 LKETA   = 1.728324E-3
*)
*
```

With 32 bins, this model has 3040 model parameters !

BSIM Corner Models


- Often 4 corners in addition to nominal TT, FF, FS, SF, and SS
 - five different BSIM models !

```
.MODEL CMOSN NMOS (
+VERSION = 3.1          TNOM    = 27          TOX      = 1.42E-8
+XJ      = 1.5E-7       NCH     = 1.7E17       VTH0     = 0.629035
+K1      = 0.8976376    K2     = -0.09255      K3       = 24.0984767
+K3B     = -8.2369696   W0     = 1.041146E-8  NLX      = 1E-9
+DVT0W   = 0           DVT1W  = 0           DVT2W    = 0
+DVT0    = 2.7123969   DVT1   = 0.4232931   DVT2     = -0.1403765
+U0      = 451.2322004  UA     = 3.091785E-13  UB       = 1.702517E-18
+UC      = 1.22401E-11  VSAT   = 1.715884E5   A0       = 0.6580918
+AGS     = 0.130484    B0     = 2.446405E-6   B1       = 5E-6
+KETA    = -3.043349E-3 A1     = 8.18159E-7    A2       = 0.3363058
+RDSW    = 1.367055E3  PRWG   = 0.0328586    PRWB     = 0.0104806
+WR      = 1           WINT   = 2.443677E-7  LINT     = 6.999776E-8
+XL      = 1E-7        XW     = 0           DWG      = -1.256454E-8
+DWB     = 3.676235E-8  VOFF   = -1.493503E-4  NFACTOR  = 1.0354201
+CIT     = 0           CDSC   = 2.4E-4        CDSCD    = 0
+CDSCB   = 0           ETA0   = 2.342963E-3    ETAB     = -1.5324E-4
+DSUB    = 0.0764123   PCLM   = 2.5941582    PDIBLC1  = 0.8187825
+PDIBLC2 = 2.366707E-3 PDIBLCB = -0.0431505    DROUT    = 0.9919348
+PSCBE1  = 6.611774E8  PSCBE2 = 3.238266E-4  PVAG     = 0
+DRIFTA  = 0.01        RSH    = 83.5         MORMOD   = 1
+PRT     = 0           UTE    = -1.5         KT1      = -0.11
+KT1L    = 0           KT2    = 0.022        UA1      = 4.31E-9
+UB1     = -7.61E-18   UC1    = -5.6E-11     AT       = 3.3E4
+WL      = 0           WLN    = 1           WW       = 0
+WWN     = 1           WWL    = 0           LL       = 0
+LLN     = 1           LW     = 0           LWN     = 1
+LWL     = 0           CAPMOD = 2           XPART    = 0.5
+CGDO    = 2.32E-10    CGSO   = 2.32E-10    CGBO     = 1E-9
+CJ      = 4.282017E-4  PB     = 0.9317787    MJ       = 0.4495867
+CJSW    = 3.034055E-10 PBSW   = 0.8           MJSW    = 0.1713852
+CJSWG   = 1.64E-10   PBSWG  = 0.8           MJSWG   = 0.1713852
+CF      = 0           PVTH0  = 0.0520855    PRDSW   = 112.8875816
+PK2     = -0.0289036  WKETA  = -0.0237483   LKETA    = 1.728324E-3
*)
```


TT: typical-typical
FF: fast n, fast p
FS: fast n, slow p
SF: slow n, fast p
SS: slow n, slow p

With 4 corners, this model has 475 model parameters !

Hierarchical Model Comparisons

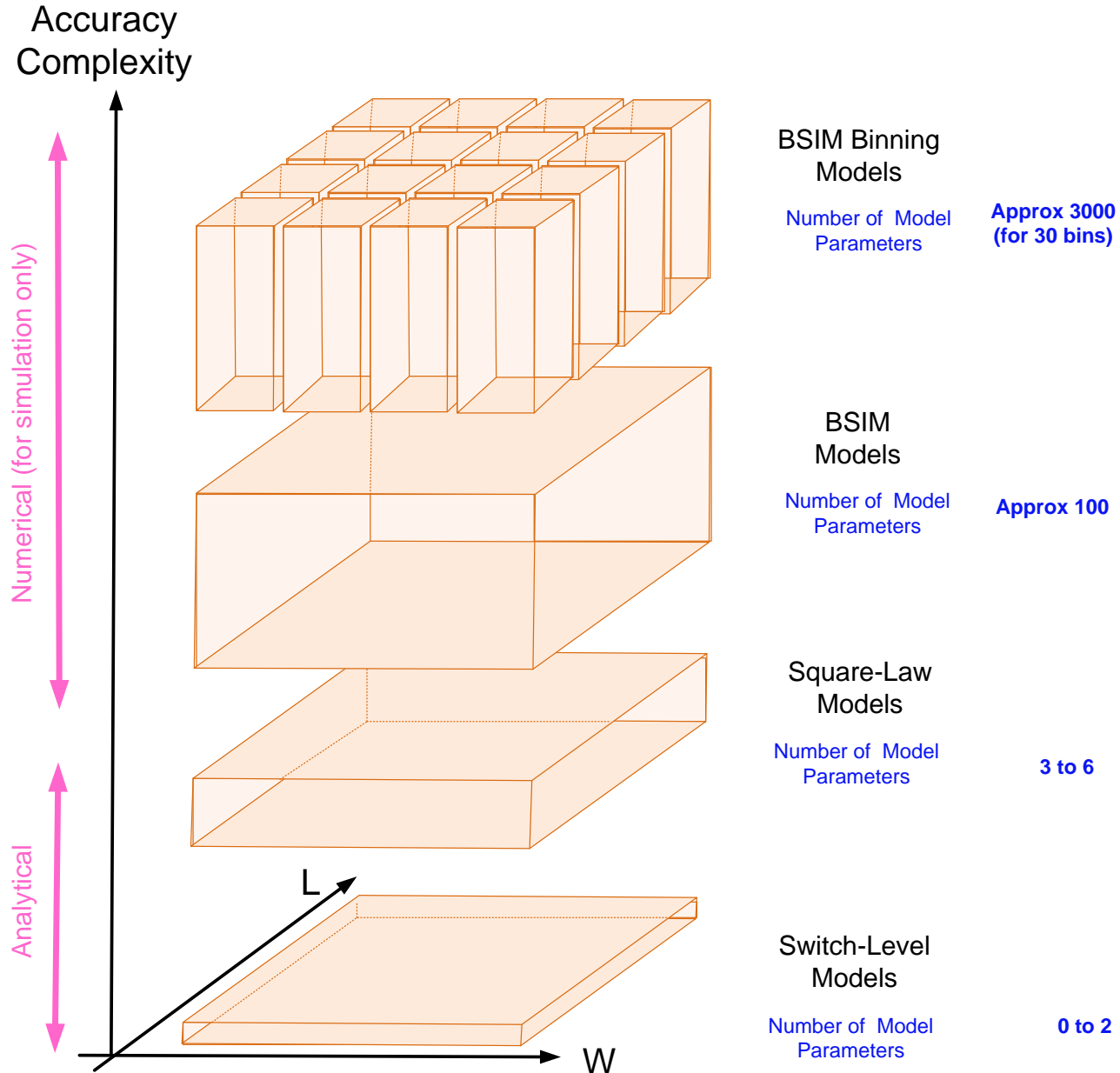

Corner Models

 

Applicable at any level in model hierarchy (same model, different parameters)

Often 4 corners (FF, FS, SF, SS) used but sometimes many more

Designers must provide enough robustness so good yield at all corners



Stay Safe and Stay Healthy !

End of Lecture 17