

# EE 330


## Lecture 22

- Bipolar Transistor Challenges
- Amplifiers
- Small Signal Analysis


# Fall 2023 Exam Schedule

Exam 1	Friday Sept 22	
Exam 2	Friday Oct 20	
Exam 3	Friday Nov. 17	
Final	Monday Dec 11	12:00 – 2:00 p.m.

Review from Last Lecture


 


# Review from Last Lecture

 

**B-B' Section**

# The vertical npn transistor

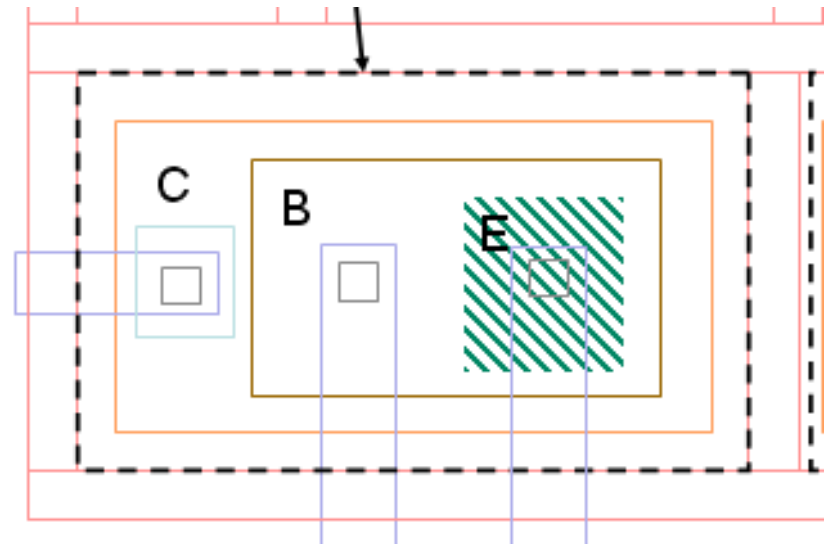 

- Emitter area only geometric parameter that appears in basic device model !
- B and C areas large to get top contact to these regions
- Transistor much larger than emitter
- Multiple-emitter devices often used (TTL Logic) and don't significantly increase area
- Multiple B and C contacts often used (and multiple E contacts as well if  $A_E$  large)

# Quirks in modeling the BJT

<sup>a</sup> Parameters are defined in Chapters 3 and 4.



<sup>b</sup> Some of these Gummel-Poon parameters differ considerably from those given in Table 2C.4. They have been obtained from curve fitting and should give good results with computer simulations. The parameters of Table 2C.4 should be used for hand analysis.

<sup>c</sup> Parameters that are strongly area-dependent are based upon an npn emitter area of 390  $\mu^2$  and perimeter of 80  $\mu$ , a base area of 2200  $\mu^2$  and perimeter of 200  $\mu$ , and a collector area of 10,500  $\mu^2$  and perimeter of 425  $\mu$ . The lateral pnp has rectangular collectors and emitters spaced 10  $\mu$  apart with areas of 230  $\mu^2$  and perimeters of 60  $\mu$ . The base area of the pnp is 7400  $\mu^2$  and the base perimeter is 345  $\mu$ .

<sup>d</sup> CJS is set to zero for the lateral transistor because it is essentially nonexistent. The parasitic capacitance from base to substrate, which totals 1.0 pF for this device, must be added externally to the BJT.

- In contrast to the MOSFET where process parameters are independent of geometry, the bipolar transistor model is for a specific transistor !
- Area emitter factor is used to model other devices
- Often multiple specific device models are given and these devices are used directly
- Often designer can not arbitrarily set  $A_E$  but rather must use parallel combinations of specific devices and layouts


# A challenge in modeling the BJT

  

$$I_C = \sum_{i=1}^7 \frac{A_E}{7} J_S e^{\frac{V_{BE}}{V_t}} = A_E J_S e^{\frac{V_{BE}}{V_t}}$$

This looks consistent but ...

consider an individual slice

 


Lateral flow of base current causes a drop in base voltage across the base region

$$V_{BRk} \neq V_{BLk} \quad I_{Ck} = \frac{A_E}{7} J_S e^{\frac{V_{BEk}}{V_t}}$$


What is  $V_{BEk}$ ?

# A challenge in modeling the BJT

 

$$I_C = \sum_{i=1}^7 \frac{A_E}{7} J_S e^{\frac{V_{BE}}{V_t}} = A_E J_S e^{\frac{V_{BE}}{V_t}}$$

This looks consistent but ...

 


- Lateral flow of base current causes a drop in base voltage across the base region
- And that drop differs from one slice to the next
- So  $V_{BE}$  is not fixed across the slices
- Since current is exponentially related to  $V_{BE}$ , effects can be significant
- Termed **base spreading resistance** problem
- Causes “**Current Crowding**”
- Base resistance and base spreading resistance both exist and represent different phenomenon
- Strongly dependent upon layout and contact placement
- No good models to include this effect
- Major reason designer does not have control of transistor layout detail in some bipolar processes
- Similar issue does not exist in MOSFET because the corresponding gate voltage does not change with position since  $I_G=0$



# A challenge in modeling the BJT

What can be done about this problem ?

Top View of Vertical npn

 

- Often double rows of contacts used
- Area overhead can be significant
- Effects can be reduced but current flow paths are irregular

# MOS and Bipolar Area Comparisons

How does the area required to realize a MOSFET compare to that required to realize a BJT?

 
**Will consider a minimum-sized device in both processes**

**TABLE 2C.2**  
**Design rules for a typical bipolar process ( $\lambda = 2.5 \mu$ )**  
**(See Table 2C.3 in color plates for graphical interpretation)**

	<b>Dimension</b>
1. $n^+$ buried collector diffusion (Yellow, Mask #1)	
1.1 Width	$3\lambda$
1.2 Overlap of p-base diffusion (for vertical npn)	$2\lambda$
1.3 Overlap of $n^+$ emitter diffusion (for collector contact of vertical npn)	$2\lambda$
1.4 Overlap of p-base diffusion (for collector and emitter of lateral pnp)	$2\lambda$
1.5 Overlap of $n^+$ emitter diffusion (for base contact of lateral pnp)	$2\lambda$
2. Isolation diffusion (Orange, Mask #2)	
2.1 Width	$4\lambda$
2.2 Spacing	$24\lambda$
2.3 Distance to $n^+$ buried collector	$14\lambda$
3. p-base diffusion (Brown, Mask #3)	
3.1 Width	$3\lambda$
3.2 Spacing	$5\lambda$
3.3 Distance to isolation diffusion	$14\lambda$
3.4 Width (resistor)	$3\lambda$
3.5 Spacing (as resistor)	$3\lambda$
4. $n^+$ emitter diffusion (Green, Mask #4)	
4.1 Width	$3\lambda$
4.2 Spacing	$3\lambda$
4.3 p-base diffusion overlap of $n^+$ emitter diffusion (emitter in base)	$2\lambda$
4.4 Spacing to isolation diffusion (for collector contact)	$12\lambda$
4.5 Spacing to p-base diffusion (for base contact of lateral pnp)	$6\lambda$
4.6 Spacing to p-base diffusion (for collector contact of vertical npn)	$6\lambda$

5. Contact (Black, Mask #5)	
5.1 Size (exactly)	$4\lambda \times 4\lambda$
5.2 Spacing	$2\lambda$
5.3 Metal overlap of contact	$\lambda$
5.4 $n^+$ emitter diffusion overlap of contact	$2\lambda$
5.5 p-base diffusion overlap of contact	$2\lambda$
5.6 p-base to $n^+$ emitter	$3\lambda$
5.7 Spacing to isolation diffusion	$4\lambda$
6. Metalization (Blue, Mask #6)	
6.1 Width	$2\lambda$
6.2 Spacing	$2\lambda$
6.3 Bonding pad size	$100 \mu \times 100 \mu$
6.4 Probe pad size	$75 \mu \times 75 \mu$
6.5 Bonding pad separation	$50 \mu$
6.6 Bonding to probe pad	$30 \mu$
6.7 Probe pad separation	$30 \mu$
6.8 Pad to circuitry	$40 \mu$
6.9 Maximum current density	$0.8 \text{ mA}/\mu \text{ width}$
7. Passivation (Purple, Mask #7)	
7.1 Minimum bonding pad opening	$90 \mu \times 90 \mu$
7.2 Minimum probe pad opening	$65 \mu \times 65 \mu$

Consider Initially the Emitter in the BJT surrounded by a base region

 


**TABLE 2C.2**  
**Design rules for a typical bipolar process ( $\lambda = 2.5 \mu$ )**  
**(See Table 2C.3 in color plates for graphical interpretation)**

	<b>Dimension</b>
1. $n^+$ buried collector diffusion (Yellow, Mask #1)	
1.1 Width	$3\lambda$
1.2 Overlap of p-base diffusion (for vertical npn)	$2\lambda$
1.3 Overlap of $n^+$ emitter diffusion (for collector contact of vertical npn)	$2\lambda$
1.4 Overlap of p-base diffusion (for collector and emitter of lateral pnp)	$2\lambda$
1.5 Overlap of $n^+$ emitter diffusion (for base contact of lateral pnp)	$2\lambda$
2. Isolation diffusion (Orange, Mask #2)	
2.1 Width	$4\lambda$
2.2 Spacing	$24\lambda$
2.3 Distance to $n^+$ buried collector	$14\lambda$
3. p-base diffusion (Brown, Mask #3)	
3.1 Width	$3\lambda$
3.2 Spacing	$5\lambda$
3.3 Distance to isolation diffusion	$14\lambda$
3.4 Width (resistor)	$3\lambda$
3.5 Spacing (as resistor)	$3\lambda$
4. $n^+$ emitter diffusion (Green, Mask #4)	
4.1 Width	$3\lambda$
4.2 Spacing	$3\lambda$
4.3 p-base diffusion overlap of $n^+$ emitter diffusion (emitter in base)	$2\lambda$
4.4 Spacing to isolation diffusion (for collector contact)	$12\lambda$
4.5 Spacing to p-base diffusion (for base contact of lateral pnp)	$6\lambda$
4.6 Spacing to p-base diffusion (for collector contact of vertical npn)	$6\lambda$

5. Contact (Black, Mask #5)	
5.1 Size (exactly)	$4\lambda \times 4\lambda$
5.2 Spacing	$2\lambda$
5.3 Metal overlap of contact	$\lambda$
5.4 $n^+$ emitter diffusion overlap of contact	$2\lambda$
5.5 p-base diffusion overlap of contact	$2\lambda$
5.6 p-base to $n^+$ emitter	$3\lambda$
5.7 Spacing to isolation diffusion	$4\lambda$
6. Metalization (Blue, Mask #6)	
6.1 Width	$2\lambda$
6.2 Spacing	$2\lambda$
6.3 Bonding pad size	$100 \mu \times 100 \mu$
6.4 Probe pad size	$75 \mu \times 75 \mu$
6.5 Bonding pad separation	$50 \mu$
6.6 Bonding to probe pad	$30 \mu$
6.7 Probe pad separation	$30 \mu$
6.8 Pad to circuitry	$40 \mu$
6.9 Maximum current density	$0.8 \text{ mA}/\mu \text{ width}$
7. Passivation (Purple, Mask #7)	
7.1 Minimum bonding pad opening	$90 \mu \times 90 \mu$
7.2 Minimum probe pad opening	$65 \mu \times 65 \mu$

From design rules (left to right) 4.3, 5.1, 5.4, 5.6, 5.5

 




**TABLE 2C.2**  
**Design rules for a typical bipolar process ( $\lambda = 2.5 \mu$ )**  
**(See Table 2C.3 in color plates for graphical interpretation)**

	Dimension
1. $n^+$ buried collector diffusion (Yellow, Mask #1)	
1.1 Width	$3\lambda$
1.2 Overlap of p-base diffusion (for vertical npn)	$2\lambda$
1.3 Overlap of $n^+$ emitter diffusion (for collector contact of vertical npn)	$2\lambda$
1.4 Overlap of p-base diffusion (for collector and emitter of lateral pnp)	$2\lambda$
1.5 Overlap of $n^+$ emitter diffusion (for base contact of lateral pnp)	$2\lambda$
2. Isolation diffusion (Orange, Mask #2)	
2.1 Width	$4\lambda$
2.2 Spacing	$24\lambda$
2.3 Distance to $n^+$ buried collector	$14\lambda$
3. p-base diffusion (Brown, Mask #3)	
3.1 Width	$3\lambda$
3.2 Spacing	$5\lambda$
3.3 Distance to isolation diffusion	$14\lambda$
3.4 Width (resistor)	$3\lambda$
3.5 Spacing (as resistor)	$3\lambda$
4. $n^+$ emitter diffusion (Green, Mask #4)	
4.1 Width	$3\lambda$
4.2 Spacing	$3\lambda$
4.3 p-base diffusion overlap of $n^+$ emitter diffusion (emitter in base)	$2\lambda$
4.4 Spacing to isolation diffusion (for collector contact)	$12\lambda$
4.5 Spacing to p-base diffusion (for base contact of lateral pnp)	$6\lambda$
4.6 Spacing to p-base diffusion (for collector contact of vertical npn)	$6\lambda$

Add n+ buried for collector  
From design rule 1.2

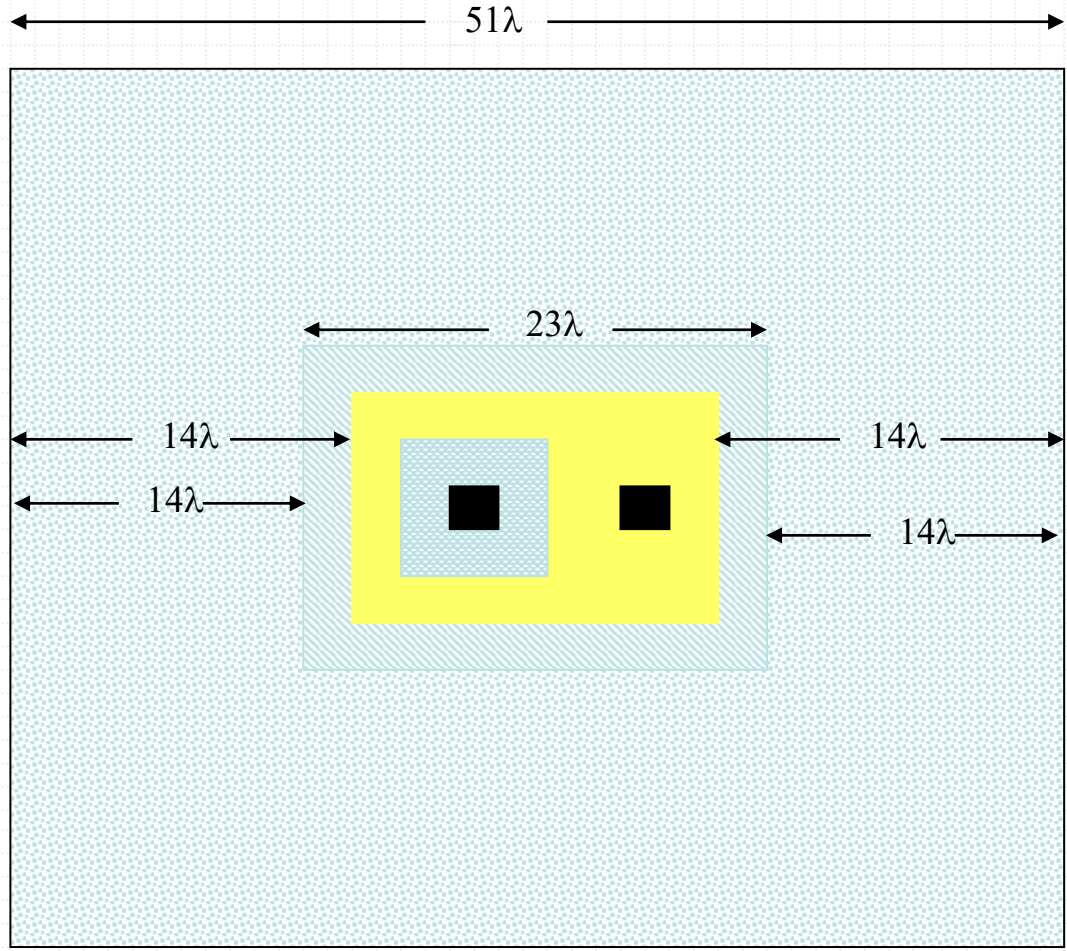


**TABLE 2C.2**  
**Design rules for a typical bipolar process ( $\lambda = 2.5 \mu$ )**  
**(See Table 2C.3 in color plates for graphical interpretation)**

	<b>Dimension</b>
1. $n^+$ buried collector diffusion (Yellow, Mask #1)	
1.1 Width	$3\lambda$
1.2 Overlap of p-base diffusion (for vertical npn)	$2\lambda$
1.3 Overlap of $n^+$ emitter diffusion (for collector contact of vertical npn)	$2\lambda$
1.4 Overlap of p-base diffusion (for collector and emitter of lateral pnp)	$2\lambda$
1.5 Overlap of $n^+$ emitter diffusion (for base contact of lateral pnp)	$2\lambda$
2. Isolation diffusion (Orange, Mask #2)	
2.1 Width	$4\lambda$
2.2 Spacing	$24\lambda$
2.3 Distance to $n^+$ buried collector	$14\lambda$
3. p-base diffusion (Brown, Mask #3)	
3.1 Width	$3\lambda$
3.2 Spacing	$5\lambda$
3.3 Distance to isolation diffusion	$14\lambda$
3.4 Width (resistor)	$3\lambda$
3.5 Spacing (as resistor)	$3\lambda$
4. $n^+$ emitter diffusion (Green, Mask #4)	
4.1 Width	$3\lambda$
4.2 Spacing	$3\lambda$
4.3 p-base diffusion overlap of $n^+$ emitter diffusion (emitter in base)	$2\lambda$
4.4 Spacing to isolation diffusion (for collector contact)	$12\lambda$
4.5 Spacing to p-base diffusion (for base contact of lateral pnp)	$6\lambda$
4.6 Spacing to p-base diffusion (for collector contact of vertical npn)	$6\lambda$

1 5 10 15 20 25 30 35 40 45 50 55 60 65 70 75

# Add n-epi region from design rules 2.3 and 3.3




5. Contact (Black, Mask #5)	
5.1 Size (exactly)	4λ × 4λ
5.2 Spacing	2λ
5.3 Metal overlap of contact	λ
5.4 n <sup>+</sup> emitter diffusion overlap of contact	2λ
5.5 p-base diffusion overlap of contact	2λ
5.6 p-base to n <sup>+</sup> emitter	3λ
5.7 Spacing to isolation diffusion	4λ
6. Metalization (Blue, Mask #6)	
6.1 Width	2λ
6.2 Spacing	2λ
6.3 Bonding pad size	100 μ × 100 μ
6.4 Probe pad size	75 μ × 75 μ
6.5 Bonding pad separation	50 μ
6.6 Bonding to probe pad	30 μ
6.7 Probe pad separation	30 μ
6.8 Pad to circuitry	40 μ
6.9 Maximum current density	0.8 mA/μ width
7. Passivation (Purple, Mask #7)	
7.1 Minimum bonding pad opening	90 μ × 90 μ
7.2 Minimum probe pad opening	65 μ × 65 μ
 
# Add contact to n-epi region from design rules 2.3 and 3.3

1 5 10 15 20 25 30 35 40 45 50 55 60 65 70 75

5  
10  
15  
20  
25  
30  
35  
40  
45  
50  
55



Should extend the buried collector to under the collector contact !

**TABLE 2C.2**  
**Design rules for a typical bipolar process ( $\lambda = 2.5 \mu$ )**  
**(See Table 2C.3 in color plates for graphical interpretation)**


	<b>Dimension</b>
1. $n^+$ buried collector diffusion (Yellow, Mask #1)	
1.1 Width	$3\lambda$
1.2 Overlap of p-base diffusion (for vertical npn)	$2\lambda$
1.3 Overlap of $n^+$ emitter diffusion (for collector contact of vertical npn)	$2\lambda$
1.4 Overlap of p-base diffusion (for collector and emitter of lateral pnp)	$2\lambda$
1.5 Overlap of $n^+$ emitter diffusion (for base contact of lateral pnp)	$2\lambda$
2. Isolation diffusion (Orange, Mask #2)	
2.1 Width	$4\lambda$
2.2 Spacing	$24\lambda$
2.3 Distance to $n^+$ buried collector	$14\lambda$
3. p-base diffusion (Brown, Mask #3)	
3.1 Width	$3\lambda$
3.2 Spacing	$5\lambda$
3.3 Distance to isolation diffusion	$14\lambda$
3.4 Width (resistor)	$3\lambda$
3.5 Spacing (as resistor)	$3\lambda$
4. $n^+$ emitter diffusion (Green, Mask #4)	
4.1 Width	$3\lambda$
4.2 Spacing	$3\lambda$
4.3 p-base diffusion overlap of $n^+$ emitter diffusion (emitter in base)	$2\lambda$
4.4 Spacing to isolation diffusion (for collector contact)	$12\lambda$
4.5 Spacing to p-base diffusion (for base contact of lateral pnp)	$6\lambda$
4.6 Spacing to p-base diffusion (for collector contact of vertical npn)	$6\lambda$

5. Contact (Black, Mask #5)	
5.1 Size (exactly)	4λ × 4λ
5.2 Spacing	2λ
5.3 Metal overlap of contact	λ
5.4 n <sup>+</sup> emitter diffusion overlap of contact	2λ
5.5 p-base diffusion overlap of contact	2λ
5.6 p-base to n <sup>+</sup> emitter	3λ
5.7 Spacing to isolation diffusion	4λ
6. Metalization (Blue, Mask #6)	
6.1 Width	2λ
6.2 Spacing	2λ
6.3 Bonding pad size	100 μ × 100 μ
6.4 Probe pad size	75 μ × 75 μ
6.5 Bonding pad separation	50 μ
6.6 Bonding to probe pad	30 μ
6.7 Probe pad separation	30 μ
6.8 Pad to circuitry	40 μ
6.9 Maximum current density	0.8 mA/μ width
7. Passivation (Purple, Mask #7)	
7.1 Minimum bonding pad opening	90 μ × 90 μ
7.2 Minimum probe pad opening	65 μ × 65 μ




1 5 10 15 20 25 30 35 40 45 50 55 60 65 70 75  
But, there are some rather strict rules relating to the epi contact

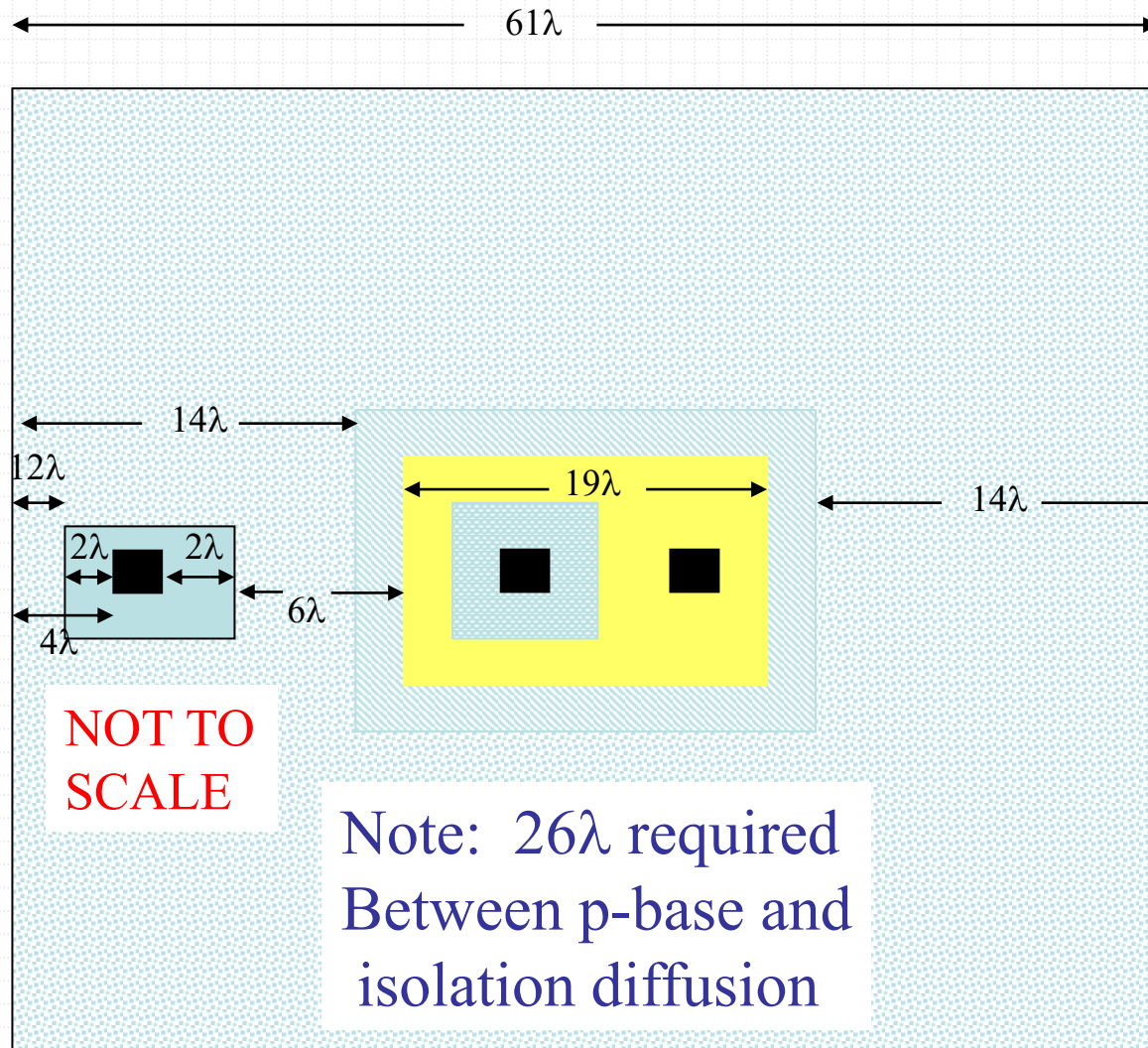
5 from (left to right) rules 4.4, 5.4, 4.6




Should extend the buried collector to under the collector contact !

 Consider a structure with a collector contact on both sides of epi




 

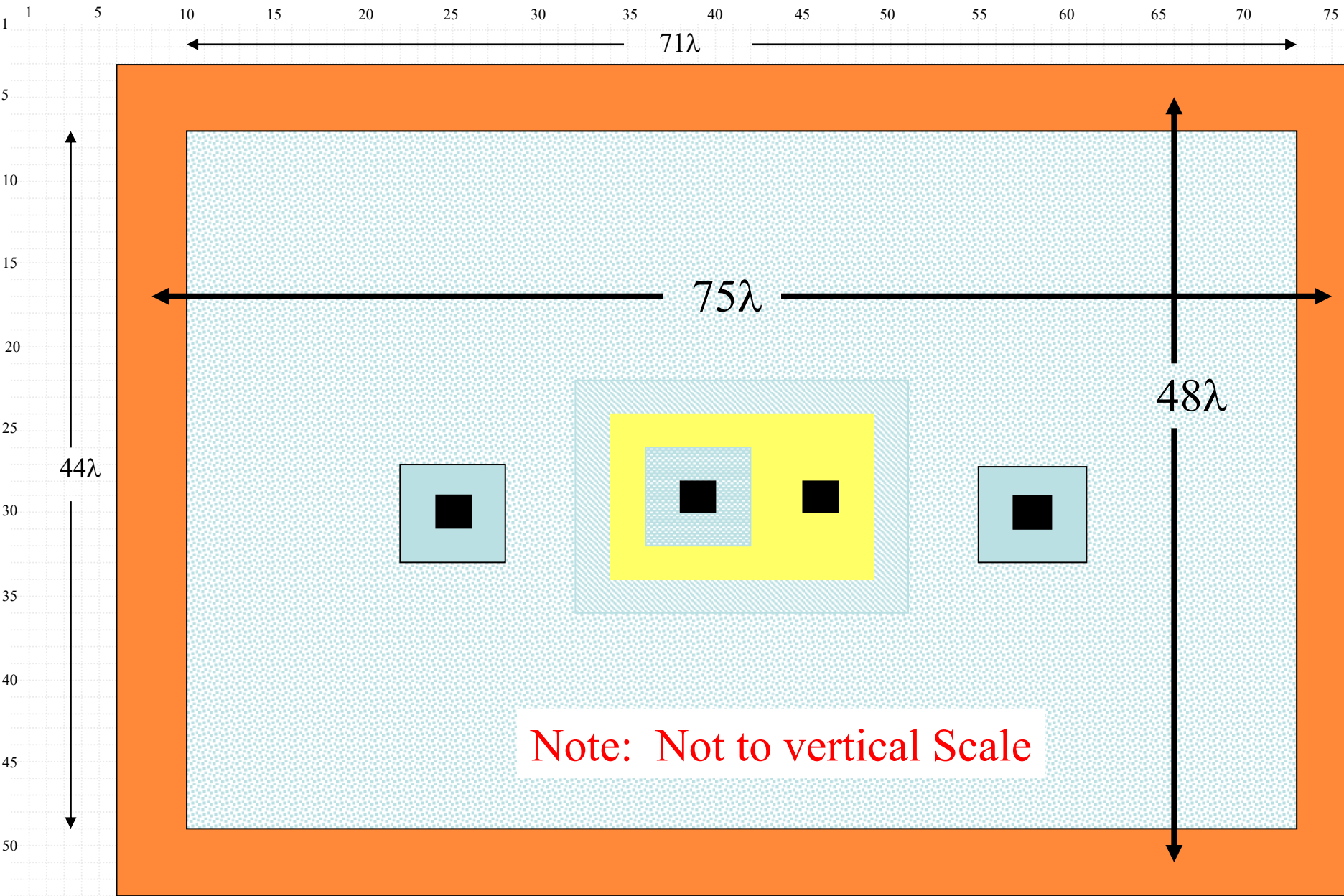Should extend the buried collector to under the collector contact !




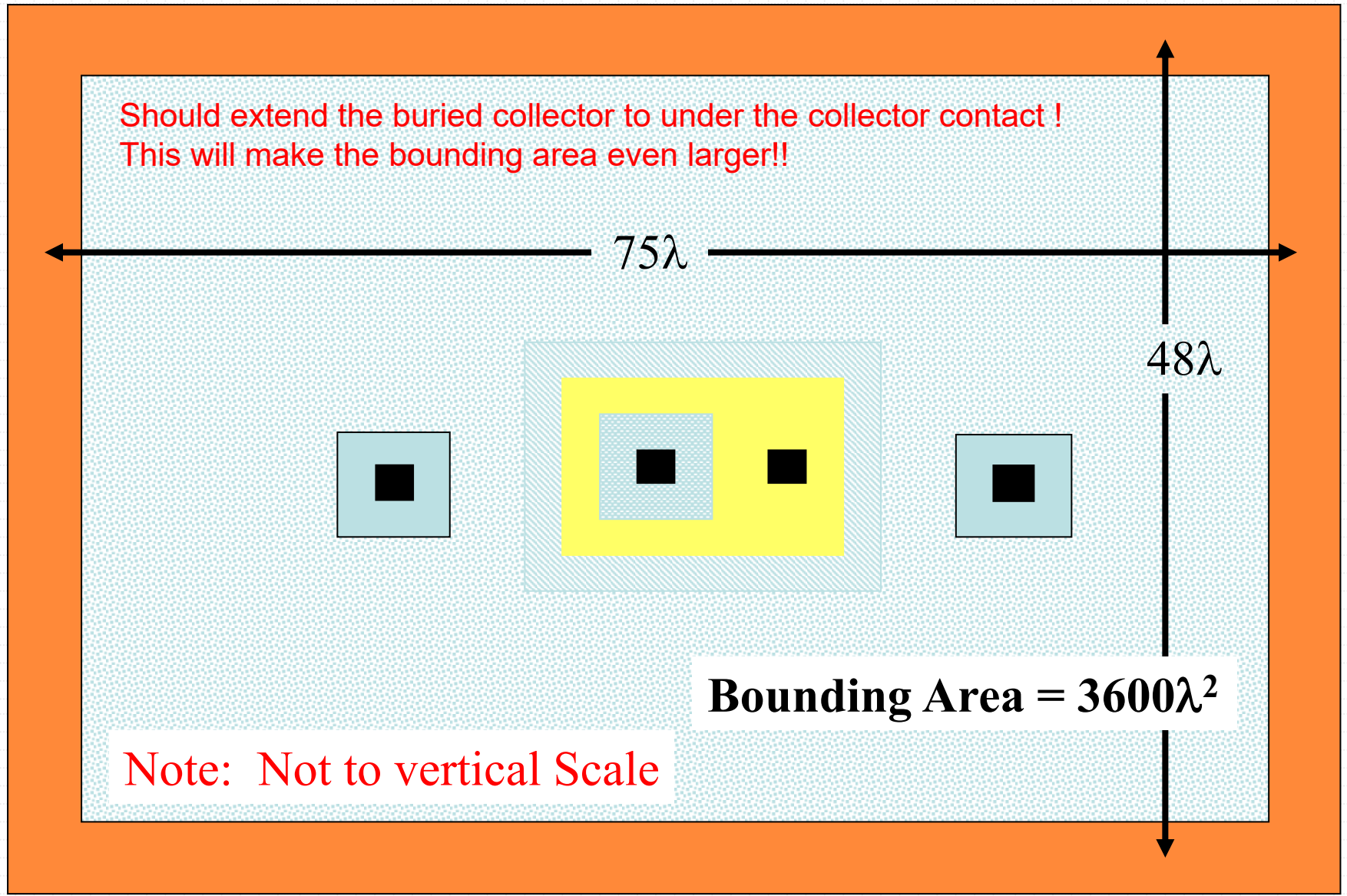Should extend the buried collector to under the collector contact !




Major contributor to large size of BJT is the isolation diffusion which diffuses laterally a large distance beyond the drawn edges of the isolation mask
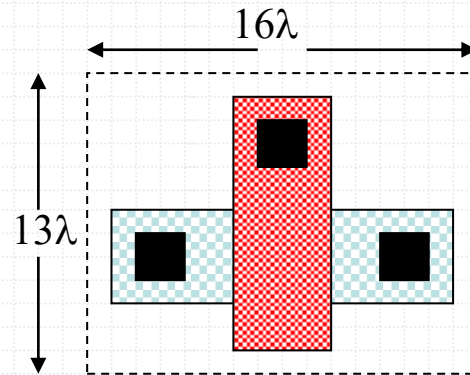
# Comparison with Area for n-channel MOSFET in Bulk CMOS



Bounding Area =  $208\lambda^2$

# Minimum-Sized MOSFET

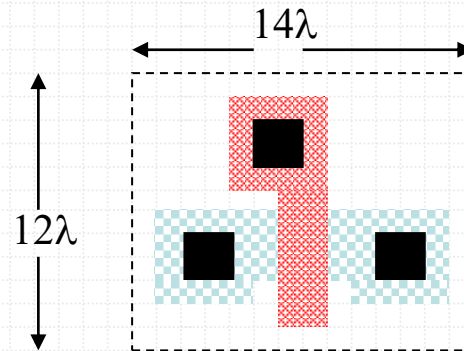

Bounding Area =  $168\lambda^2$

Active Area =  $6\lambda^2$

1 5 10 15 20 25 30 35 40 45 50 55 60 65 70 75

1

5

10

15

20

25

30


35

40

45

50

55

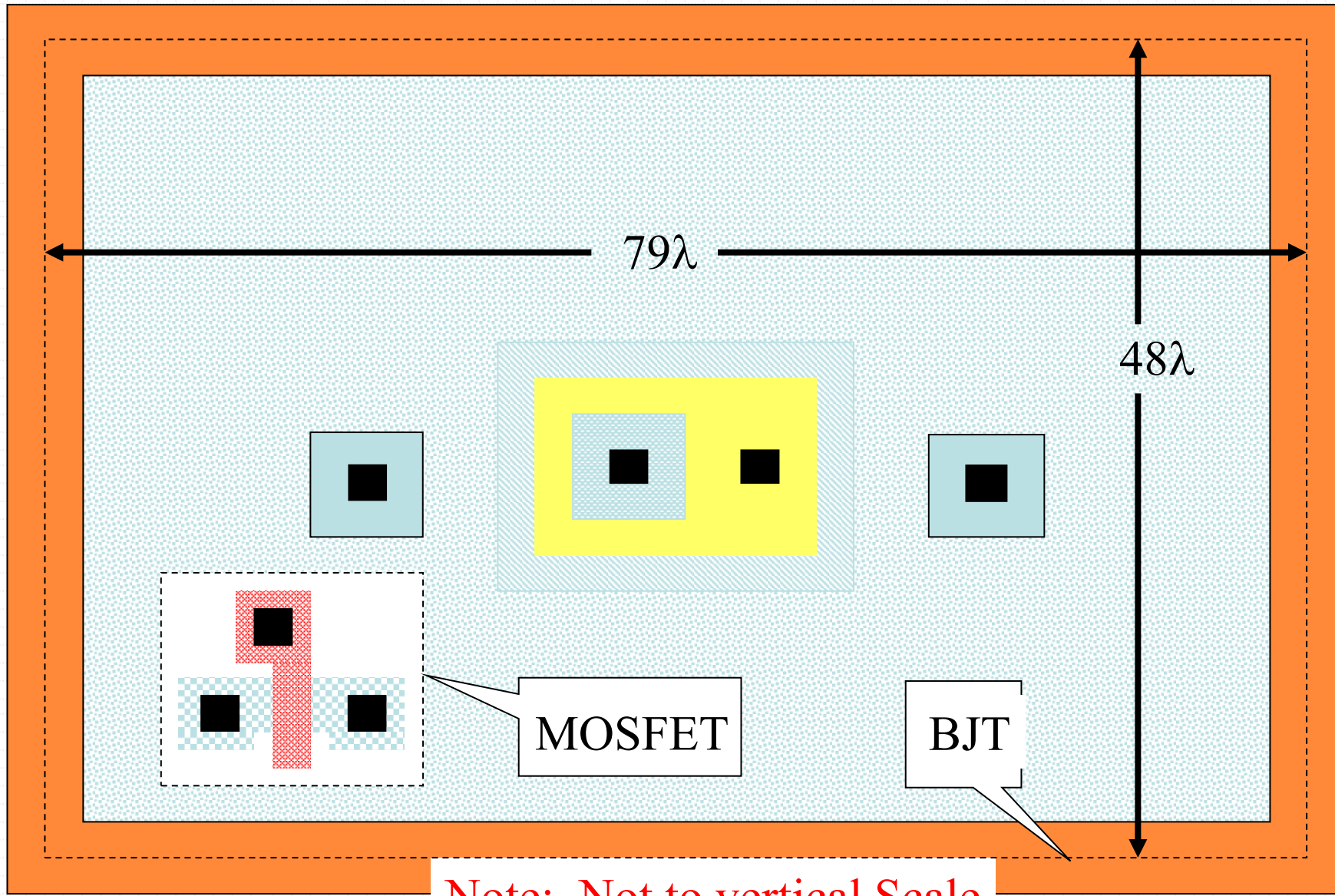

MOSFET

BJT

Note: Not to vertical Scale



# Area Comparison between BJT and MOSFET

- BJT Area =  $3792 \lambda^2$
- n-channel MOSFET Area =  $168 \lambda^2$
- Area Ratio  $\approx 23:1$

# Small-Signal Models

- MOSFET
- BJT
- Diode (of limited use)



# Modeling of the MOSFET

Goal: Obtain a mathematical relationship between the port variables of a device.


$$I_D = f_1(V_{GS}, V_{DS}, V_{BS})$$

$$I_G = f_2(V_{GS}, V_{DS}, V_{BS})$$

$$I_B = f_3(V_{GS}, V_{DS}, V_{BS})$$

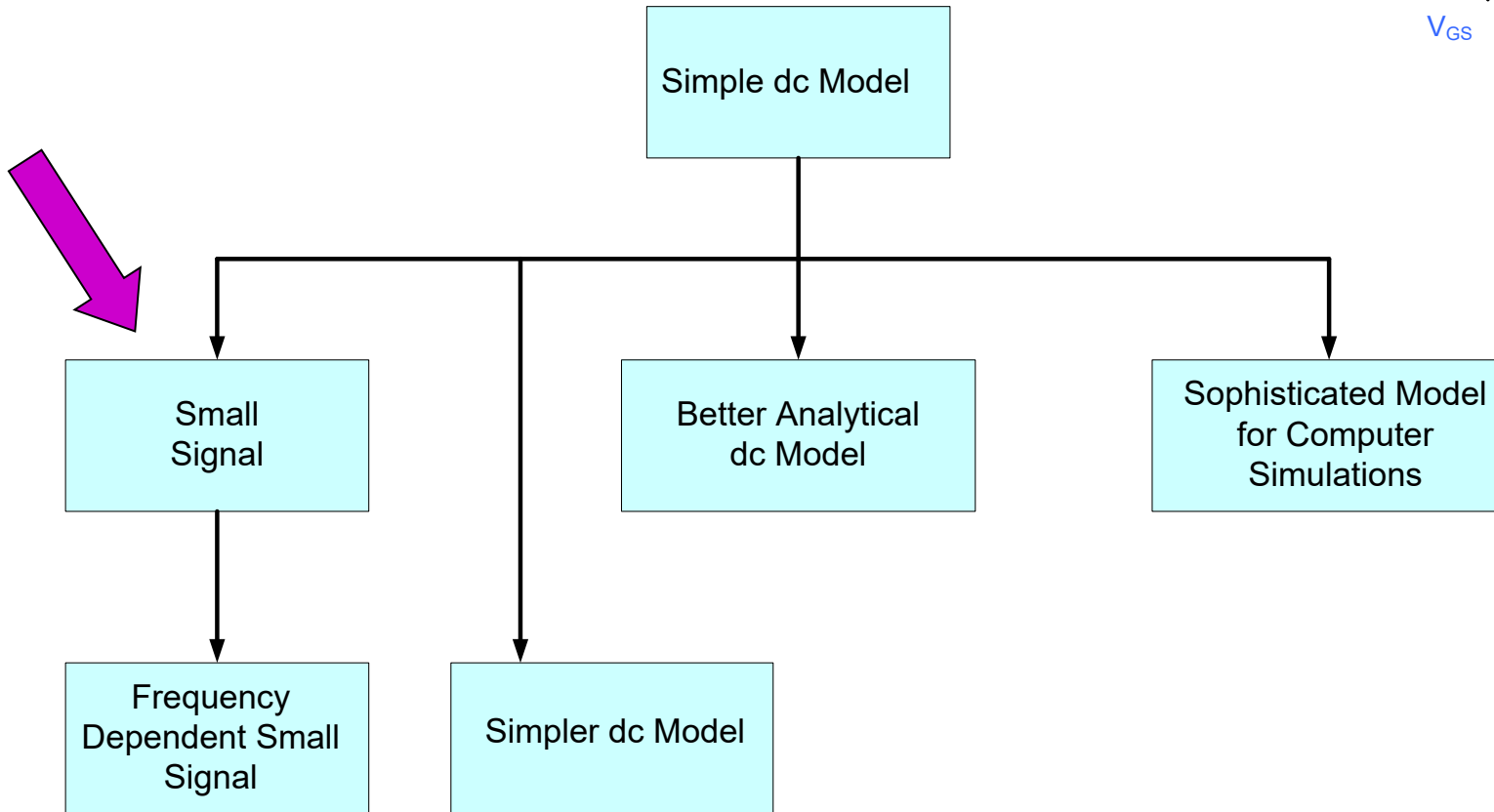 


# Small-Signal Operation

 



Throughout the small input range, the “distant” nonlinearities do not affect performance

# Small-Signal Operation

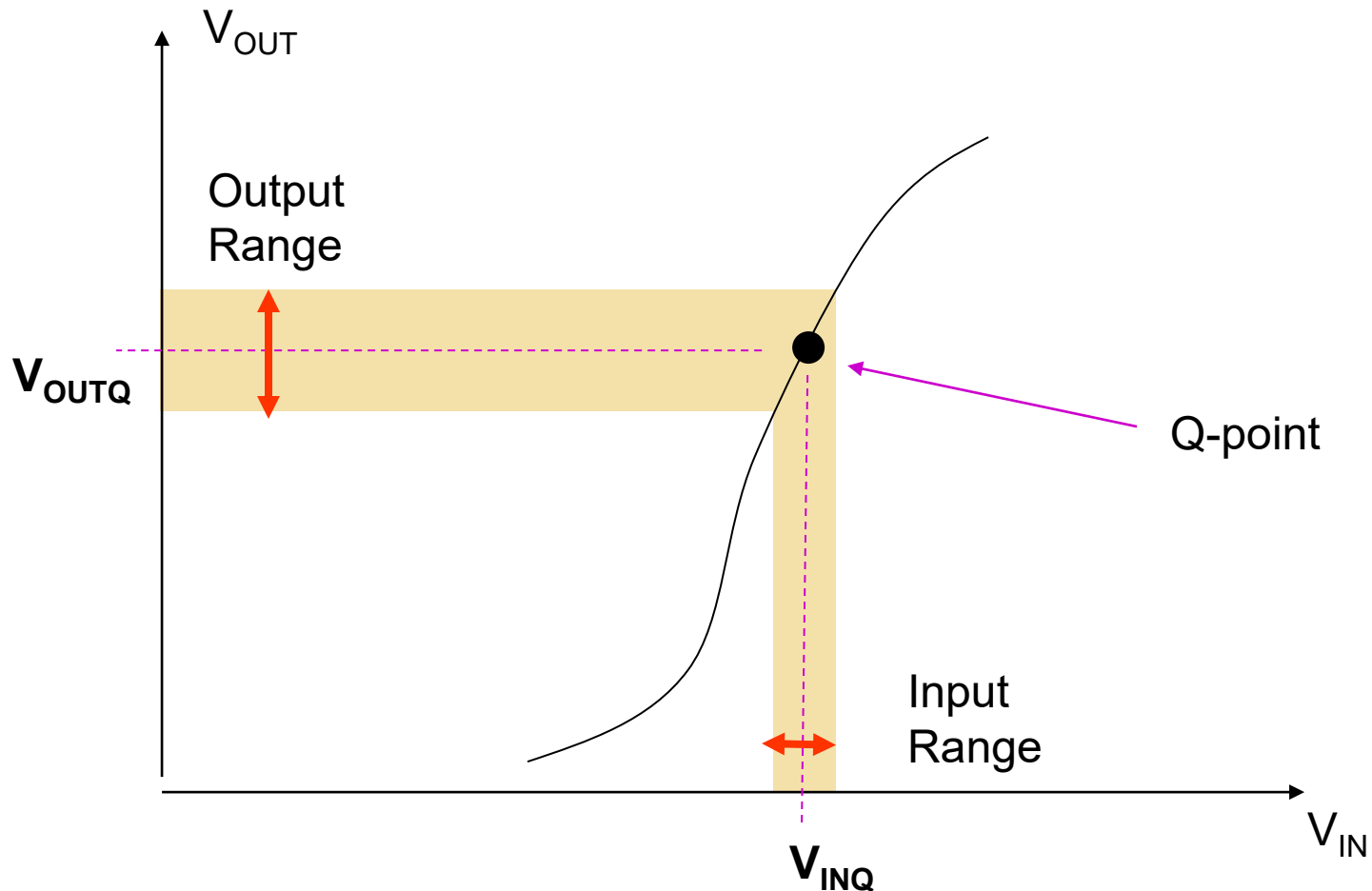

- If slope is steep, output range can be much larger than input range
- The slope can be viewed as the voltage gain of the circuit
- Nonlinear circuit behaves as a linear circuit near Q-point with small-signal inputs

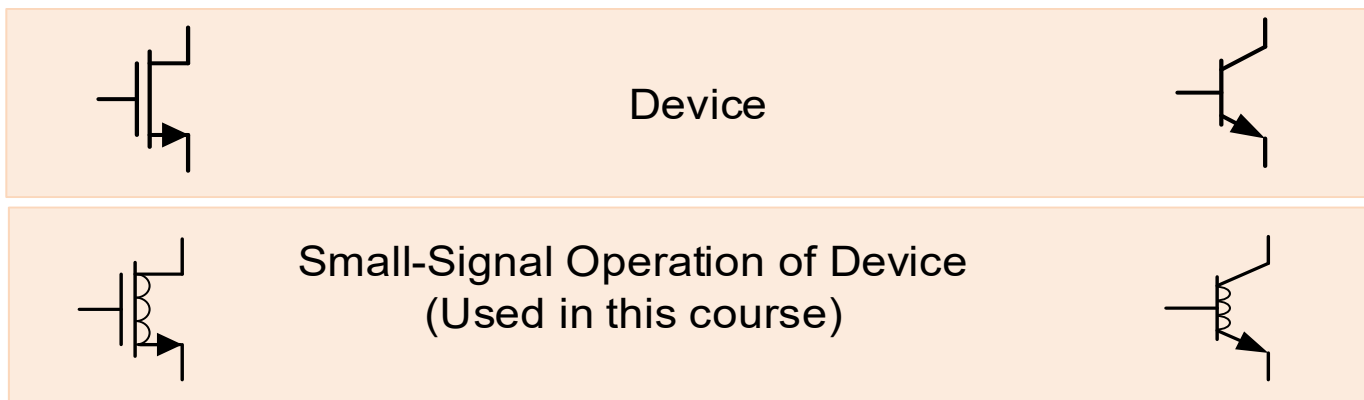
 
# Regions where small-signal operation is most useful



# Small signal operation of nonlinear circuits

$$V_{IN} = V_m \sin \omega t + V_{INQ}$$

$V_M$  is small

 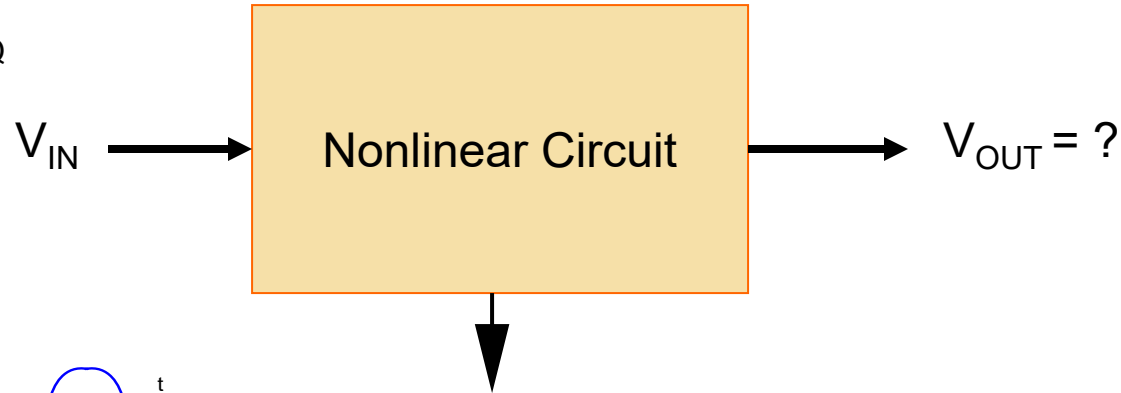

- **Small signal concepts often apply when building amplifiers**
- **If small signal concepts do not apply, usually the amplifier will not perform well**
- **Small signal operation is usually synonymous with “locally linear”**
- **Small signal operation is relative to an “operating point”**

# Operating Point of Electronic Circuits

Often interested in circuits where a small signal input is to be amplified (e.g.  $V_M$  in previous slide is small)

The electrical port variables where the small signals goes to 0 are termed the Operating Points, the Bias Points, the Quiescent Points, or simply the Q-Points

By setting the small signal inputs to 0, it means replacing small voltage inputs with short circuits and small current inputs with open circuits

When analyzing small-signal amplifiers, it is necessary to obtain the Q-point







When designing small-signal amplifiers, establishing of the desired Q-point is termed “biasing”

- Capacitors become open circuits (and inductors short circuits) when determining Q-points
- Simplified dc models of the MOSFET (saturation region) or BJT (forward active region) are usually adequate for determining the Q-point in practical amplifier circuits
- DC voltage and current sources remain when determining Q-points
- Small-signal voltage and current sources are set to 0 when determining Q-points


      
# Operating Point of Electronic Circuits


(small signal inputs, if there are any, are set to 0)



# Operating Point Analysis of MOS and Bipolar Devices

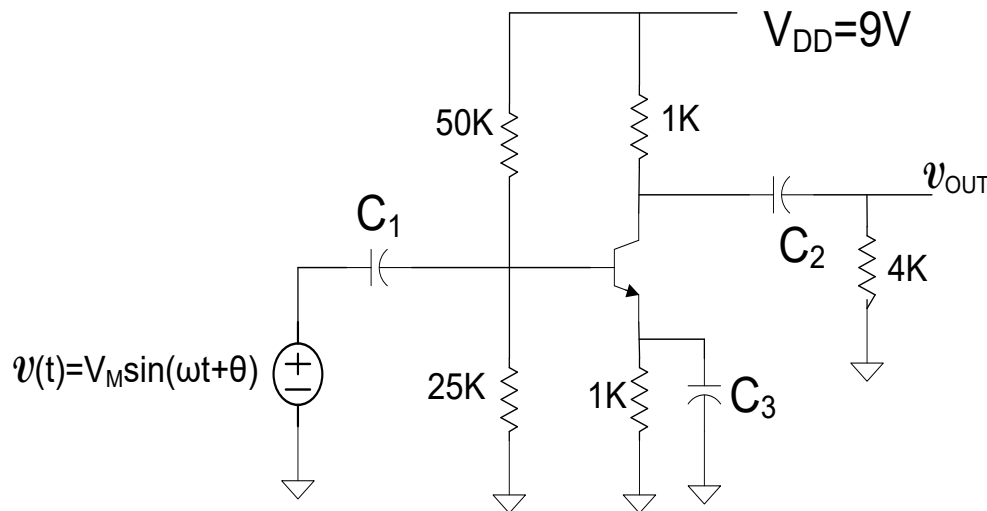Example:

Determine  $V_{OUTQ}$  and  $V_{CQ}$  Assume  $V_M$  is small





Will formally go through the process in this example, will go into more detail about finding the operating point later

# Operating Point Analysis of MOS and Bipolar Devices

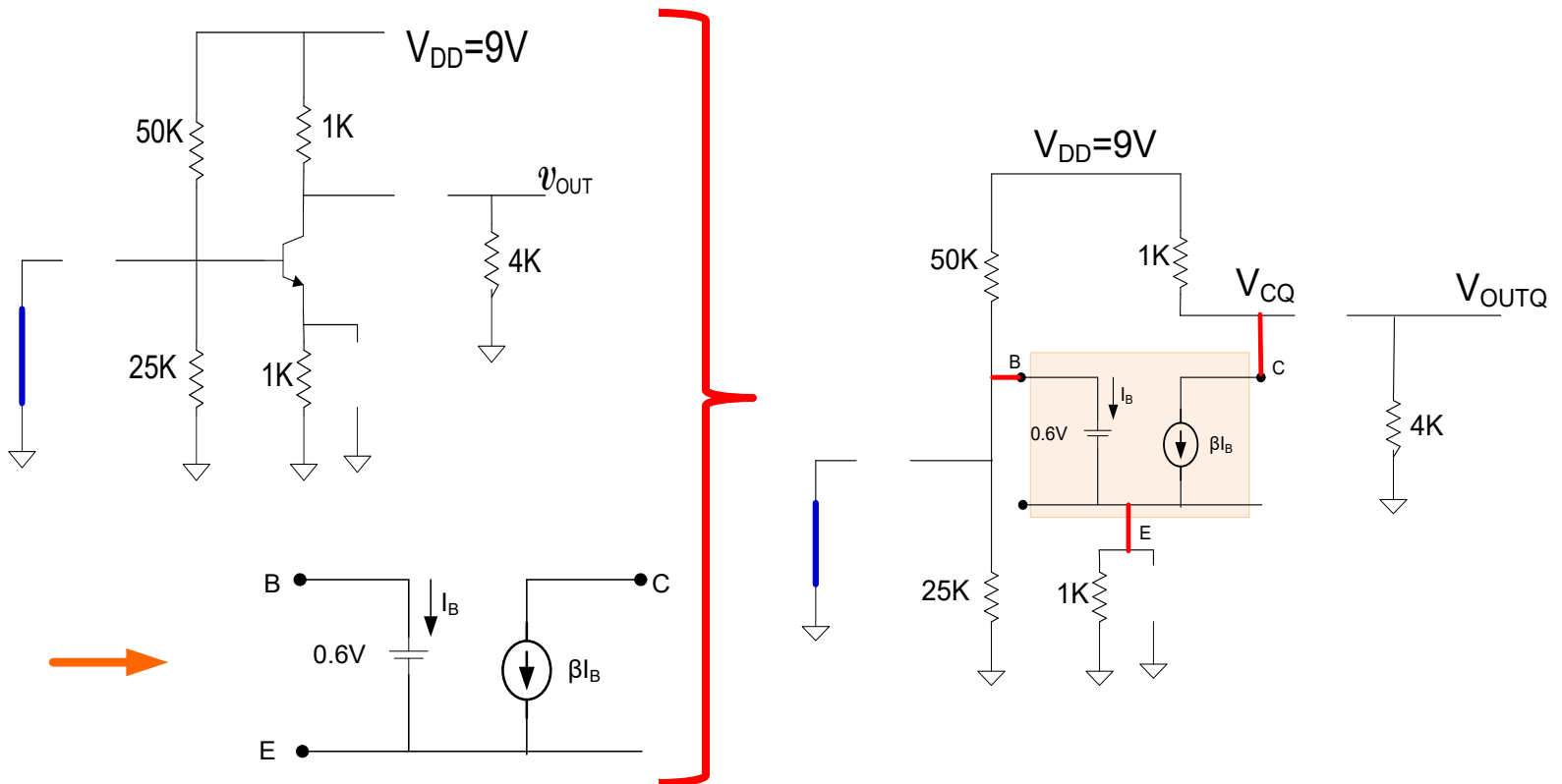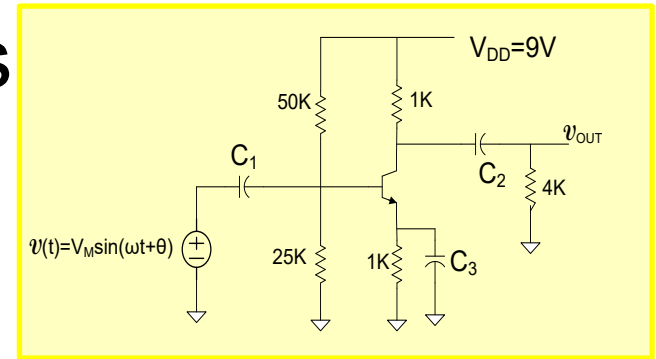Example:


Determine  $V_{OUTQ}$  and  $V_{CQ}$  Assume  $V_M$  is small



# Operating Point Analysis of MOS and Bipolar Devices

Example:

Determine  $V_{OUTQ}$  and  $V_{CQ}$

 

Assume  $\beta=100$

Assume  $I_B \ll I_1$  (must verify)

$$V_{BQ} = \frac{9V}{3} = 3V$$

$$V_{EQ} = 3V - 0.6V = 2.4V$$

$$I_{EQ} = I_{CQ} = \frac{2.4V}{1K} = 2.4mA$$

$$V_{CQ} = 9V - I_{CQ} \cdot 1K = 9V - 2.4V = 6.6V$$

$$V_{OUTQ} = I_{RL} \cdot 4K = 0V$$

$$V_{CQ} = 6.6V$$

$$V_{OUTQ} = 0V$$

# Amplification with Transistors

From Wikipedia: (Oct. 2019 and October 2020)

An **amplifier**, **electronic amplifier** or (informally) **amp** is an electronic device that can increase the power of a signal (a time-varying voltage or current).

What is the “power” of a signal?

Can an amplifier make decisions?

Does Wikipedia have such a basic concept right?

# Amplification with Transistors

From Wikipedia: (Oct. 2019, Oct. 2020, Oct 2021, March 2022)

An **amplifier**, **electronic amplifier** or (informally) **amp** is an electronic device that can increase the power of a signal (a time-varying voltage or current).

It is a two-port electronic circuit that uses electric power from a power supply to increase the amplitude of a signal applied to its input terminals, producing a proportionally greater amplitude signal at its output. The amount of amplification provided by an amplifier is measured by its gain: the ratio of output voltage, current, or power to input. An amplifier is a circuit that has a power gain greater than one.<sup>[1][2][3]</sup>

Self-inconsistent definition !

# Amplification with Transistors

From Wikipedia: ( October 2023)

An **amplifier**, **electronic amplifier** or (informally) **amp** is an electronic device that can increase the magnitude of a [signal](#) (a time-varying [voltage](#) or [current](#)).

It is a [two-port](#) electronic circuit that uses electric power from a [power supply](#) to increase the [amplitude](#) (magnitude of the voltage or current) of a signal applied to its input terminals, producing a [proportionally](#) greater amplitude signal at its output. The amount of amplification provided by an amplifier is measured by its [gain](#): the ratio of output voltage, current, or power to input. An amplifier is defined as a circuit that has a [power gain](#) greater than one.<sup>[2][3][4]</sup>

Even more self-inconsistent definition !

We have had “amplifiers” for over 100 years – will we ever have a consensus on what an amplifier is?

# Amplification with Transistors

From Wikipedia: (Feb. 2017)

An **amplifier**, **electronic amplifier** or (informally) **amp** is an electronic device that increases the [power](#) of a [signal](#) (a time varying voltage or current).

From Wikipedia: (Oct. 2015)

An **amplifier**, **electronic amplifier** or (informally) **amp** is an electronic device that increases the [power](#) of a [signal](#).


From Wikipedia: (approx. 2010)

Generally, an **amplifier** or simply **amp**, is any [device](#) that changes, usually increases, the amplitude of a [signal](#). The "signal" is usually voltage or current.

These “minor” differences in definition are not trivial !




# Signal and Power Levels

 

$$P_{RL} < P_{VIN}$$


$$V_{OUT} < V_{IN}$$

 $P_{RL}$  will be maximum when load impedance matches source impedance



$$P_{RL} > P_{VIN}$$


$$V_{OUT} = V_{IN}$$

 

$$P_{RL} > P_{VIN}$$


$V_{OUT}$  can be larger or smaller than  $V_{IN}$

# Signal and Power Levels

 


$$P_{RL} < P_{VIN}$$

$$V_{OUT} < V_{IN}$$

 

$$P_{RL} > P_{VIN}$$




 
$V_{OUT}$  can be larger or smaller than  $V_{IN}$



$V_{OUT}$  can be larger or smaller than  $V_{IN}$

$P_{RL}$  can be larger or smaller than  $P_{VIN}$

# Signal and Power Levels

    

In most electronic circuit “amplifier” applications, there is little concern about whether the power in the load is larger or smaller than the power supplied by the source

Impedance matching for the purpose of delivering power to a load is seldom of concern or even used in most electronic circuits

# Amplification with Transistors

From Wikipedia: (Oct. 2023)

An **amplifier**, **electronic amplifier** or (informally) **amp** is an electronic device that can increase the magnitude of a [signal](#) (a time-varying [voltage](#) or [current](#)).

- It is difficult to increase the voltage or current very much with passive RC circuits
- Voltage and current levels can be increased a lot with transformers but transformers not practical in integrated circuits
- Power levels can not be increased with passive elements (R, L, C, and Transformers)
- Often an amplifier is defined to be a circuit that **can** be used to increase power delivered to a resistive load (be careful with Wikipedia and WWW even when some of the most basic concepts are discussed !!)
- Transistors can be used to increase not only signal levels but power levels to a load
- In transistor circuits, power that is delivered in the signal path is supplied by a biasing network
- Signals that are amplified are often not time varying

In the electronics community, there is often little or no concern about the power delivered to a load and the term “amplifier” generally refers to an electronic device that changes the level of a voltage or current, converts from one unit to another (V to I or I to V), or provides the power needed to drive a predetermined load.



Stay Safe and Stay Healthy !

End of Lecture 22