

# EE 330

## Lecture 25

- Small Signal Analysis
- Small Signal Models for MOSFET and BJT

# Exam Schedule

Exam 1	Friday Sept 24
Exam 2	Friday Oct 22
Exam 3	Friday Nov 19
Final	Tues Dec 14 12:00 p.m.


Photo courtesy of the director of the National Institute of Health ( NIH)



As a courtesy to fellow classmates, TAs, and the instructor


**Wearing of masks during lectures and in the laboratories for this course would be appreciated irrespective of vaccination status**

# Small-Signal Analysis



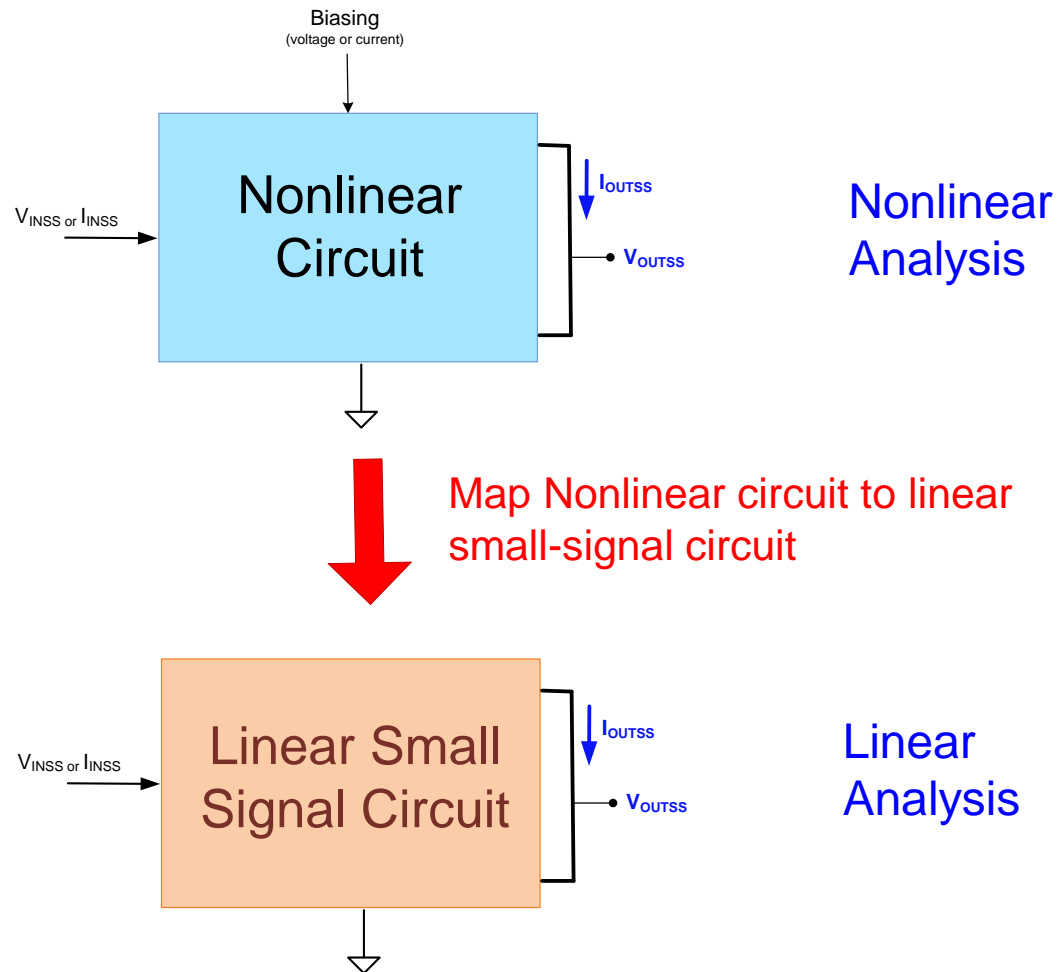


- Will commit next several lectures to developing this approach
- Analysis will be MUCH simpler, faster, and provide significantly more insight
- Applicable to many fields of engineering
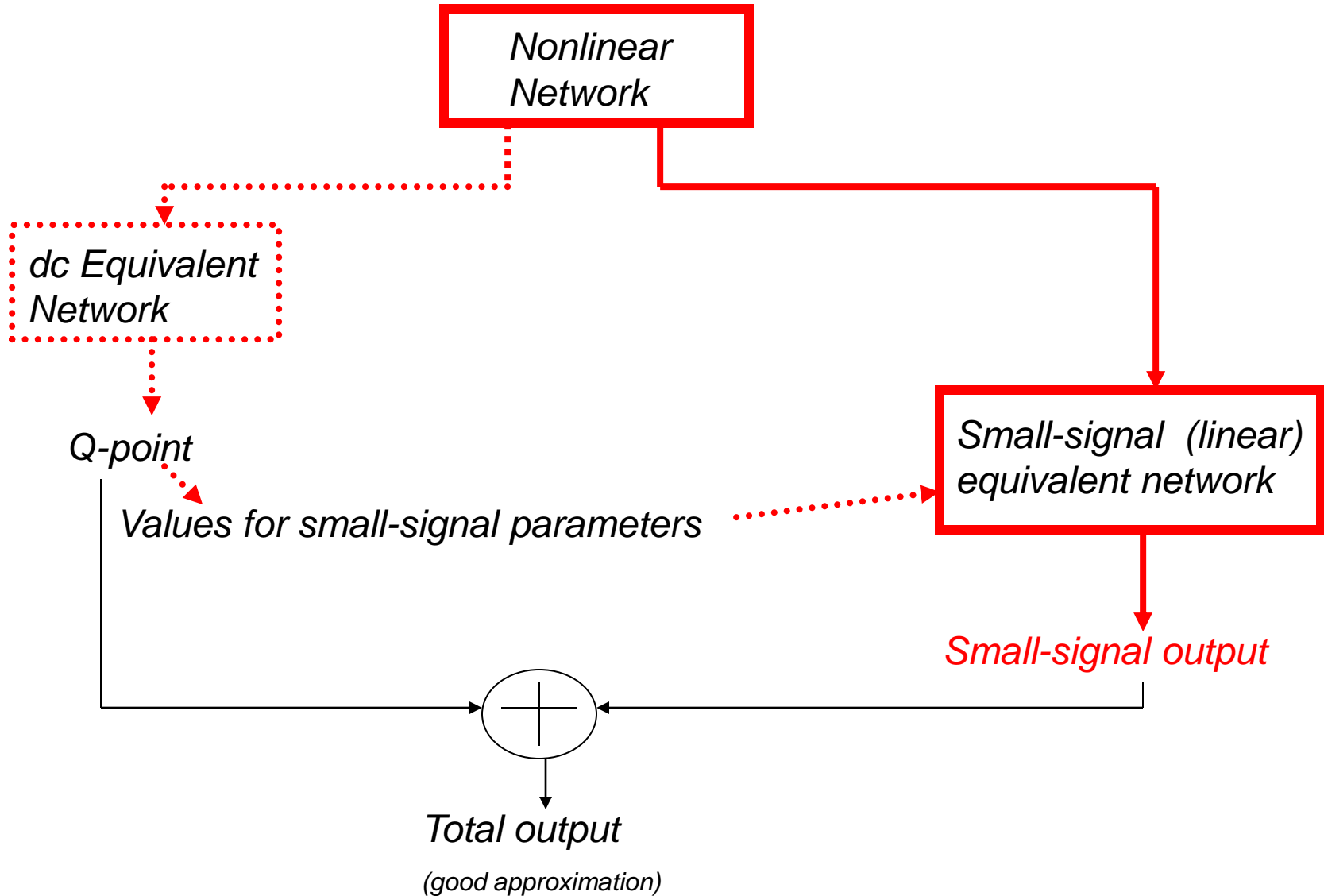
# “Alternative” Approach to small-signal analysis of nonlinear networks



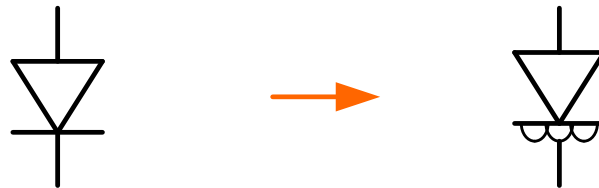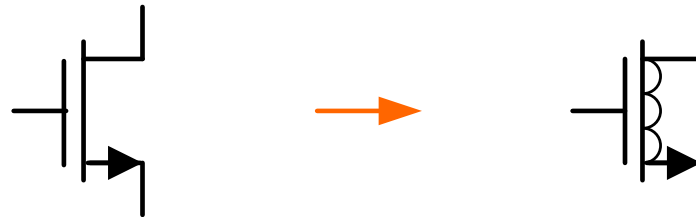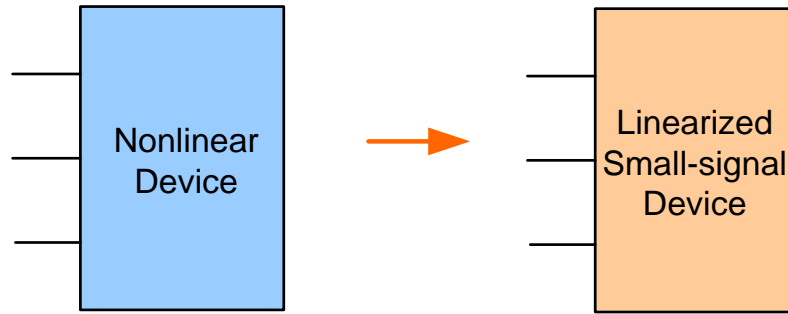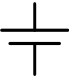

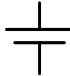












# Linearized nonlinear devices



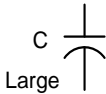
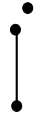
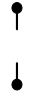
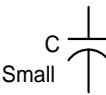
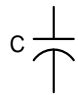
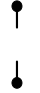
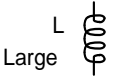
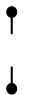
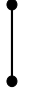
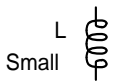
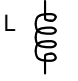
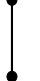
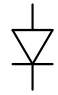

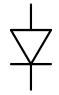
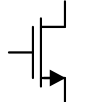
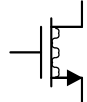
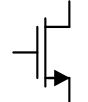
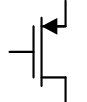
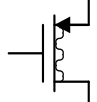
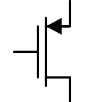
This terminology will be used in THIS course to emphasize difference between nonlinear model and linearized small signal model

## Review from Last Lecture

# Small-signal and simplified dc equivalent elements

	Element	ss equivalent	Simplified dc equivalent
dc Voltage Source	$V_{DC}$ 		$V_{DC}$ 
ac Voltage Source	$V_{AC}$ 	$V_{AC}$ 	
dc Current Source	$I_{DC}$ 		$I_{DC}$ 
ac Current Source	$I_{AC}$ 	$I_{AC}$ 	
Resistor	$R$ 	$R$ 	$R$ 


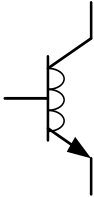









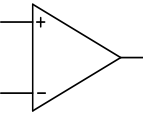
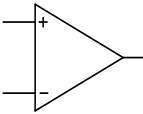
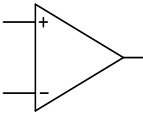
# Small-signal and simplified dc equivalent elements

	Element	ss equivalent	Simplified dc equivalent
Capacitors	<p>C</p>  <p>Large</p>		
	<p>C</p>  <p>Small</p>		
Inductors	<p>L</p>  <p>Large</p>		
	<p>L</p>  <p>Small</p>		
Diodes			 <p>Simplified</p>
MOS transistors (MOSFET (enhancement or depletion), JFET)			 <p>Simplified</p>
			 <p>Simplified</p>




Review from Last Lecture

# Small-signal and simplified dc equivalent elements

	Element	ss equivalent	Simplified dc equivalent
Bipolar Transistors			 Simplified
			 Simplified
Dependent Sources (Linear)			
	$V_O = A_V V_{IN}$ $I_O = A_I I_{IN}$ $V_O = R_T I_{IN}$ $I_O = G_T V_{IN}$		
			
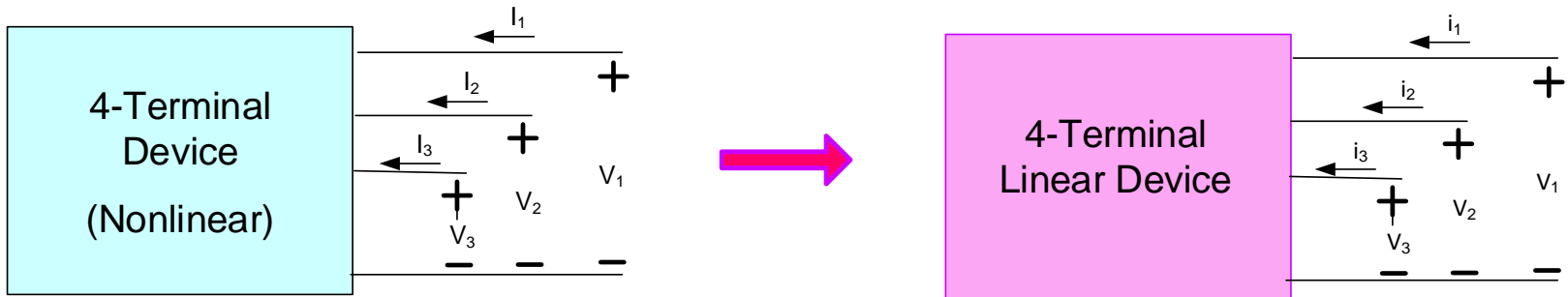
# Small-Signal Model of 4-Terminal Network



$$\left. \begin{aligned} I_1 &= f_1(V_1, V_2, V_3) \\ I_2 &= f_2(V_1, V_2, V_3) \\ I_3 &= f_3(V_1, V_2, V_3) \end{aligned} \right\}$$

$$\left. \begin{aligned} i_1 &= g_1(v_1, v_2, v_3) \\ i_2 &= g_2(v_1, v_2, v_3) \\ i_3 &= g_3(v_1, v_2, v_3) \end{aligned} \right\}$$

Mapping is unique (with same models)

# Small Signal Model

$$\dot{\mathbf{i}}_1 = y_{11}\mathbf{u}_1 + y_{12}\mathbf{u}_2 + y_{13}\mathbf{u}_3$$

$$\dot{\mathbf{i}}_2 = y_{21}\mathbf{u}_1 + y_{22}\mathbf{u}_2 + y_{23}\mathbf{u}_3$$

$$\dot{\mathbf{i}}_3 = y_{31}\mathbf{u}_1 + y_{32}\mathbf{u}_2 + y_{33}\mathbf{u}_3$$


where

$$\mathbf{y}_{ij} = \left. \frac{\partial \mathbf{f}_i(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial \mathbf{V}_j} \right|_{\bar{\mathbf{v}} = \bar{\mathbf{v}}_Q}$$

- This is a small-signal model of a 4-terminal network and it is linear
- 9 small-signal parameters characterize the linear 4-terminal network
- Small-signal model parameters dependent upon Q-point !
- Termed the y-parameter model or “admittance” –parameter model
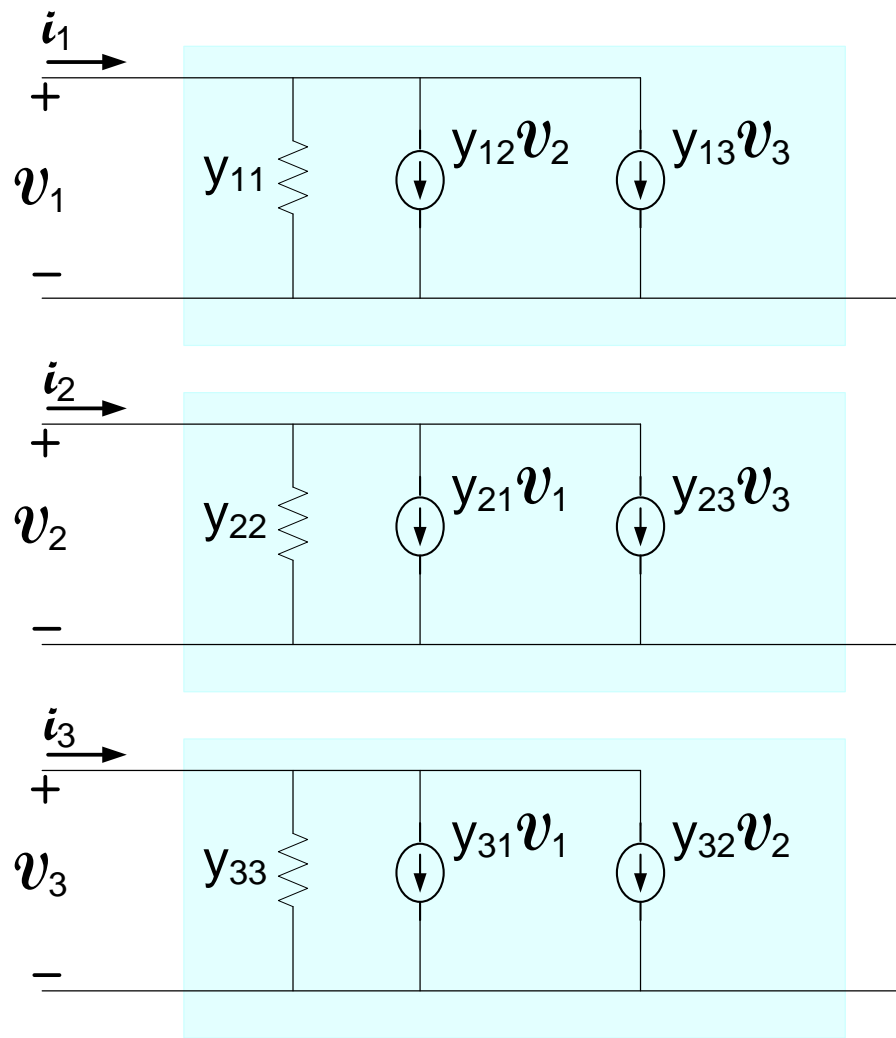
## Review from Last Lecture


A small-signal equivalent circuit of a 4-terminal nonlinear network  
(equivalent circuit because has exactly the same port equations)



$$y_{ij} = \left. \frac{\partial f_i(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial \mathbf{V}_j} \right|_{\bar{\mathbf{V}} = \bar{\mathbf{V}}_Q}$$

Equivalent circuit is not unique  
Equivalent circuit is a three-port network

# Small-Signal Model

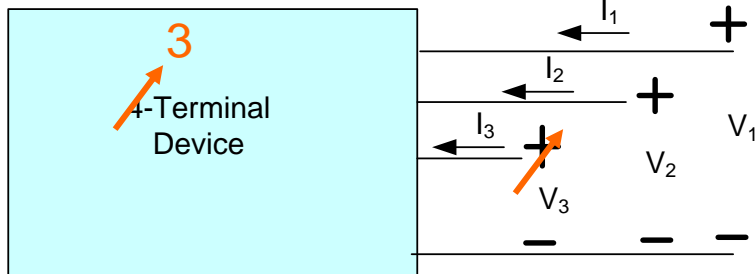

$$\left. \begin{aligned} \dot{i}_1 &= g_1(v_1, v_2, v_3) \\ \dot{i}_2 &= g_2(v_1, v_2, v_3) \\ \dot{i}_3 &= g_3(v_1, v_2, v_3) \end{aligned} \right\}$$


$$\dot{i}_1 = y_{11}v_1 + y_{12}v_2 + y_{13}v_3$$

$$\dot{i}_2 = y_{21}v_1 + y_{22}v_2 + y_{23}v_3$$

$$\dot{i}_3 = y_{31}v_1 + y_{32}v_2 + y_{33}v_3$$

$$y_{ij} = \left. \frac{\partial f_i(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial V_j} \right|_{\bar{\mathbf{v}} = \bar{\mathbf{v}}_Q}$$

# Small-Signal Model

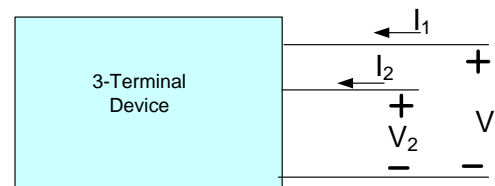


$$\begin{aligned} \dot{i}_1 &= y_{11} \mathbf{v}_1 + y_{12} \mathbf{v}_2 \\ \dot{i}_2 &= y_{21} \mathbf{v}_1 + y_{22} \mathbf{v}_2 \end{aligned}$$

$$y_{ij} = \left. \frac{\partial f_i(\mathbf{V}_1, \mathbf{V}_2)}{\partial \mathbf{V}_j} \right|_{\bar{\mathbf{V}} = \bar{\mathbf{V}}_Q}$$


$$\bar{\mathbf{V}} = \begin{pmatrix} \mathbf{V}_{1Q} \\ \mathbf{V}_{2Q} \end{pmatrix}$$

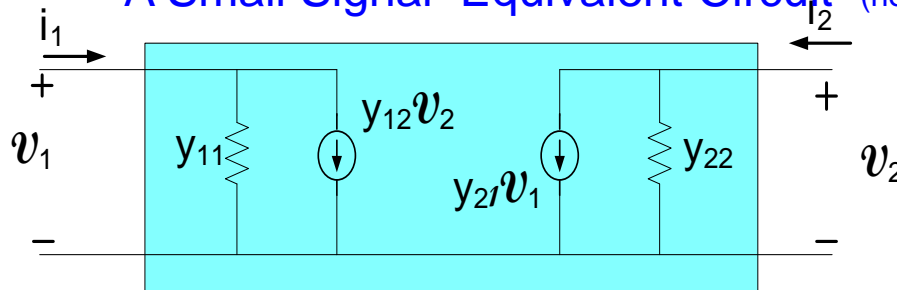A Small Signal Equivalent Circuit (not unique)



- Small-signal model is a “two-port”
- 4 small-signal parameters characterize this 3-terminal linear network
- Small signal parameters dependent upon Q-point

# Small-Signal Model

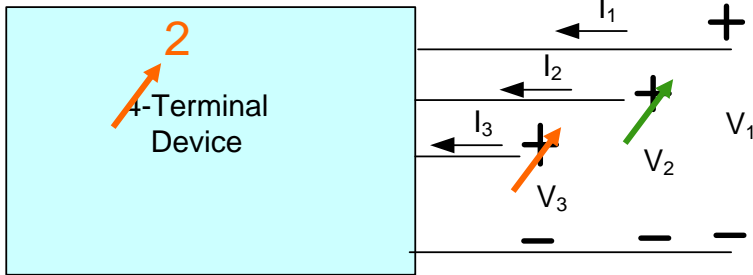

$$\dot{i}_1 = g_1(v_1, v_2, v_3)$$

$$\dot{i}_2 = g_2(v_1, v_2, v_3)$$

$$\dot{i}_3 = g_3(v_1, v_2, v_3)$$


$$\dot{i}_1 = y_{11}v_1 + y_{12}v_2 + y_{13}v_3$$

$$\dot{i}_2 = y_{21}v_1 + y_{22}v_2 + y_{23}v_3$$

$$\dot{i}_3 = y_{31}v_1 + y_{32}v_2 + y_{33}v_3$$

$$y_{ij} = \left. \frac{\partial f_i(\mathbf{v}_1, \mathbf{v}_2, \mathbf{v}_3)}{\partial v_j} \right|_{\bar{\mathbf{v}} = \bar{\mathbf{v}}_Q}$$


# Small-Signal Model

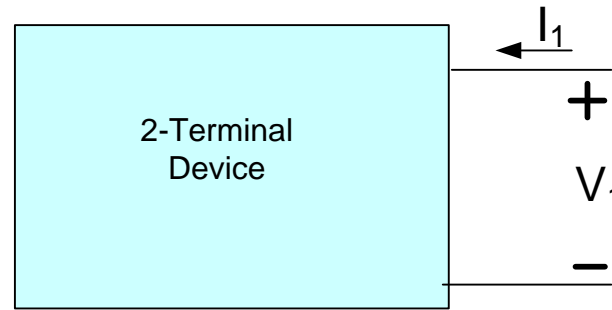

$$\mathbf{i}_1 = \mathbf{y}_{11} \mathbf{v}_1$$

$$y_{11} = \left. \frac{\partial f_1(V_1)}{\partial V_1} \right|_{\bar{V} = \bar{V}_Q} \quad \bar{V} = V_{1Q}$$

A Small Signal Equivalent Circuit

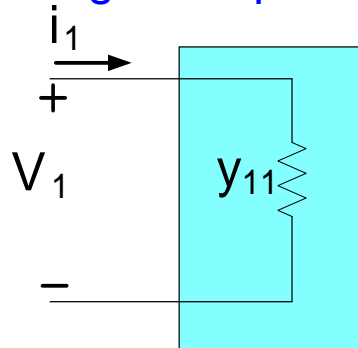





Small-signal model is a one-port

This was actually developed earlier !






# Review from Last Lecture

## *Linearized nonlinear devices*

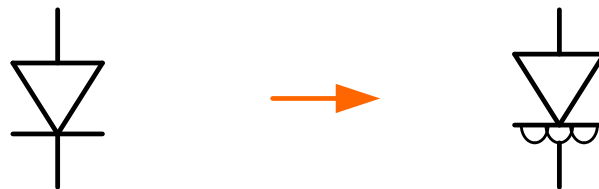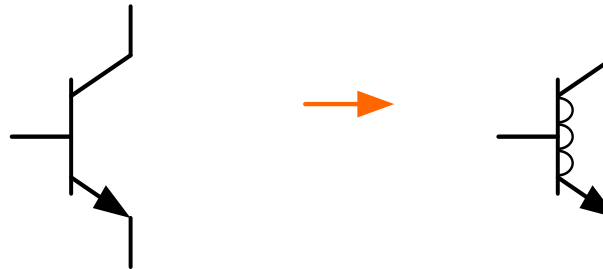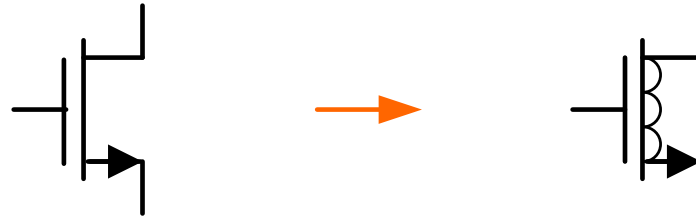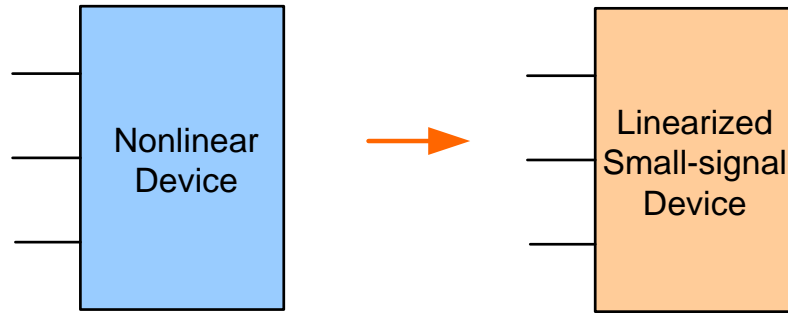


How is the small-signal equivalent circuit obtained from the nonlinear circuit?

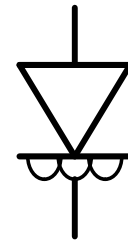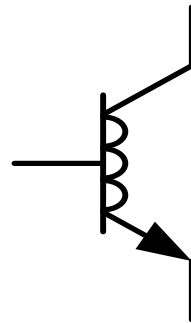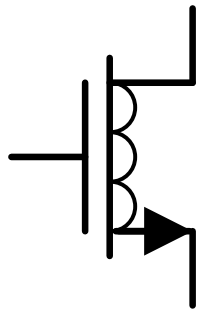
*What is the small-signal equivalent of the MOSFET, BJT, and diode ?*



# Small Signal Model of MOSFET

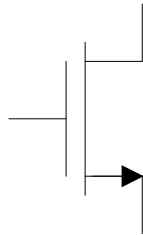

*3-terminal device*

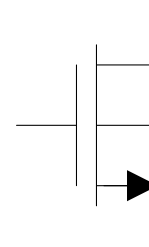


*4-terminal device*

*MOSFET is actually a 4-terminal device but for many applications acceptable predictions of performance can be obtained by treating it as a 3-terminal device by neglecting the bulk terminal*

*In this course, we have been treating it as a 3-terminal device and in this lecture will develop the small-signal model by treating it as a 3-terminal device*

*When treated as a 4-terminal device, the bulk voltage introduces one additional term to the small signal model which is often either negligibly small or has no effect on circuit performance (will develop 4-terminal ss model later)*

# Small Signal Model of MOSFET

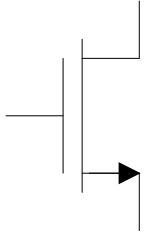


Large Signal Model

$$I_G = 0$$

3-terminal device
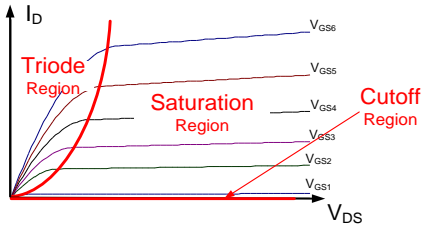
$$I_D = \begin{cases} 0 & V_{GS} \leq V_T \\ \mu C_{OX} \frac{W}{L} \left( V_{GS} - V_T - \frac{V_{DS}}{2} \right) V_{DS} & V_{GS} \geq V_T \quad V_{DS} < V_{GS} - V_T \\ \mu C_{OX} \frac{W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS}) & V_{GS} \geq V_T \quad V_{DS} \geq V_{GS} - V_T \end{cases}$$



*MOSFET is usually operated in saturation region in linear applications where a small-signal model is needed so will develop the small-signal model in the saturation region*

# Small Signal Model of MOSFET

$$I_1 = f_1(V_1, V_2) \quad \longleftrightarrow \quad I_G = 0$$

$$I_2 = f_2(V_1, V_2) \quad \longleftrightarrow \quad I_D = \mu C_{\text{OX}} \frac{W}{2L} (V_{\text{GS}} - V_{\text{T}})^2 (1 + \lambda V_{\text{DS}})$$

$$I_G = f_1(V_{\text{GS}}, V_{\text{DS}})$$

$$I_D = f_2(V_{\text{GS}}, V_{\text{DS}})$$

*Small-signal model:*

$$y_{ij} = \left. \frac{\partial f_i(V_1, V_2)}{\partial V_j} \right|_{\bar{V} = \bar{V}_Q}$$

$$y_{11} = \left. \frac{\partial I_G}{\partial V_{\text{GS}}} \right|_{\bar{V} = \bar{V}_Q}$$

$$y_{12} = \left. \frac{\partial I_G}{\partial V_{\text{DS}}} \right|_{\bar{V} = \bar{V}_Q}$$

$$y_{21} = \left. \frac{\partial I_D}{\partial V_{\text{GS}}} \right|_{\bar{V} = \bar{V}_Q}$$

$$y_{22} = \left. \frac{\partial I_D}{\partial V_{\text{DS}}} \right|_{\bar{V} = \bar{V}_Q}$$

# Small Signal Model of MOSFET

$$I_G = 0$$

$$I_D = \mu C_{\text{OX}} \frac{W}{2L} (V_{\text{GS}} - V_{\text{T}})^2 (1 + \lambda V_{\text{DS}})$$

*Small-signal model:*

$$y_{11} = \left. \frac{\partial I_G}{\partial V_{\text{GS}}} \right|_{\tilde{V} = \tilde{V}_Q} = ?$$

$$y_{12} = \left. \frac{\partial I_G}{\partial V_{\text{DS}}} \right|_{\tilde{V} = \tilde{V}_Q} = ?$$

$$y_{21} = \left. \frac{\partial I_D}{\partial V_{\text{GS}}} \right|_{\tilde{V} = \tilde{V}_Q} = ?$$

$$y_{22} = \left. \frac{\partial I_D}{\partial V_{\text{DS}}} \right|_{\tilde{V} = \tilde{V}_Q} = ?$$

Recall: termed the y-parameter model

# Small Signal Model of MOSFET

$$I_1 = f_1(V_1, V_2) \quad \longleftrightarrow \quad I_G = 0$$

$$I_2 = f_2(V_1, V_2) \quad \longleftrightarrow \quad I_D = \mu C_{\text{ox}} \frac{W}{2L} (V_{\text{GS}} - V_{\text{T}})^2 (1 + \lambda V_{\text{DS}})$$

*Small-signal model:*

$$y_{11} = \left. \frac{\partial I_G}{\partial V_{\text{GS}}} \right|_{\tilde{V} = \tilde{V}_Q} = 0$$


$$y_{12} = \left. \frac{\partial I_G}{\partial V_{\text{DS}}} \right|_{\tilde{V} = \tilde{V}_Q} = 0$$

$$y_{21} = \left. \frac{\partial I_D}{\partial V_{\text{GS}}} \right|_{\tilde{V} = \tilde{V}_Q} = 2\mu C_{\text{ox}} \frac{W}{2L} (V_{\text{GS}} - V_{\text{T}})' (1 + \lambda V_{\text{DS}}) \Big|_{\tilde{V} = \tilde{V}_Q} = \mu C_{\text{ox}} \frac{W}{L} (V_{\text{GSQ}} - V_{\text{T}}) (1 + \lambda V_{\text{DSQ}})$$

$$y_{21} \cong \mu C_{\text{ox}} \frac{W}{L} (V_{\text{GSQ}} - V_{\text{T}})$$


$$y_{22} = \left. \frac{\partial I_D}{\partial V_{\text{DS}}} \right|_{\tilde{V} = \tilde{V}_Q} = \mu C_{\text{ox}} \frac{W}{2L} (V_{\text{GS}} - V_{\text{T}})^2 \lambda \Big|_{\tilde{V} = \tilde{V}_Q} \cong \lambda I_{\text{DQ}}$$

# Small Signal Model of MOSFET

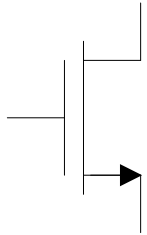

$$I_G = 0$$
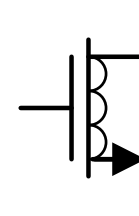
$$I_D = \mu C_{\text{OX}} \frac{W}{2L} (V_{\text{GS}} - V_{\text{T}})^2 (1 + \lambda V_{\text{DS}})$$




$$y_{12} = 0$$

$$y_{11} = 0$$

$$y_{21} \cong \mu C_{\text{OX}} \frac{W}{L} (V_{\text{GSQ}} - V_{\text{T}})$$

$$y_{22} \cong \lambda I_{\text{DQ}}$$
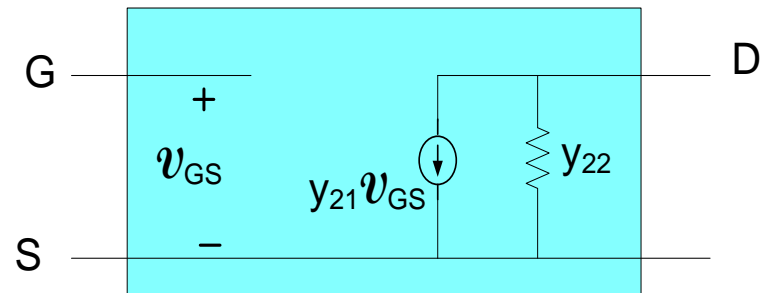
$$\begin{aligned} i_G &= y_{11} v_{\text{GS}} + y_{12} v_{\text{DS}} \\ i_D &= y_{21} v_{\text{GS}} + y_{22} v_{\text{DS}} \end{aligned}$$




An equivalent circuit

(y-parameter model)





# Small-Signal Model of MOSFET

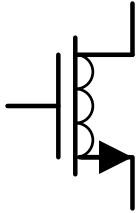

by convention,  $y_{21}=g_m$ ,  $y_{22}=g_o$

$$\therefore y_{21} \cong g_m = \mu C_{\text{OX}} \frac{W}{L} (V_{\text{GSQ}} - V_T)$$
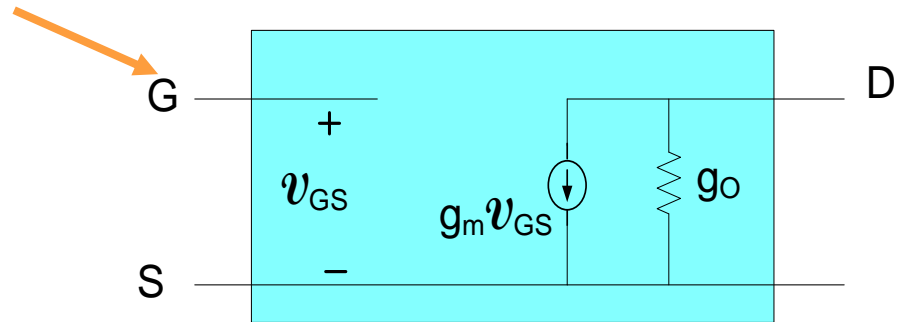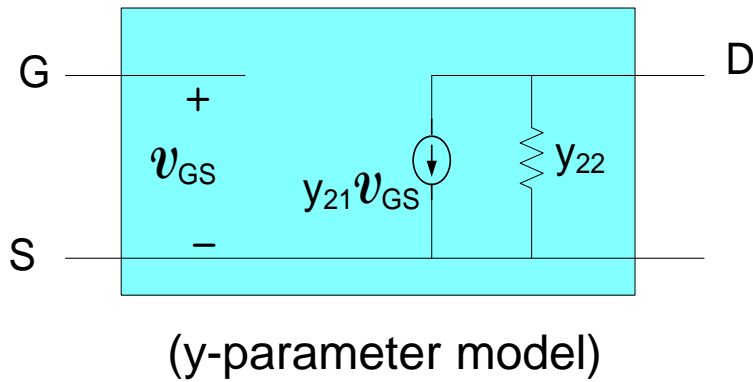
$$y_{22} = g_o \cong \lambda I_{\text{DQ}}$$




$$i_G = 0$$

$$i_D = g_m v_{GS} + g_o v_{DS}$$

Note:  $g_o$  vanishes when  $\lambda=0$


still y-parameter model  
but use "g" parameter notation

# Small-Signal Model of MOSFET

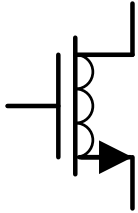

$$g_m = \mu C_{\text{ox}} \frac{W}{L} (V_{\text{GSQ}} - V_T)$$

$$g_o \cong \lambda I_{\text{DQ}}$$

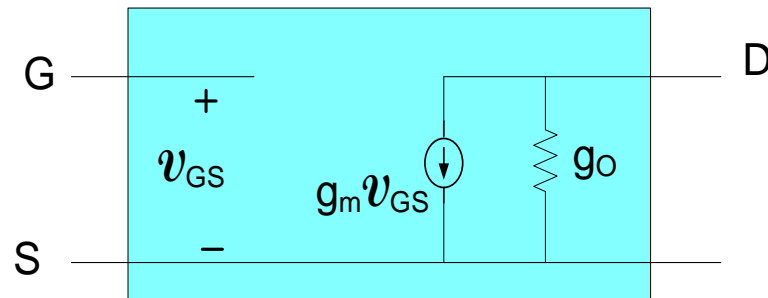

*Alternate equivalent expressions for  $g_m$ :*

$$I_{\text{DQ}} = \mu C_{\text{ox}} \frac{W}{2L} (V_{\text{GSQ}} - V_T)^2 (1 + \lambda V_{\text{DSQ}}) \cong \mu C_{\text{ox}} \frac{W}{2L} (V_{\text{GSQ}} - V_T)^2$$


$$g_m = \mu C_{\text{ox}} \frac{W}{L} (V_{\text{GSQ}} - V_T)$$

$$g_m = \sqrt{2\mu C_{\text{ox}} \frac{W}{L}} \cdot \sqrt{I_{\text{DQ}}}$$

$$g_m = \frac{2I_{\text{DQ}}}{V_{\text{GSQ}} - V_T}$$

Consider again:

## Small-signal analysis example


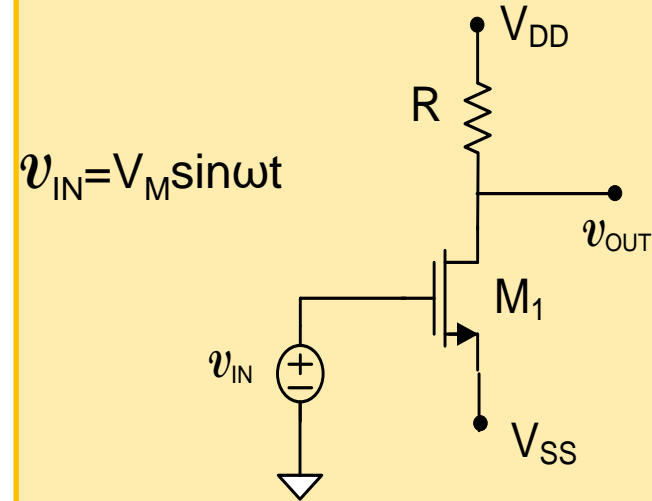


$$A_v = \frac{2I_{DQ} R}{[V_{SS} + V_T]}$$

Derived for  $\lambda=0$  (equivalently  $g_o=0$ )



$$I_D = \mu C_{ox} \frac{W}{2L} (V_{GS} - V_T)^2$$

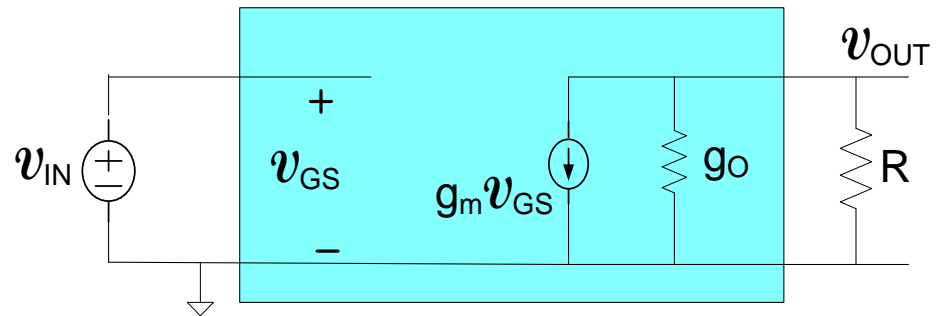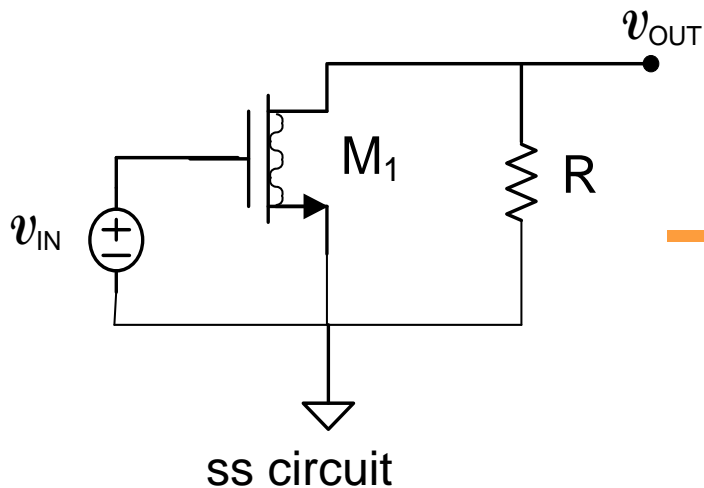Recall the derivation was very tedious and time consuming!



Consider again:


# Small-signal analysis example

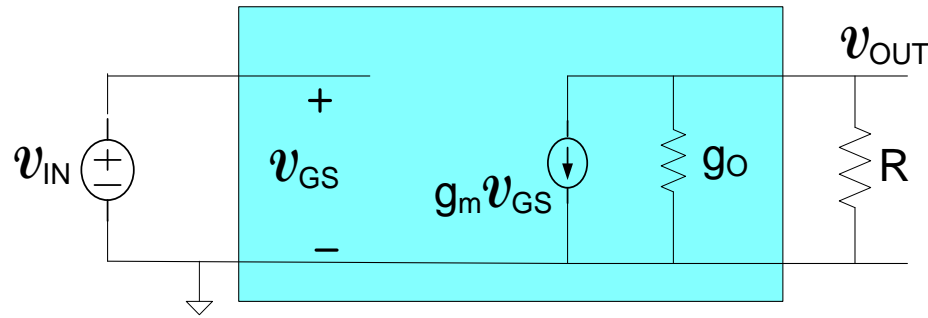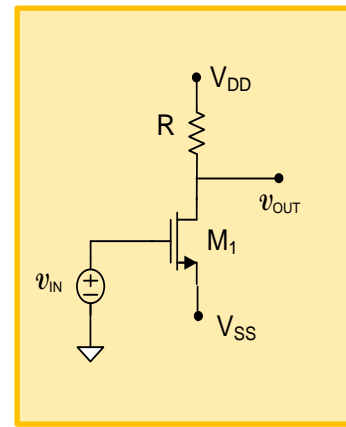

$$A_v = \frac{V_{OUT}}{V_{IN}} = -\frac{g_m}{g_o + 1/R}$$

This gain is expressed in terms of small-signal model parameters

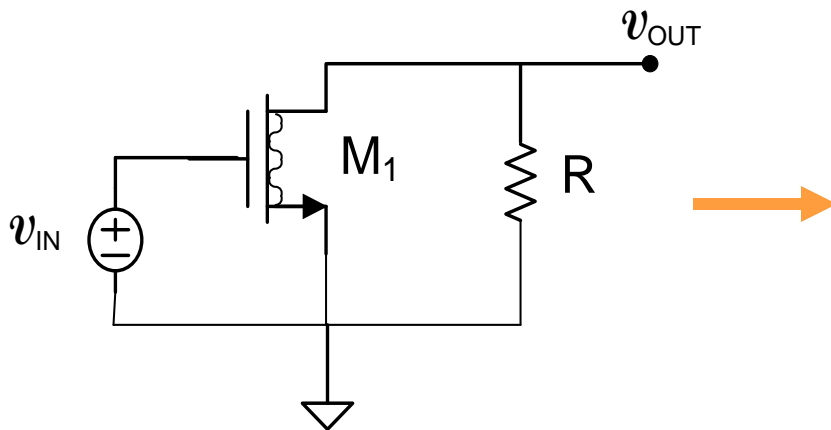For  $\lambda=0$ ,  $g_o = \lambda I_{DQ} = 0$



$$A_v = \frac{v_{OUT}}{v_{IN}} = -g_m R$$

but


$$g_m = \frac{2I_{DQ}}{V_{GSQ} - V_T} \quad V_{GSQ} = -V_{SS}$$

thus

$$A_v = \frac{2I_{DQ} R}{[V_{SS} + V_T]}$$


Consider again:

## Small-signal analysis example

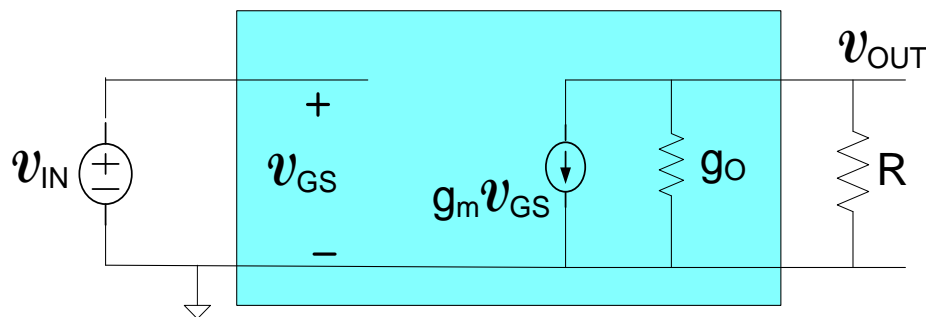

$$A_v = \frac{V_{OUT}}{V_{IN}} = -\frac{g_m}{g_o + 1/R}$$

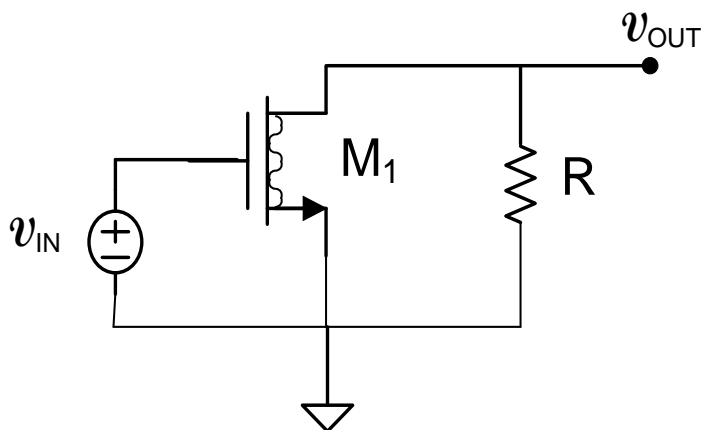For  $\lambda=0$ ,  $g_o = \lambda I_{DQ} = 0$




$$\longrightarrow A_v = \frac{2I_{DQ} R}{[V_{SS} + V_T]}$$

- Same expression as derived before !
- More accurate gain can be obtained if  $\lambda$  effects are included and does not significantly increase complexity of small-signal analysis

# Small Signal Model of BJT



*3-terminal device*

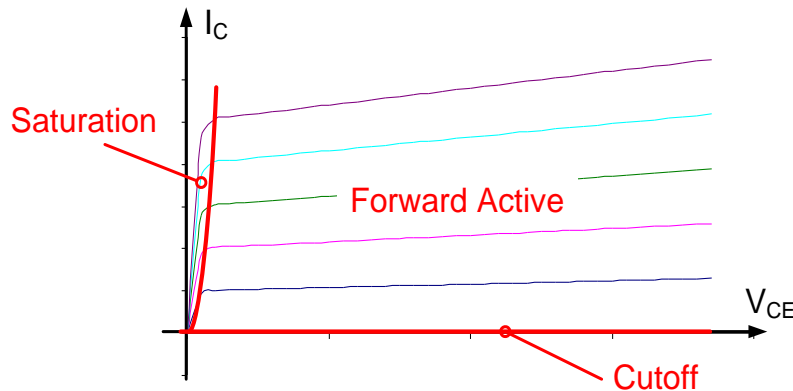

*Forward Active Model:*


$$I_C = J_S A_E e^{\frac{V_{BE}}{V_t}} \left( 1 + \frac{V_{CE}}{V_{AF}} \right)$$

$$I_B = \frac{J_S A_E}{\beta} e^{\frac{V_{BE}}{V_t}}$$

- Usually operated in Forward Active Region when small-signal model is needed
- Will develop small-signal model in Forward Active Region

# Small Signal Model of BJT

*Nonlinear model:*

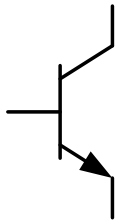

$$I_1 = f_1(V_1, V_2)$$




$$I_B = \frac{J_S A_E}{\beta} e^{\frac{V_{BE}}{V_t}}$$

$$I_2 = f_2(V_1, V_2)$$



$$I_C = J_S A_E e^{\frac{V_{BE}}{V_t}} \left( 1 + \frac{V_{CE}}{V_{AF}} \right)$$

*Small-signal model:*

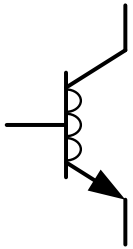

$$i_B = y_{11} v_{BE} + y_{12} v_{CE}$$

$$i_C = y_{21} v_{BE} + y_{22} v_{CE}$$

$$y_{ij} = \left. \frac{\partial f_i(V_1, V_2)}{\partial V_j} \right|_{\tilde{V} = \tilde{V}_Q} \quad \text{y-parameter model}$$

$$y_{11} = g_{\pi} = \left. \frac{\partial I_B}{\partial V_{BE}} \right|_{\tilde{V} = \tilde{V}_Q}$$

$$y_{12} = \left. \frac{\partial I_B}{\partial V_{CE}} \right|_{\tilde{V} = \tilde{V}_Q}$$


$$y_{21} = g_m = \left. \frac{\partial I_C}{\partial V_{BE}} \right|_{\tilde{V} = \tilde{V}_Q}$$

$$y_{22} = g_o = \left. \frac{\partial I_C}{\partial V_{CE}} \right|_{\tilde{V} = \tilde{V}_Q}$$

Note:  $g_m$ ,  $g_{\pi}$  and  $g_o$  used for notational consistency with legacy terminology

# Small Signal Model of BJT


Nonlinear model:

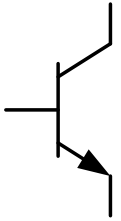

$$I_B = \frac{J_S A_E}{\beta} e^{\frac{V_{BE}}{V_t}}$$

$$I_C = J_S A_E e^{\frac{V_{BE}}{V_t}} \left( 1 + \frac{V_{CE}}{V_{AF}} \right)$$

Small-signal model:

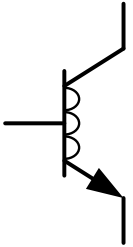

$$i_B = y_{11} v_{BE} + y_{12} v_{CE}$$

$$i_C = y_{21} v_{BE} + y_{22} v_{CE}$$

$$y_{ij} = \left. \frac{\partial f_i(V_1, V_2)}{\partial V_j} \right|_{\tilde{V} = \tilde{V}_Q}$$

$$y_{11} = g_\pi = \left. \frac{\partial I_B}{\partial V_{BE}} \right|_{\tilde{V} = \tilde{V}_Q} = ?$$

$$y_{12} = \left. \frac{\partial I_B}{\partial V_{CE}} \right|_{\tilde{V} = \tilde{V}_Q} = ?$$


$$y_{21} = g_m = \left. \frac{\partial I_C}{\partial V_{BE}} \right|_{\tilde{V} = \tilde{V}_Q} = ?$$

$$y_{22} = g_o = \left. \frac{\partial I_C}{\partial V_{CE}} \right|_{\tilde{V} = \tilde{V}_Q} = ?$$



# Small Signal Model of BJT


Nonlinear model:

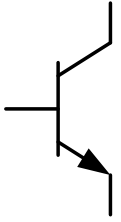

$$I_B = \frac{J_S A_E}{\beta} e^{\frac{V_{BE}}{V_t}}$$

$$I_C = J_S A_E e^{\frac{V_{BE}}{V_t}} \left( 1 + \frac{V_{CE}}{V_{AF}} \right)$$

Small-signal model:

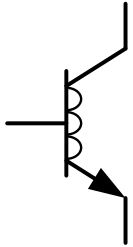

$$i_B = y_{11} v_{BE} + y_{12} v_{CE}$$

$$i_C = y_{21} v_{BE} + y_{22} v_{CE}$$

$$y_{11} = g_\pi = \left. \frac{\partial I_B}{\partial V_{BE}} \right|_{\tilde{V}=\tilde{V}_Q} = \frac{1}{V_t} \frac{J_S A_E}{\beta} e^{\frac{V_{BE}}{V_t}} \Big|_{\tilde{V}=\tilde{V}_Q} = \frac{I_{BQ}}{V_t} \cong \frac{I_{CQ}}{\beta V_t}$$


$$y_{21} = g_m = \left. \frac{\partial I_C}{\partial V_{BE}} \right|_{\tilde{V}=\tilde{V}_Q} = \frac{1}{V_t} J_S A_E e^{\frac{V_{BE}}{V_t}} \left( 1 + \frac{V_{CE}}{V_{AF}} \right) \Big|_{\tilde{V}=\tilde{V}_Q} = \frac{I_{CQ}}{V_t}$$

$$y_{12} = \left. \frac{\partial I_B}{\partial V_{CE}} \right|_{\tilde{V}=\tilde{V}_Q} = 0$$

$$y_{22} = g_o = \left. \frac{\partial I_C}{\partial V_{CE}} \right|_{\tilde{V}=\tilde{V}_Q} = \frac{J_S A_E e^{\frac{V_{BE}}{V_t}}}{V_{AF}} \Big|_{\tilde{V}=\tilde{V}_Q} \cong \frac{I_{CQ}}{V_{AF}}$$

Note: usually prefer to express in terms of  $I_{CQ}$

# Small Signal Model of BJT

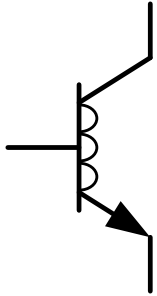

$$\begin{aligned} i_B &= y_{11} v_{BE} + y_{12} v_{CE} \\ i_C &= y_{21} v_{BE} + y_{22} v_{CE} \end{aligned}$$




$$\begin{aligned} i_B &= g_\pi v_{BE} \\ i_C &= g_m v_{BE} + g_o v_{CE} \end{aligned}$$

$$g_\pi = \frac{I_{CQ}}{\beta V_t}$$

$$g_m = \frac{I_{CQ}}{V_t}$$

$$g_o = \frac{I_{CQ}}{V_{AF}}$$

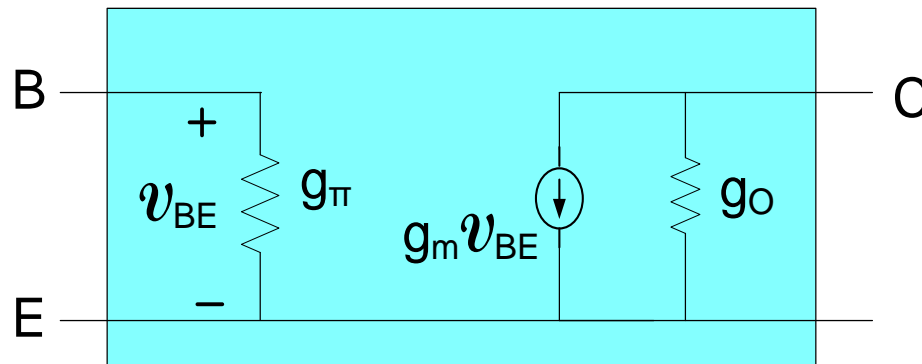


An equivalent circuit

y-parameter model using “g” parameter notation

Consider again:


# Small signal analysis example

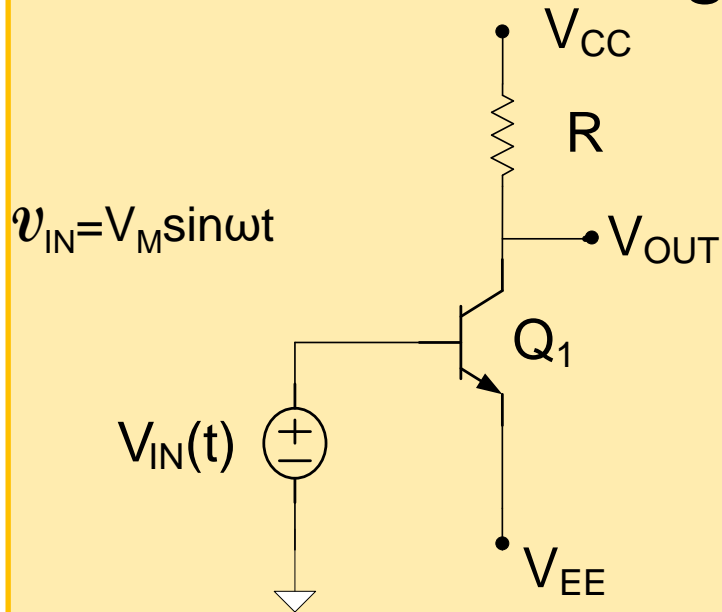

$$A_{vB} = -\frac{I_{CQ} R}{V_t}$$



Derived for  $V_{AF}=0$  (equivalently  $g_o=0$ )

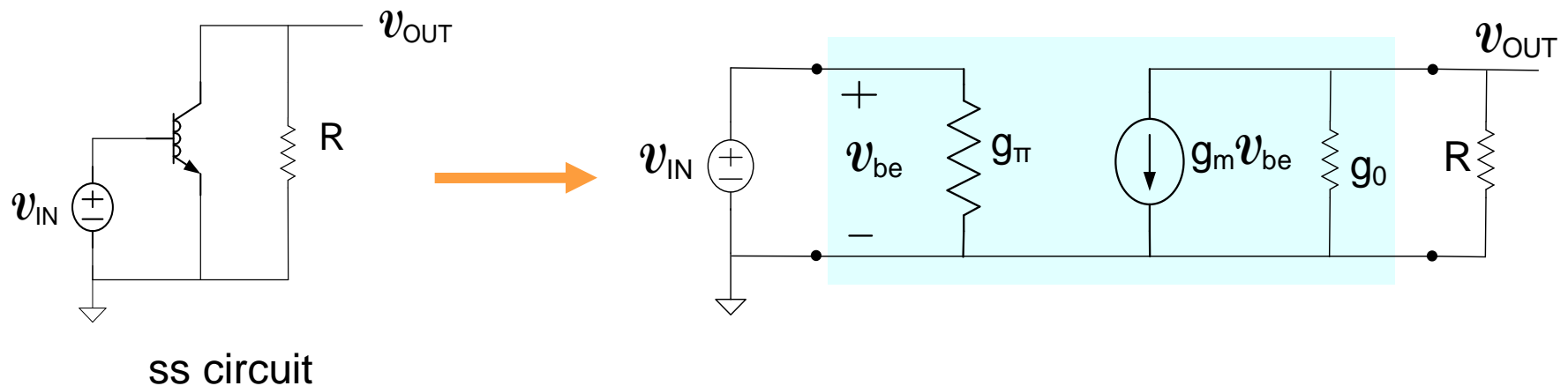Recall the derivation was very tedious and time consuming!



Neglect  $V_{AF}$  effects (i.e.  $V_{AF} = \infty$ ) to be consistent with earlier analysis

$$g_o = \frac{I_{CQ}}{V_{AF}} \Big|_{V_{AF} = \infty} = 0$$

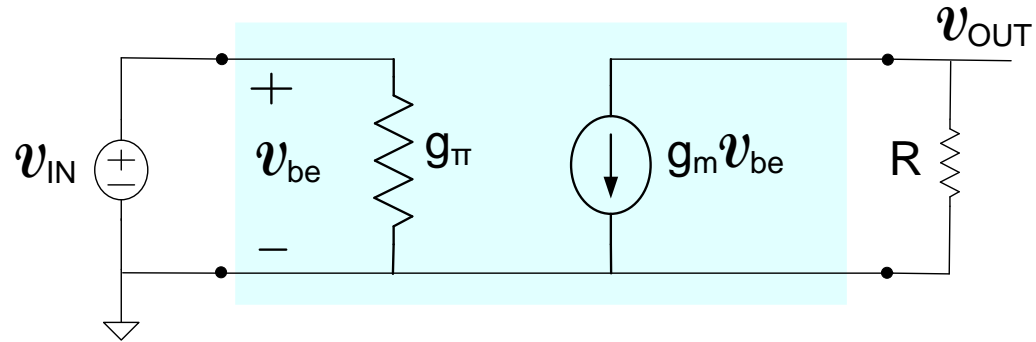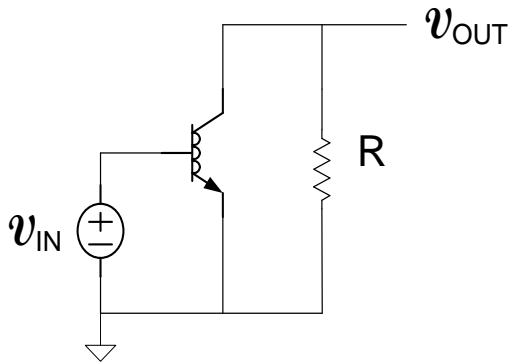

$$\left. \begin{aligned} v_{OUT} &= -g_m R v_{BE} \\ v_{IN} &= v_{BE} \end{aligned} \right\}$$


$$A_V = \frac{v_{OUT}}{v_{IN}} = -g_m R$$

$$g_m = \frac{I_{CQ}}{V_t}$$

$$A_V = -\frac{I_{CQ} R}{V_t}$$

Note this is identical to what was obtained with the direct nonlinear analysis
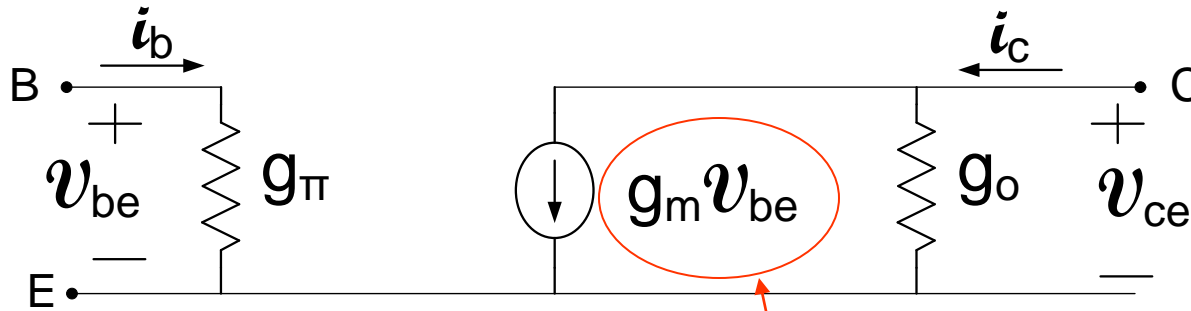
# Small Signal BJT Model – alternate representation



$$g_m = \frac{I_{CQ}}{V_t}$$

$$g_{\pi} = \frac{I_{CQ}}{\beta V_t}$$

$$g_o \cong \frac{I_{CQ}}{V_{AF}}$$


Observe :

$$g_{\pi} v_{be} = i_b$$

$$g_m v_{be} = i_b \frac{g_m}{g_{\pi}}$$


$$\frac{g_m}{g_{\pi}} = \frac{\left[ \frac{I_Q}{V_t} \right]}{\left[ \frac{I_Q}{\beta V_t} \right]} = \beta$$

$$g_m v_{be} = \beta i_b$$

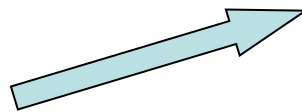

Can replace the voltage dependent current source with a current dependent current source
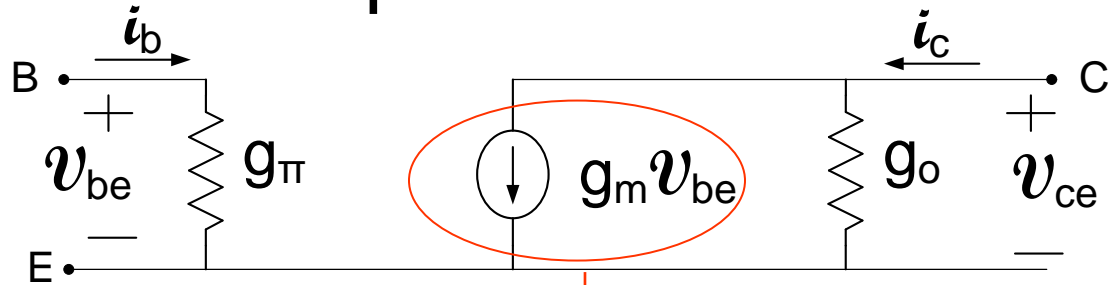
# Small Signal BJT Model – alternate representation




$$g_m = \frac{I_{CQ}}{V_t}$$

$$g_\pi = \frac{I_{CQ}}{\beta V_t}$$

$$g_o \cong \frac{I_{CQ}}{V_{AF}}$$

Alternate equivalent small signal model

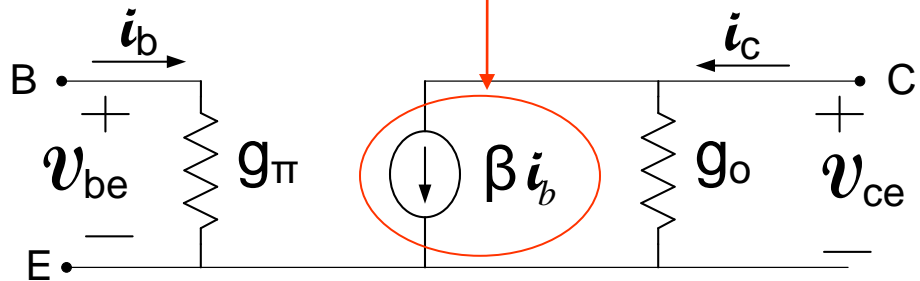


$$g_\pi = \frac{I_{CQ}}{\beta V_t}$$

$$g_o \cong \frac{I_{CQ}}{V_{AF}}$$

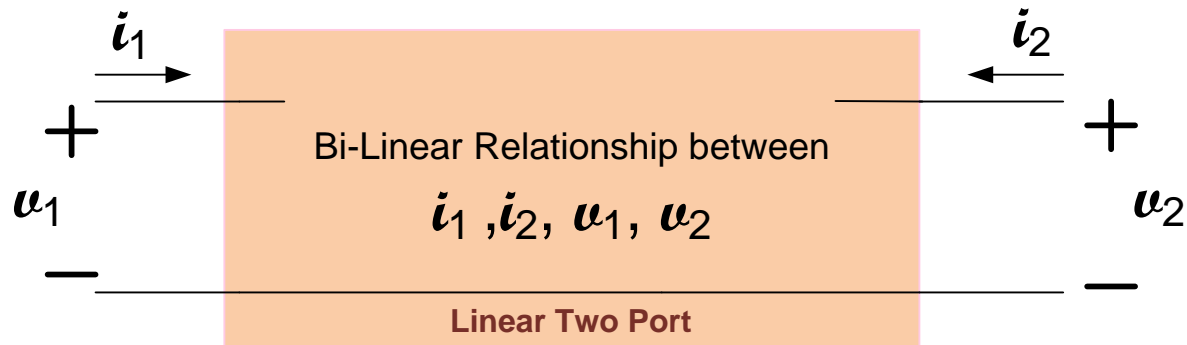
# Small-Signal Model Representations

(3-terminal network – also relevant with 4-terminal networks)





- Have developed small-signal models for the MOSFET and BJT
- Models have been based upon arbitrary assumption that  $u_1, u_2$  are independent variables
- Models are y-parameter models expressed in terms of “g” parameters
- Have already seen some alternatives for “parameter” definitions in these models
- Alternative representations are sometimes used

# Small-Signal Model Representations


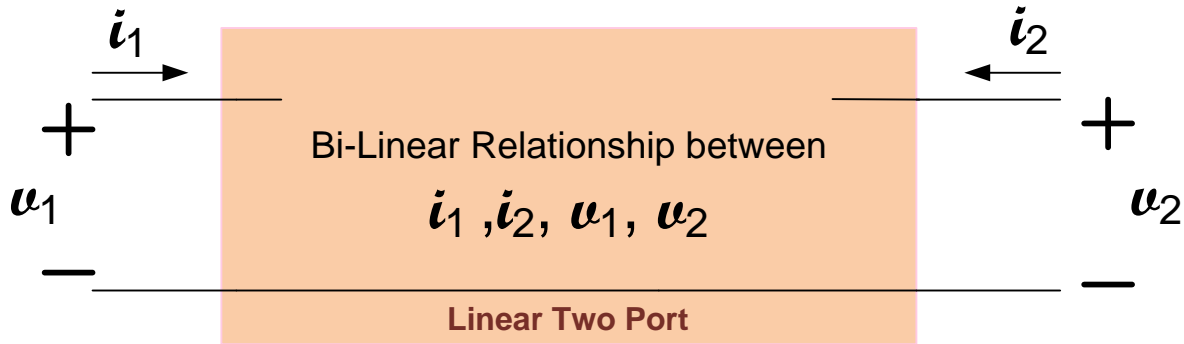


The good, the bad, and the unnecessary !!

what we have developed:

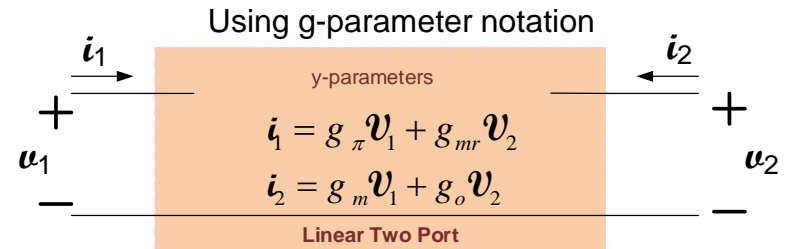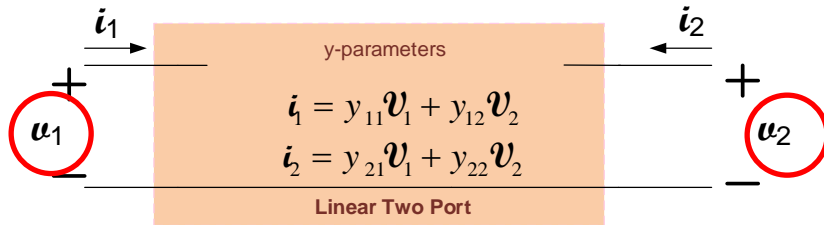


The hybrid parameters:

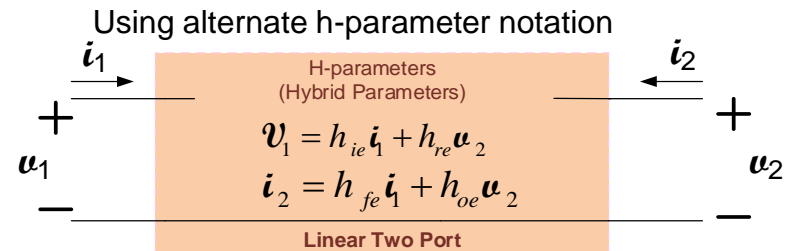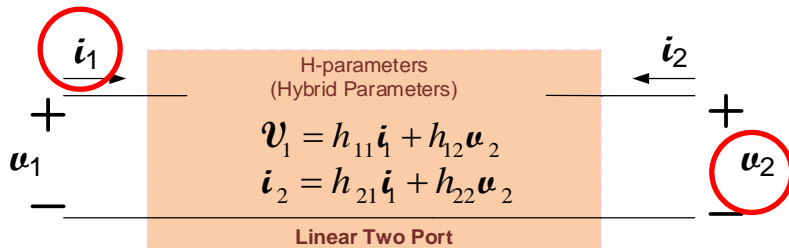


Independent parameters 




# Small-Signal Model Representations

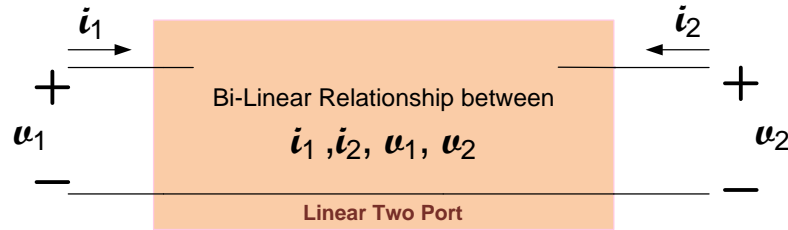


## The z-parameters

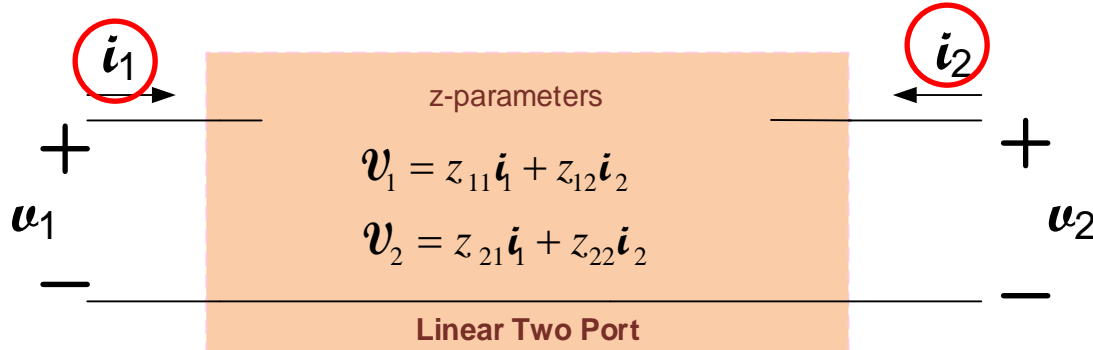


## The ABCD parameters:

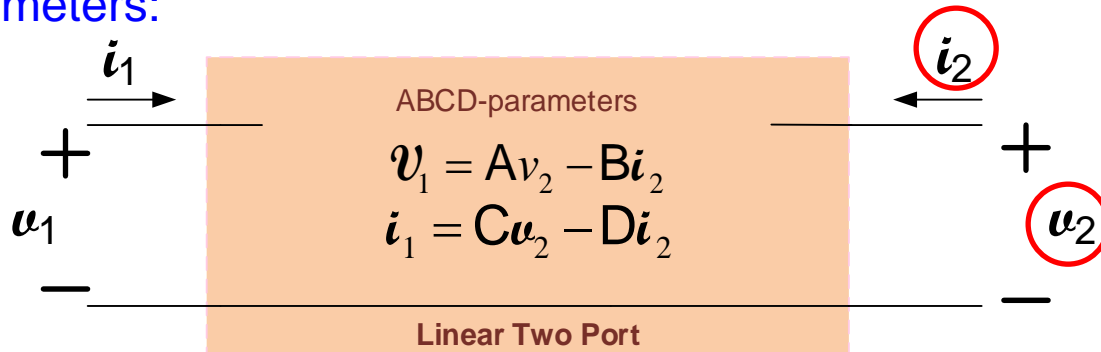

# Small-Signal Model Representations

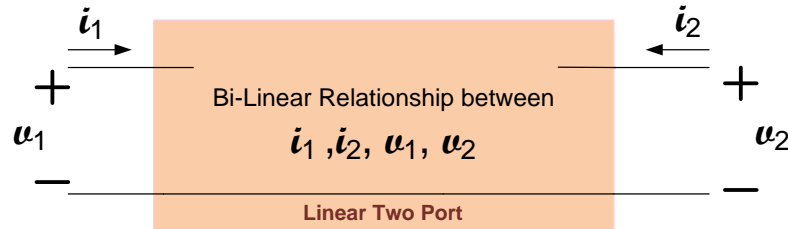


## Amplifier parameters

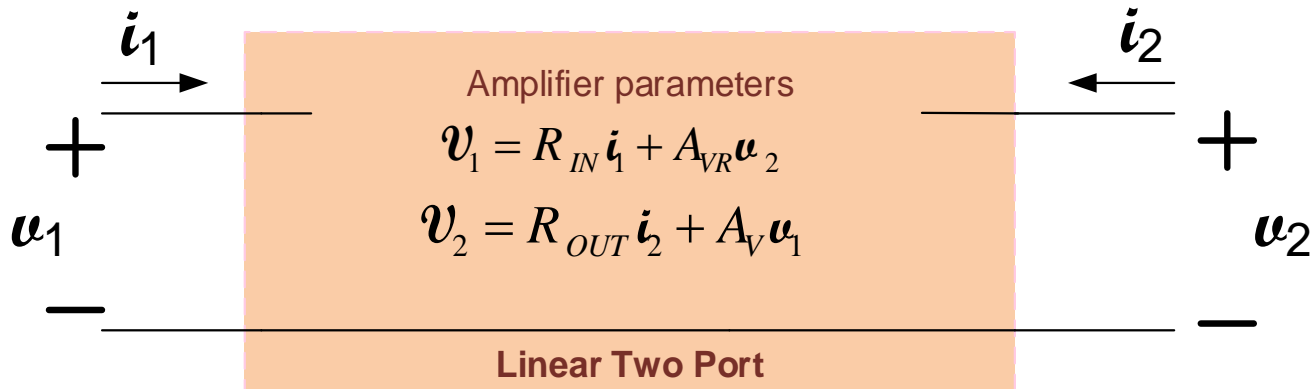


- Alternate two-port characterization but not expressed in terms of independent and dependent parameters
- Widely used notation when designing amplifiers

# Small-Signal Model Representations

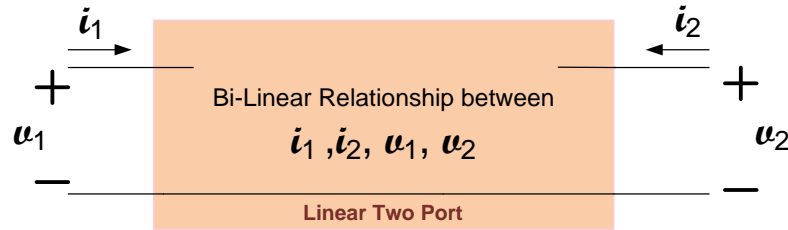


## The S-parameters

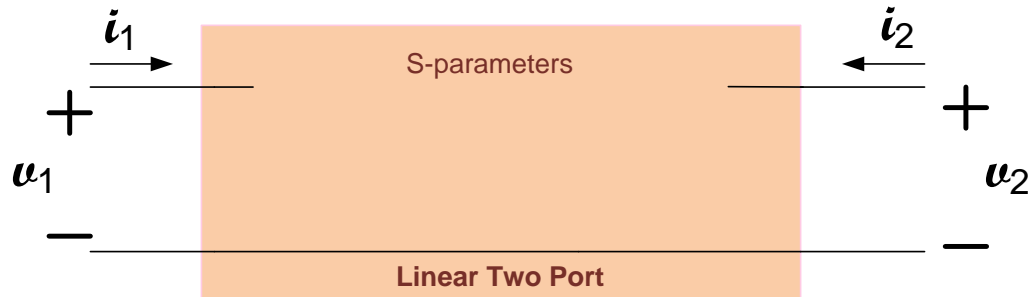


(embedded with source and load impedances)

## The T parameters:









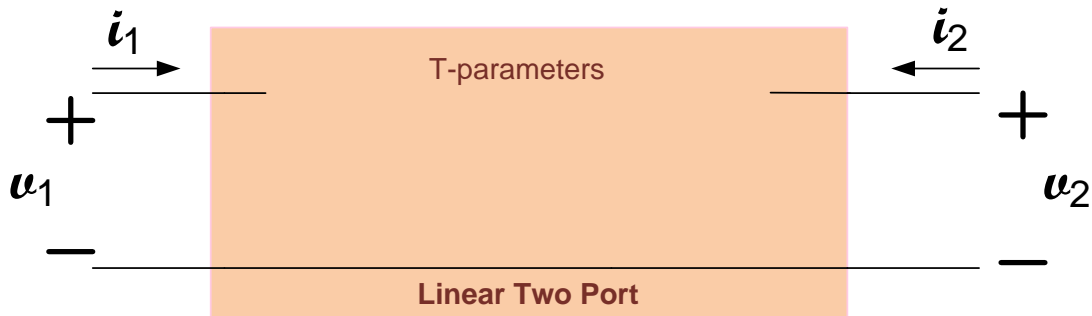


(embedded with source and load impedances)

# Small-Signal Model Representations

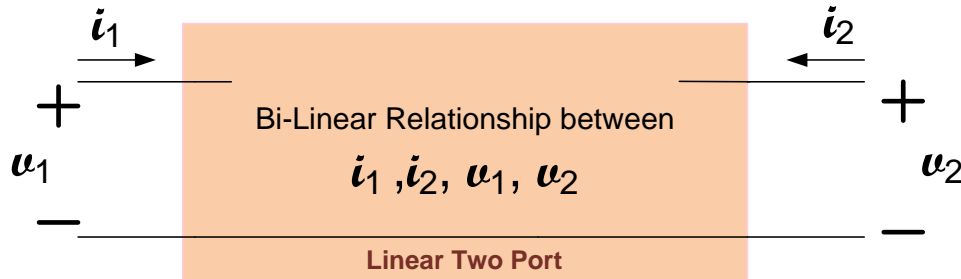


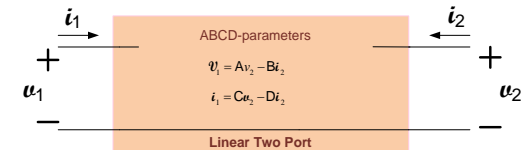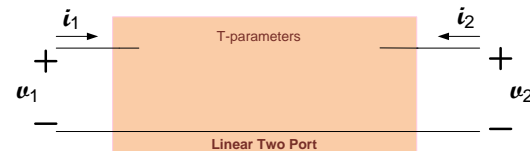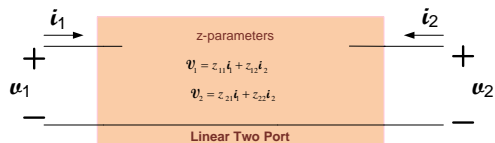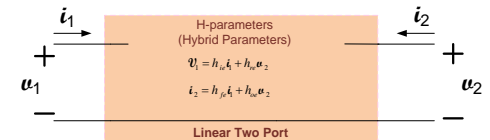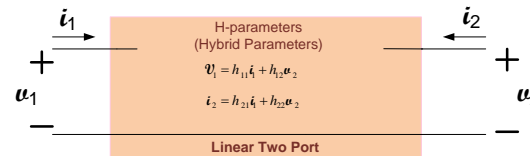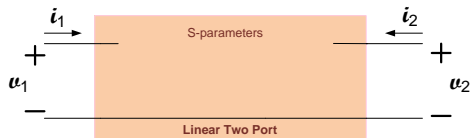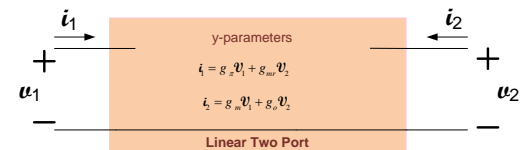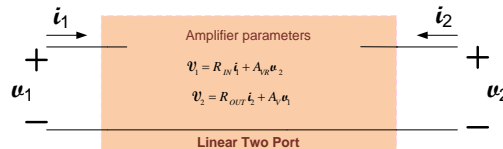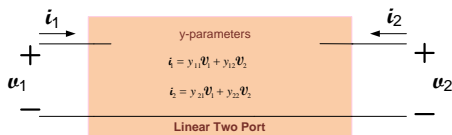The good, the bad, and the **unnecessary** !!



- Equivalent circuits often given for each representation
- All provide identical characterization
- Easy to move from any one to another

# Small-Signal Model Representations

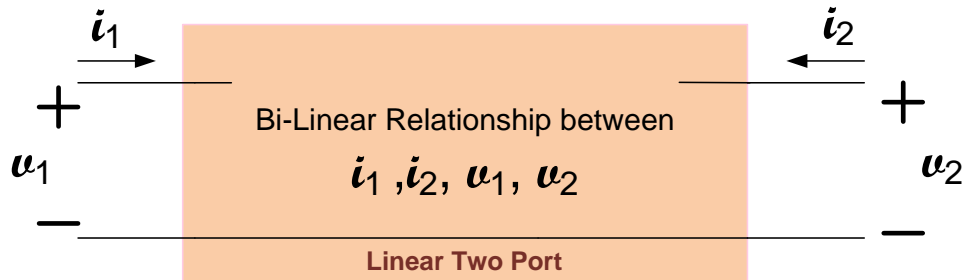

The good, the bad, and the **unnecessary** !!

IEEE TRANSACTIONS ON MICROWAVE THEORY AND TECHNIQUES, VOL. 42, NO. 2, FEBRUARY 1994

## Conversions Between $S$ , $Z$ , $Y$ , $h$ , $ABCD$ , and $T$ Parameters which are Valid for Complex Source and Load Impedances

Dean A. Frickey, *Member, IEEE*

Conversions **between S, Z, Y, H, ABCD**, and T parameters which are valid for complex source and load impedances


[DA Frickey - IEEE Transactions on microwave theory and ..., 1994 - ieeexplore.ieee.org](#)

... 2. FEBRUARY 1994 TABLE of EQUATIONS FOR THE **CONVERSION BETWEEN** s PARAMETERS

AND NORMALIZED Z, Y, h ... V. CONCLUSION This paper developed the equations for **conversion between** the various common 2-port parameters, Z, Y, h, ABCD, S, and T ...

☆ [Cited by 575](#) Related articles All 7 versions

# Small-Signal Model Representations

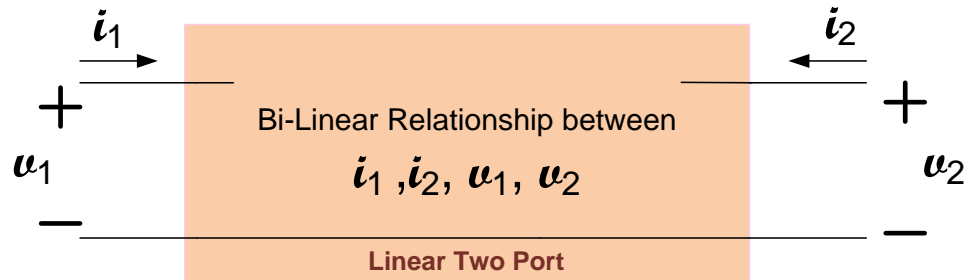

The good, the bad, and the **unnecessary** !!

IEEE TRANSACTIONS ON MICROWAVE THEORY AND TECHNIQUES, VOL. 42, NO. 2, FEBRUARY 1994

## Conversions Between $S$ , $Z$ , $Y$ , $h$ , $ABCD$ , and $T$ Parameters which are Valid for Complex Source and Load Impedances


Conversions **between**  $S$ ,  $Z$ ,  $Y$ ,  $H$ ,  $ABCD$ , and  $T$  parameters which are valid for complex source and load impedances

DA Frickey - IEEE Transactions on microwave theory and ..., 1994 - [ieeexplore.ieee.org](http://ieeexplore.ieee.org)

This paper provides tables which contain the conversion between the various common two-port parameters,  $Z$ ,  $Y$ ,  $H$ ,  $ABCD$ ,  $S$ , and  $T$ . The conversions are valid for complex normalizing impedances. An example is provided which verifies the conversions to and from  $S$

☆ 99 Cited by 370 Related articles All 5 versions

# Small-Signal Model Representations

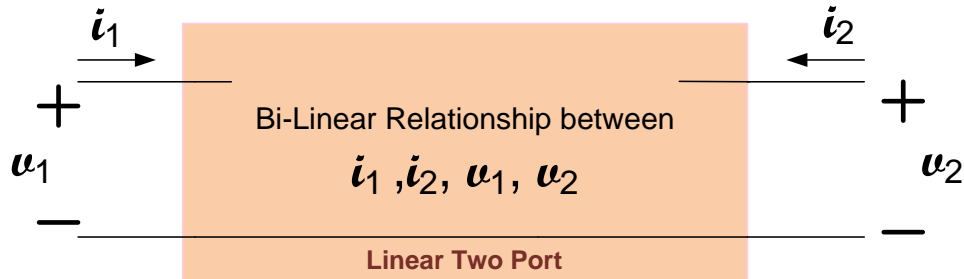

The good, the bad, and the **unnecessary** !!

IEEE TRANSACTIONS ON MICROWAVE THEORY AND TECHNIQUES, VOL. 42, NO. 2, FEBRUARY 1994

## Conversions Between $S$ , $Z$ , $Y$ , $h$ , $ABCD$ , and $T$ Parameters which are Valid for Complex Source and Load Impedances

Dean A. Frickey, *Member, IEEE*

[Conversions between  \$S\$ ,  \$Z\$ ,  \$Y\$ ,  \$H\$ ,  \$ABCD\$ , and  \$T\$  parameters which are valid for complex source and load impedances](#)

DA Frickey - IEEE Transactions on Microwave Theory and ..., 1994 - osti.gov

**Conversions between  $S$ ,  $Z$ ,  $Y$ ,  $h$ ,  $ABCD$ , and  $T$  parameters** which are valid for complex source and load impedances This paper provides tables which contain the **conversion between** the various common two-port parameters,  $Z$ ,  $Y$ ,  $h$ ,  $ABCD$ ,  $S$ , and  $T$ . The ...

[Cited by 226](#) [Related articles](#) [All 6 versions](#) [Cite](#) [Save](#) [More](#)

Comments on "[Conversions between  \$S\$ ,  \$Z\$ ,  \$Y\$ ,  \$h\$ ,  \$ABCD\$ , and  \$T\$  parameters which are valid for complex source and load impedances](#)"[with reply]


[nist.gov \[PDF\]](#)

..., DF Williams, DA Frickey - Microwave Theory and ..., 1995 - ieeexplore.ieee.org

In his recent paper, Frickey presents formulas for **conversions between** various network matrices. Four of these matrices ( $Z$ ,  $Y$ ,  $h$ , and  $ABCD$ ) relate voltages and currents at the ports; the other two ( $S$  and  $T$ ) relate wave quantities. These relationships depend on the ...

[Cited by 30](#) [Related articles](#) [All 3 versions](#) [Cite](#) [Save](#)

# Small-Signal Model Representations

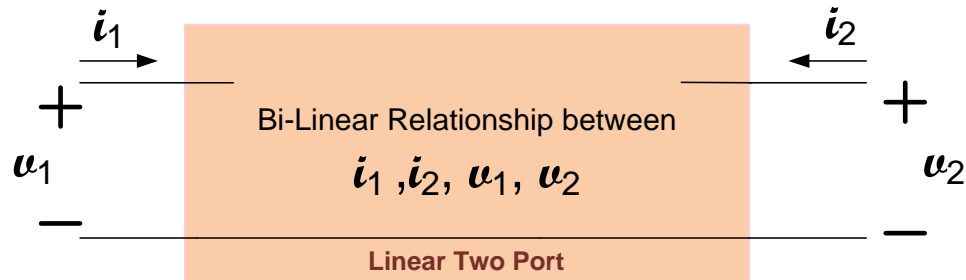

The good, the bad, and the **unnecessary** !!

IEEE TRANSACTIONS ON MICROWAVE THEORY AND TECHNIQUES, VOL. 42, NO. 2, FEBRUARY 1994

## Conversions Between $S$ , $Z$ , $Y$ , $h$ , $ABCD$ , and $T$ Parameters which are Valid for Complex Source and Load Impedances

Dean A. Frickey, *Member, IEEE*

[Conversions between S, Z, Y, H, ABCD, and T parameters which are valid for complex source and load impedances](#)

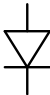

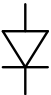
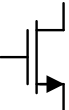
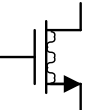
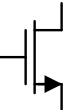
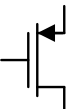
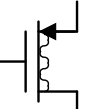
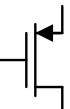
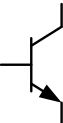
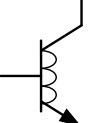
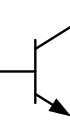
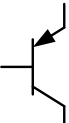
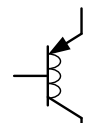

DA Frickey - ... theory and techniques, IEEE Transactions on, 1994 - [ieeexplore.ieee.org](http://ieeexplore.ieee.org)

Abstract This paper provides tables which contain the **conversion between** the various common two-port parameters, Z, Y, H, ABCD, S, and T. The **conversions** are valid for complex normalizing impedances. An example is provided which verifies the **conversions** ...

[Cited by 149](#) [Related articles](#) [All 5 versions](#) [Cite](#)



# Active Device Model Summary










	Element	ss equivalent	dc equivalent
Diodes			 Simplified
MOS transistors			 Simplified
			 Simplified
Bipolar Transistors			 Simplified
			 Simplified

What are the simplified dc equivalent models?


# Active Device Model Summary

What are the simplified dc equivalent models?

dc equivalent

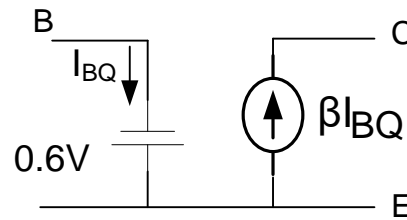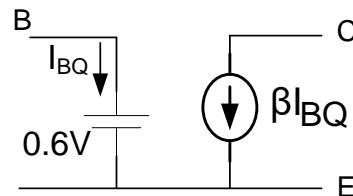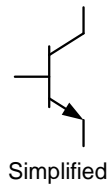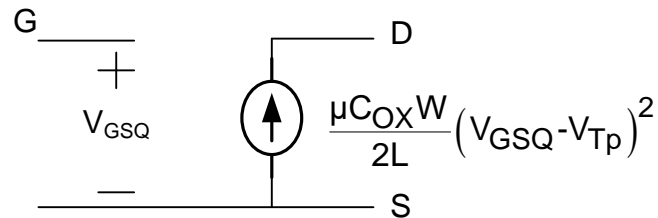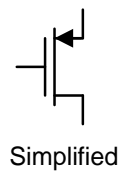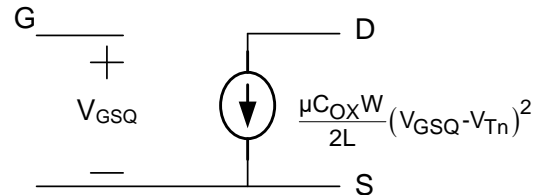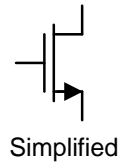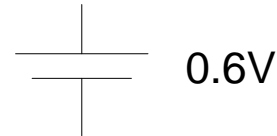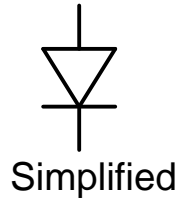

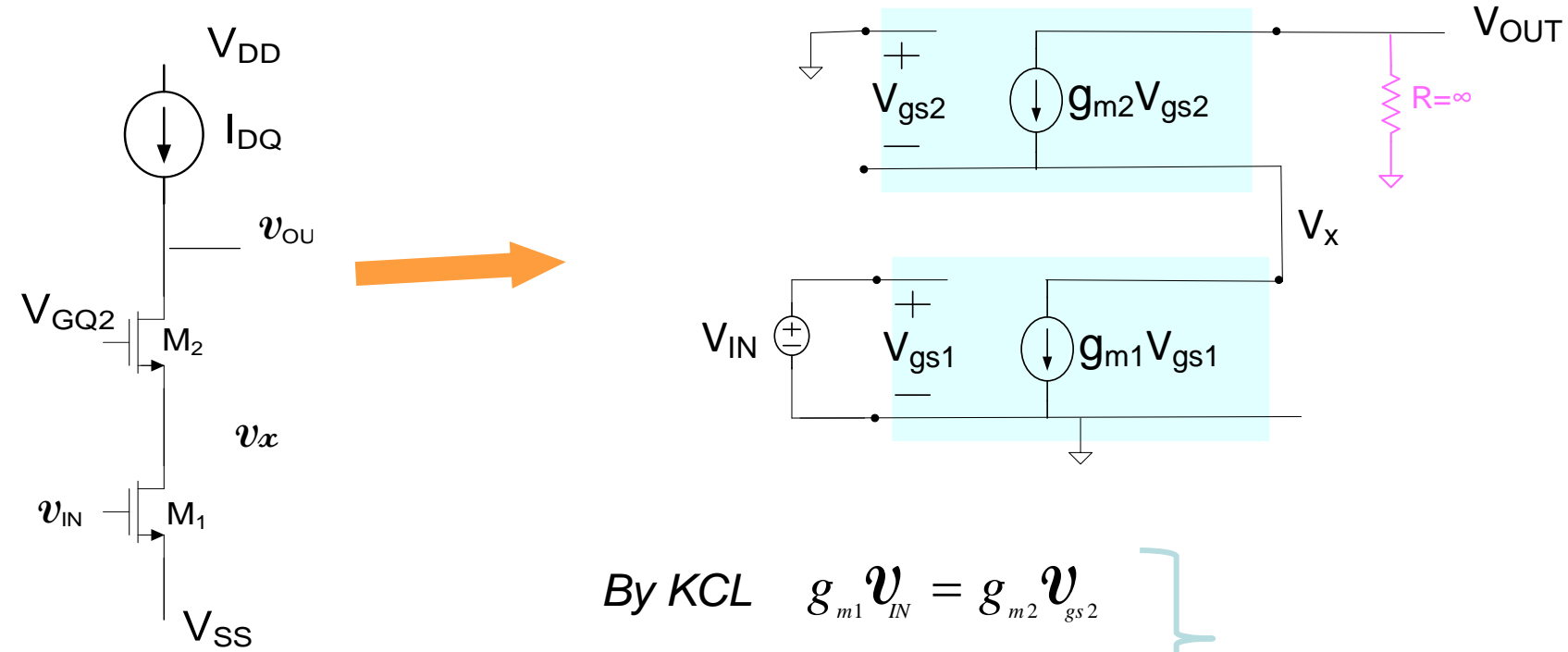Example: Determine the small signal voltage gain  $A_V = v_{OUT}/v_{IN}$ . Assume  $M_1$  and  $M_2$  are operating in the saturation region and that  $\lambda=0$



By KCL


$$\left. \begin{aligned} g_{m1} v_{IN} &= g_{m2} v_{gs2} \\ g_{m2} v_{gs2} &= -v_{OUT} \end{aligned} \right\}$$

Solving obtain:

$$A_V = \frac{v_{OUT}}{v_{IN}} = -g_{m1} R \xrightarrow{R=\infty} \infty$$

Unexpectedly large, need better device models!

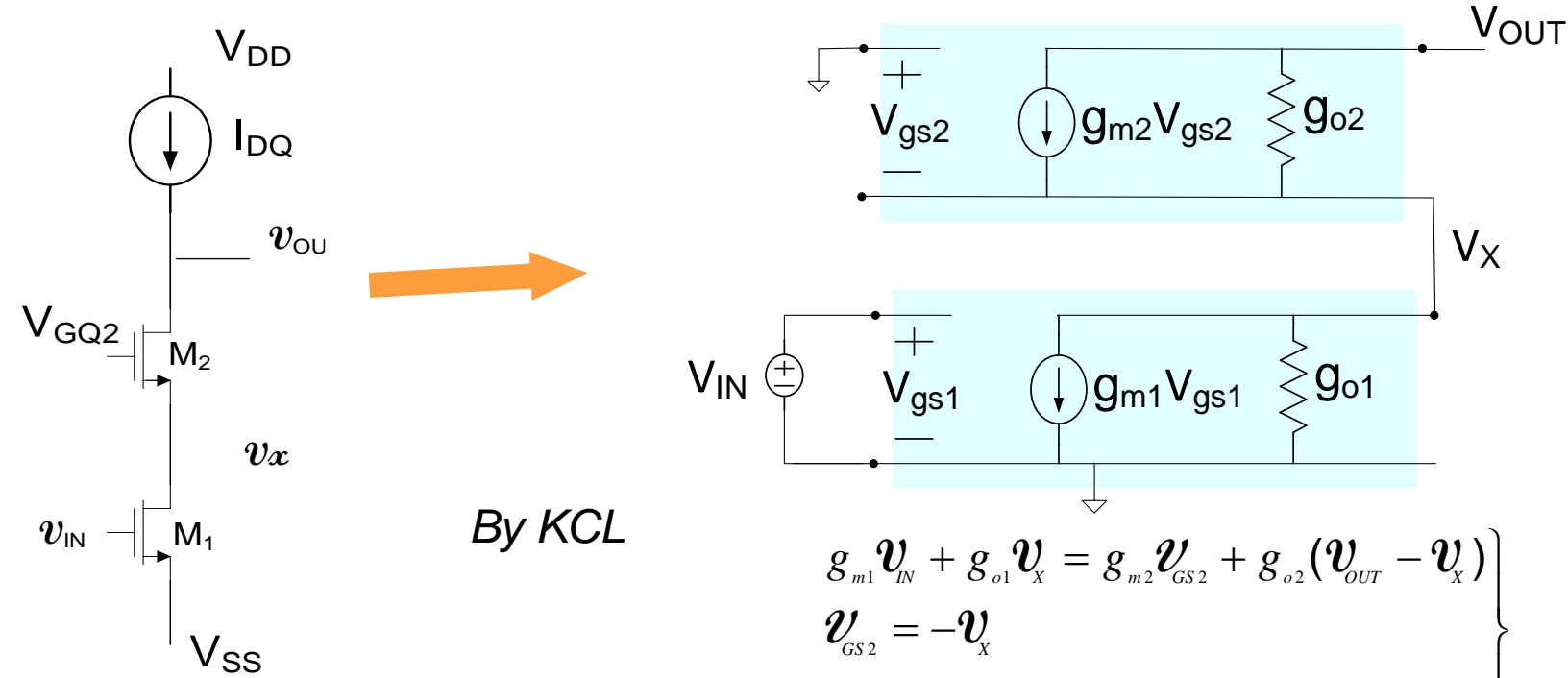Example: Determine the small signal voltage gain  $A_V = v_{OUT}/v_{IN}$ . Assume  $M_1$  and  $M_2$  are operating in the saturation region and that  $\lambda \neq 0$



By KCL

$$\left. \begin{aligned} g_{m1} v_{IN} + g_{o1} v_X &= g_{m2} v_{GS2} + g_{o2} (v_{OUT} - v_X) \\ v_{GS2} &= -v_X \\ (v_{OUT} - v_X) g_{o2} + g_{m2} v_{GS2} &= 0 \end{aligned} \right\}$$

$$\left. \begin{aligned} g_{m1} v_{IN} + (g_{m2} + g_{o1} + g_{o2}) v_X &= g_{o2} v_{OUT} \\ v_{OUT} g_{o2} &= (g_{m2} + g_{o2}) v_X \end{aligned} \right\}$$


thus:

$$A_V = \frac{v_{OUT}}{v_{IN}} = - \frac{g_{m1} g_{m2} + g_{m1} g_{o2}}{g_{o1} g_{o2}} \cong - \frac{g_{m1}}{g_{o1}} \frac{g_{m2}}{g_{o2}}$$

- Analysis is straightforward but a bit tedious
- $A_V$  is very large and would go to  $\infty$  if  $g_{o1}$  and  $g_{o2}$  were both 0
- Will look at how big this gain really is later

# Graphical Analysis and Interpretation

Consider Again

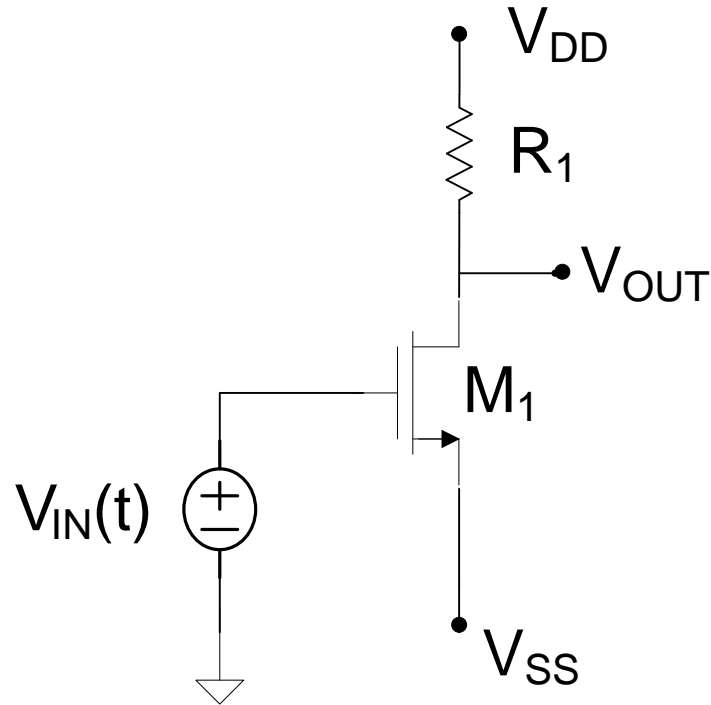



$$V_{OUT} = V_{DD} - I_D R$$

$$I_D = \frac{\mu C_{OX} W}{2L} (V_{IN} - V_{SS} - V_T)^2$$

$$I_{DQ} = \frac{\mu C_{OX} W}{2L} (V_{SS} + V_T)^2$$
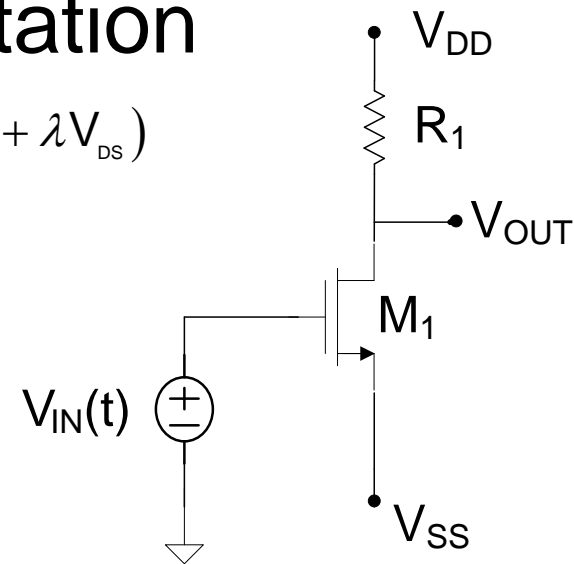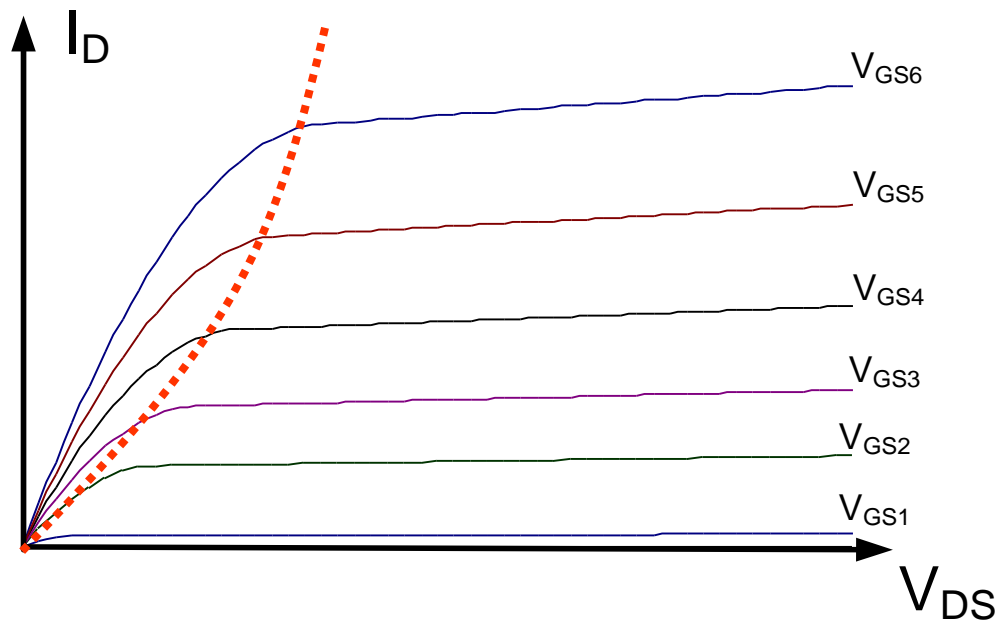
# Graphical Analysis and Interpretation

Device Model (family of curves)  $I_D = \frac{\mu C_{ox} W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$



Load Line ←


$$V_{OUT} = V_{DD} - I_D R$$

Device Model ←

$$I_D = \frac{\mu C_{ox} W}{2L} (V_{IN} - V_{SS} - V_T)^2$$


Device Model at Operating Point ←
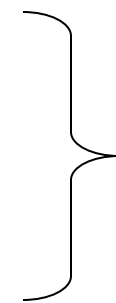
$$I_{DQ} = \frac{\mu C_{ox} W}{2L} (V_{SS} + V_T)^2$$


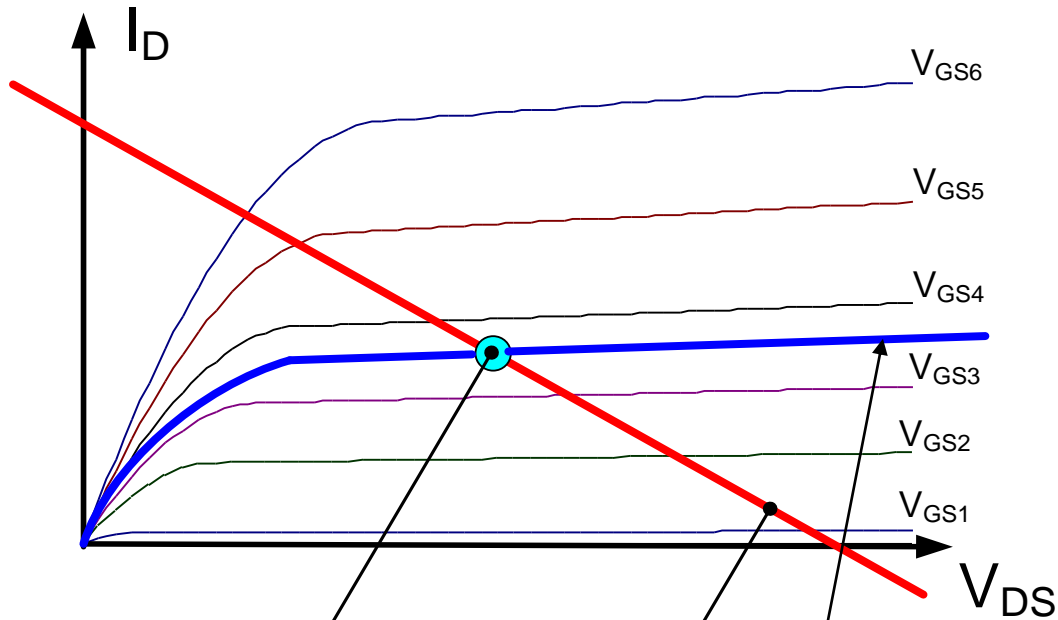
# Graphical Analysis and Interpretation

Device Model (family of curves)  $I_D = \frac{\mu C_{ox} W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$



$$V_{GSQ} = -V_{SS}$$


$$I_{DQ} \cong \frac{\mu C_{ox} W}{2L} (V_{SS} + V_T)^2$$

$$V_{GSQ} = -V_{SS}$$

$$V_{OUT} = V_{DD} - I_D R$$

$$I_D = \frac{\mu C_{ox} W}{2L} (V_{IN} - V_{SS} - V_T)^2 \quad ?$$

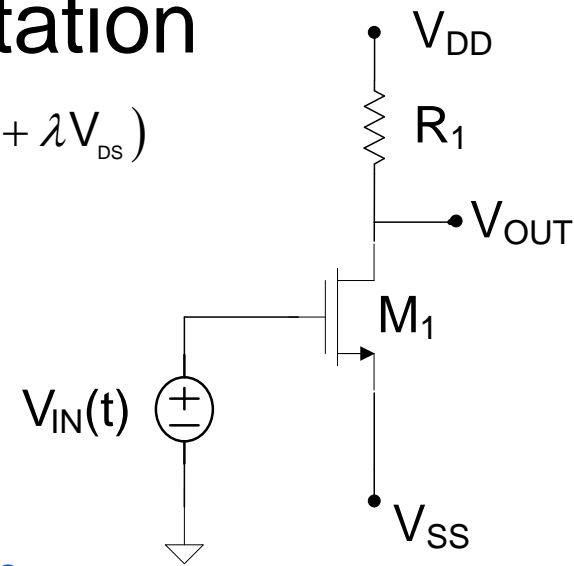Must satisfy both equations all of the time !








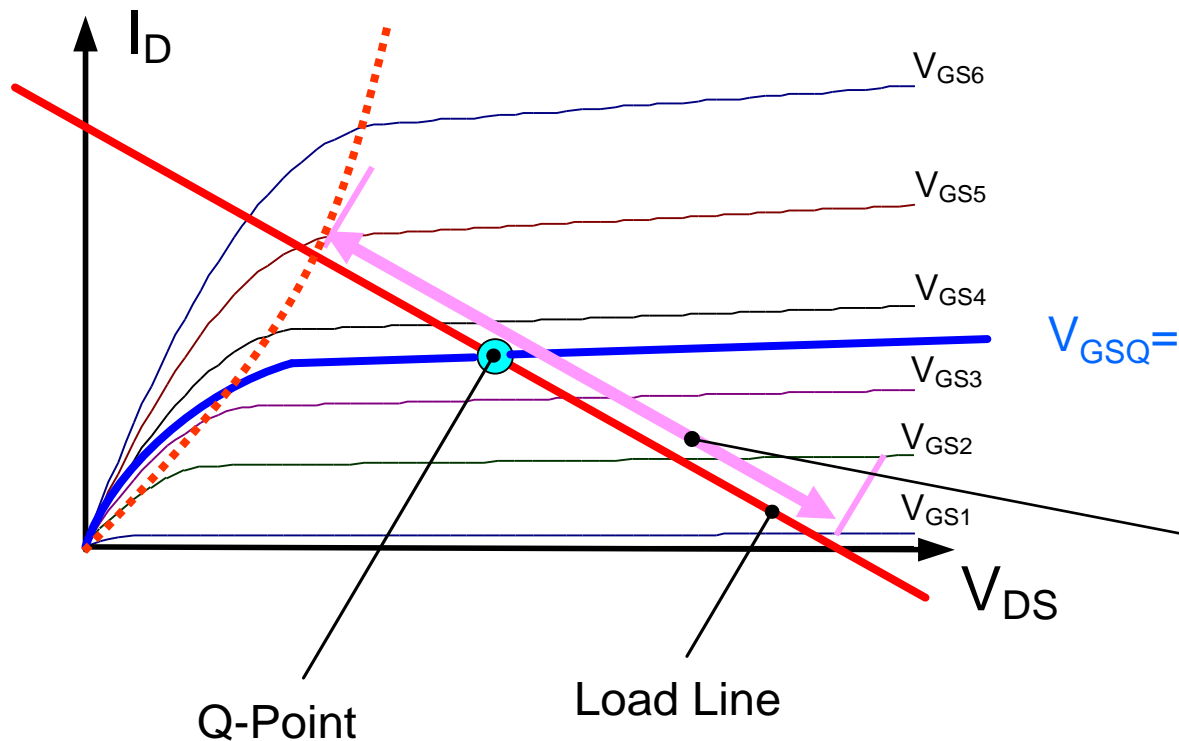
# Graphical Analysis and Interpretation

Device Model (family of curves)  $I_D = \frac{\mu C_{ox} W}{2L} (V_{IN} - V_{SS} - V_T)^2 (1 + \lambda V_{DS})$



$$V_{GSQ} = -V_{SS}$$

Saturation region

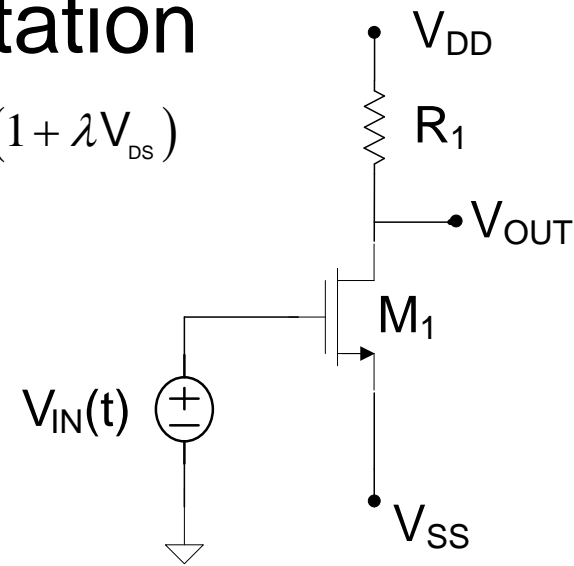



$$I_{DQ} \cong \frac{\mu C_{ox} W}{2L} (V_{SS} + V_T)^2$$

As  $V_{IN}$  changes around Q-point, due to changes  $V_{IN}$  induces in  $V_{GS}$ , the operating point must remain on the load line!


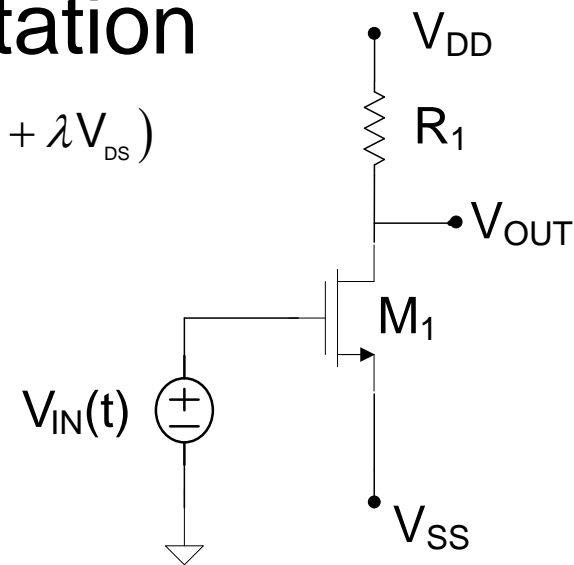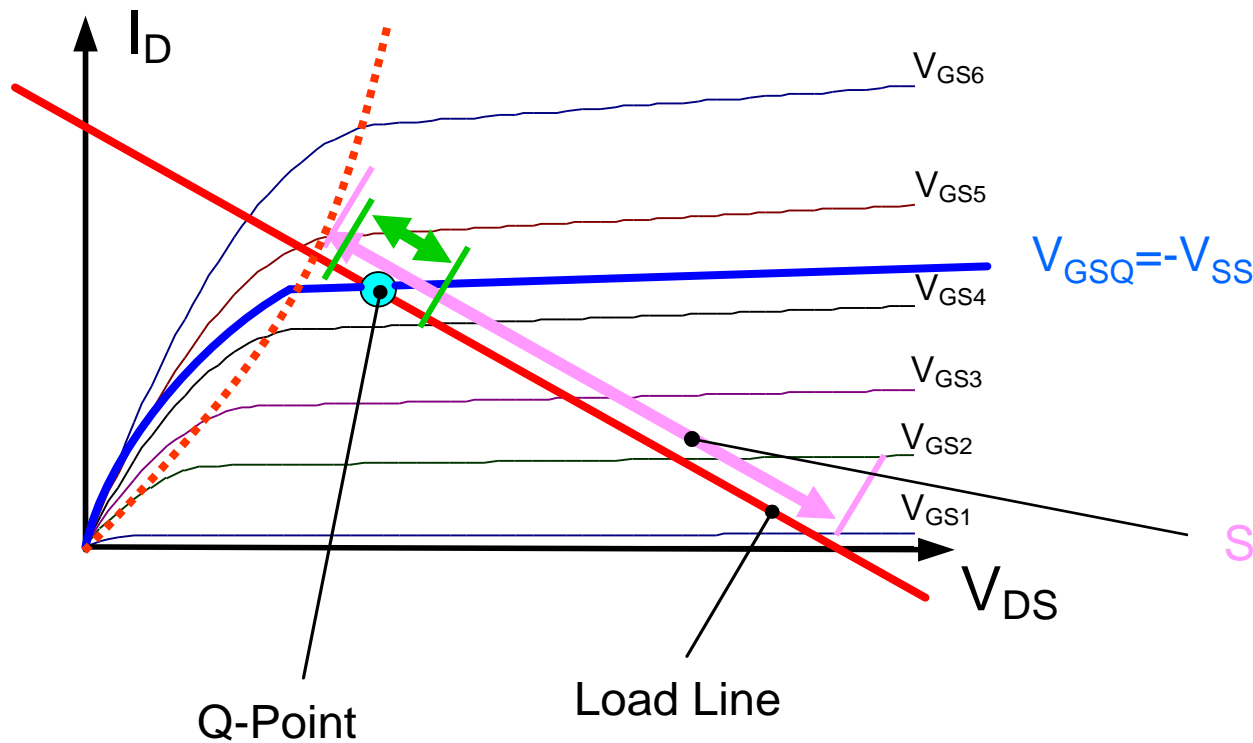
# Graphical Analysis and Interpretation

Device Model (family of curves) 
$$I_{DQ} = \frac{\mu C_{ox} W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$





$$I_{DQ} \cong \frac{\mu C_{ox} W}{2L} (V_{SS} + V_T)^2$$

Very limited signal swing with non-optimal Q-point location
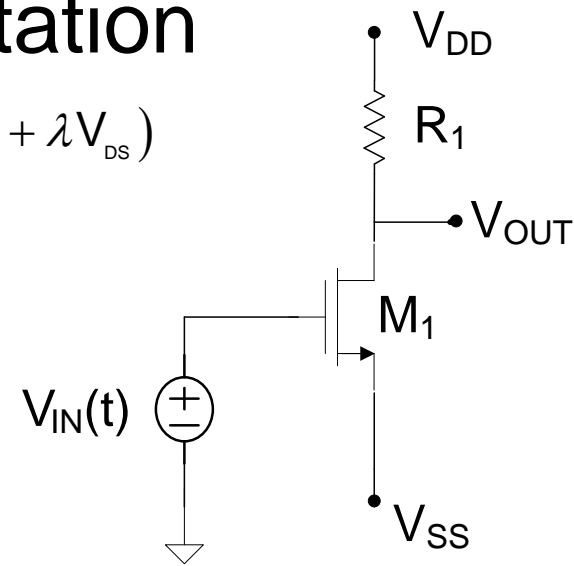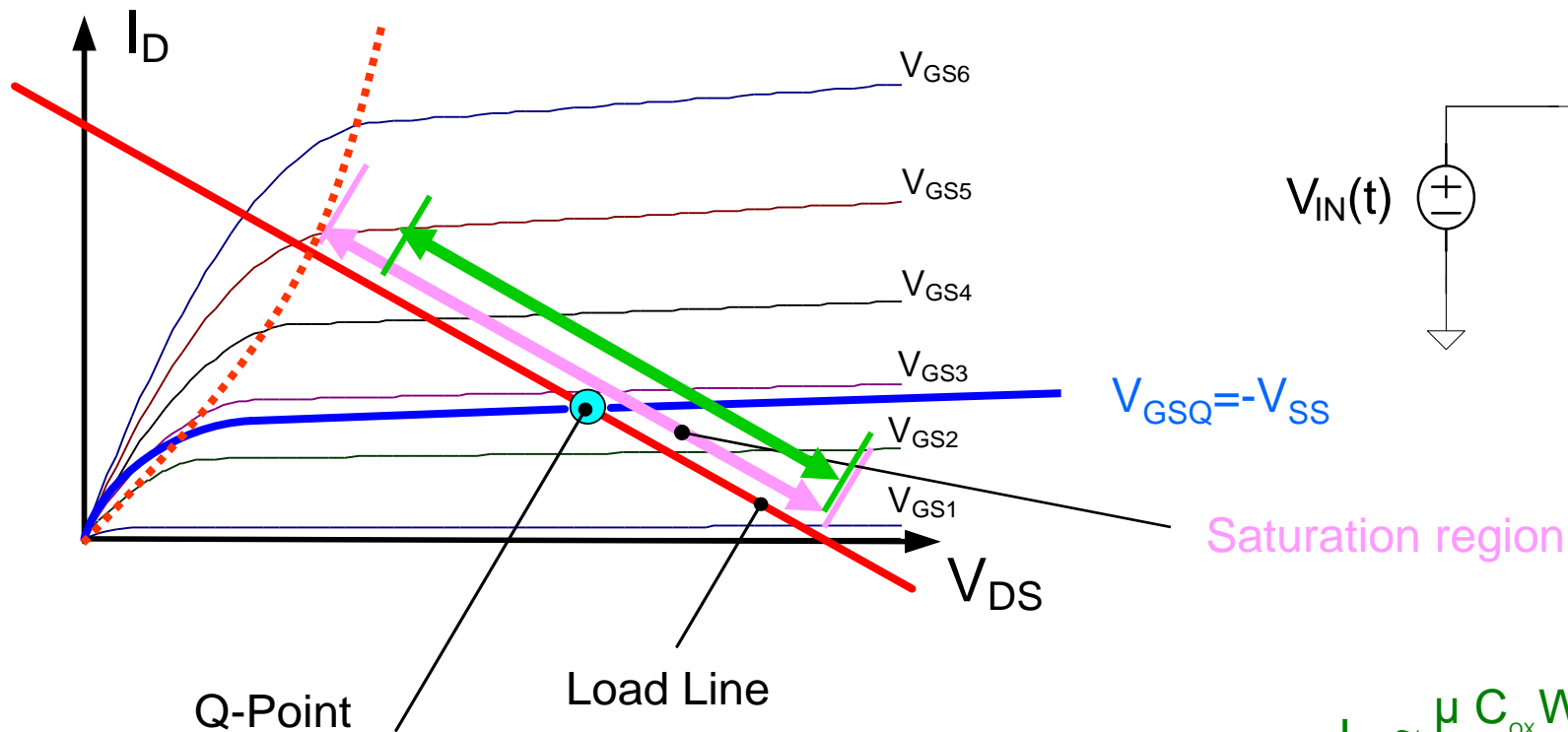
# Graphical Analysis and Interpretation

Device Model (family of curves) 
$$I_{DQ} = \frac{\mu C_{ox} W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$



$$I_{DQ} \cong \frac{\mu C_{ox} W}{2L} (V_{SS} + V_T)^2$$

- Signal swing can be maximized by judicious location of Q-point
- Often selected to be at middle of load line in saturation region



Stay Safe and Stay Healthy !

End of Lecture 25