

# EE 330

## Lecture 29

### Bipolar Processes

- Device Sizes
- Parasitic Devices
  - JFET
  - Thyristors


### Thyristors

- SCR – Basic operation


## Review From Previous Lecture
 
# Two-port representation of amplifiers

- Amplifier often **unilateral** (signal propagates in only one direction:  $y_{12}=0$ )
- One terminal is often common
- “Amplifier” parameters often used




y parameters

 


Amplifier parameters

 - 
- Amplifier parameters can also be used if not **unilateral**
  - One terminal is often common




y parameters

 

Amplifier parameters

# Relationship with Dependent Sources ?

 

Dependent sources from EE 201

Voltage Amplifier

$$v_s = \mu v_x$$

Voltage Dependent Voltage Source

$$I_s = \alpha v_x$$

Voltage Dependent Current Source

Transconductance Amplifier

Transresistance Amplifier

$$v_s = \rho I_x$$

Current Dependent Voltage Source

$$I_s = \beta I_x$$

Current Dependent Current Source

Current Amplifier

# Topical Coverage Change

Will have several additional lectures on amplifier structures but will temporarily suspend discussion of amplifiers to consider Thyristors

This is being done to get ready for the Thyristor laboratory experiments

# Outline


## Bipolar Processes

-  • Parasitic Devices in CMOS Processes
- JFET
- Other Junction Devices


## Special Bipolar Processes

- Thyristors  
SCR  
TRIAC

Review from a Previous Lecture




 


# Review from a Previous Lecture

 

**B-B' Section**



# Review from a Previous Lecture

    




# Review from a Previous Lecture

Diode (capacitor)

  

Resistor

 

p-channel JFET

Will consider next the JFET but first some additional information about MOS Devices

## Enhancement and Depletion MOS Devices

- Enhancement Mode n-channel devices

$$V_T > 0$$

- Enhancement Mode p-channel devices

$$V_T < 0$$


- Depletion Mode n-channel devices

$$V_T < 0$$

- Depletion Mode p-channel devices

$$V_T > 0$$

# Enhancement and Depletion MOS Devices

 

- Depletion mode devices require only one additional mask step
- Older n-mos and p-mos processes usually had a depletion device and an enhancement device
- Depletion devices usually not available in CMOS because applications usually do not justify the small increasing costs in processing
- The threshold voltage of either n-channel or p-channel devices is adjusted to a desired value by doing a channel implant before gate oxide is applied

# Outline

## Bipolar Processes


- Parasitic Devices in CMOS Processes
-  • JFET
- Other Junction Devices

## Special Bipolar Processes

- Thyristors  
SCR  
TRIAC

 
# The JFET

(Parasitic p-channel device in basic bipolar process)




- Gate is both above and below channel
- With no bias, channel exists between D and S

# The JFET

 


With  $V_{GS}=0$ , channel exists under gate between D and S

# The JFET

 


 With  $V_{GS}=0$ , channel exists under gate between D and S




Under small reverse bias (depletion region widens and channel thins)

# The JFET

 

 With  $V_{GS}=0$ , channel exists under gate between D and S




Under sufficiently large reverse bias (depletion region widens and channel disappears - "pinches off")






# The JFET

 

 
With  $V_{GS}=0$ , channel exists under gate between D and S




Under small reverse bias and large negative  $V_{DS}$  (channel pinches off)




# The JFET

 

n-channel

 

p-channel

 

p-channel JFET


## Square-law model of p-channel JFET

$$I_D = \begin{cases} 0 & V_{GS} > V_P \\ \frac{2I_{DSSp}}{V_P^2} \left( V_{GS} - V_P - \frac{V_{DS}}{2} \right) V_{DS} & -0.3 < V_{GS} < V_P \quad V_{GS} + 0.3 > V_{DS} > V_{GS} - V_P \\ I_{DSSp} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 & -0.3 < V_{GS} < V_P \quad V_{DS} < V_{GS} - V_P \end{cases}$$


( $I_{DSSp}$  carries negative sign)

- Functionally identical to the square-law model of MOSFET
- JFET is a depletion mode device
- Parameters  $I_{DSS}$  and  $V_P$  characterize the device
- $I_{DSS}$  proportional to  $W/L$  where  $W$  and  $L$  are width and length of n+ diff
- $V_P$  is negative for n-channel device, positive for p-channel device thus JFET is depletion mode device
- Must not forward bias GS junction by over about 300mV or excessive base current will flow (red constraint)
- Widely used as input stage for bipolar op amps


# The JFET

 

n-channel

 

p-channel

 


n-channel JFET  
(not available in this process)

## Square-law model of n-channel JFET


$$I_D = \begin{cases} 0 & V_{GS} < V_P \\ \frac{2I_{DSS}}{V_P^2} \left( V_{GS} - V_P - \frac{V_{DS}}{2} \right) V_{DS} & 0.3 > V_{GS} > V_P \quad V_{GS} - 0.3 < V_{DS} < V_{GS} - V_P \\ I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 & 0.3 > V_{GS} > V_P \quad V_{DS} > V_{GS} - V_P \end{cases}$$

- Functionally identical to the square-law model of MOSFET
- JFET is a depletion mode device
- Parameters  $I_{DSS}$  and  $V_P$  characterize the device
- $I_{DSS}$  proportional to  $W/L$  where  $W$  and  $L$  are width and length of n+ diff
- $V_P$  is negative for n-channel device, positive for p-channel device thus JFET is depletion mode device
- Must not forward bias GS junction by over about 300mV or excessive base current will flow (red constraint)
- Widely used as input stage for bipolar op amps


# The FET Devices

 


n-channel

 


p-channel

 


n-channel

 

p-channel

 

n-channel

 

p-channel

$$I_D = \begin{cases} 0 & \text{cutoff} \\ \frac{2I_{DSS}}{V_P^2} \left( V_{GS} - V_P - \frac{V_{DS}}{2} \right) V_{DS} & \text{Triode} \\ I_{DS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 & \text{Saturation} \end{cases}$$

$$I_D = \begin{cases} 0 & \text{Cutoff} \\ \frac{\mu C_{OX} W}{L} \left( V_{GS} - V_{TH} - \frac{V_{DS}}{2} \right) V_{DS} & \text{Triode} \\ \frac{\mu C_{OX} W}{2L} (V_{GS} - V_{TH})^2 & \text{Saturation} \end{cases}$$

$I_{DSS}$  proportional to  $W/L$  where  $W$  and  $L$  are width and length of n+ diff (could define  $I_{DSS} = \hat{I}_{DSS} \frac{W}{L}$ )

$V_P$  and  $V_{TH}$  are analogous

$\frac{2\hat{I}_{DSS}}{V_P^2}$  and  $\mu C_{OX}$  are analogous

Basic circuit structures are the same (with different biasing implications)

# Outline

## Bipolar Processes

- Parasitic Devices in CMOS Processes
- JFET





Other Junction Devices

## Special Bipolar Processes


- Thyristors  
SCR  
TRIAC

# The Schottky Diode

  

- Metal-Semiconductor Junction
- One contact is ohmic, other is rectifying
- Not available in all processes
- Relatively inexpensive adder in some processes
- Lower cut-in voltage than pn junction diode
- High speed

# The MESFET


 


- Metal-Semiconductor Junction for Gate
- Drain and Source contacts ohmic, other is rectifying
- Usually not available in standard CMOS processes
- Must not forward bias very much
- Lower cut-in voltage than pn junction diode
- High speed

# The Thyristor

A bipolar device in CMOS Processes

Consider a Bulk-CMOS Process

  

**Have formed a lateral pnpn device !**

Will spend some time studying pnpn devices



# Outline

## Bipolar Processes

- Parasitic Devices in CMOS Processes
- JFET
- Other Junction Devices

## Special Bipolar Processes



Thyristors  
SCR  
TRIAC

# Thyristors

The good and the bad!

# Thyristors

The good

SCRs

Triacs

The bad

Parasitic Device that can destroy integrated circuits

# Outline

## Bipolar Processes

- Parasitic Devices in CMOS Processes
- JFET
- Other Junction Devices

## Special Bipolar Processes

- Thyristors




SCR

TRIAC




# The SCR
 
## Silicon Controlled Rectifier

- Widely used to switch large resistive or inductive loads
- Widely used in the power electronics field
- Widely used in consumer electronic to interface between logic and power







Usually made by diffusions in silicon

   

Symbols


Consider first how this 4-layer 3-junction device operates

# Operation of the SCR

    


Not actually separated but useful for describing operation
 
# Variation of Current Gain ( $\beta$ ) with Bias for BJT



Note that current gain gets very small at low base current levels

# Operation of the SCR

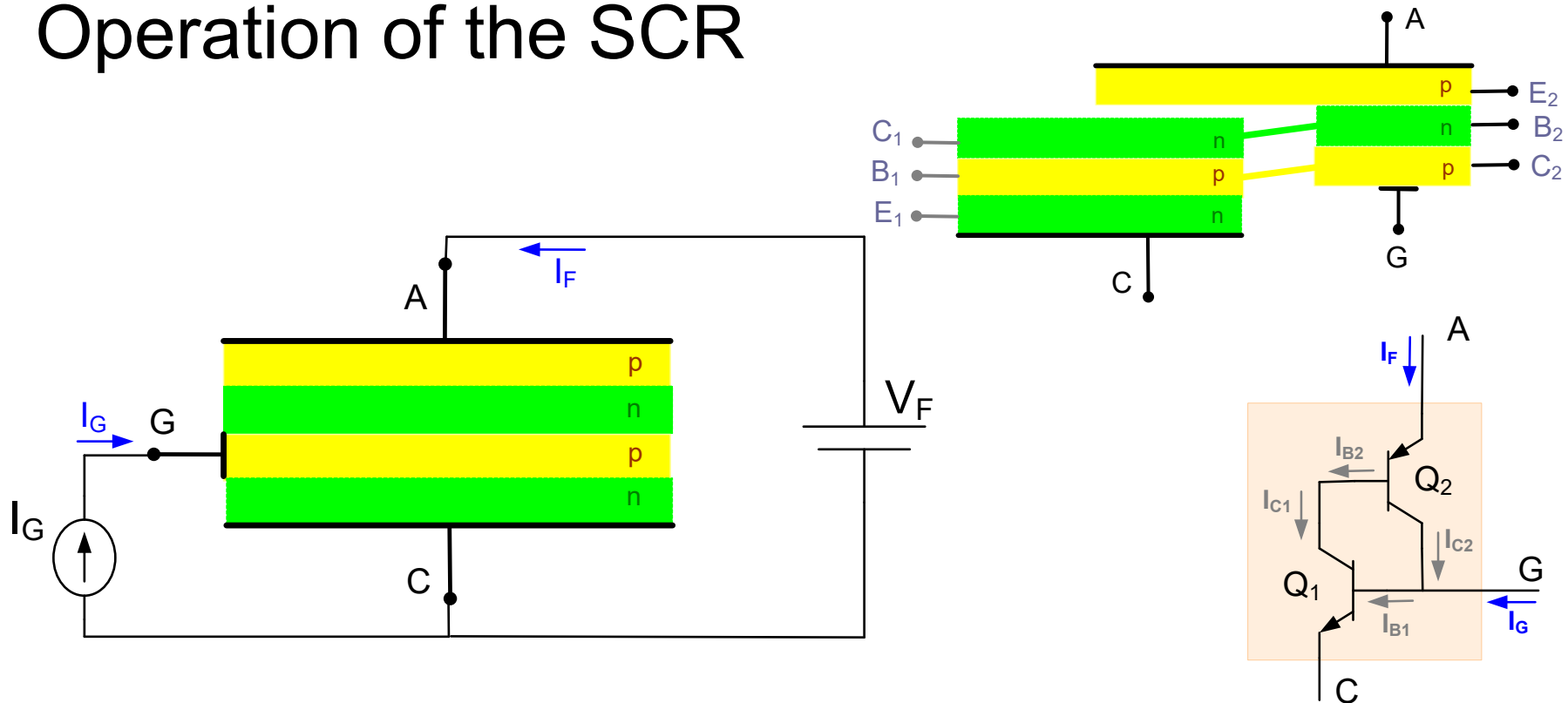

Consider a small positive bias (voltage or current) on the gate ( $V_{GC} < 0.5V$ ) and a positive and large voltage  $V_F$

Will have  $V_{C1} \geq V_F - 0.5V$




Thus  $Q_1$  has a large positive voltage on its collector

Since  $V_{BE1}$  is small,  $I_{C1}$  will be small as will  $I_{C2}$ , diode equation governs BE junction of  $Q_1$

$I_F$  will be very small



# Operation of the SCR

   

Now let bias on the gate increase ( $V_{GC}$  around 0.6V) so  $Q_1$  and  $Q_2$  in FA  $V_{C1} \geq V_F - 0.5V$

From diode equation, base voltage  $V_{BE1}$  will increase and collector current  $I_{C1}$  will increase



Thus base current  $I_{B2}$  will increase as will the collector current of  $I_{C2}$

Under assumption of operation in FA region get expression

$$I_{B1} = I_G + \beta_1 \beta_2 I_{B1}$$

This is regenerative feedback (actually can show pole in RHP)
  
# Very Approximate Analysis Showing RHP Pole



$$V_G s C_B + I_{B1} = I_{C2} + I_G$$


$$I_{C2} = \beta_1 \beta_2 I_{B1}$$

$$I_{B1} R_{BE} = V_G$$

$$V_G = I_G \frac{R_{BE}}{s R_{BE} C_B + 1 - \beta_1 \beta_2}$$

$$p = \frac{\beta_1 \beta_2 - 1}{R_{BE} C_B}$$

# Operation of the SCR

 

$$V_{C1} \cong V_F - 0.6V$$

Under assumption of operation in FA region get expression

$$I_{B1} = I_G + \beta_1 \beta_2 I_{B1}$$

What will happen with this is regenerative feedback?

If  $I_G$  is small (and thus  $\beta_1$  and  $\beta_2$  are small)  $I_F$  will be very small

If  $I_G$  larger but less than  $\beta_1 \beta_2 I_{B1}$  it can be removed and current will continue to flow

$I_{C1}$  will continue to increase and drive  $Q_1$  into SAT


This will try to drive  $V_A$  towards 0.9V (but forced to be  $V_F$ !)

The current in  $V_F$  will go towards  $\infty$

The SCR will self-destruct because of excessive heating !




 Too bad the circuit self-destructed because the small gate current was able to control a lot of current!


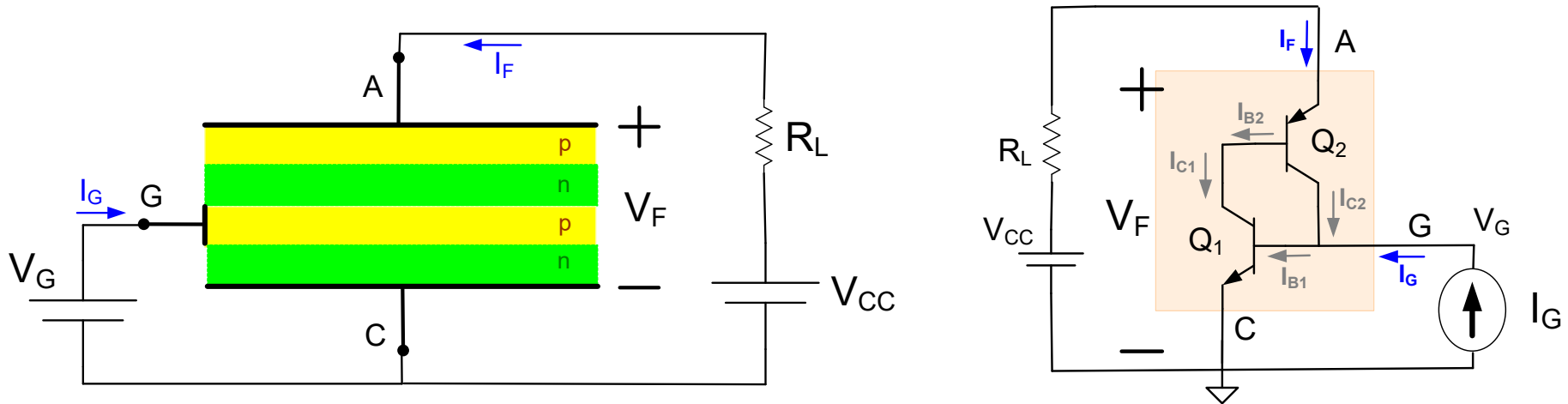
# Operation of the SCR

Consider a modified application by adding a load (depicted as  $R_L$ )



All operation is as before, but now, after the triggering occurs, the voltage  $V_F$  will drop to approximately 0.8 V and the voltage  $V_{CC} - 0.8$  will appear across  $R_L$

If  $V_{CC}$  is very large, the SCR has effectively served as a switch putting  $V_{CC}$  across the load and after triggering occurs,  $I_G$  can be removed!


But, how can we turn it off?

Will discuss that later
 
# Operation of the SCR

SCR model

$$\left. \begin{aligned} I_F &= f_1(V_F, V_G) \\ I_G &= f_2(V_G) \end{aligned} \right\}$$



As for MOSFET, Diode, and BJT, several models for SCR can be developed

The Ideal SCR Model


$$\left. \begin{aligned} I_F &= f_{1I}(V_F, I_G) \\ I_G &= f_{2I}(V_G) \end{aligned} \right\}$$

or


$$\left. \begin{aligned} I_F &= f_{1IA}(V_F, V_G) \\ I_G &= f_{2I}(V_G) \end{aligned} \right\}$$

# Operation of the SCR


Consider the Ideal SCR Model

 
 
$$\left. \begin{aligned} I_F &= f_{1I}(V_F, I_G) \\ I_G &= f_{2I}(V_G) \end{aligned} \right\}$$




$I_H$  is very small

 



$I_{G1}$  is small (but not too small)

# Operation of the SCR

Consider nearly Ideal SCR Model

 
  
$$\left. \begin{aligned} I_F &= f_{1I}(V_F, I_G) \\ I_G &= f_{2I}(V_G) \end{aligned} \right\}$$



- On voltage approximately 0.9V
- Major contributor to ON-state power dissipation
- Even with large currents,  $P_{ON}$  is quite small

# Operation of the SCR


## Operation with the Ideal SCR

$$I_F = f_1(V_F, V_G)$$


$$I_G = f_2(V_G)$$

Load Line:  $V_{CC} = I_F R_L + V_F$

 Analysis:  $V_{CC} = I_F R_L + V_F$   
 $I_F = f_{1I}(V_F, V_G)$



 The solution of these two equations is at the intersection of the load line and the device characteristics



when  $I_G=0$

Note three intersection points

Two (upper and lower) are stable equilibrium points, one is not

When operating at upper point,  $V_F=0$  so  $V_{CC}$  appears across  $R_L$  We say SCR is ON

When operating at lower point,  $I_F$  approx 0 so no signal across  $R_L$  We say SCR is OFF



When  $I_G=0$ , will stay in whatever state it was in



# Operation of the SCR

## Operation with the Ideal SCR

$$I_F = f_{11}(V_F, I_G)$$

  



For notational convenience will drop subscript unless emphasis is needed

$$I_F = f_{11}(V_F, I_G) \quad \longrightarrow \quad I_F = f(V_F, I_G)$$


# Operation of the SCR
  
## Operation with the Ideal SCR

Now assume it was initially in the OFF state and then a gate current was applied


 
$$\left. \begin{aligned} V_{CC} &= I_F R_L + V_F \\ I_F &= f(V_F, I_G) \end{aligned} \right\}$$



Now there is a single intersection point so a unique solution



The SCR is now ON

Removing the gate current will return to the previous solution (which has 3 intersection points) but it will remain in the ON state

# Operation of the SCR

## Operation with the Ideal SCR

Turning SCR off when  $I_G=0$

  

Reduce  $V_{CC}$  so that  $V_{CC}/R_L$  goes below  $I_H$

This will provide a single intersection point



$V_{CC}$  can then be increased again and SCR will stay off

Must not increase  $V_{CC}$  much above  $V_{BGF0}$  else will turn on

# Operation of the SCR

## Operation with the Ideal SCR

Turning SCR off when  $I_G=0$

 
 


# Operation of the SCR
  
## Operation with the Ideal SCR

Often  $V_{CC}$  is an AC signal (often 110V)

SCR will turn off whenever AC signal goes negative





# Operation of the SCR
  
## Operation with the Ideal SCR

Often  $V_{CC}$  is an AC signal (often 110V)



SCR will turn off whenever AC signal goes negative



# Operation of the SCR

## Operation with the Ideal SCR

Turning SCR off when  $I_G > 0$

  

Reduce  $V_{CC}$  so that  $V_{CC}/R_L$  goes below  $I_H$




This will provide a single intersection point

But when  $V_{CC}$  is then increased SCR will again turn on

# Operation of the SCR

## Operation with the Ideal SCR

Duty cycle control of load  $R_L$

 
 
 




# Operation of the SCR


## Operation with the Ideal SCR

Duty cycle control of load  $R_L$

   


# Operation of the SCR

## Operation with the actual SCR

 


# Operation of the SCR

Operation with the actual SCR

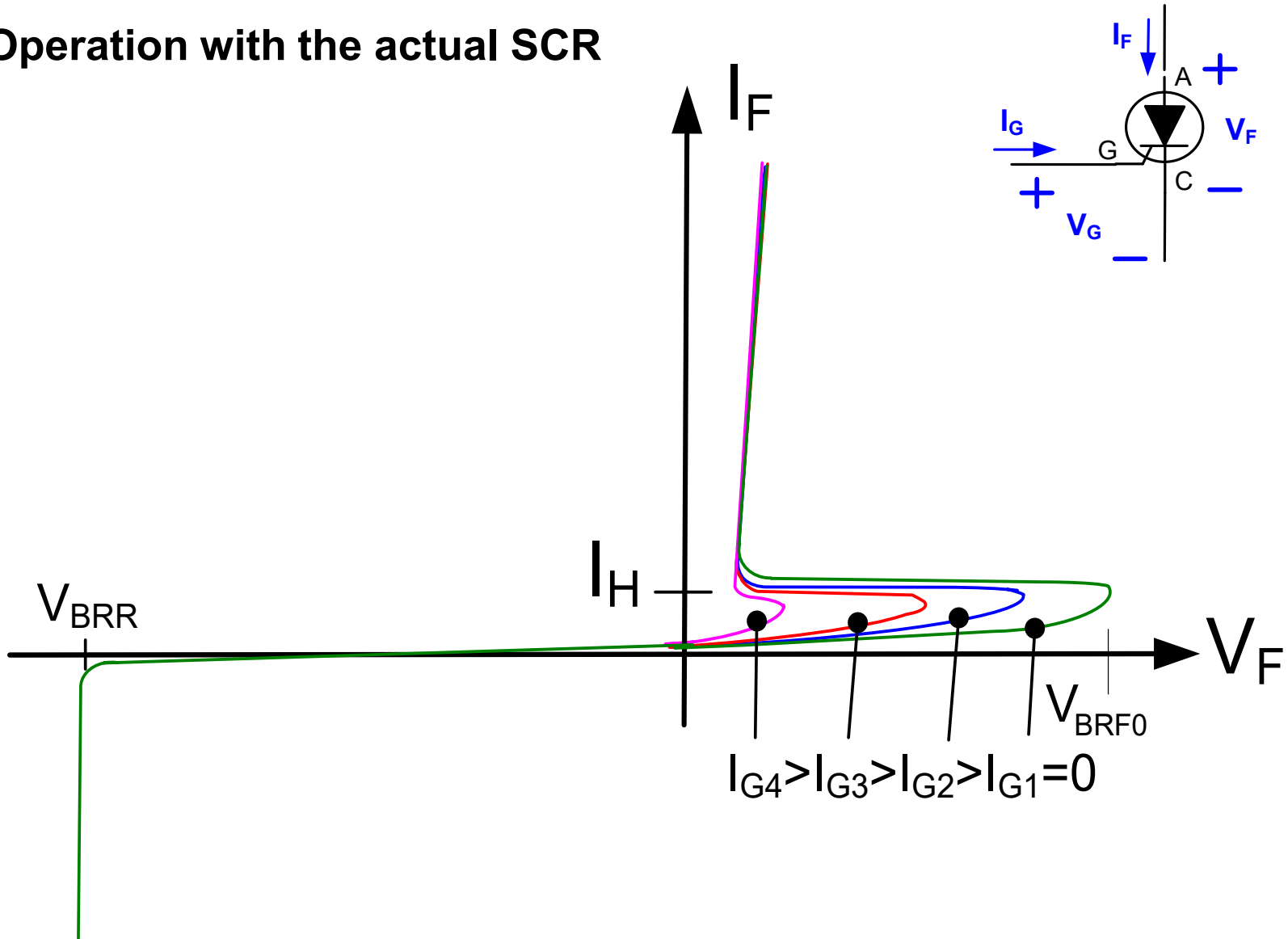

# Operation of the SCR



## Operation with the actual SCR

 

- Still two stable equilibrium points and one unstable point
- $\Delta V_F$  is quite constant and small (around 1V)
- If large current is flowing, power in anode can be large ( $P_A \approx I_F \bullet 1V$ )
- Power in gate is usually very small


# Operation of the SCR

## Operation with the actual SCR

  

To turn on, must make  $I_G$  large enough to have single intersection point

# SCR Terminology

 

$I_H$  is the holding current

$I_L$  is the latching current (current immediately after turn-on)

$V_{BGF0}$  is the forward break-over voltage


$V_{BRR}$  is the reverse break-down voltage

$I_{GT}$  is the gate trigger current

$V_{GT}$  is the gate trigger voltage


# SCR Terminology

## Issues and Observations

 



- Trigger parameters ( $V_{GT}$  and  $I_{GT}$ ) highly temperature dependent
- Want gate “sensitive” but not too sensitive (to avoid undesired triggering)
- SCRs can switch very large currents but power dissipation is large
- Heat sinks widely used to manage power
- Trigger parameters affected by both environment and application
- Trigger parameters generally dependent upon  $V_F$
- Exceeding  $V_{BRR}$  will usually destroy the device
- Exceeding  $V_{BGF0}$  will destroy some devices
- Lack of electronic turn-off unattractive in some applications
- Can be used in alarm circuits to attain forced reset
- Maximum 50% duty cycle in AC applications is often not attractive

# Alarm Application

 




# Performance Limitations with the SCR

  

- Very attractive properties as an electronic switch
- SCR is very useful




But:

 1. Only conducts in one direction
2. Can't easily turn off (though not major problem in AC switching)


   
# Observations about Basic SRC Circuit




Assume  $V_{CC}$  is an AC signal (often 110V) and  $V_G$  is static




SCR is always off
   
# Observations about Basic SRC Circuit

Assume  $V_{CC}$  is an AC signal (often 110V) and  $V_G$  is static







SCR is ON about 50% of the time

 
    
# Observations about Basic SRC Circuit



Assume  $V_{CC}$  is an AC signal (often 110V) and  $V_G$  is static




SCR is ON less than 50% of the time (duty cycle depends upon  $V_G$ )

Often use electronic circuit to generate  $V_G$

# Performance Limitations with the SCR

  

 - Very attractive properties as an electronic switch
- SCR is very useful




But:

1. Only conducts in one direction
2. Can't easily turn off (though not major problem in AC switching)


Would be useful in many additional applications if:

1. Could conduct in both directions
2. Can easily turn off with  $I_G$

# Improvement Concept

 

 1. Only conducts in one direction
2. Can't easily turn off (though not major problem in AC switching)



1. Could conduct in both directions
2. Generating two gate voltages referenced to different cathodes a bit cumbersome

Will investigate bi-directional devices in next lecture



Stay Safe and Stay Healthy !

End of Lecture 29