

EE 330

Lecture 31

Basic amplifier architectures

- Common Emitter/Source
- Common Collector/Drain
- Common Base/Gate

Exam Schedule

Exam 2 will be given on Friday March 11

Exam 3 will be given on Friday April 15

Photo courtesy of the director of the National Institute of Health (NIH)






As a courtesy to fellow classmates, TAs, and the instructor

Wearing of masks during lectures and in the laboratories for this course would be appreciated irrespective of vaccination status



Basic Amplifier Structures

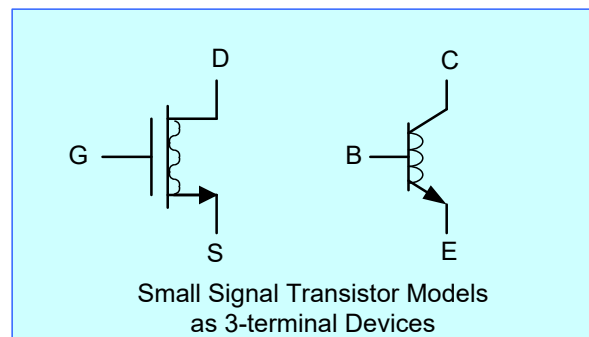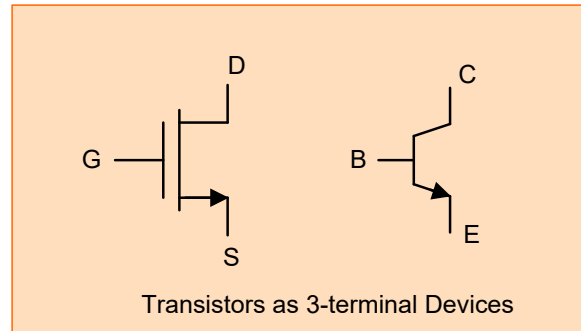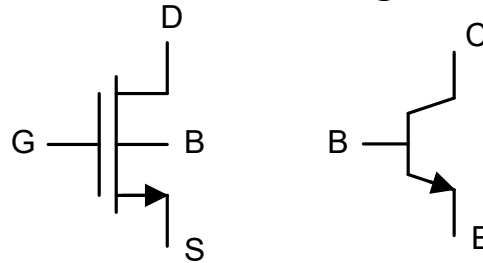- MOS and Bipolar Transistors both have 3 primary terminals
- MOS transistor has a fourth terminal that is generally considered a parasitic terminal



Basic Amplifier Structures

Observation:

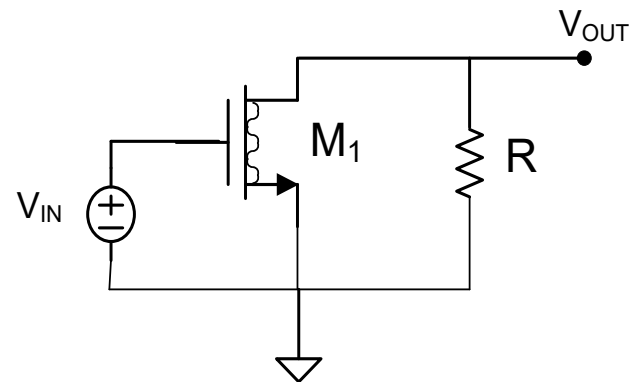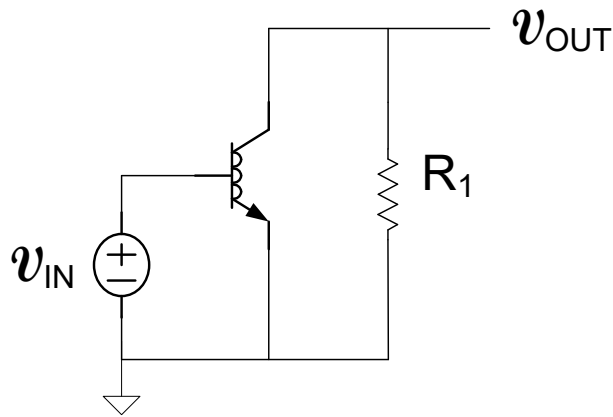

These circuits considered previously have a terminal (emitter or source) common to the input and output in the small-signal equivalent circuit


For BJT, E is common, input on B, output on C

Termed “Common Emitter”

For MOSFET, S is common, input on G, output on D

Termed “Common Source”

Basic Amplifier Structures

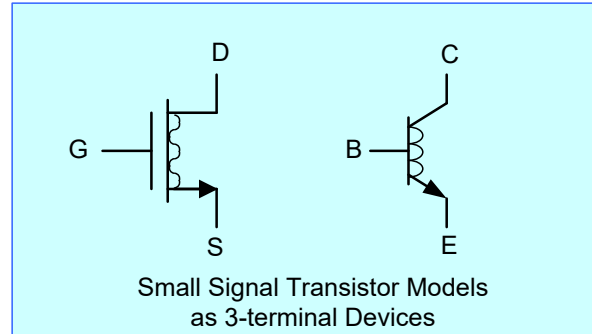


Amplifiers using these devices generally have one terminal common and use remaining terminals as input and output

Since devices are nearly unilateral, designation of input and output terminals is uniquely determined

Three different ways to designate the common terminal

Source or Emitter	termed Common Source or Common Emitter
Gate or Base	termed Common Gate or Common Base
Drain or Collector	termed Common Drain or Common Collector

Basic Amplifier Structures

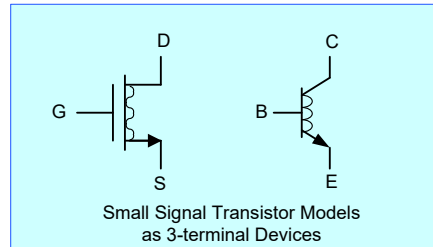


	MOS			BJT		
	Common	Input	Output	Common	Input	Output
Common Source or Common Emitter	S	G	D	E	B	C
Common Gate or Common Base	G	S	D	B	E	C
Common Drain or Common Collector	D	G	S	C	B	E

Identification of Input and Output Terminals is not arbitrary

It will be shown that all 3 of the basic amplifiers are useful !

Basic Amplifier Structures

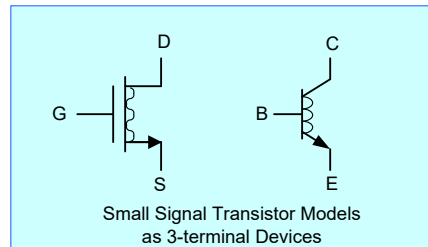


Common Source or Common Emitter

Common Gate or Common Base


Common Drain or Common Collector

Objectives in Study of Basic Amplifier Structures

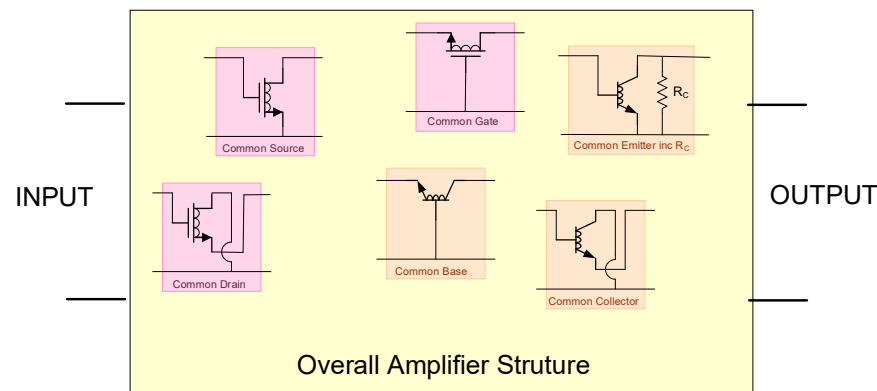
1. Obtain key properties of each basic amplifier
2. Develop method of designing amplifiers with specific characteristics using basic amplifier structures








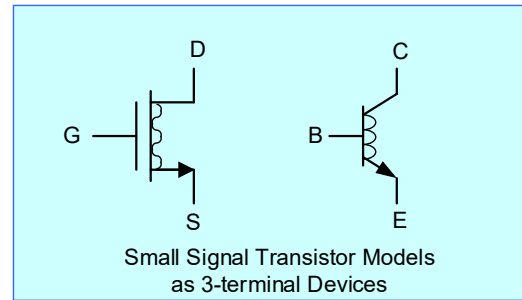
Characterization of Basic Amplifier Structures



- Observe that the small-signal equivalent of any 3-terminal network is a two-port
- Thus to characterize any of the 3 basic amplifier structures, it suffices to determine the two-port equivalent network
- Since small signal model when expressed in terms of small-signal parameters of BJT and MOSFET differ only in the presence/absence of g_{π} term, can analyze the BJT structures and then obtain characteristics of corresponding MOS structure by setting $g_{\pi}=0$


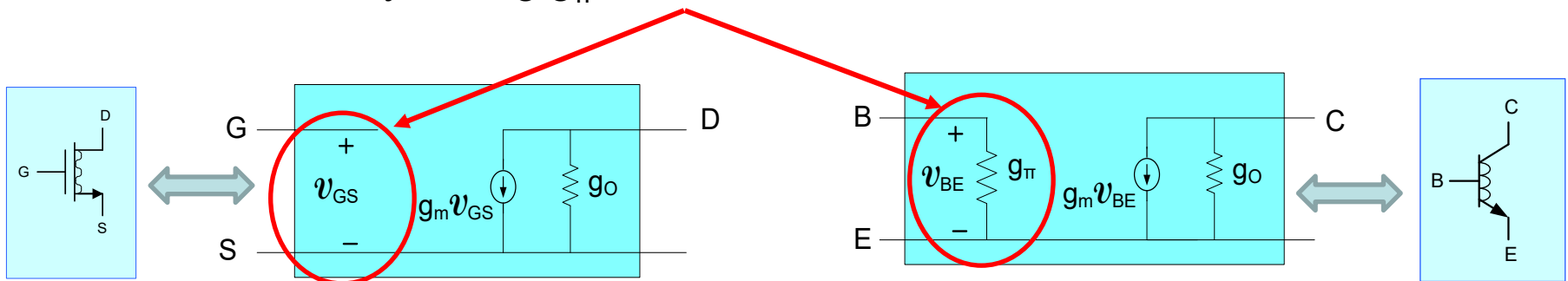


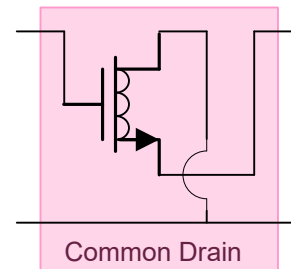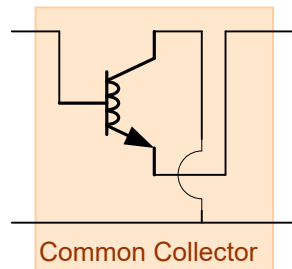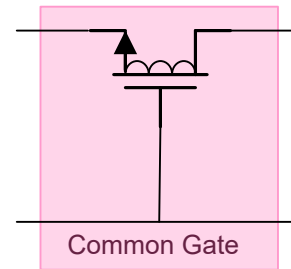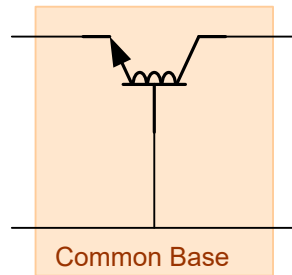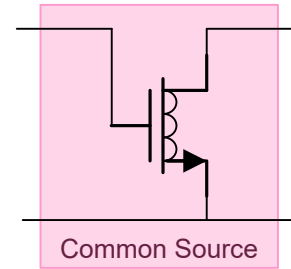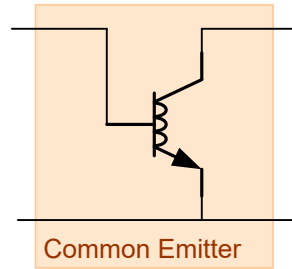The three basic amplifier types for both MOS and bipolar processes





Will focus on the performance of the bipolar structures and then obtain performance of the MOS structures by observation

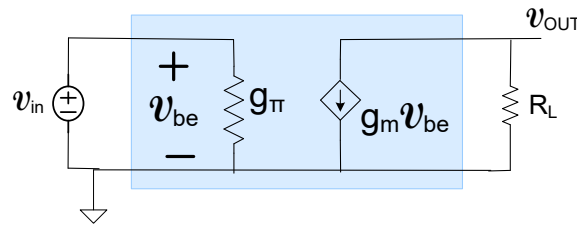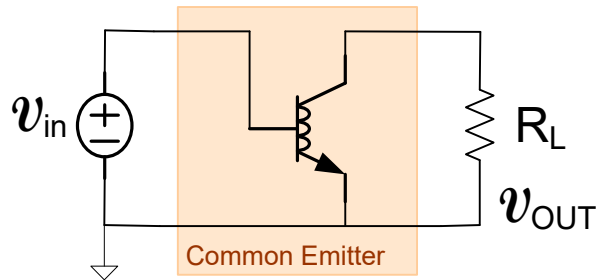The three basic amplifier types for both MOS and bipolar processes





$$\left. \begin{aligned} v_{OUT} &= -g_m R_L v_{be} \\ v_{IN} &= v_{be} \end{aligned} \right\}$$
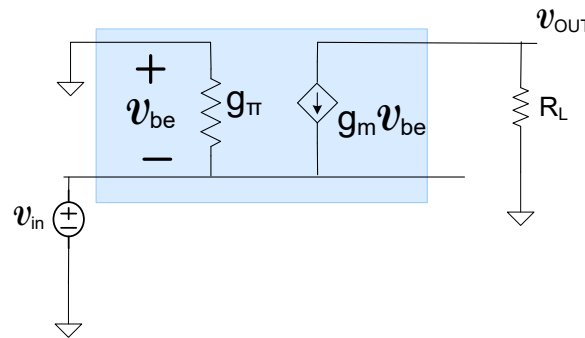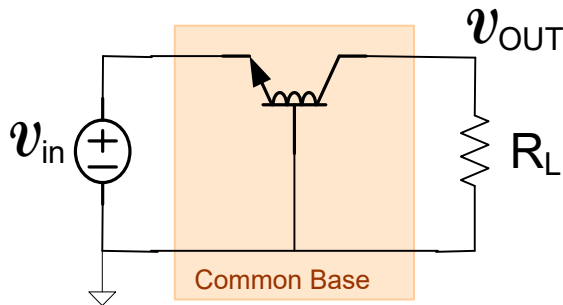
$$A_V = \frac{v_{OUT}}{v_{IN}} = -g_m R_L$$



$$\left. \begin{aligned} v_{OUT} &= -g_m R_L v_{be} \\ v_{IN} &= -v_{be} \end{aligned} \right\}$$
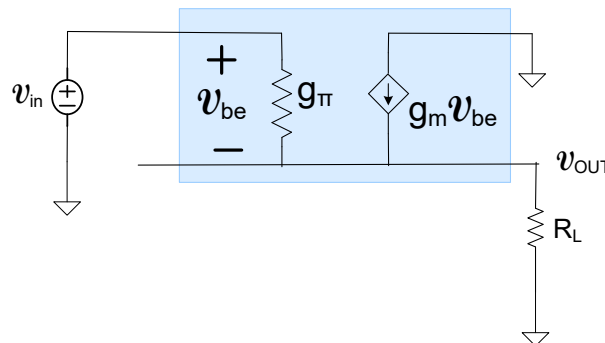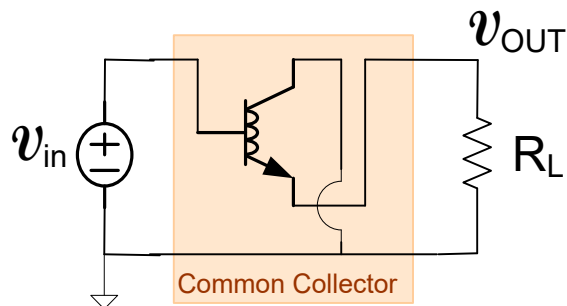
$$A_V = \frac{v_{OUT}}{v_{IN}} = g_m R_L$$












$$\left. \begin{aligned} v_{OUT} &= (g_m + g_\pi) v_{be} R_L \\ v_{IN} &= v_{be} + (g_m + g_\pi) v_{be} R_L \end{aligned} \right\}$$

$$A_V = \frac{v_{OUT}}{v_{IN}} = \frac{(g_m + g_\pi) R_L}{1 + (g_m + g_\pi) R_L} \cong 1$$

- Significantly different gain characteristics for the three basic amplifiers
- There are other significant differences too (R_{IN} , R_{OUT} , ...) as well

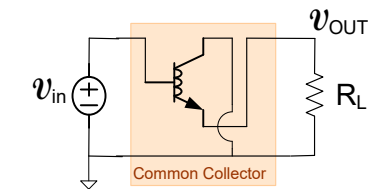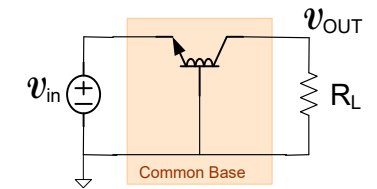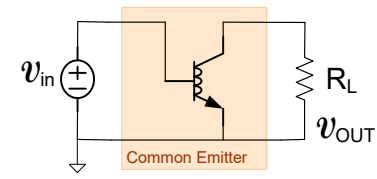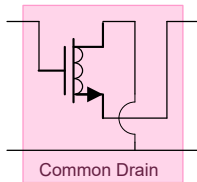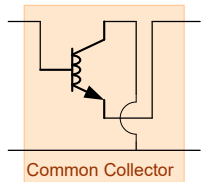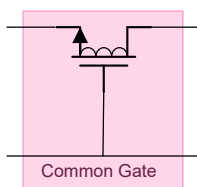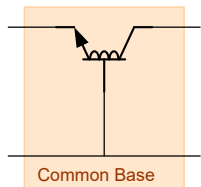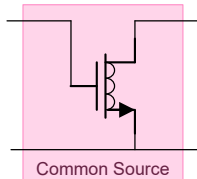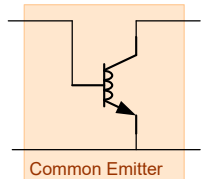The three basic amplifier types for both MOS and bipolar processes




More general models are needed to accommodate biasing, understand performance capabilities, and include effects of loading of the basic structures

Two-port models are useful for characterizing the basic amplifier structures

How can the two-port parameters be obtained for these or any other linear two-port networks?

Two-Port Models of Basic Amplifiers widely used for Analysis and Design of Amplifier Circuits

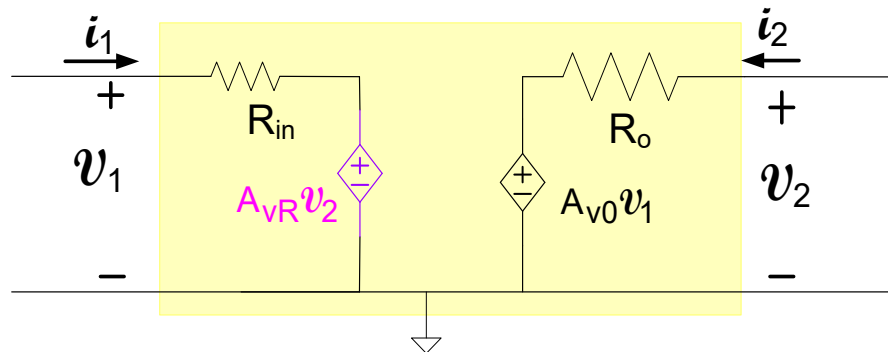Methods of Obtaining Amplifier Two-Port Network



1. $v_{\text{TEST}} : i_{\text{TEST}}$ Method (considered in a previous lecture)

2. Write $v_1 : v_2$ equations in standard form

$$v_1 = i_1 R_{\text{IN}} + A_{\text{VR}} v_2$$

$$v_2 = i_2 R_{\text{O}} + A_{\text{V0}} v_1$$


3. Thevenin-Norton Transformations

4. Ad Hoc Approaches


Any of these methods can be used to obtain the two-port model

$v_{\text{test}} : i_{\text{test}}$ Method for Obtaining Two-Port Amplifier Parameters


SUMMARY from PREVIOUS LECTURE

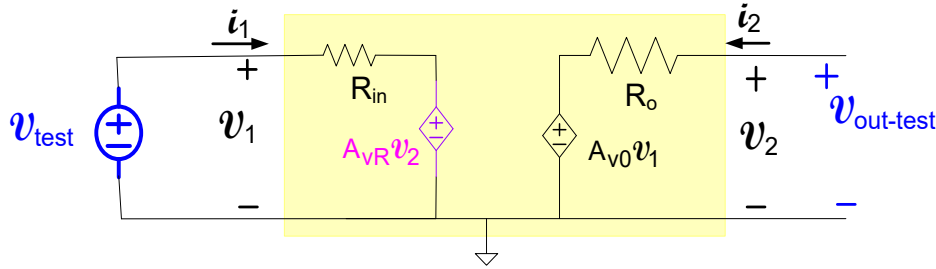

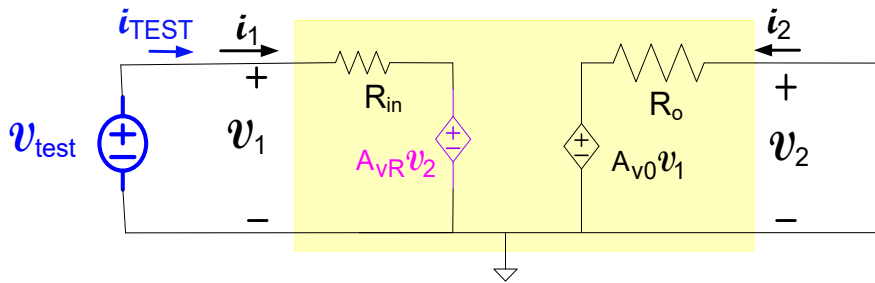
$$A_{v0} = \frac{v_{\text{out-test}}}{v_{\text{test}}}$$


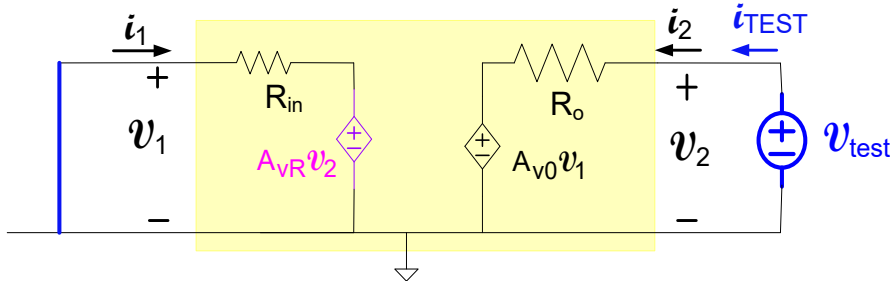
$$R_{\text{in}} = \frac{v_{\text{test}}}{i_{\text{test}}}$$



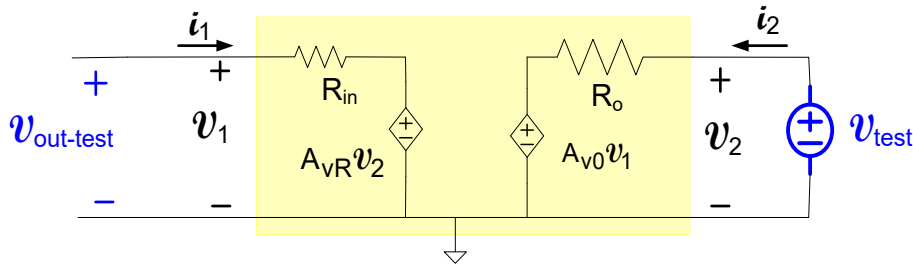
$$R_o = \frac{v_{\text{test}}}{i_{\text{test}}}$$




$$A_{vR} = \frac{v_{\text{out-test}}}{v_{\text{test}}}$$

If Unilateral $A_{vR} = 0$

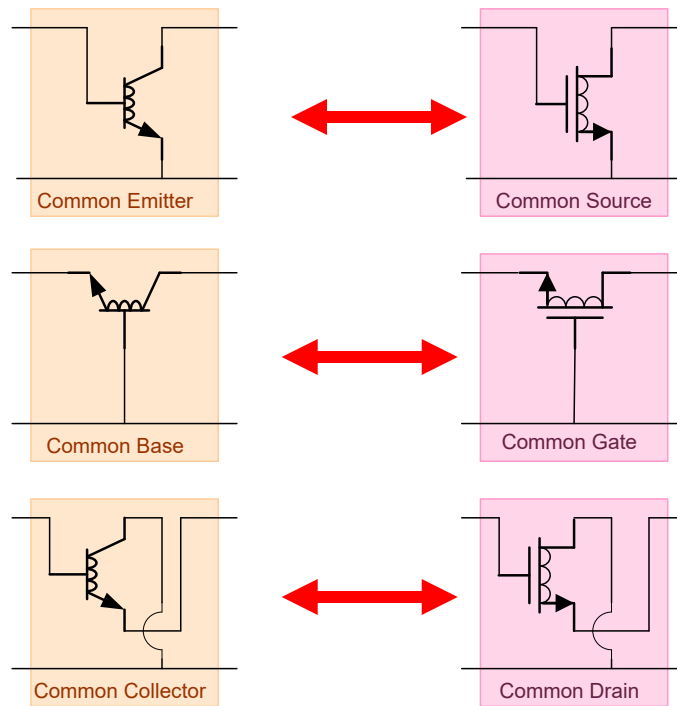Will now develop two-port model for each of the three basic amplifiers and look at one widely used application of each



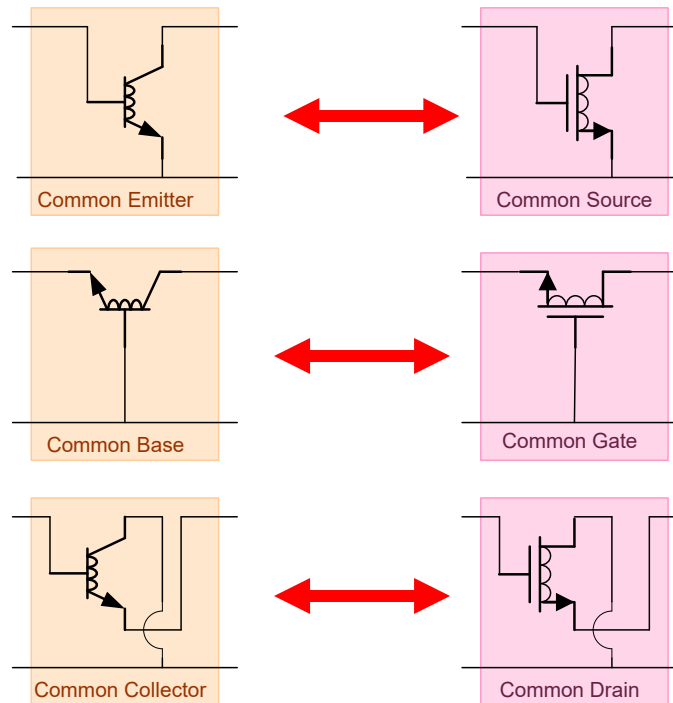Parameter Domains for Small-Signal Models for Any Devices



- Small-signal parameter domain

 - Y-parameters, g-parameters, amplifier parameters, ...


- Model Parameters and Operating Point (MPOP)

 - Small-signal analysis naturally results in small-signal parameter domain
 - More insight often in MPOP domain
 - Mixed-parameter domains possible but often difficult to obtain insight

Parameter Domains for Small-Signal Models for Any Devices


- Small-signal parameter domain
Y-parameters, g-parameters, amplifier parameters, ...
- Model Parameters and Operating Point (MPOP)

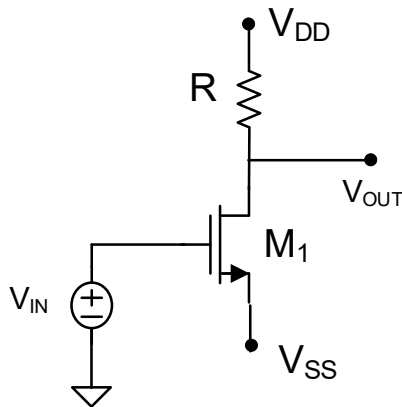Example: Give A_V for basic amplifier in ss parameter domain and MPOP domain



Small-Signal parameter domain

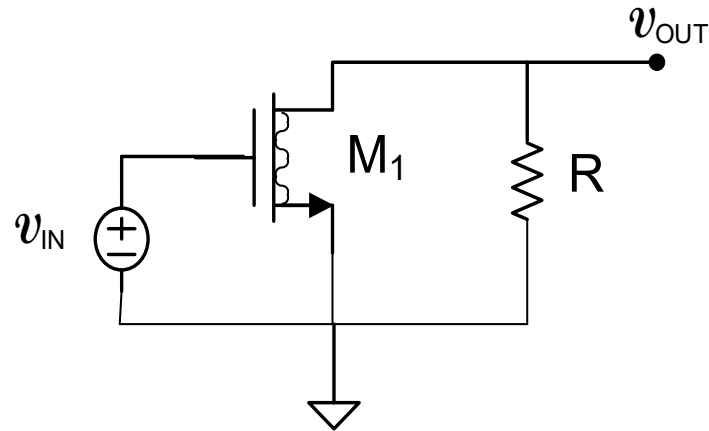
$$A_V = \frac{v_{OUT}}{v_{IN}} = -g_m R$$



MPOP domain





$$A_V = \frac{v_{OUT}}{v_{IN}} = -2 \frac{I_{DQ} R}{V_{EB}}$$

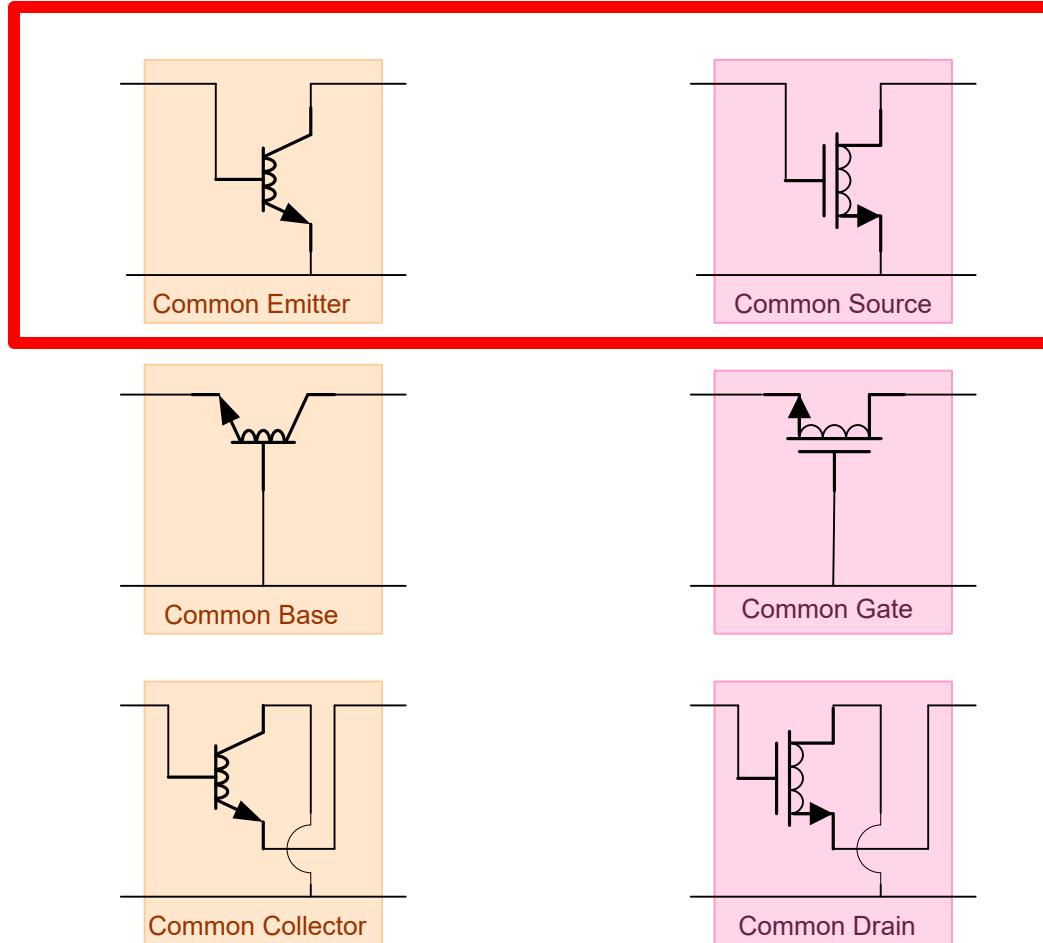Consider Common Emitter/Common Source Two-port Models



- Will focus on Bipolar Circuit since MOS counterpart is a special case obtained by setting $g_{\pi}=0$
- Will consider both two-port model and a widely used application




Basic CE/CS Amplifier Structures

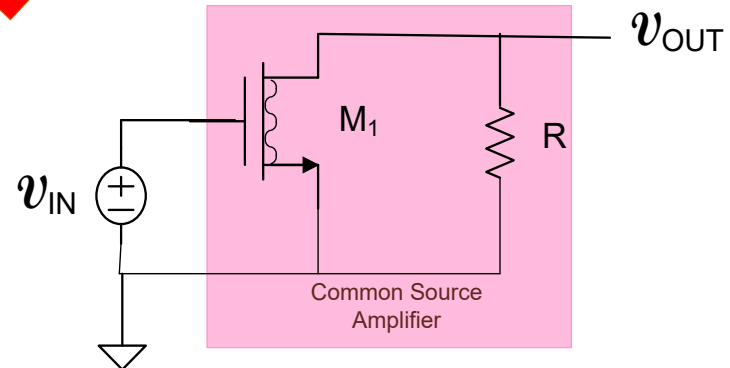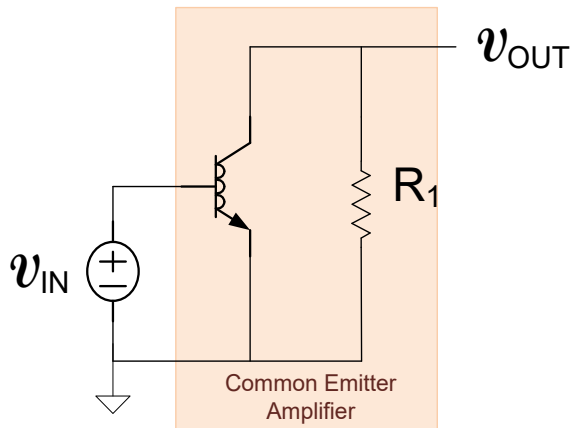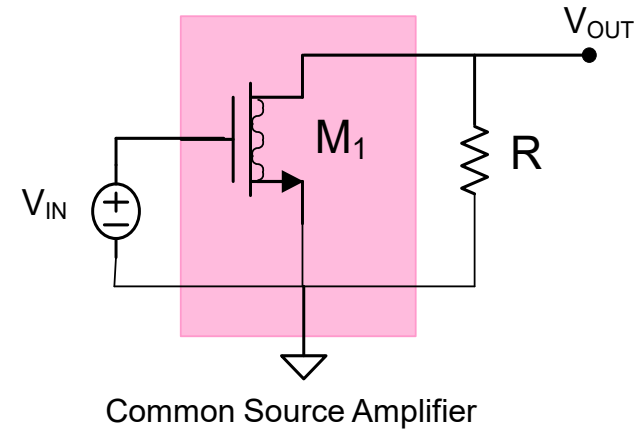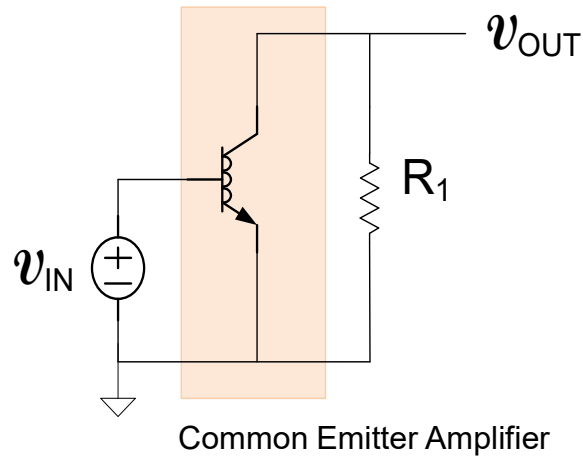

Can include or exclude R and R_1 in two-port models (of course they are different circuits)

The CE and CS amplifiers are themselves two-ports !

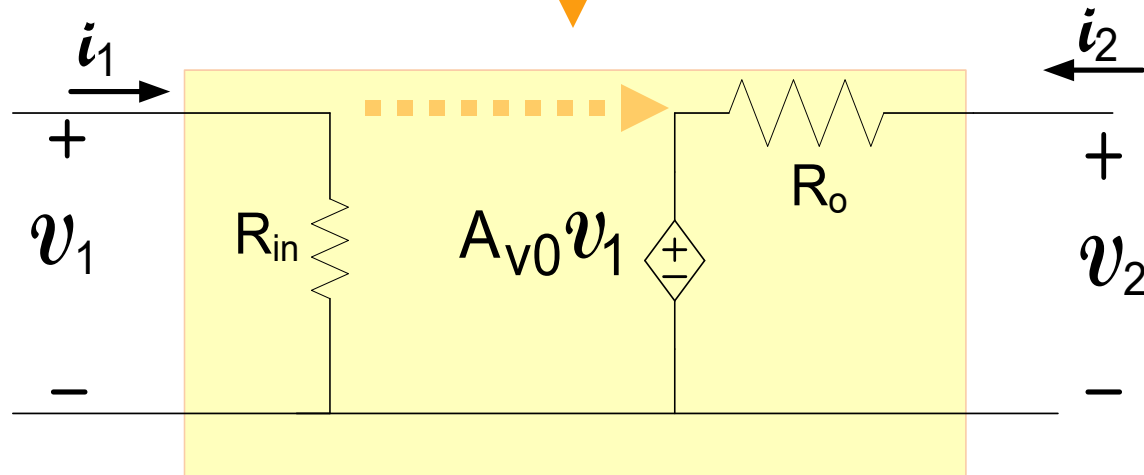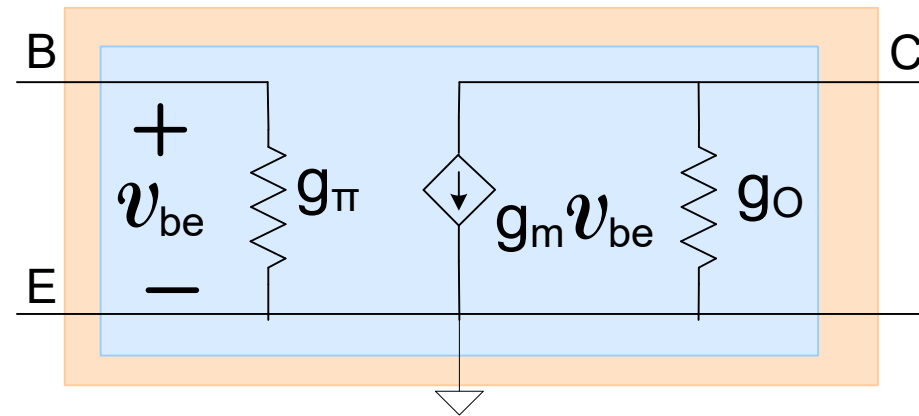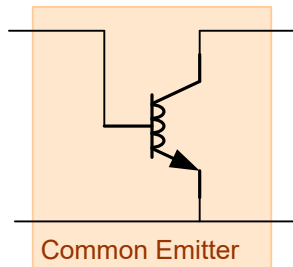
Two-port model for Common Emitter Configuration



$\{R_i, A_{v0} \text{ and } R_o\}$

Two-Port Models of Basic Amplifiers widely used for Analysis and Design of Amplifier Circuits

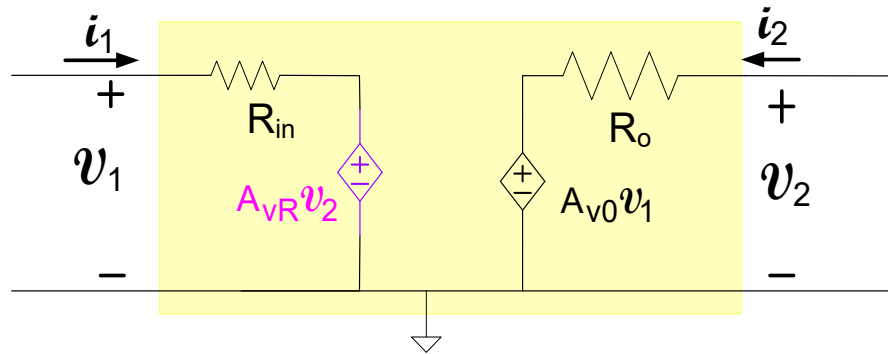Methods of Obtaining Amplifier Two-Port Network






1. $v_{\text{TEST}} : i_{\text{TEST}}$ Method
2. Write $v_1 : v_2$ equations in standard form
$$v_1 = i_1 R_{\text{IN}} + A_{\text{VR}} v_2$$
$$v_2 = i_2 R_{\text{O}} + A_{\text{V0}} v_1$$



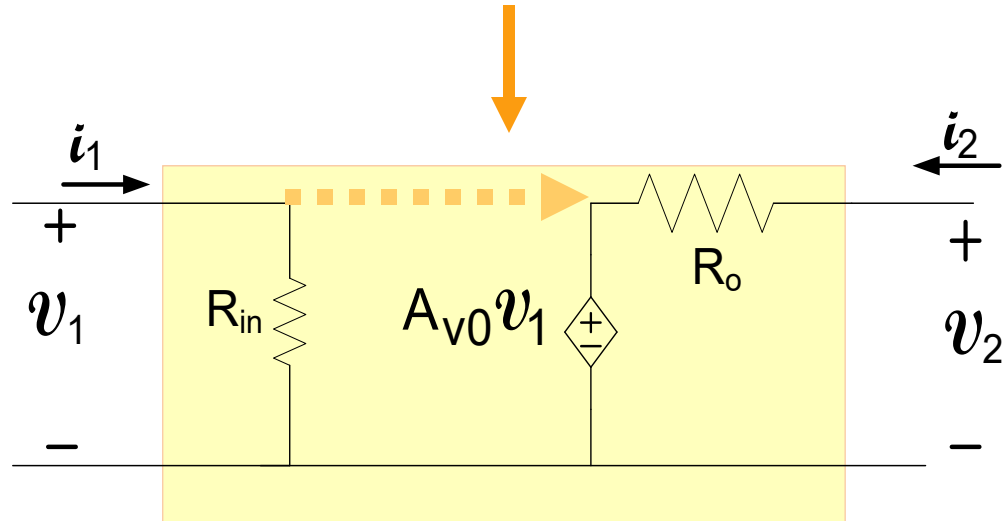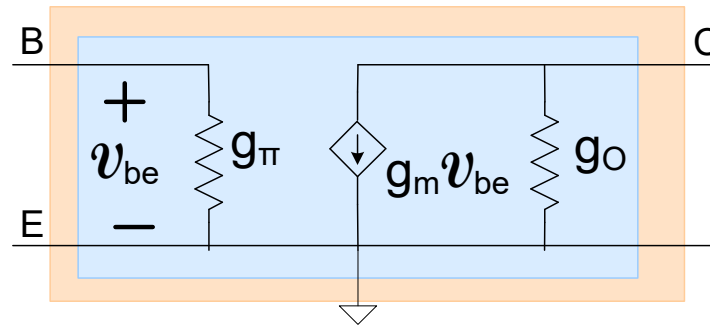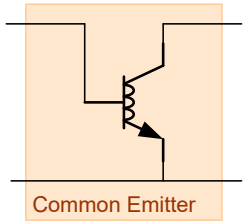3. Thevenin-Norton Transformations
4. Ad Hoc Approaches

Two-port model for Common Emitter Configuration



By Thevenin : Norton Transformations

$$R_{in} = \frac{1}{g_{\pi}}$$


$$A_{V0} = -\frac{g_m}{g_o}$$

$$R_o = \frac{1}{g_o}$$

$$A_{VR} = 0$$

Two-Port Models of Basic Amplifiers widely used for Analysis and Design of Amplifier Circuits

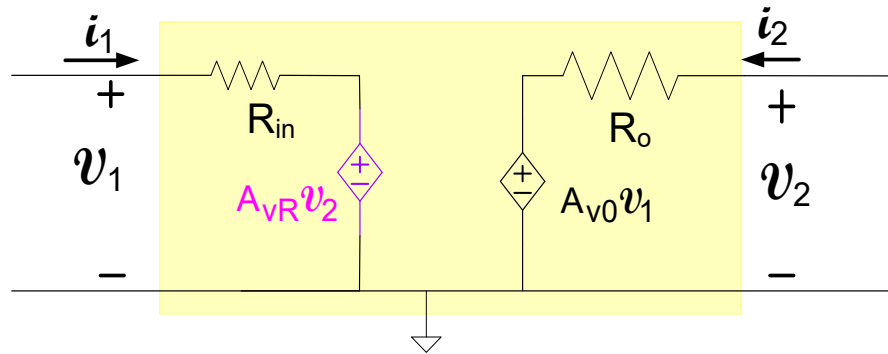Methods of Obtaining Amplifier Two-Port Network






1. $v_{TEST} : i_{TEST}$ method
2. Write $v_1 : v_2$ equations in standard form
$$v_1 = i_1 R_{IN} + A_{VR} v_2$$
$$v_2 = i_2 R_O + A_{V0} v_1$$
3. Thevenin-Norton Transformations
4. Ad Hoc Approaches



Two-port model for Common Emitter Configuration

Alternately, by $v_{\text{TEST}} : i_{\text{TEST}}$ Method

To obtain R_{in}

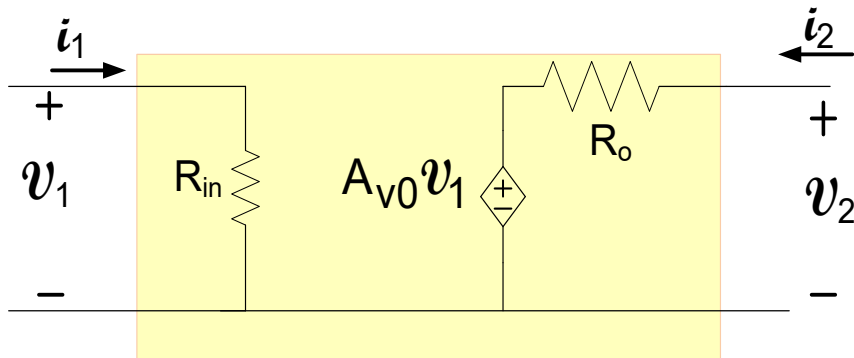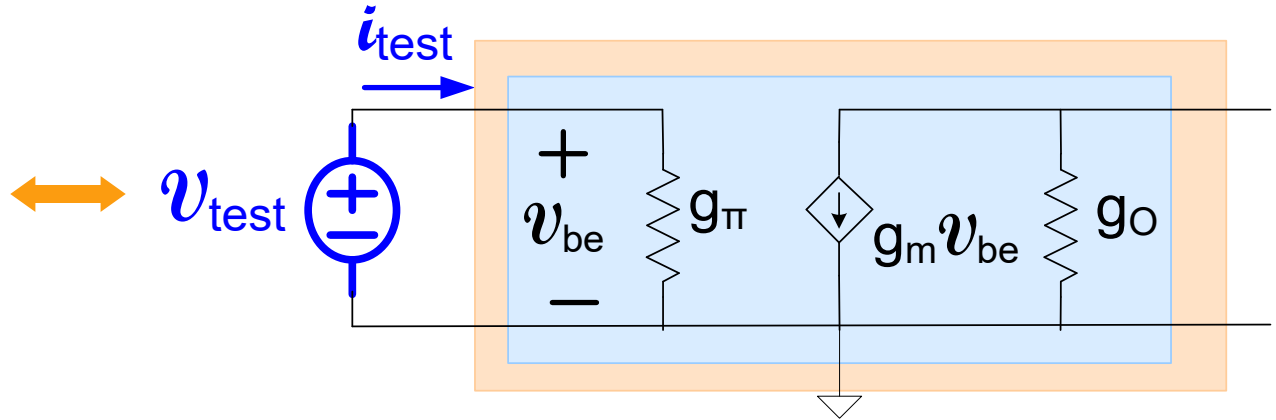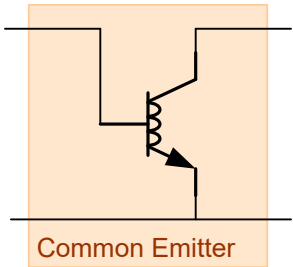

$$R_{\text{in}} = \frac{v_{\text{test}}}{i_{\text{test}}}$$




$$R_{\text{in}} = \frac{1}{g_{\pi}}$$

$\{R_{\text{in}}, A_{v0} \text{ and } R_o\}$



Two-port model for Common Emitter Configuration

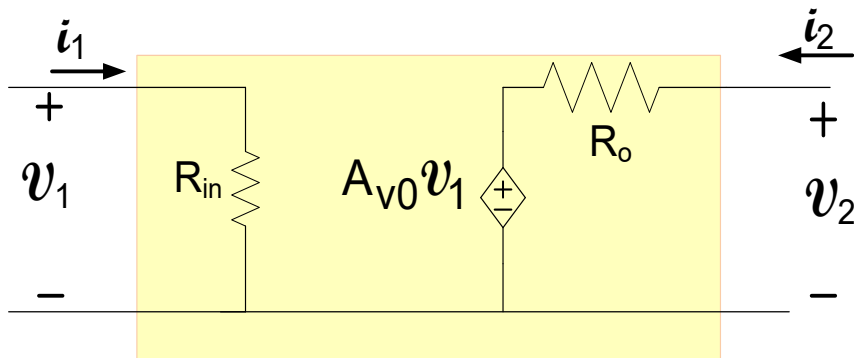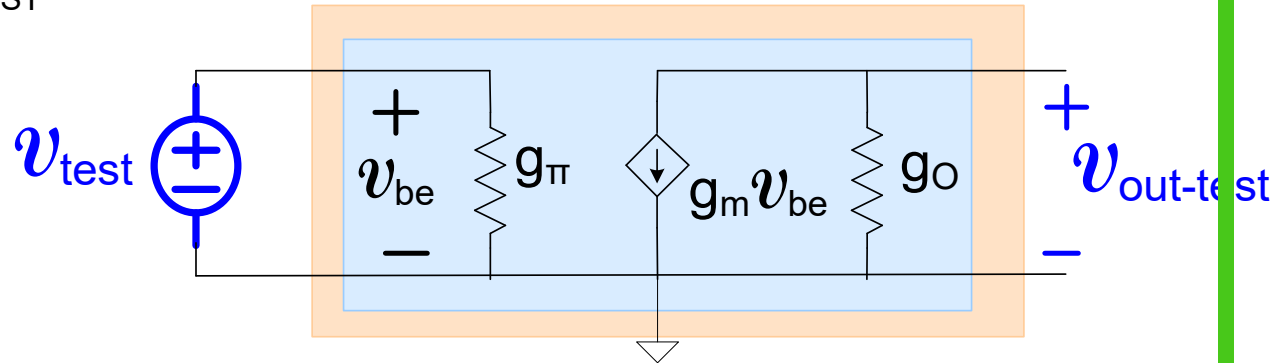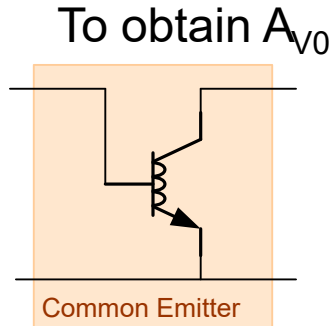Alternately, by $v_{\text{TEST}} : i_{\text{TEST}}$ Method



$$A_{V0} = \frac{v_{\text{out-test}}}{v_{\text{test}}}$$

$$v_{\text{out-test}} = v_{\text{test}} \left(-\frac{g_m}{g_o} \right)$$

$$A_{V0} = -\frac{g_m}{g_o}$$



$\{R_{\text{in}}, A_{V0} \text{ and } R_o\}$



Two-port model for Common Emitter Configuration

Alternately, by $v_{TEST} : i_{TEST}$ Method


To obtain g_0

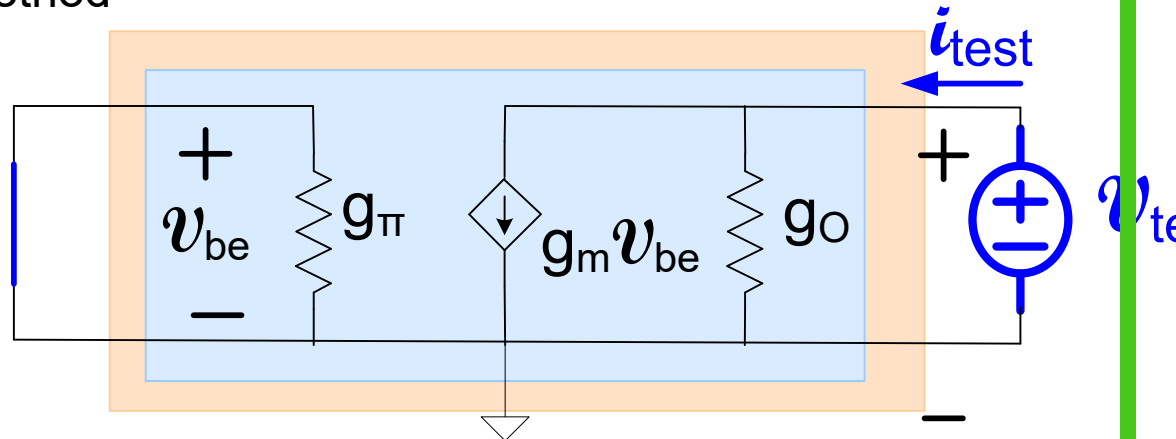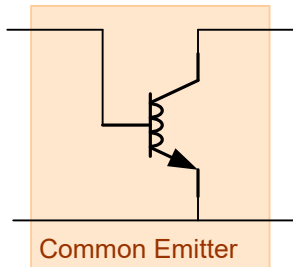

$$R_0 = \frac{v_{test}}{i_{test}}$$

$$v_{test} = i_{test} (g_0)$$

$$R_0 = \frac{1}{g_0}$$

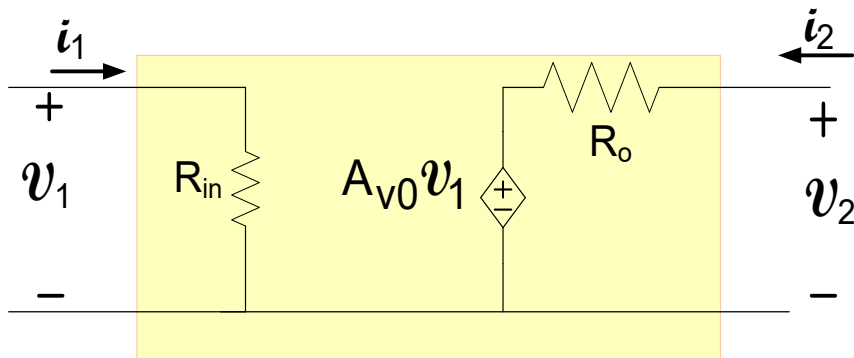

$\{R_{in}, A_{v0}$ and $R_o\}$




Impedance Range and Classification



The terms “High Impedance” and “ Low Impedance” are often used

Whether an impedance is considered high or low or mid-range is a relative assessment

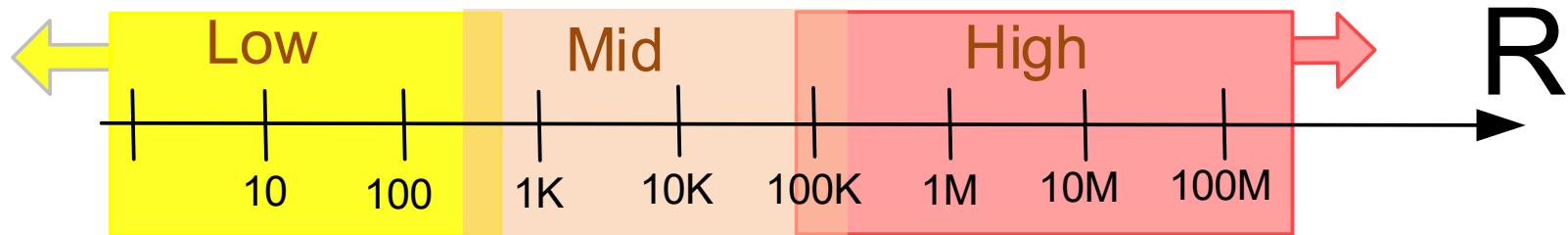When building MOS or BJT amplifiers, the following relative notation of impedance levels is often useful (though there may be some extreme applications where even this notation is not standard)




Impedance Range and Classification

Ideal Port Impedance of the four basic amplifiers

Amplifier Type	R_{IN}	R_{OUT}
Voltage	∞	0
Current	0	∞
Transconductance	∞	∞
Transresistance	0	0

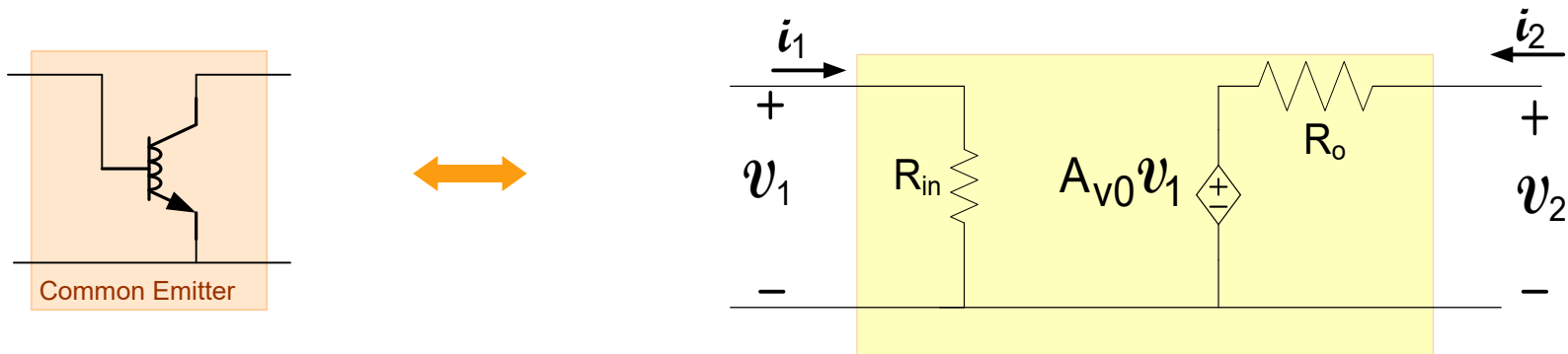Two-port model for Common Emitter Configuration



In terms of small signal model parameters:

$$R_{in} = \frac{1}{g_{\pi}} \quad A_{V0} = -\frac{g_m}{g_o} \quad R_o = \frac{1}{g_o} \quad A_{VR} = 0$$

In terms of operating point and model parameters:

$$R_i = \frac{\beta V_t}{I_{CQ}} \quad A_{V0} = -\frac{V_{AF}}{V_t} \quad R_o = \frac{V_{AF}}{I_{CQ}} \quad A_{VR} = 0$$




Characteristics:

- Input impedance is mid-range
- Voltage Gain is Large and Inverting
- Output impedance is large
- Unilateral
- Widely used to build voltage amplifiers

Common Emitter Configuration

Consider the following CE application

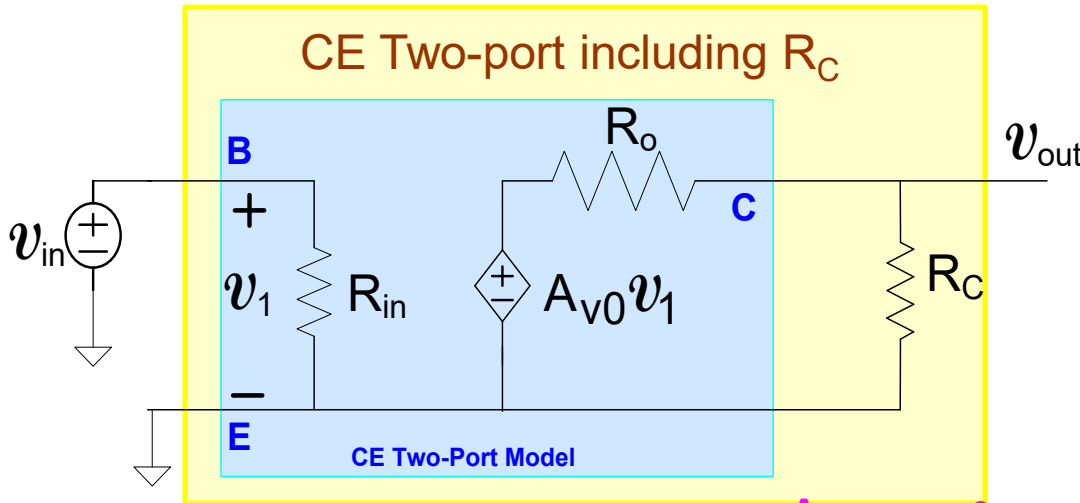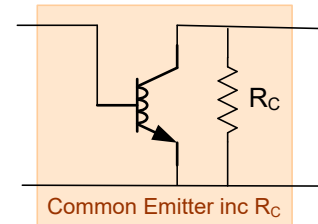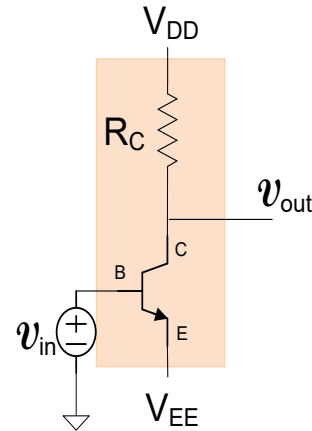(this will also generate a two-port model for this CE application)



$$g_C \stackrel{\text{def}}{=} \frac{1}{R_C}$$

$$\frac{g_o}{g_C} = \frac{I_{CQ} R_C}{V_{AF}} \ll 1$$

$$v_{out} (g_C + g_o) = g_o A_{V0} v_{in} \quad \xrightarrow{A_{VR} = 0} \quad A_{VC} = \frac{v_{out}}{v_{in}} = \frac{g_o A_{V0}}{g_o + g_C} = \frac{-g_m}{g_o + g_C} \stackrel{g_o \ll g_C}{\cong} -g_m R_C$$


$$R_{inC} = R_{in} = r_{\pi}$$

$$R_{outC} = R_o // R_C \quad \xrightarrow{\quad} \quad R_{outC} = R_o // R_C = \frac{1}{g_o + g_C} \stackrel{g_o \ll g_C}{\cong} R_C$$


Common Emitter Configuration

Consider the following CE application

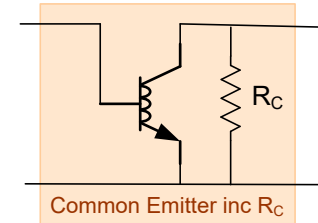(this will also generate a two-port model for this CE application)



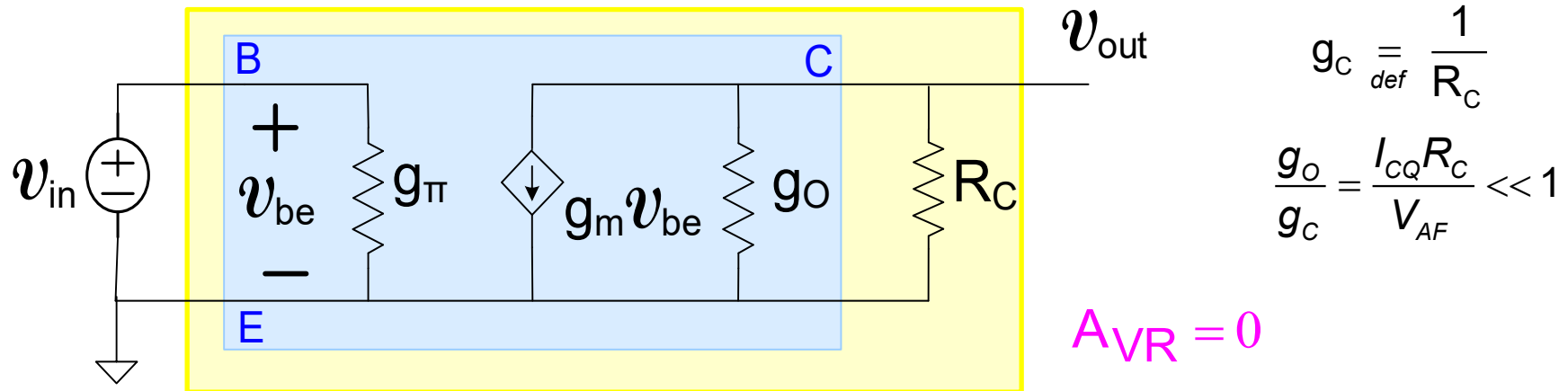This circuit can also be analyzed directly without using 2-port model for CE configuration (use standard 2-port transistor model instead)




$$v_{out} = -g_m v_{in} \left(\frac{1}{g_o + g_C} \right) \quad \longrightarrow \quad A_v = \frac{v_{out}}{v_{in}} = - \left(\frac{g_m}{g_o + g_C} \right) \stackrel{g_o \ll g_C}{\cong} -g_m R_C$$

$$R_{in} = r_{\pi} \qquad R_{out} = \frac{1}{g_o + g_C} \stackrel{g_o \ll g_C}{\cong} R_C$$

Common Emitter Configuration

Consider the following CE application

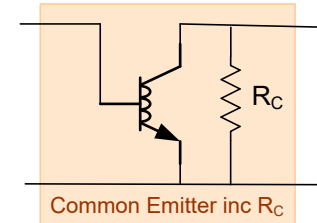(this is also a two-port model for this CE application)



Small-signal parameter domain

$$A_v \stackrel{g_0 \ll g_c}{\cong} -g_m R_C$$

$$R_{out} = \frac{1}{g_0 + g_c} \stackrel{g_0 \ll g_c}{\cong} R_C$$

$$R_{in} = r_{\pi}$$

$$A_{VR} = 0$$

Operating point and model parameter domain

$$A_v \stackrel{g_0 \ll g_c}{\cong} -\frac{I_{CQ} R_C}{V_t}$$


$$R_{out} \stackrel{g_0 \ll g_c}{\cong} R_C$$

$$R_{in} = \frac{\beta V_t}{I_{CQ}}$$

Characteristics:

- Input impedance is mid-range
- Voltage Gain is large and Inverting
- Output impedance is mid-range
- Unilateral
- Widely used as a voltage amplifier

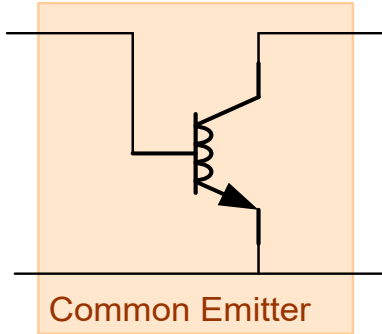Common Source/ Common Emitter Configurations



$$R_{in} = \frac{1}{g_{\pi}}$$


$$A_{V0} = -\frac{g_m}{g_o}$$

$$R_0 = \frac{1}{g_o}$$

$$A_{VR} = 0$$

$$A_{VR} = 0$$

$$R_{in} = \infty$$

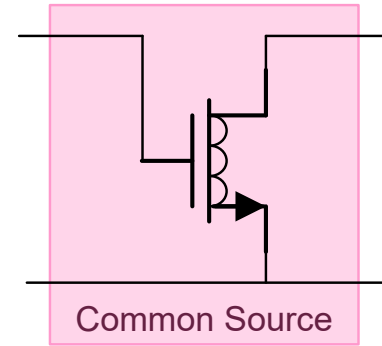

$$A_{V0} = -\frac{g_m}{g_o}$$

$$R_0 = \frac{1}{g_o}$$

In terms of operating point and model parameters:

$$R_{in} = \frac{\beta V_t}{I_{CQ}}$$

$$A_{V0} = -\frac{V_{AF}}{V_t}$$

$$R_0 = \frac{V_{AF}}{I_{CQ}}$$

$$R_{in} = \infty$$

$$R_0 = \frac{1}{\lambda I_{DQ}} = \frac{V_{AF}}{I_{DQ}}$$



$$A_{V0} = -\frac{2}{\lambda V_{EBQ}} = -2 \frac{V_{AF}}{V_{EBQ}}$$

Characteristics:

- Input impedance is mid-range (infinite for MOS)
- Voltage Gain is Large and Inverting
- Output impedance is large
- Unilateral
- Widely used to build voltage amplifiers

Common Source/Common Emitter Configuration

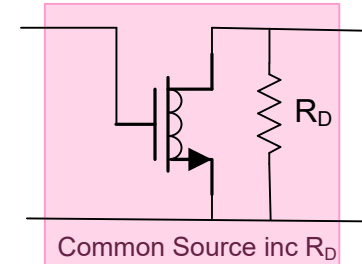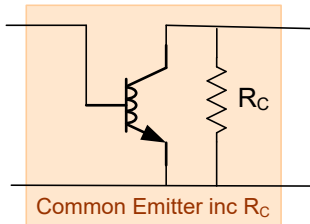Widely used CE application (but also a two-port)



$$R_{out} = \frac{1}{g_0 + g_C} \stackrel{g_0 \ll g_C}{\cong} R_C$$

$$A_v \stackrel{g_0 \ll g_C}{\cong} -g_m R_C$$

$$R_{in} = r_{\pi}$$

$$A_{VR} = 0 \quad | \quad A_{VR} = 0$$

$$R_{out} = \frac{1}{g_0 + g_D} \stackrel{g_0 \ll g_D}{\cong} R_D$$

$$A_v \stackrel{g_0 \ll g_D}{\cong} -g_m R_D$$

$$R_{in} = \infty$$

In terms of operating point and model parameters:

$$A_v \stackrel{g_0 \ll g_C}{\cong} -\frac{I_{CQ} R_C}{V_t}$$

$$R_{out} \stackrel{g_0 \ll g_C}{\cong} R_C$$

$$R_{in} = \frac{\beta V_t}{I_{CQ}}$$

$$A_v \stackrel{g_0 \ll g_D}{\cong} -\frac{2I_{DQ} R_D}{V_{EBQ}}$$







$$R_{in} = \infty$$

$$R_{out} \stackrel{g_0 \ll g_D}{\cong} R_D$$

Characteristics:




- Input impedance is mid-range (infinite for MOS)
- Voltage Gain is Large and Inverting
- Output impedance is mid-range
- Unilateral
- Widely used as a voltage amplifier

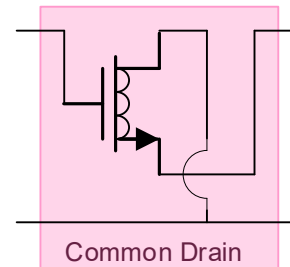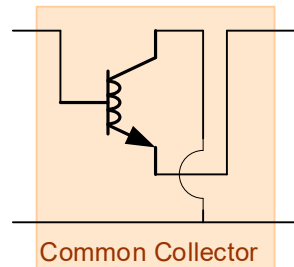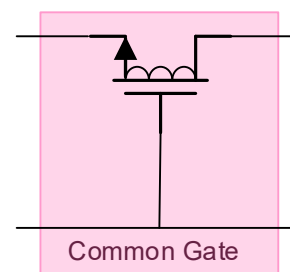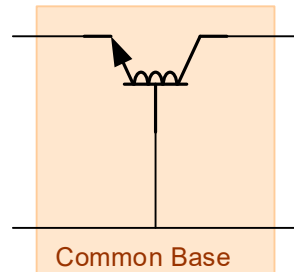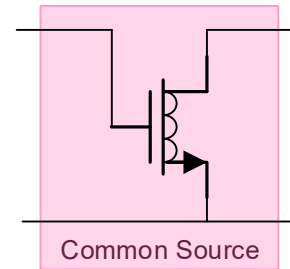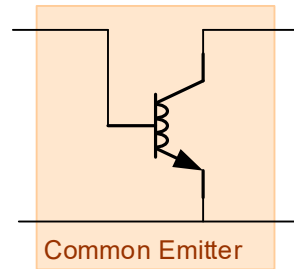Consider Common Collector/Common Drain Two-port Models



- Will focus on Bipolar Circuit since MOS counterpart is a special case obtained by setting $g_{\pi}=0$
- Will consider both two-port model and a widely used application

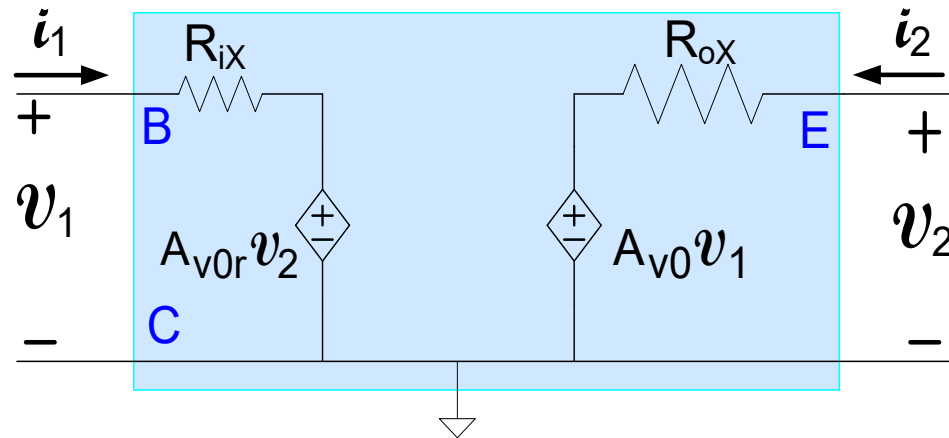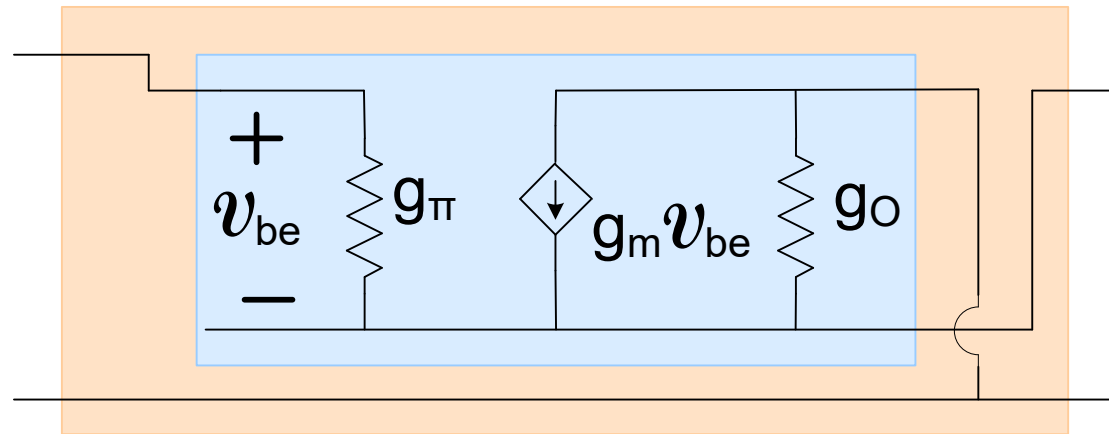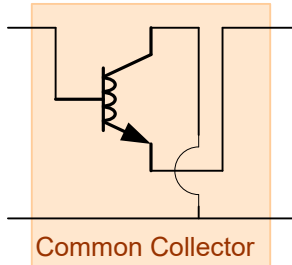
Two-port model for Common Collector Configuration



$\{R_{ix}, A_{v0}, A_{v0r} \text{ and } R_{ox}\}$

Two-Port Models of Basic Amplifiers widely used for Analysis and Design of Amplifier Circuits

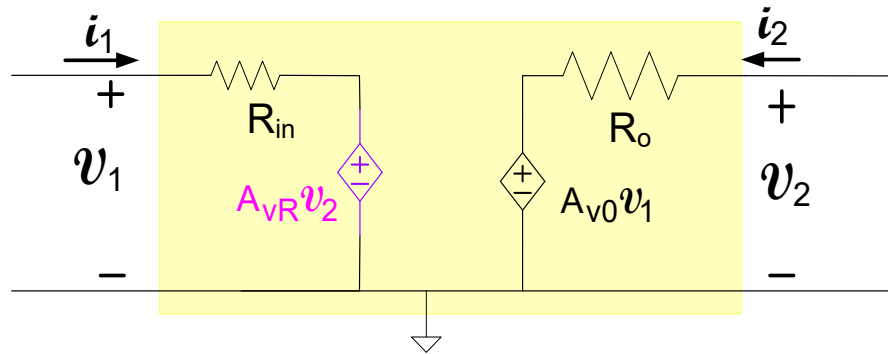Methods of Obtaining Amplifier Two-Port Network



1. $v_{TEST} : i_{TEST}$ Method



2. Write $v_1 : v_2$ equations in standard form


$$v_1 = i_1 R_{IN} + A_{VR} v_2$$

$$v_2 = i_2 R_O + A_{V0} v_1$$

3. Thevenin-Norton Transformations

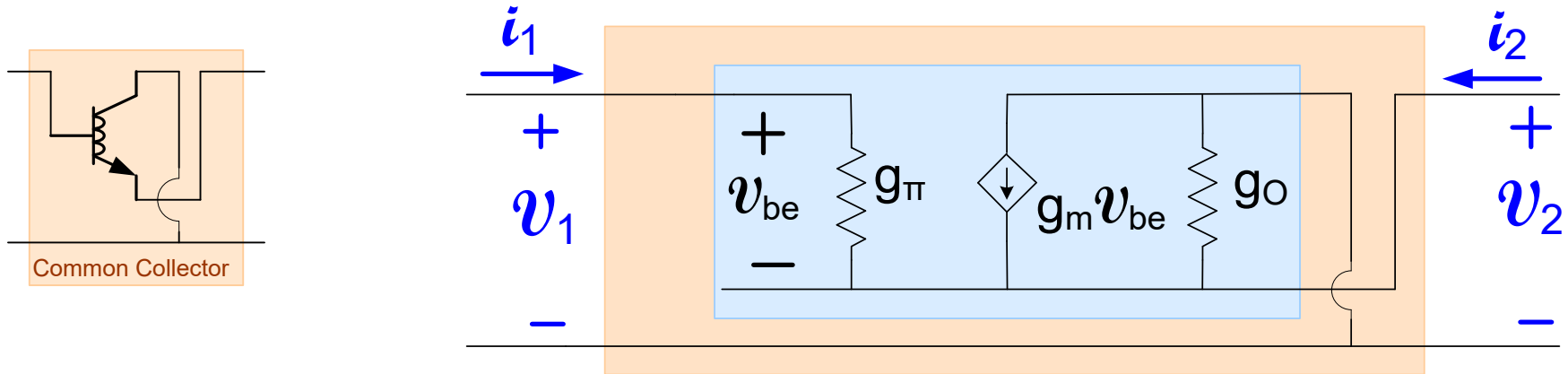4. Ad Hoc Approaches

Two-port model for Common Collector Configuration




Applying KCL at the input and output node, obtain

$$\left. \begin{aligned} i_1 &= (v_1 - v_2)g_\pi \\ i_2 &= (g_m + g_\pi + g_o)v_2 - (g_m + g_\pi)v_1 \end{aligned} \right\}$$

These can be rewritten as

$$\left. \begin{aligned} v_1 &= i_1 r_\pi + v_2 \\ v_2 &= \left(\frac{1}{g_m + g_\pi + g_o} \right) i_2 + \left(\frac{g_m + g_\pi}{g_m + g_\pi + g_o} \right) v_1 \end{aligned} \right\}$$

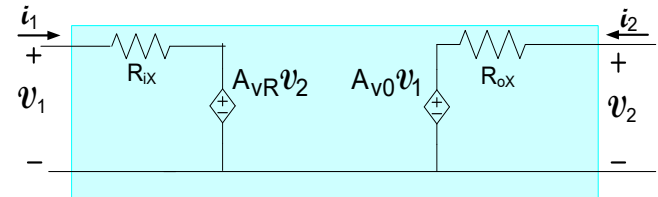Standard Two-Port Amplifier Representation



$$v_1 = i_1 R_{ix} + A_{VR} v_2$$




$$v_2 = i_2 R_{ox} + A_V v_1$$

$v_1 : v_2$ equations in standard form

It thus follows that

$$R_{ix} = r_\pi \quad A_{VR} = 1 \quad R_{ox} = \left(\frac{1}{g_m + g_\pi + g_o} \right) \quad A_{V0} = \left(\frac{g_m + g_\pi}{g_m + g_\pi + g_o} \right)$$

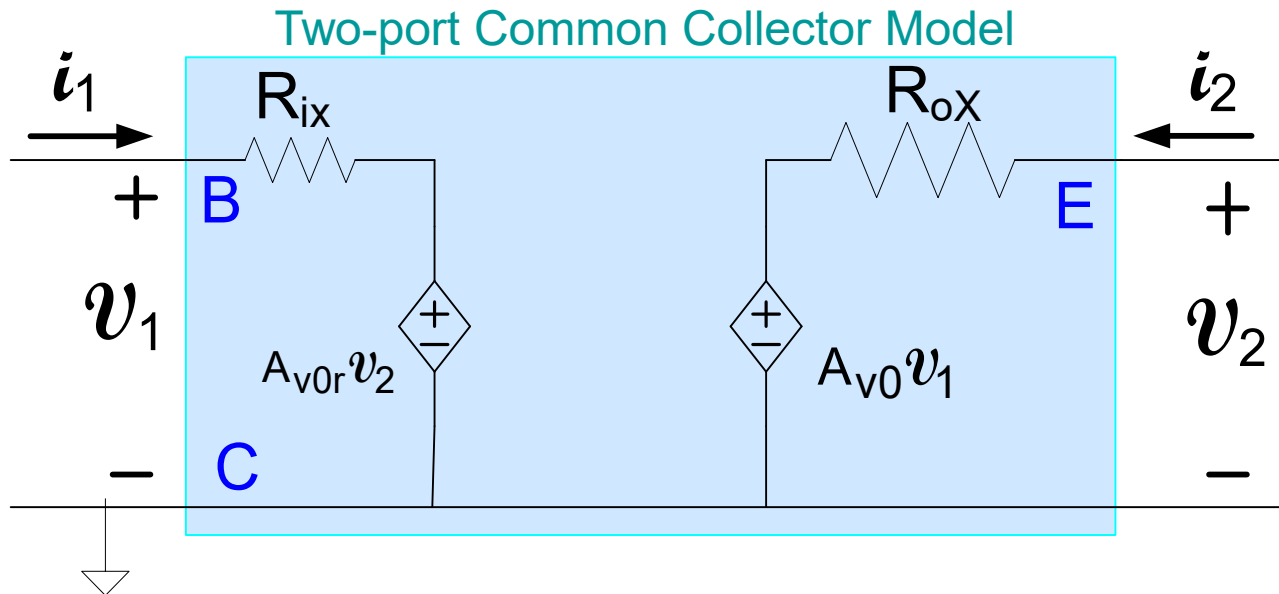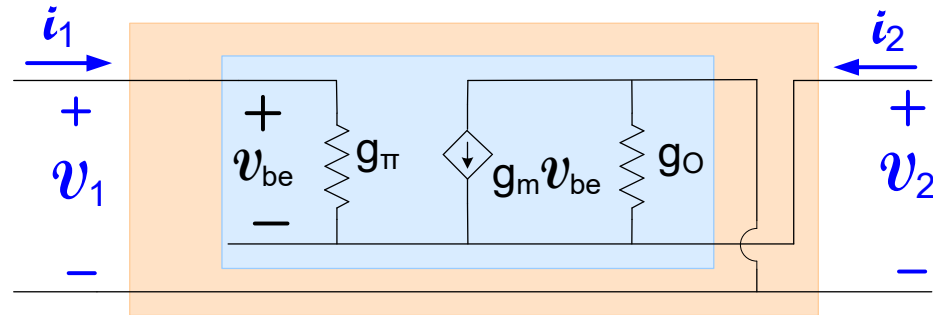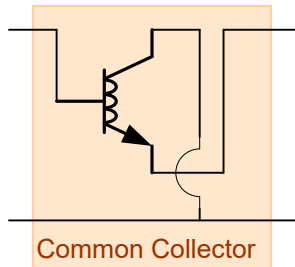Two-port model for Common Collector Configuration





$$R_{iX} = r_{\pi}$$

$$A_{V0r} = 1$$

$$R_{oX} = \left(\frac{1}{g_m + g_{\pi} + g_o} \right) \cong \frac{1}{g_m}$$

$$A_{V0} = \left(\frac{g_m + g_{\pi}}{g_m + g_{\pi} + g_o} \right) \cong 1$$

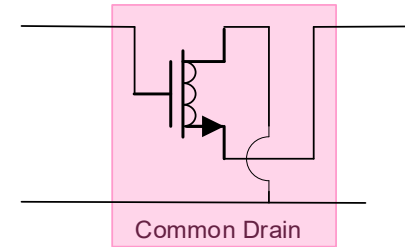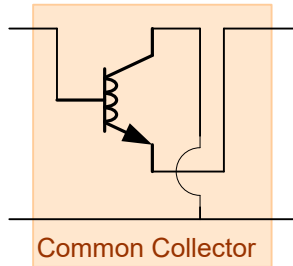Two-port model for Common Collector Configuration



		$A_{VR} = 1$	$A_{VR} = 1$		
$R_{in} = r_{\pi}$	$A_{V0} = 1$	$R_0 = \frac{1}{g_m}$		$R_{in} = \infty$	$A_{V0} = 1$
					$R_0 = \frac{1}{g_m}$

In terms of operating point and model parameters:

$R_{in} = \frac{\beta V_t}{I_{CQ}}$	$A_{V0} = 1$	$R_0 = \frac{V_t}{I_{CQ}}$		$R_{in} = \infty$	$A_{V0} = 1$	$R_0 = \frac{V_{EB}}{2I_{DQ}}$
-------------------------------------	--------------	----------------------------	--	-------------------	--------------	--------------------------------

Characteristics:




- Input impedance is mid-range (infinite for MOS)
- Voltage Gain is nearly 1
- Output impedance is very low
- Slightly non-unilateral (critical though in increasing input impedance when R_E added)
- Widely used as a buffer

Common Collector Configuration

Consider the following popular CC application

Determine R_{in} , R_o , and A_v

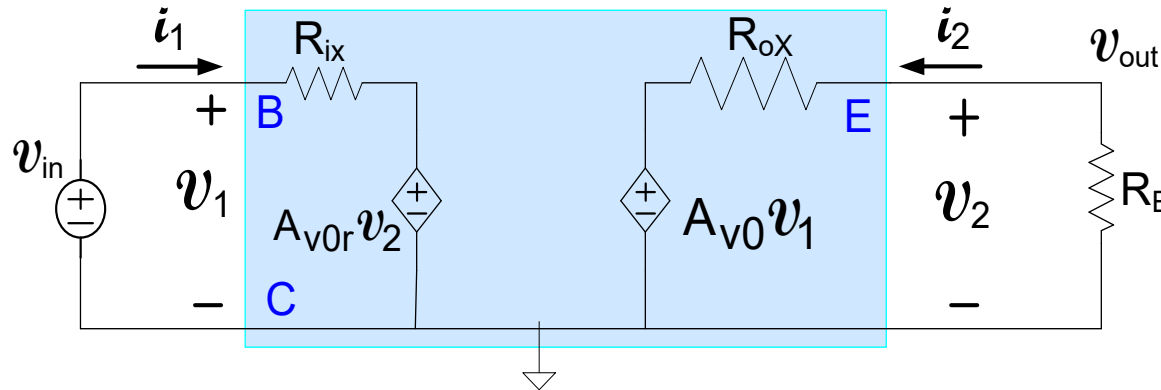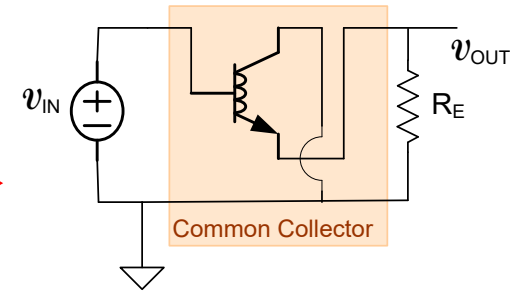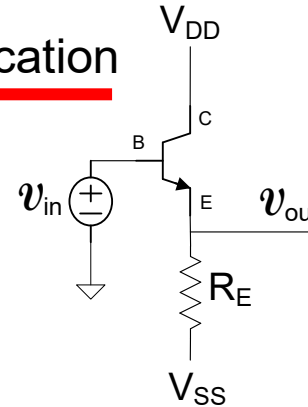(this is not asking for a two-port model for the CC application – R_{in} and A_v defined for no additional load on output, R_o defined for short-circuit input)



$$\frac{g_m}{g_{RE}} = \frac{I_{CQ} R_E}{V_t} \gg 1$$

$$A_v = A_{V0} \frac{g_{ox}}{g_{ox} + g_{RE}} = \frac{g_m + g_\pi}{g_m + g_\pi + g_o} \left(\frac{g_m + g_\pi + g_o}{g_m + g_\pi + g_o + g_{RE}} \right) = \frac{g_m + g_\pi}{g_m + g_\pi + g_o + g_{RE}} \cong \frac{g_m}{g_m + g_{RE}} \cong 1 \quad \text{if } g_m \gg g_{RE}$$


$$v_{in} = i_1 R_{ix} + A_{V0r} A_{V0} \frac{g_{oX}}{g_{oX} + g_{RE}} v_{in} \quad \rightarrow \quad R_{in} = \frac{r_\pi}{1 - \frac{g_m + g_\pi}{g_m + g_\pi + g_o + g_{RE}}} = r_\pi \frac{g_m + g_\pi + g_o + g_{RE}}{g_o + g_{RE}} \cong r_\pi + \beta R_E \quad \text{if } g_{RE} \gg g_o$$

$$R_o \cong \frac{1}{g_m + g_{RE} + g_o + g_\pi} = \frac{1}{g_m + g_{RE}} = \frac{R_E}{1 + g_m R_E} \cong \frac{1}{g_m} \quad \text{if } g_m \gg g_{RE}$$


Common Collector Configuration

Consider the following popular CC application

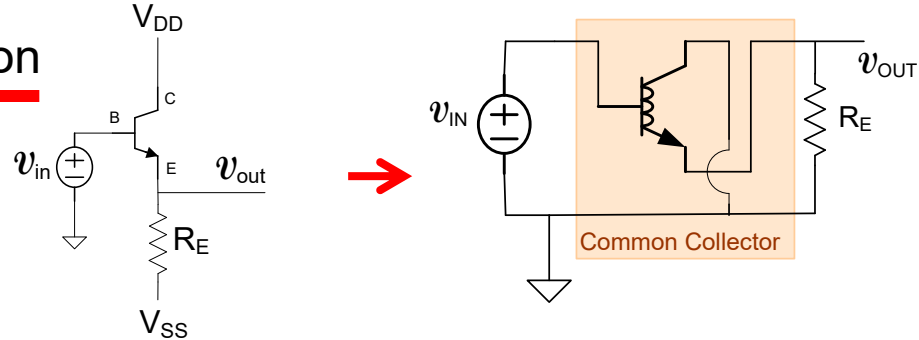(this is not asking for a two-port model for the CC application, - R_{in} and A_v defined for no additional load on output, R_o defined for short-circuit input -)



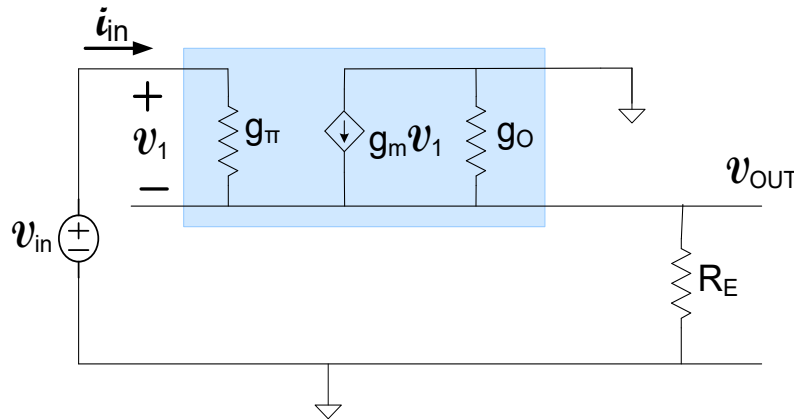Alternately, this circuit can also be analyzed directly



$$\frac{g_m}{g_{RE}} = \frac{I_{CQ}R_E}{V_t} \gg 1$$

$$v_{out}(g_{RE} + g_o + g_\pi) = v_{in}g_\pi + g_m v_1$$

$$v_{in} = v_1 + v_{out}$$

$$i_{in} = g_\pi(v_{in} - v_{out})$$

$$v_{out}(g_m + g_{RE} + g_o + g_\pi) = v_{in}(g_\pi + g_m)$$

$$v_{out}(g_m + g_{RE} + g_o + g_\pi) = v_{in}(g_\pi + g_m)$$

$$A_v = \frac{g_\pi + g_m}{g_m + g_{RE} + g_o + g_\pi} \cong \frac{g_m}{g_m + g_{RE}} = \frac{I_{CQ}R_E}{I_{CQ}R_E + V_t} \cong 1$$




$$i_{in}(g_m + g_\pi + g_{RE} + g_o) = g_\pi v_{in}(g_{RE} + g_o)$$

$$R_{in} = r_\pi \frac{g_m + g_\pi + g_o + g_{RE}}{g_o + g_{RE}} \stackrel{\substack{g_{RE} \gg g_o \\ \beta \gg 1}}{\cong} r_\pi + \beta R_E$$

Common Collector Configuration

Consider the following popular CC application

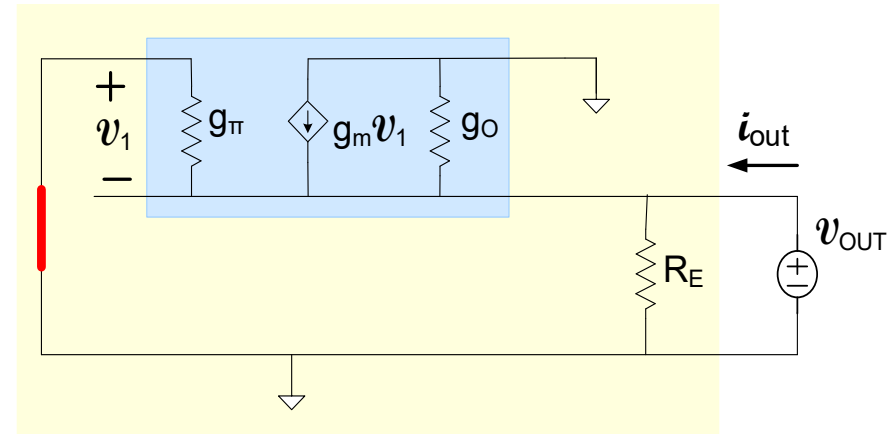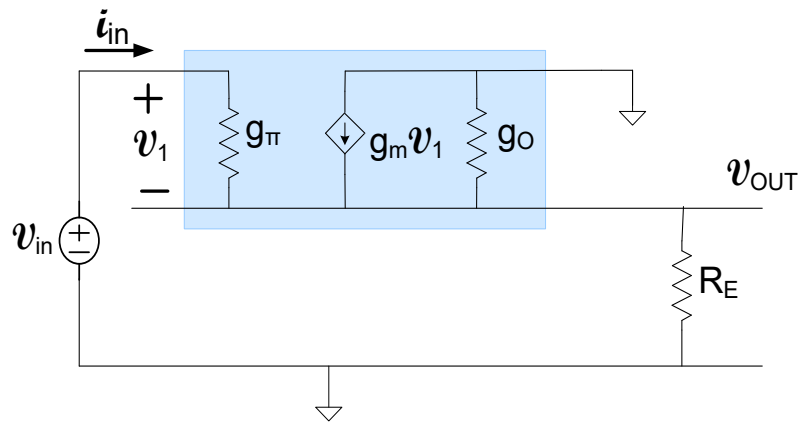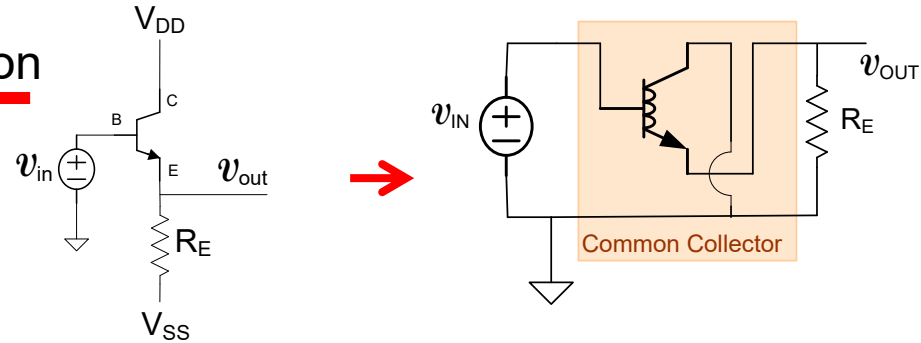(this is not asking for a two-port model for the CC application, - R_{in} and A_v defined for no additional load on output, R_o defined for short-circuit input -)



To obtain R_o , set $v_{in} = 0$

$$\frac{g_m}{g_{RE}} = \frac{I_{CQ} R_E}{V_t} \gg 1$$



$$i_{out} = v_{out} (g_{RE} + g_o + g_\pi) - g_m (-v_{out})$$

$$R_{out} = \frac{1}{g_m + g_\pi + g_o + g_{RE}} \stackrel{g_E \ll g_m}{\cong} \frac{1}{g_m}$$

Common Collector Configuration

Consider the following popular CC application

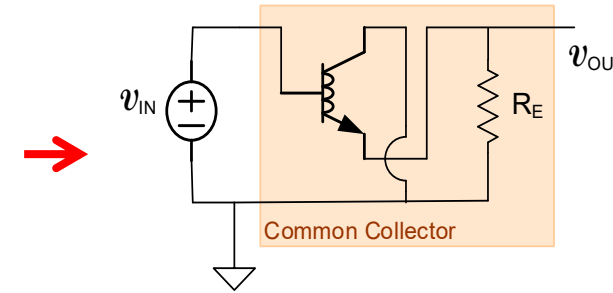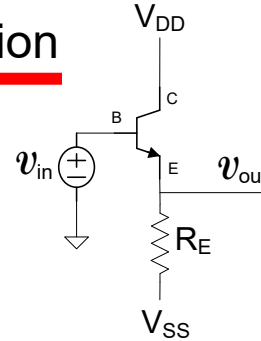(this is not asking for a two-port model for the CC application, - R_{in} and A_v defined for no additional load on output, R_o defined for short-circuit input -)




$$A_v = \frac{g_\pi + g_m}{g_m + g_{RE} + g_o + g_\pi} \cong \frac{g_m}{g_m + g_{RE}} = \frac{I_{CQ}R_E}{I_{CQ}R_E + V_t} \cong 1$$

$$R_{in} = r_\pi \frac{g_m + g_\pi + g_o + g_{RE}}{g_o + g_{RE}} \stackrel{g_{RE} \gg g_o}{\cong} r_\pi + \beta R_E$$

$$R_{out} = \frac{1}{g_m + g_\pi + g_o + g_{RE}} \stackrel{g_E \ll g_o}{\cong} \frac{1}{g_m}$$

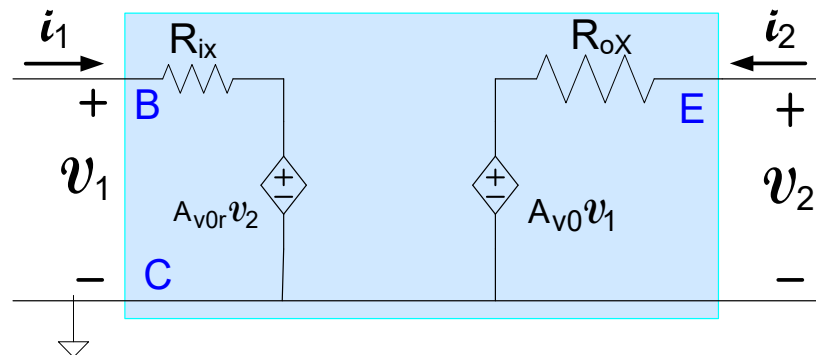Question: Why are these not the two-port parameters of this circuit?


- R_{in} defined for open-circuit on output instead of short-circuit (see previous slide : -2 slides)
- $A_{v0r} \neq 0$



Common Collector Configuration with R_C

Consider the following popular CC application

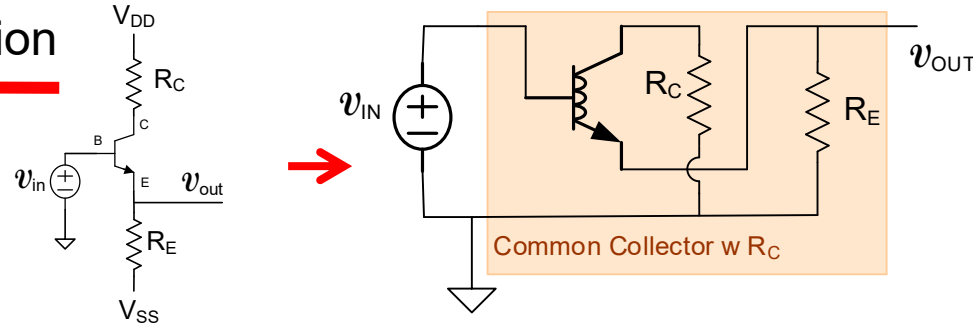(though not real common, sometimes a resistor is included in the collector)



It can be readily shown that unless R_C is very large, it has little effect on the performance and have same expressions for A_V , R_{IN} , and R_{OUT}

$$A_V \cong \frac{g_m}{g_m + g_E} = \frac{I_{CQ} R_E}{I_{CQ} R_E + V_t} \cong 1$$

$$R_{in} \cong r_{\pi} + \beta R_E$$



$$R_{out} \cong \frac{1}{g_m}$$

Intuitively this can be expected since if g_0 is neglected, R_C is in series with a current source in the ss BJT model

Common Collector Configuration

For this popular CC application

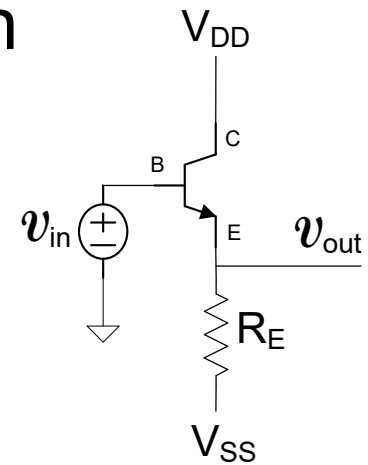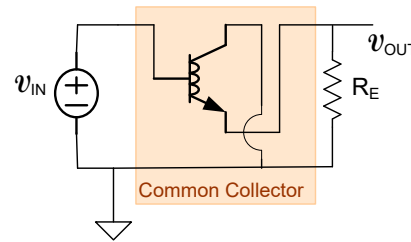(this is not a two-port model for this CC application)



Small signal parameter domain

$$A_V = \frac{g_\pi + g_m}{g_m + g_{RE} + g_0 + g_\pi} \stackrel{\text{if } g_m \gg g_{RE}}{\cong} 1$$

$$R_{in} \stackrel{g_E \gg g_0}{\cong} r_\pi + \beta R_E$$

$$R_0 \cong \frac{R_E}{1 + g_m R_E} \stackrel{g_m R_E \gg 1}{\cong} \frac{1}{g_m}$$

Operating point and model parameter domain

$$A_V \cong \frac{I_{CQ} R_E}{I_{CQ} R_E + V_t} \stackrel{I_{CQ} R_E \gg V_t}{\cong} 1$$

$$R_{in} \stackrel{I_{CQ} R_E \gg V_t}{\cong} r_\pi + \beta R_E$$


$$R_0 \stackrel{I_{CQ} R_E \gg V_t}{\cong} \frac{V_t}{I_{CQ}}$$

Characteristics:

- Output impedance is low
- A_{V0} is positive and near 1
- Input impedance is very large
- Widely used as a buffer
- Not completely unilateral but output-input transconductance (or A_{Vr}) is small and effects are generally negligible though magnitude same as A_V

Common Collector/Common Drain Configurations

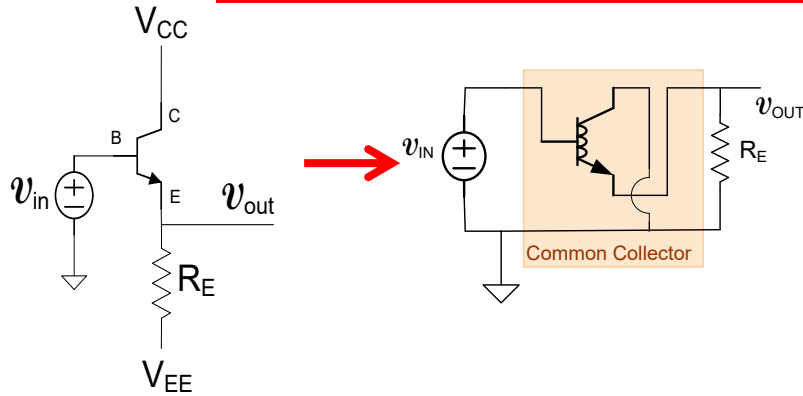For these popular CC/CD applications (not two-port models for these applications)



$$A_V = \frac{g_\pi + g_m}{g_m + g_E + g_0 + g_\pi} \quad \text{if } g_m \gg g_E \cong 1$$


$$R_{in} \stackrel{g_E \gg g_0}{\cong} r_\pi + \beta R_E$$

$$R_0 \cong \frac{R_E}{1 + g_m R_E} \stackrel{g_m R_E \gg 1}{\cong} \frac{1}{g_m}$$

In terms of operating point and model parameters:

$$A_V \cong \frac{I_{CQ} R_E}{I_{CQ} R_E + V_t} \stackrel{I_{CQ} R_E \gg V_t}{\cong} 1 \quad R_0 \cong \frac{V_t}{I_{CQ}}$$
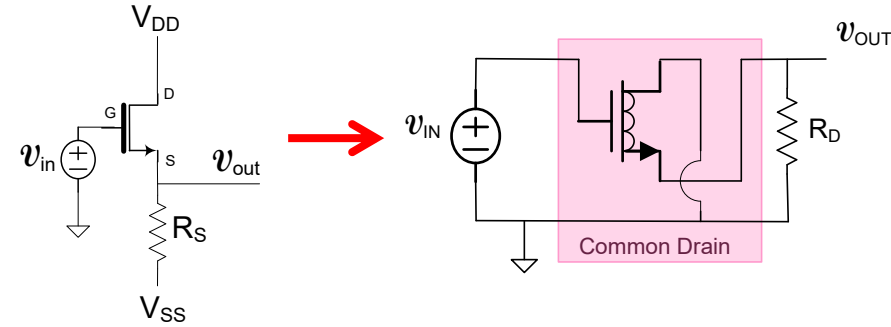
$$R_{in} \stackrel{I_{CQ} R_E \gg V_t}{\cong} r_\pi + \beta R_E$$



$$A_V = \frac{g_m}{g_m + g_S + g_0} \quad \text{if } g_m \gg g_S \cong 1$$

$$R_{in} = \infty$$

$$R_0 \cong \frac{R_S}{1 + g_m R_S} \stackrel{g_m R_S \gg 1}{\cong} \frac{1}{g_m}$$

$$A_V \cong \frac{2I_{DQ} R_S}{2I_{DQ} R_S + V_{EBQ}} \stackrel{\text{if } 2I_{DQ} R_S \gg V_{EBQ}}{\cong} 1$$

$$R_0 \cong \frac{V_{EBQ} R_S}{V_{EBQ} + 2I_{DQ} R_S} \stackrel{2I_{DQ} R_S \gg V_{EBQ}}{\cong} \frac{V_{EBQ}}{2I_{DQ}}$$

$$R_{in} = \infty$$

- Output impedance is low
- A_{V0} is positive and near 1
- Input impedance is very large







- Widely used as a buffer
- Not completely unilateral but output-input transconductance is small



Stay Safe and Stay Healthy !



End of Lecture 31

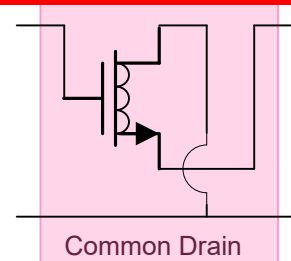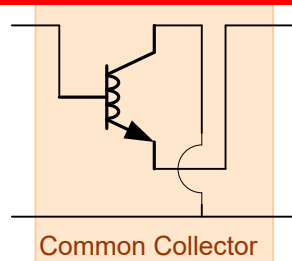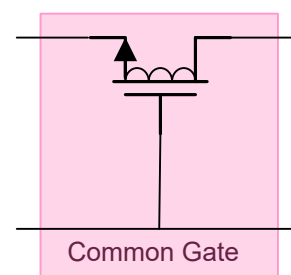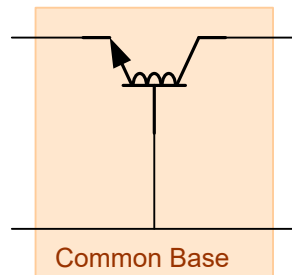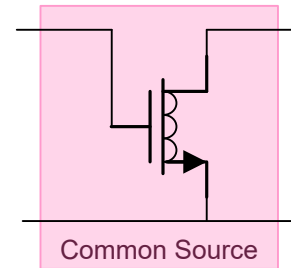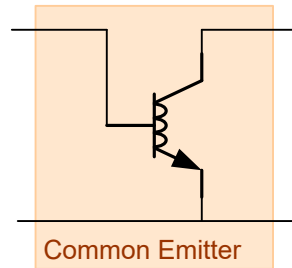Consider Common Base/Common Gate Two-port Models



- Will focus on Bipolar Circuit since MOS counterpart is a special case obtained by setting $g_{\pi}=0$
- Will consider both two-port model and a widely used application

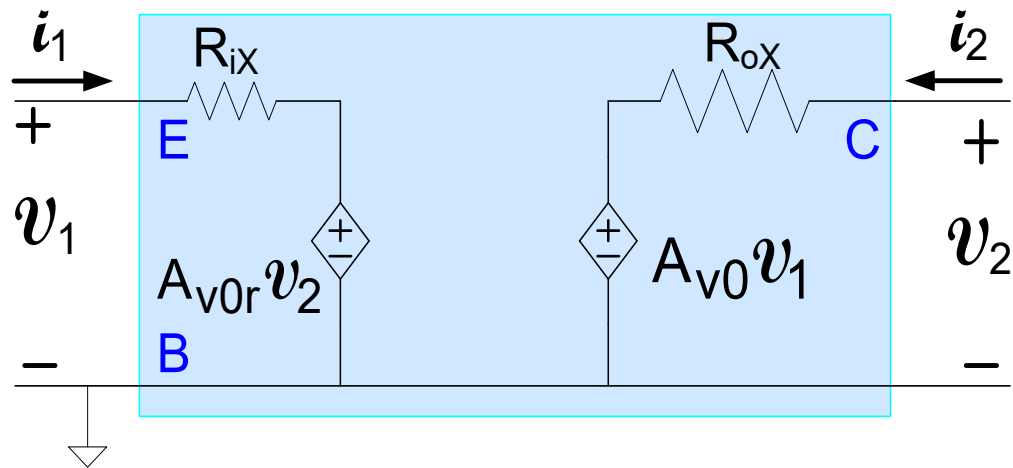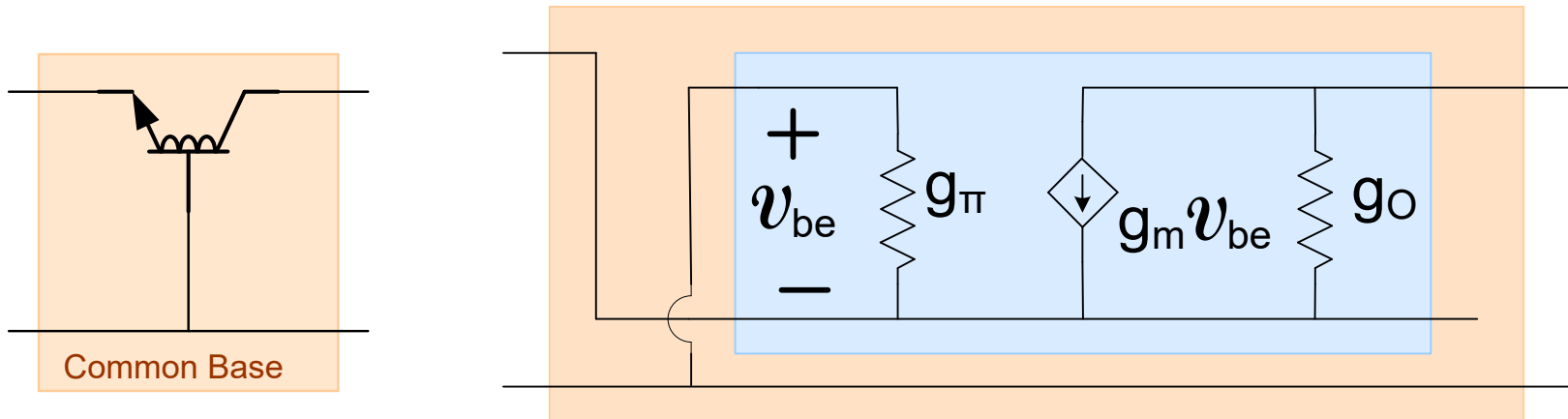
Two-port model for Common Base Configuration



$\{R_{ix}, A_{v0}, A_{v0r} \text{ and } R_{ox}\}$

Two-Port Models of Basic Amplifiers widely used for Analysis and Design of Amplifier Circuits

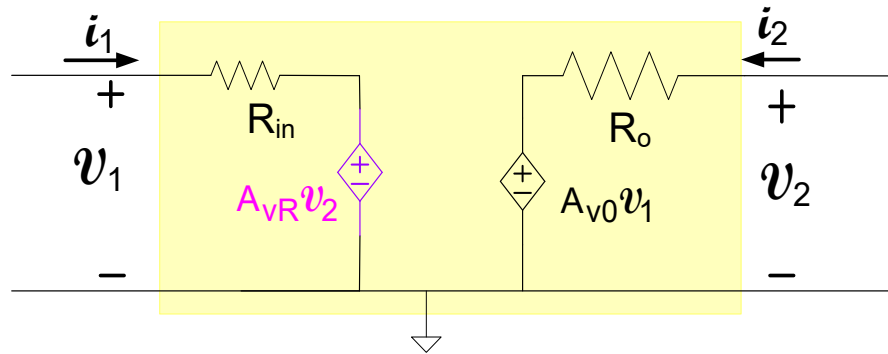Methods of Obtaining Amplifier Two-Port Network



1. $v_{TEST} : i_{TEST}$ Method



2. Write $v_1 : v_2$ equations in standard form


$$v_1 = i_1 R_{IN} + A_{VR} v_2$$

$$v_2 = i_2 R_O + A_{V0} v_1$$

3. Thevenin-Norton Transformations

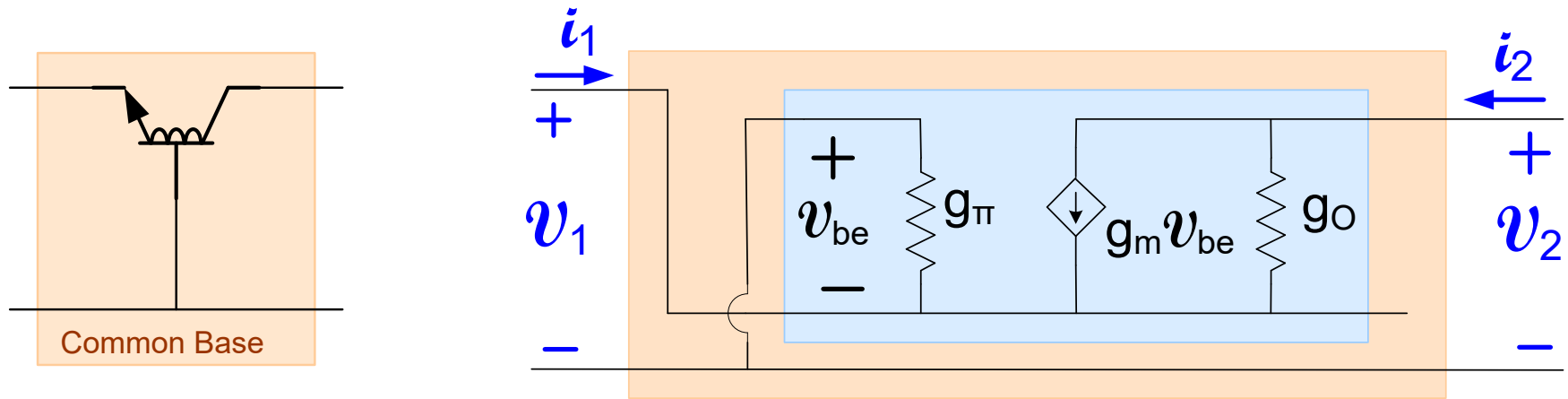4. Ad Hoc Approaches

Two-port model for Common Base Configuration



From KCL

$$\left. \begin{aligned} i_1 &= v_1 g_\pi + (v_1 - v_2) g_o + g_m v_1 \\ i_2 &= (v_2 - v_1) g_o - g_m v_1 \end{aligned} \right\}$$

These can be rewritten as


$$v_1 = \left(\frac{1}{g_m + g_\pi + g_o} \right) i_1 + \left(\frac{g_o}{g_m + g_\pi + g_o} \right) v_2$$

$$v_2 = \left(\frac{1}{g_o} \right) i_2 + \left(1 + \frac{g_m}{g_o} \right) v_1$$

It thus follows that:



$$R_{iX} = \frac{1}{g_m + g_\pi + g_o} \cong \frac{1}{g_m} \quad A_{VOr} = \frac{g_o}{g_m + g_\pi + g_o} \quad A_{V0} = 1 + \frac{g_m}{g_o} \cong \frac{g_m}{g_o} \quad R_{oX} = \frac{1}{g_o}$$

Standard Form for Amplifier Two-Port

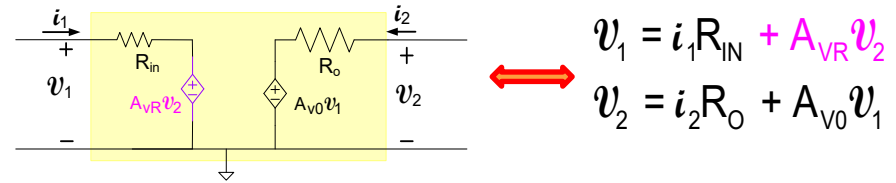


$v_1 : v_2$ equations in standard form

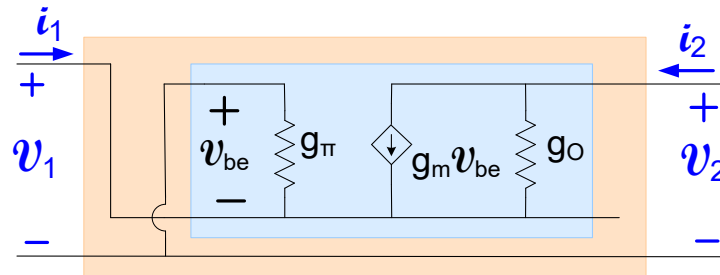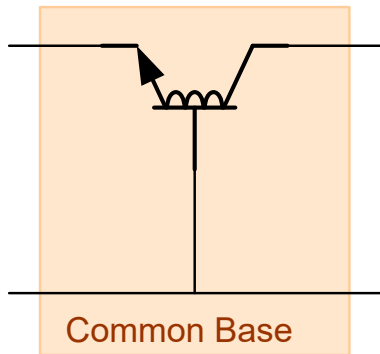Two-port model for Common Base Configuration



Two-port Common Base Model

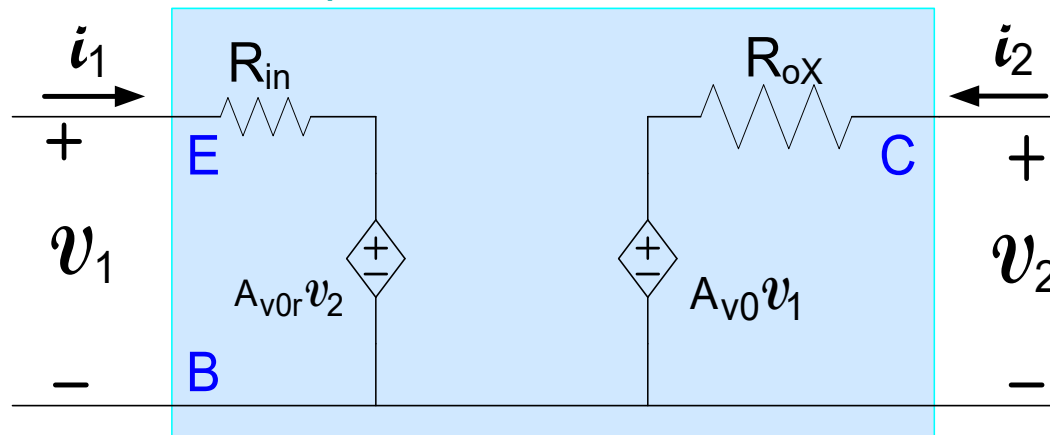

$$R_{iX} = \frac{1}{g_m + g_\pi + g_o} \cong \frac{1}{g_m}$$

$$A_{V0} = 1 + \frac{g_m}{g_o} \cong \frac{g_m}{g_o}$$



$$A_{V0r} = \frac{g_o}{g_m + g_\pi + g_o} \cong \frac{g_o}{g_m}$$

$$R_{oX} = \frac{1}{g_o}$$

Common Base Configuration

Consider the following popular CB application

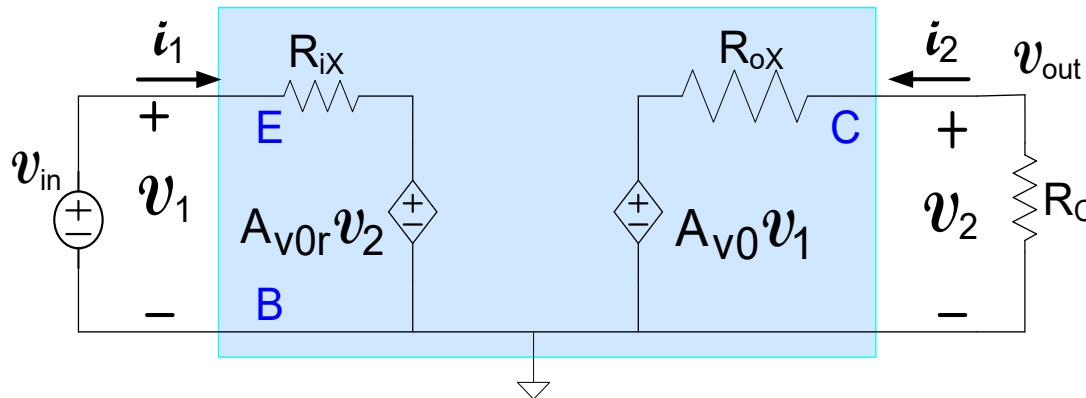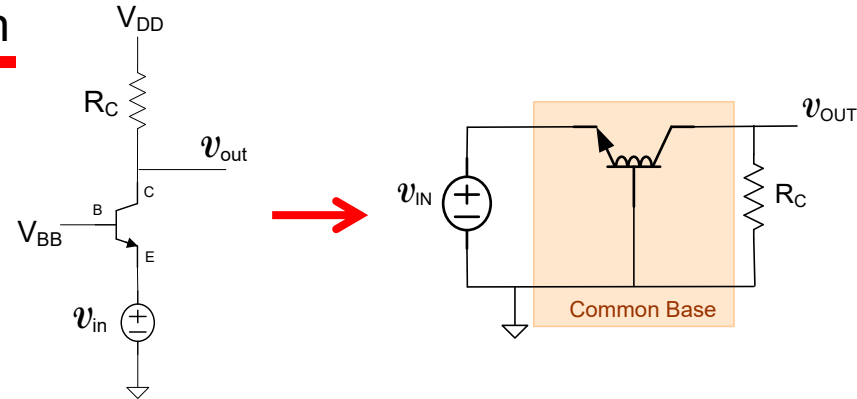(this is not asking for a two-port model for this CB application - - R_{in} and A_V defined for no load on output, R_o defined for short-circuit input)



$$A_V = A_{V0} \frac{R_C}{R_C + R_{0X}} = \left(\frac{g_m + g_0}{g_0} \right) \left(\frac{g_0}{g_C + g_0} \right) = \frac{g_m + g_0}{g_C + g_0} \cong g_m R_C$$


$$R_{in} = \frac{v_{in}}{i_1} = \frac{i_1 R_{iX} + A_{V0} v_{out}}{i_1} \longrightarrow R_{in} = \frac{R_{iX}}{1 - A_{V0} A_V} = \frac{g_0 + g_C}{g_C (g_m + g_\pi + g_0) + g_\pi g_0} \cong \frac{1}{g_m}$$

$$R_{out} = R_C // R_{0X} \longrightarrow R_{out} = \frac{R_C}{1 + g_0 R_C}$$


Common Base Configuration

Consider the following popular CB application

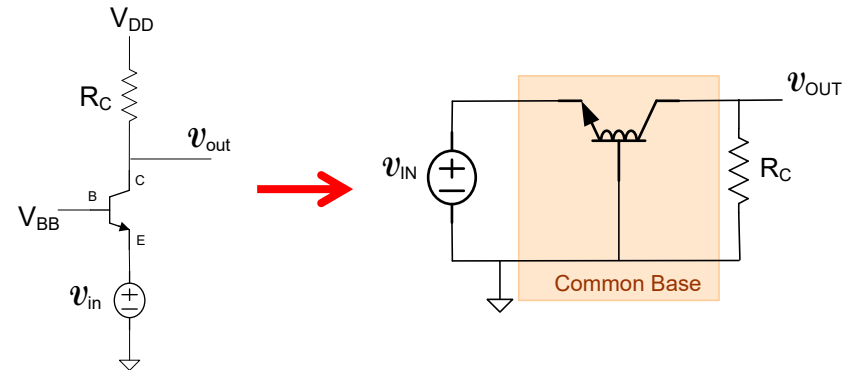(this is not asking for a two-port model for this CB application – R_{in} and A_V defined for no load on output, R_o defined for short-circuit input)



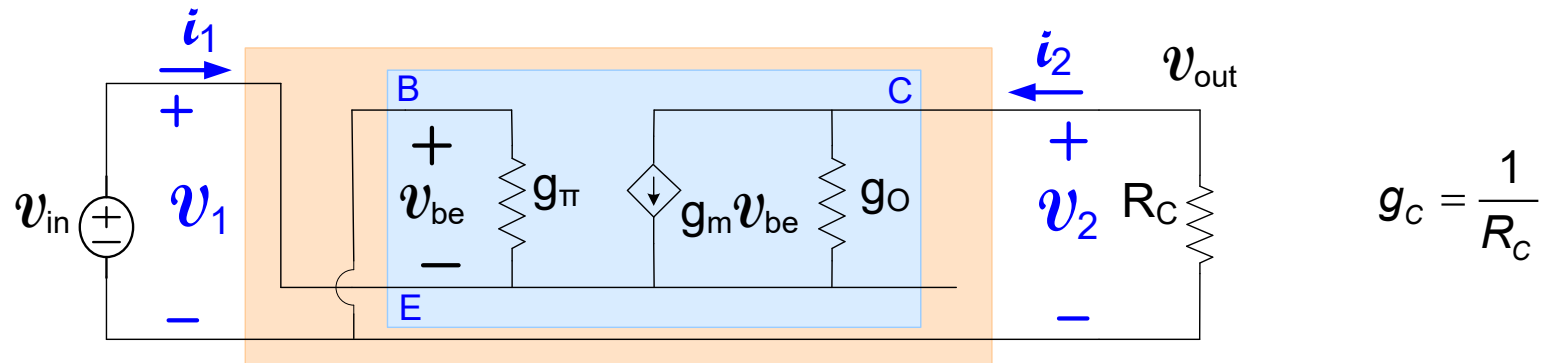Alternately, this circuit can also be analyzed directly with BJT model



By KCL at the output node, obtain

$$(g_C + g_0) v_0 = (g_m + g_0) v_{in} \quad \longrightarrow \quad A_V = \frac{g_m + g_0}{g_C + g_0} \cong g_m R_C$$


By KCL at the emitter node, obtain

$$i_1 = (g_m + g_\pi + g_0) v_{in} - g_0 v_{out} \quad \longrightarrow \quad R_{in} = \frac{g_0 + g_C}{g_C (g_m + g_\pi + g_0) + g_\pi g_0} \cong \frac{1}{g_m}$$

$$R_{out} = R_C // r_0 \quad \longrightarrow \quad R_{out} = \frac{R_C}{1 + g_0 R_C} \cong R_C$$

Popular Common Base Application

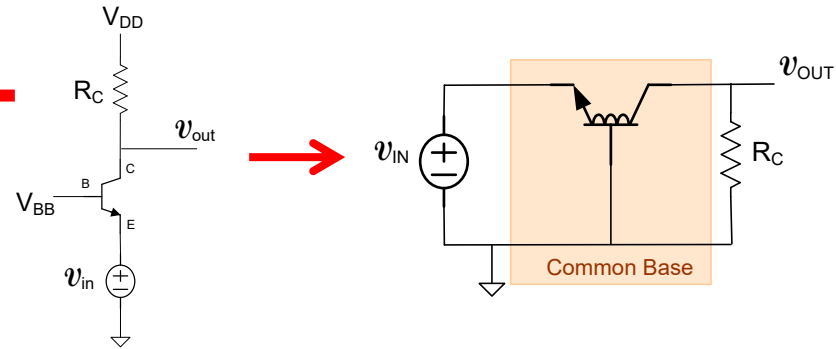(this is not a two-port model for this CB application)



$$A_V \cong g_m R_C$$
$$R_{in} \cong \frac{1}{g_m}$$
$$R_{out} \cong R_C$$

$R_c \ll r_o$

$$A_V \cong \frac{I_{CQ} R_C}{V_t}$$
$$R_{in} \cong \frac{V_t}{I_{CQ}}$$
$$R_{out} \cong R_C$$


$R_c \ll r_o$

Characteristics:


- Output impedance is mid-range
- A_{V0} is large and positive (equal in mag to that to CE)
- Input impedance is very low
- Not completely unilateral but output-input transconductance is small

Common Base/Common Gate Application

(these are not a two-port models)

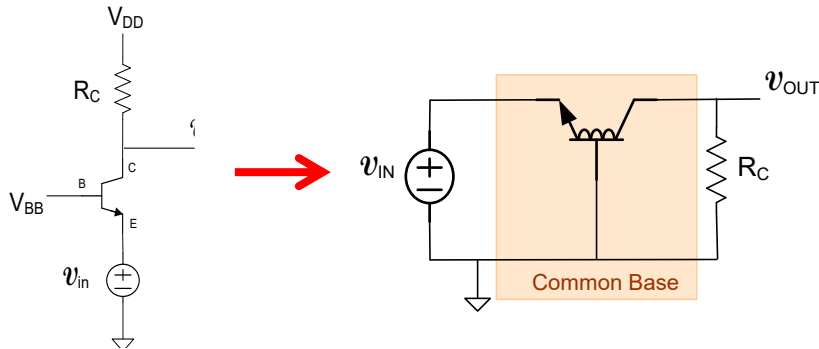
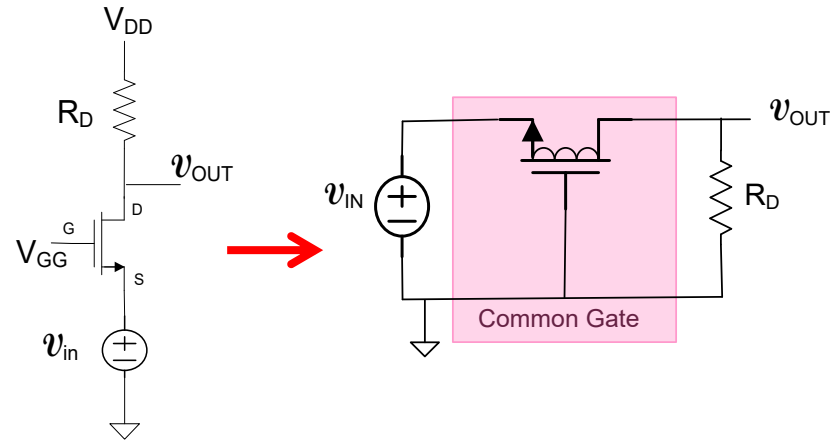
$$A_V \cong g_m R_C \quad R_{in} \cong \frac{1}{g_m} \quad R_{out} \cong R_C \quad R_C \ll r_o$$



$$A_V \cong g_m R_D \quad R_{in} \cong \frac{1}{g_m} \quad R_{out} \cong R_D \quad R_D \ll r_o$$

In terms of operating point and model parameters:


$$A_V \cong \frac{I_{CQ} R_C}{V_t} \quad R_{in} \cong \frac{V_t}{I_{CQ}} \quad R_{out} \cong R_C \quad I_{CQ} R_C \ll V_{AF}$$

$$A_V \cong \frac{2I_{DQ} R_D}{V_{EBQ}} \quad R_{in} \cong \frac{V_{EBQ}}{2I_{DQ}} \quad R_{out} \cong R_D \quad I_{DQ} R_D \ll \frac{1}{\lambda}$$


Characteristics:

- Output impedance is mid-range
- A_{V0} is large and positive (equal in mag to that to CE)
- Input impedance is very low
- Not completely unilateral but output-input transconductance is small

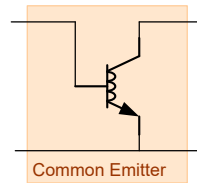
The three basic amplifier types for both MOS and bipolar processes




Common Emitter

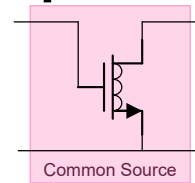


Common Source

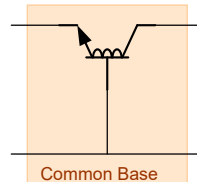


Common Base

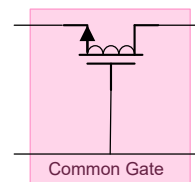

Common Gate

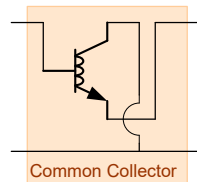


Common Collector

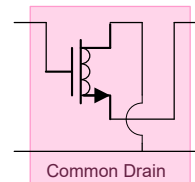


Common Drain

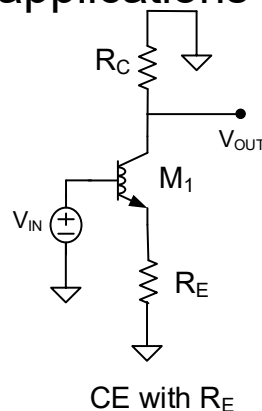- Have developed both two-ports and a widely used application of all 6
- A fourth structure (two additional applications) is also quite common so will be added to list of basic applications




CE with R_E

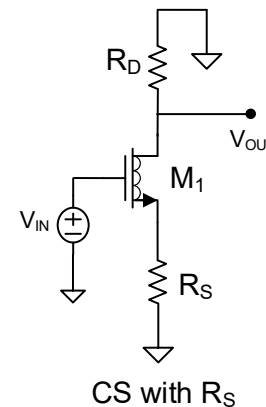

CS with R_S

Common Emitter with Emitter Resistor Configuration Application

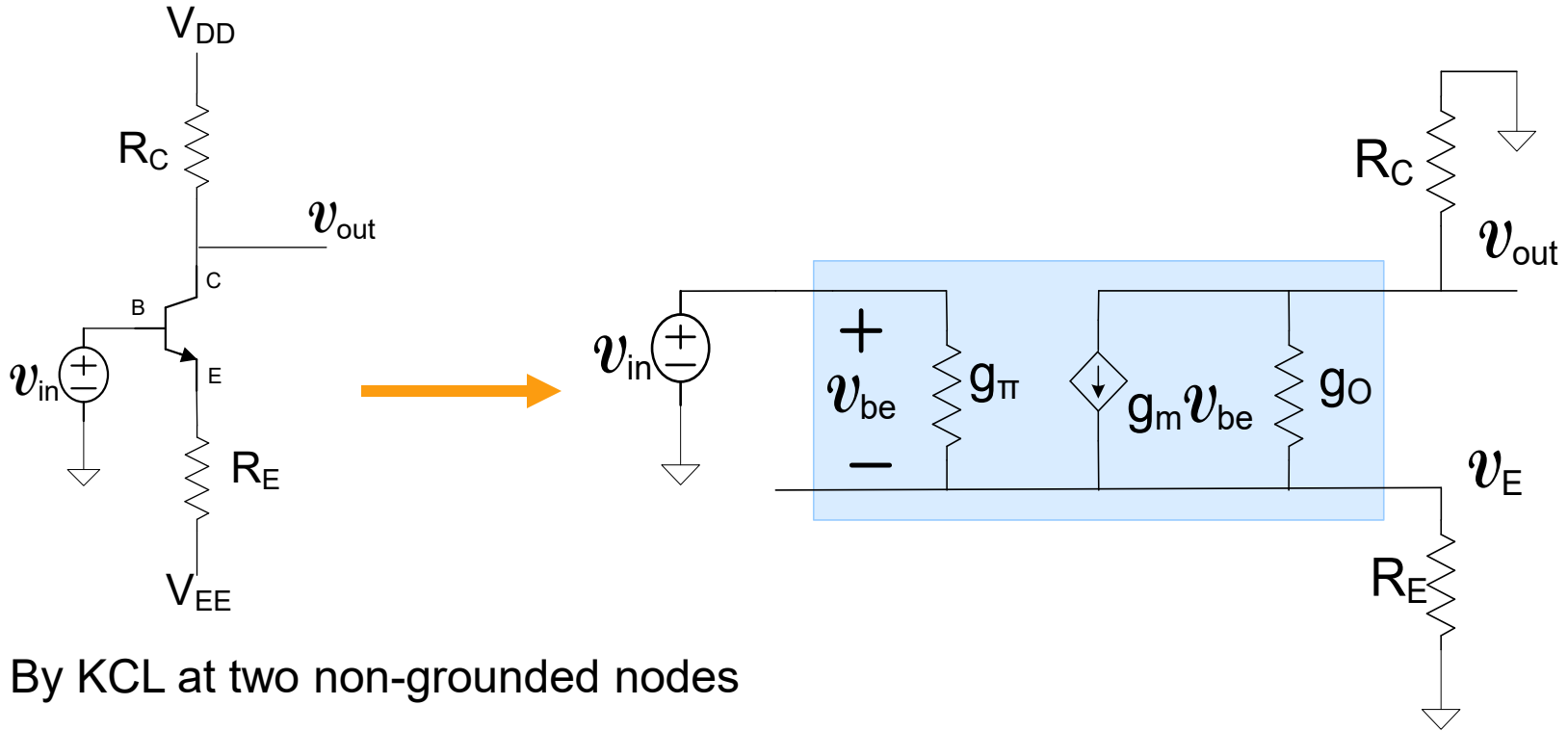(this is not a two-port model for this CE with R_E application)



By KCL at two non-grounded nodes


$$v_{out} (g_C + g_o) + (v_{in} - v_E) g_m = g_o v_E$$

$$v_E (g_E + g_o + g_{\pi}) - (v_{in} - v_E) g_m = g_o v_{out} + g_{\pi} v_{in}$$

$$A_V = \frac{v_{out}}{v_{in}} = \frac{-g_m g_E + g_o g_{\pi}}{g_C g_m + g_C (g_o + g_{\pi} + g_E) + g_o (g_{\pi} + g_E)} \cong -\frac{R_C}{R_E}$$

Common Emitter with Emitter Resistor Configuration Application

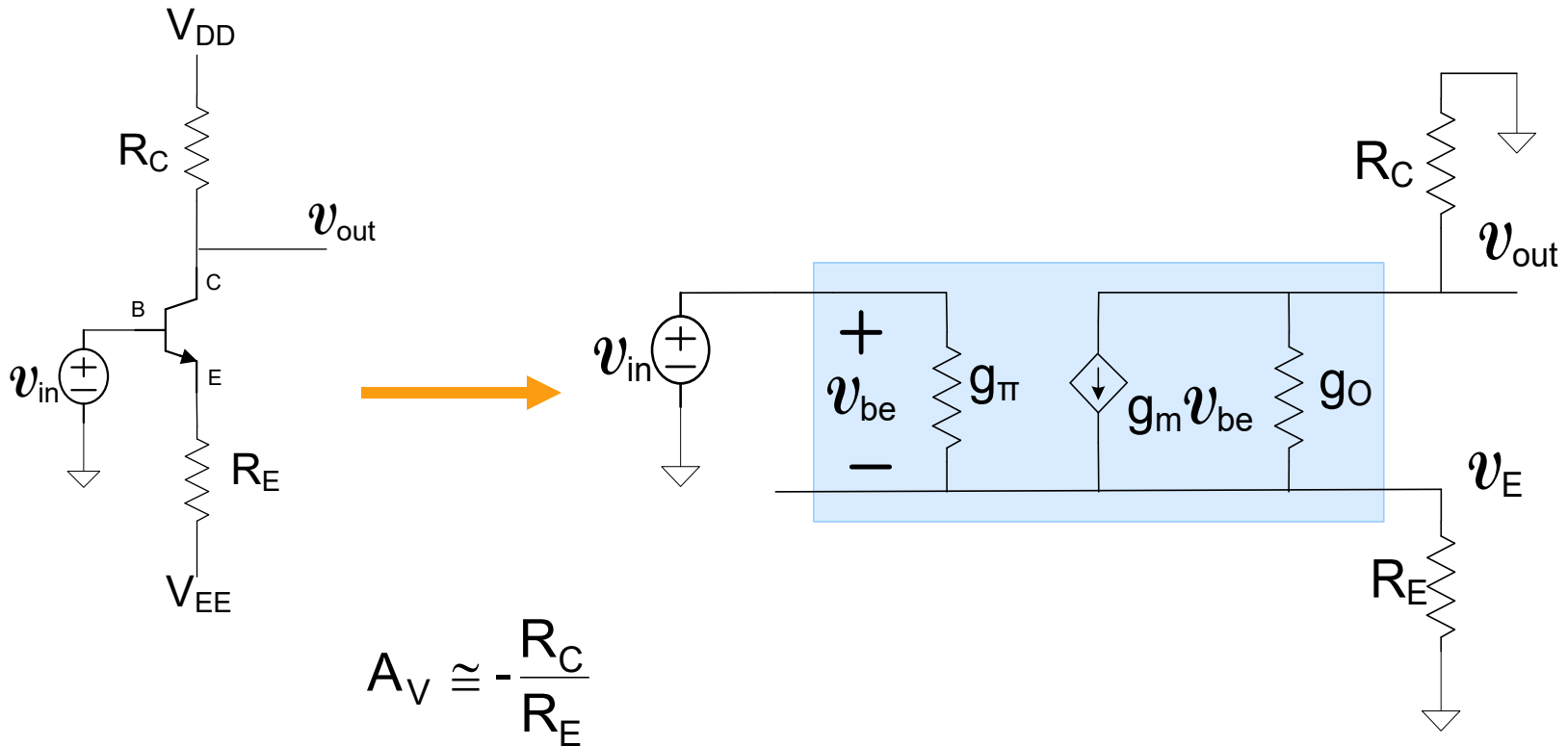(this is not a two-port model for this CE with R_E application)



$$A_V \cong -\frac{R_C}{R_E}$$

It can also be shown that


$$R_{in} \cong r_{\pi} + \beta R_E$$

$$R_{out} \cong R_C$$

Nearly unilateral (is unilateral if $g_o=0$)

Common Emitter with Emitter Resistor Configuration Application

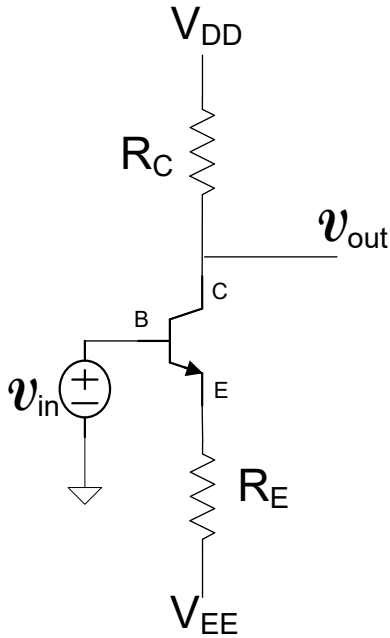(this is not a two-port model for this CE with R_E application)



$$A_V \cong -\frac{R_C}{R_E}$$

$$R_{in} \cong r_{\pi} + \beta R_E$$

$$R_{out} \cong R_C$$

(this is not a two-port model)









Characteristics:

- Analysis would simplify if g_0 were set to 0 in model
- Gain can be accurately controlled with resistor ratios
- Useful for reasonably accurate low gains
- Input impedance is high

Basic Two-Port Amplifier Gain Table

	CE/CS		CC/CD		CB/CG	
	BJT	MOS	BJT	MOS	BJT	MOS
A_V	$-\frac{I_{CQ}R_C}{V_t}$	$-\frac{2I_{DQ}R_D}{V_{EB}}$	1	1	$\frac{V_{AF}}{V_t}$	$\frac{2}{\lambda V_{EB}}$
R_{in}	$\frac{r_{\pi}}{\beta} = \frac{V_t}{I_{CQ}}$	∞	$r_{\pi} = \beta \left(\frac{V_t}{I_{CQ}} \right)$	∞	$\frac{1}{g_m + g_{\pi} + g_o} = \frac{V_t}{I_{CQ}}$	$\frac{1}{g_m + g_o} = \frac{V_{EB}}{2I_{DQ}}$
R_{out}	$\frac{1}{g_o}$	$\frac{1}{g_o}$	$\frac{1}{g_m + g_{\pi} + g_o} = \frac{V_t}{I_{CQ}}$	$\frac{1}{g_m + g_o} = \frac{V_{EB}}{2I_{DQ}}$	$\frac{1}{g_o}$	$\frac{1}{\lambda I_{DQ}}$
A_{VR}	0	0	1	1	$\frac{g_o}{g_m + g_{\pi} + g_o} = \frac{g_o}{g_m}$	$\frac{g_o}{g_m + g_o} = \frac{g_o}{g_m}$
	0	0	1	1	$\frac{V_t}{V_{AF}}$	$\frac{\lambda V_{EB}}{2}$

Basic Amplifier Application Gain Table

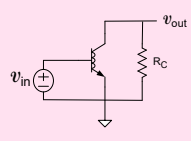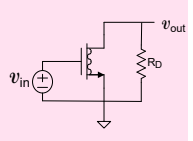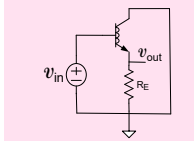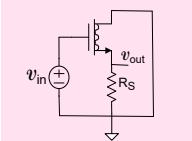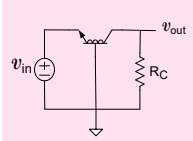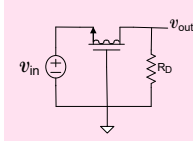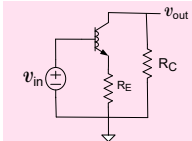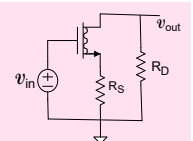	CE/CS		CC/CD		CB/CG		CEwRE/CSwRS	
	BJT	MOS	BJT	MOS	BJT	MOS	BJT	MOS
A_V	 $-g_m R_C$ $\frac{I_{CQ} R_C}{V_t}$	 $-\frac{2I_{DQ} R_D}{V_{EB}}$	 $\frac{g_m}{g_m + g_E}$ $\frac{I_{CQ} R_E}{I_{CQ} R_E + V_t}$	 $\frac{2I_{DQ} R_E}{2I_{DQ} R_E + V_{EB}}$	 $g_m R_C$ $\frac{I_{CQ} R_C}{V_t}$	 $\frac{2I_{DQ} R_C}{V_{EB}}$	 $-\frac{R_C}{R_E}$	 ∞
R_{in}	r_{π} $\frac{\beta V_t}{I_{CQ}}$	∞	$r_{\pi} + \beta R_E$ $r_{\pi} + \beta R_E$	∞	g_m^{-1} $\frac{V_t}{I_{CQ}}$	$\frac{V_{EB}}{2I_{DQ}}$	$r_{\pi} + \beta R_E$ $\beta \left(\frac{V_t}{I_{CQ}} + R_E \right)$	∞
R_{out}	R_C	R_C	g_m^{-1} $\frac{V_t}{I_{CQ}}$	$\frac{V_{EB}}{2I_{DQ}}$	R_C	R_C	R_C	R_C

(not two-port models for the four structures)

Can use these equations only when small signal circuit is EXACTLY like that shown !!



Stay Safe and Stay Healthy !

End of Lecture 31