

# EE 330

## Lecture 33









- High Gain Amplifiers
- Current Sources and Mirrors

# Fall 2023 Exam Schedule

Exam 1	Friday Sept 22	
Exam 2	Friday Oct 20	
Exam 3	Friday Nov. 17	
Final	Monday Dec 11	12:00 – 2:00 p.m.

# Review From Previous Lecture

## Basic Amplifier Application Gain Table

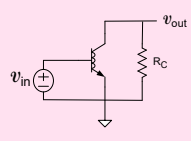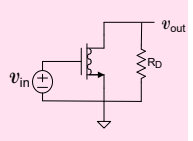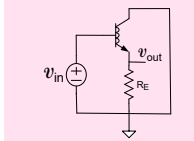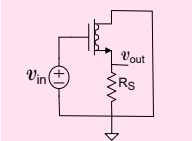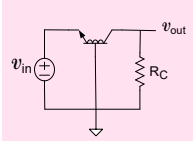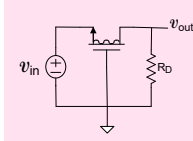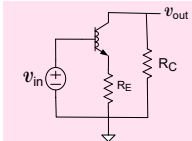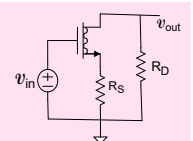
	CE/CS		CC/CD		CB/CG		CEwRE/CSwRS	
	BJT	MOS	BJT	MOS	BJT	MOS	BJT	MOS
$A_V$	 $-g_m R_C$ $\frac{I_{CQ} R_C}{V_t}$	 $-\frac{2I_{DQ} R_D}{V_{EB}}$	 $\frac{g_m}{g_m + g_E}$ $\frac{I_{CQ} R_E}{I_{CQ} R_E + V_t}$	 $\frac{2I_{DQ} R_E}{2I_{DQ} R_E + V_{EB}}$	 $g_m R_C$ $\frac{I_{CQ} R_C}{V_t}$	 $\frac{2I_{DQ} R_C}{V_{EB}}$	 $-\frac{R_C}{R_E}$	
$R_{in}$	$r_{\pi}$ $\frac{\beta V_t}{I_{CQ}}$	$\infty$	$r_{\pi} + \beta R_E$ $\beta \left( \frac{V_t}{I_{CQ}} + R_E \right)$	$\infty$	$g_m^{-1}$ $\frac{V_t}{I_{CQ}}$	$\frac{V_{EB}}{2I_{DQ}}$	$r_{\pi} + \beta R_E$ $\beta \left( \frac{V_t}{I_{CQ}} + R_E \right)$	$\infty$
$R_{out}$	$R_C$		$g_m^{-1}$ $\frac{V_t}{I_{CQ}}$	$\frac{V_{EB}}{2I_{DQ}}$	$R_C$		$R_C$	

(not two-port models for the four structures)

Can use these equations only when small signal circuit is **EXACTLY** like that shown !!


# Cascaded Amplifier Analysis and Operation

## Adjacent Stage Coupling Only

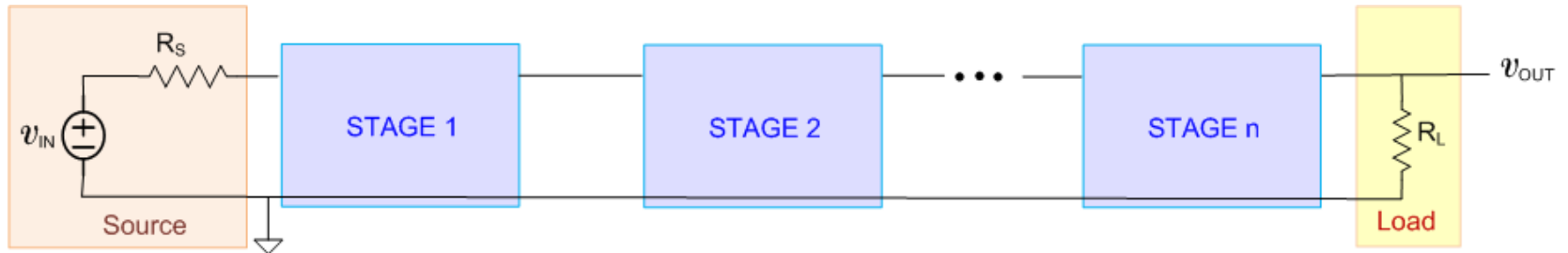

- Systematic Methods of Analysis/Design will be Developed

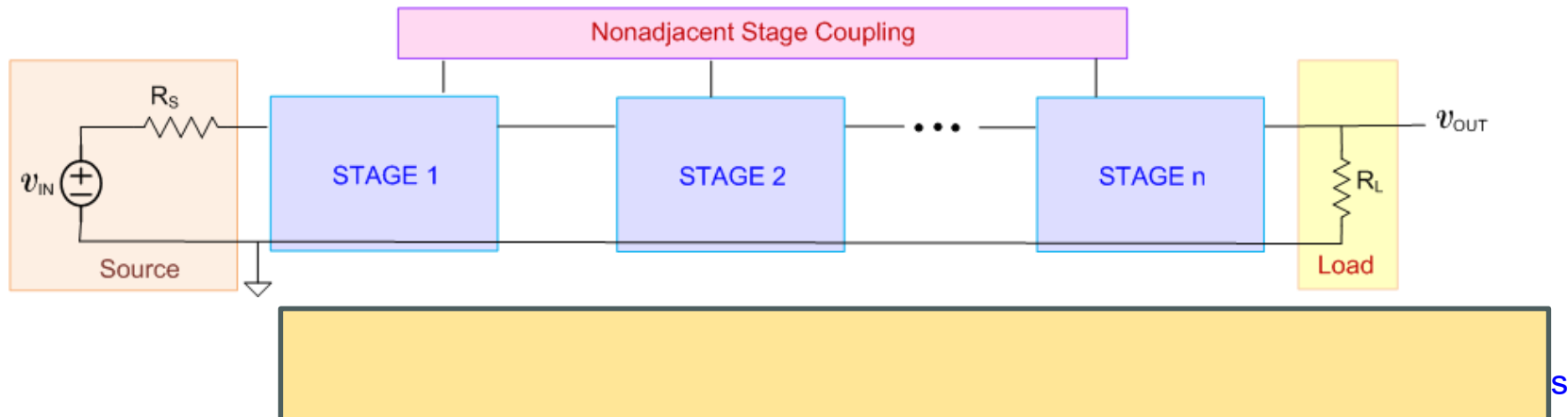
## One or more couplings of nonadjacent stages



# Cascaded Amplifier Analysis and Operation


Case 2: One or more stages are not unilateral

➤ Standard two-port cascade

 


Analysis by creating new two-port of entire amplifier quite tedious because of the reverse-gain elements

 ➤ Right-to-left nested  $R_{inx}$ ,  $A_{VKX}$  approach




- $R_{inx}$  includes effects of all loading
- $A_{VKX}$  is the voltage ratio from input to output of a stage
- $A_{VKX}$ 's include all loading
- Can not change any loading without recalculating everthing!

 
# Review: Small-signal equivalent of a one-port




“Diode-connected transistor”

 


“GS - connected transistor”

 

 
# Review: Small-signal equivalent of a one-port




“Diode-connected transistor”

 

“BE - connected transistor”

 

# High-gain BJT amplifier

 

$$A_V = \frac{-g_m}{g_0 + G_C} \cong -g_m R_C$$

To make the gain large, it appears that all one needs to do is make  $R_C$  large !

$$A_V \cong -g_m R_C = \frac{-I_{CQ} R_C}{V_t}$$

But  $V_t$  is fixed at approx 25mV and to keep  $Q_1$  in forward active with large signal swing,  $I_{CQ} R_C < (V_{DD} - V_{EE})/2$

$$|A_V| < \frac{V_{DD} - V_{EE}}{2V_t}$$

If  $V_{DD} - V_{EE} = 5V$ ,

$$|A_V| < \frac{5V}{2 \cdot 25mV} = 100$$

- Gain is practically limited with this supply voltage to around 100
- And in extreme case, limited to about 200 with this supply voltage with very small signal swing



# High-gain MOS amplifier

$$A_V = \frac{-g_m}{g_0 + G_D} \cong -g_m R_D$$

To make the gain large, it appears that all one needs to do is make  $R_D$  large !

$$A_V \cong -g_m R_D = \frac{-2I_{DQ}R_D}{V_{EB}}$$

But  $V_{EB}$  is practically limited to around 100mV and for good signal swing,  $I_{DQ}R_D < (V_{DD} - V_{SS})/2$


$$|A_V| < \frac{V_{DD} - V_{SS}}{V_{EB}}$$

If  $V_{DD} - V_{SS} = 5V$  and  $V_{EB} = 100mV$ ,




$$|A_V| < \frac{5V}{100mV} = 50$$

**Gain is practically limited with this supply voltage to around 50**

 **Are these fundamental limits on the gain of the BJT and MOS Amplifiers?**



# High-gain amplifier

   

$$A_V = \frac{-g_m}{0} = -\infty$$

**Fundamentally a different circuit**




**Current source is biasing  $Q_1$**

**This gain is very large !**

**Too good to be true !**

**Need better model of BJT and MOS device (but we already have it) !**

# High-gain amplifier

   

$$A_V = \frac{-g_m}{g_o}$$

$$A_V = \frac{-I_{CQ}}{V_t I_{CQ}/V_{AF}} = -\frac{V_{AF}}{V_t}$$


$$A_V = -\frac{V_{AF}}{V_t} \cong \frac{200V}{25mV} = -8000$$

**This gain is very large (but realistic) !**


**And no design parameters affect the gain**

**But how can we make a current source?**

# High-gain amplifier

 

$$A_V \cong -8000$$

 


Same gain with both npn and pnp transistors


How can we build the ideal current source?

What is the small-signal model of an actual current source?

# High-gain amplifier

 

$$A_V \cong -8000$$



 


Same gain with both npn and pnp transistors

Will now focus on creating current sources and then return to using these current sources to build high gain amplifiers.

# Simple Current Sources

a “sinking” current source

   

Since  $I_X$  is independent of  $V_{DCS}$ , acts as an ideal current source (with this model)

Termed a “sinking” current source since current is pulled out of the load

If  $V_{XX}$  is available, each dc current source requires only one additional transistor !

Have several methods for generating  $V_{XX}$  from  $V_{DD}$  (see HW problems)



But how good is this current “sink”?

And may not have both MOS and Bipolar devices in most processes!

But for the npn high-gain amplifier considered need a sourcing current

# Simple Current Sources

a “sourcing” current source

  

Since  $I_X$  is independent of  $V_{DCS}$ , acts as an ideal current source (with this model)

Termed a “sourcing” current source since pushed into the load

If  $V_{YY}$  is available, each dc current source requires only one additional transistor !



Have several methods for generating  $V_{YY}$  from  $V_{DD}$  (see HW problems)

But how good is this current “source”?

And may not have both MOS and Bipolar devices in most processes!

# Simple Current Sources

a “sinking” current source

  

Since  $I_X$  is independent of  $V_{CCS}$ , acts as an ideal current source (with this model)

Termed a “sinking” current source since current is pulled out of the load

If  $V_{XX}$  is available, each dc current source requires only one additional transistor !

Have several methods for generating  $V_{XX}$  from  $V_{DD}$  (see HW problems)



But for the npn high-gain amplifier considered need a sourcing current

But how good is this current “sink”?



# Simple Current Sources

a “sourcing” current source

 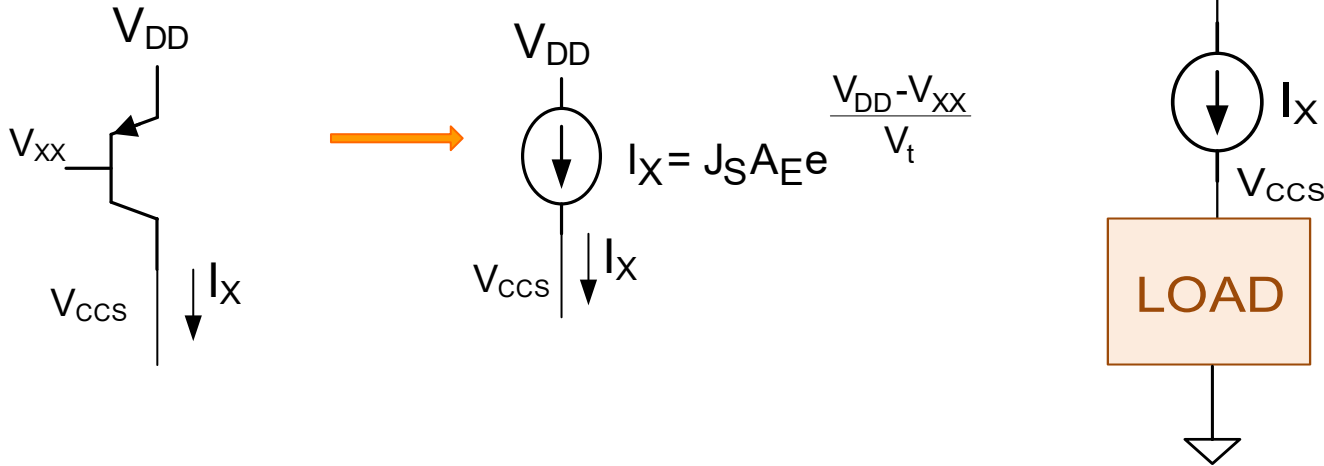

Since  $I_X$  is independent of  $V_{CCS}$ , acts as an ideal current source (with this model)

Termed a “sourcing” current source since pushed into the load

If  $V_{XX}$  is available, each dc current source requires only one additional transistor !


Current highly sensitive to  $V_{XX}$  if generated with dc voltage source

Have several methods for generating  $V_{XX}$  from  $V_{DD}$  (see HW problems)


But how good is this current “source”?

Before addressing the issue of how a current source is designed, will consider another circuit that uses current source biasing

## The Basic Differential Amplifier


 


If  $A_V$  is large

 

Operational Amplifier (Op Amp)

 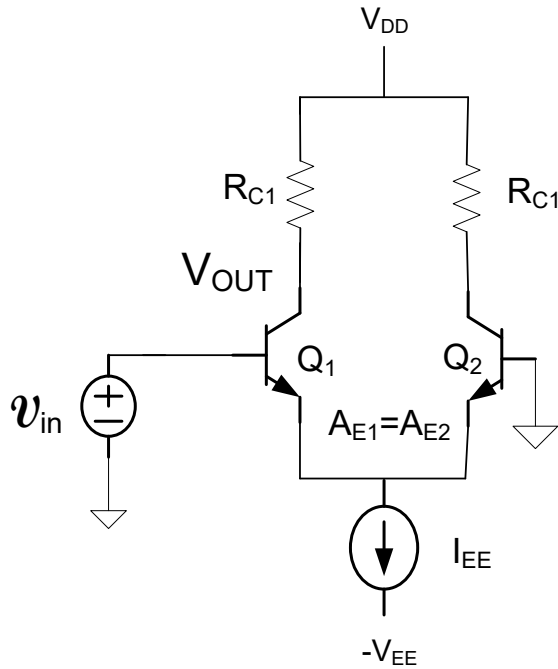
Example: Determine the voltage gain of the following circuit




Since symmetric when  $v_{IN}=0$

$$I_{C1Q} = I_{C2Q} = \frac{I_{EE}}{2}$$
 
$$g_{m1} = g_{m2} = \frac{I_{EE}}{2V_t}$$



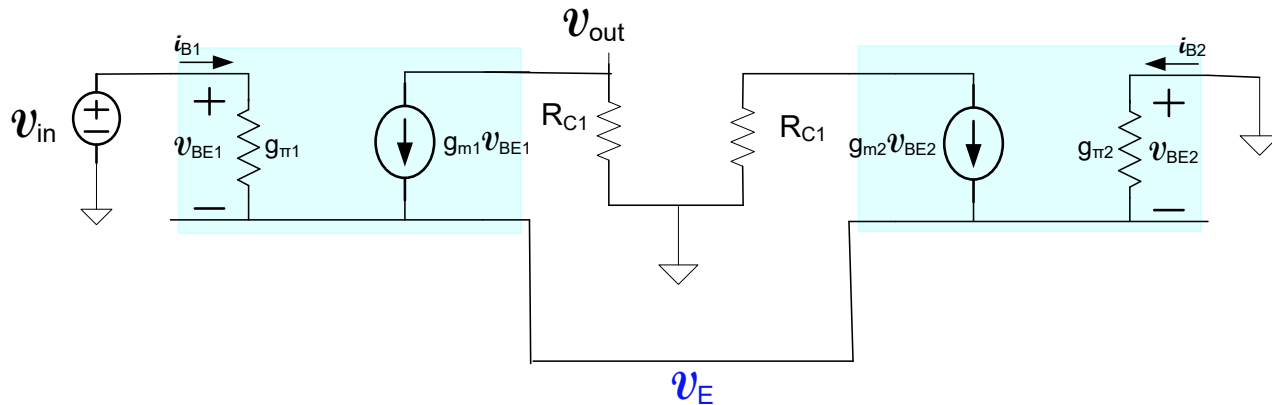Example: Determine the voltage gain of the following circuit



$$v_E (g_{\pi 1} + g_{\pi 1}) = g_{\pi 1} v_{IN} + g_{m 1} (v_{IN} - v_E) + g_{m 2} (-v_E)$$

$$v_{OUT} = -R_{C 1} g_{m 1} (v_{IN} - v_E)$$


$$v_E (g_{\pi 1} + g_{\pi 2} + g_{m 1} + g_{m 2}) = v_{IN} (g_{m 1} + g_{\pi 1})$$

$$v_E = \frac{(g_{m 1} + g_{\pi 1})}{(g_{\pi 1} + g_{\pi 2} + g_{m 1} + g_{m 2})} v_{IN}$$

$$v_{OUT} = -R_{C 1} g_{m 1} v_{IN} \left[ 1 - \frac{(g_{m 1} + g_{\pi 1})}{(g_{\pi 1} + g_{\pi 2} + g_{m 1} + g_{m 2})} \right]$$

$$v_{OUT} = -R_{C 1} g_{m 1} v_{IN} \left[ \frac{g_{\pi 1} + g_{\pi 2} + g_{m 1} + g_{m 2} - (g_{m 1} + g_{\pi 1})}{(g_{\pi 1} + g_{\pi 2} + g_{m 1} + g_{m 2})} \right]$$

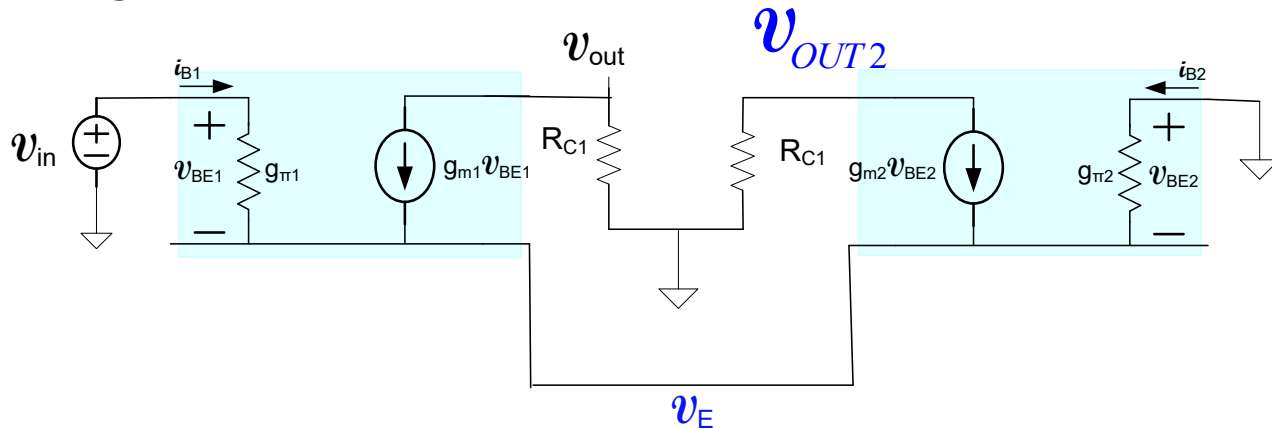Example: Determine the voltage gain of the following circuit




$$v_{OUT} = -R_{C1}g_{m1}v_{IN} \left[ \frac{g_{\pi1} + g_{\pi2} + g_{m1} + g_{m2} - (g_{m1} + g_{\pi1})}{(g_{\pi1} + g_{\pi2} + g_{m1} + g_{m2})} \right]$$

$$v_{OUT} \cong -R_{C1}g_{m1}v_{IN} \left[ \frac{g_{m2}}{(g_{m1} + g_{m2})} \right]$$

$$v_{OUT} \cong \left[ \frac{-R_{C1}g_{m1}}{2} \right] v_{IN}$$

$$v_{OUT2} \cong \left[ \frac{R_{C1}g_{m1}}{2} \right] v_{IN}$$

# Differential amplifier


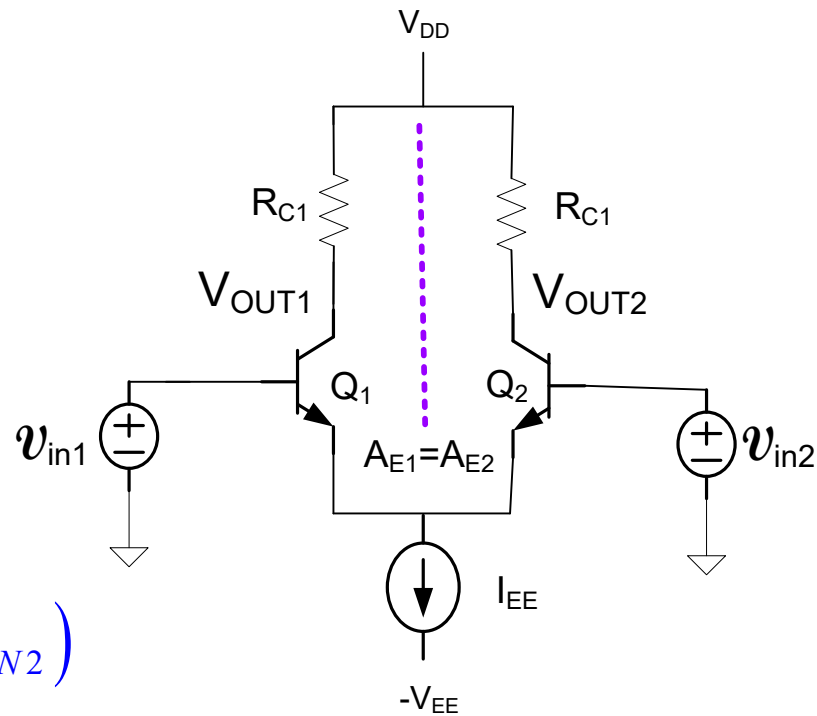


$$v_{OUT1} \cong -\left[\frac{R_{C1}g_{m1}}{2}\right](v_{IN1} - v_{IN2})$$

$$v_{OUT2} \cong \left[\frac{R_{C1}g_{m1}}{2}\right](v_{IN1} - v_{IN2})$$

- Very useful circuit
- This is a basic Op Amp
- Uses a current source and  $V_{DD}$  for biasing (no biasing resistors or caps!)
- But – needs a dc current source !!!!


# Simple Current Sources

  

But how good are these current sources?


# Model of dc Current Source

“Reasonable dc Current Source”

 


$I_{XX}$  independent of  $V_1$  and  $t$ ,  $R_S$  large

 Small-signal model of dc current source (since one-port)




want  $R_{IN}$  large

## Ideal dc Current Source

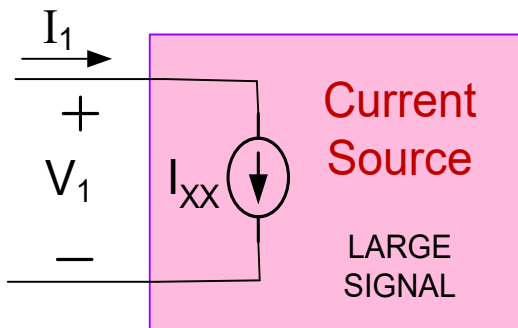

 $I_{XX}$  independent of  $V_1$  and  $t$




$R_{IN} = \infty$


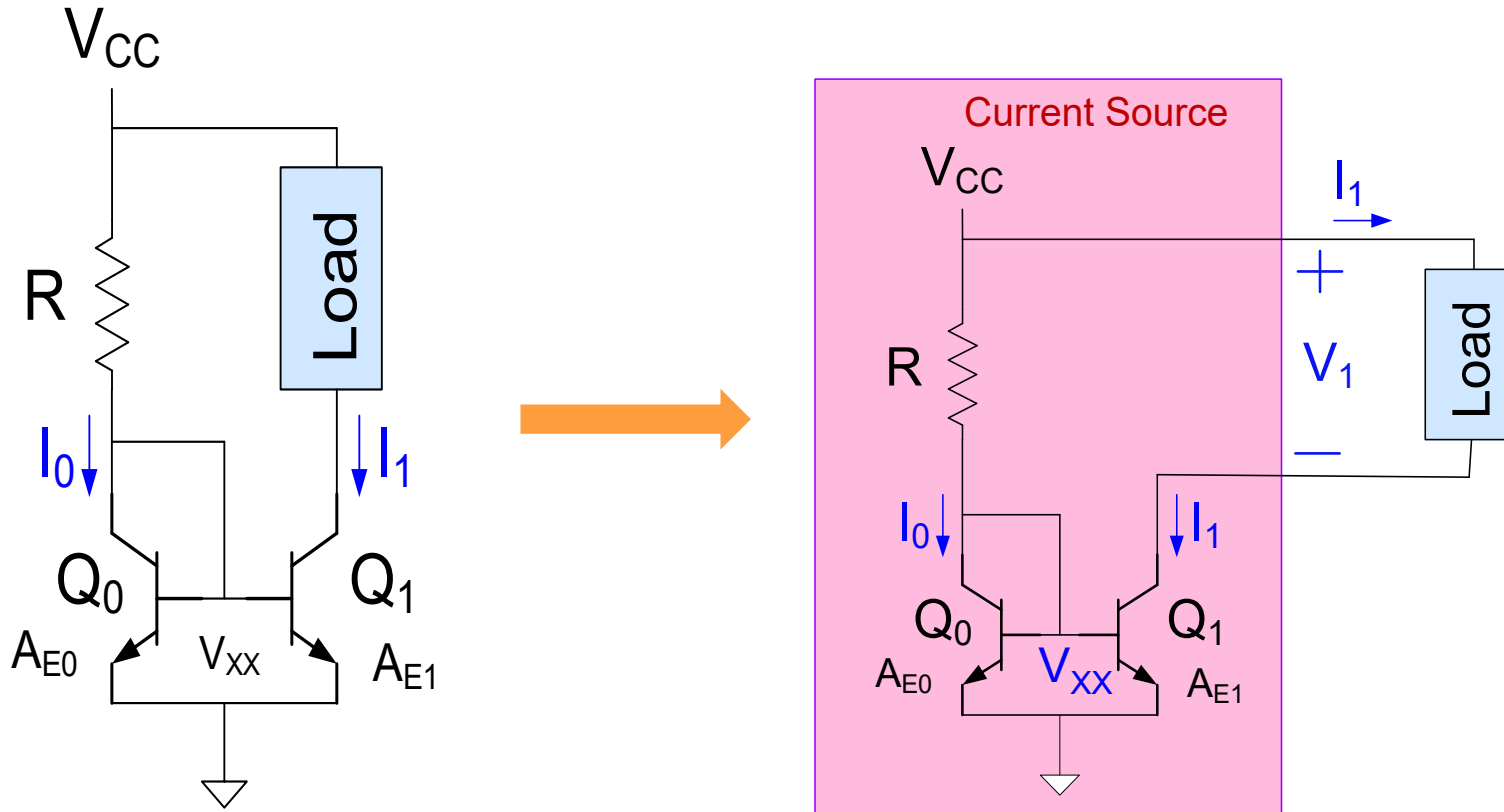
# Current Sources/Mirrors


Will show circuit in red behaves as a current source



$R$  and  $Q_0$  simply generate voltage  $V_{XX}$  in previous circuit

But sensitivity of  $I_1$  is much smaller than using voltage source for generating  $V_{XX}$


# Current Sources/Mirrors

 

$$I_0 \cong \frac{(V_{CC} - 0.6V)}{R}$$

If the base currents are neglected

# Current Sources/Mirrors

 

$$I_0 \cong \frac{(V_{CC} - 0.6V)}{R}$$

If the base currents are neglected

$$\left. \begin{aligned} I_0 &= J_S A_{E0} e^{\frac{V_{BE0}}{V_t}} \\ I_1 &= J_S A_{E1} e^{\frac{V_{BE1}}{V_t}} \end{aligned} \right\}$$

since  $V_{BE1} = V_{BE2}$


$$I_1 \cong \left( \frac{A_{E1}}{A_{E0}} \right) I_0 = \left( \frac{A_{E1}}{A_{E0}} \right) \frac{V_{CC} - 0.6V}{R}$$

Note  $I_1$  is not a function of  $V_1$

**Behaves as a current sink ! So is ideal with this model !!**


**And does not require an additional dc voltage source !!!**

# Current Sources/Mirrors

 

- **Multiple Outputs Possible**
- **Can be built for sourcing or sinking currents**
- **Also useful as a current amplifier**
- **MOS counterparts work very well and are not plagued by base current**


# Current Sources/Mirrors

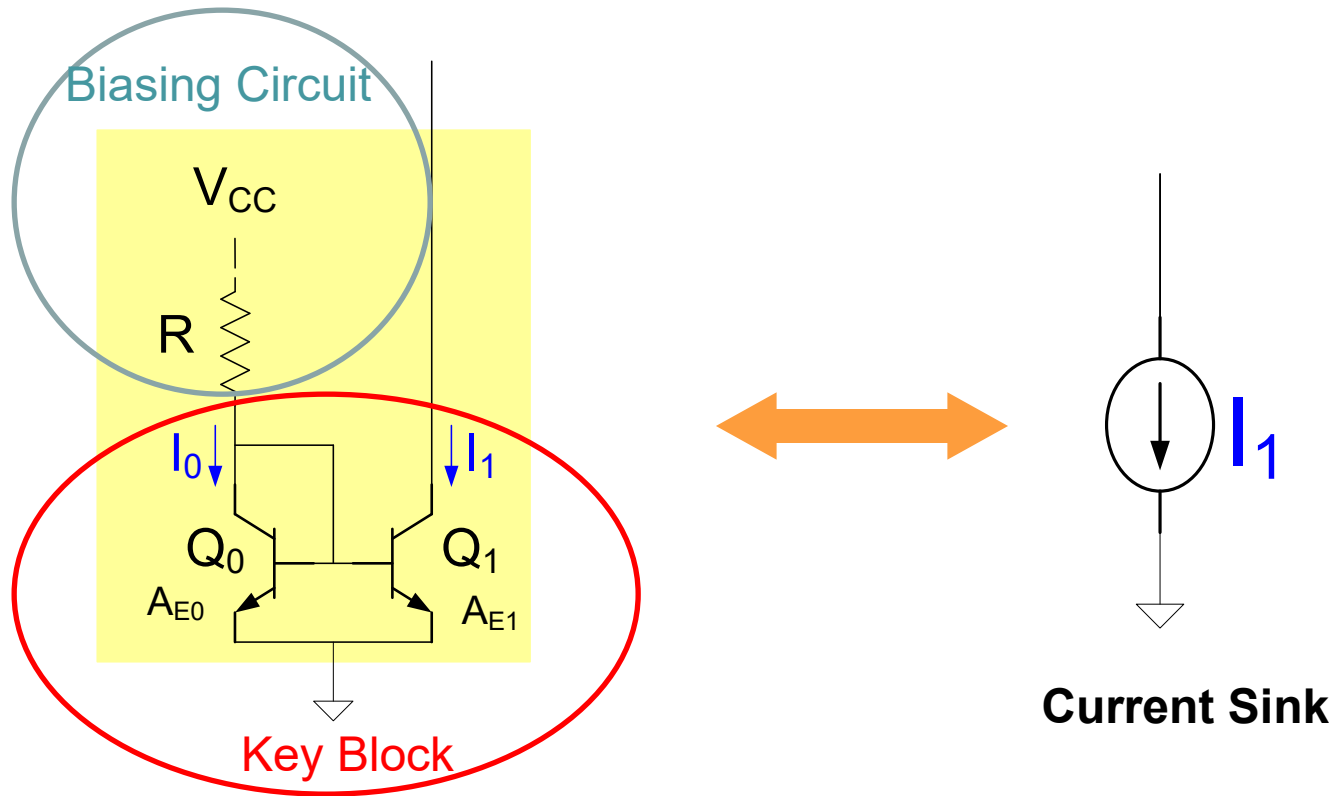

Two ways to look at this circuit:

- $Q_0$  and  $R$  bias  $Q_1$
- $R$  biases the  $Q_0 : Q_1$  block

# Current Sources/Mirrors

 

Current Sources are Seldom Available in Basic Laboratories:


Biasing of board-level and discrete electronic circuits is usually done with voltage sources, resistors, and capacitors

Biasing resistors and capacitors are used very sparingly in MOS circuits

Will show on-chip current sources can be very small

Biasing of on-chip circuits is often done with current sources instead of R's and C's

# Current Sources/Mirrors

 


**Multiple-Output Bipolar Current Sink**

**If the base currents are neglected**

$$I_k = \left[ \frac{A_{Ek}}{A_{E0}} \right] I_0$$

# Current Sources/Mirrors

 


**Multiple-Output Bipolar Current Source**

**If the base currents are neglected**

$$I_k = \left[ \frac{A_{Ek}}{A_{E0}} \right] I_0$$




# Current Sources/Mirrors

 

**Multiple-Output Bipolar Current Source and Sink**

$$I_{nk} = ? \quad I_{pk} = ?$$


# Current Sources/Mirrors

 

**Multiple-Output Bipolar Current Source and Sink**  
 If the base currents are neglected

$$I_{nk} = \left[ \frac{A_{Enk}}{A_{E0}} \right] I_0 \quad I_{pk} = \left[ \frac{A_{En1}}{A_{E0}} \right] \left[ \frac{A_{Epk}}{A_{Ep0}} \right] I_0$$

# Current Sources/Mirrors

 


$$I_{out} = \left[ \frac{A_{E1}}{A_{E0}} \right] I_{in}$$

This circuit is termed a “current mirror”

Will re-derive the transfer characteristics of the current mirror assuming  $I_B$  is small compared to  $I_C$

$$\left. \begin{aligned} I_{IN} &= J_S A_{E0} e^{\frac{V_{BE}}{V_t}} \\ I_{OUT} &= J_S A_{E1} e^{\frac{V_{BE}}{V_t}} \end{aligned} \right\} \Rightarrow \frac{I_{OUT}}{I_{IN}} = \frac{J_S A_{E1} e^{\frac{V_{BE}}{V_t}}}{J_S A_{E0} e^{\frac{V_{BE}}{V_t}}} = \frac{A_{E1}}{A_{E0}}$$

# Current Sources/Mirrors

 

## npn Current Mirror


If the base currents are neglected

$$I_{out} = \left[ \frac{A_{E1}}{A_{E0}} \right] I_{in}$$

- Output current linearly dependent on  $I_{in}$
- Small-signal and large-signal relationships the same since linear
- Serves as a current amplifier
- Widely used circuit

**But  $I_{in}$  must be positive !**

# Current Sources/Mirrors

 

npn current mirror amplifier

$i_{out} = ?$

$$\frac{i_{OUT} + M I_{BS}}{i_{in} + I_{BS}} = M$$


$$i_{OUT} + M I_{BS} = M (i_{in} + I_{BS})$$

$$i_{OUT} + M \cancel{I}_{BS} = M (i_{in} + \cancel{I}_{BS})$$

$$\frac{i_{OUT}}{i_{in}} = M$$

But  $I_{BS} + i_{in} > 0$  !

# Current Sources/Mirrors

 


$$i_{\text{out}} = \left[ \frac{A_{E1}}{A_{E0}} \right] i_{\text{in}}$$

Amplifies both positive and negative currents (provided  $i_{\text{IN}} > -I_{\text{BS}}$ )


Current amplifiers are easy to build !!

Current gain can be accurately controlled with appropriate layout !!

# Current Sources/Mirrors

 


**npn Current Mirror**

 

**n-channel Current Mirror**

$$I_{out} = ?$$

# Current Sources/Mirrors

 

**n-channel Current Mirror**

$$\left. \begin{aligned} I_{in} &= \frac{\mu C_{OX} W_0}{2L_0} (V_{GS0} - V_{T0})^2 \\ I_{out} &= \frac{\mu C_{OX} W_1}{2L_1} (V_{GS1} - V_{T1})^2 \end{aligned} \right\}$$


If process parameters are matched, it follows that

$$I_{out} = \left[ \frac{W_1}{W_0} \frac{L_0}{L_1} \right] I_{in}$$

- Current mirror gain can be accurately controlled !
- Layout is important to get accurate gain (for both MOS and BJT)




 
# n-channel current mirror current amplifier



$$i_{\text{out}} = \left[ \frac{W_2}{W_1} \frac{L_1}{L_2} \right] i_{\text{in}}$$

**Amplifies both positive and negative currents**


# Current Sources/Mirrors

  

$$I_k = \left[ \frac{W_k L_0}{W_0 L_k} \right] I_0$$
 
# Current Sources/Mirrors

multiple sourcing and sinking current outputs




$$I_{pj} = \left[ \frac{W_{pj}}{L_{pj}} \cdot \frac{L_{p0}}{W_{p0}} \right] M I_0$$

$$M = \left[ \frac{W_{n0}}{L_{n0j}} \cdot \frac{L_0}{W_0} \right]$$

$$I_{nj} = \left[ \frac{W_{nj}}{L_{nj}} \cdot \frac{L_0}{W_0} \right] I_0$$


m and k may be different  
Often M=1

# Current Sources/Mirrors Summary

 

 **npn Current Mirror**

$$I_{out} = \left[ \frac{A_{E1}}{A_{E0}} \right] I_{in}$$




**n-channel Current Mirror**


$$I_{out} = \left[ \frac{W_1}{W_0} \frac{L_0}{L_1} \right] I_{in}$$

- Current mirror gain can be accurately controlled !
- Layout is important to get accurate gain (for both MOS and BJT)

# Layout of Current Mirrors

 


Example with  $M = 2$

 

Standard layout
 
$$M = \left[ \frac{W_2}{W_1} \frac{L_1}{L_2} \right]$$




Gate area after fabrication depicted 

$$M = \left[ \frac{W_2 + 2\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_2 + 2\Delta L} \right]$$

$$M = \left[ \frac{2W_1 + 2\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] \neq 2$$

# Layout of Current Mirrors


Example with  $M = 2$

 

Standard layout

$$M = \left[ \frac{W_2}{W_1} \frac{L_1}{L_2} \right]$$
 
$$M = \left[ \frac{2W_1 + 2\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] \neq 2$$




Better Layout

$$M = \left[ \frac{2W_1 + 4\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] = 2$$

# Layout of Current Mirrors

Example with  $M = 2$

 

**Better Layout**

Linear Gradient Direction  
of a model parameter  
(e.g.  $\mu$  or  $V_{TH}$ )

$$M = \left[ \frac{2W_1 + 4\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] = 2$$

But this analysis was based upon assumption of matching of process parameters




$$\left. \begin{aligned} I_{in} &= \frac{\mu_0 C_{OX} W_0}{2L_0} (V_{GS0} - V_{T0})^2 \\ I_{out} &= \frac{\mu_1 C_{OX} W_1}{2L_1} (V_{GS1} - V_{T1})^2 \end{aligned} \right\}$$

Even with this better layout, the current ratio will not be 2 if gradient effects such as those depicted here are shown

And both magnitude and direction of gradient effects are a random variable which will vary across a die

# Centroid and Common Centroid

✕ Denotes Geometric Centroid

 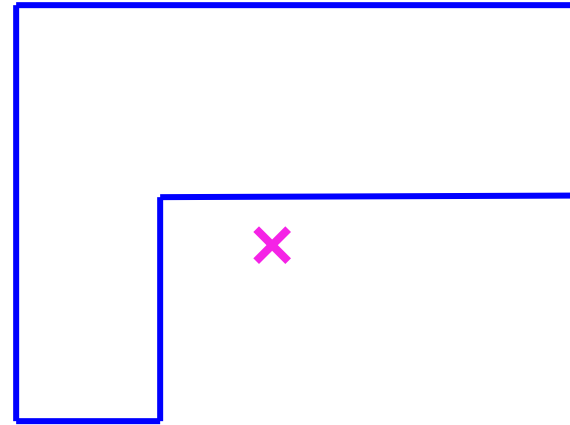 





# Centroid and Common Centroid

Geometric Centroids of Channel

Two Transistors:

 


Two Parts of One Transistor:

 

# Centroid and Common Centroid


Two Transistors each with two parts:

 

# Centroid and Common Centroid

Common Centroid for Ideally Matched Devices


Two Transistors each with two parts:

 

# Centroid and Common Centroid

Common Centroid for Matched Devices


Two Transistors each with two parts:

 

 
# Centroid and Common Centroid

Common Centroid for Ratioed Devices  $M = \frac{W_2 L_1}{W_1 L_2} = 2$

Two Transistors with different effective widths:



# Gradient

 

Threshold voltage  
dependent upon position

$$V_{TH}(x,y)$$


- Significant changes in threshold voltage can occur due to gradient effects
- This can seriously degrade matching in matching-critical circuits

- If the threshold voltage of a transistor changes with position, it can be reasonably accurately modeled with an “equivalent” threshold voltage
- For linear gradient,  $V_{THEQ} = V_{TH}(X_C, Y_C)$

$$\times : (X_C, Y_C)$$


# Layout of Current Mirrors

Example with  $M = 2$

 


Standard layout
 
$$M = \left[ \frac{W_2 L_1}{W_1 L_2} \right]$$



Better Layout
 
$$M = \left[ \frac{2W_1 + 4\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] = 2$$





Even Better Layout

$$M = \left[ \frac{2W_1 + 4\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] = 2$$

- This is termed a common-centroid layout
- Linear gradient mismatch eliminated with common-centroid layout !

# Current Sources/Mirrors

  

If  $I_0$  is practically generated (it can be), now have available a large number of accurate current sources or sinks that can be used for biasing and for other purposes on chip !





Stay Safe and Stay Healthy !

End of Lecture 33