

EE 330

Lecture 34

Layout of Current Mirrors

Common-Centroid Layouts




High Gain Amplifiers

Cascode Amplifiers

Fall 2023 Exam Schedule

Exam 1	Friday Sept 22	
Exam 2	Friday Oct 20	
Exam 3	Friday Nov. 17	
Final	Monday Dec 11	12:00 – 2:00 p.m.

High-gain amplifier

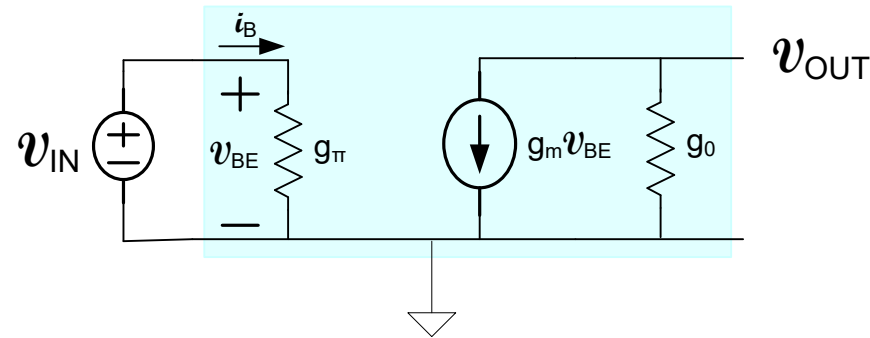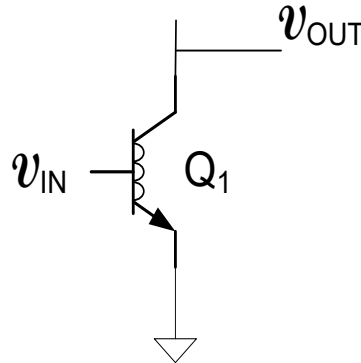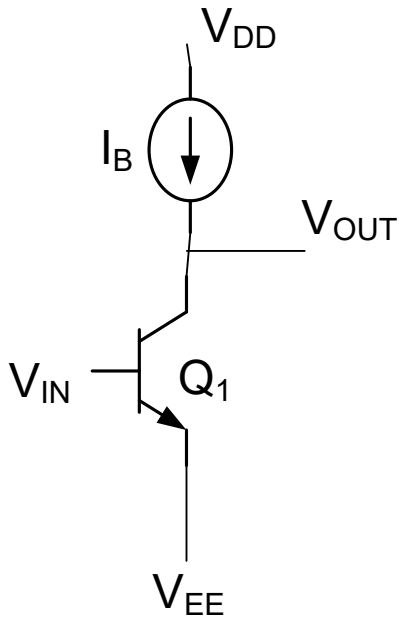

$$A_V = \frac{-g_m}{g_o}$$

$$A_V = \frac{-I_{CQ}}{V_t I_{CQ} / V_{AF}} = -\frac{V_{AF}}{V_t}$$

$$A_V =$$


This gain is very large (but realistic) !

And no design parameters affect the gain

But how can we make a current source?

Current Sources/Mirrors

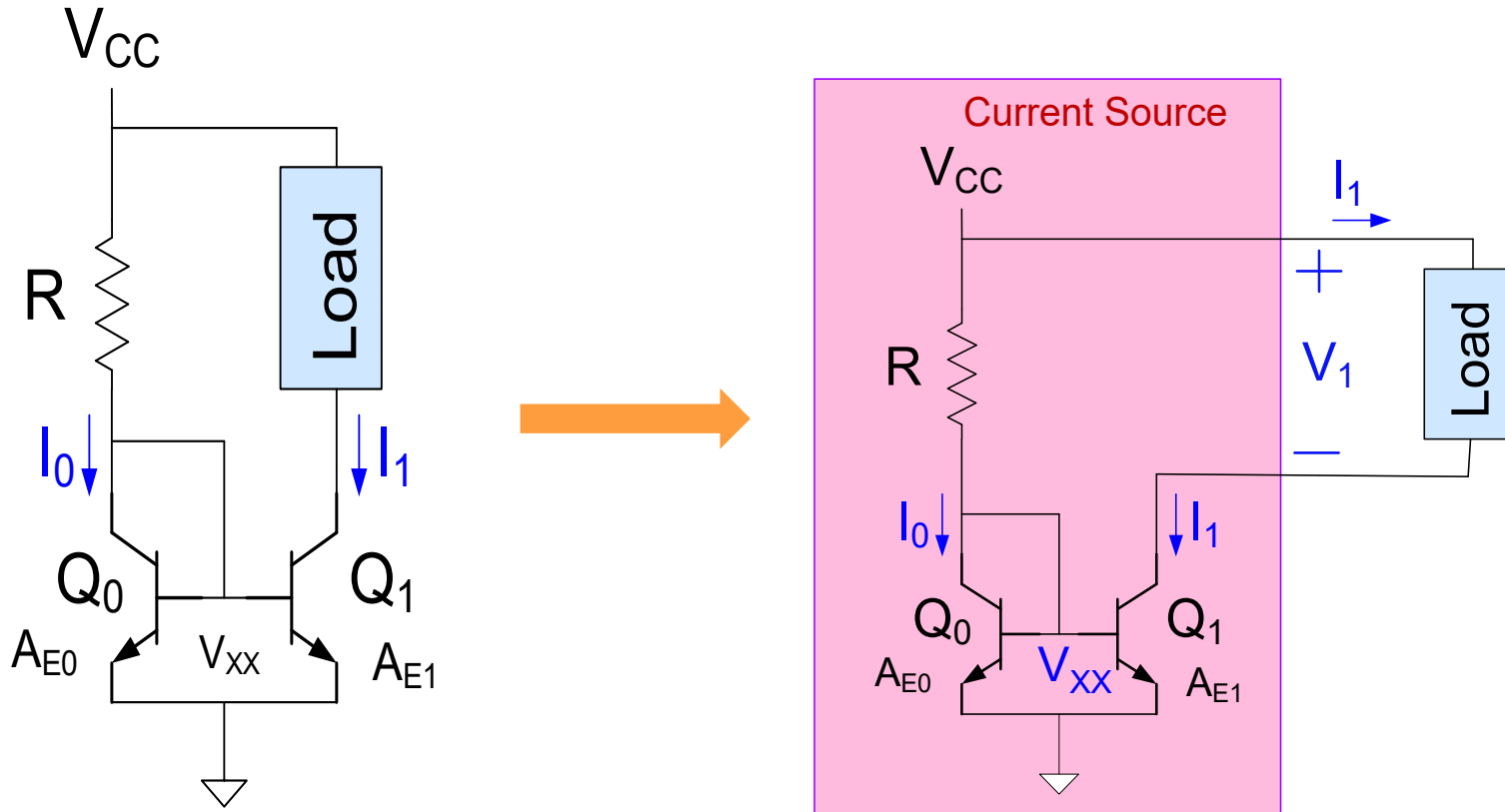
Will show circuit in red behaves as a current source



R and Q_0 simply generate voltage V_{XX} in previous circuit


But sensitivity of I_1 is much smaller than using voltage source for generating V_{XX}

Current Sources/Mirrors Summary

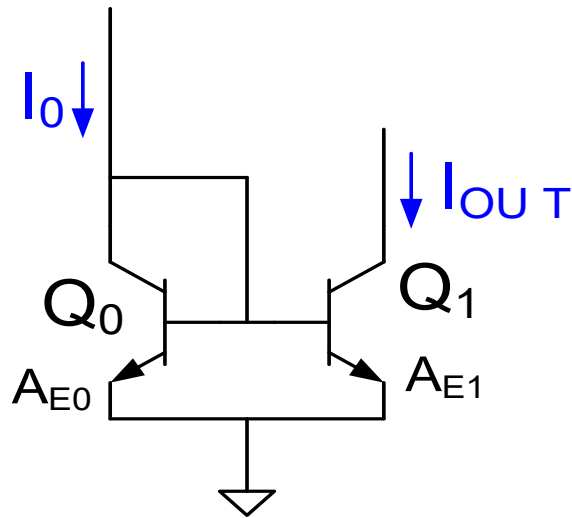

npn Current Mirror
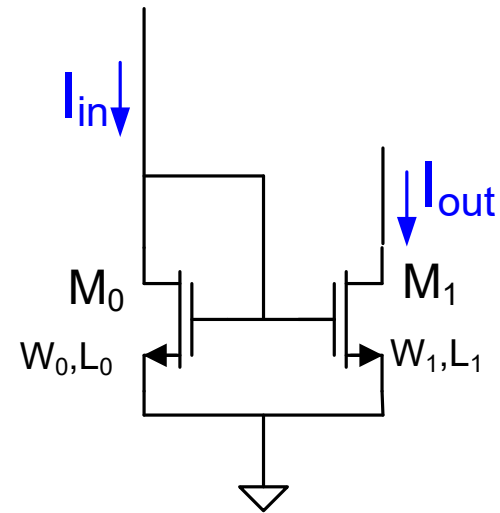
$$I_{out} = \left[\frac{A_{E1}}{A_{E0}} \right] I_{in}$$




n-channel Current Mirror


$$I_{out} = \left[\frac{W_1}{W_0} \frac{L_0}{L_1} \right] I_{in}$$

- Current mirror gain can be accurately controlled !
- Layout is important to get accurate gain (for both MOS and BJT)

Layout of Current Mirrors

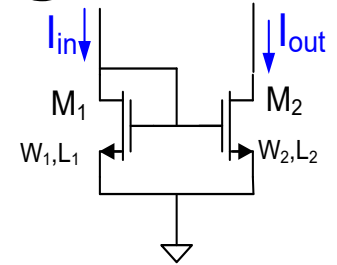


Example with $M = 2$

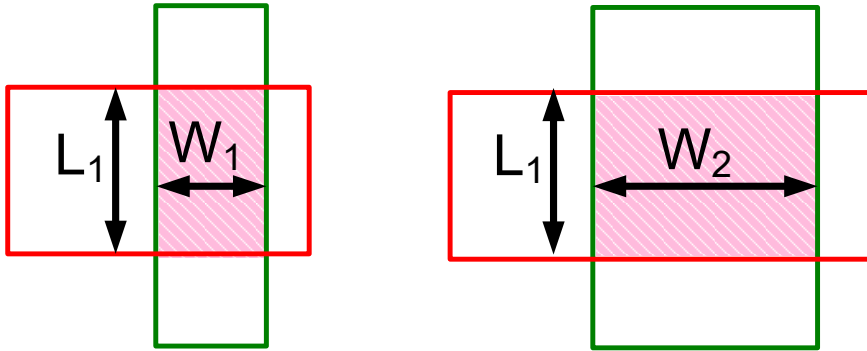

Standard layout
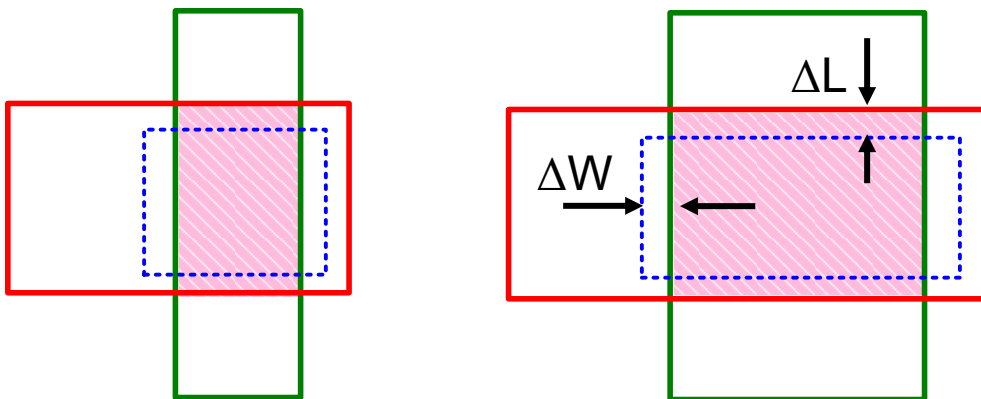
$$M = \left[\frac{W_2}{W_1} \frac{L_1}{L_2} \right]$$




Gate area after fabrication depicted 

$$M = \left[\frac{W_2 + 2\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_2 + 2\Delta L} \right]$$

$$M = \left[\frac{2W_1 + 2\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] \neq 2$$

Layout of Current Mirrors


Example with $M = 2$

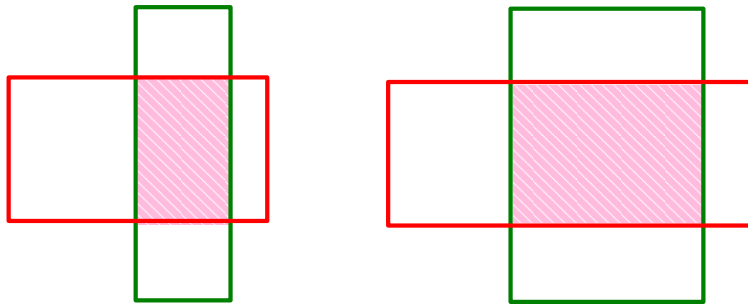

Standard layout

$$M = \left[\frac{W_2 L_1}{W_1 L_2} \right]$$
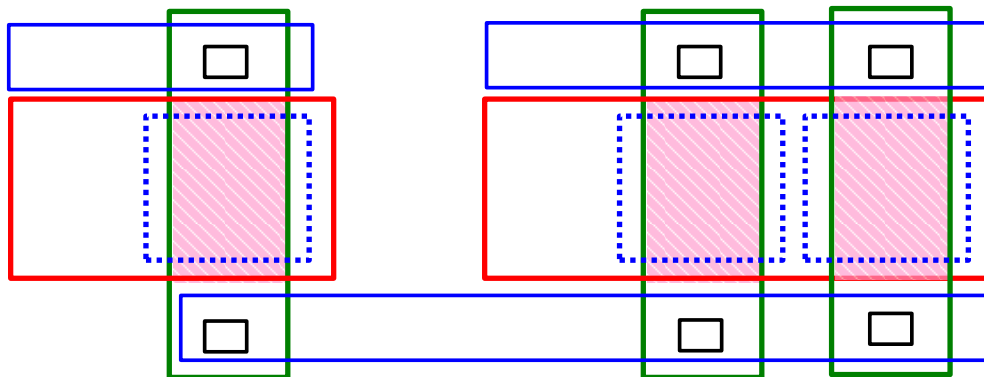
$$M = \left[\frac{2W_1 + 2\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] \neq 2$$




Better Layout

$$M = \left[\frac{2W_1 + 4\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] = 2$$

Layout of Current Mirrors

Example with $M = 2$

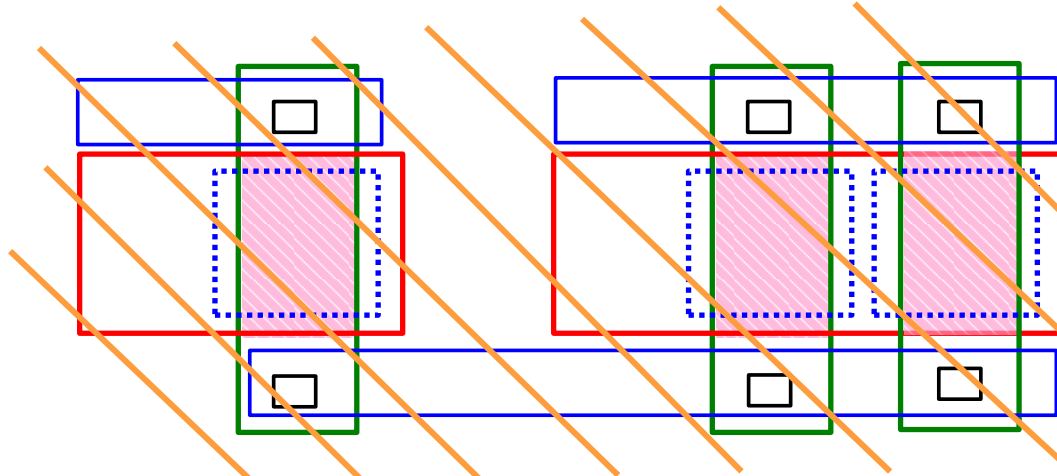

Better Layout

Linear Gradient Direction
of a model parameter
(e.g. μ or V_{TH})

$$M = \left[\frac{2W_1 + 4\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] = 2$$

But this analysis was based upon assumption of matching of process parameters




$$\left. \begin{aligned} I_{in} &= \frac{\mu_0 C_{OX} W_0}{2L_0} (V_{GS0} - V_{T0})^2 \\ I_{out} &= \frac{\mu_1 C_{OX} W_1}{2L_1} (V_{GS1} - V_{T1})^2 \end{aligned} \right\}$$

Even with this better layout, the current ratio will not be 2 if gradient effects such as those depicted here are shown

And both magnitude and direction of gradient effects are a random variable which will vary across a die

Centroid and Common Centroid


✕ Denotes Geometric Centroid

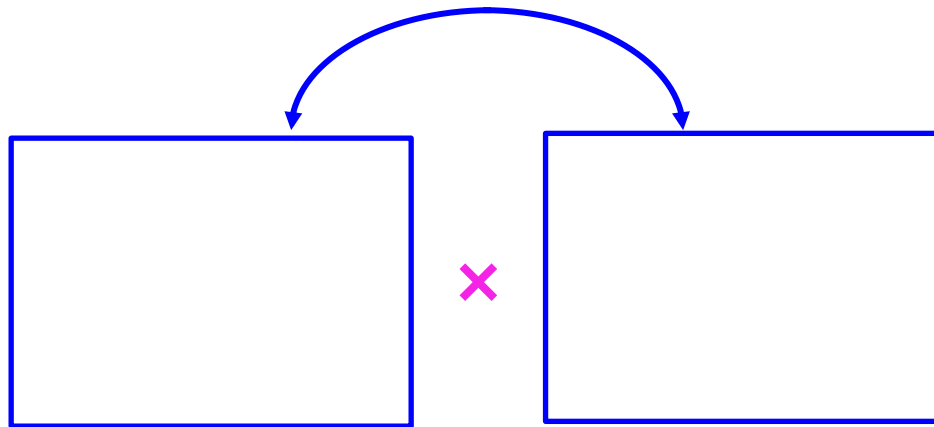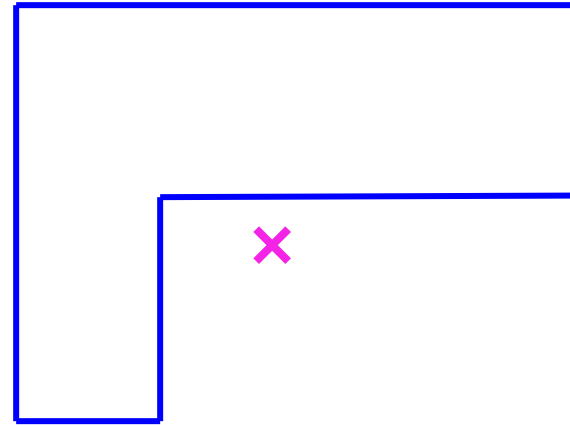 


Centroid and Common Centroid

Geometric Centroids of Channel

Two Transistors:

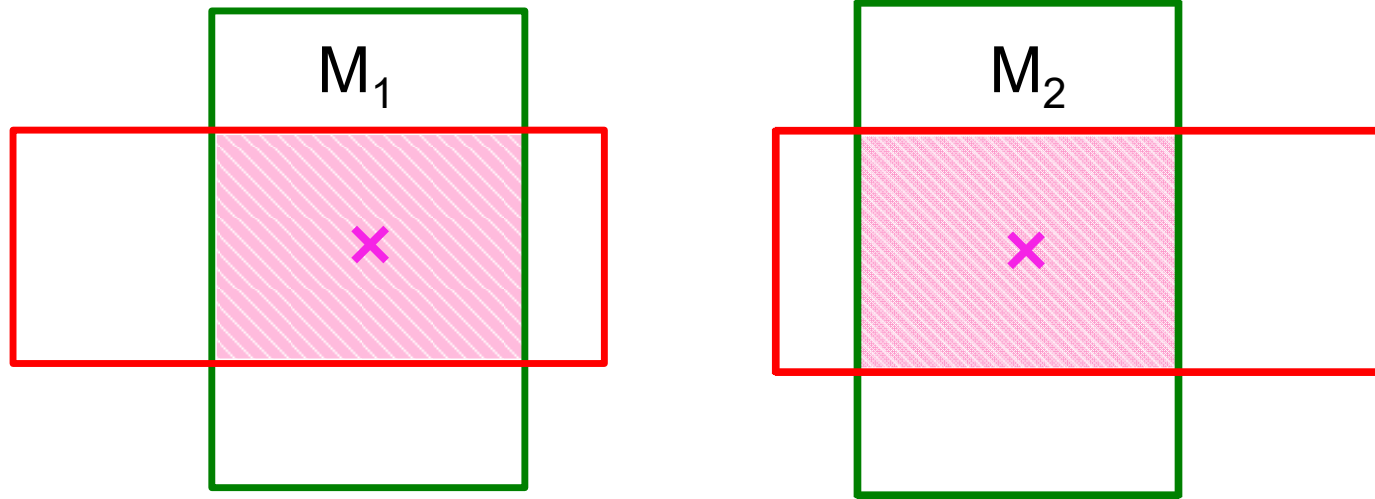


Two Parts of One Transistor:

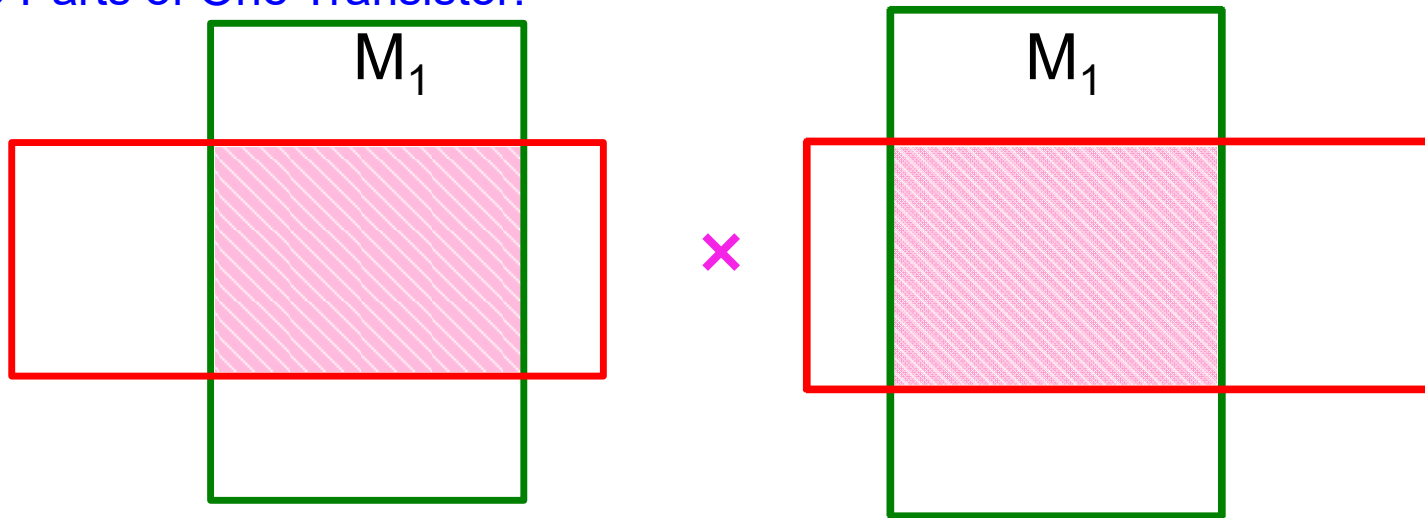

Centroid and Common Centroid


Two Transistors each with two parts:

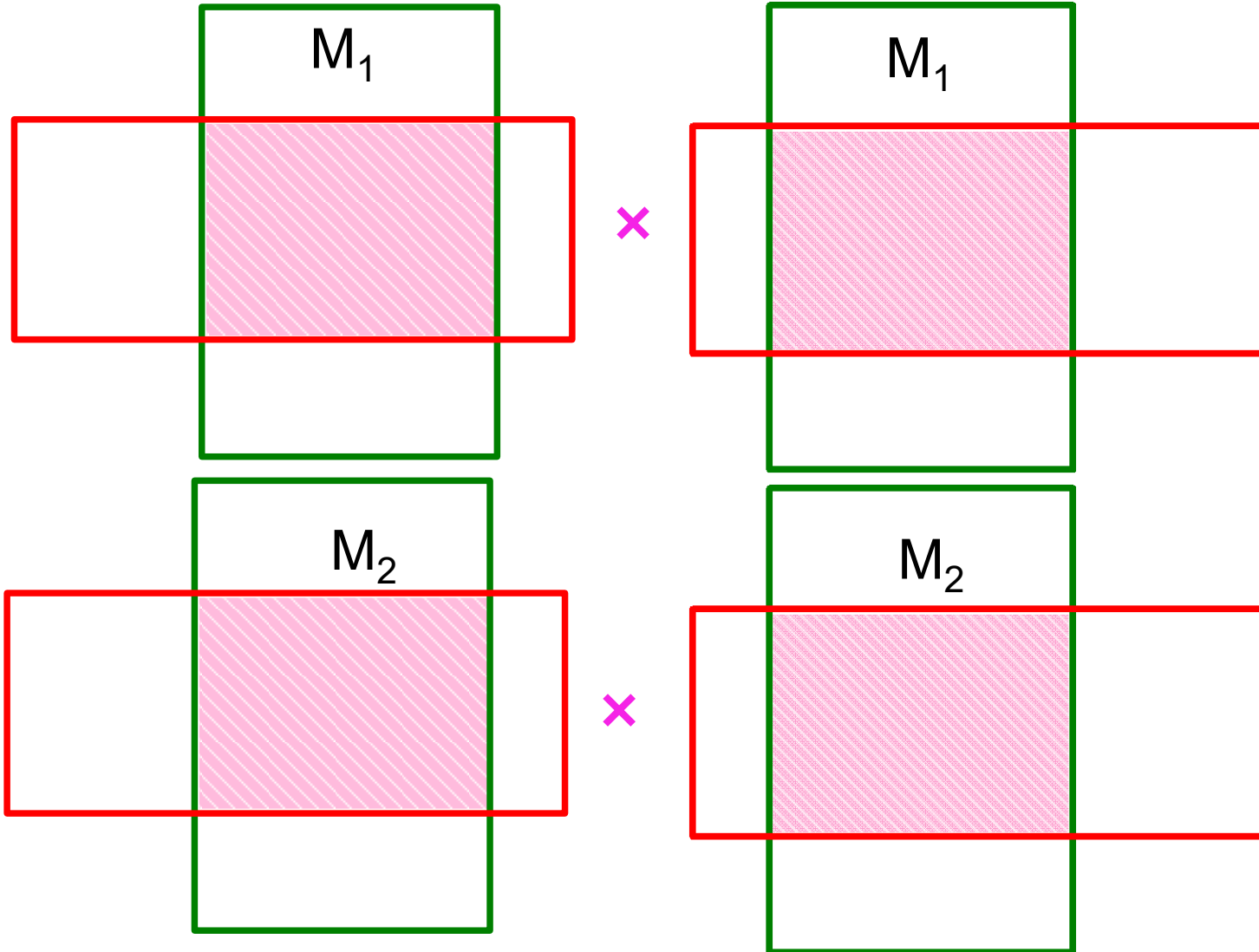

Centroid and Common Centroid

Common Centroid for Ideally Matched Devices


Two Transistors each with two parts:

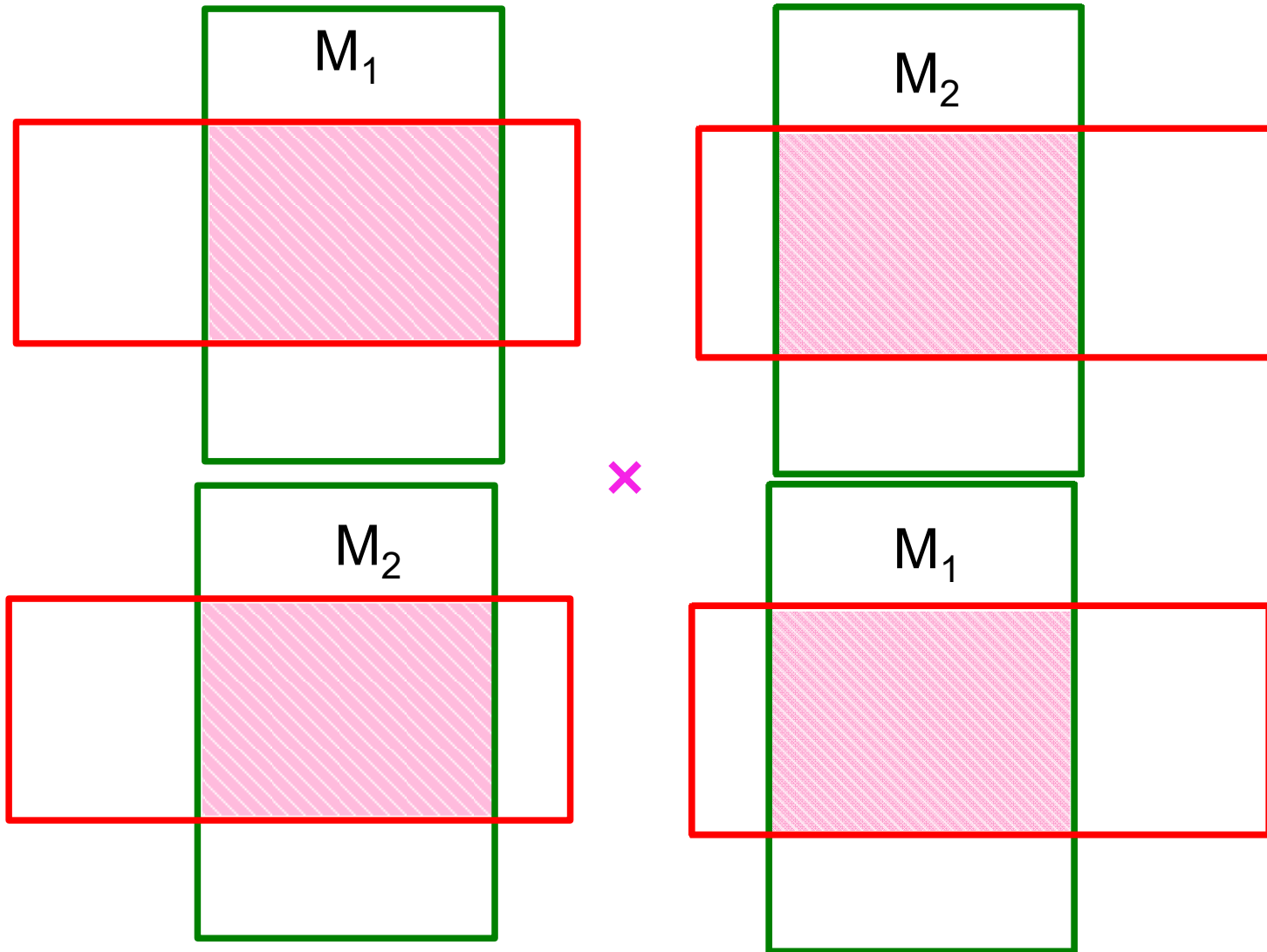

Centroid and Common Centroid

Common Centroid for Matched Devices


Two Transistors each with two parts:

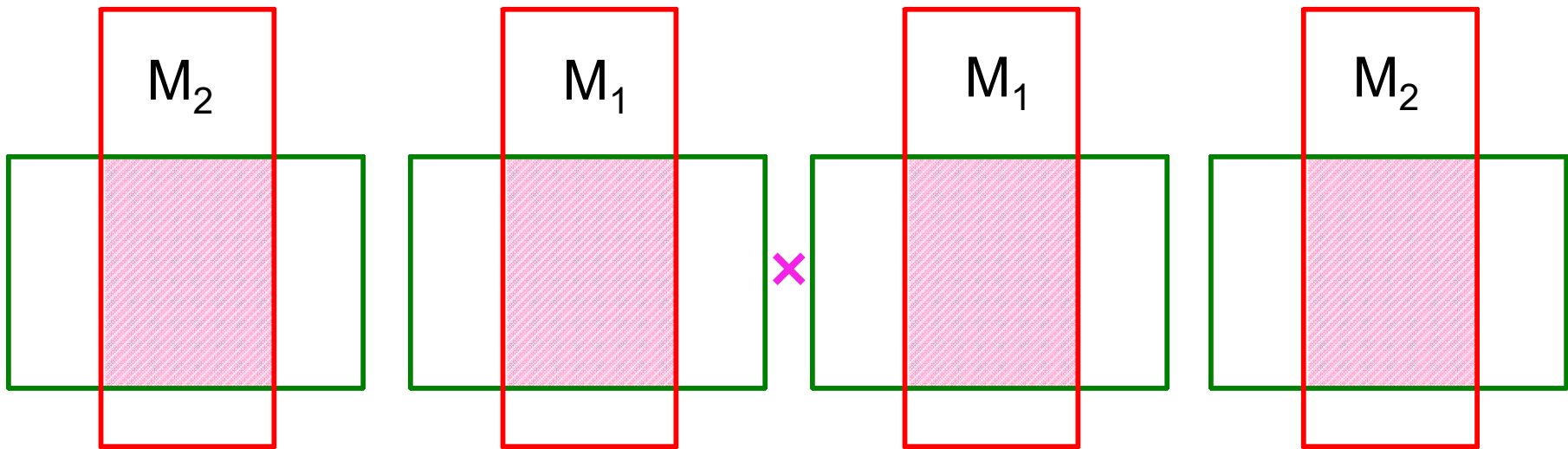


Centroid and Common Centroid

Common Centroid for Ratioed Devices $M = \frac{W_2 L_1}{W_1 L_2} = 2$

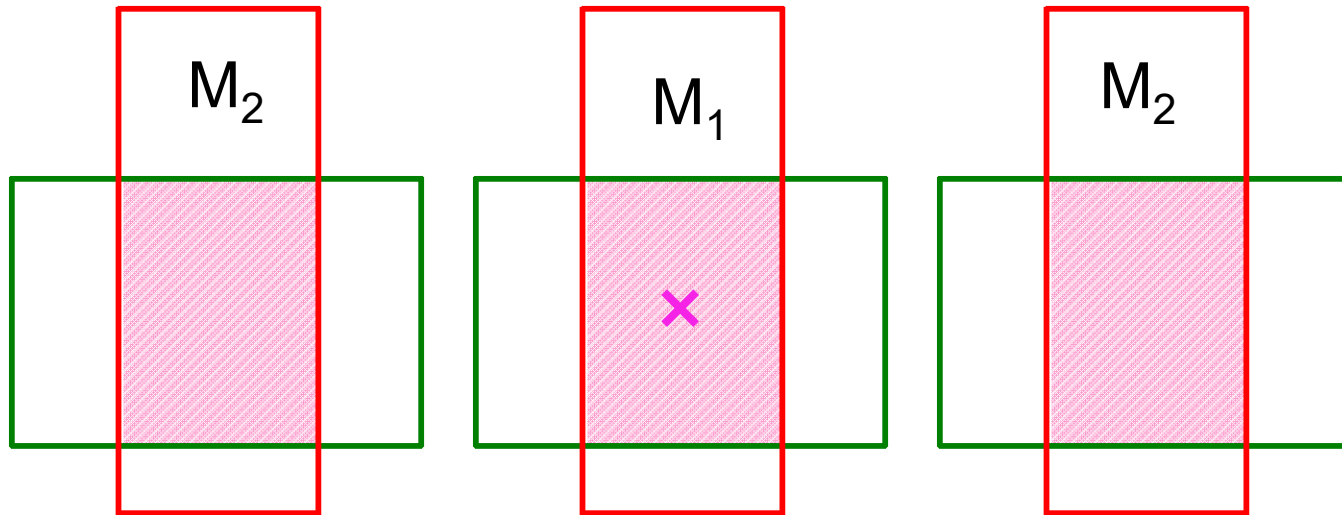Two Transistors with different effective widths:



Gradient

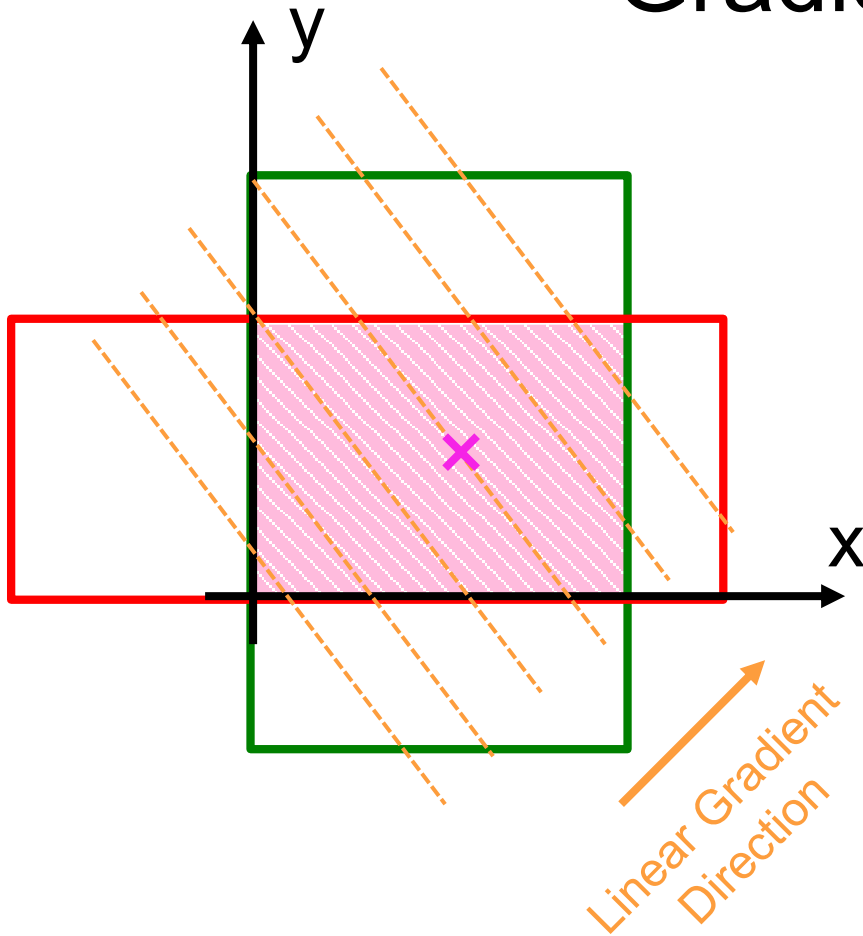

Threshold voltage
dependent upon position

$$V_{TH}(x,y)$$


- Significant changes in threshold voltage can occur due to gradient effects
- This can seriously degrade matching in matching-critical circuits

- If the threshold voltage of a transistor changes with position, it can be reasonably accurately modeled with an “equivalent” threshold voltage
- For linear gradient, $V_{THEQ} = V_{TH}(X_C, Y_C)$

$$\times : (X_C, Y_C)$$


Layout of Current Mirrors

Example with $M = 2$

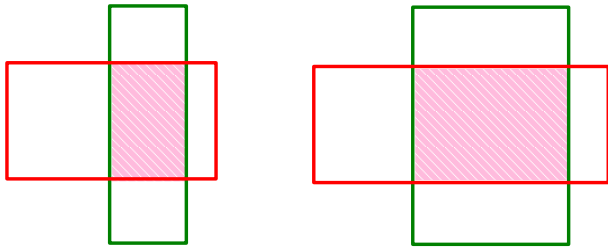


Standard layout
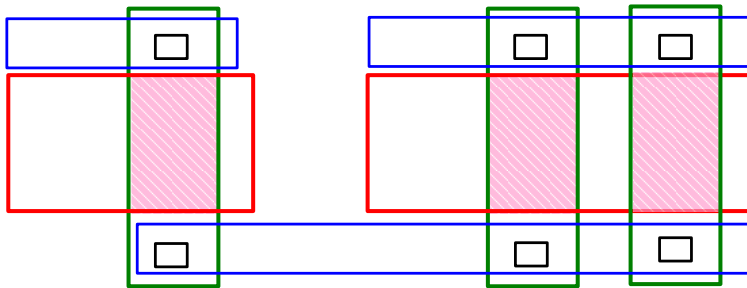
$$M = \left[\frac{W_2 L_1}{W_1 L_2} \right]$$



Better Layout
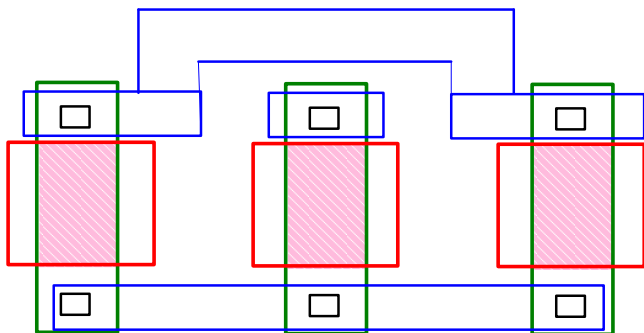
$$M = \left[\frac{2W_1 + 4\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] = 2$$




Even Better Layout


$$M = \left[\frac{2W_1 + 4\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] = 2$$

- This is termed a common-centroid layout
- Linear gradient mismatch eliminated with common-centroid layout !

Common-Centroid Layouts

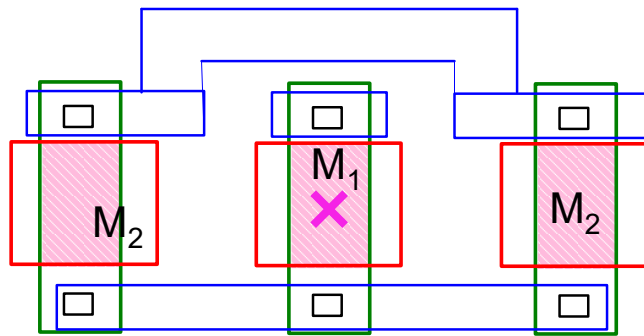


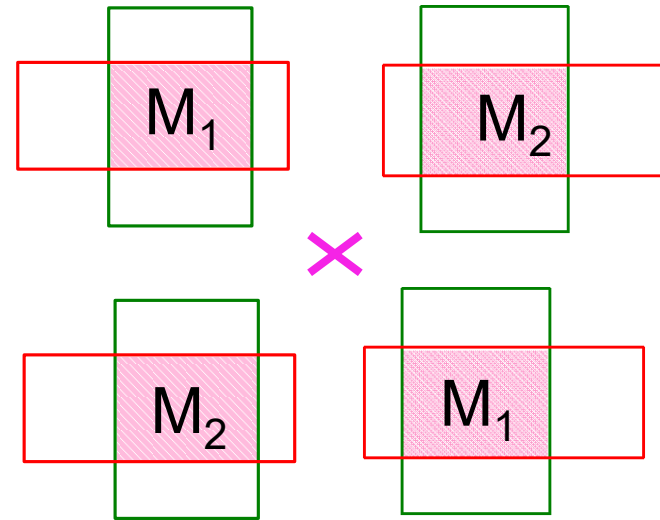
$$M = \left[\frac{2W_1}{W_1} \cdot \frac{L_1}{L_1} \right] = 2$$



$$M = \left[\frac{2W_1}{2W_1} \cdot \frac{L_1}{L_1} \right] = 1$$

- Individual transistors often decomposed into parallel multiple unary devices connected in parallel
- Common-Centroid layout approach widely used to minimize (ideally cancel) gradient effects in matching-critical circuits
- Applications extend well beyond current mirrors
- More than 2 devices can share a common centroid


Current Sources/Mirrors

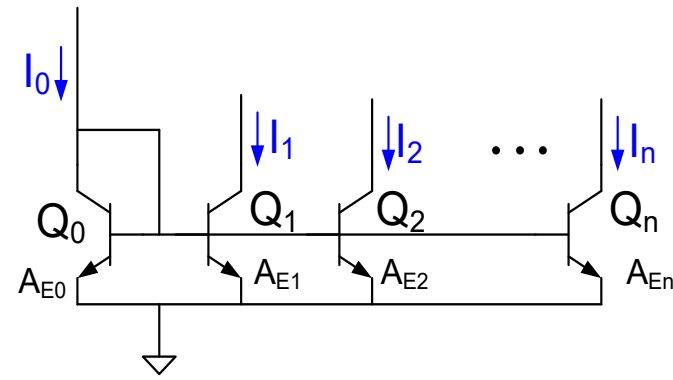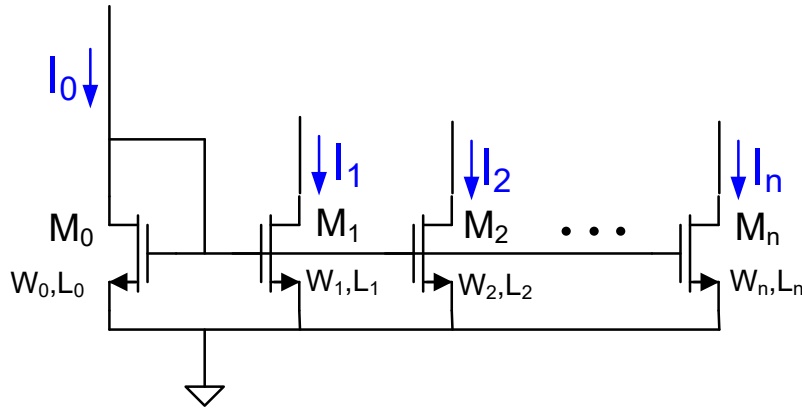


If I_0 is practically generated (it can be), now have available a large number of accurate current sources or sinks that can be used for biasing and for other purposes on chip !

High-gain amplifier

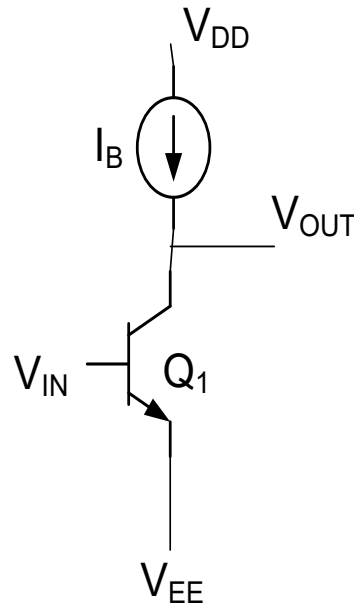Will now return to discussion of high gain amplifiers



High-gain amplifier

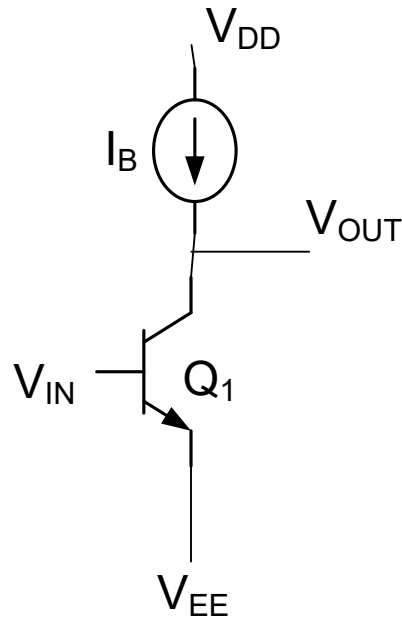


$$A_V \cong -8000$$

Why are we interested in high-gain amplifiers?

- High gain amplifiers typically have some very undesirable properties
Nonlinear, gain highly dependent upon process variations and temperature, frequency response poor, noisy,
- So we can build feedback amplifiers !!

High-gain amplifier

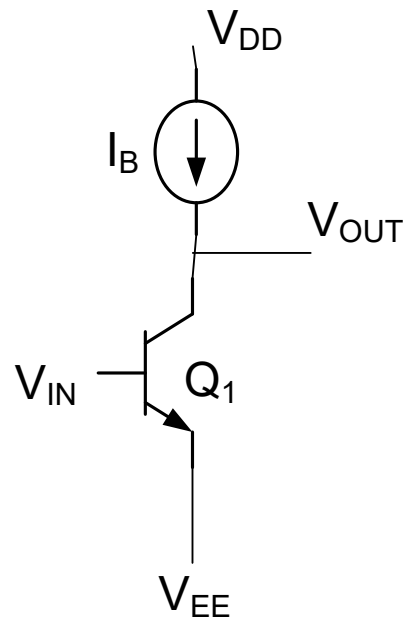


$$A_V \cong -8000$$

→ How can we build the current source?


What is the small-signal model of an actual current source?

Basic Current Sources and Sinks

Bipolar Mirror-Based Current Sink

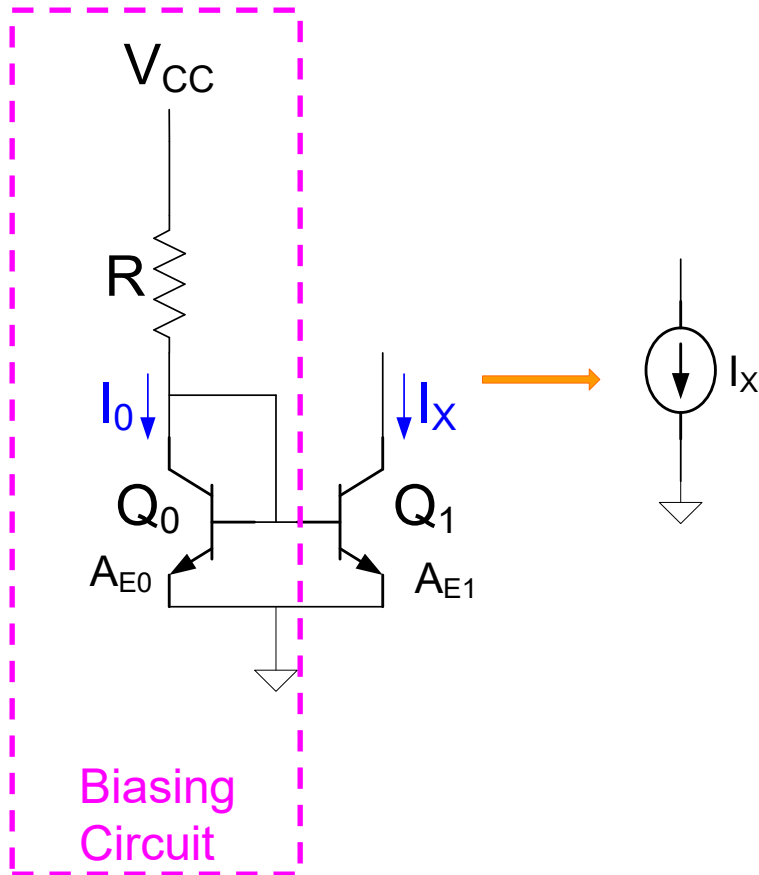


Bipolar Mirror-Based Current Source

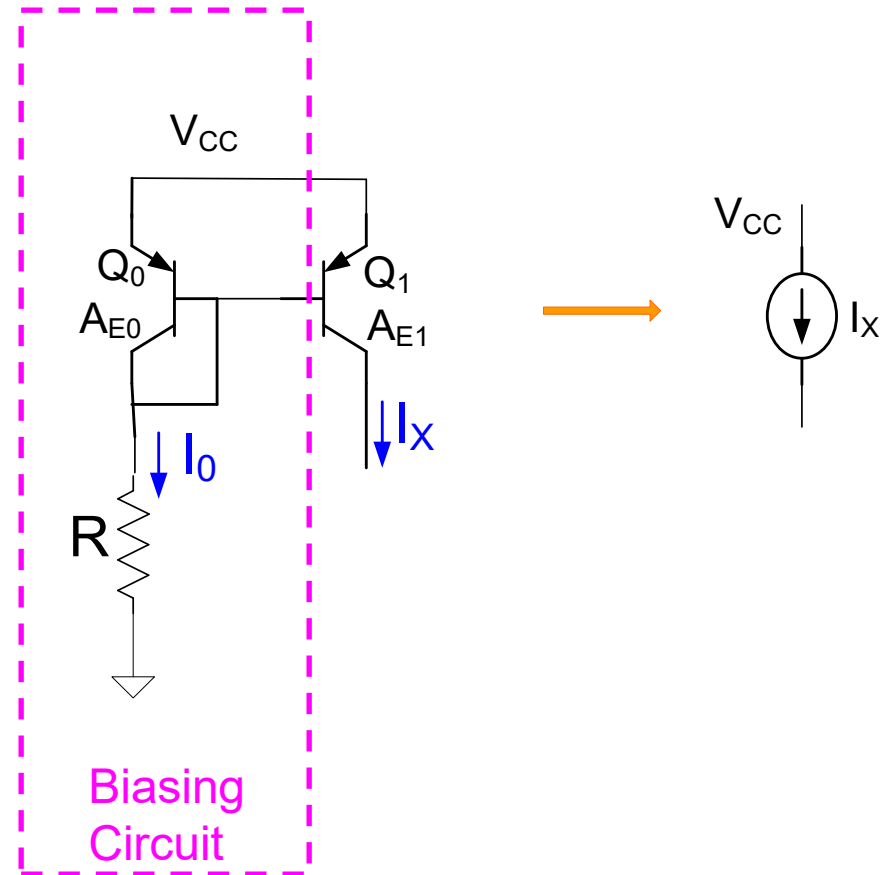



Biassing circuit uses same V_{CC} as amplifier and no other independent sources

High-gain amplifier

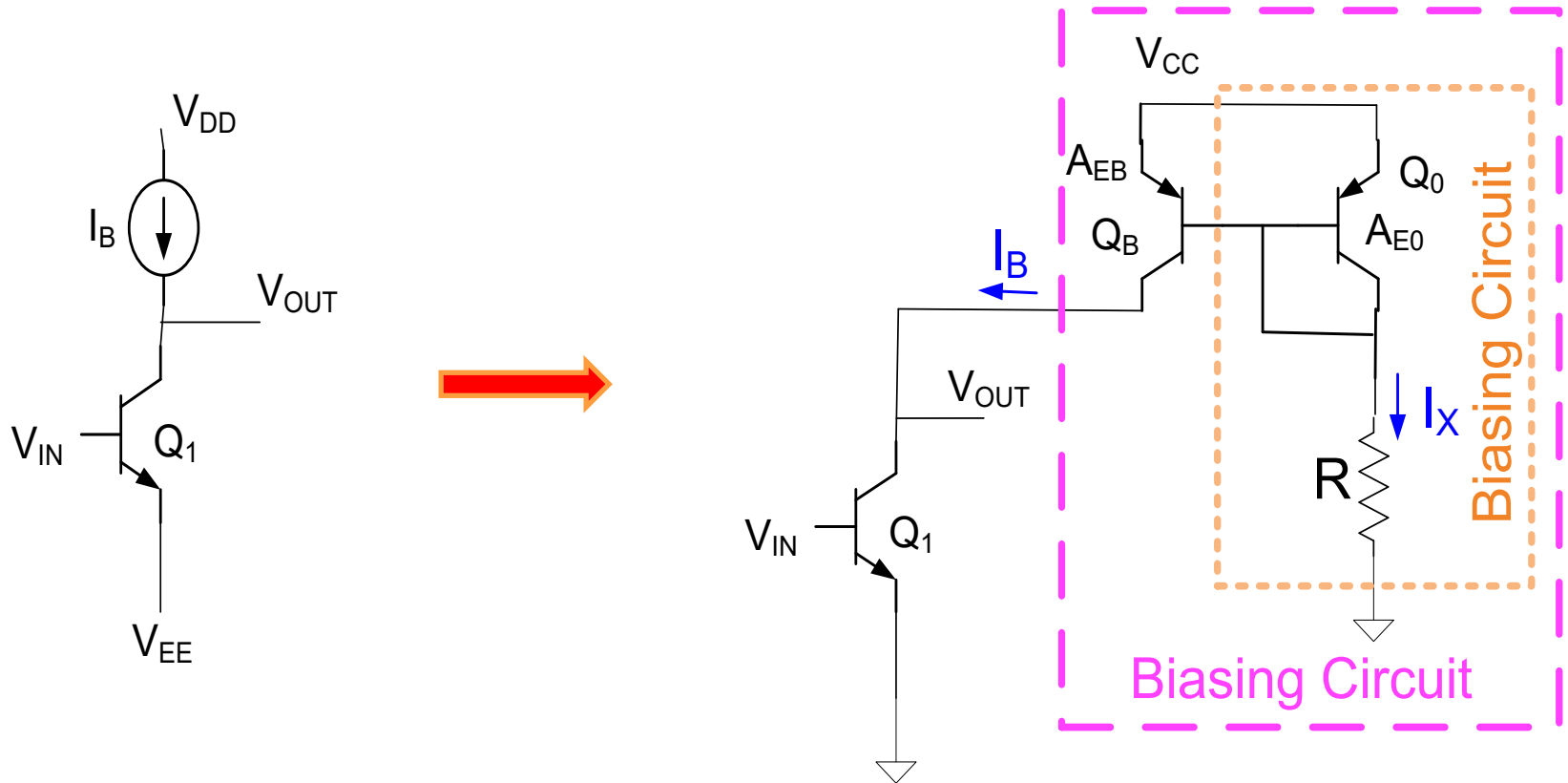

- Bias circuitry requires only a single independent dc voltage source, resistor, and BJT !
- Incremental overhead is only one transistor, Q_B

High-gain amplifier

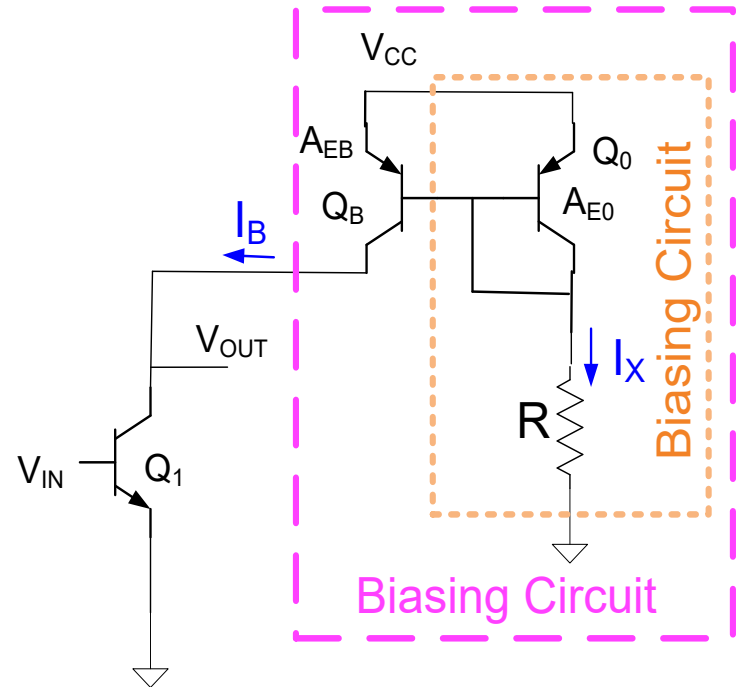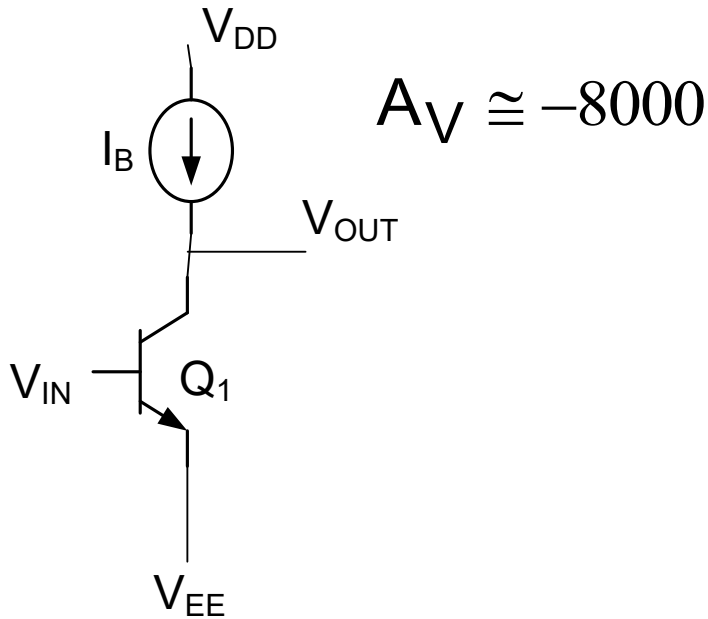


How can we build the current source?

→ What is the small-signal model of an actual current source?


Basic Current Sources and Sinks

What is the small-signal model of an actual current source?

Basic Bipolar Current Sinks

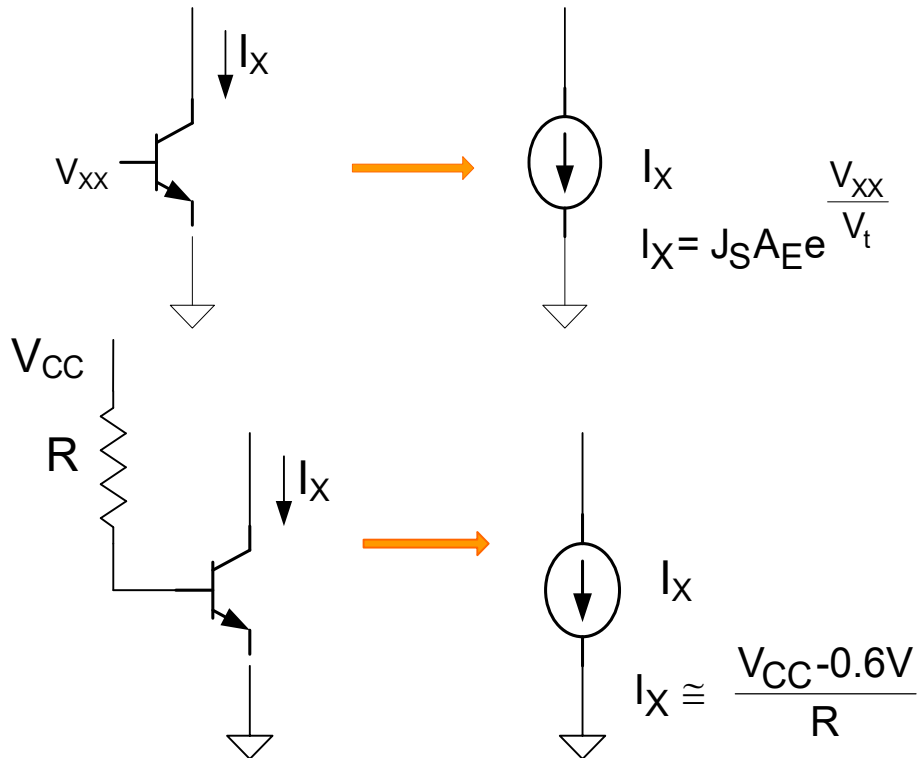



Basic Bipolar Current Sources

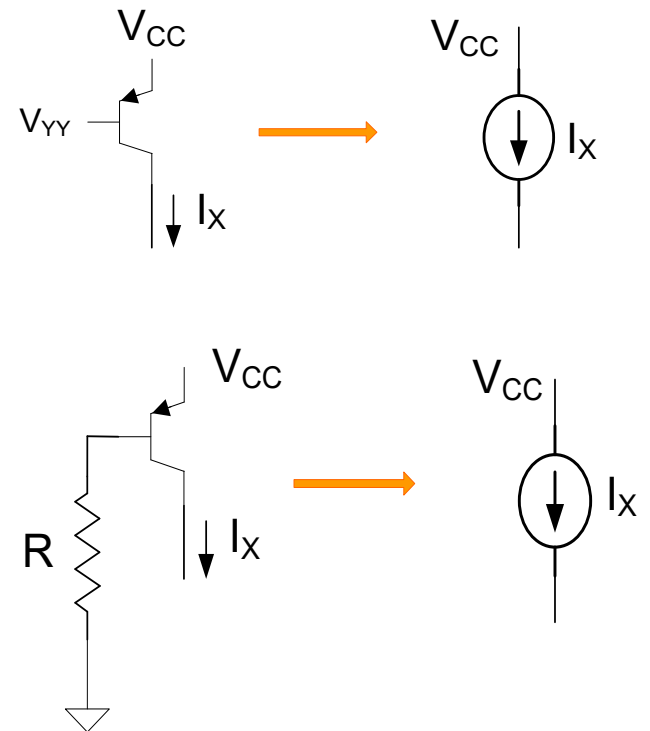



- Very practical methods for biasing the BJTs (or MOSFETs) can be used
- Current Mirrors often used for generating sourcing and sinking currents
- Can think of biasing transistors with V_{XX} and V_{YY} in these current sources

Basic Current Sources and Sinks

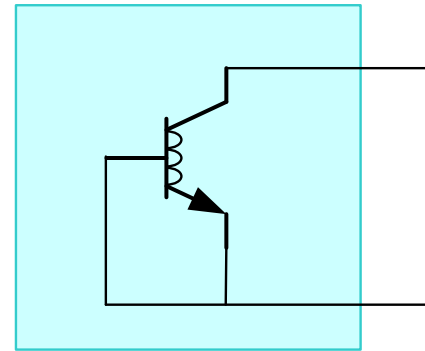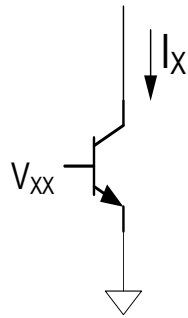Small-signal Model of BJT Current Sinks and Sources





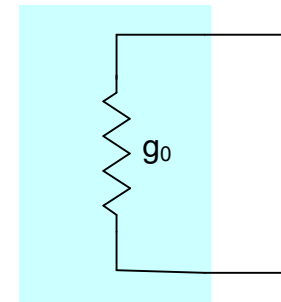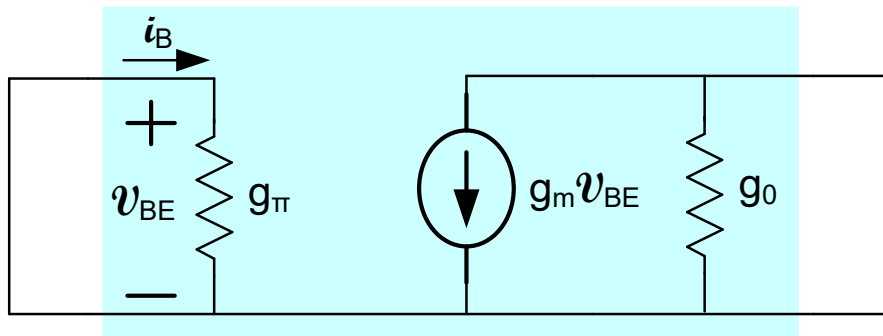Small-signal BE-Connected
(Not Diode Connected !)





Basic Current Sources and Sinks

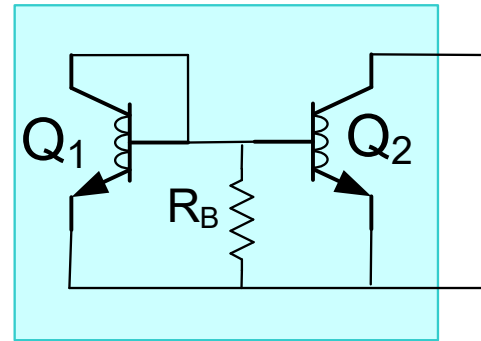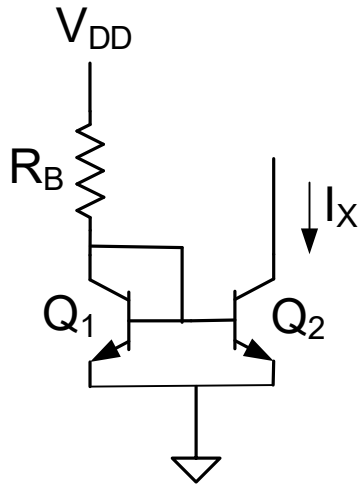Small-signal Model of BJT Current Sinks and Sources




Small-signal of Q_1
Diode connected

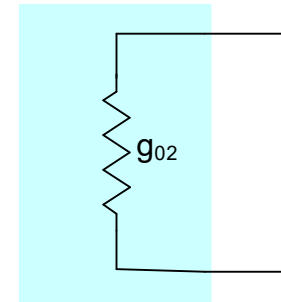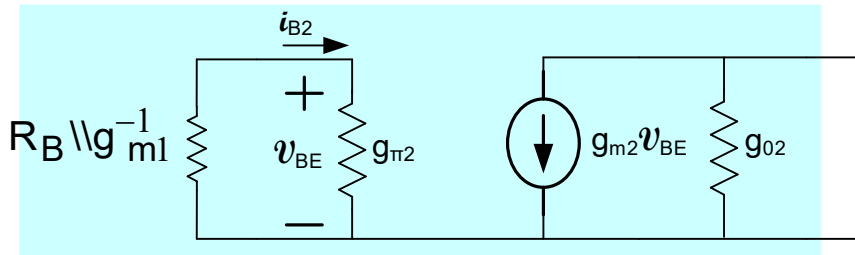

Small-signal model of all other BJT Sinks and Sources introduced so far are the same



Basic Current Sources and Sinks

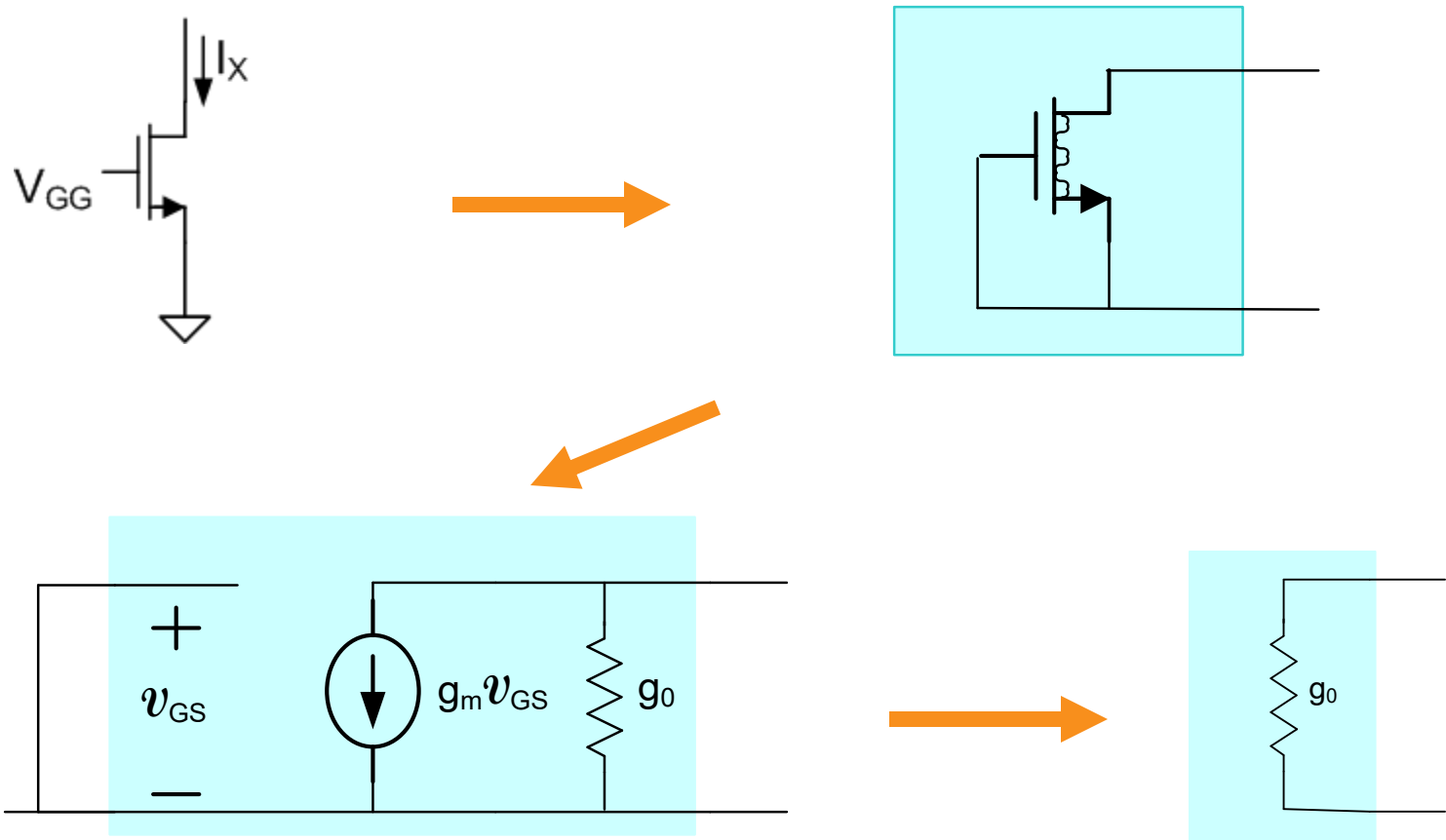Small-signal Model of MOS Current Sinks and Sources






Small-signal model of all other MOS Sinks and Sources introduced thus far are the same

High-gain amplifier

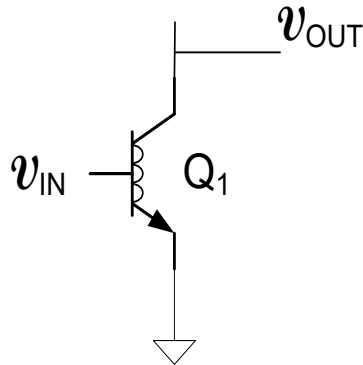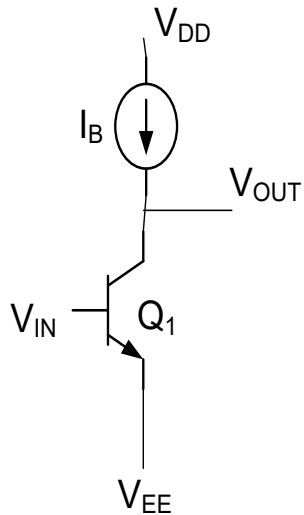


$$A_V = \frac{-g_m}{g_o}$$

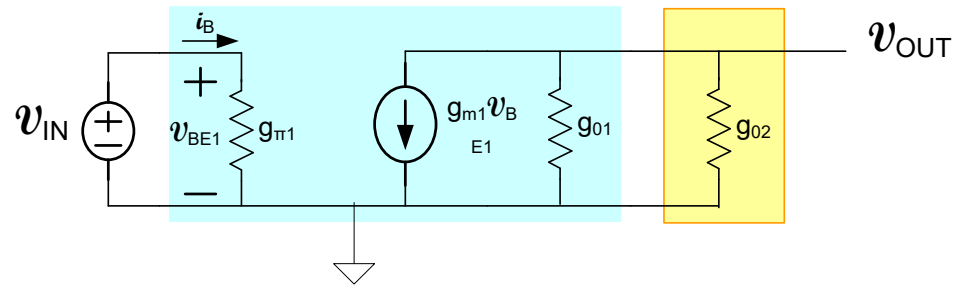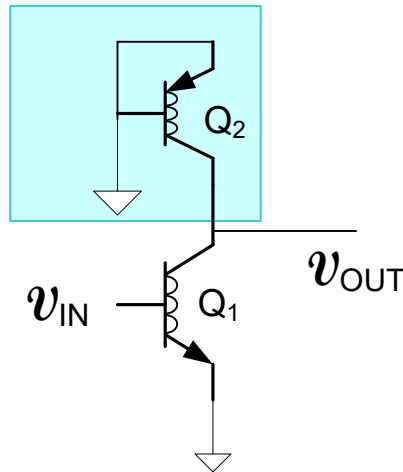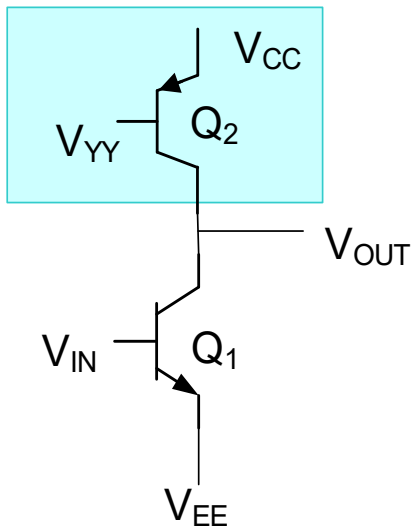


$$A_V = \frac{-g_{m1}}{g_{o1} + g_{o2}} \approx \frac{-g_{m1}}{2g_{o1}}$$

High-gain amplifier

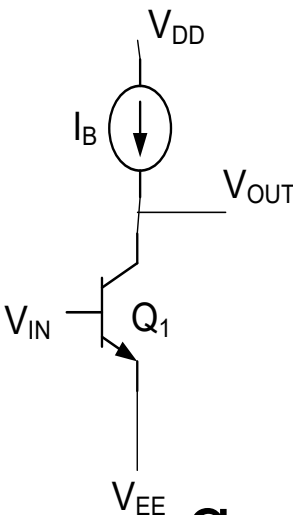

$$A_V = \frac{-g_m}{g_0} = -8000$$
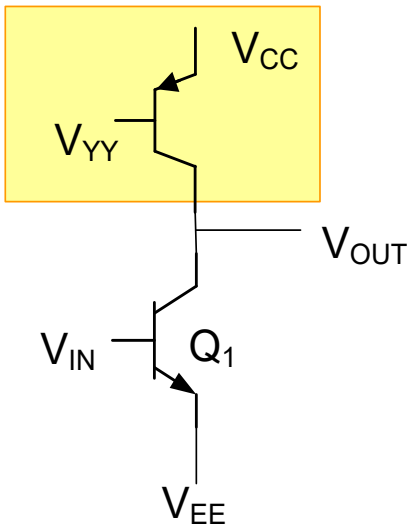
$$\frac{g_m}{g_0} = \frac{g_{m1}}{g_{01}} = \frac{V_{AF}}{V_t} \cong 8000$$



$$A_V \cong \frac{-g_{m1}}{2g_{01}} = -4000$$

- Nonideal current source decreased the gain by a factor of 2
- But the voltage gain is still quite large (-4000)





Can the gain be made even larger?

High-gain amplifier


Can the gain be made even larger?

Discuss

The Cascode Configuration

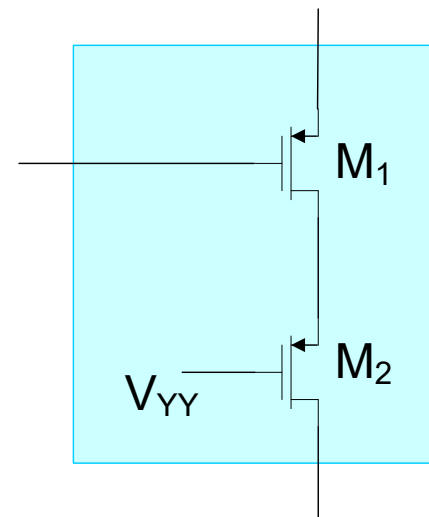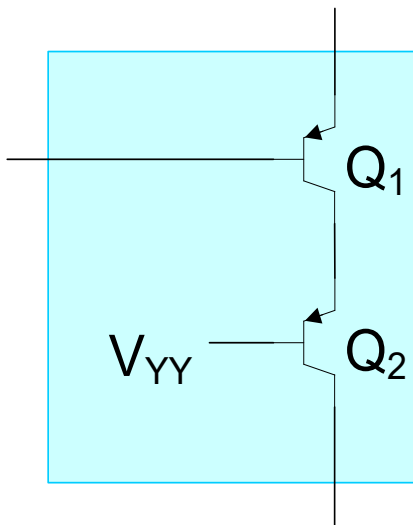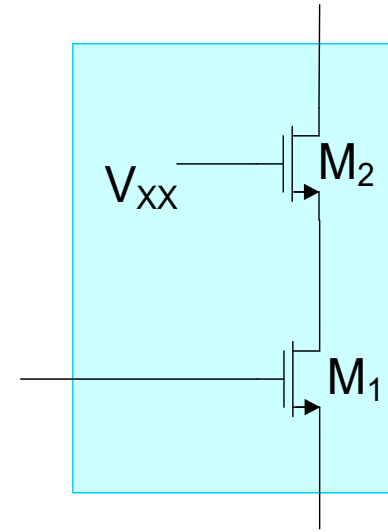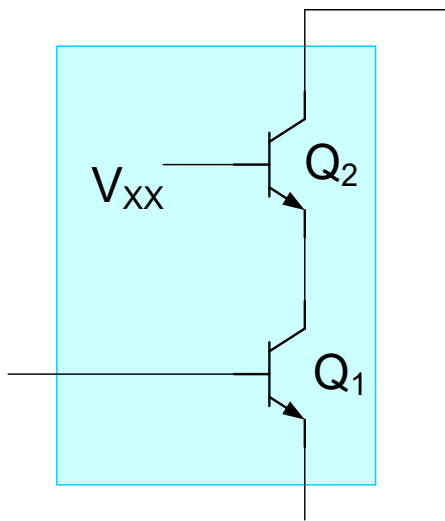

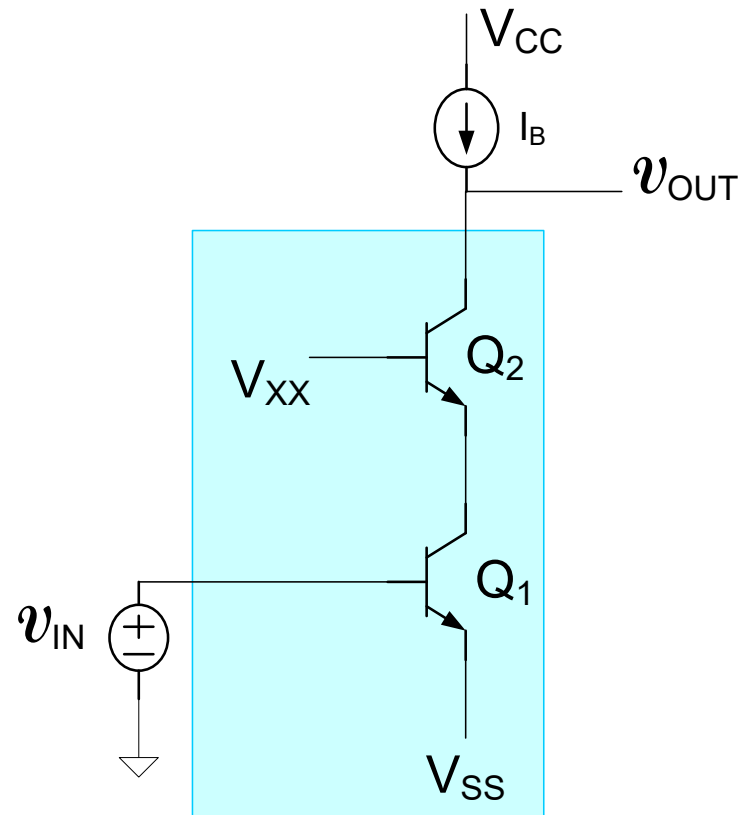The Cascode Amplifier (consider npn BJT version)



Discuss

- **Actually a cascade of a CE stage followed by a CB stage but usually viewed as a “single-stage” structure**
- **Cascode structure is widely used**




Basic Amplifier Structures

Discuss

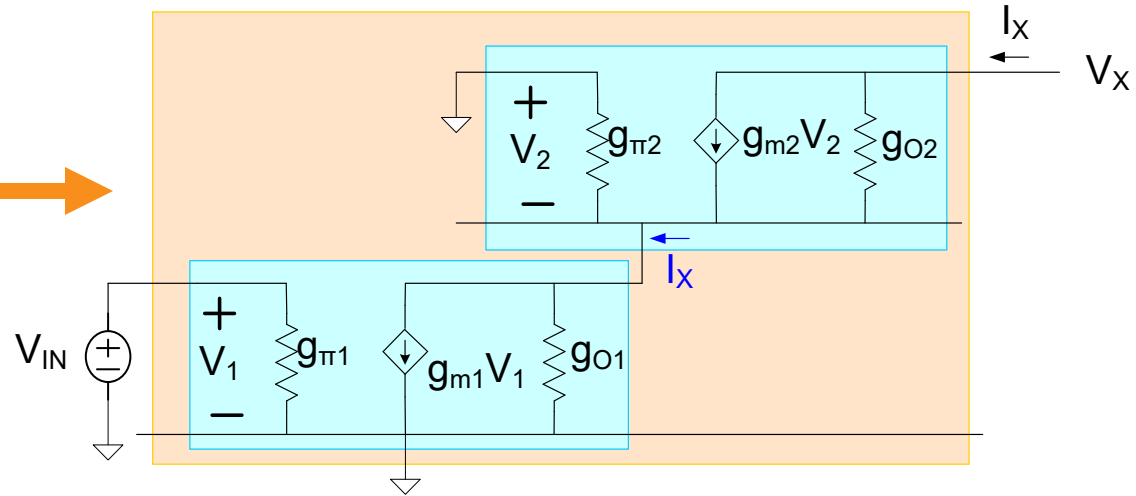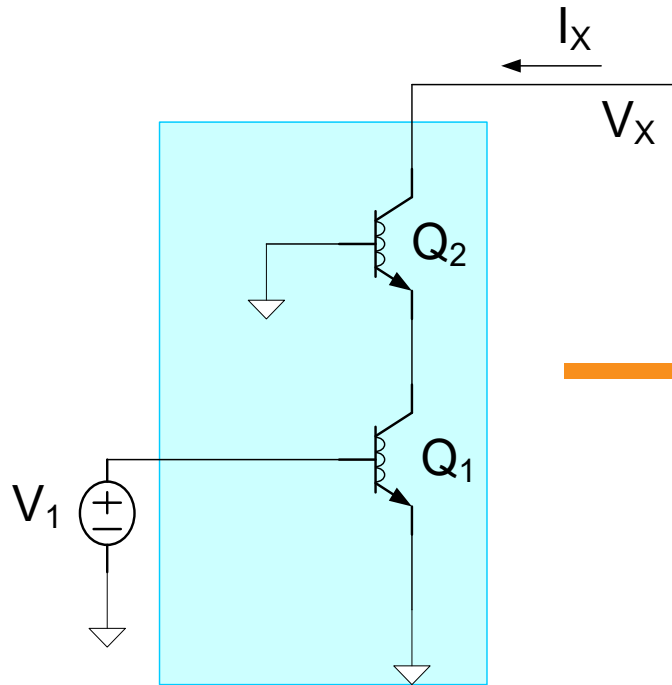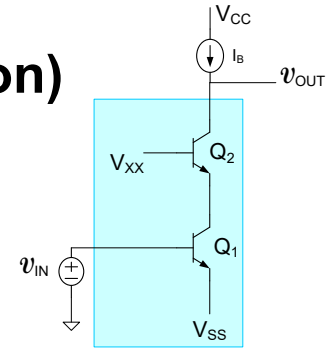1. Common Emitter/Common Source
2. Common Collector/Common Drain
3. Common Base/Common Gate
4. Common Emitter with R_E / Common Source with R_S
- 5. Cascode (actually CE:CB or CS:CD cascade)
6. Darlington (special CE:CE or CS:CS cascade)


The first 4 are most popular

The Cascode Amplifier (consider npn BJT version)




Cascode Configuration

Discuss

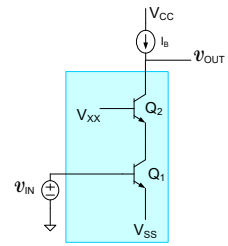


Two-port model of cascode amplifier

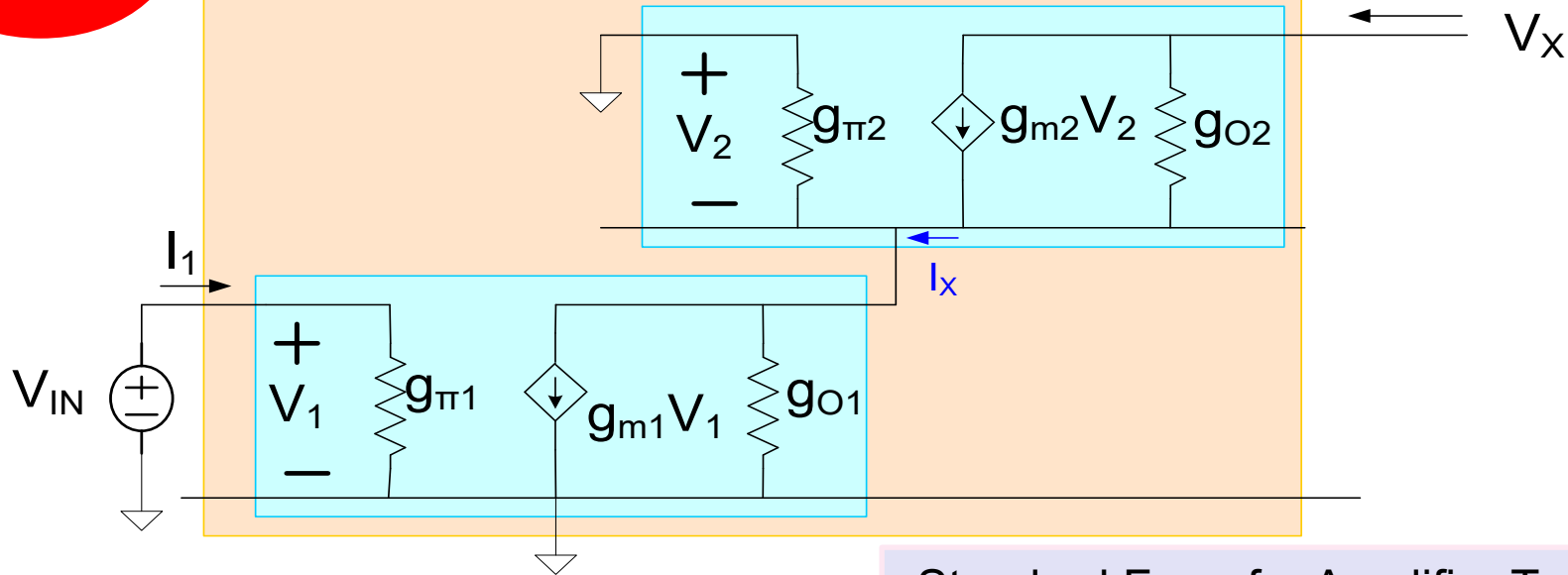

$$\left. \begin{aligned} (V_X + V_2)g_{o2} + V_2g_{m2} &= I_X \\ V_1 g_{m1} - V_2 (g_{o1} + g_{\pi2}) &= I_X \end{aligned} \right\}$$

Standard Form for Amplifier Two-Port

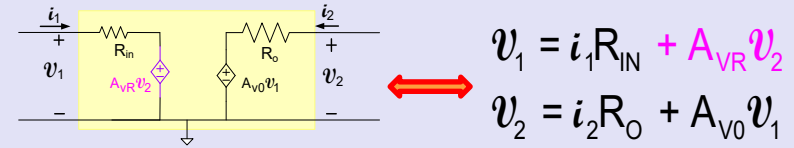

Observing $V_1 = V_{IN}$ and eliminating V_2 between these two equations, we obtain


$$V_{IN} = I_1 \cdot \frac{1}{g_{\pi1}}$$

and

$$V_X = I_X \cdot \left[\frac{g_{o1} + g_{o2} + g_{\pi2} + g_{m2}}{g_{o2} (g_{o1} + g_{\pi2})} \right] - V_{IN} \cdot \left[\frac{g_{m1} (g_{o2} + g_{m2})}{g_{o2} (g_{\pi2} + g_{o1})} \right]$$

Cascode Configuration

Discuss

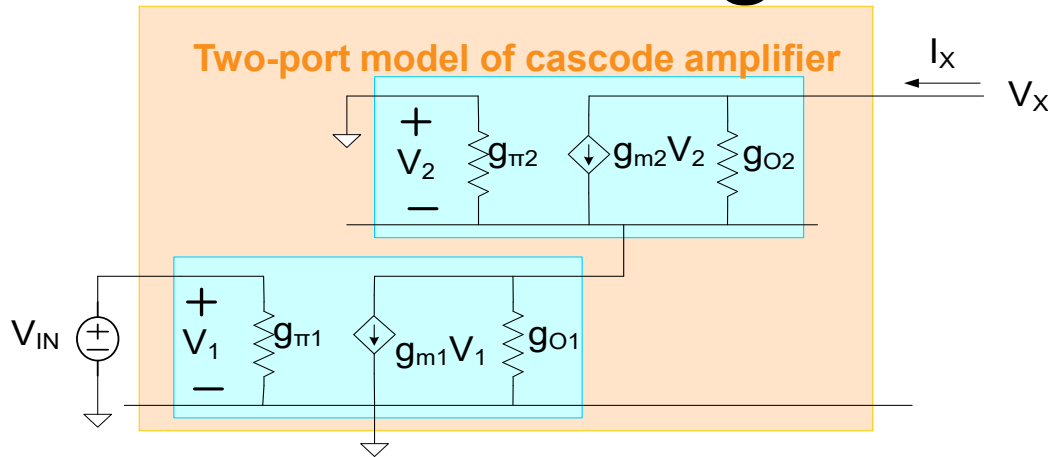

$$V_X = I_X \cdot \left[\frac{g_{o1} + g_{o2} + g_{\pi2} + g_{m2}}{g_{o2}(g_{o1} + g_{\pi2})} \right] - V_{IN} \cdot \left[\frac{g_{m1}(g_{o2} + g_{m2})}{g_{o2}(g_{\pi2} + g_{o1})} \right]$$


$$V_{IN} = I_X \cdot \frac{1}{g_{\pi1}}$$

It thus follows for the npn bipolar structure that :

$$A_{VCC} = - \left[\frac{g_{m1}(g_{o2} + g_{m2})}{g_{o2}(g_{\pi2} + g_{o1})} \right] \cong - \left[\frac{g_{m1}g_{m2}}{g_{o2}g_{\pi2}} \right]$$


$$g_{oCC} = \left[\frac{g_{o2}(g_{o1} + g_{\pi2})}{g_{o1} + g_{o2} + g_{\pi2} + g_{m2}} \right] \cong \left[\frac{g_{o2}g_{\pi2}}{g_{m2}} \right]$$

$$g_{\pi CC} = g_{\pi1}$$

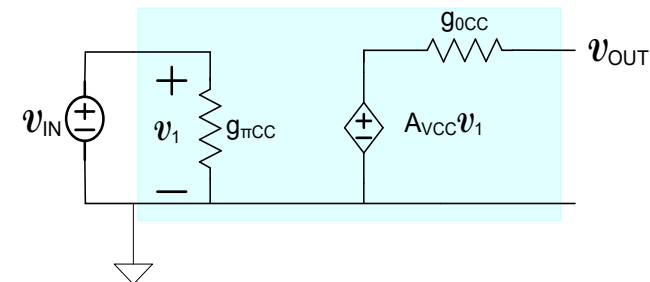

Cascode Configuration

Discuss

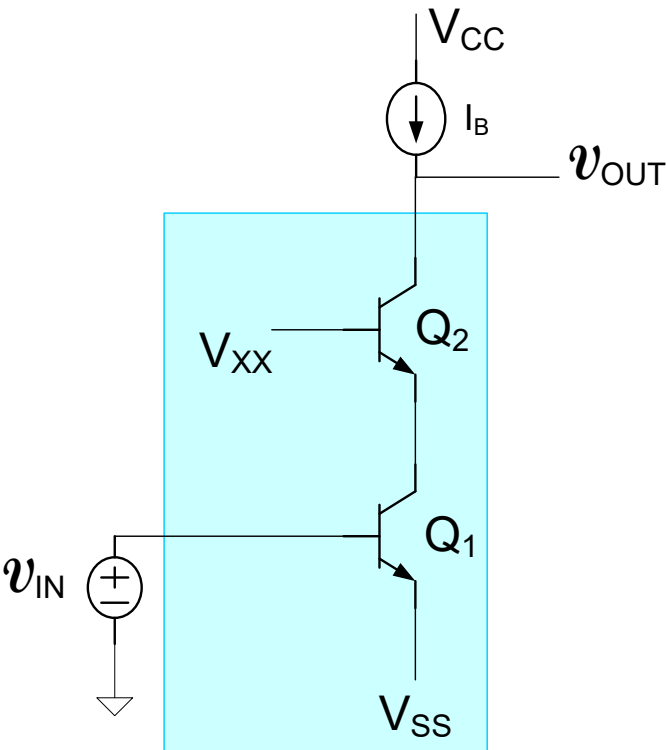

$$A_{V_{CC}} \cong - \left[\frac{g_{m1} g_{m2}}{g_{o2} g_{\pi 2}} \right]$$

$$g_{oCC} \cong \left[\frac{g_{o2} g_{\pi 2}}{g_{m2}} \right]$$

$$g_{\pi CC} = g_{\pi 1}$$


$$A_{V_{CC}} \cong - \left[\frac{g_{m1}}{g_{o2}} \beta \right] \cong - \left[\frac{g_{m1}}{g_{o1}} \right] \beta$$

$$g_{oCC} \cong \frac{g_{o1}}{\beta}$$

- Voltage gain is a factor of β larger than that of the CE amplifier with current source load
- Output impedance is a factor of β larger than that of the CE amplifier

Cascode Configuration

Discuss

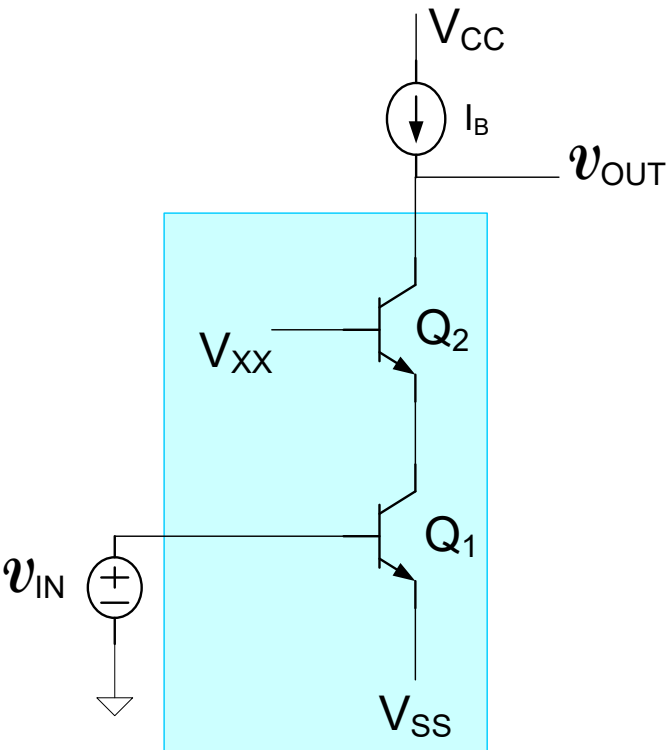

$$A_{V_{CC}} \cong - \left[\frac{g_{m1} \beta}{g_{o2}} \right] \cong - \left[\frac{g_{m1}}{g_{o1}} \right] \beta$$

$$g_{o_{CC}} \cong \frac{g_{o2}}{\beta}$$


$$A_{V_{CC}} \cong - \left[\frac{g_{m1}}{g_{o1}} \right] \beta = \left[\frac{2V_{AF}}{V_t} \right] \beta = [-8000]100$$

$$A_{V_{CC}} \cong -800,000$$


This gain is very large and only requires two transistors!

What happens to the gain if a transistor-level current source is used for I_B ?


Cascode Configuration

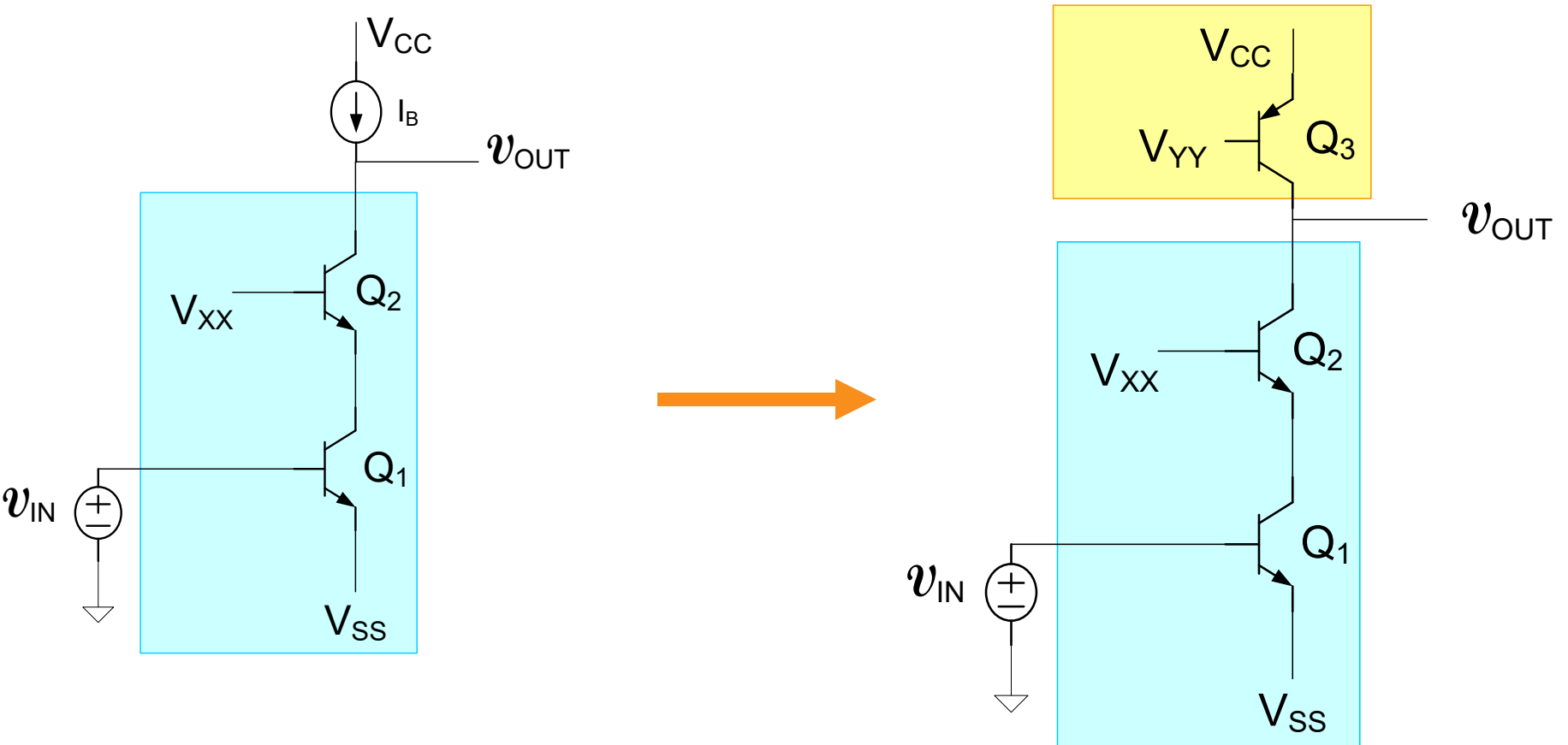

Cascode Configuration

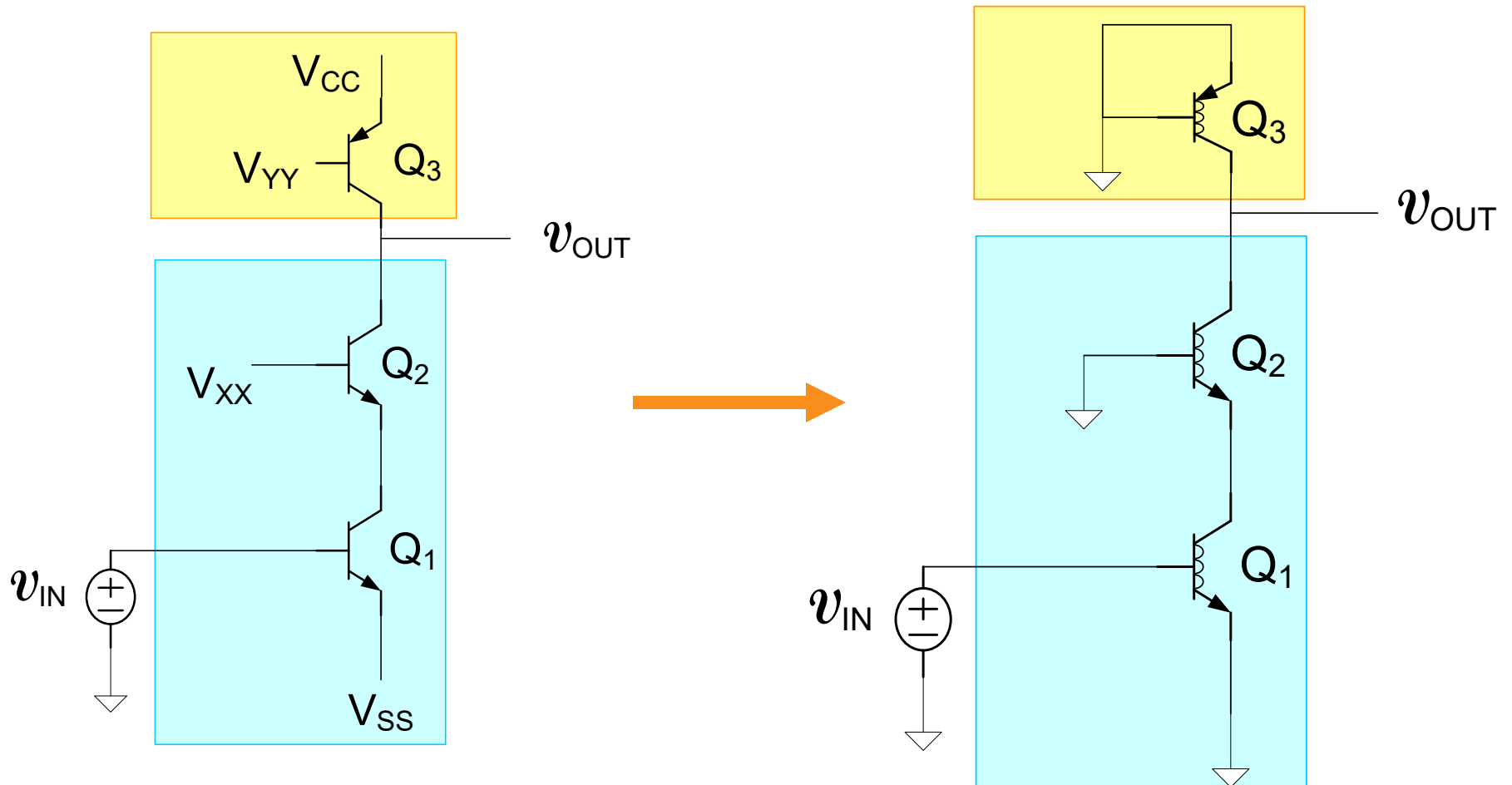

High-gain amplifier comparisons

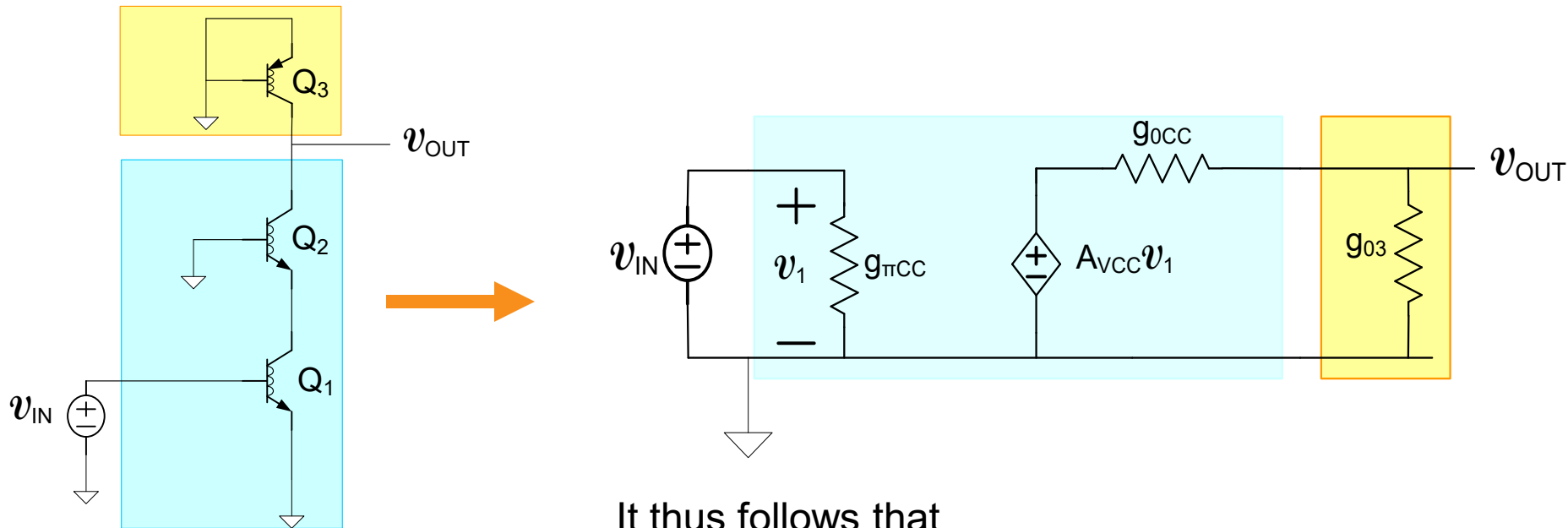

It thus follows that


$$A_V = A_{VCC} \left[\frac{g_{0CC}}{g_{03} + g_{0CC}} \right]$$

But $g_{0CC} \simeq g_{01}/\beta = g_{03}/\beta$

$$A_V \simeq A_{VCC} \left[\frac{g_{0CC}}{g_{03}} \right] \simeq \frac{A_{VCC}}{\beta}$$

This is a dramatic reduction in gain compared to what the ideal current source biasing provided

Cascode Configuration

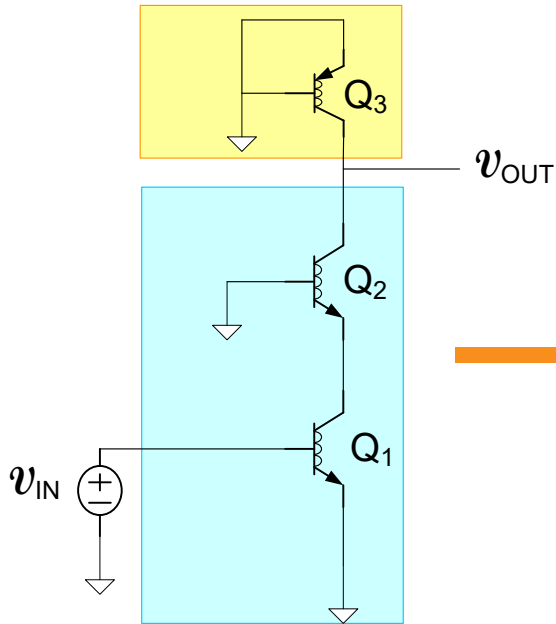

$$A_V \cong A_{VCC} \left[\frac{g_{0CC}}{g_{03}} \right] \cong \frac{A_{VCC}}{\beta}$$

But recall

$$A_{VCC} \cong - \left[\frac{g_{m1}}{g_{01}} \right] \beta$$


Thus

$$A_V \cong - \left[\frac{g_{m1}}{g_{01}} \right]$$


$$A_V \cong - \left[\frac{I_{CQ} / V_t}{I_{CQ} / V_{AF}} \right] = - \left[\frac{V_{AF}}{V_t} \right] \cong -8000$$

- This is still a factor of 2 better than that of the CE amplifier with transistor current source $\left(A_{VCE} \cong - \left[\frac{g_{m1}}{2g_{01}} \right] \right)$
- It only requires one additional transistor
- But its not nearly as good as the gain the cascode circuit seemed to provide


Cascode Configuration Comparisons

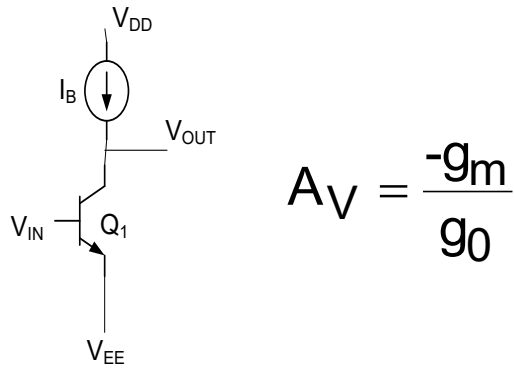


$$A_V = \frac{-g_m}{g_0}$$

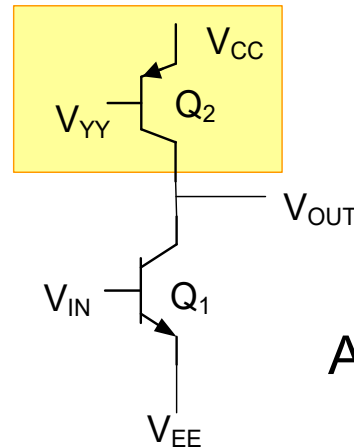
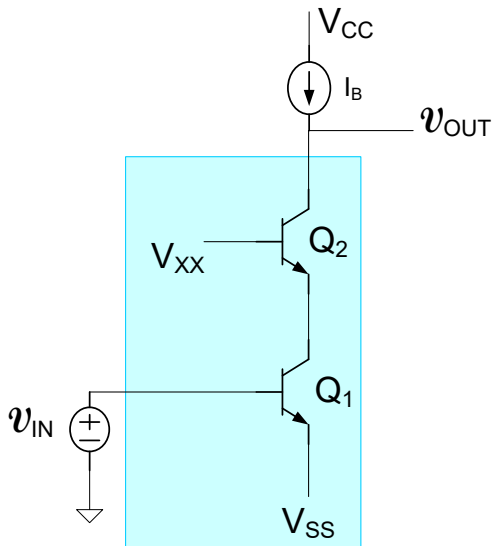
$$A_V \cong \frac{-g_{m1}}{g_{01} + g_{02}} = \frac{-g_{m1}}{2g_{01}}$$


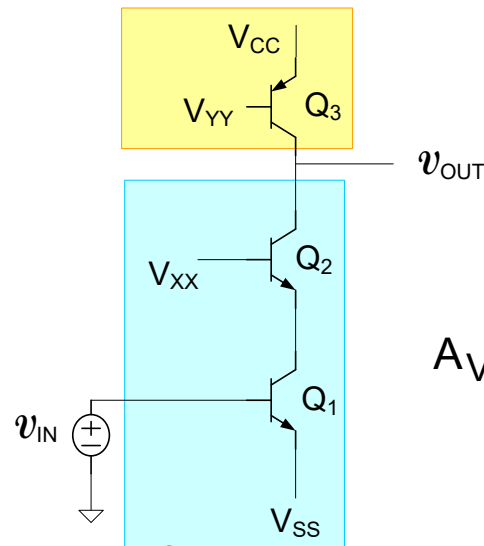
$$A_V \cong - \left[\frac{g_{m1}}{g_{01}} \right] \beta$$



$$A_V \cong - \left[\frac{g_{m1}}{\frac{g_{01}}{\beta} + g_{03}} \right] \cong - \left[\frac{g_{m1}}{g_{03}} \right]$$

Gain limited by output impedance of current source !!

Can we design a better current source?

In particular, one with a higher output impedance?

Better current sources

Need a higher output impedance than g_o




The output impedance of the cascode circuit itself was very large !


$$g_{oCC} \approx \frac{g_{o1}}{\beta}$$

Can a current source be built with the cascode circuit ?








Cascode current sources

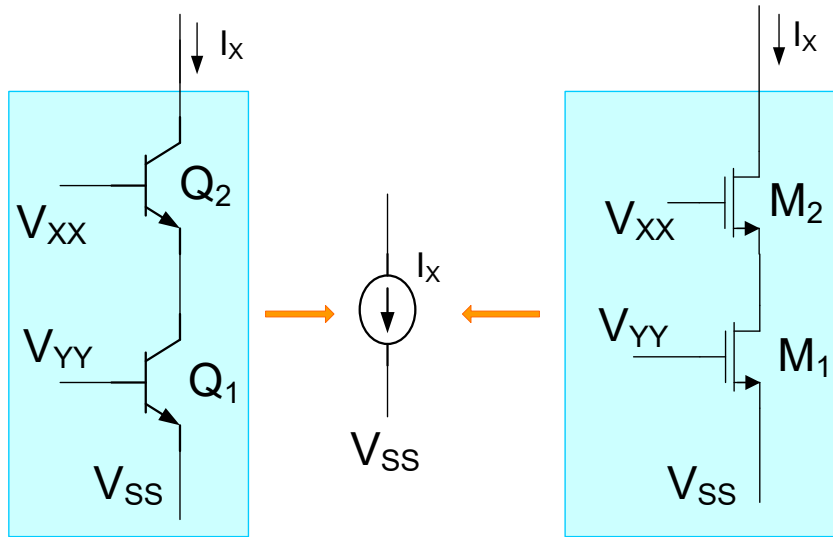

Discuss

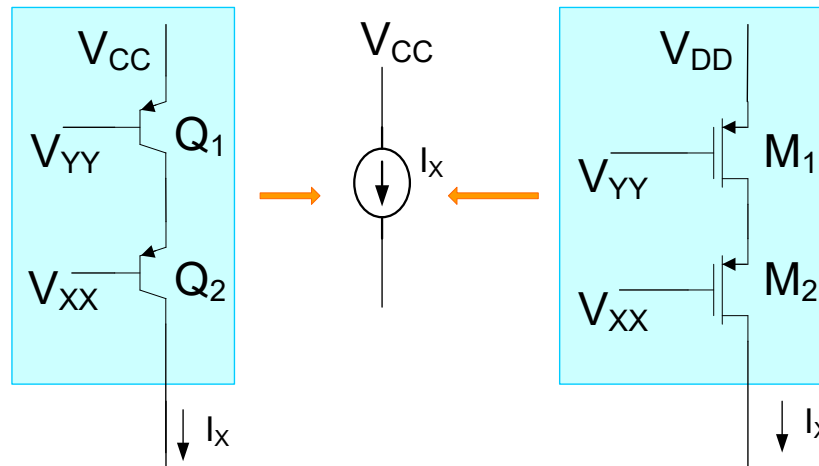


Cascode current sources

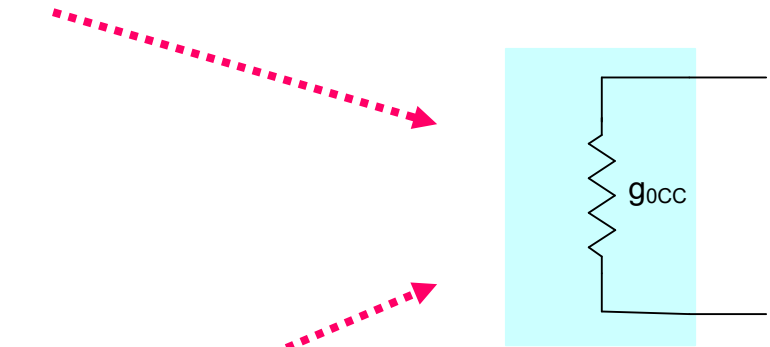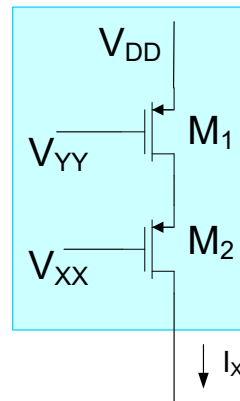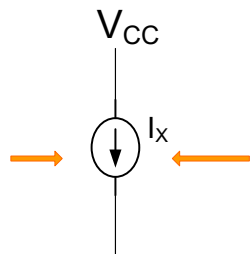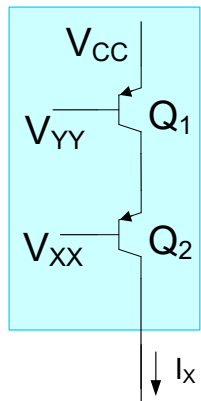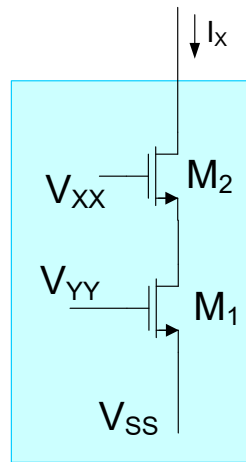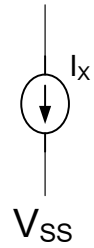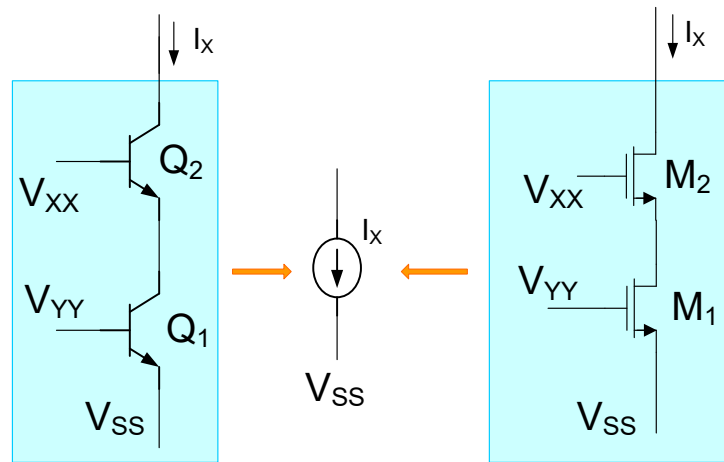

All have the same small-signal model


$$g_{0CC} = \left[\frac{g_{02} (g_{01} + g_{\pi 2})}{g_{01} + g_{02} + g_{\pi 2} + g_{m2}} \right]$$

Cascode current sources

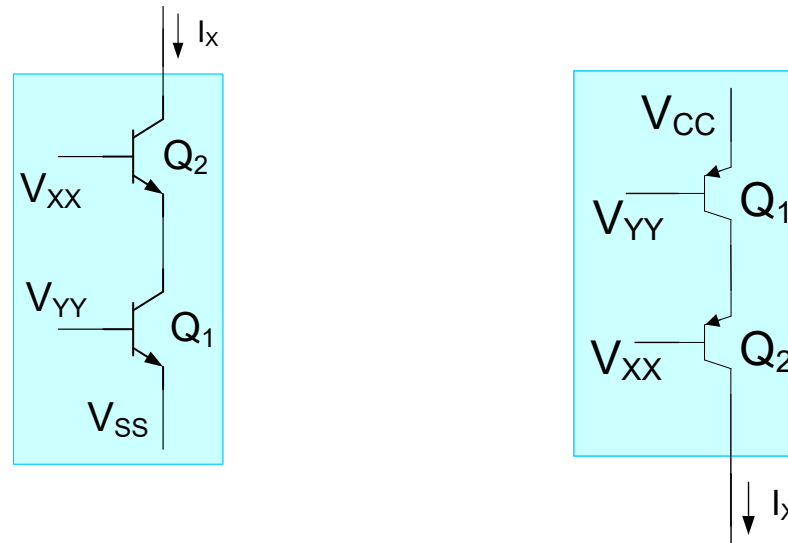


For the BJT cascode current sources
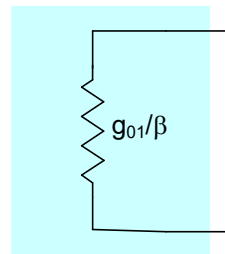
$$g_{oCC} = \left[\frac{g_{o2}(g_{o1} + g_{\pi 2})}{g_{o1} + g_{o2} + g_{\pi 2} + g_{m2}} \right] \cong \left[\frac{g_{o2}g_{\pi 2}}{g_{m2}} \right] = \frac{g_{o1}}{\beta}$$




Cascode Configuration

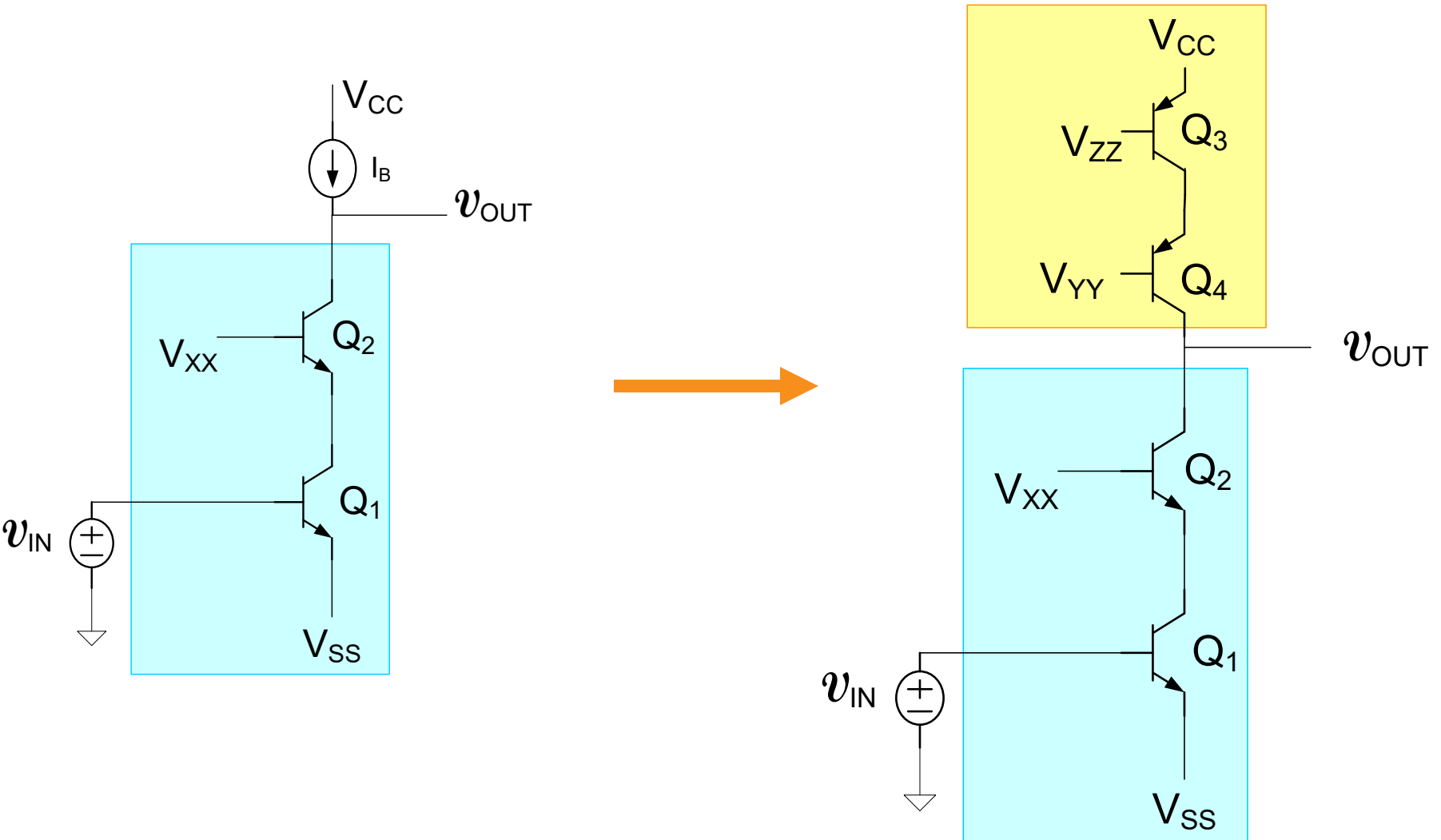

Cascode Configuration

Discuss

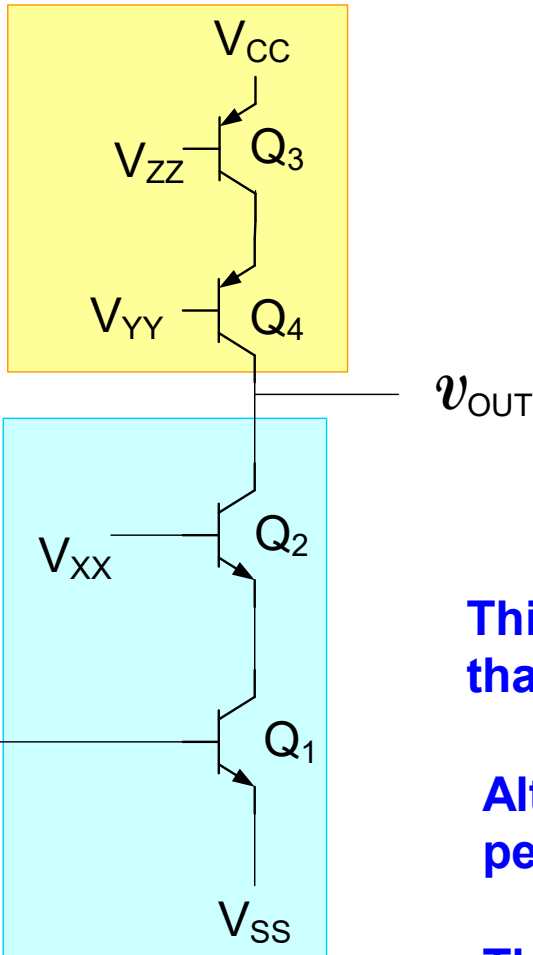

$$A_V \cong - \left[\frac{g_{m1}}{\frac{g_{o1}}{\beta_1} + g_{oCC}} \right] \cong - \left[\frac{g_{m1}}{\frac{g_{o1}}{\beta_1} + \frac{g_{o3}}{\beta_3}} \right]$$

If $\beta_1 = \beta_3 = \beta$

$$A_V = - \left[\frac{g_{m1}}{g_{o1}} \right] \frac{\beta}{2}$$



$$A_V = - [8000] \frac{100}{2} \cong -400,000$$

This gain is very large and is a factor of 2 below that obtained with an ideal current source biasing

Although the factor of 2 is not desired, the performance of this circuit is still very good



This factor of 2 gain reduction is that same as was observed for the CE amplifier when a transistor-level current source was used

Cascode Configuration Comparisons

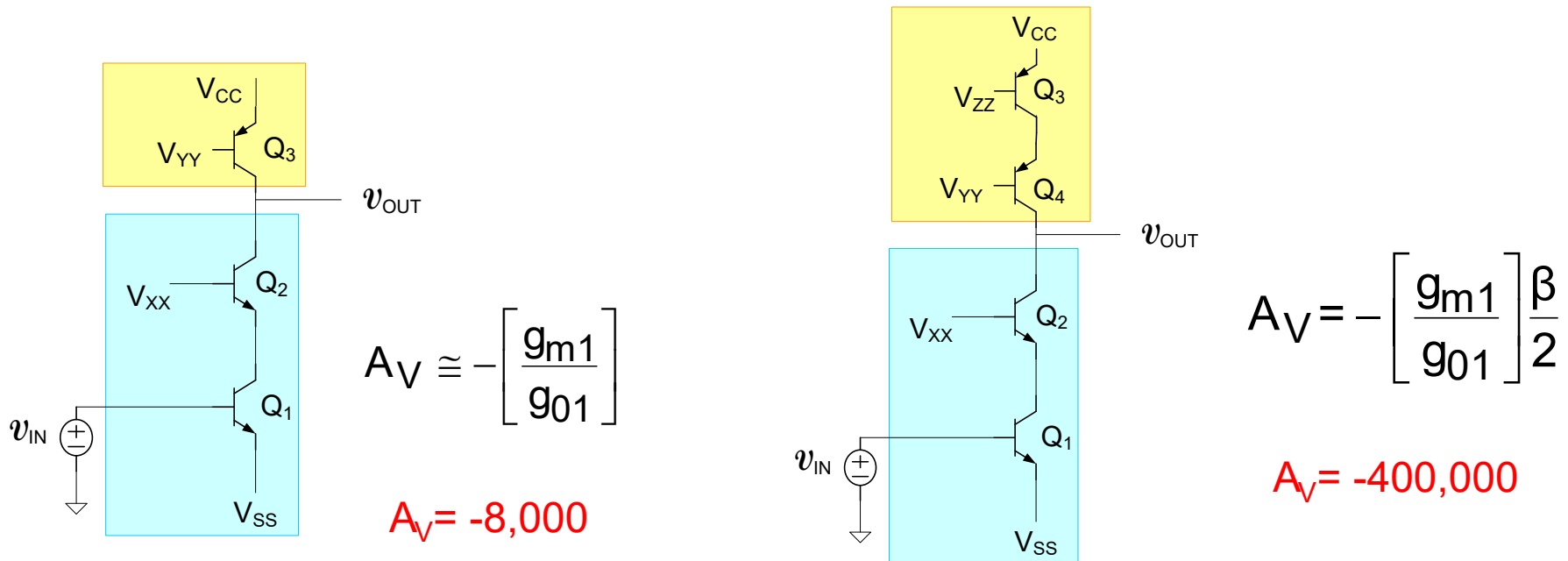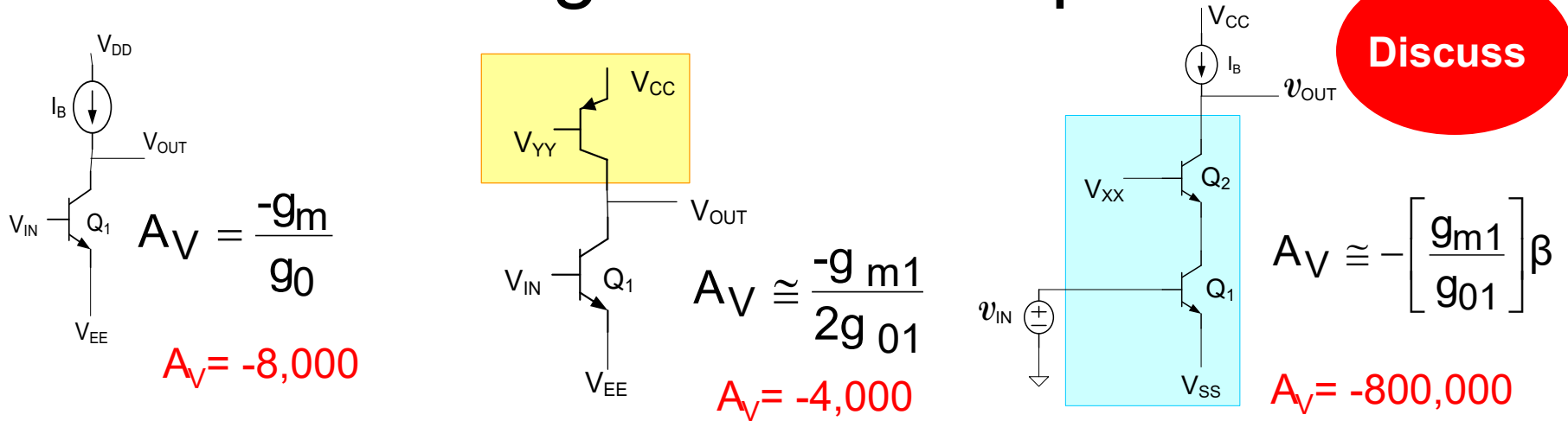

Can we use more cascoding to further increase the gain?

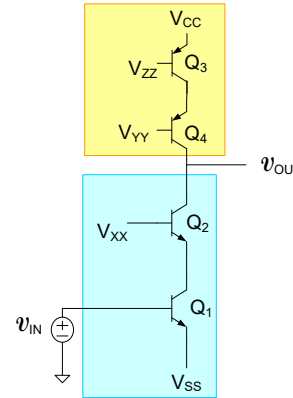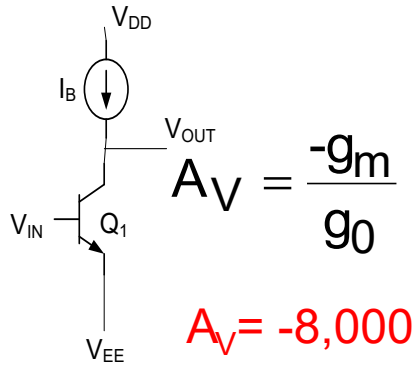
High Gain Amplifiers Seldom Used Open Loop



$$A_V = - \left[\frac{g_{m1}}{g_{o1}} \right] \frac{\beta}{2}$$

$A_V = -400,000$

Discuss

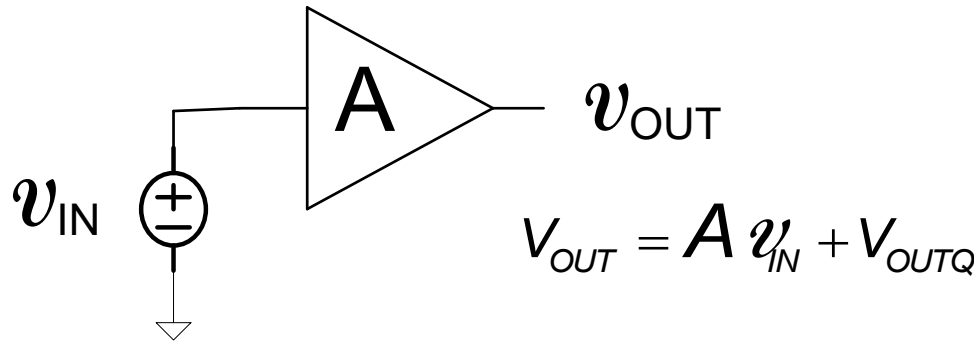


If $A_V = -400,000$ and v_{IN} increases by 1mV, what would happen at the output?

v_{OUT} would decrease by $400,000 \times 1\text{mV} = -400\text{V}$

The Cascode Amplifier (consider n-ch MOS version)

Discuss

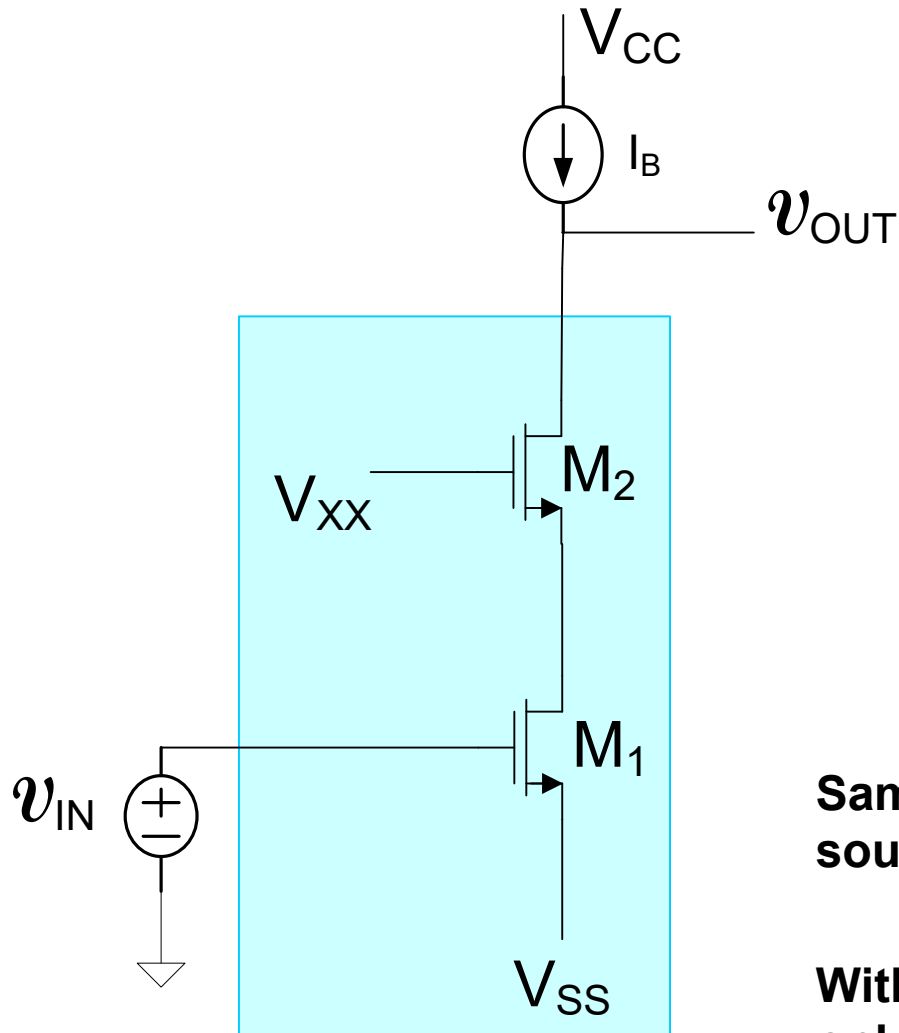

$$A_{V_{CC}} \cong - \left[\frac{g_{m1} g_{m2}}{g_{o1} g_{o2}} \right]$$


$$g_{o_{CC}} \cong \left[\frac{g_{o1} g_{o2}}{g_{m2}} \right]$$

Same issues for biasing with current source as for BJT case


With cascode current source for I_B , gain only drops by a factor of 2 from value with ideal current source

The Cascode Amplifier (consider n-ch MOS version)


Discuss

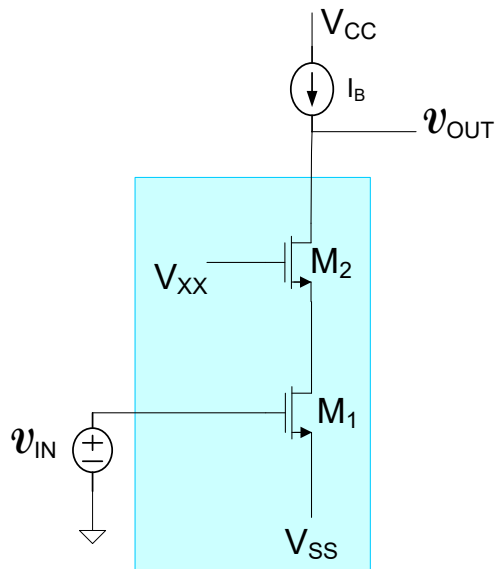
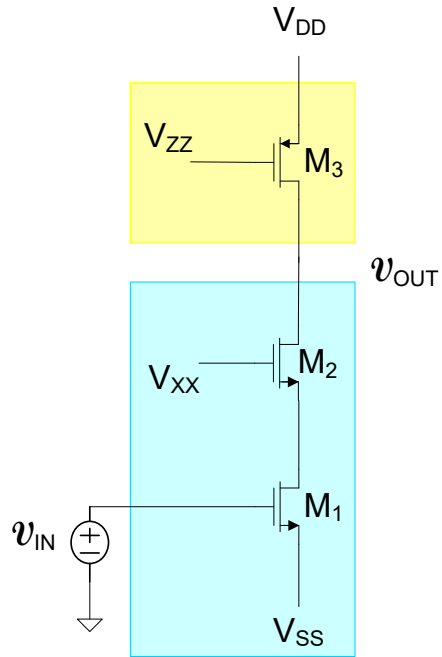
$$A_{VCC} \cong - \left[\frac{g_{m1} g_{m2}}{g_{o1} g_{o2}} \right]$$




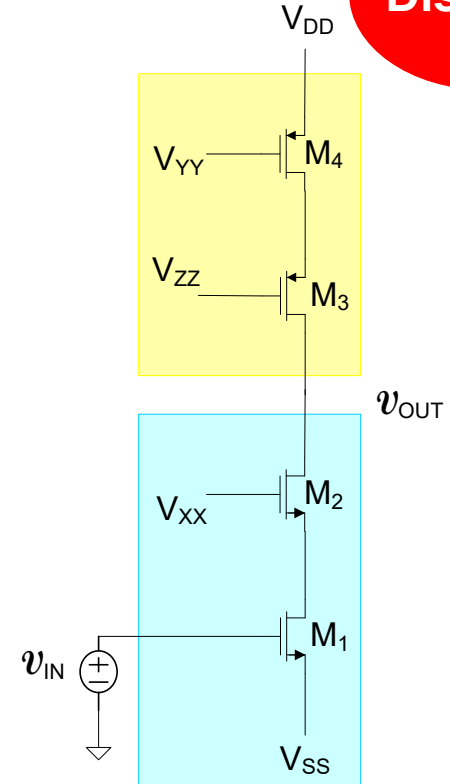
$$A_{VCC} \cong - \left[\frac{g_{m1}}{g_{o1}} \right]$$



$$A_{VCC} \cong - \frac{1}{2} \left[\frac{g_{m1} g_{m2}}{g_{o1} g_{o2}} \right]$$



Current Source Summary (BJT)

Basic

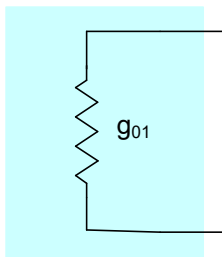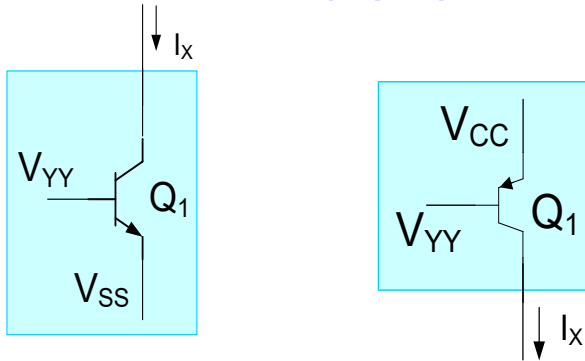


$$g_0 \cong g_{01}$$

Cascode



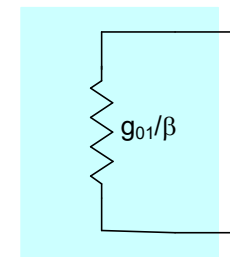
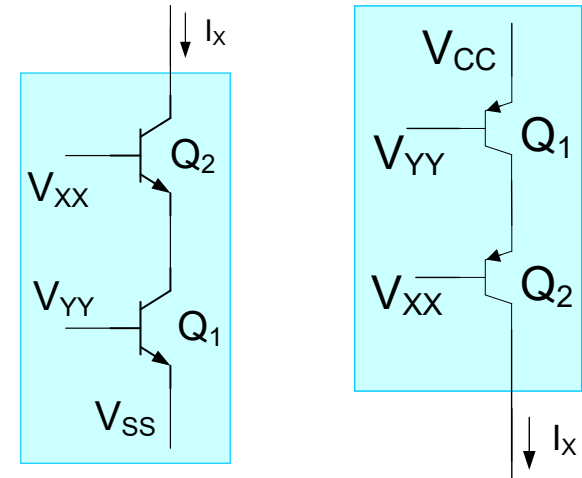


$$g_{0CC} \cong \frac{g_{01}}{\beta}$$

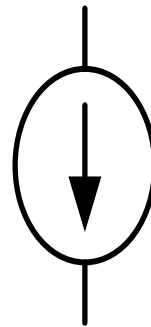




Current Source Summary (MOS)

Basic

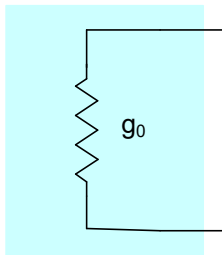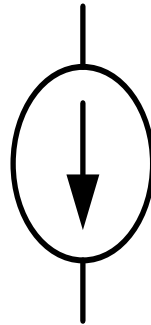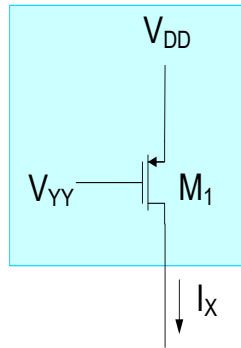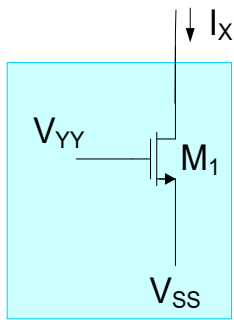


$$g_0 \cong g_{01}$$

Cascode

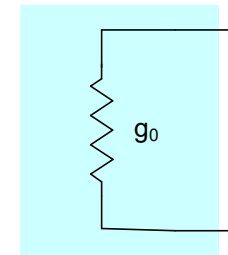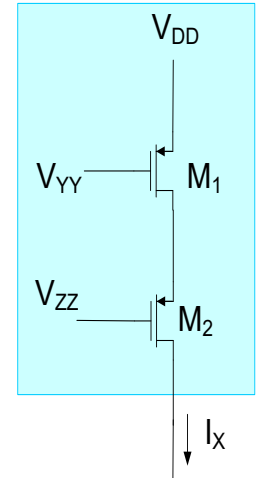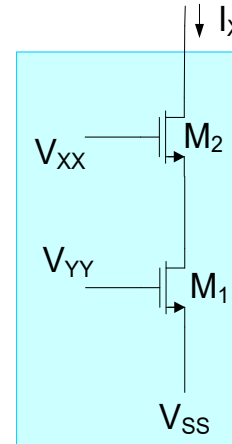


$$g_0 \cong g_{01} \frac{g_{02}}{g_{m2}}$$

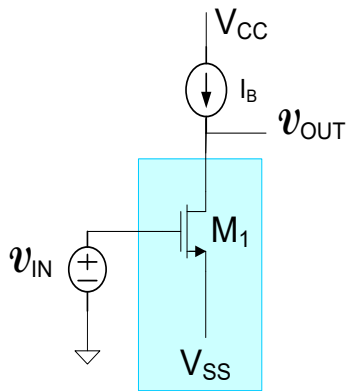
High Gain Amplifier Comparisons (n-ch MOS)



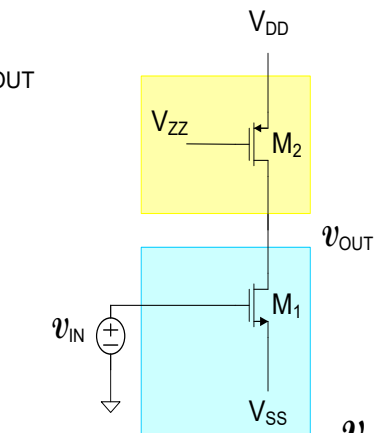
$$A_V \cong - \left[\frac{g_{m1}}{g_{o1}} \right]$$



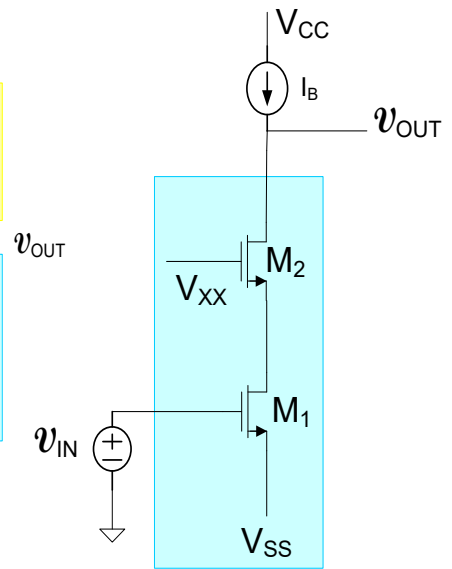
$$A_V \cong - \frac{1}{2} \left[\frac{g_{m1}}{g_{o1}} \right]$$


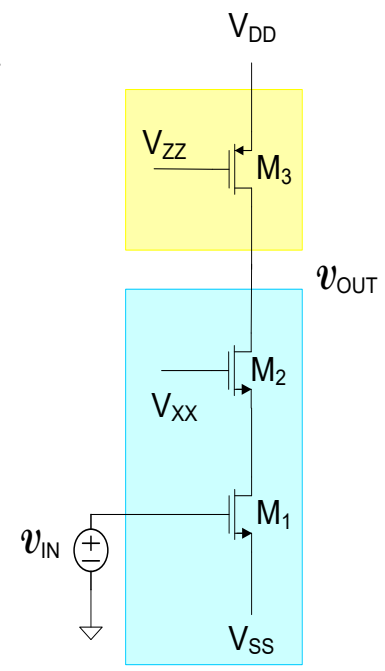
$$A_{VCC} \cong - \left[\frac{g_{m1}g_{m2}}{g_{o1}g_{o2}} \right]$$







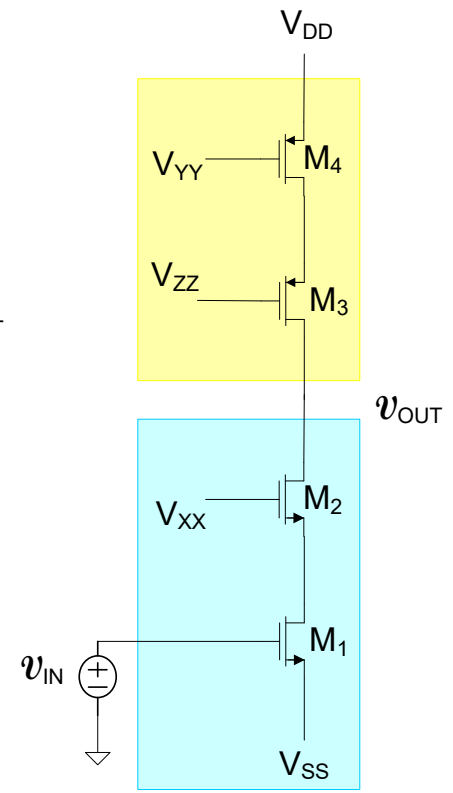
$$A_{VCC} \cong - \left[\frac{g_{m1}}{g_{o1}} \right]$$



$$A_{VCC} \cong - \frac{1}{2} \left[\frac{g_{m1}g_{m2}}{g_{o1}g_{o2}} \right]$$

High Gain Amplifier Comparisons (BJT)

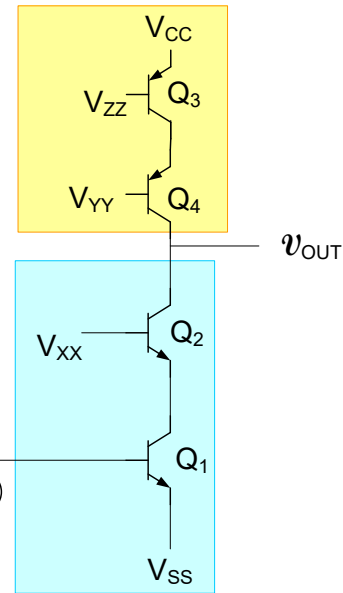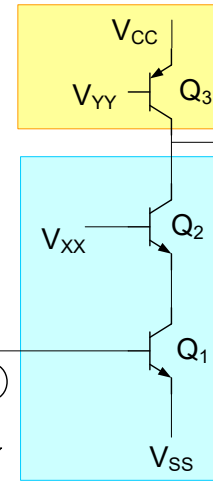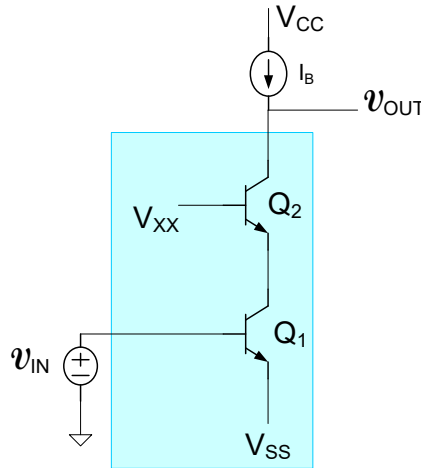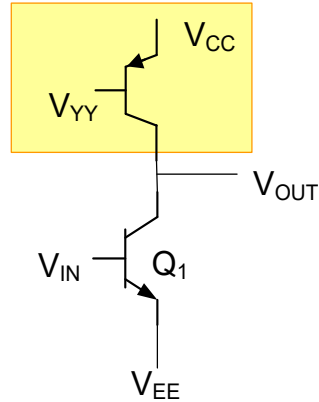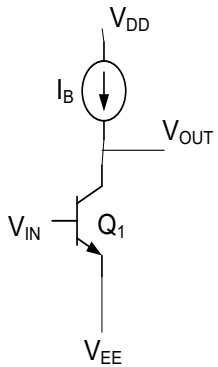

$$A_V = \frac{-g_m}{g_0}$$

$$A_V \cong -\frac{1}{2} \frac{g_{m1}}{g_{01}}$$

$$A_V \cong -\left[\frac{g_{m1}}{g_{01}} \right] \beta$$

$$A_V \cong -\left[\frac{g_{m1}}{g_{01}} \right]$$

$$A_V = -\left[\frac{g_{m1}}{g_{01}} \right] \frac{\beta}{2}$$

- Single-ended high-gain amplifiers inherently difficult to bias (because of the high gain)
- Biasing becomes practical when used in differential applications
- These structures are widely used but usually with differential inputs



Stay Safe and Stay Healthy !

End of Lecture 34