

EE 330

Lecture 34

- High Gain Amplifiers
- Cascode and Cascade Configurations

Exam Schedule

Exam 2 will be given on Friday March 11

Exam 3 will be given on Friday April 15

Review Session for Exam 3 6:00 p.m. this evening Rm 1011 Coover




Photo courtesy of the director of the National Institute of Health (NIH)



As a courtesy to fellow classmates, TAs, and the instructor

Wearing of masks during lectures and in the laboratories for this course would be appreciated irrespective of vaccination status

High-gain amplifier

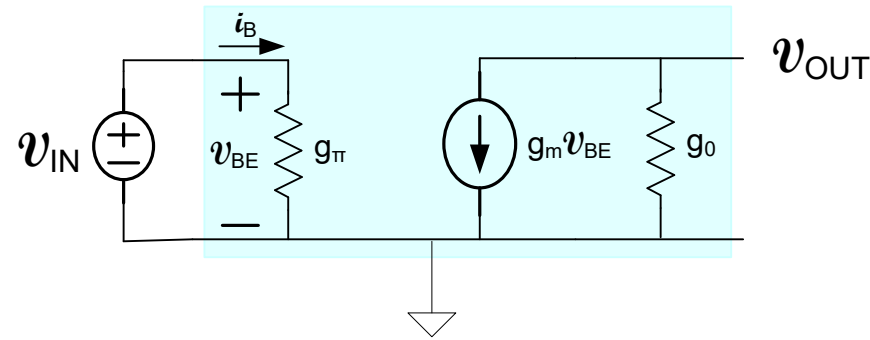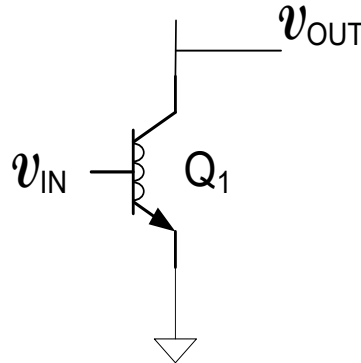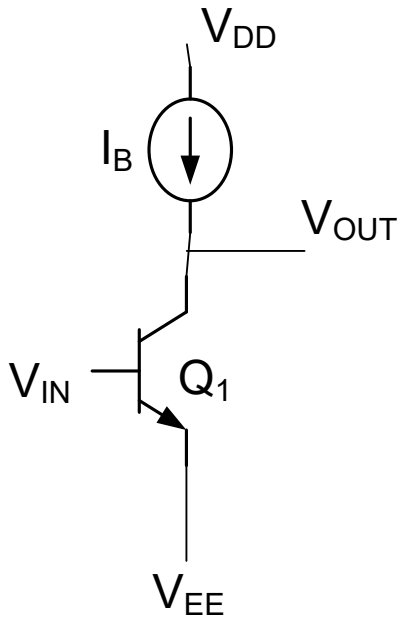

$$A_V = \frac{-g_m}{g_o}$$

$$A_V = \frac{-I_{CQ}}{V_t I_{CQ} / V_{AF}} = -\frac{V_{AF}}{V_t}$$

$$A_V = -\frac{V_{AF}}{V_t} \cong \frac{200V}{25mV} = -8000$$


This gain is very large (but realistic) !

And no design parameters affect the gain



But how can we make a current source?

Simple Current Sources

a “sinking” current source

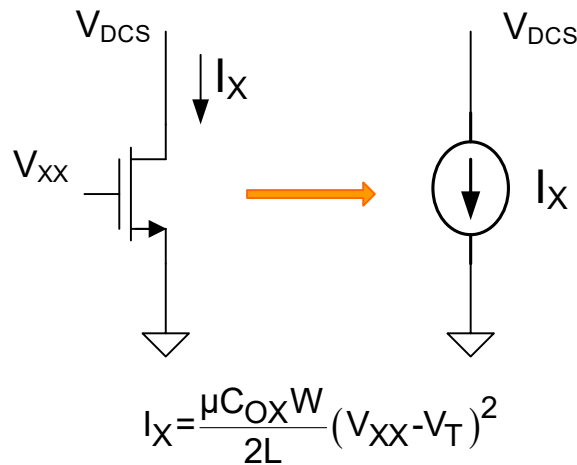
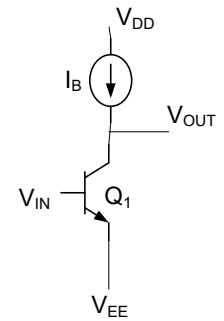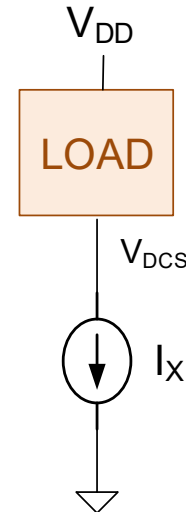
$$I_X = \frac{\mu C_{OX} W}{2L} (V_{XX} - V_T)^2$$



Since I_X is independent of V_{DCS} , acts as an ideal current source (with this model)

Termed a “sinking” current source since current is pulled out of the load

If V_{XX} is available, each dc current source requires only one additional transistor !


Have several methods for generating V_{XX} from V_{DD} (see HW problems)

But for the npn high-gain amplifier considered need a sourcing current


But how good is this current “sink”?

Simple Current Sources

a “sourcing” current source

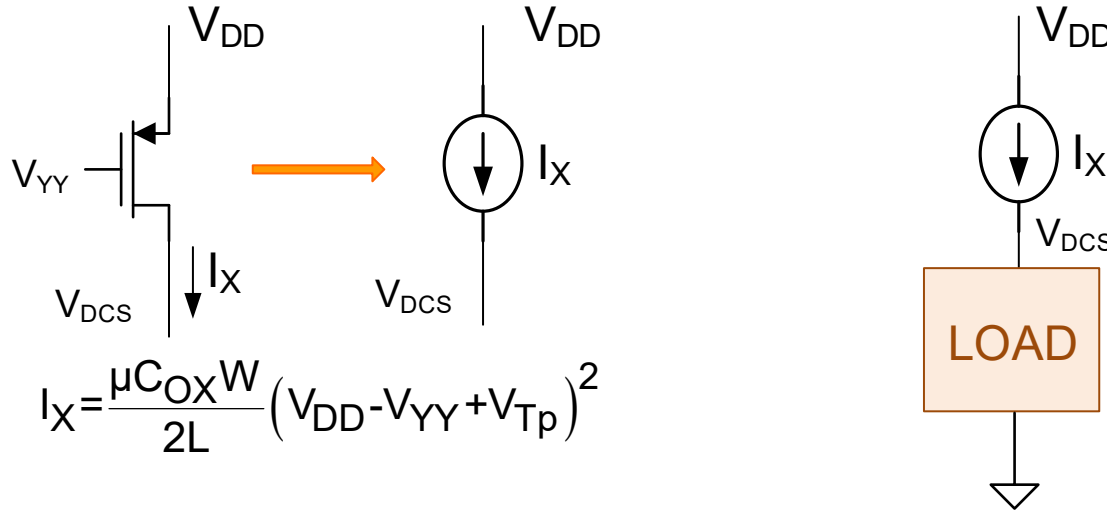
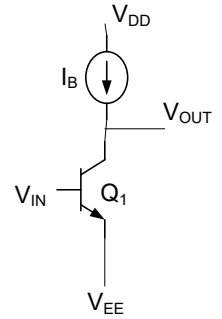
$$I_X = \frac{\mu C_{OX} W}{2L} (V_{DD} - V_{YY} + V_{Tp})^2$$



Since I_X is independent of V_{DCS} , acts as an ideal current source (with this model)


Termed a “sourcing” current source since pushed into the load

If V_{YY} is available, each dc current source requires only one additional transistor !

Have several methods for generating V_{YY} from V_{DD} (see HW problems)

But how good is this current “source”?


Current Sources/Mirrors

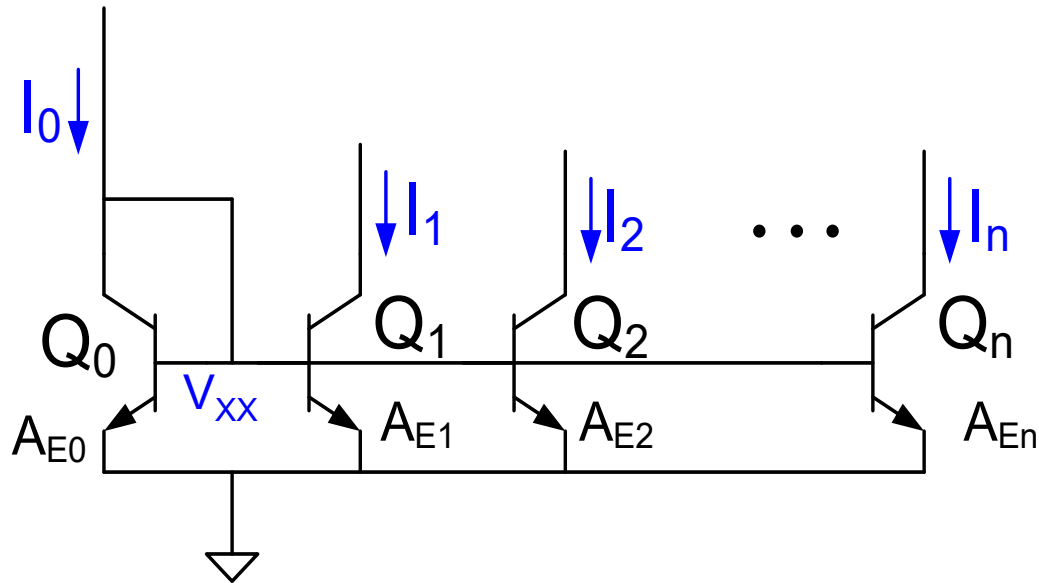

Multiple-Output Bipolar Current Sink

$$I_k = \left[\frac{A_{Ek}}{A_{E0}} \right] I_0$$


Current Sources/Mirrors

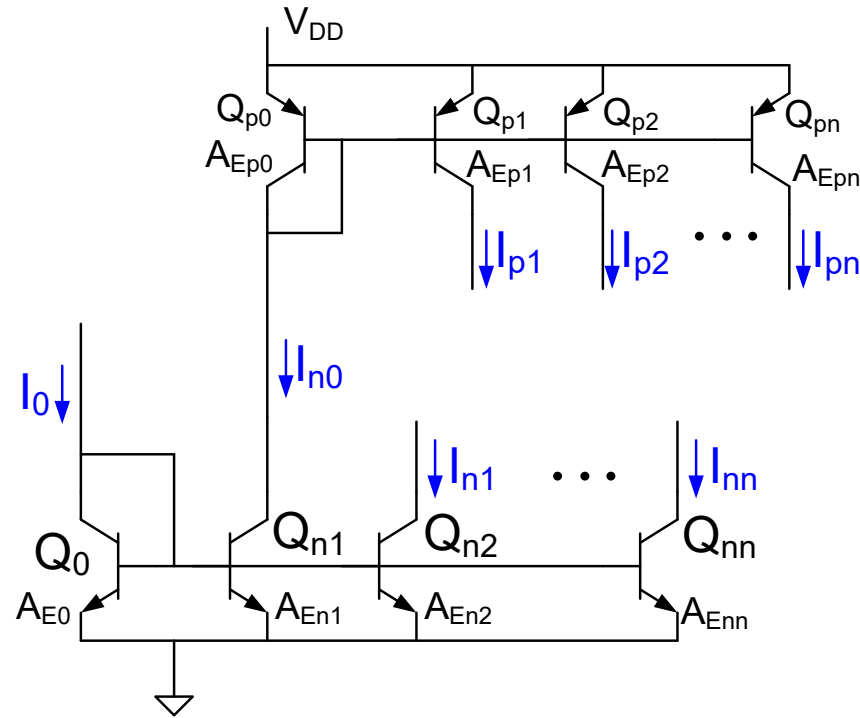

Multiple-Output Bipolar Current Source and Sink

$$I_{nk} = \left[\frac{A_{Enk}}{A_{E0}} \right] I_0 \quad I_{pk} = \left[\frac{A_{En1}}{A_{E0}} \right] \left[\frac{A_{Epk}}{A_{Ep0}} \right] I_0$$

Current Sources/Mirrors

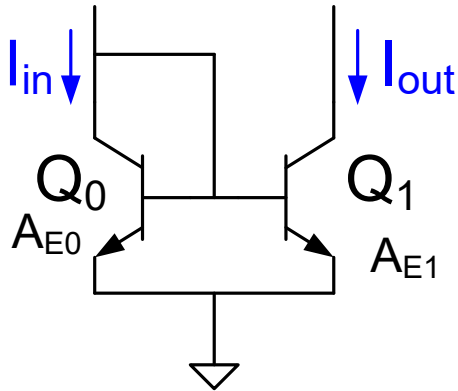


$$I_{out} = \left[\frac{A_{E1}}{A_{E0}} \right] I_{in}$$

This circuit is termed a “current mirror”

Will re-derive the transfer characteristics of the current mirror assuming I_B is small compared to I_C

$$\left. \begin{aligned} I_{IN} &= J_S A_{E0} e^{\frac{V_{BE}}{V_t}} \\ I_{OUT} &= J_S A_{E1} e^{\frac{V_{BE}}{V_t}} \end{aligned} \right\} \Rightarrow \frac{I_{OUT}}{I_{IN}} = \frac{J_S A_{E1} e^{\frac{V_{BE}}{V_t}}}{J_S A_{E0} e^{\frac{V_{BE}}{V_t}}} = \frac{A_{E1}}{A_{E0}}$$

Current Sources/Mirrors

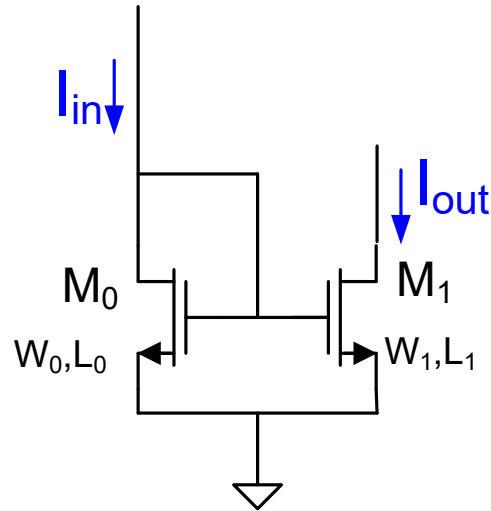

n-channel Current Mirror


$$\left. \begin{aligned} I_{in} &= \frac{\mu C_{OX} W_0}{2L_0} (V_{GS0} - V_{T0})^2 \\ I_{out} &= \frac{\mu C_{OX} W_1}{2L_1} (V_{GS1} - V_{T1})^2 \end{aligned} \right\}$$

If process parameters are matched, it follows that

$$I_{out} = \left[\frac{W_1}{W_0} \frac{L_0}{L_1} \right] I_{in}$$

- Current mirror gain can be accurately controlled !
- Layout is important to get accurate gain (for both MOS and BJT)


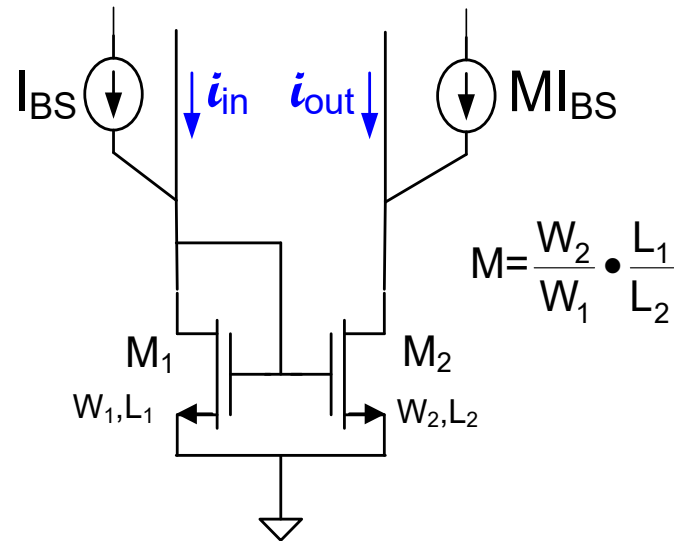
n-channel current mirror current amplifier



$$i_{\text{out}} = \left[\frac{W_2}{W_1} \frac{L_1}{L_2} \right] i_{\text{in}}$$

Amplifies both positive and negative currents


Current Sources/Mirrors

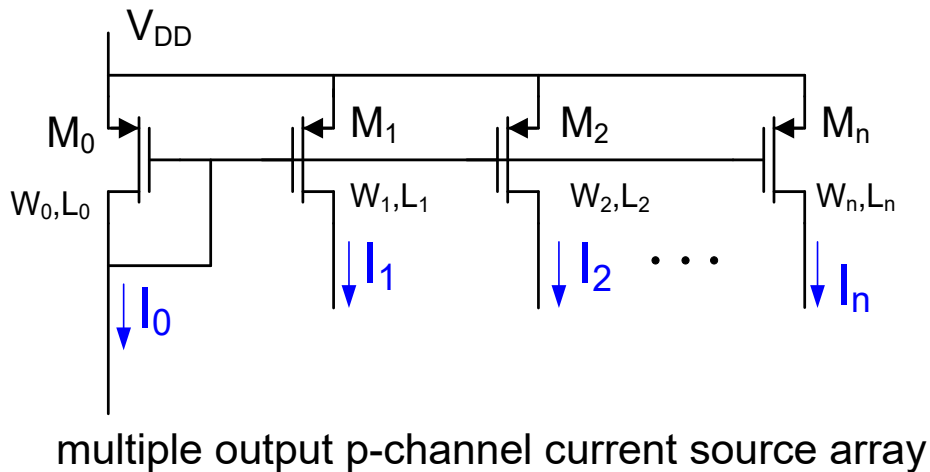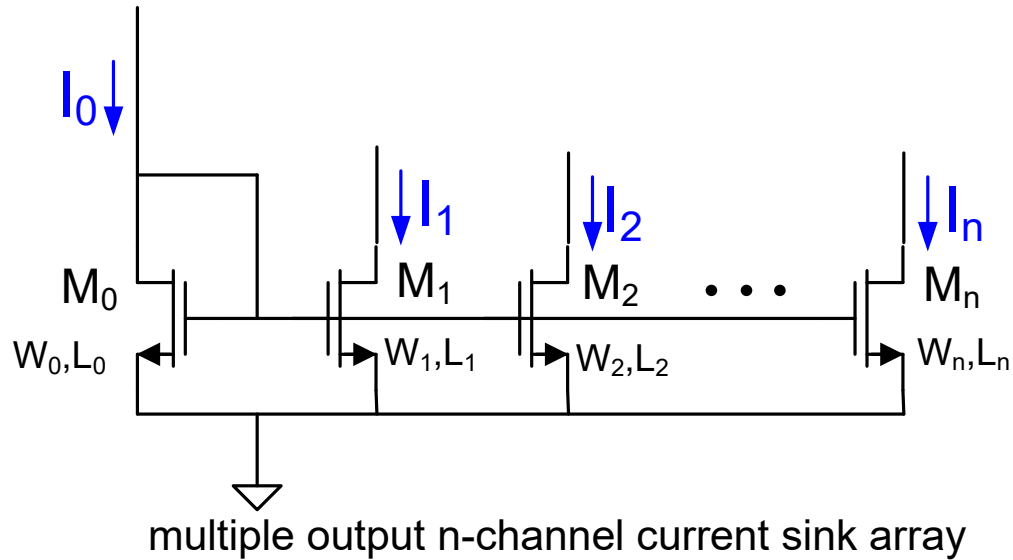

$$I_k = \left[\frac{W_k L_0}{W_0 L_k} \right] I_0$$

Current Sources/Mirrors

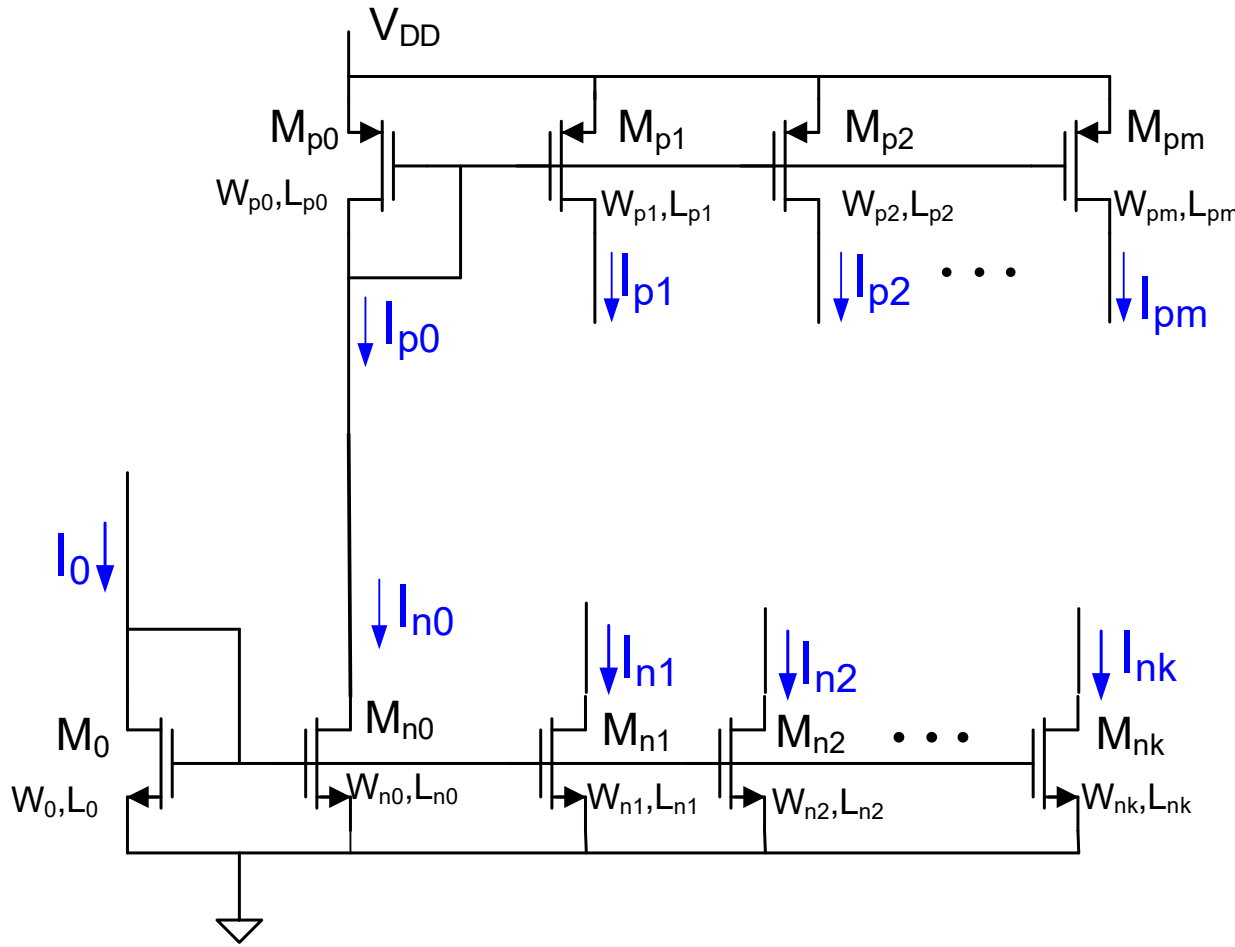multiple sourcing and sinking current outputs




$$I_{pj} = \left[\frac{W_{pj}}{L_{pj}} \cdot \frac{L_{p0}}{W_{p0}} \right] M I_0$$

$$M = \left[\frac{W_{n0}}{L_{n0j}} \cdot \frac{L_0}{W_0} \right]$$

$$I_{nj} = \left[\frac{W_{nj}}{L_{nj}} \cdot \frac{L_0}{W_0} \right] I_0$$


m and k may be different
Often M=1

Current Sources/Mirrors Summary

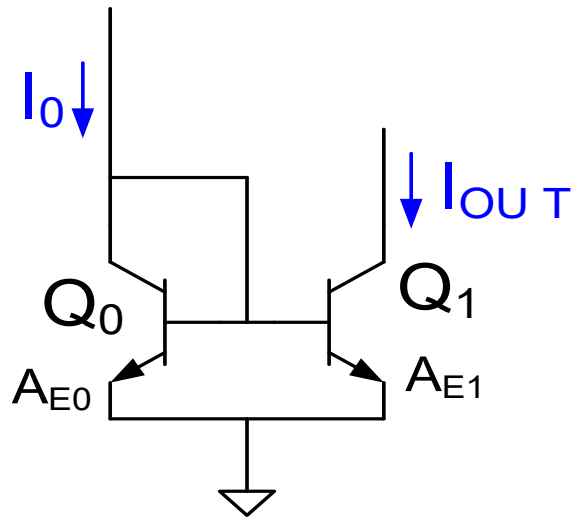

npn Current Mirror
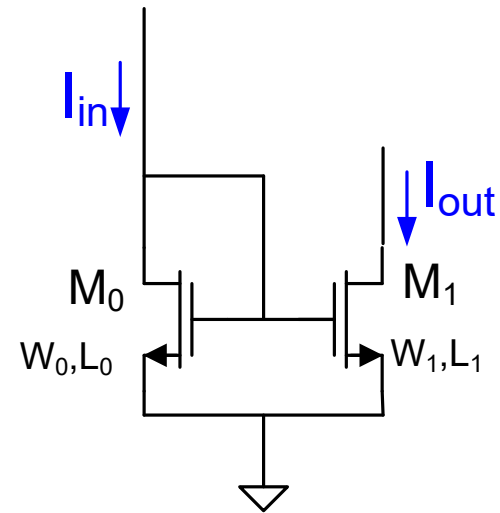
$$I_{out} = \left[\frac{A_{E1}}{A_{E0}} \right] I_{in}$$




n-channel Current Mirror


$$I_{out} = \left[\frac{W_1}{W_0} \frac{L_0}{L_1} \right] I_{in}$$

- Current mirror gain can be accurately controlled !
- Layout is important to get accurate gain (for both MOS and BJT)

Layout of Current Mirrors

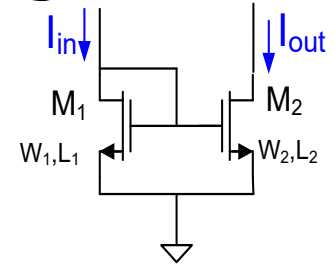


Example with $M = 2$

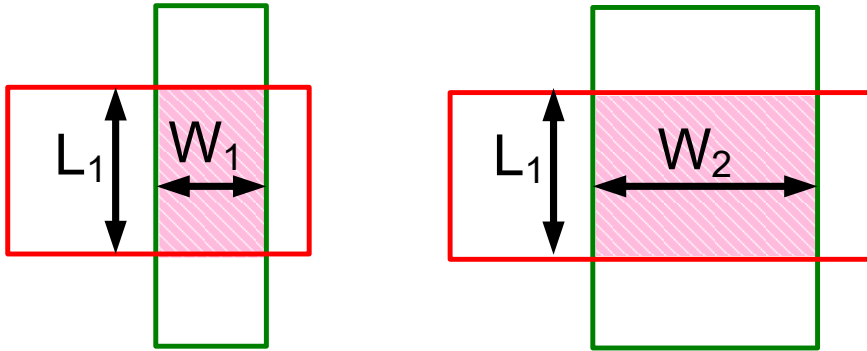

Standard layout
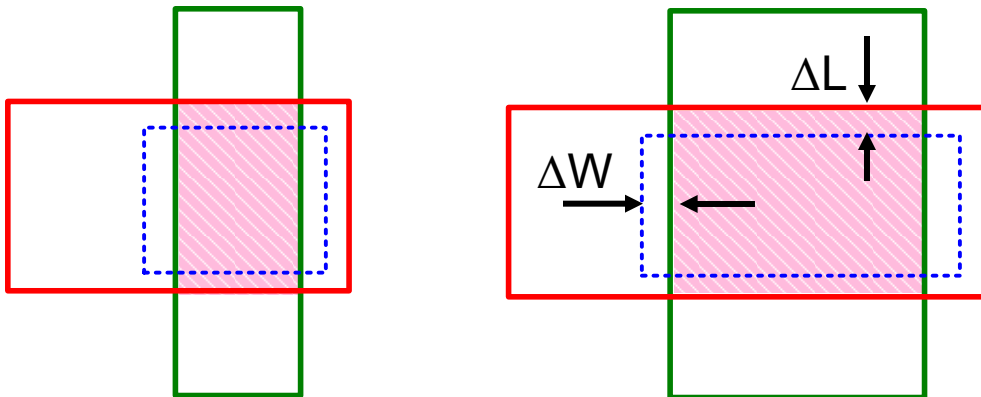
$$M = \left[\frac{W_2}{W_1} \frac{L_1}{L_2} \right]$$



Gate area after fabrication depicted




$$M = \left[\frac{W_2 + 2\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_2 + 2\Delta L} \right]$$

$$M = \left[\frac{2W_1 + 2\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] \neq 2$$

Layout of Current Mirrors


Example with $M = 2$

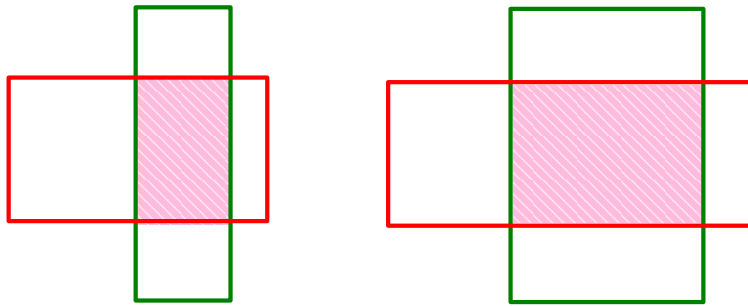

Standard layout

$$M = \left[\frac{W_2}{W_1} \frac{L_1}{L_2} \right]$$
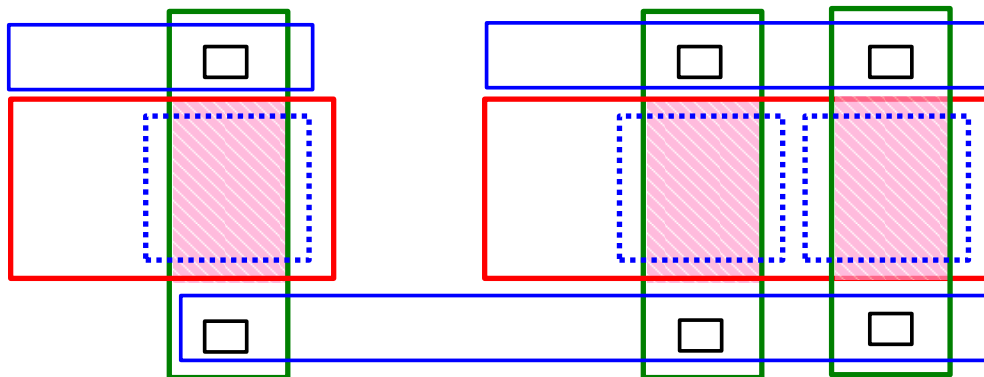
$$M = \left[\frac{2W_1 + 2\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] \neq 2$$






Better Layout

$$M = \left[\frac{2W_1 + 4\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] = 2$$


Centroid and Common Centroid

✕ Denotes Geometric Centroid

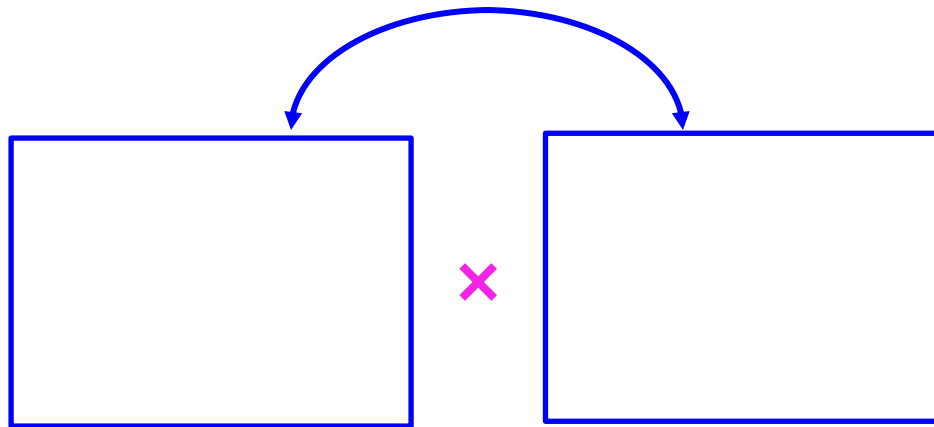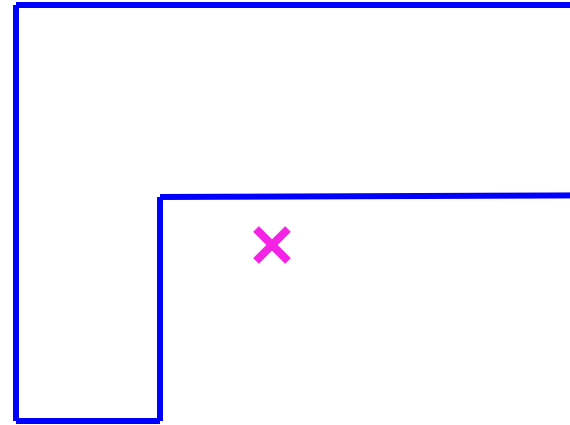 


Centroid and Common Centroid

Geometric Centroids of Channel

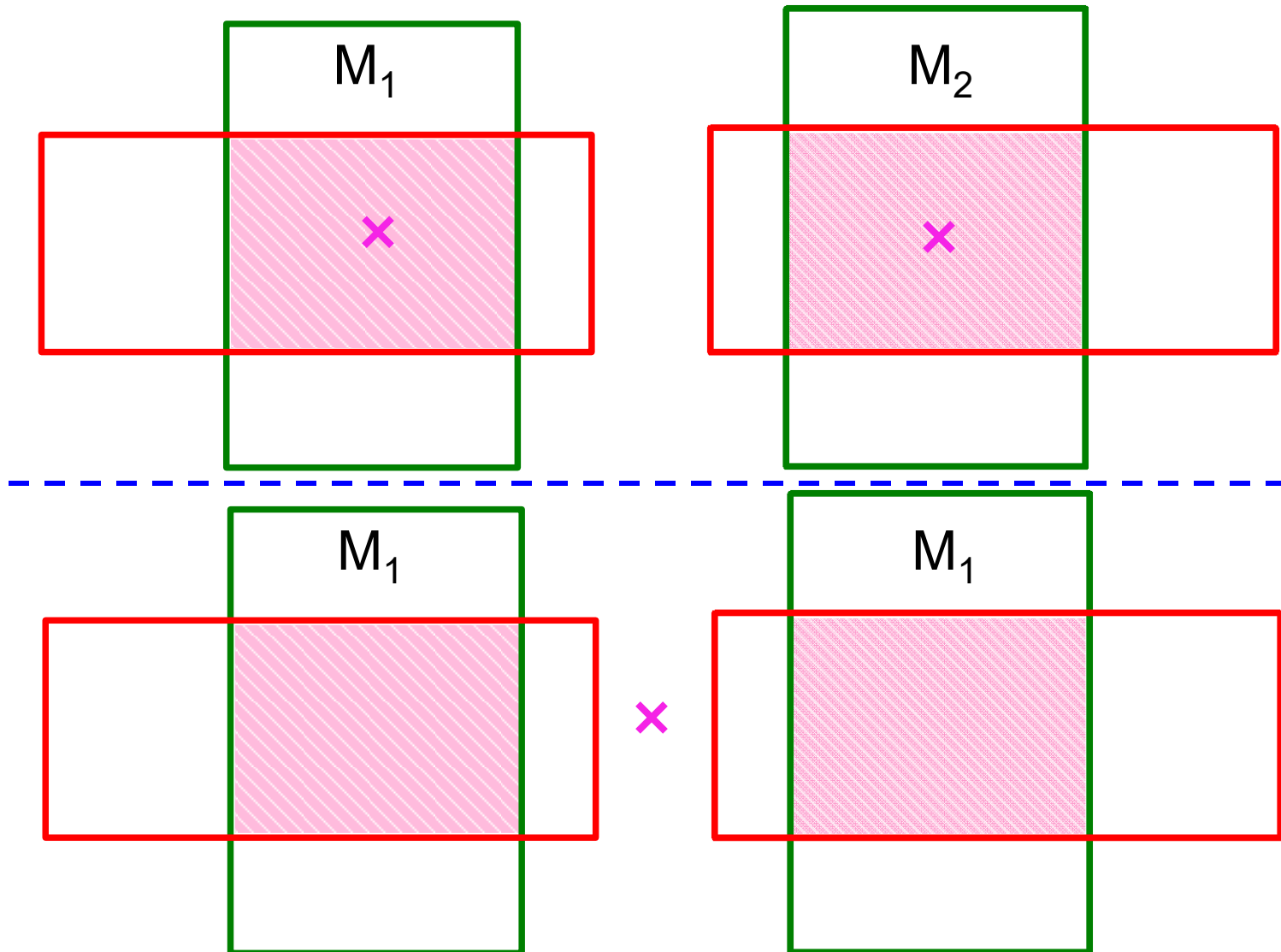


Centroid and Common Centroid

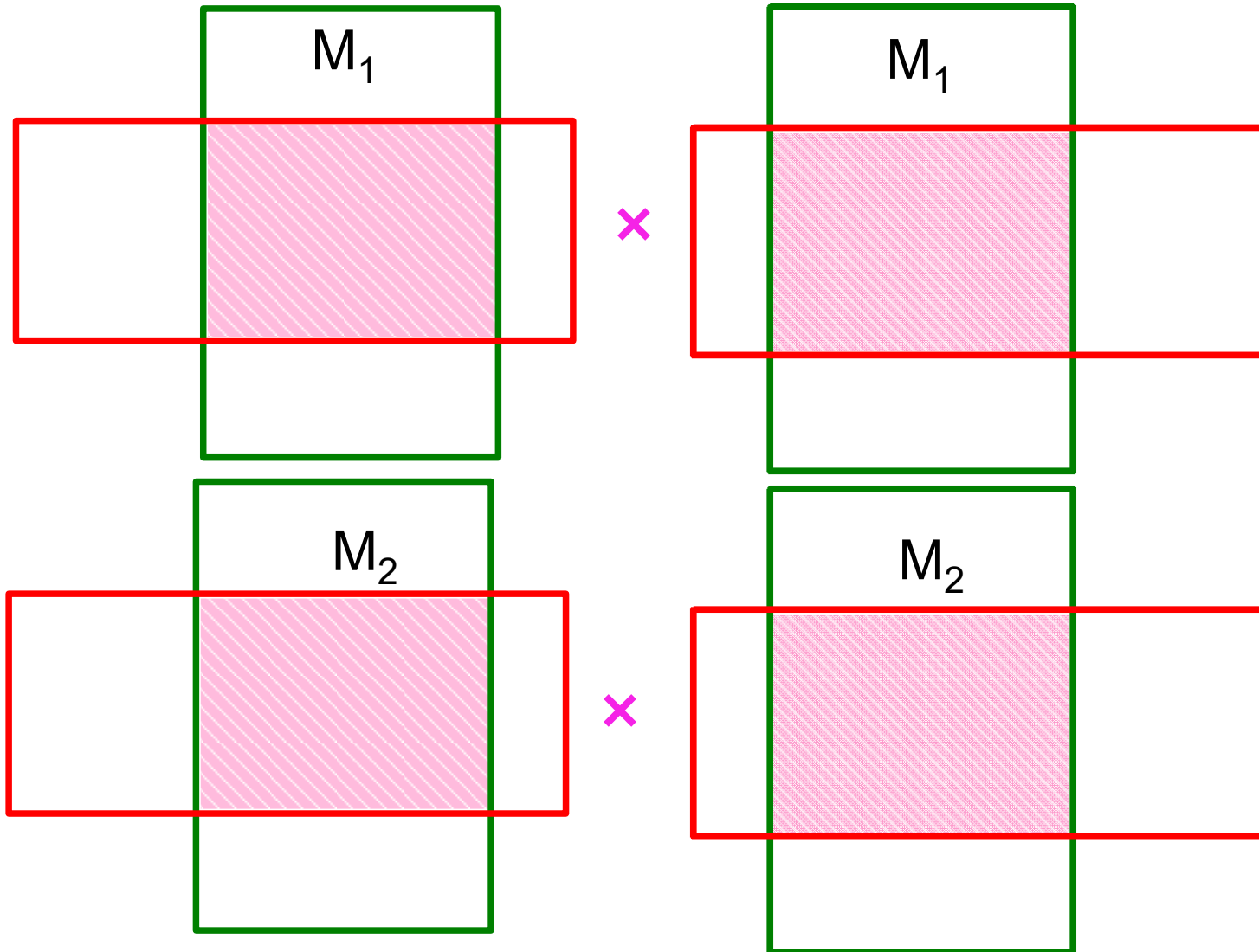


Centroid and Common Centroid

Common Centroid for Matched Devices

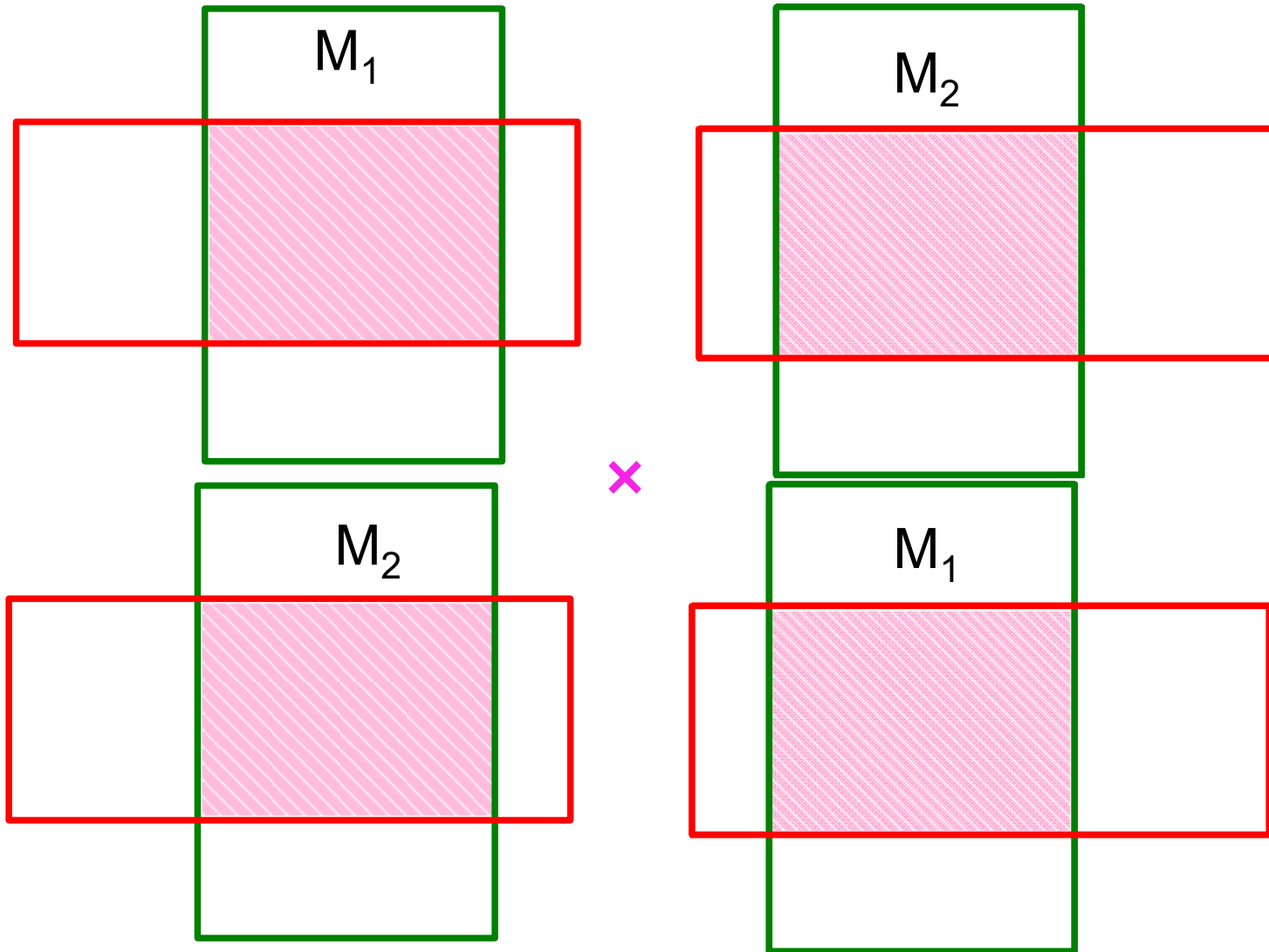


Centroid and Common Centroid

Common Centroid for Matched Devices

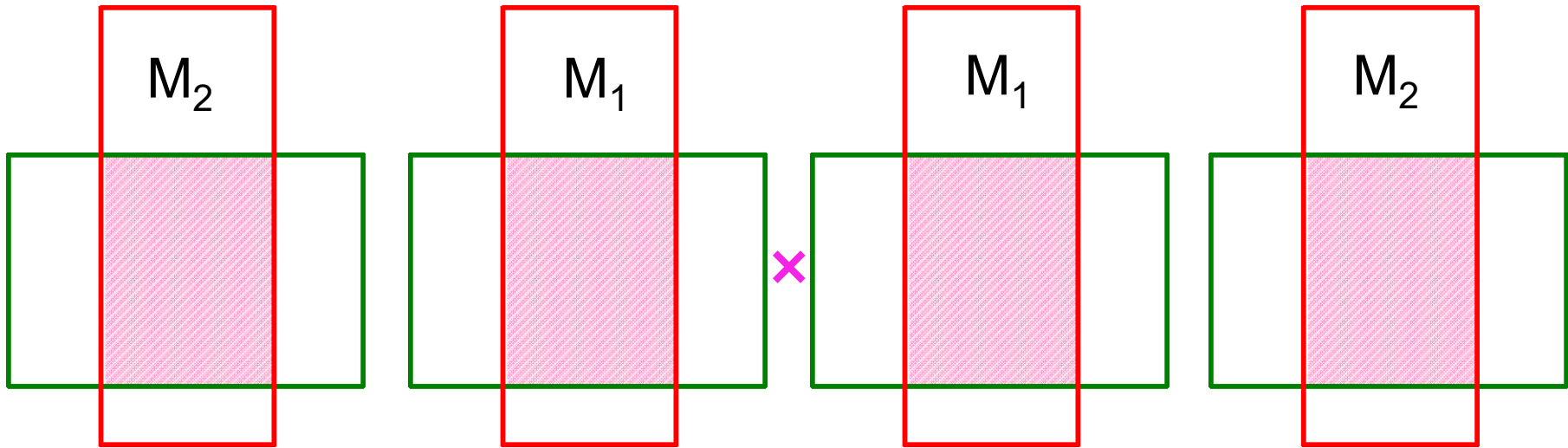


Centroid and Common Centroid

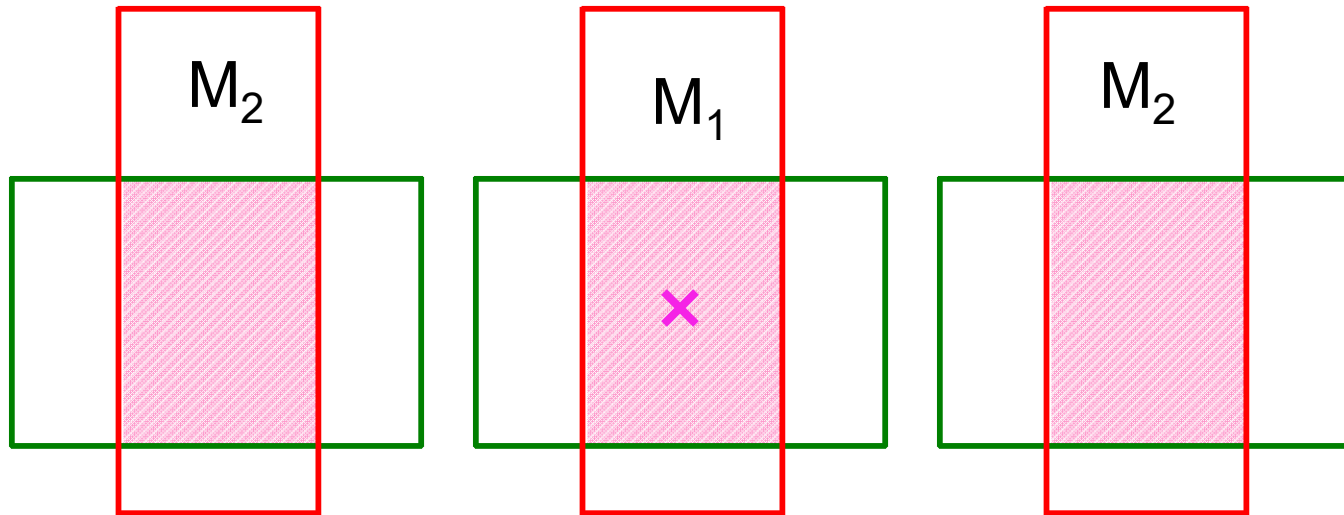Common Centroid for Ratioed Devices $M = \frac{W_2 L_1}{W_1 L_2} = 2$



Gradient

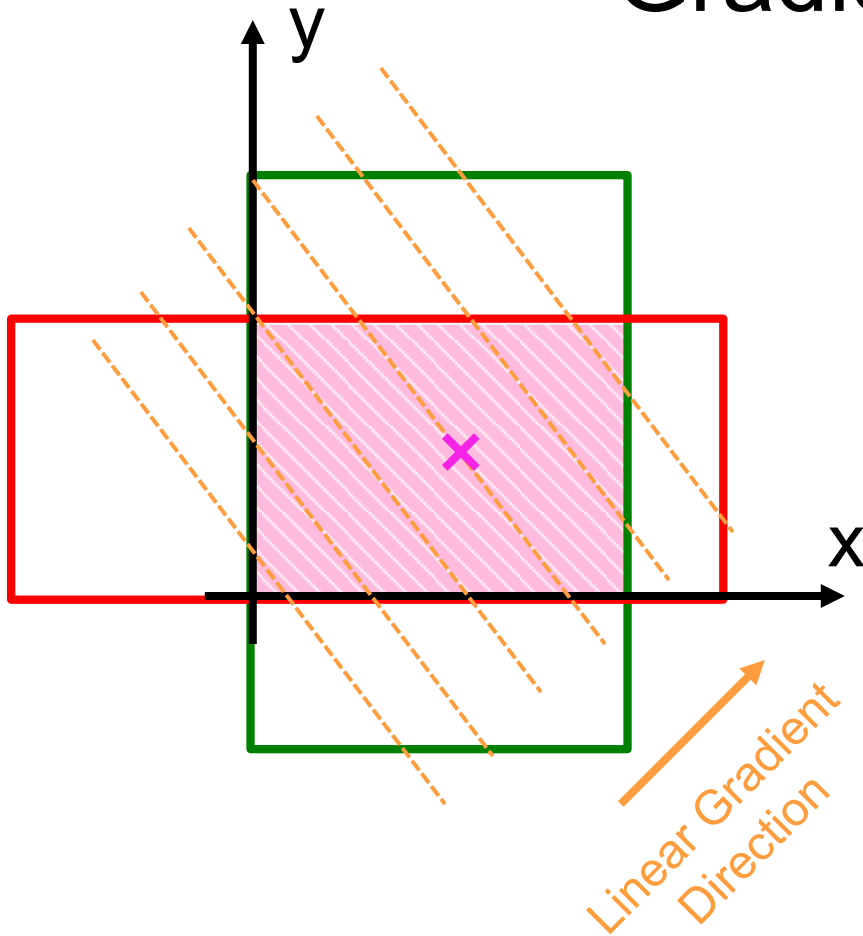

Threshold voltage
dependent upon position

$$V_{TH}(x,y)$$


- Significant changes in threshold voltage can occur due to gradient effects
- This can seriously degrade matching in matching-critical circuits

- If the threshold voltage of a transistor changes with position, it can be reasonably accurately modeled with an “equivalent” threshold voltage
- For linear gradient, $V_{THEQ} = V_{TH}(X_C, Y_C)$

$$\times : (X_C, Y_C)$$


Layout of Current Mirrors

Example with $M = 2$

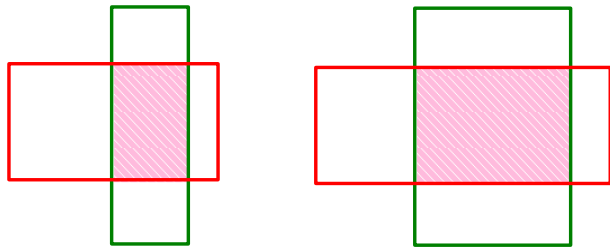


Standard layout
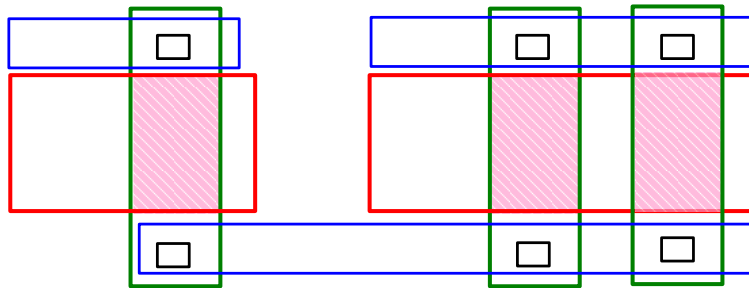
$$M = \left[\frac{W_2}{W_1} \frac{L_1}{L_2} \right]$$



Better Layout
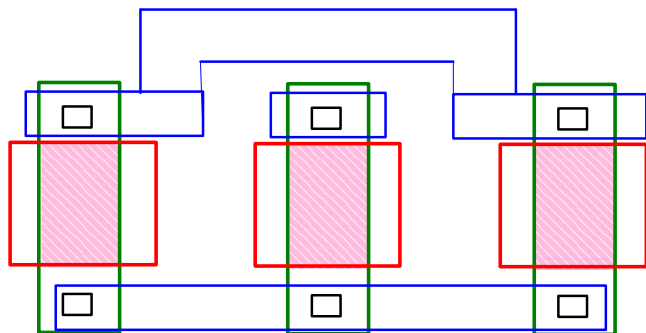
$$M = \left[\frac{2W_1 + 4\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] = 2$$




Even Better Layout

$$M = \left[\frac{2W_1 + 4\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] = 2$$

- This is termed a common-centroid layout
- Linear gradient mismatch eliminated with common-centroid layout !

High-gain amplifier

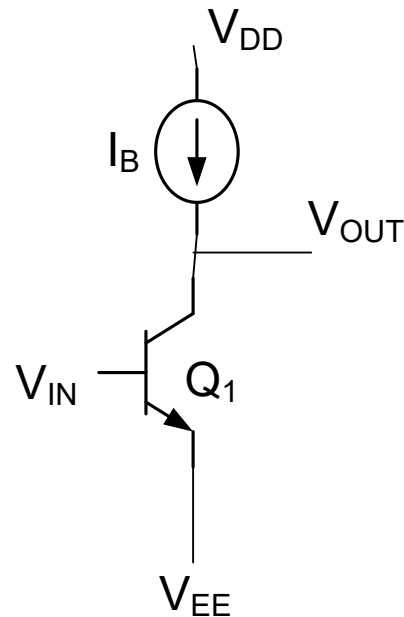


$$A_V \cong -8000$$

Why are we interested in high-gain amplifiers?

- High gain amplifiers typically have some very undesirable properties
Nonlinear, gain highly dependent upon process variations and temperature, frequency response poor, noisy,
- So we can build feedback amplifiers !!

High-gain amplifier

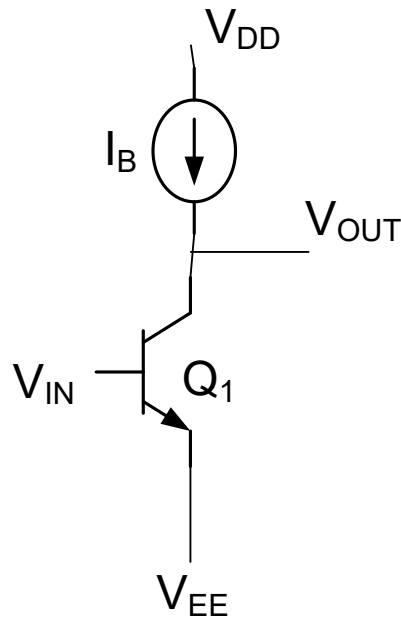


$$A_V \cong -8000$$

→ How can we build the current source?


What is the small-signal model of an actual current source?

Basic Current Sources and Sinks

Bipolar Mirror-Based Current Sink

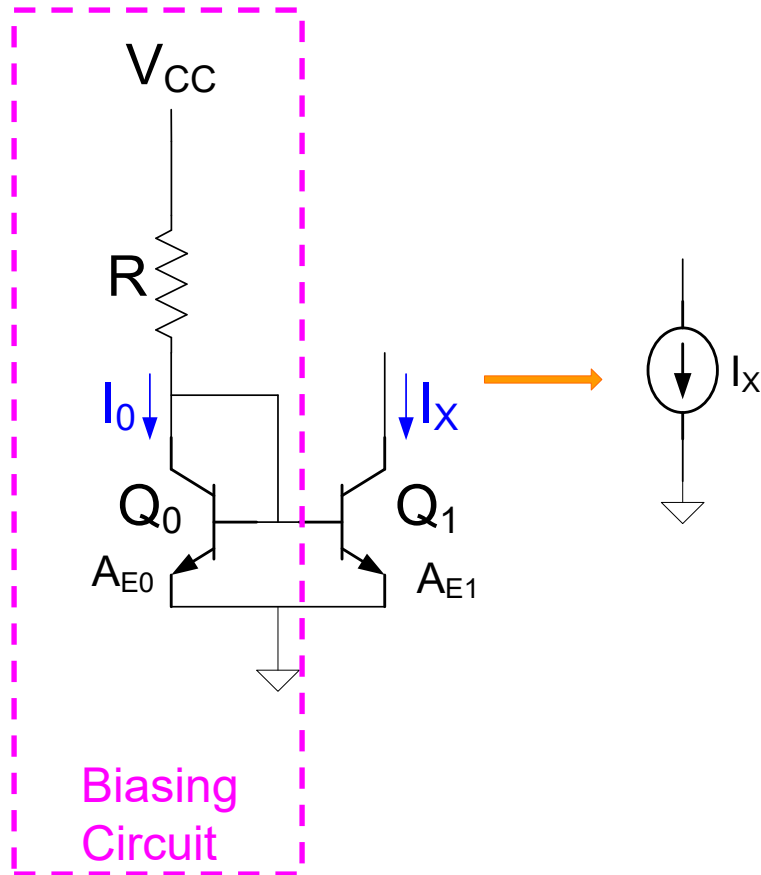


Bipolar Mirror-Based Current Source

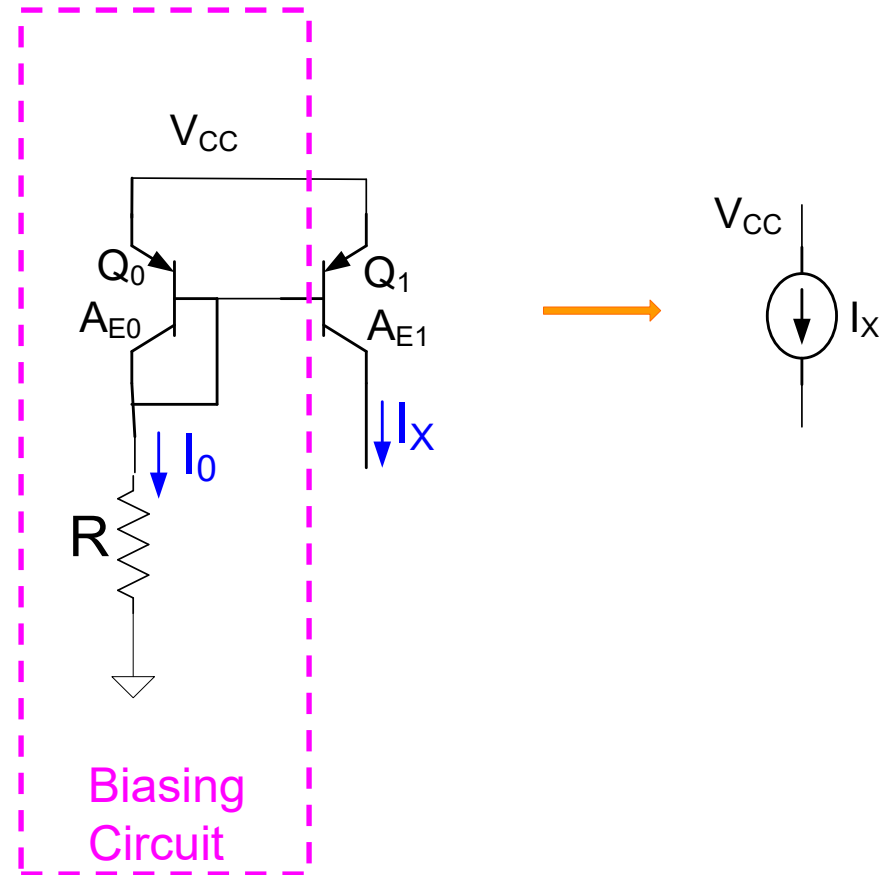

Biasing circuit uses same V_{CC} as amplifier and no other independent sources


High-gain amplifier

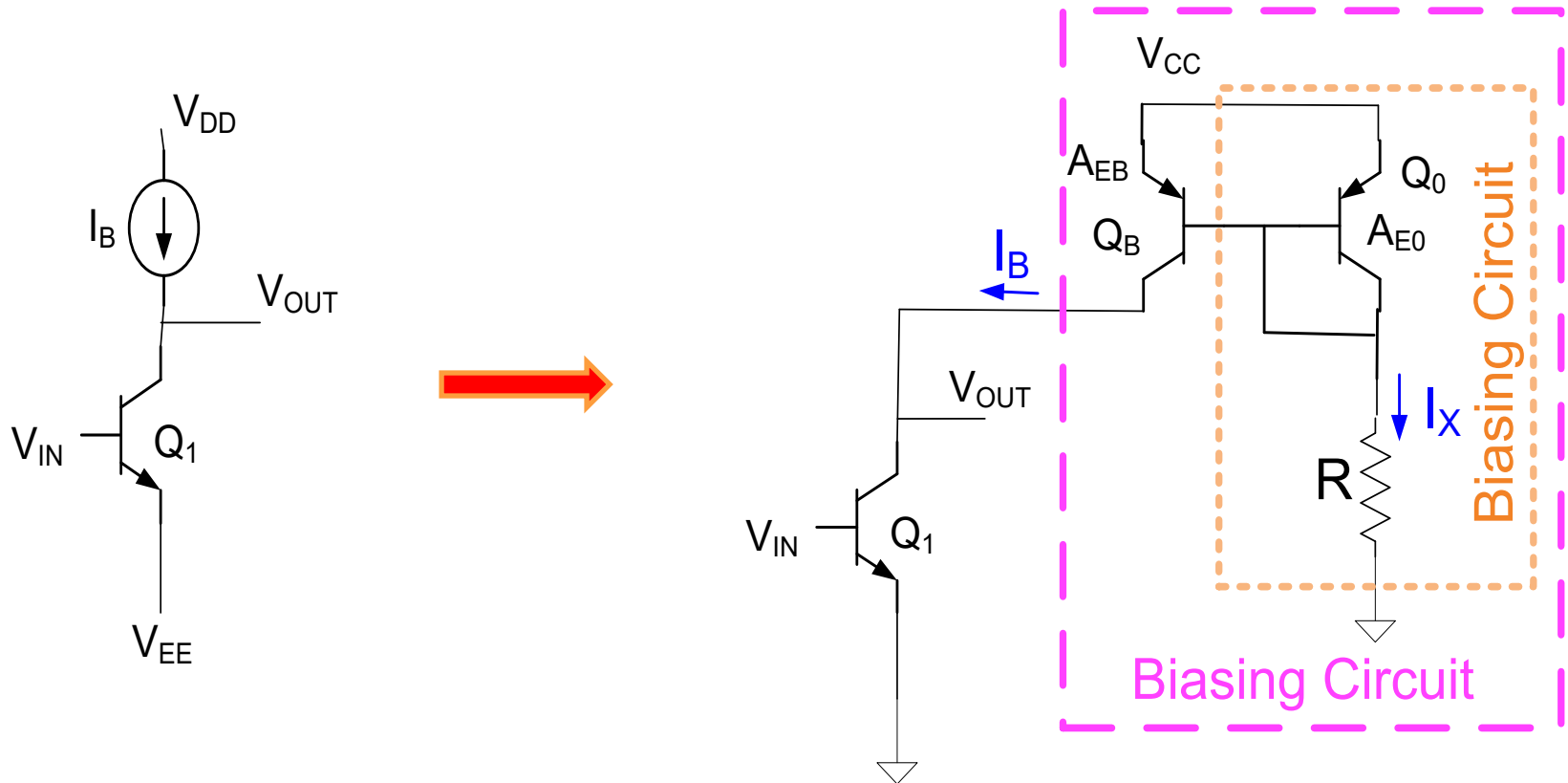


- Bias circuitry requires only a single independent dc voltage source !
- Incremental overhead is only one transistor, Q_B

Basic Current Sources and Sinks

Basic Bipolar Current Sinks

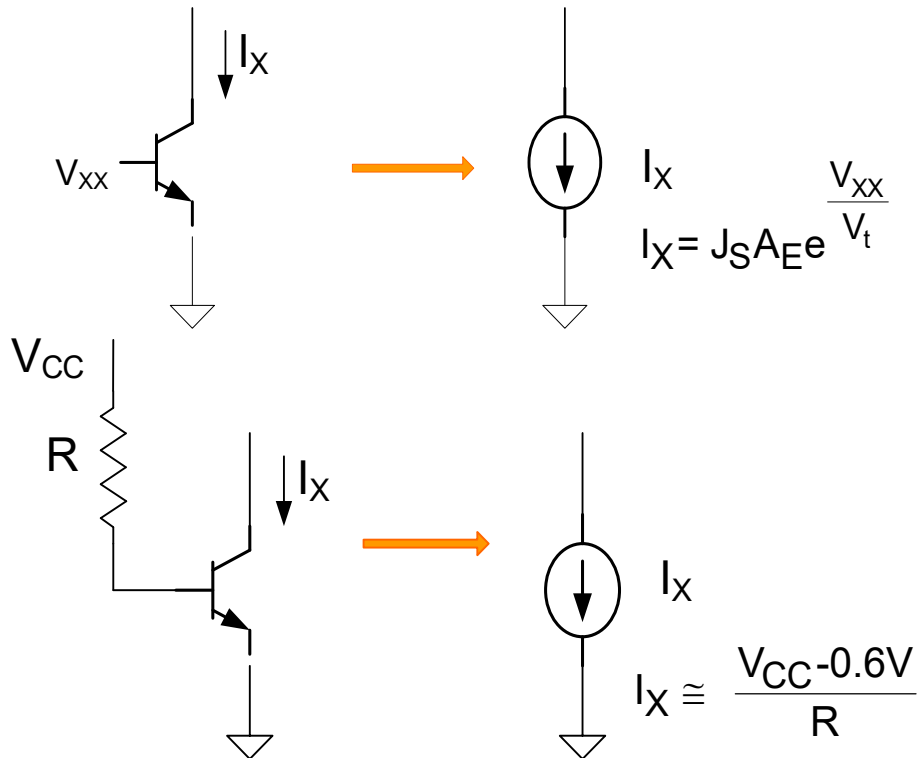


Basic Bipolar Current Sources

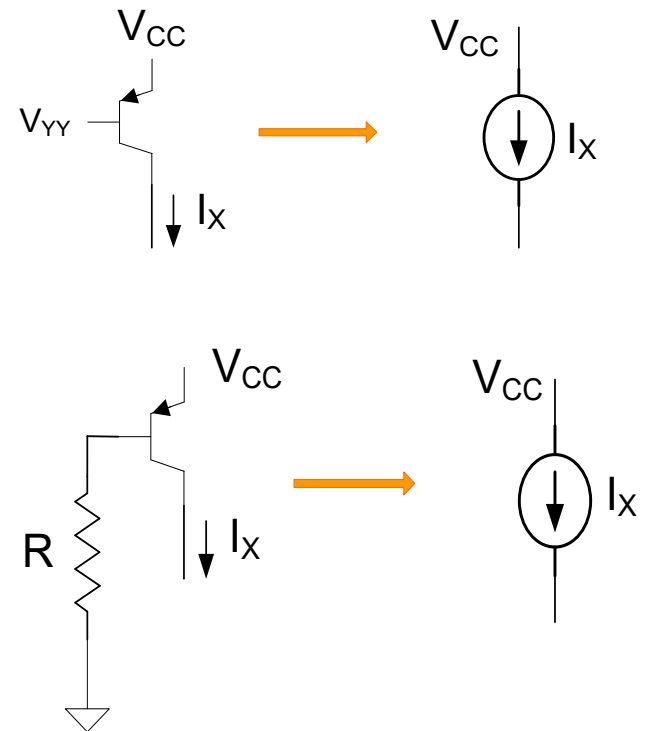

- Very practical methods for biasing the BJTs (or MOSFETs) can be used
- Current Mirrors often used for generating sourcing and sinking currents
- Can think of biasing transistors with V_{xx} and V_{yy} in these current sources

High-gain amplifier

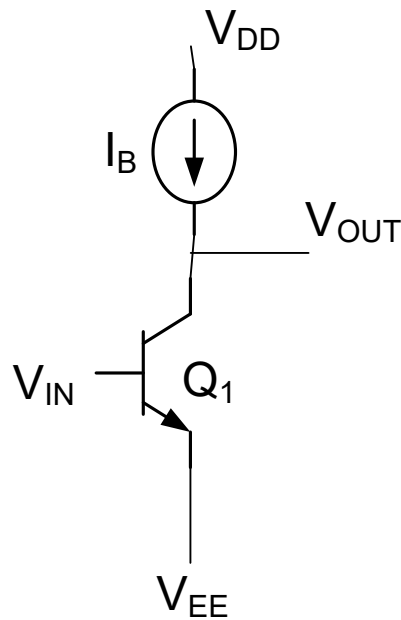


$$A_V \cong -8000$$

How can we build the current source?

→ What is the small-signal model of an actual current source?

Basic Current Sources and Sinks

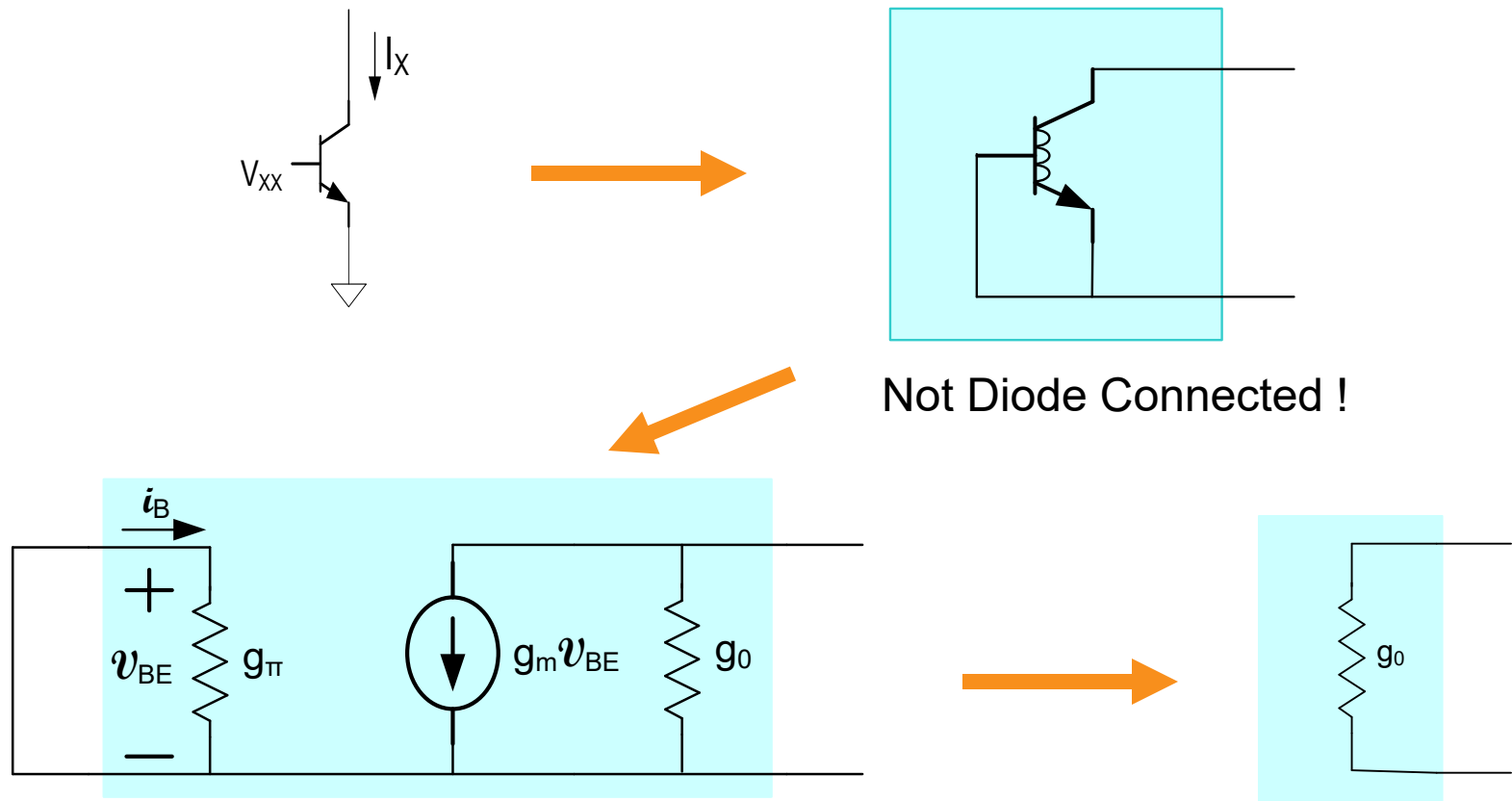
Small-signal Model of BJT Current Sinks and Sources



Small-signal model of all other BJT Sinks and Sources introduced so far are the same



Basic Current Sources and Sinks

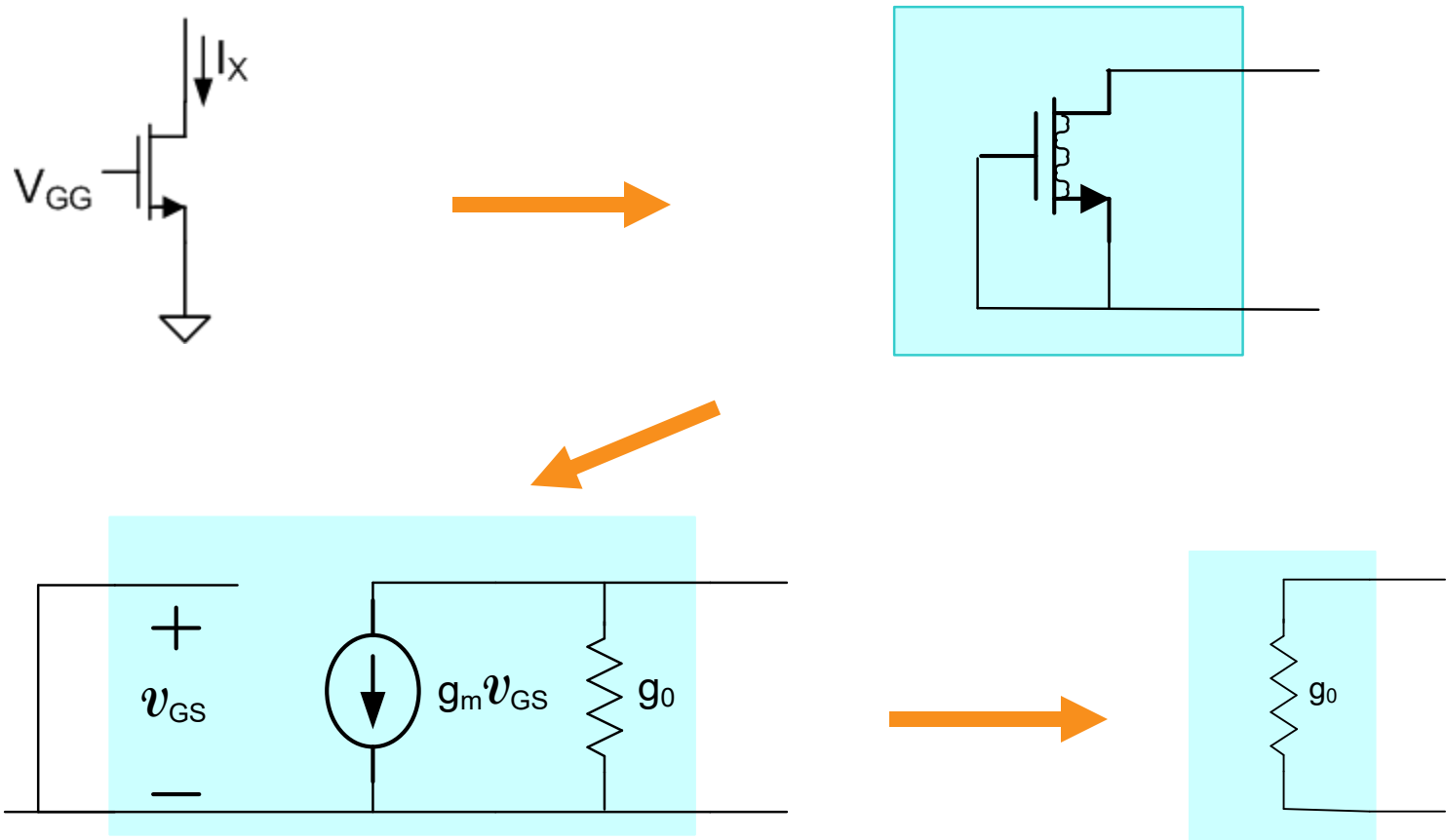Small-signal Model of MOS Current Sinks and Sources






Small-signal model of all other MOS Sinks and Sources introduced thus far are the same

High-gain amplifier

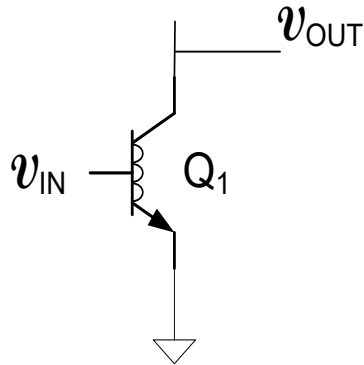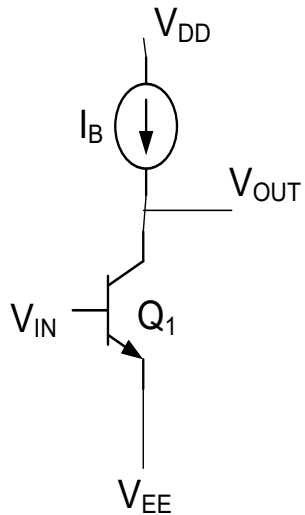


$$A_V = \frac{-g_m}{g_o}$$

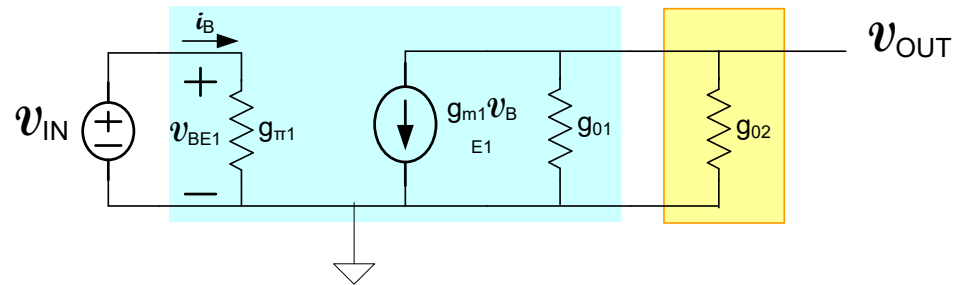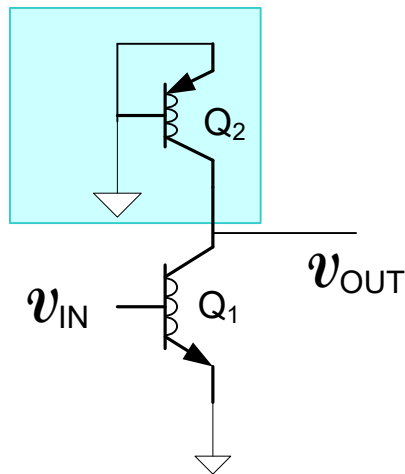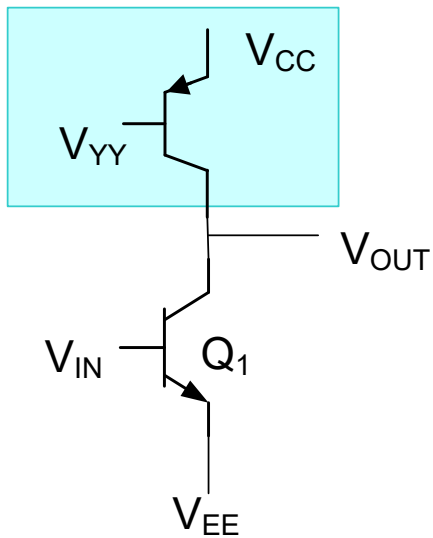

$$A_V = \frac{-g_{m1}}{g_{o1} + g_{o2}} \approx \frac{-g_{m1}}{2g_{o1}}$$


High-gain amplifier

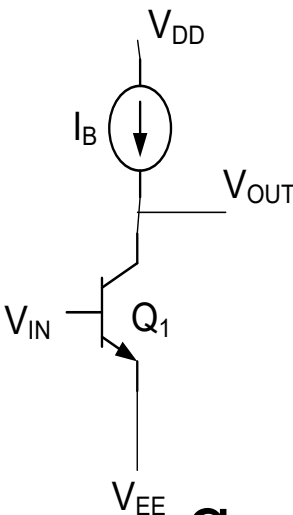

A circuit diagram of a common-emitter amplifier. The base of the transistor Q_1 is connected to an input terminal V_{IN} . The emitter is connected to a negative supply terminal V_{EE} . The collector is connected to a positive supply terminal V_{DD} through a current source I_B . The output terminal V_{OUT} is taken from the collector. The current source I_B is represented by a circle with a downward arrow.

$$A_V = \frac{-g_m}{g_0} = -8000$$
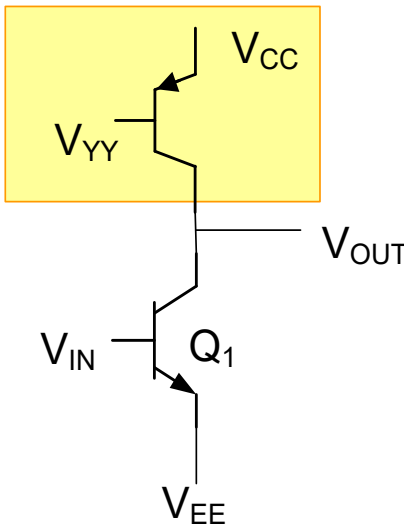
$$\frac{g_m}{g_0} = \frac{g_{m1}}{g_{01}} = \frac{V_{AF}}{V_t} \cong 8000$$



A circuit diagram of a common-emitter amplifier, similar to the first one, but with a different load. The collector is connected to a positive supply terminal V_{CC} through a current source I_{YY} . The output terminal V_{OUT} is taken from the collector. The current source I_{YY} is represented by a circle with a downward arrow and is highlighted with a yellow box.

$$A_V \cong \frac{-g_{m1}}{2g_{01}} = -4000$$

- Nonideal current source decreased the gain by a factor of 2
- But the voltage gain is still quite large (-4000)





Can the gain be made even larger?

High-gain amplifier


Can the gain be made even larger?

Discuss

The Cascode Configuration

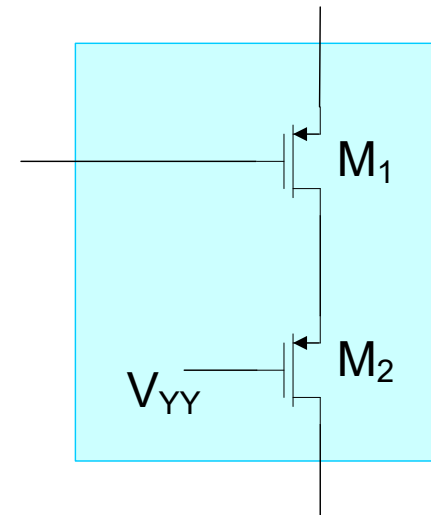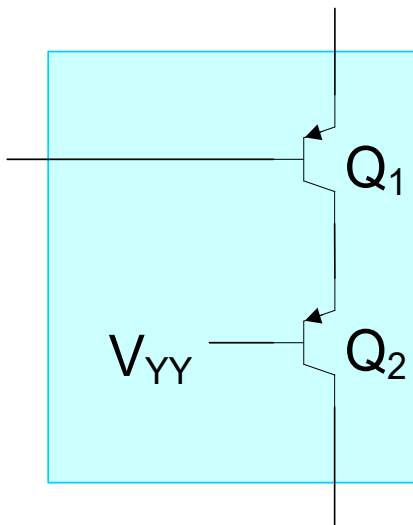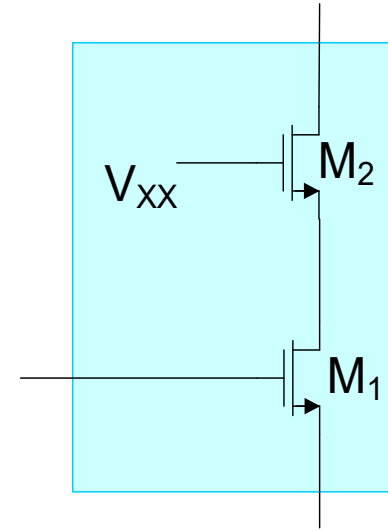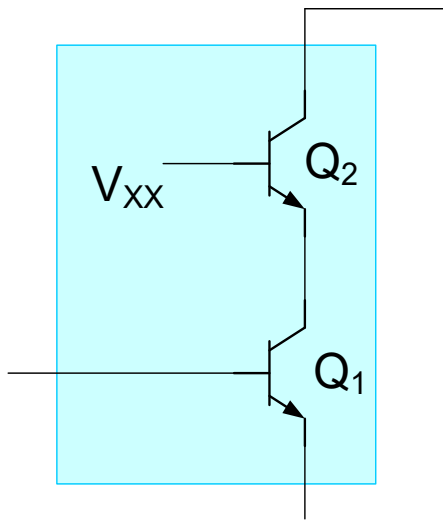

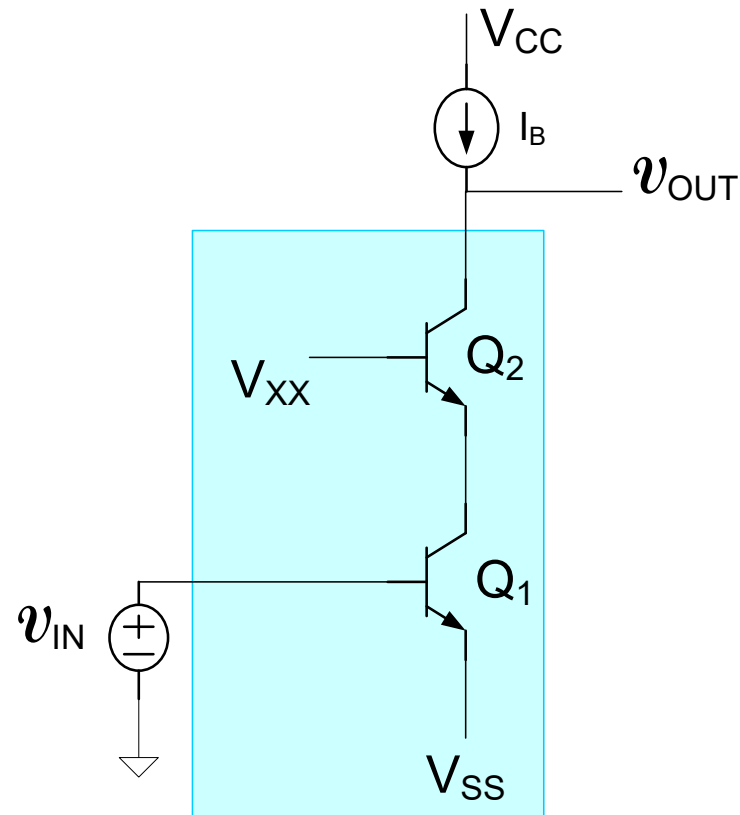The Cascode Amplifier (consider npn BJT version)



Discuss

- **Actually a cascade of a CE stage followed by a CB stage but usually viewed as a “single-stage” structure**
- **Cascode structure is widely used**

Basic Amplifier Structures


Discuss

1. Common Emitter/Common Source
2. Common Collector/Common Drain
3. Common Base/Common Gate
4. Common Emitter with R_E / Common Source with R_S
- 5. Cascode (actually CE:CB or CS:CD cascade)
6. Darlington (special CE:CE or CS:CS cascade)

The first 4 are most popular


Cascode Configuration

Discuss

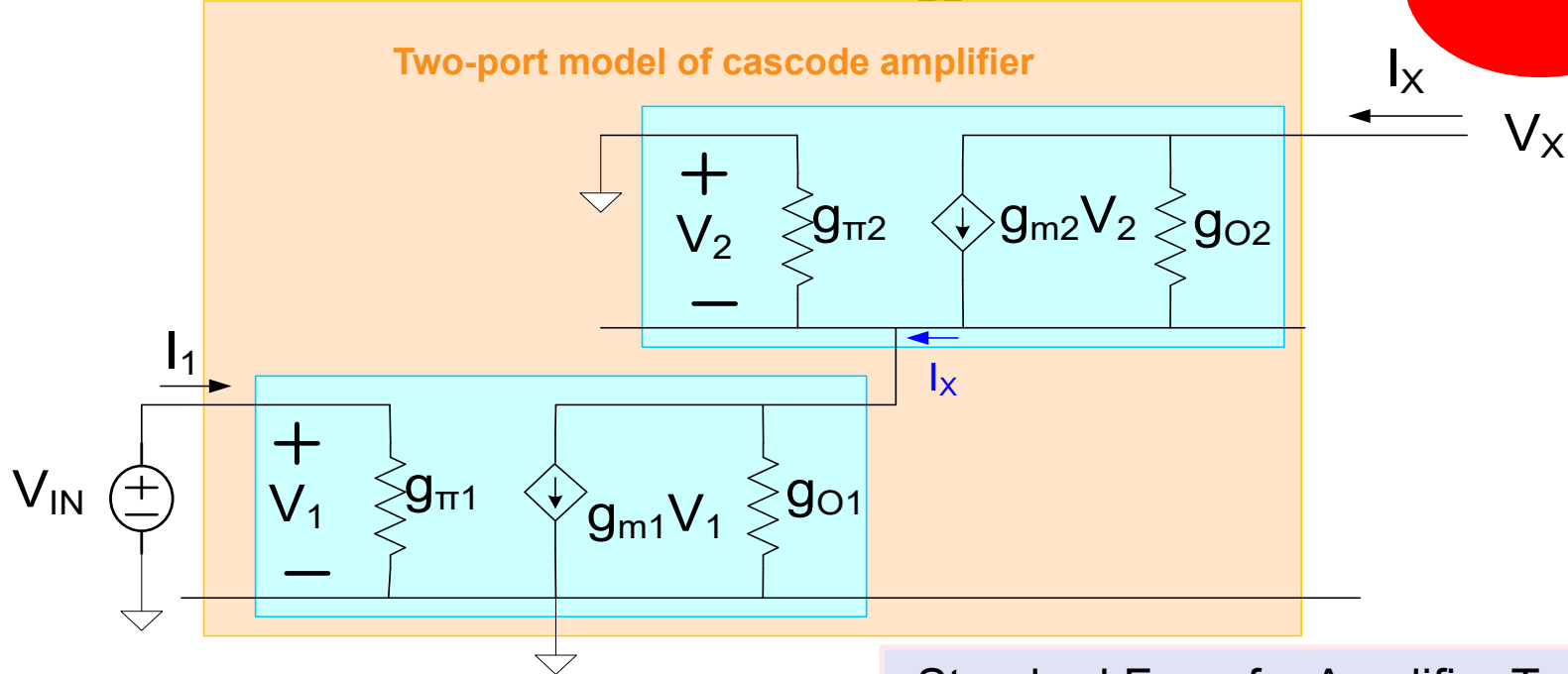

$$\left. \begin{aligned} (V_X + V_2)g_{o2} + V_2g_{m2} &= I_X \\ V_1 g_{m1} - V_2 (g_{o1} + g_{\pi2}) &= I_X \end{aligned} \right\}$$

Standard Form for Amplifier Two-Port

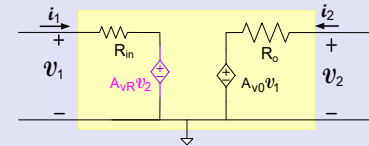

$$\begin{aligned} v_1 &= i_1 R_{IN} + A_{VR} v_2 \\ v_2 &= i_2 R_O + A_{VO} v_1 \end{aligned}$$

Observing $V_1 = V_{IN}$ and eliminating V_2 between these two equations, we obtain


$$V_{IN} = I_1 \cdot \frac{1}{g_{\pi1}}$$

and

$$V_X = I_X \cdot \left[\frac{g_{o1} + g_{o2} + g_{\pi2} + g_{m2}}{g_{o2} (g_{o1} + g_{\pi2})} \right] - V_{IN} \cdot \left[\frac{g_{m1} (g_{o2} + g_{m2})}{g_{o2} (g_{\pi2} + g_{o1})} \right]$$

Cascode Configuration

Discuss

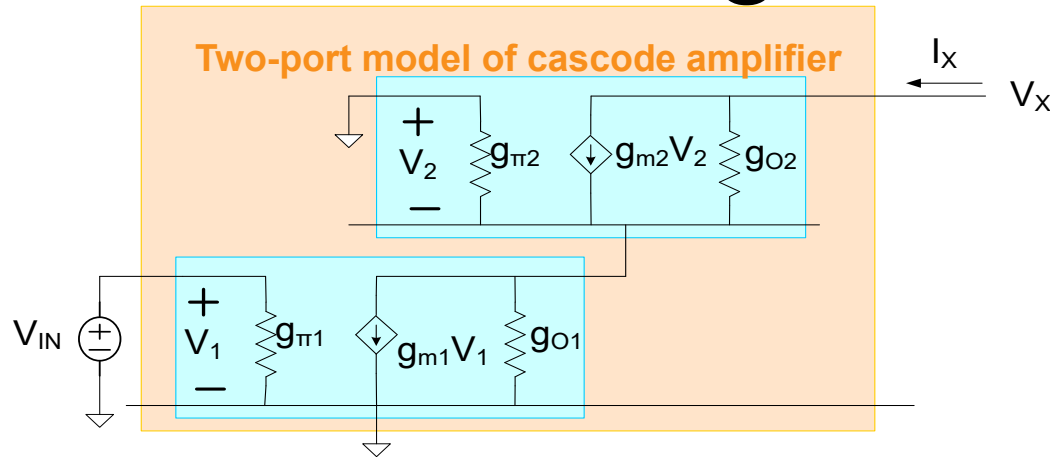

$$V_X = I_X \cdot \left[\frac{g_{o1} + g_{o2} + g_{\pi2} + g_{m2}}{g_{o2}(g_{o1} + g_{\pi2})} \right] - V_{IN} \cdot \left[\frac{g_{m1}(g_{o2} + g_{m2})}{g_{o2}(g_{\pi2} + g_{o1})} \right]$$


$$V_{IN} = I_1 \cdot \frac{1}{g_{\pi1}}$$

It thus follows for the npn bipolar structure that :

$$A_{VCC} = - \left[\frac{g_{m1}(g_{o2} + g_{m2})}{g_{o2}(g_{\pi2} + g_{o1})} \right] \cong - \left[\frac{g_{m1}g_{m2}}{g_{o2}g_{\pi2}} \right]$$


$$g_{oCC} = \left[\frac{g_{o2}(g_{o1} + g_{\pi2})}{g_{o1} + g_{o2} + g_{\pi2} + g_{m2}} \right] \cong \left[\frac{g_{o2}g_{\pi2}}{g_{m2}} \right]$$

$$g_{\pi CC} = g_{\pi1}$$

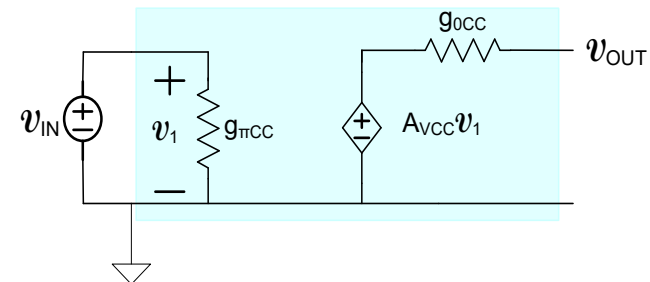

Cascode Configuration

Discuss

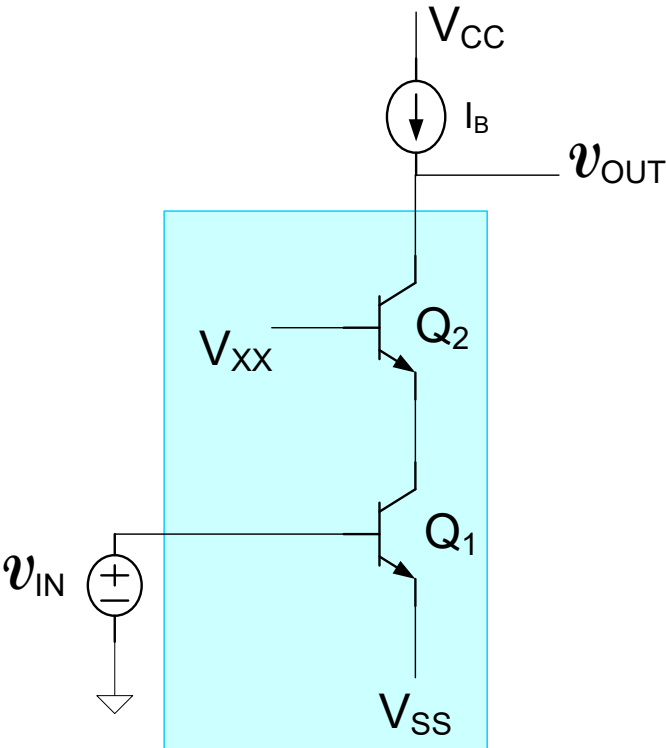

$$A_{V_{CC}} \cong - \left[\frac{g_{m1} g_{m2}}{g_{o2} g_{\pi 2}} \right]$$

$$g_{o_{CC}} \cong \left[\frac{g_{o2} g_{\pi 2}}{g_{m2}} \right]$$

$$g_{\pi_{CC}} = g_{\pi 1}$$


$$A_{V_{CC}} \cong - \left[\frac{g_{m1}}{g_{o2}} \beta \right] \cong - \left[\frac{g_{m1}}{g_{o1}} \right] \beta$$

$$g_{o_{CC}} \cong \frac{g_{o1}}{\beta}$$

- Voltage gain is a factor of β larger than that of the CE amplifier with current source load
- Output impedance is a factor of β larger than that of the CE amplifier

Cascode Configuration

Discuss

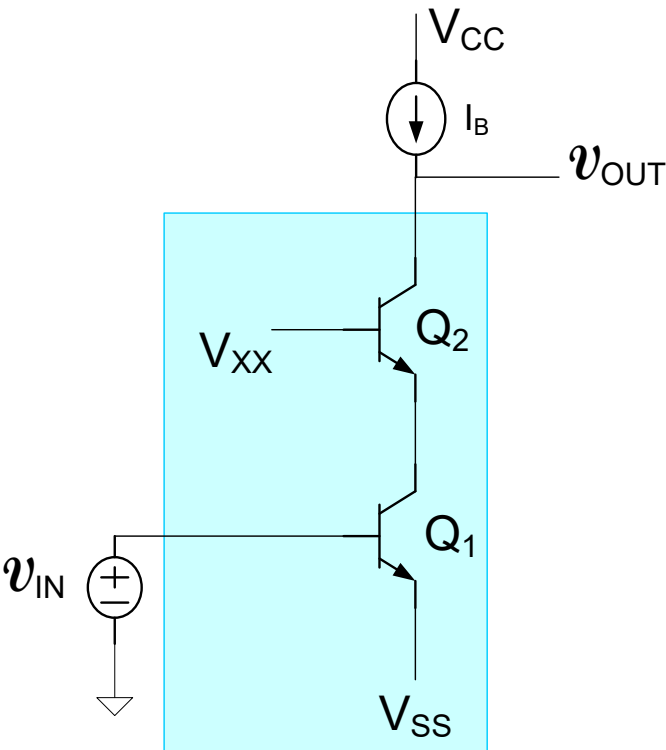

$$A_{V_{CC}} \cong - \left[\frac{g_{m1} \beta}{g_{o2}} \right] \cong - \left[\frac{g_{m1}}{g_{o1}} \right] \beta$$

$$g_{o_{CC}} \cong \frac{g_{o2}}{\beta}$$


$$A_{V_{CC}} \cong - \left[\frac{g_{m1}}{g_{o1}} \right] \beta = \left[\frac{2V_{AF}}{V_t} \right] \beta = [-8000]100$$

$$A_{V_{CC}} \cong -800,000$$


This gain is very large and only requires two transistors!

What happens to the gain if a transistor-level current source is used for I_B ?


Cascode Configuration

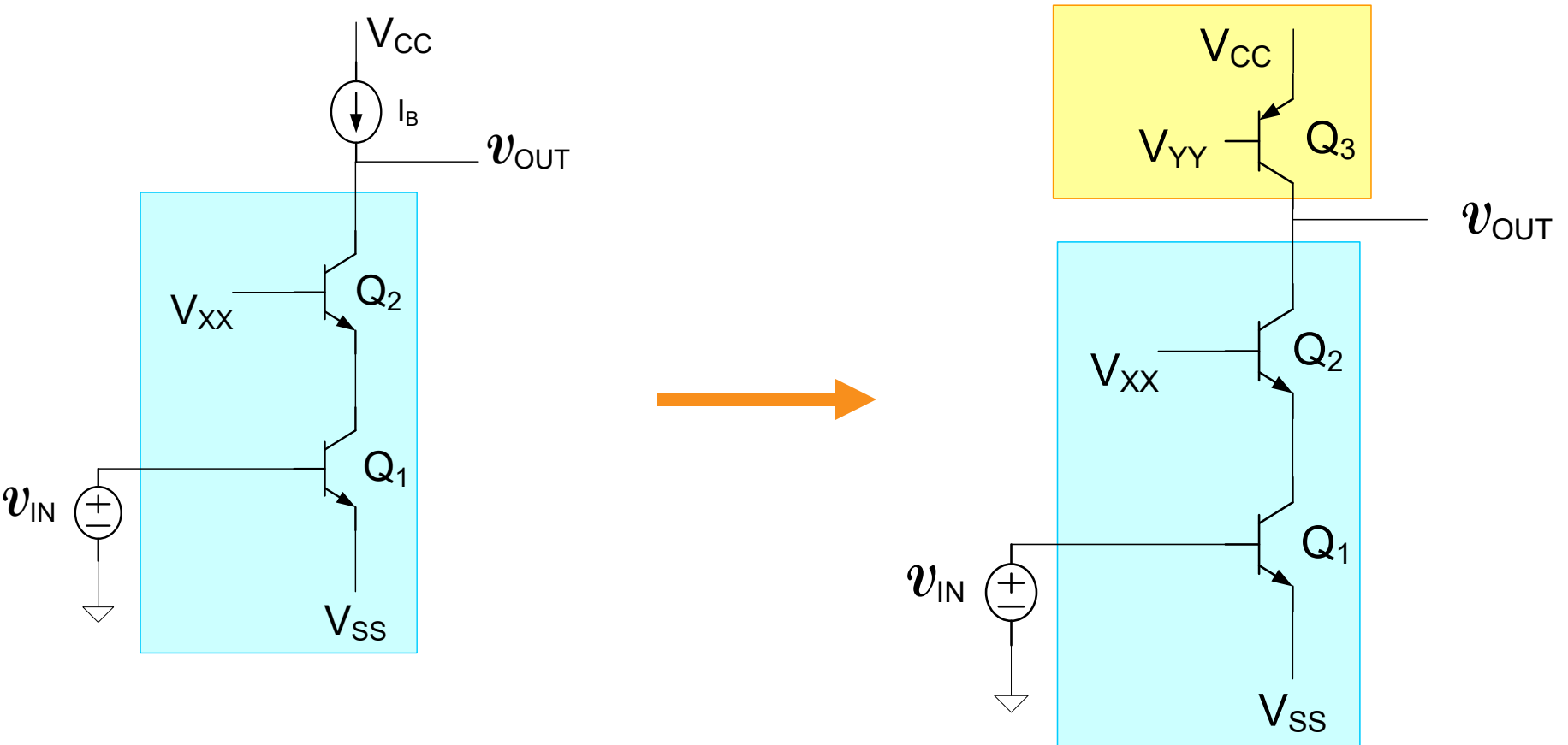

Cascode Configuration

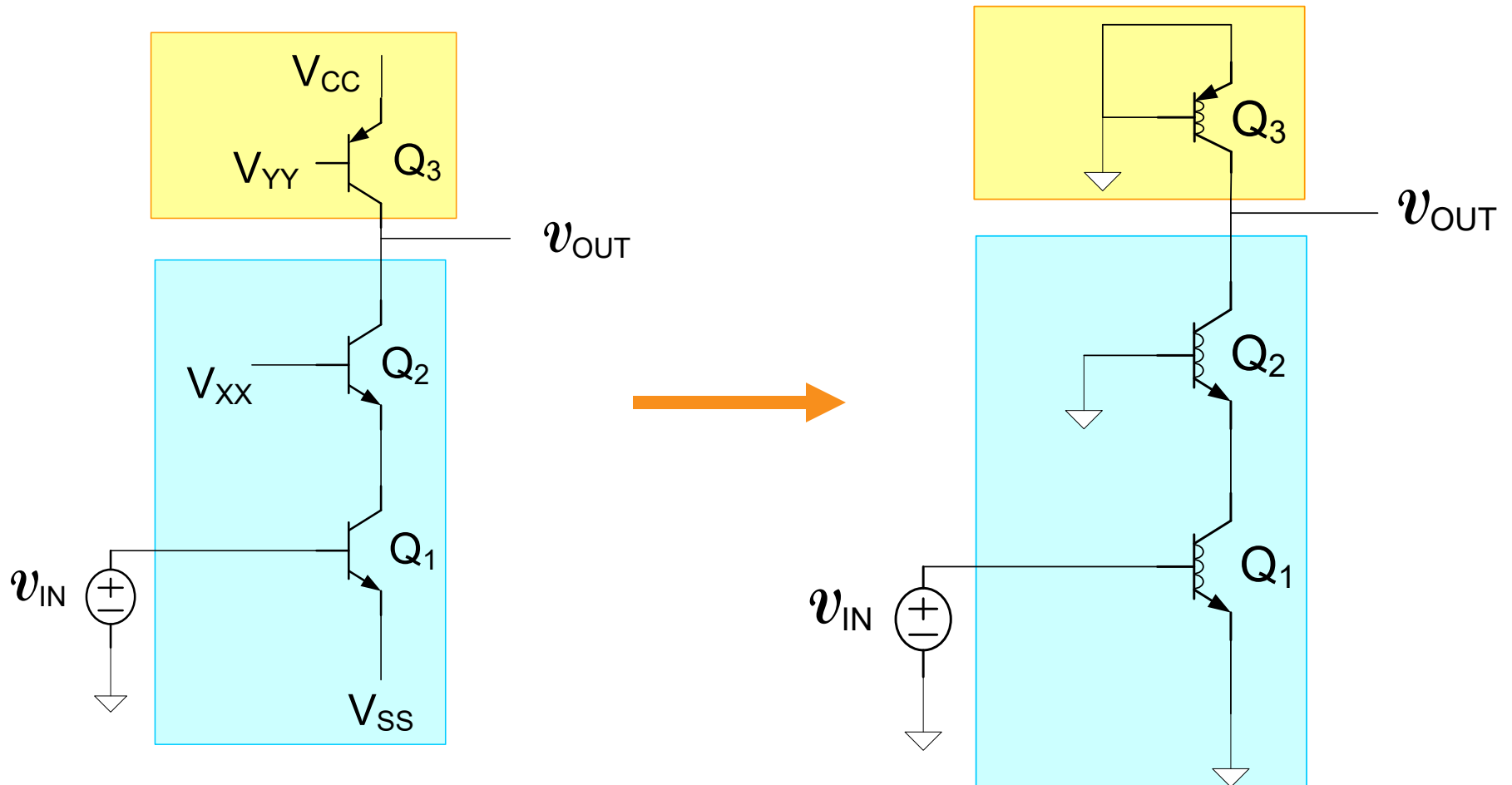

High-gain amplifier comparisons

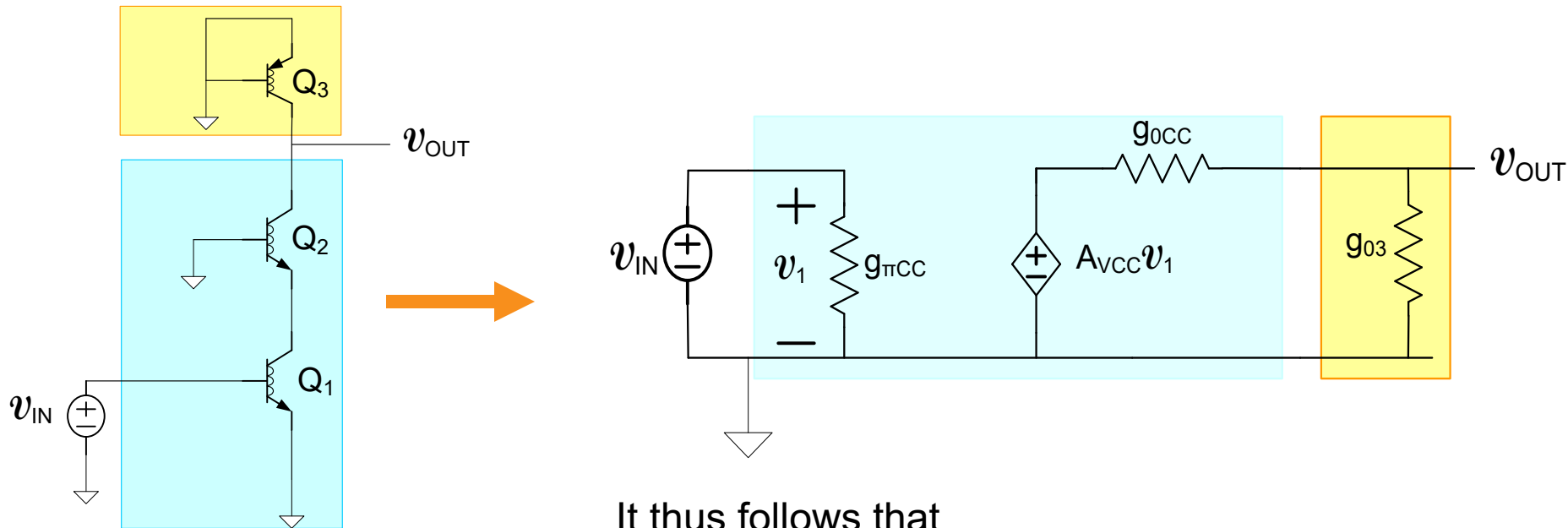

It thus follows that


$$A_V = A_{VCC} \left[\frac{g_{0CC}}{g_{03} + g_{0CC}} \right]$$

But $g_{0CC} \simeq g_{03}/\beta$

$$A_V \simeq A_{VCC} \left[\frac{g_{0CC}}{g_{03}} \right] \simeq \frac{A_{VCC}}{\beta}$$

This is a dramatic reduction in gain compared to what the ideal current source biasing provided

Cascode Configuration

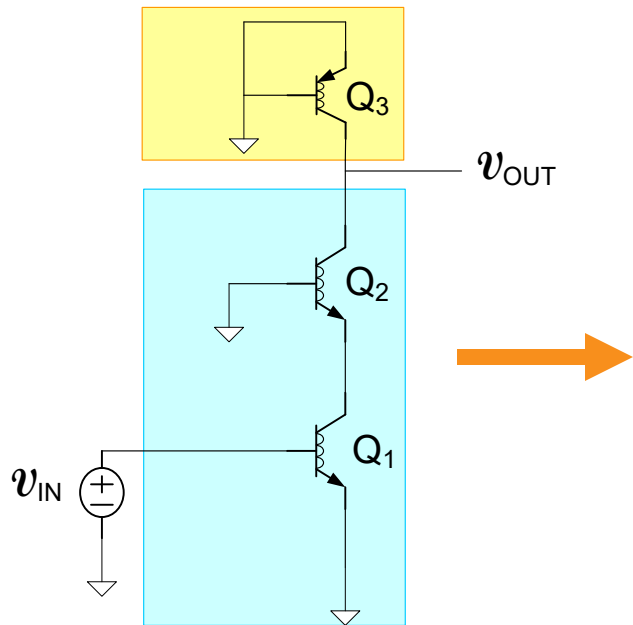

$$A_V \cong A_{VCC} \left[\frac{g_{0CC}}{g_{03}} \right] \cong \frac{A_{VCC}}{\beta}$$

But recall

$$A_{VCC} \cong - \left[\frac{g_{m1}}{g_{01}} \right] \beta$$


Thus

$$A_V \cong - \left[\frac{g_{m1}}{g_{01}} \right]$$


$$A_V \cong - \left[\frac{I_{CQ} / V_t}{I_{CQ} / V_{AF}} \right] = - \left[\frac{V_{AF}}{V_t} \right] \cong -8000$$

- This is still a factor of 2 better than that of the CE amplifier with transistor current source $\left(A_{VCE} \cong - \left[\frac{g_{m1}}{2g_{01}} \right] \right)$
- It only requires one additional transistor
- But its not nearly as good as the gain the cascode circuit seemed to provide


Cascode Configuration Comparisons

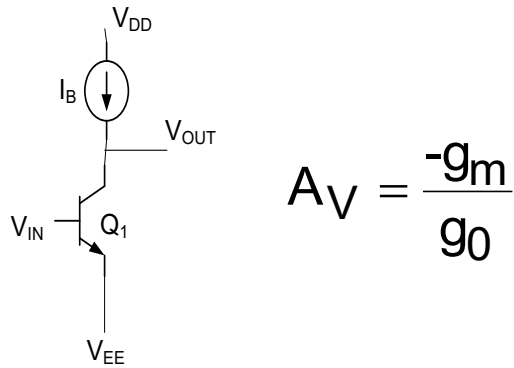


$$A_V = \frac{-g_m}{g_0}$$

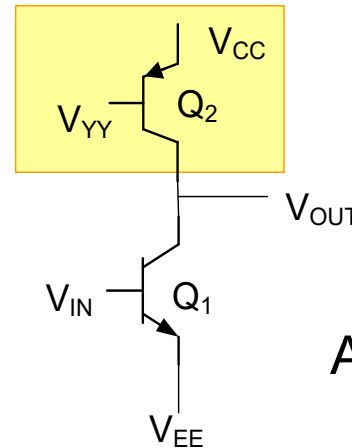
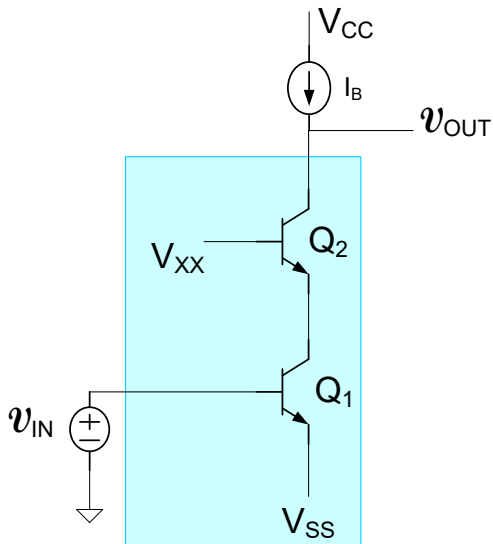
$$A_V \cong \frac{-g_{m1}}{g_{01} + g_{02}} = \frac{-g_{m1}}{2g_{01}}$$


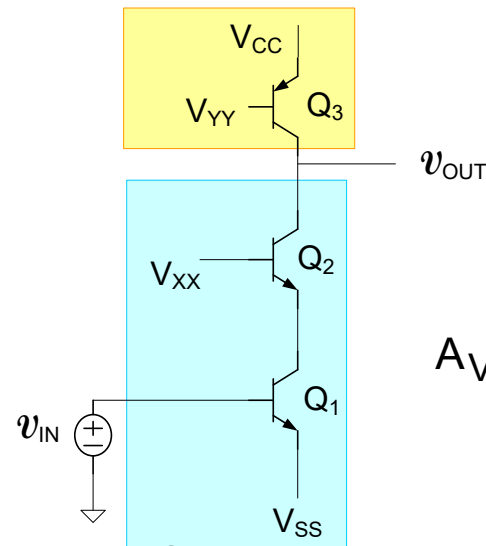
$$A_V \cong - \left[\frac{g_{m1}}{g_{01}} \right] \beta$$



$$A_V \cong - \left[\frac{g_{m1}}{\frac{g_{01}}{\beta} + g_{03}} \right] \cong - \left[\frac{g_{m1}}{g_{03}} \right]$$

Gain limited by output impedance of current source !!

Can we design a better current source?

In particular, one with a higher output impedance?

Better current sources

Need a higher output impedance than g_o



The output impedance of the cascode circuit itself was very large !



$$g_{oCC} \approx \frac{g_{o1}}{\beta}$$

Can a current source be built with the cascode circuit ?




Cascode current sources



Discuss

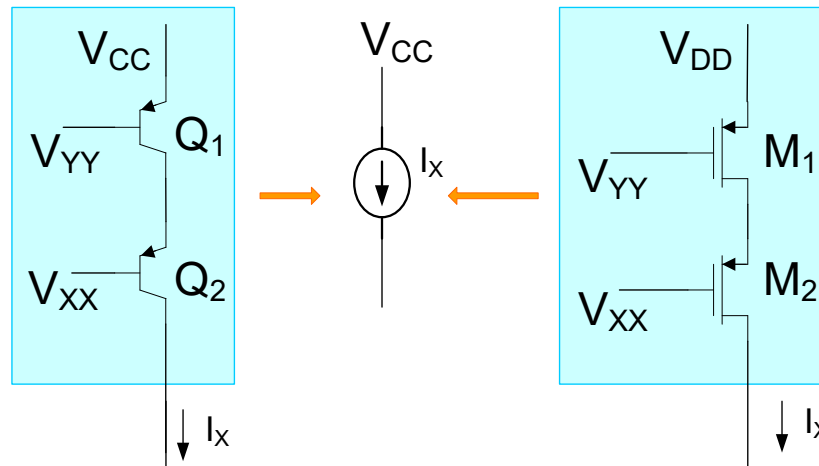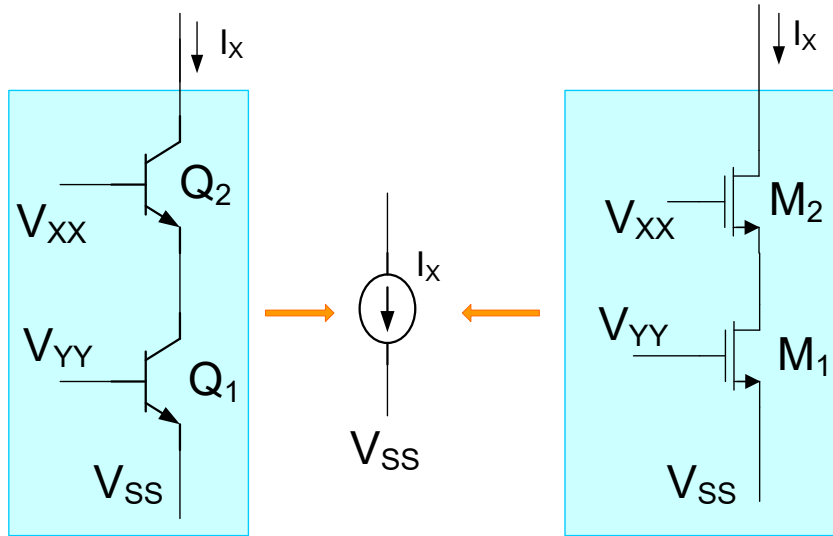

Cascode current sources

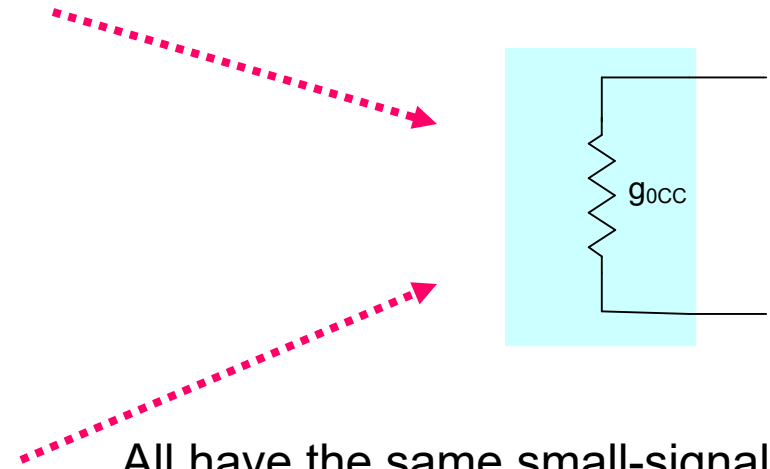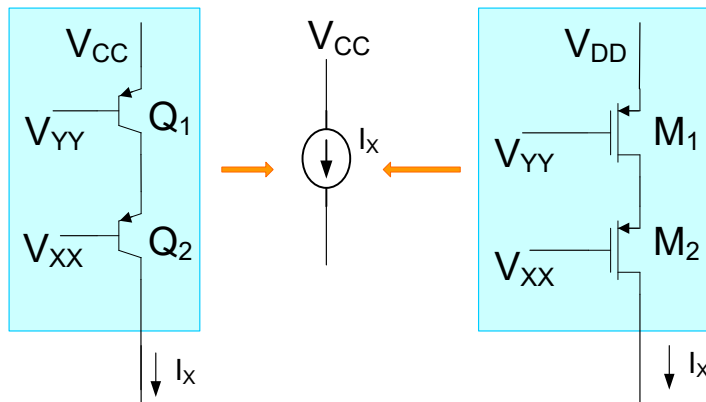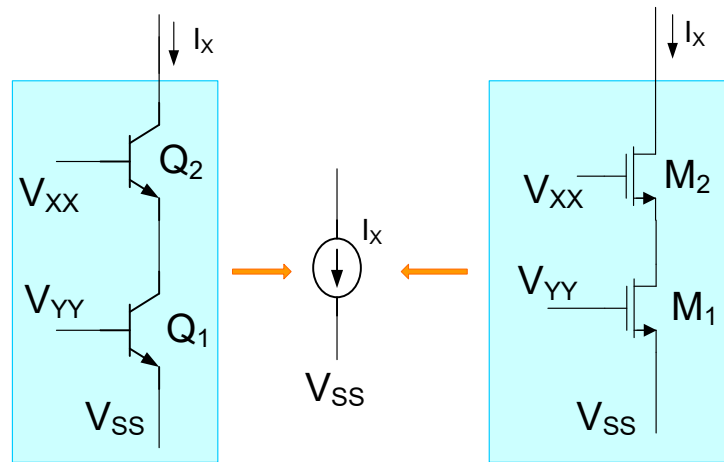


All have the same small-signal model

$$g_{0CC} = \left[\frac{g_{02} (g_{01} + g_{\pi 2})}{g_{01} + g_{02} + g_{\pi 2} + g_{m2}} \right]$$

Cascode Configuration

Discuss

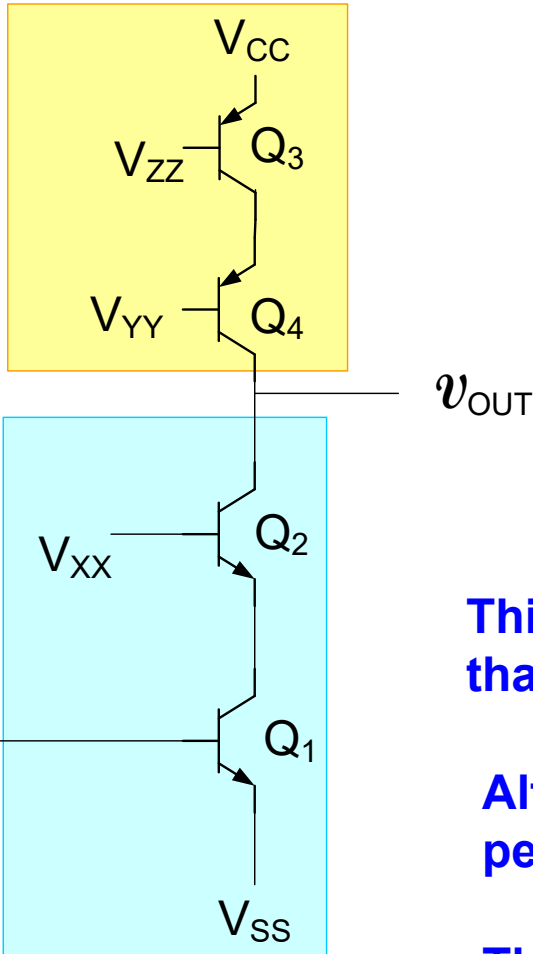

$$A_V = - \left[\frac{g_{m1}}{g_{o1}} \right] \frac{\beta}{2}$$



$$A_V = - [8000] \frac{100}{2} \cong -400,000$$

This gain is very large and is a factor of 2 below that obtained with an ideal current source biasing

Although the factor of 2 is not desired, the performance of this circuit is still very good



This factor of 2 gain reduction is that same as was observed for the CE amplifier when a transistor-level current source was used

Cascode Configuration Comparisons

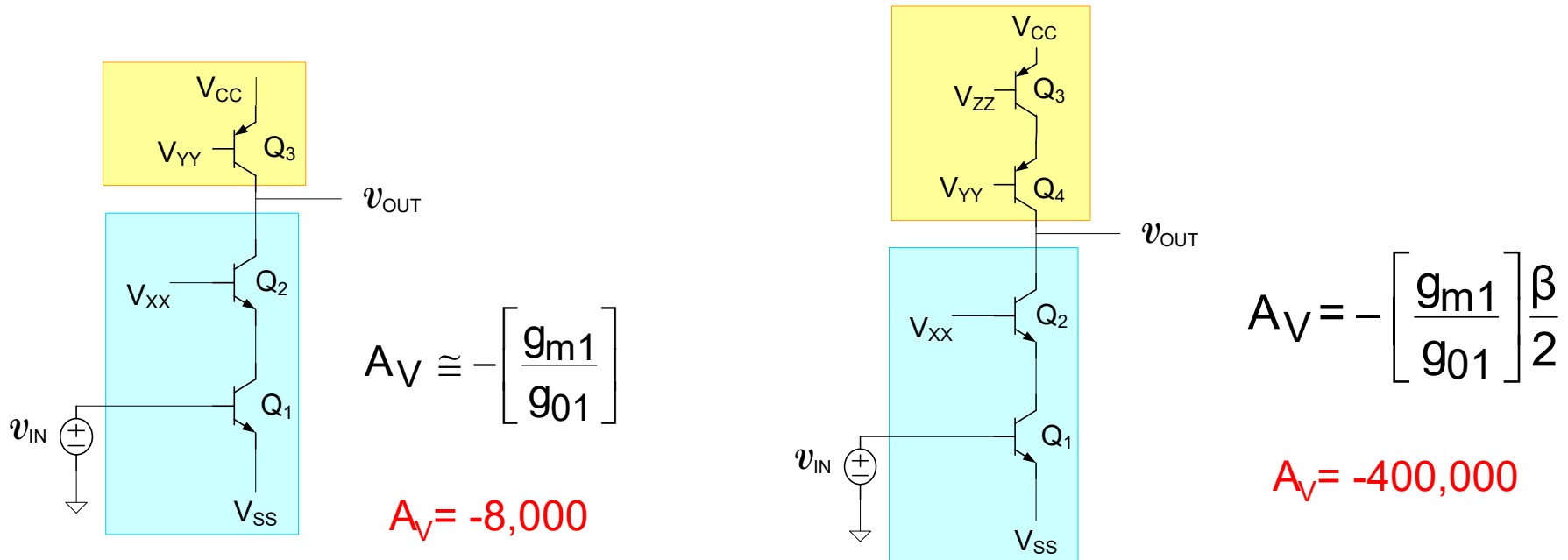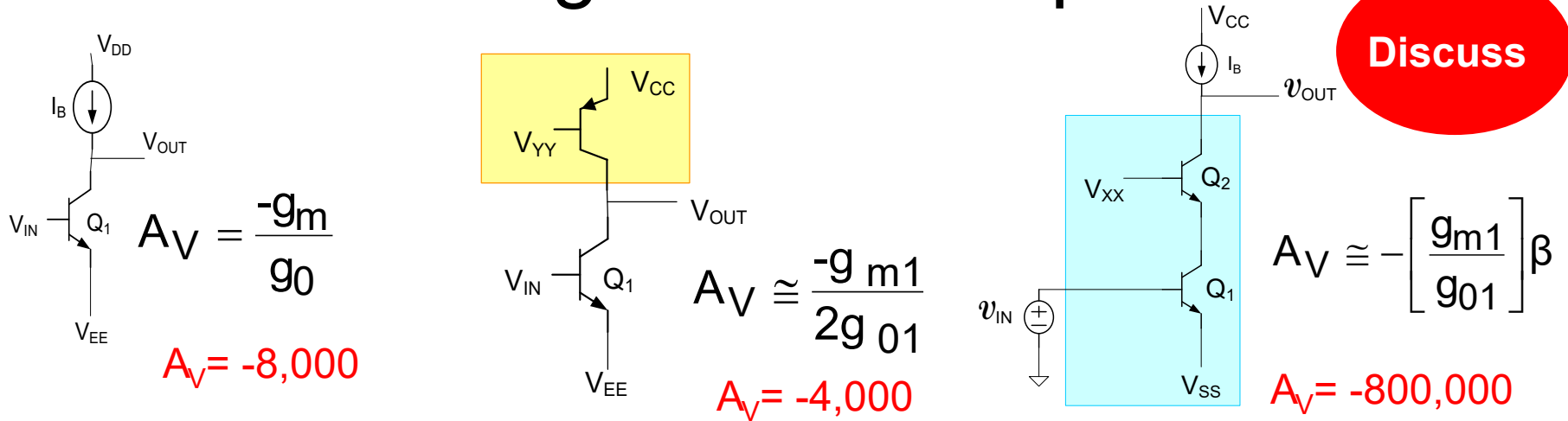

Can we use more cascoding to further increase the gain?

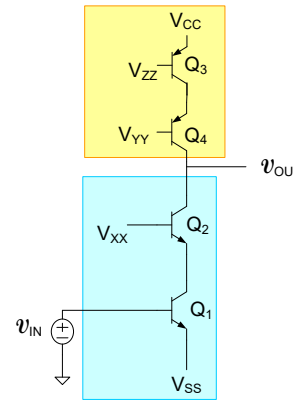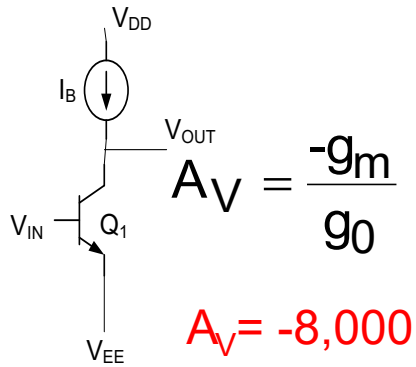
High Gain Amplifiers Seldom Used Open Loop



$$A_V = - \left[\frac{g_{m1}}{g_{o1}} \right] \frac{\beta}{2}$$

$A_V = -400,000$

Discuss

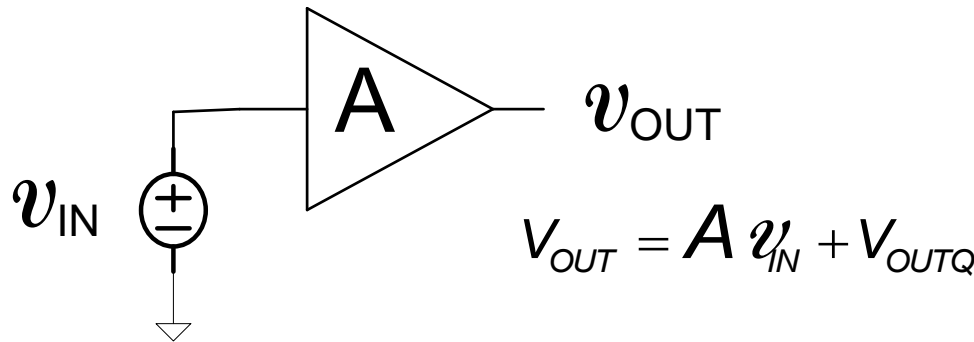


If $A_V = -400,000$ and V_{IN} increases by 1mV, what would happen at the output?

V_{OUT} would decrease by $400,000 \times 1\text{mV} = -400\text{V}$

The Cascode Amplifier (consider n-ch MOS version)

Discuss

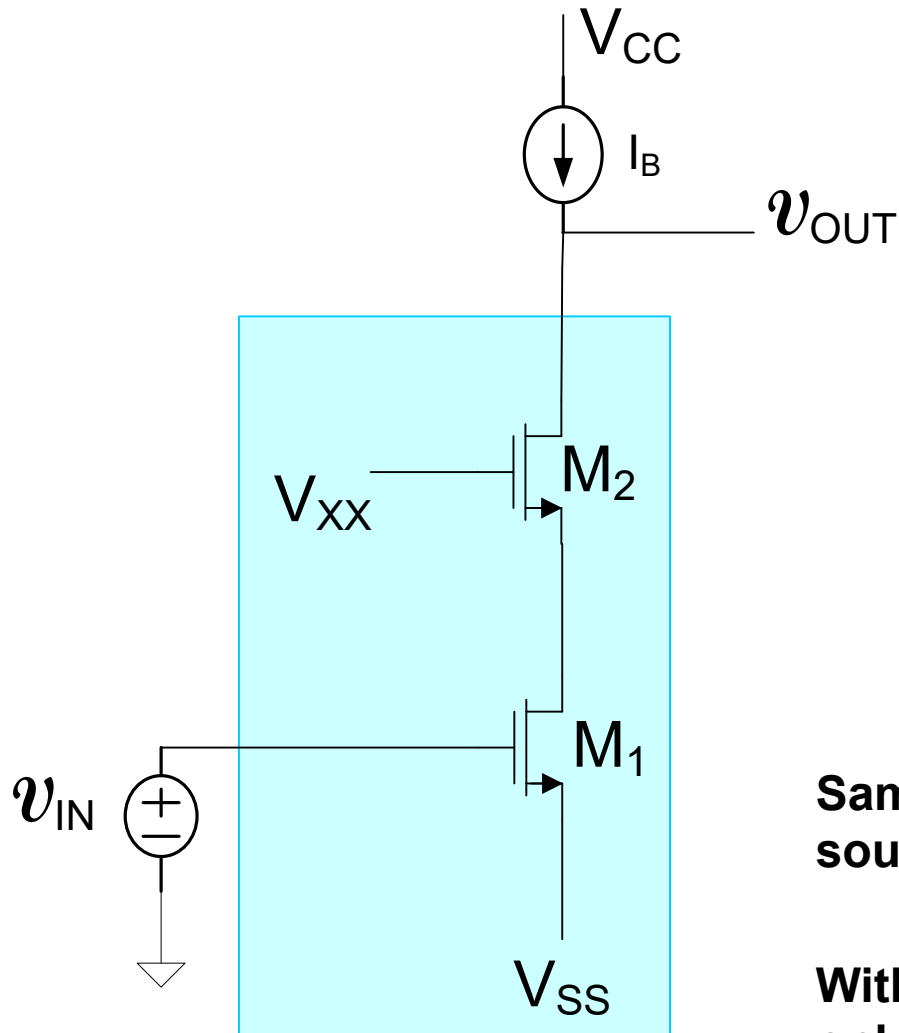

$$A_{V_{CC}} \cong - \left[\frac{g_{m1} g_{m2}}{g_{o1} g_{o2}} \right]$$


$$g_{o_{CC}} \cong \left[\frac{g_{o1} g_{o2}}{g_{m2}} \right]$$

Same issues for biasing with current source as for BJT case


With cascode current source for I_B , gain only drops by a factor of 2 from value with ideal current source

The Cascode Amplifier (consider n-ch MOS version)


Discuss

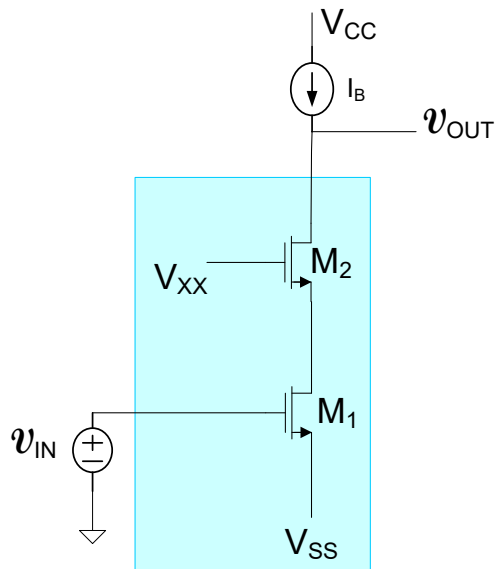
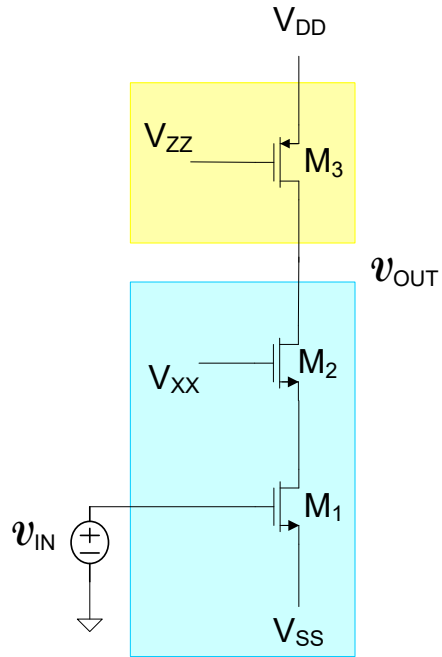
$$A_{VCC} \cong - \left[\frac{g_{m1} g_{m2}}{g_{o1} g_{o2}} \right]$$




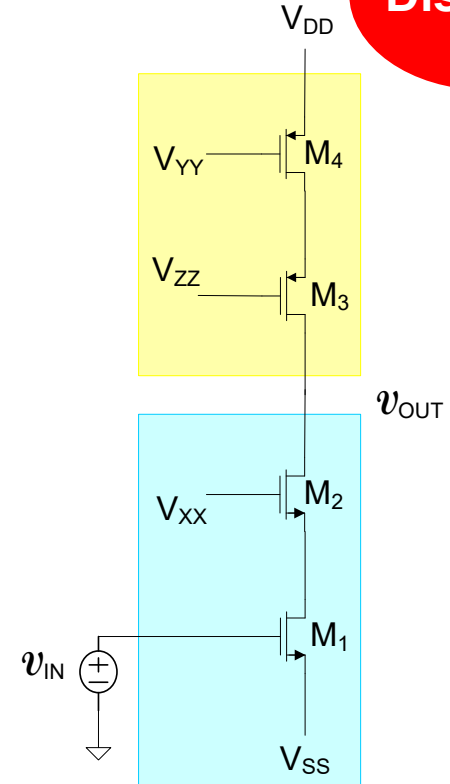
$$A_{VCC} \cong - \left[\frac{g_{m1}}{g_{o1}} \right]$$



$$A_{VCC} \cong - \frac{1}{2} \left[\frac{g_{m1} g_{m2}}{g_{o1} g_{o2}} \right]$$



Current Source Summary (BJT)

Basic

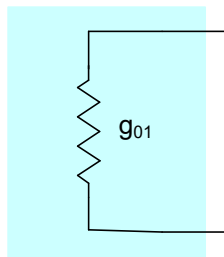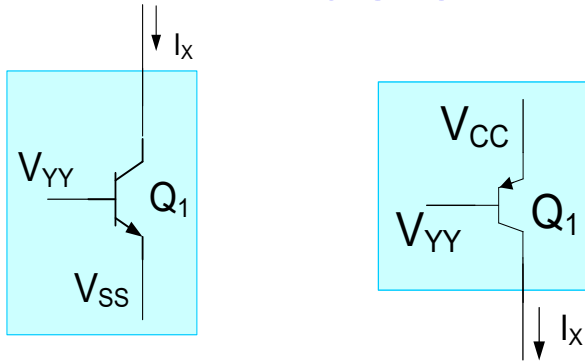


$$g_0 \cong g_{01}$$

Cascode


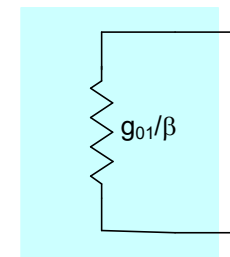
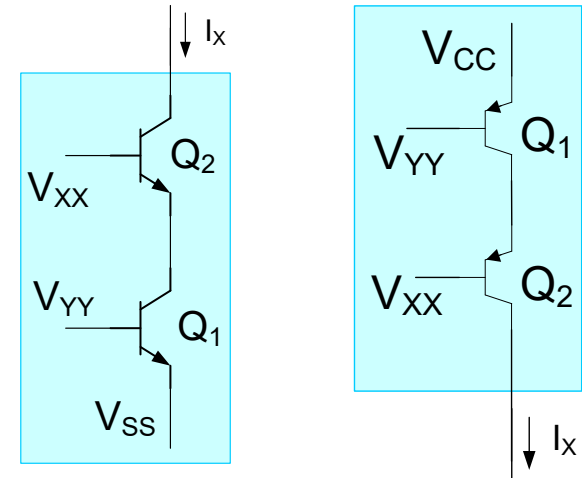


$$g_{0CC} \cong \frac{g_{01}}{\beta}$$

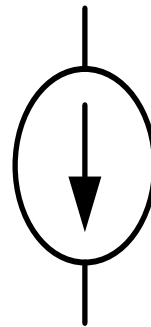



Current Source Summary (MOS)

Basic

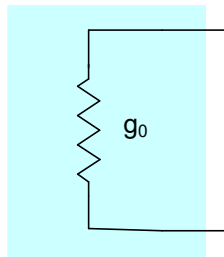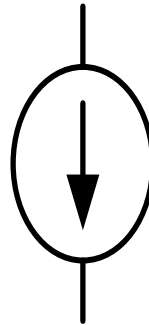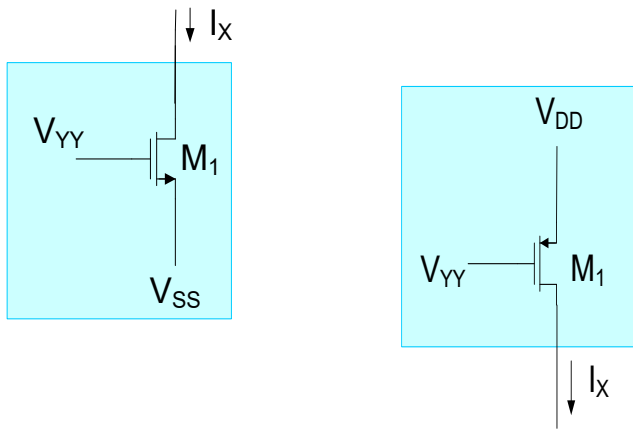


$$g_0 \cong g_{01}$$

Cascode

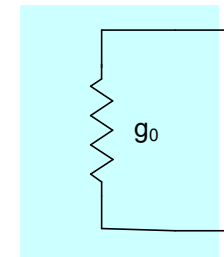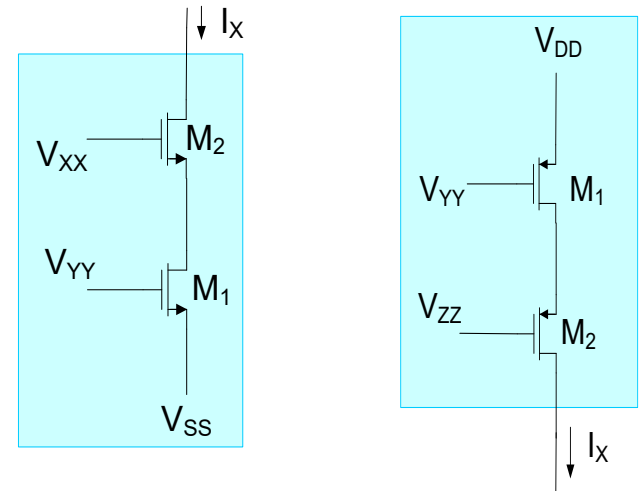


$$g_0 \cong g_{01} \frac{g_{02}}{g_{m2}}$$

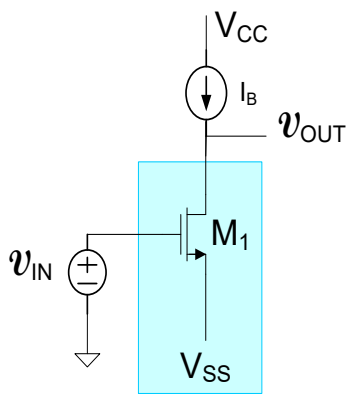
High Gain Amplifier Comparisons (n-ch MOS)



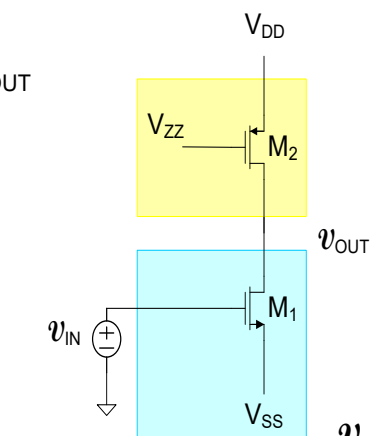
$$A_V \cong - \left[\frac{g_{m1}}{g_{o1}} \right]$$



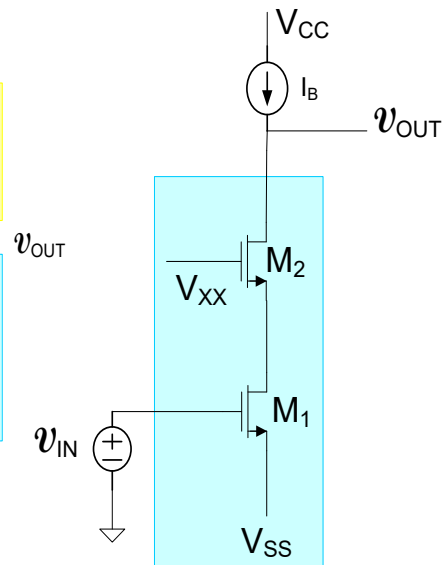
$$A_V \cong - \frac{1}{2} \left[\frac{g_{m1}}{g_{o1}} \right]$$


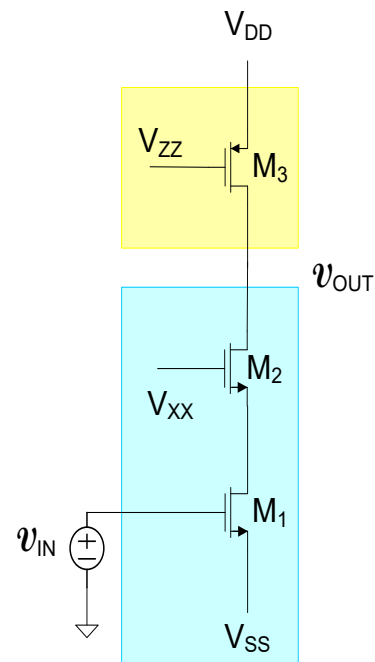
$$A_{VCC} \cong - \left[\frac{g_{m1}g_{m2}}{g_{o1}g_{o2}} \right]$$







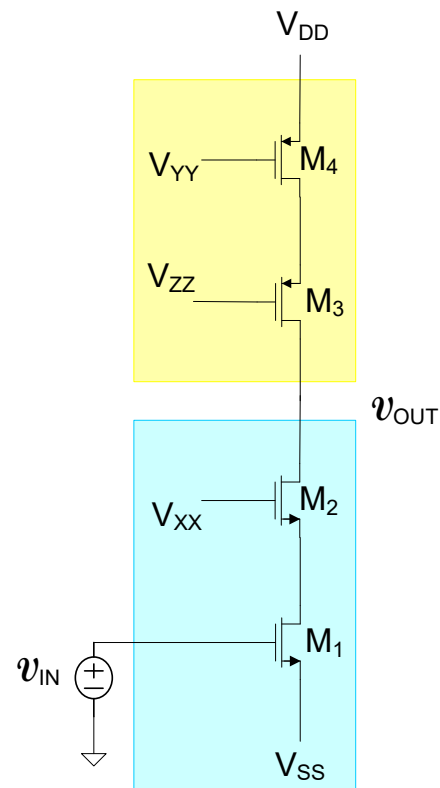
$$A_{VCC} \cong - \left[\frac{g_{m1}}{g_{o1}} \right]$$



$$A_{VCC} \cong - \frac{1}{2} \left[\frac{g_{m1}g_{m2}}{g_{o1}g_{o2}} \right]$$

High Gain Amplifier Comparisons (BJT)

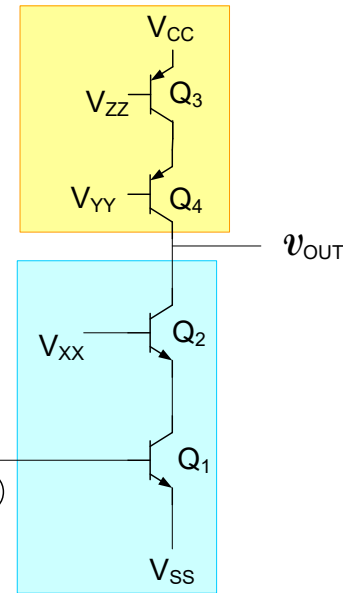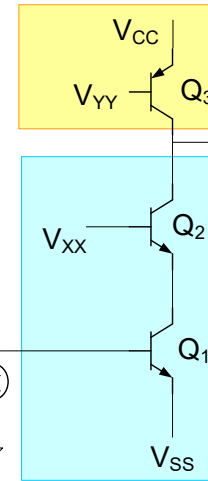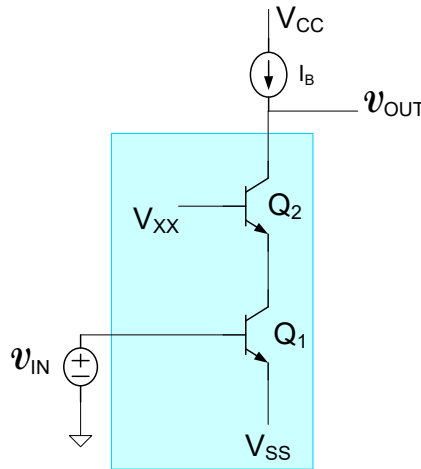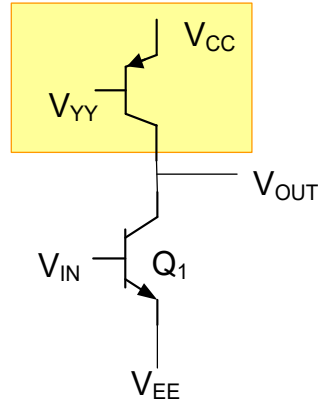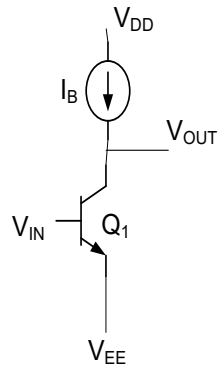

$$A_V = \frac{-g_m}{g_0}$$

$$A_V \cong -\frac{1}{2} \frac{g_{m1}}{g_{01}}$$

$$A_V \cong -\left[\frac{g_{m1}}{g_{01}} \right] \beta$$


$$A_V \cong -\left[\frac{g_{m1}}{g_{01}} \right]$$

$$A_V = -\left[\frac{g_{m1}}{g_{01}} \right] \frac{\beta}{2}$$

- Single-ended high-gain amplifiers inherently difficult to bias (because of the high gain)
- Biasing becomes practical when used in differential applications
- These structures are widely used but usually with differential inputs



The Cascode Amplifier

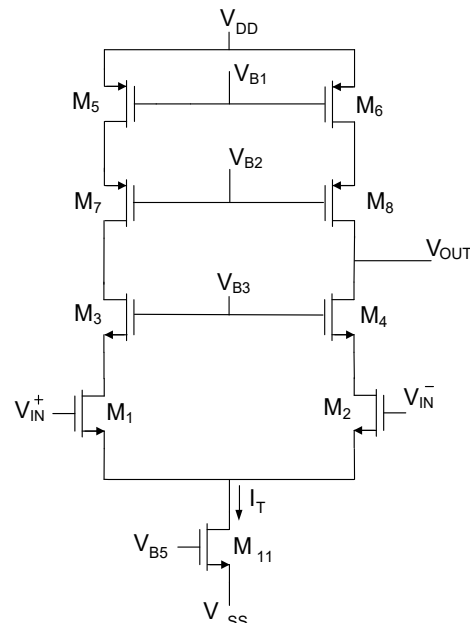- Operational amplifiers often built with basic cascode configuration
- CMFB used to address the biasing problem
- Usually configured as a differential structure when building op amps
- Have high output impedance (but can be buffered)
- Terms “telescopic cascode”, “folded-cascode”, and “regulated cascode” often refer to op amps based upon the cascode configuration



Telescopic Cascode Op Amp
(CMFB feedback biasing not shown)

Cascade Configurations

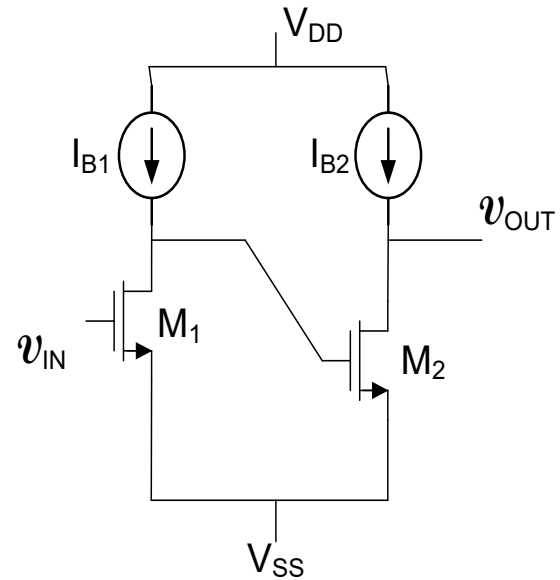
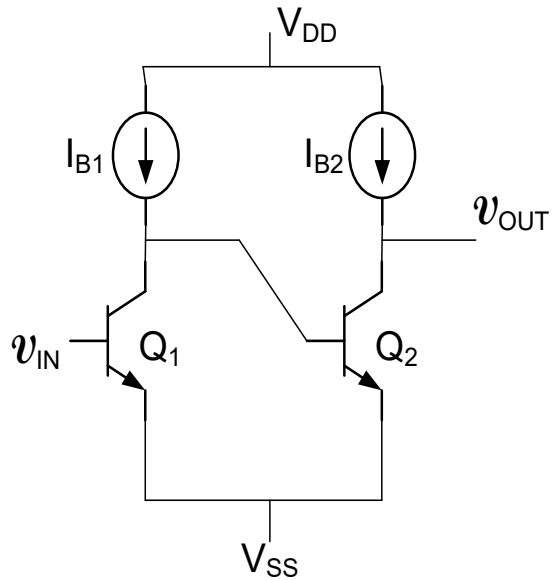


Two-stage CE:CE or CS:CS Cascade

$$A_{V_{CB}} = ?$$

$$A_{V_{CM}} = ?$$

Cascade Configurations

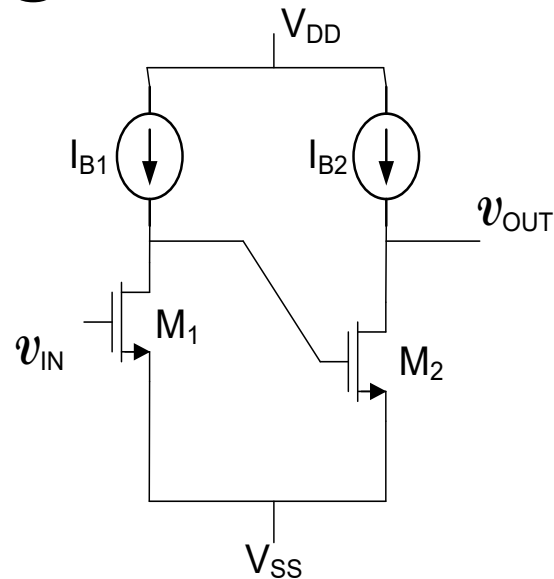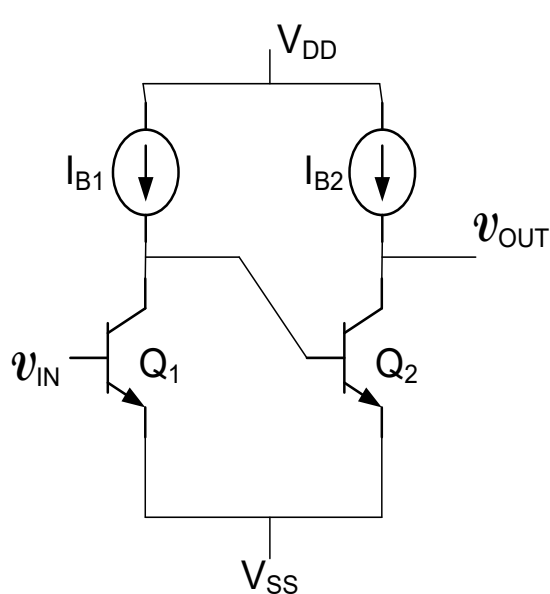



Two-stage CE:CE or CS:CS Cascade

$$A_{VCB} \cong \left[\frac{-g_{m1}}{g_{o1} + g_{\pi 2}} \right] \left[\frac{-g_{m2}}{g_{o2}} \right] \cong \frac{g_{m1} g_{m2}}{g_{\pi 2} g_{o2}} = \beta \frac{g_{m1}}{g_{o2}}$$

$$A_{VCM} = \left[\frac{-g_{m1}}{g_{o1}} \right] \left[\frac{-g_{m2}}{g_{o2}} \right] = \frac{g_{m1} g_{m2}}{g_{o1} g_{o2}}$$

- Significant increase in gain
- Gain is noninverting
- Comparable to that obtained with the cascode but noninverting

Cascade Configurations

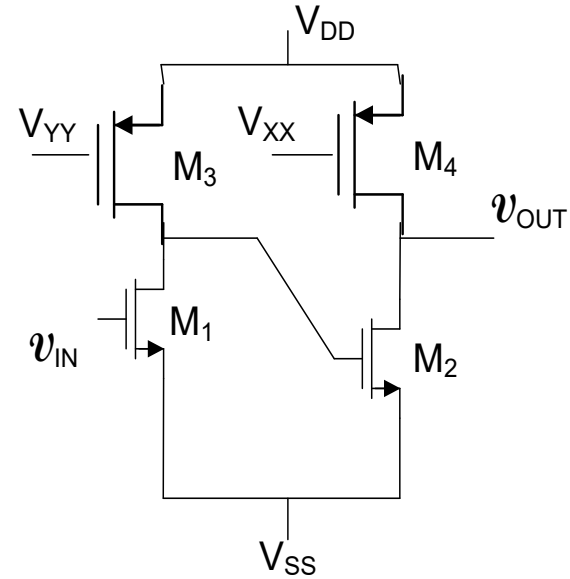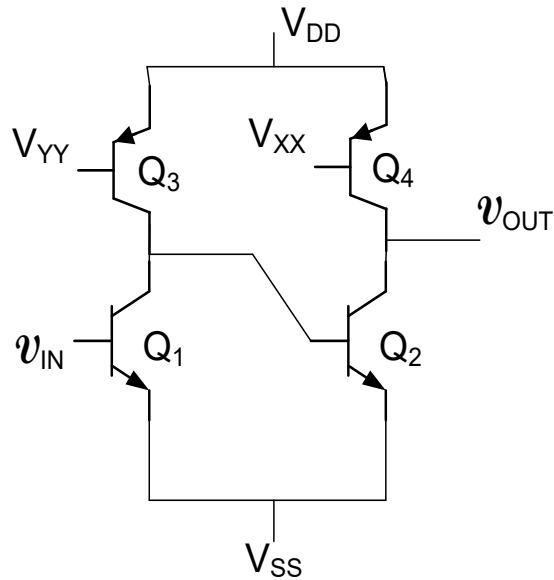


Two-stage CE:CE or CS:CS Cascade

$$A_{VCB} \cong \left[\frac{-g_{m1}}{g_{o1} + g_{o3} + g_{\pi 2}} \right] \left[\frac{-g_{m2}}{g_{o2} + g_{o4}} \right] \cong \frac{g_{m1} g_{m2}}{2g_{\pi} 2g_{o2}} = \beta \frac{g_{m1}}{2g_{o2}}$$


$$A_{VCM} = \left[\frac{-g_{m1}}{g_{o1} + g_{o3}} \right] \left[\frac{-g_{m2}}{g_{o2} + g_{o4}} \right] = \frac{g_{m1} g_{m2}}{4g_{o1} g_{o2}}$$

Note factor of 2 and 4 reduction in gain due to actual current source bias

Cascade Configurations

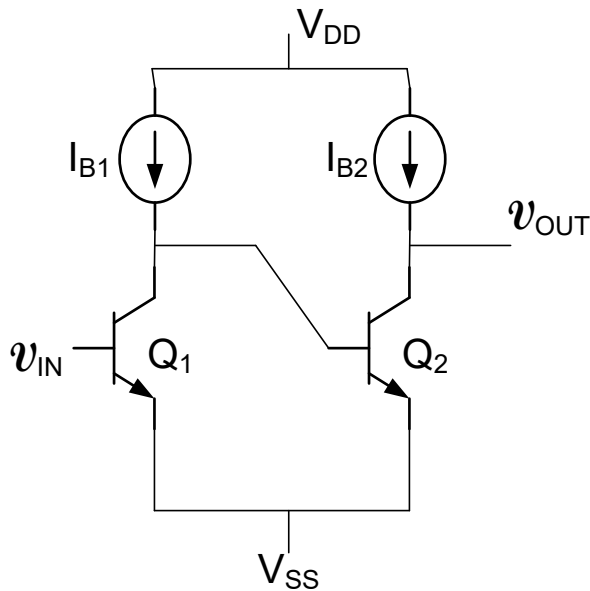


Two-stage CE Cascade

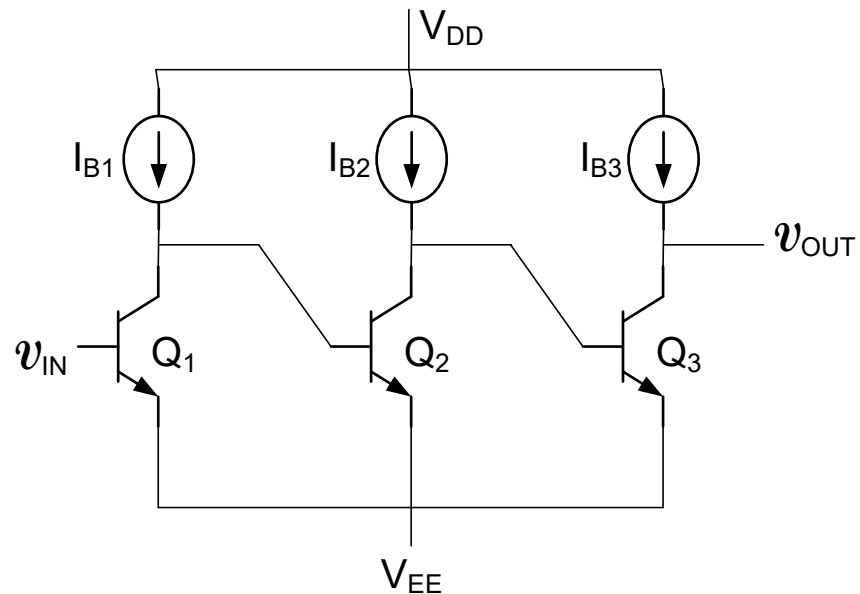

Three-stage CE Cascade

- Large gains can be obtained by cascading
- Gains are multiplicative (when loading is included)
- Large gains used to build “Op Amps” and feedback used to control gain value
- Some attention is needed for biasing but it is manageable
- Minor variant of the two-stage cascade often used to build Op Amps
- Compensation of two-stage cascade needed if feedback is applied to maintain stability
- For many years three or more stages were seldom cascaded because of challenges in compensation to maintain stability though recently some industrial adoptions

Differential Amplifiers

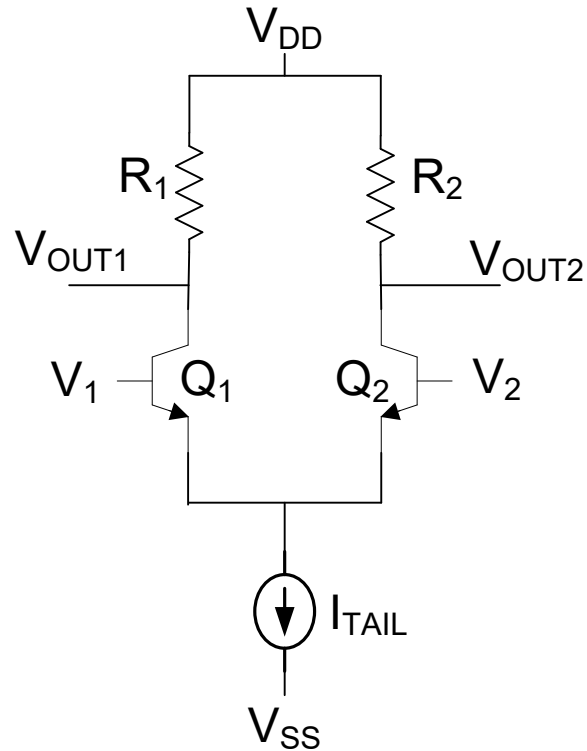

Basic operational amplifier circuit



Stay Safe and Stay Healthy !

End of Lecture 34