

# EE 330

## Lecture 39

### Digital Circuits

Ratio Logic

Other MOS Logic Families

Propagation Delay – basic characterization

Device Sizing (Inverter and multiple-input gates)

# Exam Schedule

<b>Exam 1</b>	<b>Friday Sept 24</b>
<b>Exam 2</b>	<b>Friday Oct 22</b>
<b>Exam 3</b>	<b>Friday Nov 19</b>
<b>Final</b>	<b>Tues Dec 14 12:00 p.m.</b>

Photo courtesy of the director of the National Institute of Health ( NIH)



As a courtesy to fellow classmates, TAs, and the instructor


**Wearing of masks during lectures and in the laboratories for this course would be appreciated irrespective of vaccination status**



Review from last lecture

# Transfer characteristics of the static CMOS inverter

(Neglect  $\lambda$  effects)

 

From Case 3 analysis:

$$V_{IN} = \frac{(V_{Tn}) + (V_{DD} + V_{Tp}) \sqrt{\frac{\mu_p}{\mu_n} \frac{W_2}{W_1} \frac{L_1}{L_2}}}{1 + \sqrt{\frac{\mu_p}{\mu_n} \frac{W_2}{W_1} \frac{L_1}{L_2}}}$$



Review from last lecture

# How should $M_1$ and $M_2$ be sized?

Pick  $L_1=L_2=L_{\min}$

One popular sizing strategy:

  1. Pick  $W_1=W_{\min}$  to minimize area of  $M_1$
  2. Pick  $W_2$  to set trip-point at  $V_{DD}/2$
- Observe Case 3 provides expression for  $V_{TRIP}$



Summary:  $V_{TRIP} = \frac{V_{DD}}{2}$  sizing strategy

$$L_1=L_2=L_{\min}$$

$$W_1=W_{\min}$$

$$W_2 = \frac{\mu_n}{\mu_p} W_{\min} \approx 3W_{\min}$$

(dependent upon assumption  $V_{Tp} = -V_{Tn}$ )

Other sizing strategies will be discussed later !

# Digital Circuit Design


- Hierarchical Design
  - Basic Logic Gates
  - Properties of Logic Families
  - Characterization of CMOS Inverter
  - Static CMOS Logic Gates
    - Ratio Logic
      - Propagation Delay
      - Simple analytical models
        - FI/OD
        - Logical Effort
          - Elmore Delay
  - Sizing of Gates
    - The Reference Inverter
- 

- Propagation Delay with Multiple Levels of Logic
- Optimal driving of Large Capacitive Loads
- Power Dissipation in Logic Circuits
- Other Logic Styles
- Array Logic
- Ring Oscillators

→ **done**

→ **partial**


# General Logic Family

 

 **Compound Gate in CMOS Process**

p-channel PUN  
n-channel PDN


$V_H = V_{DD}$ ,  $V_L = 0V$  (same as for inverter!)




**Arbitrary PUN  
and PDN**




# Other MOS Logic Families

 

Enhancement Load  
NMOS


 


Enhancement Load  
Pseudo-NMOS

 


Depletion Load  
NMOS

# Other CMOS/MOS Logic Families

  


# NMOS example

 


Enhancement  
Load NMOS

$V_{TH}$		1
$W_1/L_1$		4
$W_2/L_2$		1
$V_{DD}$		5


Inverter

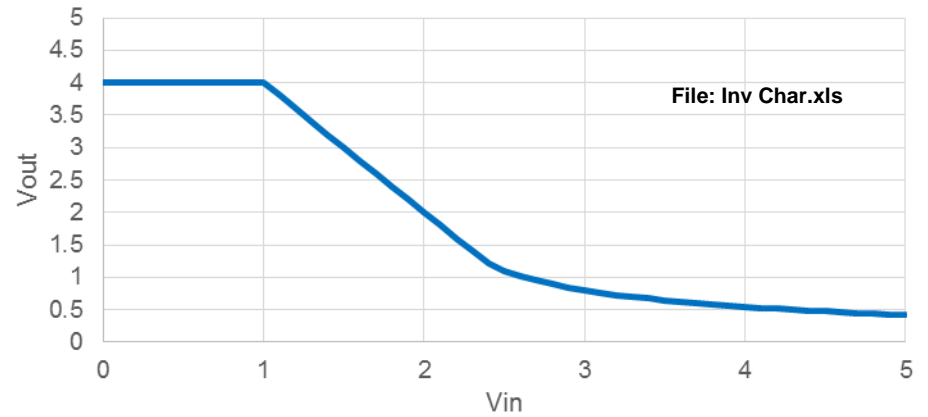

Inverter Pair

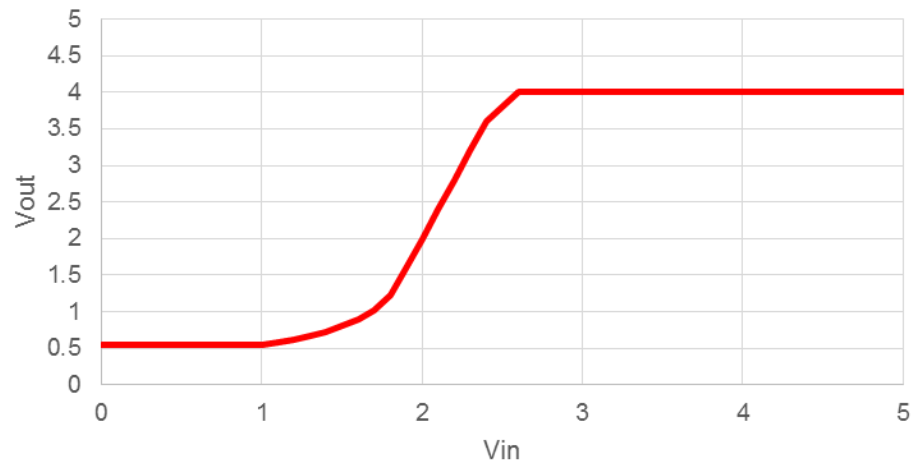


# NMOS example

 

V <sub>TH</sub>	1
W <sub>1</sub> /L <sub>1</sub>	4
W <sub>2</sub> /L <sub>2</sub>	1
V <sub>DD</sub>	5

Inverter Pair


 








 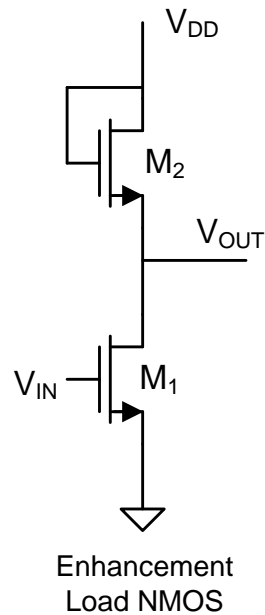

$$V_H = 4V$$

$$V_L = 0.55V$$


$$V_{TRIP} = 2V$$

# Other CMOS/MOS Logic Families




- High and low swings are reduced
- Response time is slow on LH output transitions
- Static Power Dissipation Large when  $V_{OUT}$  is low (will sl 
- Very economical process 
- Termed “ratio logic” (because logic values dependent on device W/L ratios – USE UP DOF!)
- May not work for some device sizes 
- Compact layout (no wells !)
- Can use very low cost process 
- Available to use in standard CMOS process 


# Other CMOS/MOS Logic Families

 

Enhancement  
Load NMOS

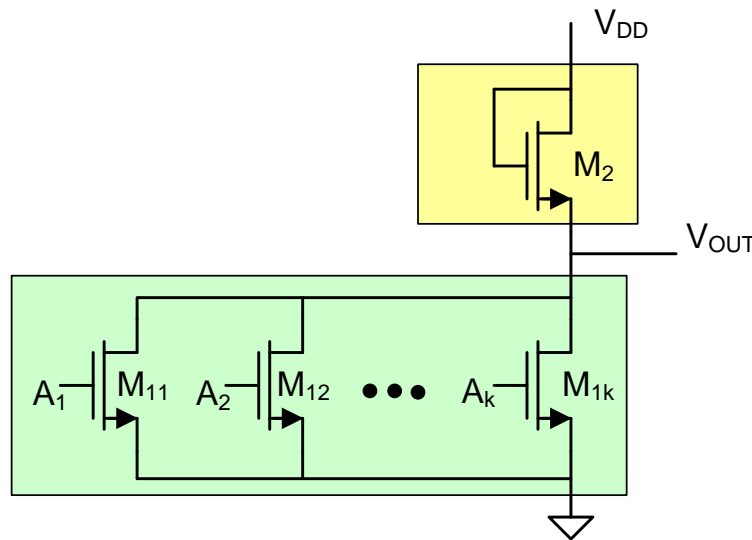

**k-input NOR**

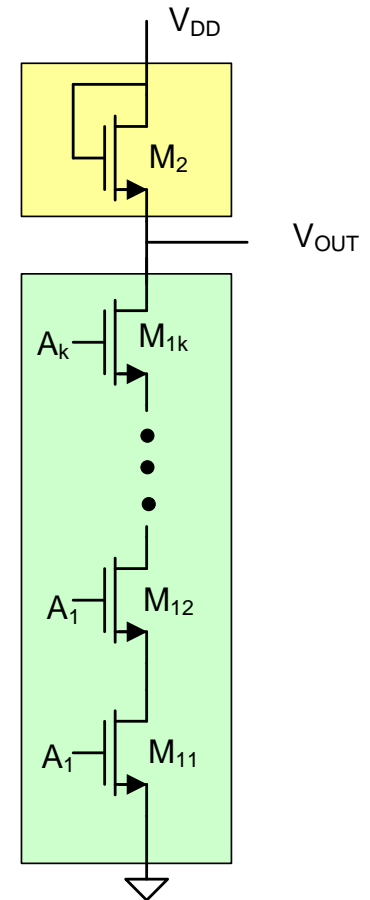

**k-input NAND**



- **Multiple-input gates require single transistor for each additional input**



- **Still useful if many inputs are required**  
(will be shown that static power does not increase with k)




# Other CMOS/MOS Logic Families

 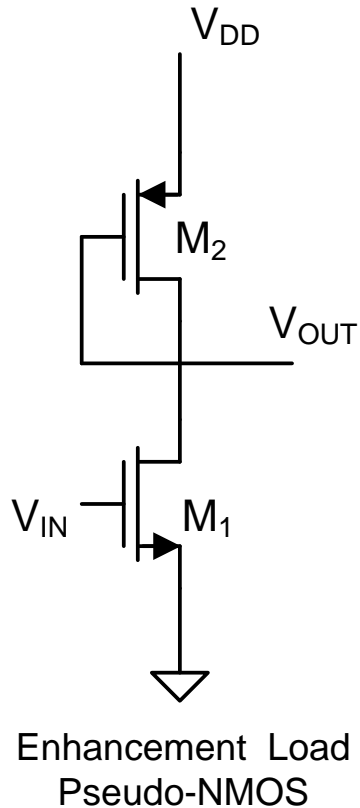


- High and low swings are reduced
- Response time is slow on LH output transitions
- Static Power Dissipation Large when  $V_{OUT}$  is low
- Multiple-input gates require single transistor for each additional input
- Termed “ratio” logic
- Available to use in standard CMOS process



# Other CMOS/MOS Logic Families

 

$V_{TD} < 0$




 


Depletion  
Load NMOS

- **Low swing is degraded** 😞
- **Static Power Dissipation Large when  $V_{OUT}$  is low** 😞
- **Very economical process** 😊
- **Better than Enhancement Load NMOS**
- **Termed “ratio” logic**
- **Compact layout (no wells !)** 😊
- **Response time slow on L-H output transitions** 😞
- **Dominant MOS logic until about 1985**
- **Depletion device not available in most processes today** 😞







# Other CMOS/MOS Logic Families

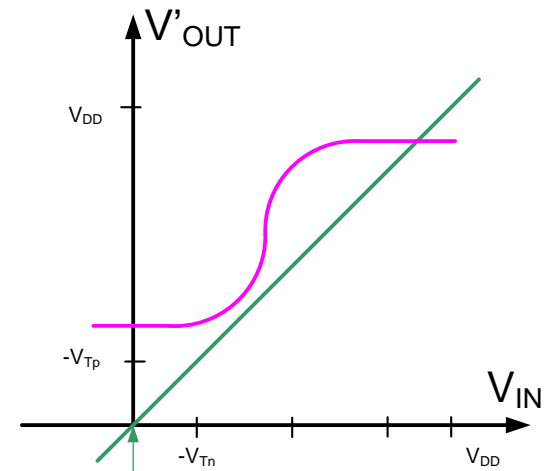 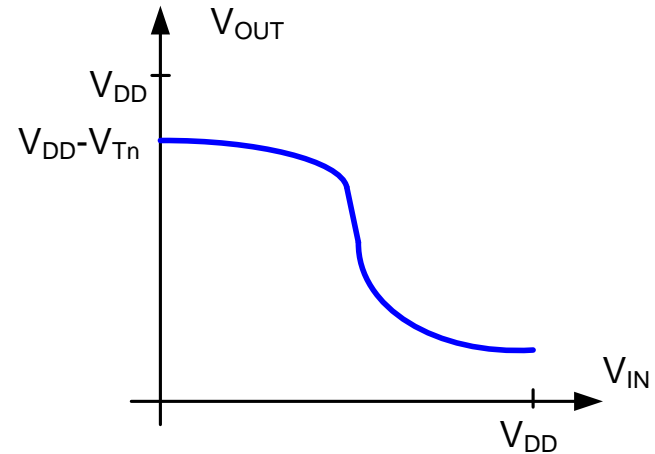 





- **Reduced  $V_H - V_L$**
- **Device sizing critical for even basic operation**
- **Shallow slope at  $V_{TRIP}$**

# Other CMOS/MOS Logic Families

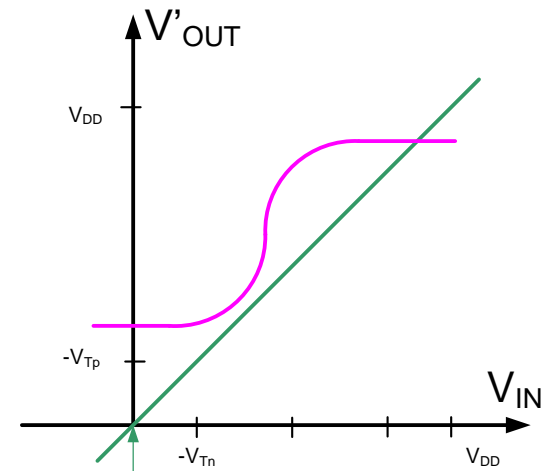  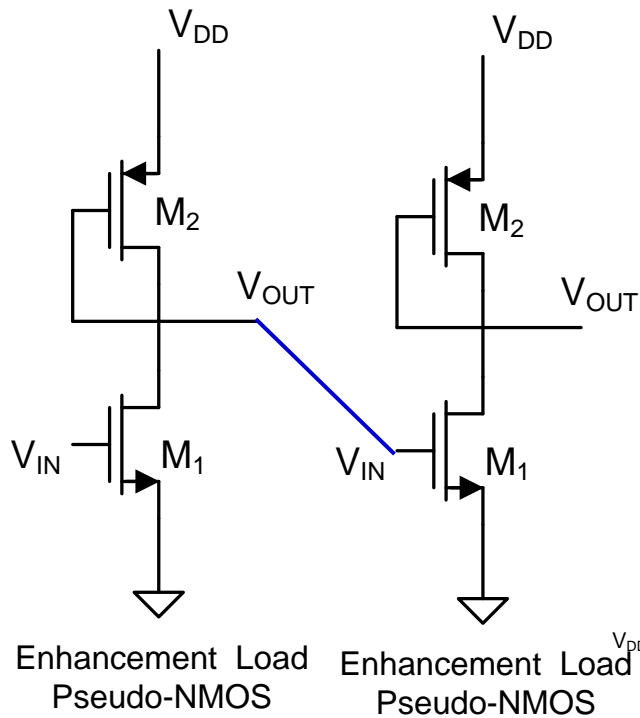

- **Reduced  $V_H - V_L$**
- **Device sizing critical for even basic operation (DOF)**
- **Shallow slope at  $V_{TRIP}$**

# Other CMOS/MOS Logic Families

 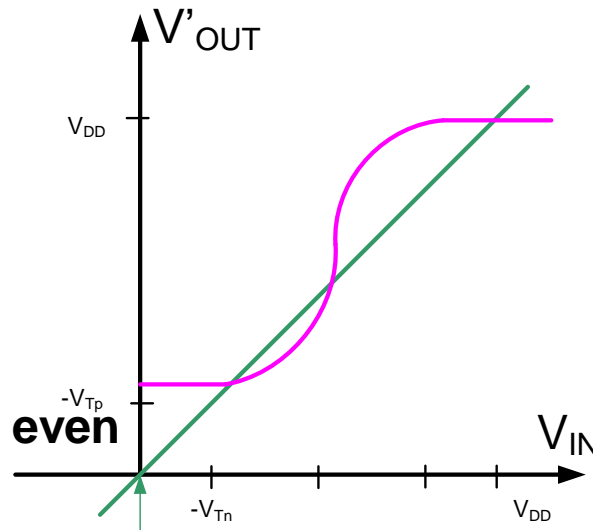 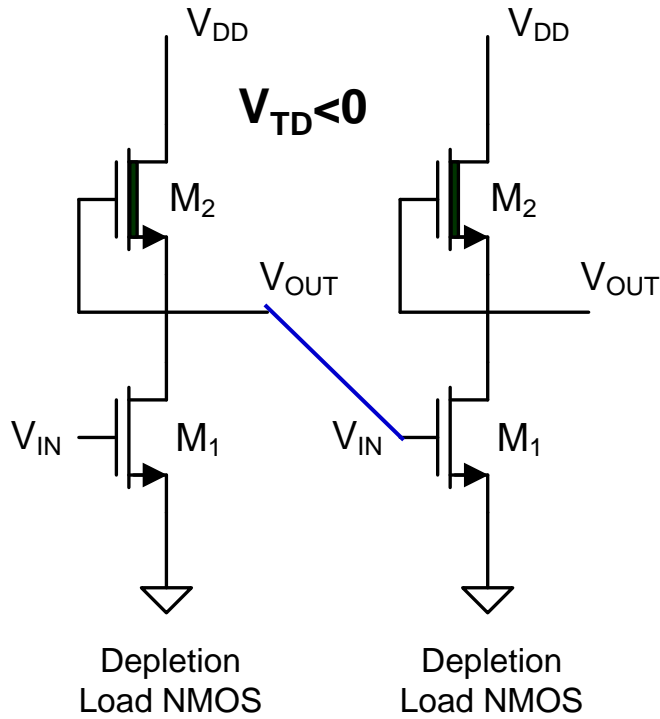

- **Reduced  $V_H - V_L$**
- **Device sizing critical for even basic operation**
- **Shallow slope at  $V_{TRIP}$**

# Digital Circuit Design


- Hierarchical Design
  - Basic Logic Gates
  - Properties of Logic Families
  - Characterization of CMOS Inverter
  - Static CMOS Logic Gates
    - Ratio Logic
  - Propagation Delay
    - Simple analytical models
      - FI/OD
      - Logical Effort
    - Elmore Delay
  - Sizing of Gates
    - The Reference Inverter
- Propagation Delay with Multiple Levels of Logic
  - Optimal driving of Large Capacitive Loads
  - Power Dissipation in Logic Circuits
    - Other Logic Styles
    - Array Logic
    - Ring Oscillators

---

→ **done**

→ **partial**
 
# Static Power Dissipation in Static CMOS Family




When  $V_{IN}$  is Low and  $V_{OUT}$  is High,  $M_1$  is off and  $I_{D1}=0$

When  $V_{IN}$  is High and  $V_{OUT}$  is Low,  $M_2$  is off and  $I_{D2}=0$

Thus,  $P_{STATIC}=0$

 **This is a key property of the static CMOS Logic Family → the major reason Static CMOS Logic is so dominant**




It can be shown that this zero static power dissipation property can be preserved if the PUN is comprised of p-channel devices, the PDN is comprised of n-channel devices and they are never both driven into the conducting states at the same time

Compound Gate in CMOS Process

# Static Power Dissipation in Ratio Logic Families

**Example:**

 

**Assume  $V_{DD}=5V$**

**$V_T=1V$ ,  $\mu C_{OX}=10^{-4}A/V^2$ ,  $W_1/L_1=1$  and  $M_2$  sized so that  $V_L$  is close to  $V_{Tn}$**

**Observe:**

$$V_H = V_{DD} - V_{Tn}$$

**If  $V_{IN}=V_H$ ,  $V_{OUT}=V_L$  so**


$$I_{D1} = \frac{\mu C_{OX} W_1}{L_1} \left( V_{GS1} - V_T - \frac{V_{DS1}}{2} \right) V_{DS1}$$

$$I_{D1} = 10^{-4} \left( 5 - 1 - 1 - \frac{1}{2} \right) \cdot 1 = 0.25mA$$

$$P_L = (5V)(0.25mA) = 1.25mW$$

# Static Power Dissipation in Ratio Logic Families

**Example:**

 

**Assume  $V_{DD}=5V$**


**$V_T=1V$ ,  $\mu C_{OX}=10^{-4}A/V^2$ ,  $W_1/L_1=1$  and  $M_2$  sized so that  $V_L$  is close to  $V_{Tn}$**

$$P_L=(5V)(0.25mA)=1.25mW$$

**If a circuit has 100,000 gates and half of them are in the  $V_{OUT}=V_L$  state, the static power dissipation will be**

# Static Power Dissipation in Ratio Logic Families

Example:

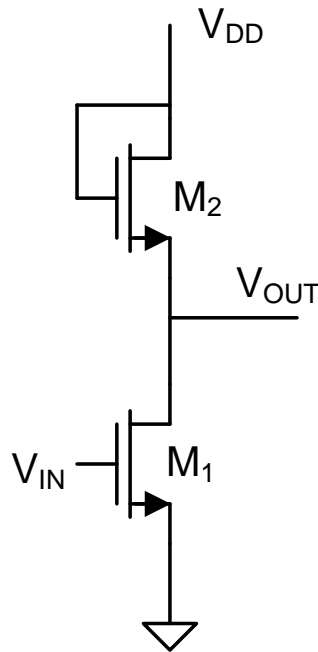

Enhancement  
Load NMOS

Assume  $V_{DD}=5V$

$V_T=1V$ ,  $\mu C_{OX}=10^{-4}A/V^2$ ,  $W_1/L_1=1$  and  $M_2$  sized so that  $V_L$  is close to  $V_{Tn}$

$$P_L=(5V)(0.25mA)=1.25mW$$

If a circuit has 100,000 gates and half of them are in the  $V_{OUT}=V_L$  state, the static power dissipation will be

$$P_{STATIC} = \frac{1}{2} 10^5 \cdot 1.25mW = \mathbf{62.5W}$$

**This power dissipation is way too high and would be even larger in circuits with 100 million or more gates – the level of integration common in SoC circuits today**



# Digital Circuit Design

- Hierarchical Design
- Basic Logic Gates
- Properties of Logic Families
- Characterization of CMOS Inverter
- Static CMOS Logic Gates
  - Ratio Logic
- Propagation Delay
  - Simple analytical models
    - FI/OD
    - Logical Effort
      - Elmore Delay
- Sizing of Gates
  - The Reference Inverter

- Propagation Delay with Multiple Levels of Logic
- Optimal driving of Large Capacitive Loads
- • Power Dissipation in Logic Circuits
- Other Logic Styles
- Array Logic
- Ring Oscillators


---

→ **done**

→ **partial**

# Propagation Delay in Static CMOS Family


(Review from earlier discussions)

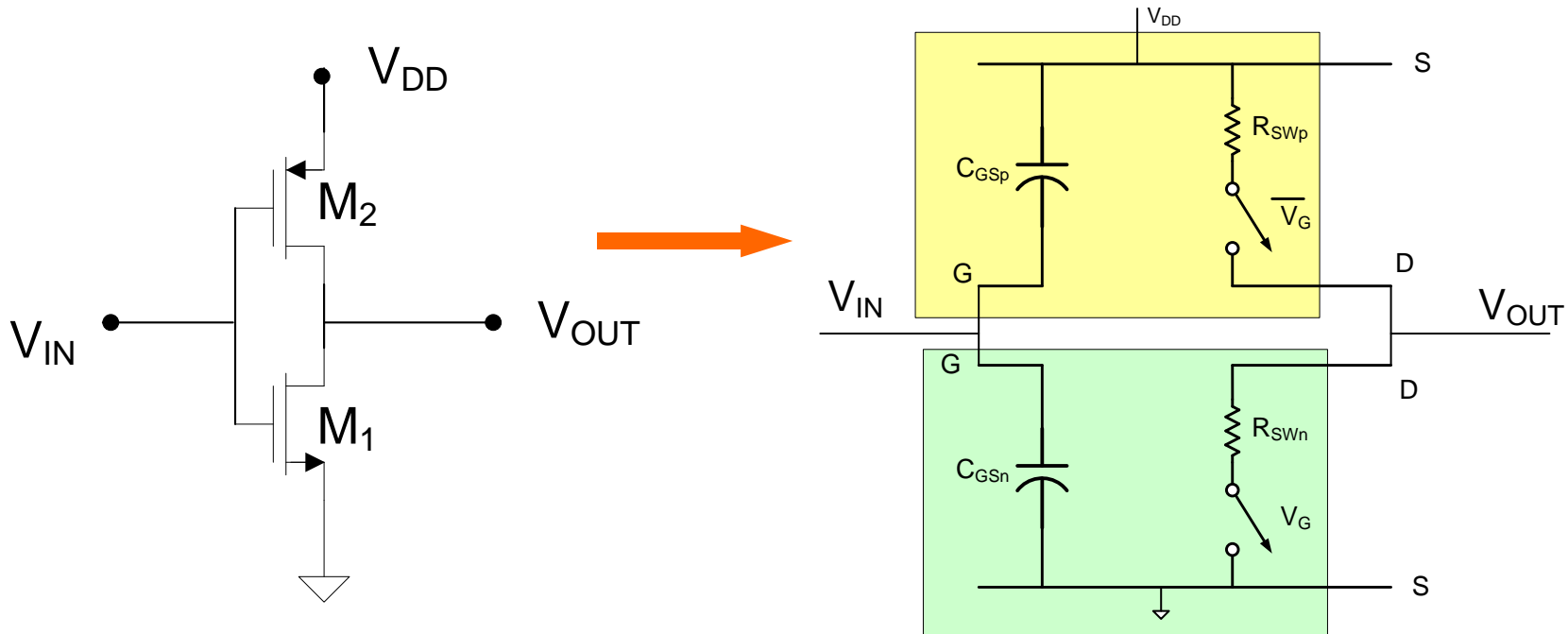

**Switch-level model of Static CMOS inverter (neglecting diffusion parasitics)**

# Propagation Delay in Static CMOS Family



(Review from earlier discussions)

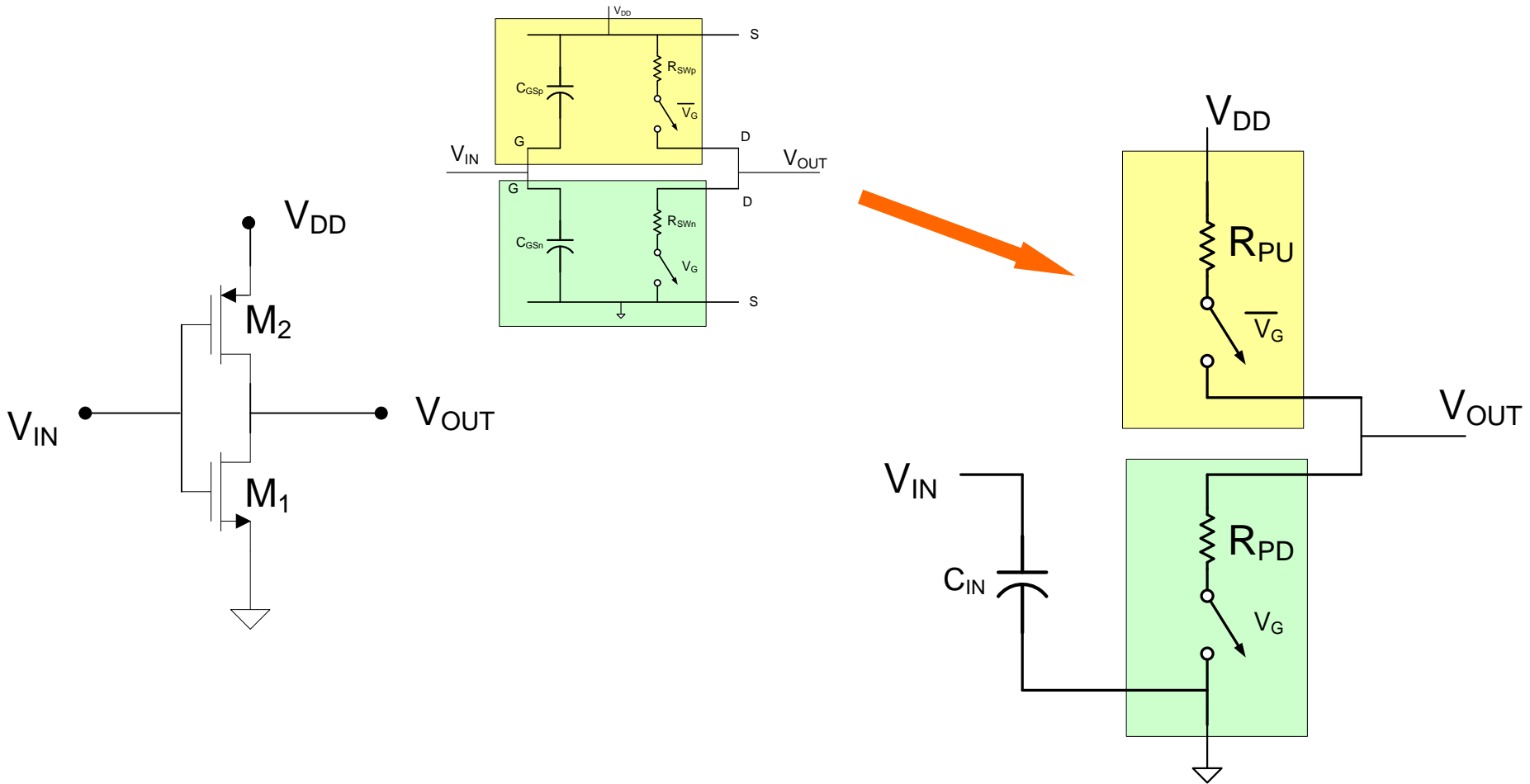

**Switch-level model of Static CMOS inverter (neglecting diffusion parasitics)**

# Propagation Delay in Static CMOS Family

(Review from earlier discussions)

  

Since conducting transistor operating in triode through most of transition:

$$I_D \cong \frac{\mu C_{OX} W}{L} \left( V_{GS} - V_T - \frac{V_{DS}}{2} \right) V_{DS} \cong \frac{\mu C_{OX} W}{L} (V_{GS} - V_T) V_{DS}$$



$$R_{PD} = \frac{V_{DS}}{I_D} = \frac{L_1}{\mu_n C_{OX} W_1 (V_{DD} - V_{Tn})}$$

$$R_{PU} = \frac{V_{DS}}{I_D} = \frac{L_2}{\mu_p C_{OX} W_2 (V_{DD} + V_{Tp})}$$

$$C_{IN} = C_{OX} (W_1 L_1 + W_2 L_2)$$

# Propagation Delay in Static CMOS Family

(Review from earlier discussions)

  

$$R_{PD} = \frac{L_1}{\mu_n C_{OX} W_1 (V_{DD} - V_{Tn})}$$

$$R_{PU} = \frac{L_2}{\mu_p C_{OX} W_2 (V_{DD} + V_{Tp})}$$

$$C_{IN} = C_{OX} (W_1 L_1 + W_2 L_2)$$

## Example: Minimum-sized $M_1$ and $M_2$

If  $\mu_n C_{OX} = 100 \mu A V^{-2}$ ,  $C_{OX} = 4 \text{ fF} \mu^{-2}$ ,  $V_{Tn} = V_{DD}/5$ ,  $V_{Tp} = -V_{DD}/5$ ,  $\mu_n/\mu_p = 3$ ,  $L_1 = W_1 = L_{MIN}$ ,  $L_2 = W_2 = L_{MIN}$ ,  $L_{MIN} = 0.5 \mu$  and  $V_{DD} = 5V$

(Note: This  $C_{OX}$  is somewhat larger than that in the 0.5u ON process)




$$R_{PD} = \frac{1}{10^{-4} \cdot 0.8 V_{DD}} = 2.5 K\Omega$$

$$C_{IN} = 4 \cdot 10^{-15} \cdot 2 L_{MIN}^2 = 2 \text{ fF}$$

$$R_{PU} = \frac{1}{10^{-4} \cdot \frac{1}{3} \cdot 0.8 V_{DD}} = 7.5 K\Omega$$

# Propagation Delay in Static CMOS Family

(Review from earlier discussions)

 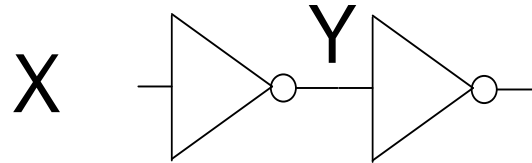 

In typical process with **Minimum-sized  $M_1$  and  $M_2$**  :


$$R_{PD} \cong 2.5K\Omega$$

$$R_{PU} \cong 3R_{PD} = 7.5K\Omega$$

$$C_{IN} \cong 2fF$$

# Propagation Delay in Static CMOS Family

(Review from earlier discussions)

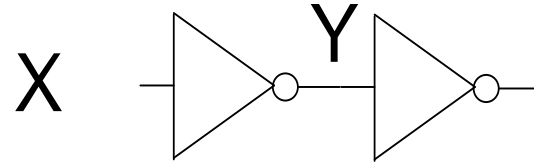


In typical process with **Minimum-sized  $M_1$  and  $M_2$**  :

$$R_{PD} \cong 2.5K\Omega$$

$$R_{PU} \cong 3R_{PD} = 7.5K\Omega$$

$$C_{IN} \cong 2fF$$

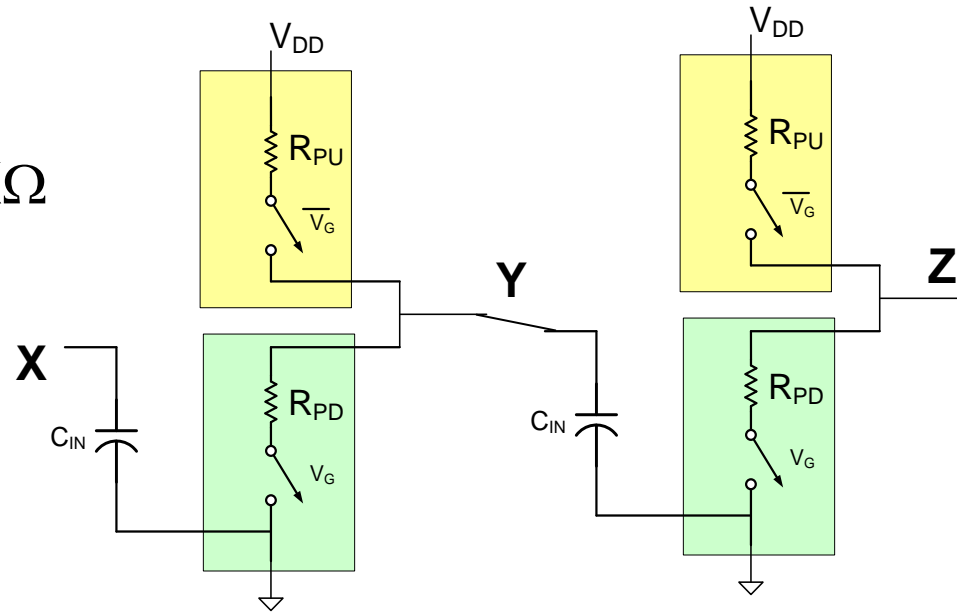


**How long does it take for a signal to propagate from x to y?**

# Propagation Delay in Static CMOS Family


(Review from earlier discussions)

Consider:

 For HL output transition,  $C_L$  charged to  $V_{DD}$



Ideally:

 





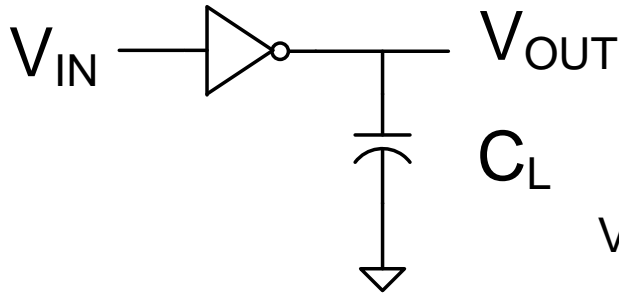
# Propagation Delay in Static CMOS Family

(Review from earlier discussions)

For HL output transition,  $C_L$  charged to  $V_{DD}$





Actually:

  

What is the transition time  $t_{HL}$  ?

# Propagation Delay in Static CMOS Family





(Review from earlier discussions)

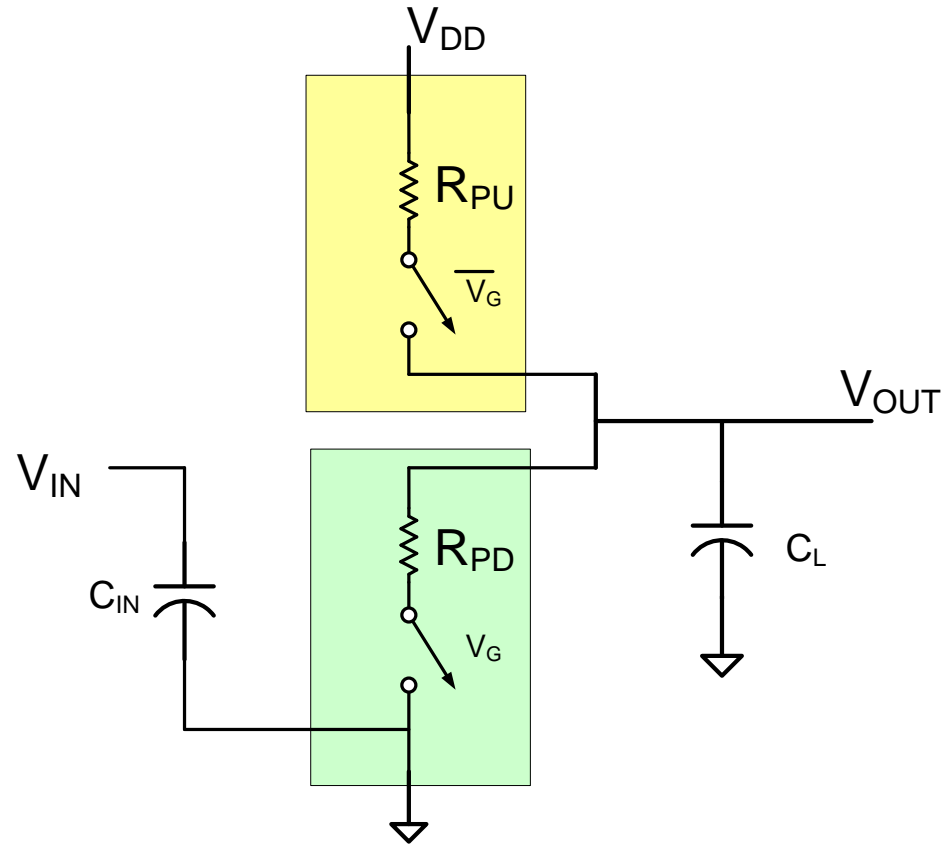 
    
# Propagation Delay in Static CMOS Family

(Review from earlier discussions)

For HL output transition,  $C_L$  charged to  $V_{DD}$



$$V_{OUT}(t) = F + (I - F)e^{\frac{-t}{\tau}} = 0 + (V_{DD} - 0)e^{\frac{-t}{R_{PD}C_L}}$$





$$\frac{V_{DD}}{e} = V_{DD}e^{\frac{-t_1}{R_{PD}C_L}} \quad \longrightarrow \quad t_1 = R_{PD}C_L$$

If  $V_{TRIP}$  is close to  $V_{DD}/2$ ,  $t_{HL}$  is close to  $t_1$
    
# Propagation Delay in Static CMOS Family

(Review from earlier discussions)

For HL output transition,  $C_L$  charged to  $V_{DD}$



$$t_{LH} \cong t_2 = R_{PU} C_L$$



**Summary:**  $t_{LH} \cong R_{PU} C_L$

$$t_{HL} \cong R_{PD} C_L$$

For  $V_{TRIP}$  close to  $V_{DD}/2$

# Propagation Delay in Static CMOS Family

(Review from earlier discussions)

  

In typical process with **Minimum-sized  $M_1$  and  $M_2$**  :

$$t_{HL} \cong R_{PD}C_L \cong 2.5K \cdot 2fF = 5ps$$

$$t_{LH} \cong R_{PU}C_L \cong 7.5K \cdot 2fF = 15ps$$

(Note: This  $C_{ox}$  is somewhat larger than that in the 0.5u ON process)

**Note: LH transition is much slower than HL transition**


# Propagation Delay in Static CMOS Family

**Defn:** The Propagation Delay of a gate is defined to be the sum of  $t_{HL}$  and  $t_{LH}$ , that is,  $t_{PROP} = t_{HL} + t_{LH}$

$$t_{PROP} = t_{HL} + t_{LH} \cong C_L (R_{PU} + R_{PD})$$

Propagation delay represents a fundamental limit on the speed a gate can be clocked at

 For basic two-inverter cascade in static 0.5um CMOS logic



# Propagation Delay in Static CMOS Family

$$t_{PROP} = t_{HL} + t_{LH} \cong C_L (R_{PU} + R_{PD})$$

$$R_{PD} = \frac{L_1}{\mu_n C_{OX} W_1 (V_{DD} - V_{Tn})} \quad R_{PU} = \frac{L_2}{\mu_p C_{OX} W_2 (V_{DD} + V_{Tp})} \quad C_{IN} = C_{OX} (W_1 L_1 + W_2 L_2)$$

$$\text{If } V_{Tn} = -V_{Tp} = V_T$$

$$t_{PROP} = C_{OX} (W_1 L_1 + W_2 L_2) \left( \frac{L_1}{\mu_n C_{OX} W_1 (V_{DD} - V_T)} + \frac{L_2}{\mu_p C_{OX} W_2 (V_{DD} - V_T)} \right)$$

$$\text{If } L_2 = L_1 = L_{min}, \mu_n = 3\mu_p,$$

$$t_{PROP} = \frac{L_{min}^2}{\mu_n (V_{DD} - V_T)} (W_1 + W_2) \left( \frac{1}{W_1} + \frac{3}{W_2} \right) = \frac{L_{min}^2}{\mu_n (V_{DD} - V_T)} \left( 4 + \frac{W_2}{W_1} + 3 \frac{W_1}{W_2} \right)$$

Note speed is a function of device sizing !

Can  $t_{PROP}$  be minimized?

# Propagation Delay in Static CMOS Family

For  $L_2 = L_1 = L_{\min}$ ,  $\mu_n = 3\mu_p$ ,

$$t_{PROP} = \frac{L_{\min}^2}{\mu_n (V_{DD} - V_T)} \left( 4 + \frac{W_2}{W_1} + 3 \frac{W_1}{W_2} \right)$$

Can  $t_{PROP}$  be minimized?

Assume  $W_1 = W_{\min}$

$$\frac{\partial t_{PROP}}{\partial W_2} = \left[ \frac{L_{\min}^2}{\mu_n (V_{DD} - V_{TH})} \right] \left[ \frac{1}{W_{\min}} - 3 \frac{W_{\min}}{W_2^2} \right] = 0$$

$$\frac{1}{W_{\min}} - 3 \frac{W_{\min}}{W_2^2} = 0$$

$$W_2 = \sqrt{3} W_{\min}$$

$$t_{PROP} = \frac{L_{\min}^2}{\mu_n (V_{DD} - V_T)} (4 + 2\sqrt{3}) \cong \frac{L_{\min}^2}{\mu_n (V_{DD} - V_T)} (7.5) \quad (7.5)$$



# Propagation Delay in Static CMOS Family

$$t_{\text{PROP}} = t_{\text{HL}} + t_{\text{LH}} \cong C_L (R_{\text{PU}} + R_{\text{PD}})$$

$$R_{\text{PD}} = \frac{L_1}{\mu_n C_{\text{OX}} W_1 (V_{\text{DD}} - V_{\text{Tn}})} \quad R_{\text{PU}} = \frac{L_2}{\mu_p C_{\text{OX}} W_2 (V_{\text{DD}} + V_{\text{Tp}})} \quad C_{\text{IN}} = C_{\text{OX}} (W_1 L_1 + W_2 L_2)$$

If  $V_{\text{Tn}} = -V_{\text{Tp}} = V_{\text{T}}$

$$t_{\text{PROP}} = C_{\text{OX}} (W_1 L_1 + W_2 L_2) \left( \frac{L_1}{\mu_n C_{\text{OX}} W_1 (V_{\text{DD}} - V_{\text{T}})} + \frac{L_2}{\mu_p C_{\text{OX}} W_2 (V_{\text{DD}} - V_{\text{T}})} \right)$$

If  $L_2 = L_1 = L_{\text{min}}, \mu_n = 3\mu_p,$

$$t_{\text{PROP}} = \frac{L_{\text{min}}^2}{\mu_n (V_{\text{DD}} - V_{\text{T}})} (W_1 + W_2) \left( \frac{1}{W_1} + \frac{3}{W_2} \right) = \frac{L_{\text{min}}^2}{\mu_n (V_{\text{DD}} - V_{\text{T}})} \left( 4 + \frac{W_2}{W_1} + 3 \frac{W_1}{W_2} \right)$$

For min size:

$$W_2 = W_1 = W_{\text{min}}$$

$$t_{\text{PROP}} = \frac{8L_{\text{min}}^2}{\mu_n (V_{\text{DD}} - V_{\text{T}})}$$

For equal rise/fall:

$$W_2 = 3W_1$$

$$t_{\text{PROP}} = \frac{8L_{\text{min}}^2}{\mu_n (V_{\text{DD}} - V_{\text{T}})}$$


For min delay:

$$W_2 = \sqrt{3}W_1$$

$$t_{\text{PROP}} = \frac{(4 + 2\sqrt{3})L_{\text{min}}^2}{\mu_n (V_{\text{DD}} - V_{\text{T}})} \quad (4 + 2\sqrt{3}) \cong 7.5$$

**Propagation Delay About the Same for 3 Sizing Strategies**

 
# Propagation Delay in Static CMOS Family



**The propagation delay through k levels of logic is approximately the sum of the individual propagation delays in the same path**

# Propagation Delay in Static CMOS Family

Example:

 

$$t_{HL} = t_{HL4} + t_{LH3} + t_{HL2} + t_{LH1}$$


$$t_{LH} = t_{LH4} + t_{HL3} + t_{LH2} + t_{HL1}$$

$$t_{PROP} = t_{LH} + t_{HL} = (t_{LH4} + t_{HL3} + t_{LH2} + t_{HL1}) + (t_{HL4} + t_{LH3} + t_{HL2} + t_{LH1})$$

$$t_{PROP} = t_{LH} + t_{HL} = (t_{LH4} + t_{HL4}) + (t_{LH3} + t_{HL3}) + (t_{LH2} + t_{HL2}) + (t_{LH1} + t_{HL1})$$

$$t_{PROP} = t_{PROP4} + t_{PROP3} + t_{PROP2} + t_{PROP1}$$
 
# Propagation Delay in Static CMOS Family



## Propagation through k levels of logic

$$t_{HL} \cong t_{HLk} + t_{LH(k-1)} + t_{HL(k-2)} + \dots + t_{XY1}$$

$$t_{LH} \cong t_{LHk} + t_{HL(k-1)} + t_{LH(k-2)} + \dots + t_{YX1}$$

where X=H and Y=L if k odd and X=L and Y=h if k even

$$t_{PROP} = \sum_{i=1}^k t_{PROP_i}$$

Will return to propagation delay after we discuss device sizing

# Digital Circuit Design

- Hierarchical Design
  - Basic Logic Gates
  - Properties of Logic Families
  - Characterization of CMOS Inverter
  - Static CMOS Logic Gates
    - Ratio Logic
    - Propagation Delay
      - Simple analytical models
        - FI/OD
        - Logical Effort
          - Elmore Delay
  - Sizing of Gates
    - The Reference Inverter
- Propagation Delay with Multiple Levels of Logic
  - Optimal driving of Large Capacitive Loads
  - Power Dissipation in Logic Circuits
  - Other Logic Styles
  - Array Logic
  - Ring Oscillators

---

→ **done**

→ **partial**

Observation:

$$|V_{T_p}| \approx V_{T_n} \approx V_{DD}/5 \text{ in many processes}$$




Question:



Why is  $|V_{T_p}| \approx V_{T_n} \approx V_{DD}/5$  in many processes ?



# Device Sizing

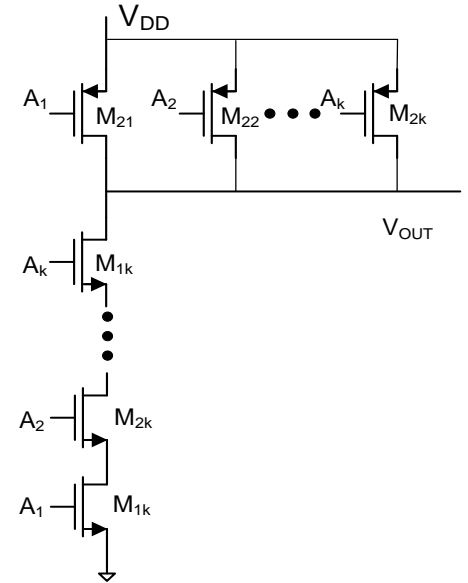  


**Strategies?**

**Degrees of Freedom?**

**Will consider the inverter first**

# Device Sizing

 


**Degrees of Freedom?**

**Strategies?**


 
# Device Sizing

- Since not ratio logic,  $V_H$  and  $V_L$  are independent of device sizes for this inverter
- With  $L_1=L_2=L_{\min}$ , there are 2 degrees of freedom ( $W_1$  and  $W_2$ )



## Sizing Strategies


- **Minimum Size**
- **Fixed  $V_{TRIP}$**
- **Equal rise-fall times**  
(equal worst-case rise and fall times)
- **Minimum power dissipation**
- **Minimum time required to drive a given load**
- **Minimum input capacitance**

# Device Sizing

Assume  $V_{Tn}=0.2V_{DD}$ ,  $V_{Tp}=-0.2V_{DD}$ ,  $\mu_n/\mu_p=3$ ,  $L_1=L_2=L_{min}$

Sizing Strategy: minimum sized

 $W_n=?$ ,  $W_p=?$ ,  $V_{trip}=?$ ,  $t_{HL}=?$ ,  $t_{LH}=?$



$$R_{PD} = \frac{L_1}{\mu_n C_{OX} W_1 (V_{DD} - V_{Tn})}$$

$$R_{PU} = \frac{L_2}{\mu_p C_{OX} W_2 (V_{DD} + V_{Tp})}$$

$$C_{IN} = C_{OX} (W_1 L_1 + W_2 L_2)$$

# Device Sizing

Assume  $V_{Tn}=0.2V_{DD}$ ,  $V_{Tp}=-0.2V_{DD}$ ,  $\mu_n/\mu_p=3$ ,  $L_1=L_2=L_{min}$

Sizing Strategy: minimum sized

$W_n=?$ ,  $W_p=?$ ,  $V_{trip}=?$ ,  $t_{HL}=?$ ,  $t_{LH}=?$

$$W_1=W_2=W_{MIN}$$

also provides minimum input capacitance

It follows that  $R_{PU} = \mu_n/\mu_p R_{PD}$

$$t_{HL} = R_{PD} C_L$$


$$t_{LH} = 3 R_{PD} C_L$$

$t_{LH}$  is longer than  $t_{HL}$

$$t_{PROP} = 4 R_{PD} C_L$$

$$V_{TRIP} = \frac{(V_{Tn}) + (V_{DD} + V_{Tp}) \sqrt{\frac{\mu_p}{\mu_n} \frac{W_2 L_1}{W_1 L_2}}}{1 + \sqrt{\frac{\mu_p}{\mu_n} \frac{W_2 L_1}{W_1 L_2}}}$$
 
$$V_{TRIP} = \frac{(0.2V_{DD}) + (V_{DD} - 0.2V_{DD}) \sqrt{\frac{1}{3}}}{1 + \sqrt{\frac{1}{3}}} = .42V_{DD}$$




# Device Sizing

Assume  $V_{Tn}=0.2V_{DD}$ ,  $V_{Tp}=-0.2V_{DD}$ ,  $\mu_n/\mu_p=3$ ,  $L_1=L_2=L_{min}$

Sizing strategy: Equal (worst case) rise and fall times

 $W_n=?$ ,  $W_p=?$ ,  $V_{trip}=?$ ,  $t_{HL}=?$ ,  $t_{LH}=?$




$$R_{PD} = \frac{L_{min}}{\mu_n C_{OX} W_1 (0.8V_{DD})}$$

$$R_{PU} = \frac{L_{min}}{3\mu_n C_{OX} W_2 (0.8V_{DD})}$$

# Device Sizing

Assume  $V_{Tn}=0.2V_{DD}$ ,  $V_{Tp}=-0.2V_{DD}$ ,  $\mu_n/\mu_p=3$ ,  $L_1=L_2=L_{min}$

 **Sizing strategy: Equal (worst case) rise and fall times**



$$\frac{t_{LH}}{t_{HL}} = 1 = \frac{R_{PU} C_{IN}}{R_{PD} C_{IN}} \Rightarrow R_{PU} = R_{PD}$$

Thus

$$\frac{L_1}{u_n C_{OX} W_1 (V_{DD} - V_{Tn})} = \frac{L_2}{u_p C_{OX} W_2 (V_{DD} + V_{Tp})}$$

with  $L_1=L_2$  and  $V_{Tp}=-V_{Tn}$  we must have

$$\frac{W_2}{W_1} = \frac{\mu_n}{\mu_p} \approx 3$$

What about the second degree of freedom?

$$W_1 = W_{MIN} \quad (\text{could be something else})$$


$$V_{TRIP} = ?$$

# Device Sizing

Assume  $V_{Tn}=0.2V_{DD}$ ,  $V_{Tp}=-0.2V_{DD}$ ,  $\mu_n/\mu_p=3$ ,  $L_1=L_2=L_{min}$

Sizing strategy: Equal (worst-case) rise and fall times

 $W_n=W_{MIN}, W_p=3W_{MIN}, V_{trip}=?, t_{HL}=?, t_{LH}=?$



$$V_{TRIP} = \frac{(V_{Tn}) + (V_{DD} + V_{Tp}) \sqrt{\frac{\mu_p W_2 L_1}{\mu_n W_1 L_2}}}{1 + \sqrt{\frac{\mu_p W_2 L_1}{\mu_n W_1 L_2}}} = \frac{0.2V_{DD} + 0.8V_{DD}}{2} = \frac{V_{DD}}{2}$$

$$t_{HL} = t_{LH} = R_{pd} C_L = \frac{L_{min}}{\mu_n C_{OX} W_{min} (0.8V_{DD})} C_L$$

$$t_{PROP} = 2 R_{pd} C_L$$


For a fixed  $C_L$ , how does  $t_{prop}$  compare for the minimum-sizing compared to equal rise/fall sizing?

# Device Sizing

Assume  $V_{Tn}=0.2V_{DD}$ ,  $V_{Tp}=-0.2V_{DD}$ ,  $\mu_n/\mu_p=3$ ,  $L_1=L_2=L_{min}$

Sizing strategy: Fixed  $V_{TRIP}=V_{DD}/2$  (Could have other  $V_{TRIP}$ )

 $W_n=?$ ,  $W_p=?$ ,  $V_{trip}=?$ ,  $t_{HL}=?$ ,  $t_{LH}=?$




# Device Sizing

Assume  $V_{Tn}=0.2V_{DD}$ ,  $V_{Tp}=-0.2V_{DD}$ ,  $\mu_n/\mu_p=3$ ,  $L_1=L_2=L_{min}$

Sizing strategy: Fixed  $V_{TRIP}=V_{DD}/2$

 $W_n=?$ ,  $W_p=?$ ,  $V_{trip}=?$ ,  $t_{HL}=?$ ,  $t_{LH}=?$



Set

$$V_{TRIP}=V_{DD}/2$$

$$V_{TRIP} = \frac{(.2V_{DD}) + (V_{DD} - .2V_{DD}) \sqrt{\frac{\mu_p W_2 L_1}{\mu_n W_1 L_2}}}{1 + \sqrt{\frac{\mu_p W_2 L_1}{\mu_n W_1 L_2}}} = \frac{V_{DD}}{2}$$

Solving, obtain

$$\frac{W_2}{W_1} = \frac{\mu_n}{\mu_p}$$


$$W_n=W_{MIN}, \quad W_p=3W_{MIN}$$

- This is the same sizing as was obtained for equal worst-case rise and fall times so  $t_{HL}=t_{LH}=R_{pd}C_L$
- This is no coincidence !!! Why?
- These properties guide the definition of the process parameters provided by the foundry


 
# Device Sizing

Assume  $V_{Tn}=0.2V_{DD}$ ,  $V_{Tp}=-0.2V_{DD}$ ,  $\mu_n/\mu_p=3$ ,  $L_1=L_2=L_{min}$




## Sizing Strategies

- **Minimum Size**
- **Fixed  $V_{TRIP}$  ( $V_{TRIP}=V_{DD}/2$ )**
- **Equal rise-fall times (equal worst-case rise and fall times)**
- **Minimum power dissipation**
- **Minimum time required to drive a given load**
- **Minimum input capacitance**

# Device Sizing

Assume  $V_{Tn}=0.2V_{DD}$ ,  $V_{Tp}=-0.2V_{DD}$ ,  $\mu_n/\mu_p=3$ ,  $L_1=L_2=L_{min}$

## Sizing Strategy Summary

 

	Minimum Size	$V_{TRIP}=V_{DD}/2$	Equal Rise/Fall
Size	$W_n=W_p=W_{min}$ $L_p=L_n=L_{min}$	$W_n=W_{min}$ $W_p=3W_{min}$ $L_p=L_n=L_{min}$	$W_n=W_{min}$ $W_p=3W_{min}$ $L_p=L_n=L_{min}$
$t_{HL}$	$R_{pd}C_L$	$R_{pd}C_L$	$R_{pd}C_L$
$t_{LH}$	$3R_{pd}C_L$	$R_{pd}C_L$	$R_{pd}C_L$
$t_{PROP}$	$4R_{pd}C_L$	$2R_{pd}C_L$	$2R_{pd}C_L$
$V_{trip}$	$V_{TRIP}=0.42V_{DD}$	$V_{TRIP}=0.5V_{DD}$	$V_{TRIP}=0.5V_{DD}$

- For a fixed load  $C_L$ , the minimum-sized structure has a higher  $t_{PROP}$  but if the load is another inverter,  $C_L$  will also change so the speed improvements become less apparent
- This will be investigated later

# Question:

?

?

?

?

?

Why is  $|V_{Tp}| \approx V_{Tn} \approx V_{DD}/5$  in many processes ?

?

?

?

?



**Stay Safe and Stay Healthy !**

**End of Lecture 39**