

EE 330

Lecture 41

Digital Circuits

Overdrive Factors

Propagation Delay With Multiple Levels of Logic

Exam Schedule

Exam 1	Friday Sept 24
Exam 2	Friday Oct 22
Exam 3	Friday Nov 19
Final	Tues Dec 14 12:00 p.m.

Photo courtesy of the director of the National Institute of Health (NIH)



As a courtesy to fellow classmates, TAs, and the instructor

Wearing of masks during lectures and in the laboratories for this course would be appreciated irrespective of vaccination status

Final Tues Dec 14 (scheduled 12:00 pm)


Final Exam will be distributed by 8:00 AM on the day of exam and due on Canvas at 2:15 PM

This will be structured as a 2-hour in-person exam following the same format as the final exam from previous semesters that are posted on the class website.

Students will be expected to comply with the honor system as stipulated on previous exams in this course. If anyone is unwilling to comply with the honor system, please let me know by Friday December 10 so that alternative arrangements can be made for taking the final exam. A grade of 0 along with other sanctions will be assessed for anyone that does not comply with the honor system on this exam.

The Reference Inverter

Reference Inverter

 

Assume $\mu_n/\mu_p=3$

$W_n=W_{MIN}$, $W_p=3W_{MIN}$

$L_n=L_p=L_{MIN}$

In 0.5u proc $t_{REF}=20ps$,

$C_{REF}=4fF$, $R_{PDREF}=R_{PUREF}=2.5K$

$$R_{PDREF}=R_{PUREF}$$

$$C_{REF}=C_{IN}=4C_{OX}W_{MIN}L_{MIN}$$

$$R_{PDREF}=\frac{L_{MIN}}{\mu_n C_{OX} W_{MIN} (V_{DD}-V_{Tn})} \stackrel{V_{Tn}=.2V_{DD}}{=} \frac{L_{MIN}}{\mu_n C_{OX} W_{MIN} (0.8V_{DD})}$$

$$t_{HLREF}=t_{LHREF}=R_{PDREF}C_{REF}$$

$$t_{REF}=t_{HLREF}+t_{LHREF}=2R_{PDREF}C_{REF}$$

(Note: This C_{OX} is somewhat larger than that in the 0.5u ON process)


Device Sizing

Equal Worst-Case Rise/Fall Device Sizing Strategy

-- (same as $V_{TRIP}=V_{DD}/2$ for worst case delay in typical process considered in example)

Assume $\mu_n/\mu_p=3$ **How many degrees of freedom were available?**

$L_n=L_p=L_{MIN}$

 


INV

$W_n=W_{MIN}, W_p=3W_{MIN}$

$C_{IN}=C_{REF}$

$FI=1$

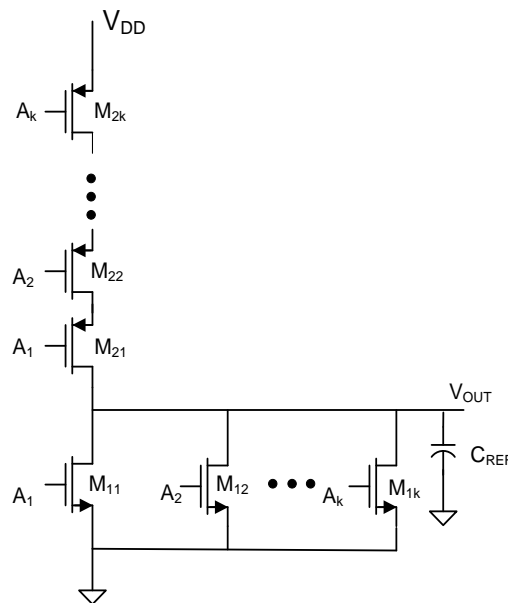


k-input NOR

$W_n=W_{MIN}, W_p=3kW_{MIN}$

$C_{IN}=\left(\frac{3k+1}{4}\right)C_{REF}$

$FI=\left(\frac{3k+1}{4}\right)$

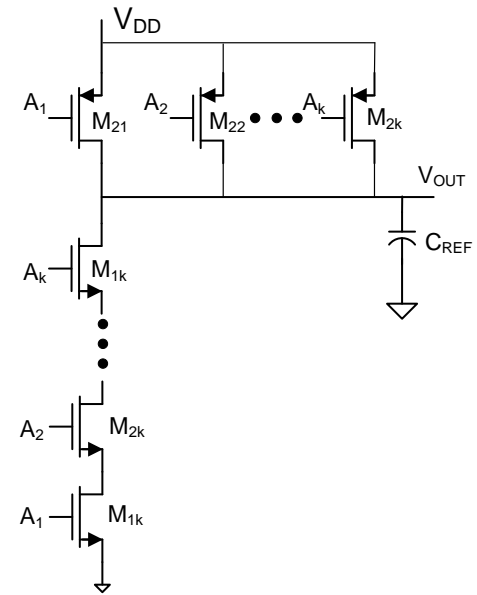

k-input NAND

$W_n=kW_{MIN}, W_p=3W_{MIN}$


$C_{IN}=\left(\frac{3+k}{4}\right)C_{REF}$

$FI=\left(\frac{3+k}{4}\right)$


Device Sizing

Multiple Input Gates:


2-input NOR

 


2-input NAND

 

k-input NOR

 

k-input NAND

 

Equal Worst Case Rise/Fall (and equal to that of ref inverter when driving C_{REF})

$W_n=?$

$W_p=?$

Fastest response (t_{HL} or t_{LH}) = ?

Worst case response (t_{PROP} , usually of most interest)?

Input capacitance (FI) = ?

Minimum Sized (assume driving a load of C_{REF})

$W_n=W_{min}$

$W_p=W_{min}$


Fastest response (t_{HL} or t_{LH}) = ?

Slowest response (t_{HL} or t_{LH}) = ?


Worst case response (t_{PROP} , usually of most interest)?

Input capacitance (FI) = ?

 
Device Sizing – minimum size driving C_{REF}



INV

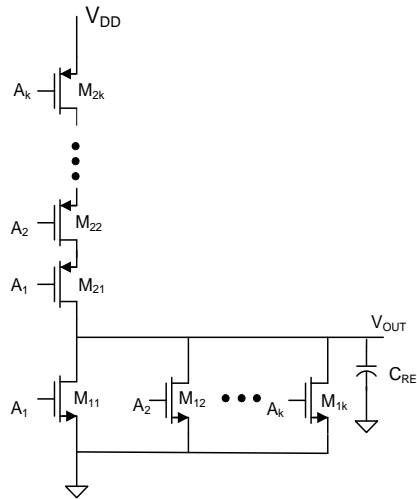

k-input NOR

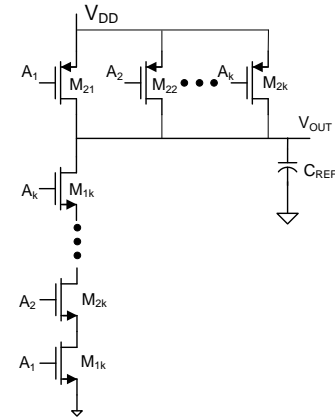

k-input NAND

worst case

$$t_{PROP} = 0.5t_{REF} + \frac{3}{2}t_{REF}$$

$$t_{PROP} = 2t_{REF}$$

$$t_{PROP} = 0.5t_{REF} + \frac{3k}{2}t_{REF}$$

$$t_{PROP} = \left(\frac{3k+1}{2}\right)t_{REF}$$

$$t_{PROP} = \frac{3}{2}t_{REF} + \frac{k}{2}t_{REF}$$

$$t_{PROP} = \frac{3+k}{2}t_{REF}$$

$$\frac{1+3k^2}{2k}t_{REF} \leq t_{PROP} \leq \frac{3k+1}{2}t_{REF}$$

$$\frac{3+k^2}{2k}t_{REF} \leq t_{PROP} \leq \frac{3+k}{2}t_{REF}$$

$$FI = \frac{C_{REF}}{2}$$

$$FI = \frac{C_{REF}}{2}$$

$$FI = \frac{C_{REF}}{2}$$

$$R_{PU} = 3R_{PDREF}$$

$$\frac{R_{PDREF}}{k} \leq R_{PD} \leq R_{PDREF}$$


$$\frac{3R_{PDREF}}{k} \leq R_{PU} \leq 3R_{PDREF}$$

$$R_{PD} = R_{PDREF}$$


$$R_{PU} = 3kR_{PDREF}$$

$$R_{PD} = kR_{PDREF}$$


Device Sizing Summary

 

INV

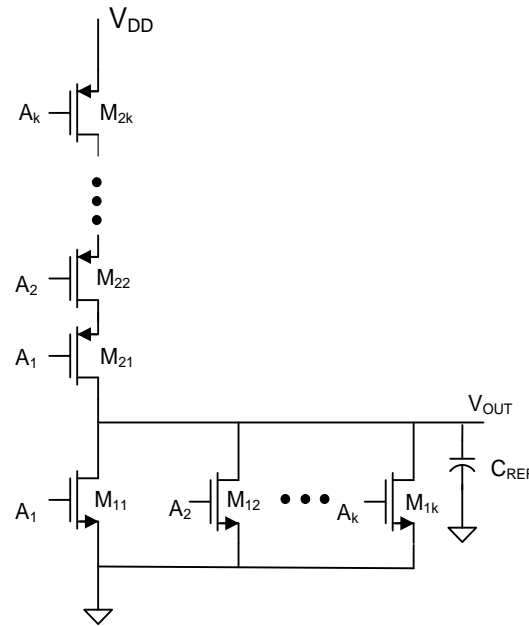

k-input NOR

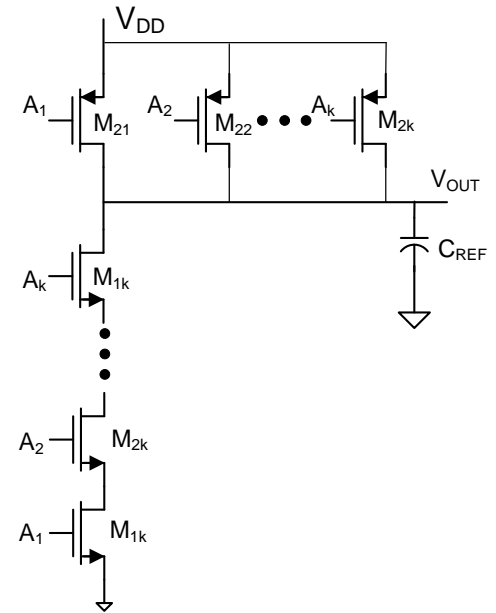


k-input NAND

C_{IN} for N_{AND} gates is considerably smaller than for NOR gates for equal worst-case rise and fall times

C_{IN} for minimum-sized structures is independent of number of inputs and much smaller than C_{IN} for the equal rise/fall time case

R_{PU} gets very large for minimum-sized NOR gate

Propagation Delay with Stage Loading

 

$$t_{REF} = 2R_{PDref} C_{REF}$$

$$C_{REF} = 4C_{OX} W_{MIN} L_{MIN}$$

FI of a capacitor

$$FI_C = \frac{C}{C_{REF}}$$

FI of a gate (input k)

$$FI_G = \frac{C_{INK}}{C_{REF}}$$

FI of an interconnect

$$FI_I = \frac{C_{INI}}{C_{REF}}$$

Overall FI

$$FI = \frac{\sum_{Gates} C_{INGi} + \sum_{Capacitances} C_{INCi} + \sum_{Interconnects} C_{INIi}}{C_{REF}}$$

FI can be expressed either in units of capacitance or normalized to C_{REF}

Most commonly FI is normalized but must determine from context


If gates sized to have same drive as ref inverter

$$t_{prop-k} = t_{REF} \cdot FI_{LOAD-k}$$

Review from Last Time

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Example

 

Assume all gates sized for equal worst-case rise/fall times

Assume all gate drives are the same as that of reference inverter

Neglect interconnect capacitance, assume load of $10C_{REF}$ on F output

Determine propagation delay from A to F

DERIVATIONS


$$Fl_2 = \frac{6}{4} C_{REF} \quad Fl_3 = C_{REF} + \frac{7}{4} C_{REF} \quad Fl_4 = \frac{7}{4} C_{REF} + \frac{13}{4} C_{REF} \quad Fl_5 = 10C_{REF}$$

$$t_{PROP1} = \frac{6}{4} t_{REF} \quad t_{PROP2} = \left(1 + \frac{7}{4}\right) t_{REF} \quad t_{PROP3} = \left(\frac{7}{4} + \frac{13}{4}\right) t_{REF} \quad t_{PROP4} = 10t_{REF}$$

$$t_{PROP} = \sum_{k=1}^n t_{PROPK} = t_{REF} \sum_{k=1}^n Fl_{(k+1)} = t_{REF} \left(\frac{6}{4} + \frac{11}{4} + \frac{20}{4} + 10 \right) = t_{REF} (19.25)$$

Propagation Delay Through Multiple Stages of Logic with Stage Loading

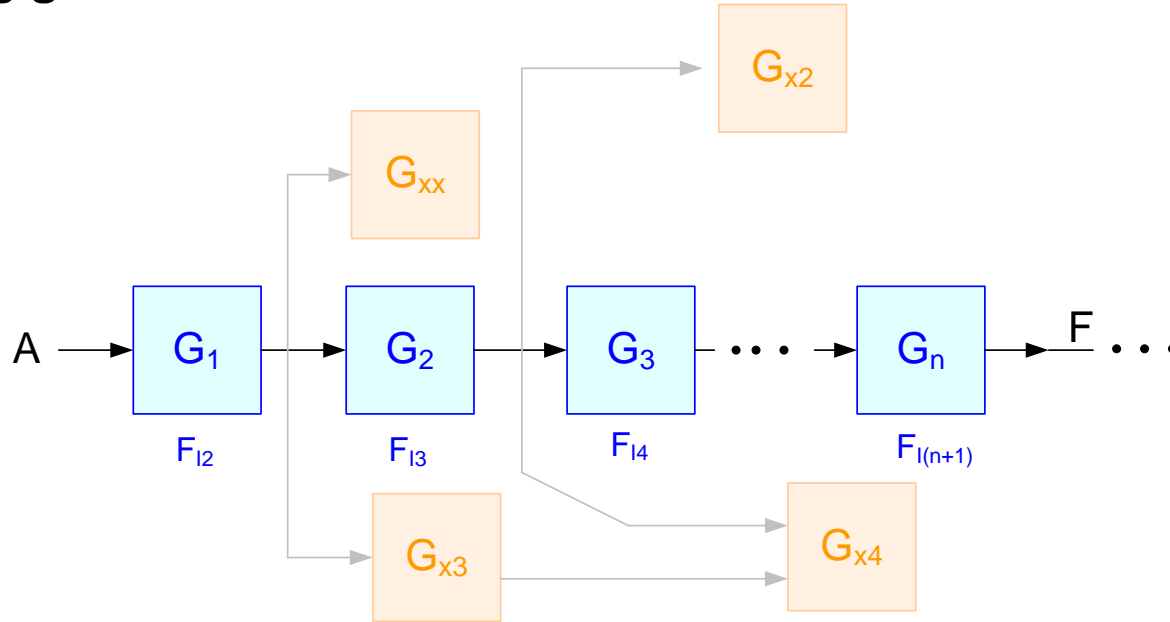(assuming gate drives are all same as that of reference inverter)



Identify the gate path from A to F

$$t_{\text{PROP}k} = t_{\text{REF}} F_{I(k+1)}$$

Propagation delay from A to F:

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n F_{I(k+1)}$$

This approach is analytically manageable, provides modest accuracy and is “faithful”


Digital Circuit Design

- Hierarchical Design
- Basic Logic Gates
- Properties of Logic Families
- Characterization of CMOS Inverter
- Static CMOS Logic Gates
 - Ratio Logic
- Propagation Delay
 - Simple analytical models
 - FI/OD
 - Logical Effort
 - Elmore Delay
- Sizing of Gates
 - The Reference Inverter
- Propagation Delay with Multiple Levels of Logic
- Optimal driving of Large Capacitive Loads
- Power Dissipation in Logic Circuits
 - Other Logic Styles
 - Array Logic
 - Ring Oscillators

→ **done**

→ **partial**

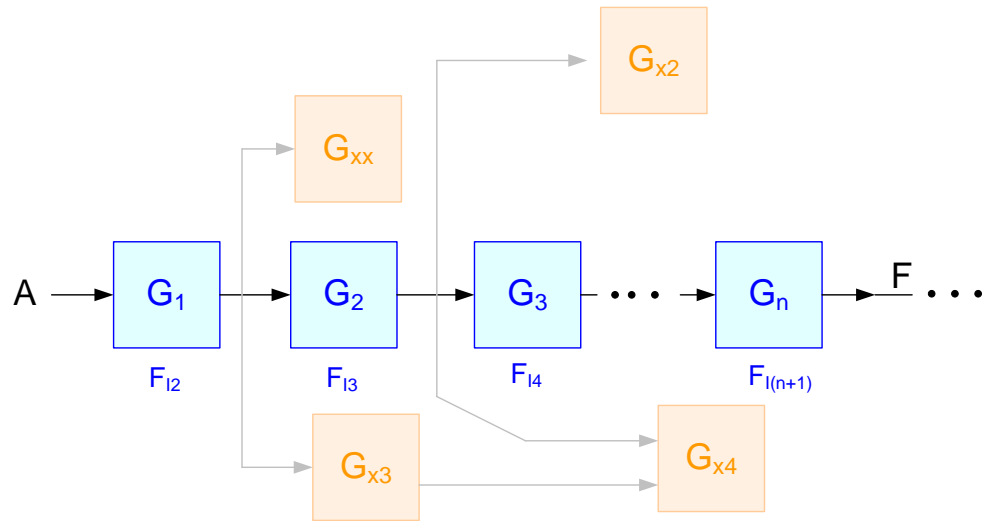What if the propagation delay is too long (or too short)?



Propagation delay from A to F :

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n F_{I(k+1)}$$


$$t_{\text{PROPK}} = t_{\text{REF}} F_{I(k+1)}$$

Recall:


Device Sizing

Multiple Input Gates:


2-input NOR

 


2-input NAND

 

k-input NOR

 

k-input NAND

 

Equal Worst Case Rise/Fall (and equal to that of ref inverter when driving C_{REF})

$W_n = ?$

$W_p = ?$

consider the fine print !

Fastest response (t_{HL} or t_{LH}) = ?

Worst case response (t_{PROP} , usually of most interest)?

Input capacitance (FI) = ?

Minimum Sized (assume driving a load of C_{REF})

$W_n = W_{min}$

$W_p = W_{min}$

Fastest response (t_{HL} or t_{LH}) = ?

Slowest response (t_{HL} or t_{LH}) = ?

Worst case response (t_{PROP} , usually of most interest)?

Input capacitance (FI) = ?

Recall:

Device Sizing

Equal Worst Case Rise/Fall

(and equal to that of ref inverter when driving C_{REF})

Multiple Input Gates: 2-input NOR

(n-channel devices sized same, p-channel devices sized the same)

Assume $L_n=L_p=L_{min}$ and driving a load of C_{REF}

$W_n=?$


$W_p=?$

Input capacitance = ?

FI=?

$t_{PROP}=?$ (worst case)

DERIVATIONS

 

One degree of freedom was used to satisfy the constraint indicated

$$W_n = W_{MIN}$$

$$W_p = 6W_{MIN}$$


Other degree of freedom was used to achieve equal rise and fall times

$$C_{INA} = C_{INB} = C_{OX}W_{MIN}L_{MIN} + 6C_{OX}W_{MIN}L_{MIN} = 7C_{OX}W_{MIN}L_{MIN} = \left(\frac{7}{4}\right)4C_{OX}W_{MIN}L_{MIN} = \left(\frac{7}{4}\right)C_{REF}$$

$$FI = \left(\frac{7}{4}\right)C_{REF} \quad \text{or} \quad FI = \frac{7}{4}$$

$$t_{PROP} = t_{REF} \quad \text{(worst case)}$$

Overdrive Factors

 


Example: Determine t_{prop} in 0.5u process if $C=10pF$ In 0.5u proc $t_{REF}=20ps$,
 $C_{REF}=4fF, R_{PDREF}=2.5K$

$$t_{PROP} = t_{REF} \cdot FI = t_{REF} \cdot \frac{10pF}{4fF} = t_{REF} \cdot 2500$$

$$t_{PROP} = 20ps \cdot 2500 = 50nsec$$

Note this is unacceptably long !

Overdrive Factors

 

Scaling widths of ALL devices by constant ($W_{\text{scaled}} = W \times \text{OD}$) will change “drive” capability relative to that of the reference inverter but not change relative value of t_{HL} and t_{LH}

$$R_{\text{PD}} = \frac{L_1}{\mu_n C_{\text{OX}} W_1 (V_{\text{DD}} - V_{\text{Tn}})}$$



$$R_{\text{PDOD}} = \frac{L_1}{\mu_n C_{\text{OX}} [\text{OD} \cdot W_1] (V_{\text{DD}} - V_{\text{Tn}})} = \frac{R_{\text{PD}}}{\text{OD}}$$

$$R_{\text{PU}} = \frac{L_2}{\mu_p C_{\text{OX}} W_2 (V_{\text{DD}} + V_{\text{Tp}})}$$



$$R_{\text{PUOD}} = \frac{L_2}{\mu_p C_{\text{OX}} [\text{OD} \cdot W_2] (V_{\text{DD}} + V_{\text{Tp}})} = \frac{R_{\text{PU}}}{\text{OD}}$$

$$t_{\text{PROP}} = t_{\text{REF}} \cdot F_{\text{IL}} \cdot \frac{1}{\text{OD}}$$

Scaling widths of ALL devices by constant will change F_{IN} to gate by OD


$$C_{\text{IN}} = C_{\text{OX}} (W_1 L_1 + W_2 L_2)$$



$$C_{\text{INOD}} = C_{\text{OX}} ([\text{OD} \cdot W_1] L_1 + [\text{OD} \cdot W_2] L_2) = \text{OD} \cdot C_{\text{IN}}$$

Overdrive Factors - Summary

(For equal worst-case rise/fall gates)

 

$$W = W_{\text{REF}} \cdot \text{OD}$$

$$R_{\text{PD-OD}} = \frac{R_{\text{PD-REF}}}{\text{OD}}$$



$$R_{\text{PU-OD}} = \frac{R_{\text{PU-REF}}}{\text{OD}}$$

Still equal worst-case rise/fall

$$t_{\text{PROP}} = t_{\text{REF}} \cdot \text{FI}_L \cdot \frac{1}{\text{OD}}$$

$$\text{FI}_{\text{IN}} = \text{OD} \cdot C_{\text{REF}}$$

Overdrive Factors

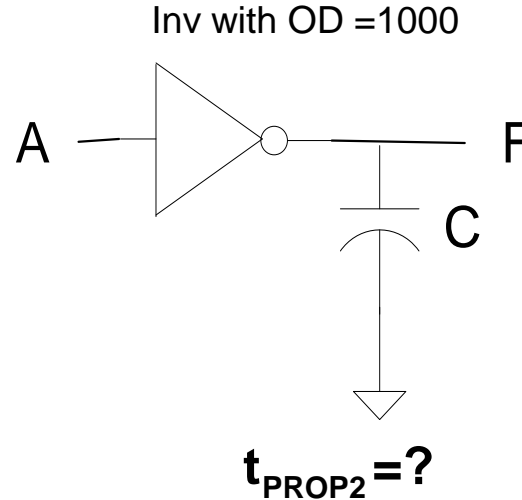 

 
Example: Determine t_{prop} in 0.5u process if $C=10\text{pF}$ and $OD=1000$

$$t_{PROP1} = t_{REF} \cdot FI \cdot \frac{1}{OD} = t_{REF} \cdot \frac{10\text{pF}}{4\text{fF}} = t_{REF} \cdot 2500$$

$$t_{PROP2} = t_{REF} \cdot FI \cdot \frac{1}{OD} = t_{REF} \cdot \frac{10\text{pF}}{4\text{fF}} \cdot \frac{1}{1000} = t_{REF} \cdot 2.5$$











Note sizing the inverter with the OD improved delay by a factor of 1000 !

Overdrive Factors



- By definition, the factor by which the W/L of all devices are scaled above those of the reference inverter is termed the overdrive factor, OD
- Scaling widths by overdrive factor **DECREASES** resistance by same factor
- Scaling all widths by a constant does not compromise the symmetry between the rise and fall times (i.e. $t_{HL}=t_{LH}$)
- Judicious use of overdrive can dramatically improve the speed of digital circuits
- Large overdrive factors are often used
- Scaling widths by overdrive factor **INCREASES** input capacitance by same factor - **So is there any net gain in speed?**

Digital Circuit Design

-  Hierarchical Design
-  Basic Logic Gates
-  Properties of Logic Families
-  Characterization of CMOS Inverter
-  Static CMOS Logic Gates
 -  Ratio Logic
-  Propagation Delay
 -  Simple analytical models
 - FI/OD
 - Logical Effort
 - Elmore Delay
-  Sizing of Gates
 -  The Reference Inverter


-  Propagation Delay with Multiple Levels of Logic
-  Optimal driving of Large Capacitive Loads
-  Power Dissipation in Logic Circuits
 - Other Logic Styles
 - Array Logic
 - Ring Oscillators

 **done**

 **partial**

Propagation Delay with Over-drive Capability

Overdrive

 

$$t_{HL} = t_{LH} = \frac{R_{PDREF}}{OD} C_L$$

$$t_{PROP} = t_{HL} + t_{LH} = 2 \frac{R_{PDREF} C_L}{OD} = \frac{t_{REF}}{OD}$$

Asymmetric Overdrive

Define the **Asymmetric Overdrive Factors** of the stage to be the factor by which PU and PD resistors are scaled relative to those of the reference inverter.

$$R_{PDEFF} = \frac{R_{PDREF}}{OD_{HL}}$$

$$R_{PUEFF} = \frac{R_{PUREF}}{OD_{LH}}$$


$$t_{HL} = \frac{R_{PDREF}}{OD_{HL}} C_L$$

$$t_{LH} = \frac{R_{PDREF}}{OD_{LH}} C_L$$

$$t_{PROP} = t_{HL} + t_{LH} = \frac{R_{PDREF}}{OD_{HL}} C_L + \frac{R_{PDREF}}{OD_{LH}} C_L = R_{PDREF} C_L \left[\frac{1}{OD_{HL}} + \frac{1}{OD_{LH}} \right] = \frac{t_{REF}}{2} \left[\frac{1}{OD_{HL}} + \frac{1}{OD_{LH}} \right] F_{IL}$$

Propagation Delay with Over-drive Capability

Overdrive

 

If an inverter with OD is sized for equal rise/fall, $OD_{HL}=OD_{LH}=OD$


$$t_{PROP} = R_{PDREF} C_L \left[\frac{1}{OD_{HL}} + \frac{1}{OD_{LH}} \right] = R_{PDREF} C_L \frac{2}{OD} = t_{REF} \frac{F_{IL}}{OD}$$

OD may be larger or smaller than 1


Propagation Delay with Over-drive Capability

 Example


Compare the propagation delays. Assume the OD is 900 in the third case and 30 in the fourth case. Don't worry about the extra inversion at this time.




$$t_{PROP} = 900t_{REF}$$

 
 
$$t_{PROP} = t_{REF} + 900t_{REF} = 901t_{REF}$$



 
$$t_{PROP} = 900t_{REF} + t_{REF} = 901t_{REF}$$



$$t_{PROP} = 30t_{REF} + 30t_{REF} = 60t_{REF}$$

- **Dramatic reduction in t_{PROP} is possible** (input is driving same in all 3 cases)
- **Will later determine what optimal number of stages and sizing is**

 Propagation Delay in Multiple-Levels of Logic with Stage Loading



F_{lk} denotes the total loading on stage k which is the sum of the F_l of all loading on stage k

Summary: Propagation delay from A to F :

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n \frac{F_{l(k+1)}}{OD_k}$$


Propagation Delay in Multiple-Levels of Logic with Stage Loading

Will consider an example with the five cases

- Equal rise/fall (no overdrive)
- Equal rise/fall with overdrive
- Minimum Sized
- Asymmetric Overdrive
- Combination of equal rise/fall, minimum size and overdrive

Will develop the analysis methods as needed

 Propagation Delay in Multiple-Levels of Logic with Stage Loading



- Equal rise/fall (no overdrive)
- Equal rise/fall with overdrive
- Minimum Sized
- Asymmetric Overdrive
- Combination of equal rise/fall, minimum size and overdrive

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n F_{l(k+1)}$$

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n \frac{F_{l(k+1)}}{\text{OD}_k}$$





$$t_{\text{PROP}} = ?$$

$$t_{\text{PROP}} = ?$$

$$t_{\text{PROP}} = ?$$

Driving Notation

    
- **Equal rise/fall (no overdrive)**
- **Equal rise/fall with overdrive**
- **Minimum Sized**
- **Asymmetric Overdrive**



Notation will be used only if it is not clear from the context what sizing is being used

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Asymmetric Overdrive

 

Recall:


Define the Asymmetric Overdrive Factors of the stage to be the factors by which PU and PD resistors are scaled relative to those of the reference inverter.

$$R_{PDEFF} = \frac{R_{PDREF}}{OD_{HL}}$$

$$R_{PUEFF} = \frac{R_{PUREF}}{OD_{LH}}$$

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Asymmetric Overdrive

 

Recall:

$$t_{\text{PROP}} = t_{\text{LH}} + t_{\text{HL}} = t_{\text{REF}} \frac{F_{\text{IL}}}{\text{OD}}$$

If inverter is not equal rise/fall



$$t_{\text{HL}} = \frac{R_{\text{PDREF}}}{\text{OD}_{\text{HL}}} C_L = \frac{1}{2} t_{\text{REF}} \frac{F_{\text{IL}}}{\text{OD}_{\text{HL}}}$$

$$t_{\text{LH}} = \frac{R_{\text{PUREF}}}{\text{OD}_{\text{LH}}} C_L = \frac{1}{2} t_{\text{REF}} \frac{F_{\text{IL}}}{\text{OD}_{\text{LH}}}$$

$$t_{\text{PROP}} = t_{\text{HL}} + t_{\text{LH}} = \frac{1}{2} t_{\text{REF}} F_{\text{IL}} \left(\frac{1}{\text{OD}_{\text{HL}}} + \frac{1}{\text{OD}_{\text{LH}}} \right)$$


Propagation Delay in Multiple-Levels of Logic with Stage Loading

Asymmetric Overdrive

  

$$t_{\text{PROP}} = t_{\text{HL}} + t_{\text{LH}} = \frac{1}{2} t_{\text{REF}} F_{\text{IL}} \left(\frac{1}{\text{OD}_{\text{HL}}} + \frac{1}{\text{OD}_{\text{LH}}} \right)$$


When propagating through n stages:

 

F_{ik} denotes the total loading on stage k which is the sum of the F_I of all loading on stage k


$$t_{\text{PROP}} = t_{\text{REF}} \cdot \left(\frac{1}{2} \sum_{k=1}^n F_{I(k+1)} \left(\frac{1}{\text{OD}_{\text{HLk}}} + \frac{1}{\text{OD}_{\text{LHk}}} \right) \right)$$

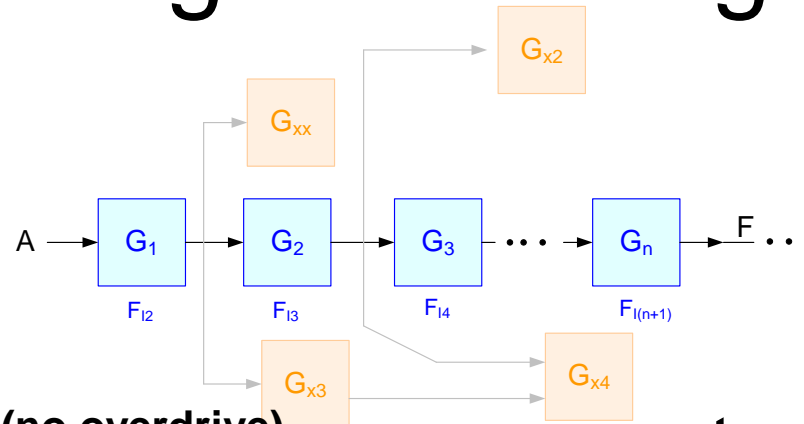Propagation Delay in Multiple-Levels of Logic with Stage Loading



- Equal rise/fall (no overdrive) $t_{\text{PROP}} = ?$
- Equal rise/fall with overdrive $t_{\text{PROP}} = ?$
- Minimum Sized $t_{\text{PROP}} = ?$
- Asymmetric Overdrive $t_{\text{PROP}} = ?$
- Combination of equal rise/fall, minimum size and overdrive $t_{\text{PROP}} = ?$

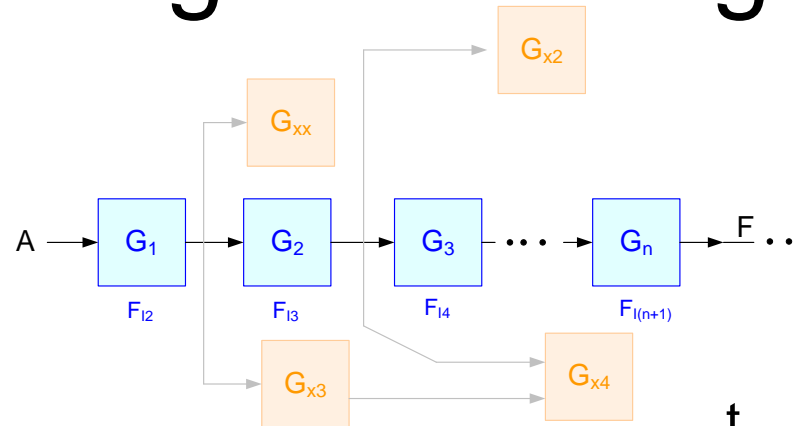Propagation Delay in Multiple-Levels of Logic with Stage Loading



- Equal rise/fall (no overdrive)

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n F_{I(k+1)}$$

- Equal rise/fall with overdrive

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n \frac{F_{I(k+1)}}{\text{OD}_k}$$

- Minimum Sized

$$t_{\text{PROP}} = ?$$

- Asymmetric Overdrive


$$t_{\text{PROP}} = t_{\text{REF}} \cdot \left(\frac{1}{2} \sum_{k=1}^n F_{I(k+1)} \left(\frac{1}{\text{OD}_{\text{HLK}}} + \frac{1}{\text{OD}_{\text{LHK}}} \right) \right)$$

- Combination of equal rise/fall, minimum size and overdrive


$$t_{\text{PROP}} = ?$$

Propagation Delay in Multiple-Levels of Logic with Stage Loading and Overdrives

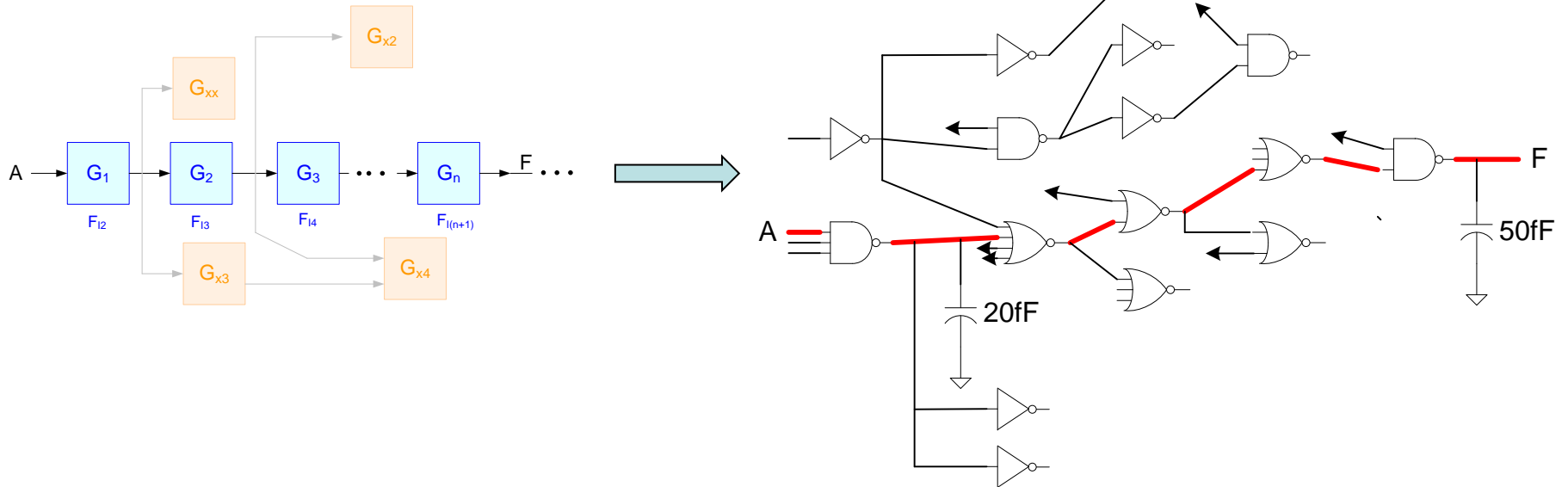Will now consider A to F propagation for this circuit as an example with different overdrives



 Propagation Delay in Multiple-Levels of Logic with Stage Loading



- Equal rise/fall (no overdrive)

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n F_{l(k+1)}$$



- Equal rise/fall with overdrive

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n \frac{F_{l(k+1)}}{\text{OD}_k}$$

- Minimum Sized

$$t_{\text{PROP}} = ?$$

- Asymmetric Overdrive


$$t_{\text{PROP}} = t_{\text{REF}} \cdot \left(\frac{1}{2} \sum_{k=1}^n F_{l(k+1)} \left(\frac{1}{\text{OD}_{\text{HLk}}} + \frac{1}{\text{OD}_{\text{LHk}}} \right) \right)$$

- Combination of equal rise/fall, minimum size and overdrive

$$t_{\text{PROP}} = ?$$

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Equal rise-fall gates, no overdrive

 

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n F_{i_{k+1}}$$



$$\frac{t_{\text{PROP}}}{t_{\text{REF}}} = \sum_{k=1}^n F_{i_{k+1}}$$

In 0.5u proc $t_{\text{REF}}=20\text{ps}$,
 $C_{\text{REF}}=4\text{fF}$, $R_{\text{PDREF}}=2.5\text{K}$

Propagation Delay in Multiple-Levels of Logic with Stage Loading


Equal rise-fall gates, no overdrive

	Equal Rise/Fall
C_{IN}/C_{REF}	
Inverter	1
NOR	$\frac{3k+1}{4}$
NAND	$\frac{3+k}{4}$
Overdrive	
Inverter	
HL	1
LH	1
NOR	
HL	1
LH	1
NAND	
HL	1
LH	1
t_{PROP}/t_{REF}	$\sum_{k=1}^n F_{(k+1)}$

Equal rise-fall gates, no overdrive

In 0.5u proc $t_{REF}=20ps$,
 $C_{REF}=4fF, R_{PDREF}=2.5K$

 
(Note: This C_{OX} is somewhat larger than that in the 0.5u ON process)



Equal rise-fall gates, no overdrive


In 0.5u proc $t_{REF}=20ps$,
 $C_{REF}=4fF, R_{PDREF}=2.5K$

 (Note: This C_{OX} is somewhat larger than that in the 0.5u ON process)



$$t_{PROP} = 32.5 t_{REF}$$

 How does this propagation delay compare to that required for a propagation of a signal through 5-levels of logic with only reference inverters (load is a ref inverter instead of 50fF as well)?




$$t_{PROP} = 5 t_{REF}$$

Loading can have a dramatic effect on propagation delay

Break here for comments by
Jonathan Crandall
of Skyworks in Cedar Rapids

 Propagation Delay in Multiple-Levels of Logic with Stage Loading



- Equal rise/fall (no overdrive)

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n F_{l(k+1)}$$



- Equal rise/fall with overdrive

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n \frac{F_{l(k+1)}}{\text{OD}_k}$$



- Minimum Sized

$$t_{\text{PROP}} = ?$$

- Asymmetric Overdrive


$$t_{\text{PROP}} = t_{\text{REF}} \cdot \left(\frac{1}{2} \sum_{k=1}^n F_{l(k+1)} \left(\frac{1}{\text{OD}_{\text{HLk}}} + \frac{1}{\text{OD}_{\text{LHk}}} \right) \right)$$

- Combination of equal rise/fall, minimum size and overdrive

$$t_{\text{PROP}} = ?$$

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Equal rise-fall gates, with overdrive

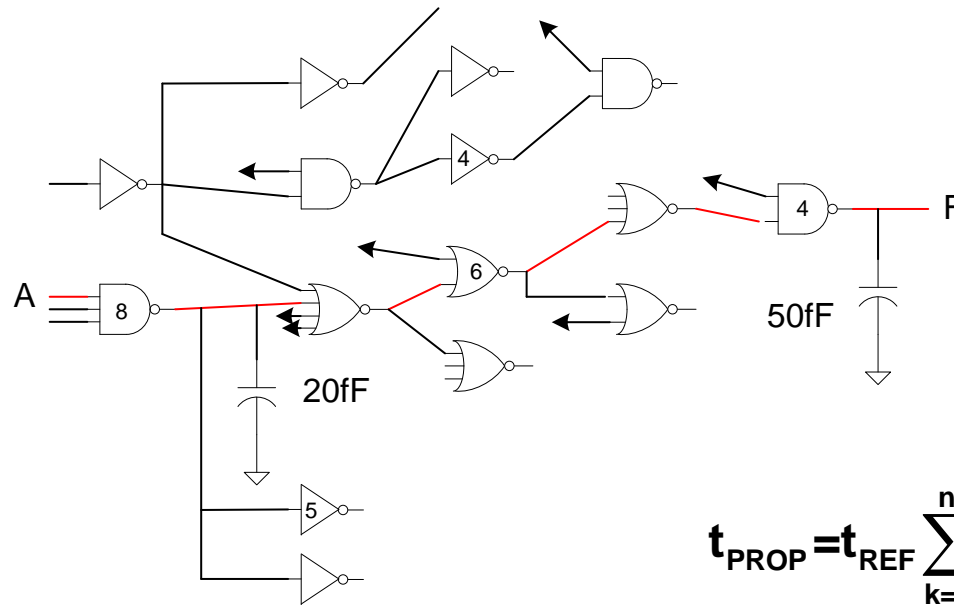

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n \frac{F_{l_{k+1}}}{\text{OD}_k}$$



$$\frac{t_{\text{PROP}}}{t_{\text{REF}}} = \sum_{k=1}^n \frac{F_{l_{k+1}}}{\text{OD}_k}$$

In 0.5u proc $t_{\text{REF}}=20\text{ps}$,
 $C_{\text{REF}}=4\text{fF}$, $R_{\text{PDREF}}=2.5\text{K}$


(Note: This C_{OX} is somewhat larger than that in the 0.5u ON process)

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Equal rise-fall gates, with overdrive

	Equal Rise/Fall	Equal Rise/Fall (with OD)
C_{IN}/C_{REF}		
Inverter	1	OD
NOR	$\frac{3k+1}{4}$	$\frac{3k+1}{4} \cdot OD$
NAND	$\frac{3+k}{4}$	$\frac{3+k}{4} \cdot OD$
Overdrive		
Inverter		
HL	1	OD
LH	1	OD
NOR		
HL	1	OD
LH	1	OD
NAND		
HL	1	OD
LH	1	OD
t_{PROP}/t_{REF}	$\sum_{k=1}^n F_{l(k+1)}$	$\sum_{k=1}^n \frac{F_{l(k+1)}}{OD_k}$

Equal rise-fall gates, with overdrive

 


In 0.5u proc $t_{REF} = 20ps$, $C_{REF} = 4fF, R_{PDREF} = 2.5K$

(Note: This C_{OX} is somewhat larger than that in the 0.5u ON process)

$t_{PROP} = 23.6 t_{REF}$

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Minimum-sized gates

 


In 0.5u proc $t_{REF}=20ps$,
 $C_{REF}=4fF, R_{PDREF}=2.5K$

$$t_{PROP} = t_{REF} \bullet ?$$

(Note: This C_{OX} is somewhat larger than that in the 0.5u ON process)

 Propagation Delay in Multiple-Levels of Logic with Stage Loading



- Equal rise/fall (no overdrive)

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n F_{l(k+1)}$$

- Equal rise/fall with overdrive

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n \frac{F_{l(k+1)}}{\text{OD}_k}$$



- Minimum Sized

$$t_{\text{PROP}} = ?$$

- Asymmetric Overdrive


$$t_{\text{PROP}} = t_{\text{REF}} \cdot \left(\frac{1}{2} \sum_{k=1}^n F_{l(k+1)} \left(\frac{1}{\text{OD}_{\text{HLk}}} + \frac{1}{\text{OD}_{\text{LHk}}} \right) \right)$$

- Combination of equal rise/fall, minimum size and overdrive

$$t_{\text{PROP}} = ?$$

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Minimum-sized gates

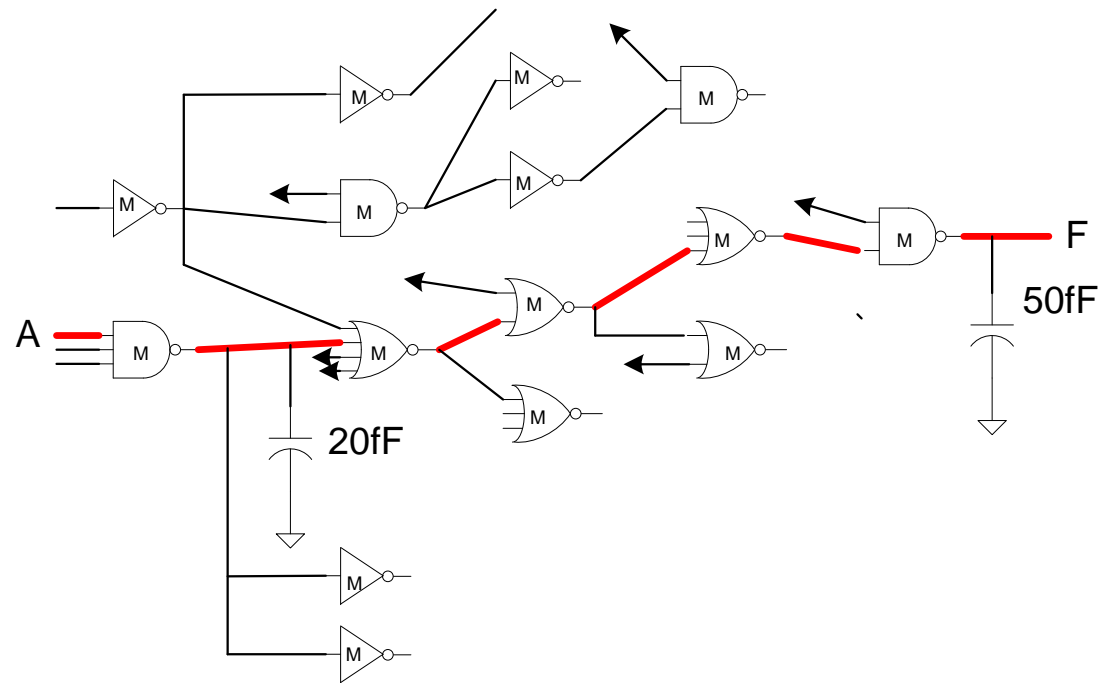


$$t_{\text{PROP}} = t_{\text{REF}} \bullet ?$$

Observe that a minimum-sized gate is simply a gate with asymmetric overdrive

Recall:

 Propagation Delay with Minimum-Sized Gates





$$t_{\text{PROP}} = t_{\text{REF}} \cdot \left(\frac{1}{2} \sum_{k=1}^n F_{I(k+1)} \left(\frac{1}{\text{OD}_{\text{HLk}}} + \frac{1}{\text{OD}_{\text{LHk}}} \right) \right)$$



$$\frac{t_{\text{PROP}}}{t_{\text{REF}}} = \left(\frac{1}{2} \sum_{k=1}^n F_{I(k+1)} \left(\frac{1}{\text{OD}_{\text{HLk}}} + \frac{1}{\text{OD}_{\text{LHk}}} \right) \right)$$

- Still need OD_{HL} and OD_{LH} for minimum-sized gates
- Still need FI for minimum-sized gates

  Propagation Delay with minimum-sized gates





$$OD_{HL}=?$$

$$OD_{HL}=1$$

$$OD_{LH}=?$$

$$OD_{LH}=\frac{1}{3k}$$

  

$$OD_{HL}=?$$

$$OD_{HL}=1/k$$

$$OD_{LH}=?$$

$$OD_{LH}=\frac{1}{3}$$

$$FI=2C_{OX}W_{MIN}L_{MIN}$$


$$C_{REF}=4C_{OX}W_{MIN}L_{MIN}$$

$$FI=\frac{C_{REF}}{2}$$


Propagation Delay in Multiple-Levels of Logic with Stage Loading

Minimum-sized gates


	Equal Rise/Fall	Equal Rise/Fall (with OD)	Minimum Sized
C_{IN}/C_{REF}			
Inverter	1	OD	
NOR	$\frac{3k+1}{4}$	$\frac{3k+1}{4} \cdot OD$	
NAND	$\frac{3+k}{4}$	$\frac{3+k}{4} \cdot OD$	
Overdrive			
Inverter			
HL	1	OD	
LH	1	OD	
NOR			
HL	1	OD	
LH	1	OD	
NAND			
HL	1	OD	
LH	1	OD	
t_{PROP}/t_{REF}	$\sum_{k=1}^n F_{l(k+1)}$	$\sum_{k=1}^n \frac{F_{l(k+1)}}{OD_k}$	

 


$$OD_{HL} = 1$$

 

$$OD_{HL} = 1/k$$

 

$$OD_{LH} = \frac{1}{3k}$$

 


$$OD_{LH} = \frac{1}{3}$$

$$FI = \frac{C_{REF}}{2}$$


Propagation Delay in Multiple-Levels of Logic with Stage Loading

Minimum-sized gates


	Equal Rise/Fall	Equal Rise/Fall (with OD)	Minimum Sized
C_{IN}/C_{REF}			
Inverter	1	OD	1/2
NOR	$\frac{3k+1}{4}$	$\frac{3k+1}{4} \cdot OD$	1/2
NAND	$\frac{3+k}{4}$	$\frac{3+k}{4} \cdot OD$	1/2
Overdrive			
Inverter			
HL	1	OD	1
LH	1	OD	1/3
NOR			
HL	1	OD	1
LH	1	OD	1/(3k)
NAND			
HL	1	OD	1/k
LH	1	OD	1/3
t_{PROP}/t_{REF}	$\sum_{k=1}^n F_{l(k+1)}$	$\sum_{k=1}^n \frac{F_{l(k+1)}}{OD_k}$	$\frac{1}{2} \sum_{k=1}^n F_{l(k+1)} \left(\frac{1}{OD_{HLk}} + \frac{1}{OD_{LHk}} \right)$

 


$$OD_{HL} = 1$$

 

$$OD_{HL} = 1/k$$

 

$$OD_{LH} = \frac{1}{3k}$$

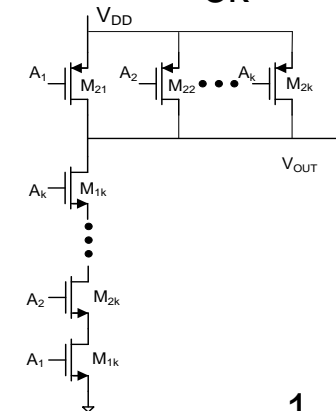

$$OD_{LH} = \frac{1}{3}$$



$$FI = \frac{C_{REF}}{2}$$

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Minimum-sized gates

	Equal Rise/Fall	Equal Rise/Fall (with OD)	Minimum Sized
C_{IN}/C_{REF}			
Inverter	1	OD	1/2
NOR	$\frac{3k+1}{4}$	$\frac{3k+1}{4} \cdot OD$	1/2
NAND	$\frac{3+k}{4}$	$\frac{3+k}{4} \cdot OD$	1/2
Overdrive			
Inverter			
HL	1	OD	1
LH	1	OD	1/3
NOR			
HL	1	OD	1
LH	1	OD	1/(3k)
NAND			
HL	1	OD	1/k
LH	1	OD	1/3
t_{PROP}/t_{REF}	$\sum_{k=1}^n F_{l(k+1)}$	$\sum_{k=1}^n \frac{F_{l(k+1)}}{OD_k}$	$\frac{1}{2} \sum_{k=1}^n F_{l(k+1)} \left(\frac{1}{OD_{HLk}} + \frac{1}{OD_{LHk}} \right)$

Minimum-sized gates

  


$$t_{PROP} = t_{REF} \cdot \left(\frac{1}{2} \sum_{k=1}^5 F_{l(k+1)} \left(\frac{1}{OD_{HLk}} + \frac{1}{OD_{LHk}} \right) \right)$$

$$t_{PROP} = t_{REF} \cdot \frac{1}{2} \left(\frac{13}{2}(3+3) + 1(12+1) + 1(6+1) + \frac{1}{2}(9+1) + 12.5(2+3) \right)$$

$$t_{PROP} = 63.25 \cdot t_{REF}$$

 Propagation Delay in Multiple-Levels of Logic with Stage Loading



- Equal rise/fall (no overdrive)

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n F_{I_{(k+1)}}$$

- Equal rise/fall with overdrive

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n \frac{F_{I_{(k+1)}}}{\text{OD}_k}$$

- Minimum Sized

$$t_{\text{PROP}} = t_{\text{REF}} \cdot \left(\frac{1}{2} \sum_{k=1}^n F_{I_{(k+1)}} \left(\frac{1}{\text{OD}_{\text{HLk}}} + \frac{1}{\text{OD}_{\text{LHk}}} \right) \right)$$



- Asymmetric Overdrive

$$t_{\text{PROP}} = t_{\text{REF}} \cdot \left(\frac{1}{2} \sum_{k=1}^n F_{I_{(k+1)}} \left(\frac{1}{\text{OD}_{\text{HLk}}} + \frac{1}{\text{OD}_{\text{LHk}}} \right) \right)$$



- Combination of equal rise/fall, minimum size and overdrive

$$t_{\text{PROP}} = ?$$



Stay Safe and Stay Healthy !

End of Lecture 41