

EE 330

Lecture 28

Two-Port Amplifier Models

Fall 2024 Exam Schedule


Exam 1	Friday	Sept 27
Exam 2	Friday	October 25
Exam 3	Friday	Nov 22
Final Exam	Monday	Dec 16 12:00 - 2:00 PM

Amplifier Characterization

- Two-Port Models
- Amplifier Parameters




Will assume amplifiers have two ports, one termed an input port and the other termed an output port

Two-Port and Three-Port Networks

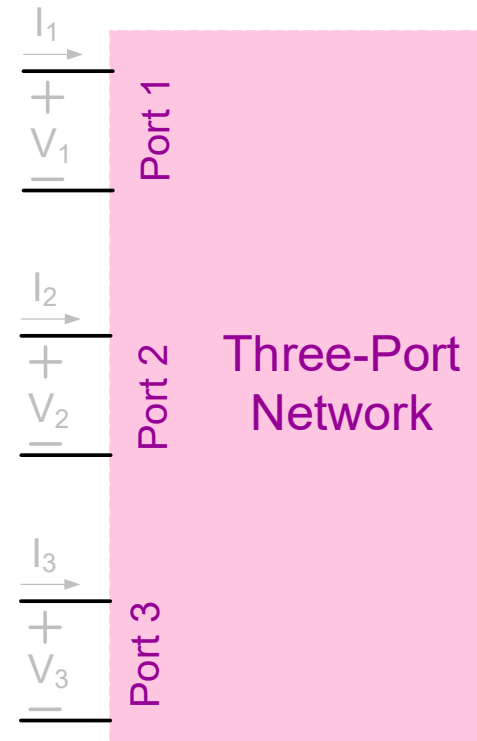

- Each port characterized by a pair of nodes (terminals)
- Can consider any number of ports
- Can be linear or nonlinear but most interest here will be in linear n-ports
- Often one node is common for all ports
- Ports are externally excited, terminated, or interconnected to form useful circuits
- Often useful for decomposing portions of a larger circuit into subcircuits to provide additional insight into operation


Two-Port Representation of Amplifiers

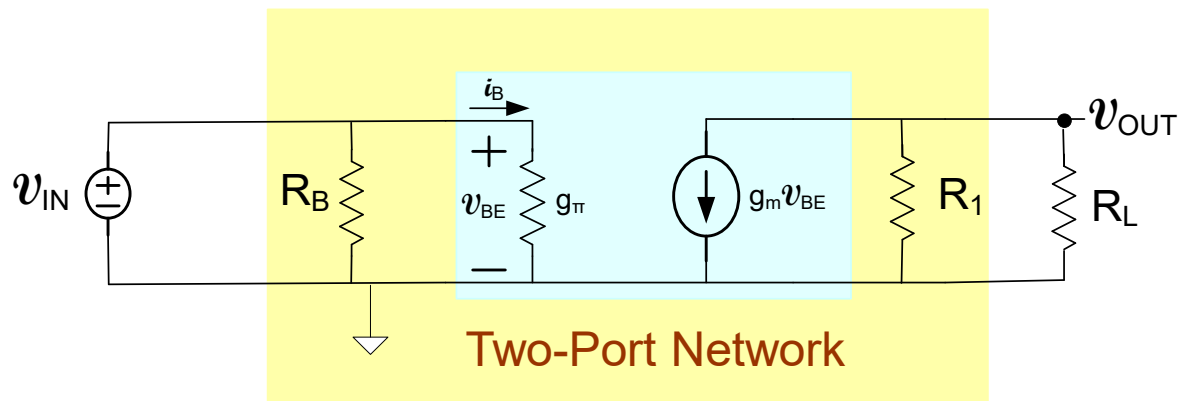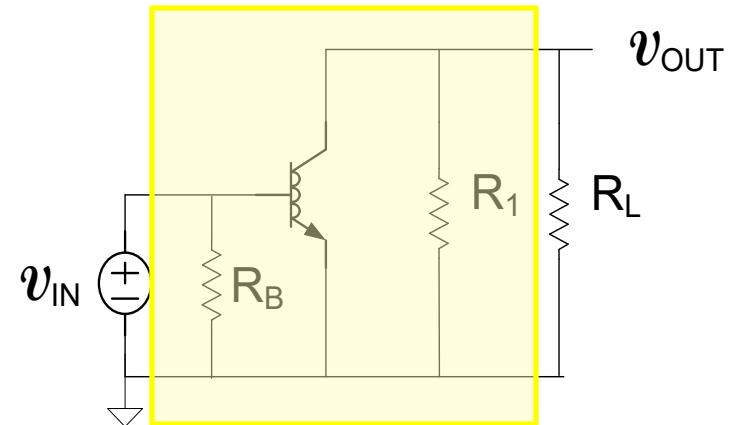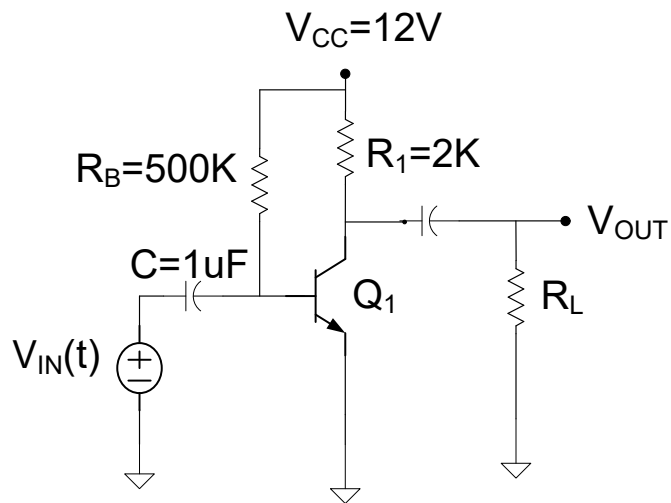

- Two-port model representation of amplifiers useful for insight into operation and analysis
- Internal circuit structure of the two-port can be quite complicated but equivalent two-port model (when circuit is linear) is quite simple

Two-port representation of amplifiers

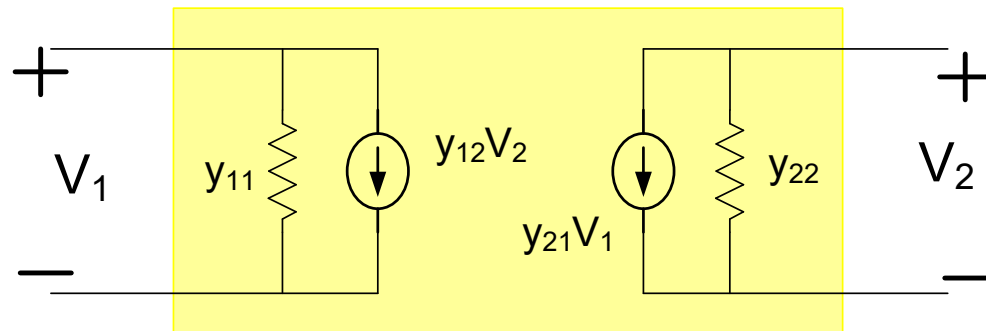
Amplifiers can be modeled as a linear two-port for small-signal operation



In terms of y-parameters


Other parameter sets could be used

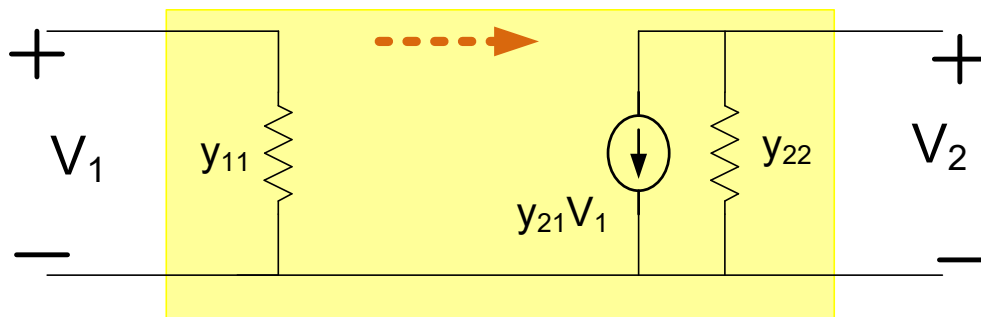- Amplifier often **unilateral** (signal propagates in only one direction: wlog $y_{12}=0$)
- One terminal is often common




Two-port representation of amplifiers

Unilateral amplifiers:

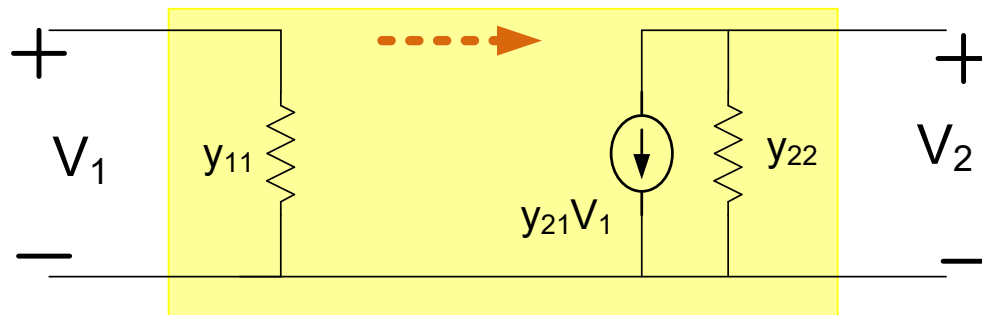

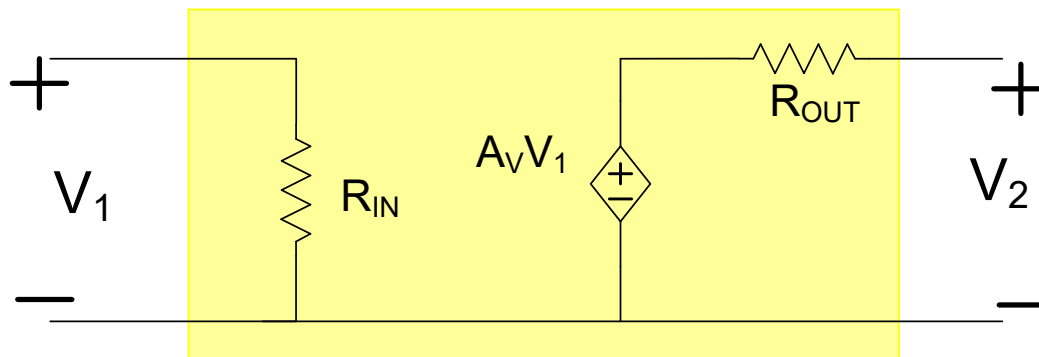- Thevenin equivalent output port often more standard
- R_{IN} , A_V , and R_{OUT} often used to characterize the two-port of amplifiers





Unilateral amplifier in terms of “amplifier” parameters

$$R_{IN} = \frac{1}{y_{11}} \quad A_V = -\frac{y_{21}}{y_{22}} \quad R_{OUT} = \frac{1}{y_{22}}$$

Amplifier input impedance, output impedance and gain are usually of interest

Why?

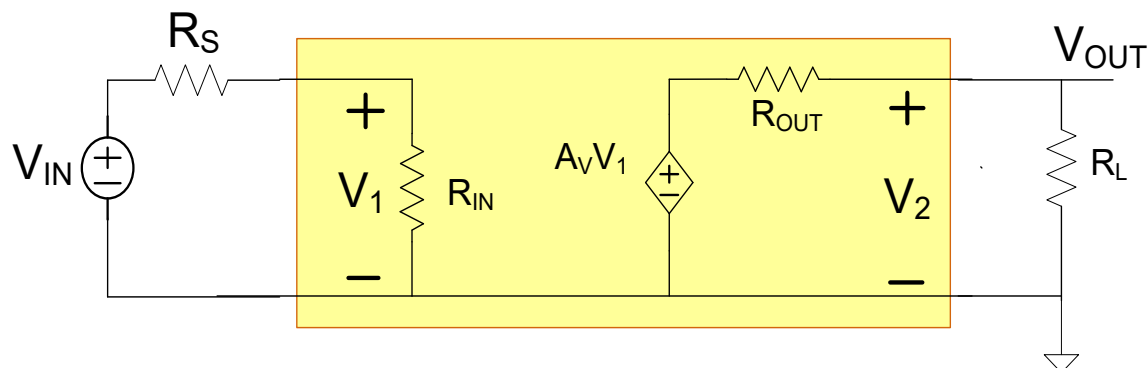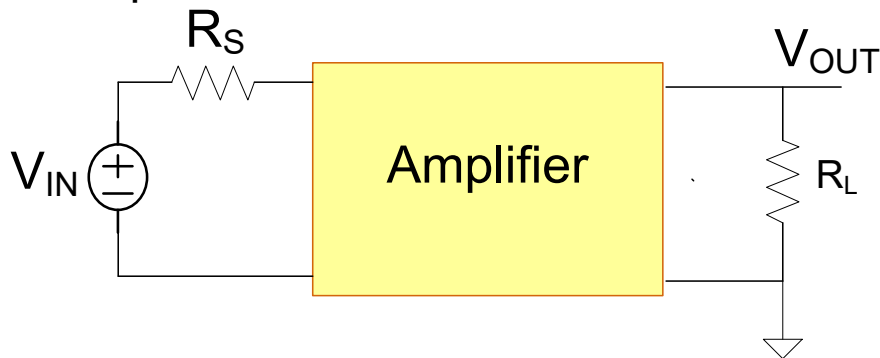Example 1: Assume amplifier is unilateral



$$V_{OUT} = \left(\frac{R_L}{R_L + R_{OUT}} \right) A_V \left(\frac{R_{IN}}{R_S + R_{IN}} \right) V_{IN}$$



$$A_{VAMP} = \frac{V_{OUT}}{V_{IN}} = \left(\frac{R_L}{R_L + R_{OUT}} \right) \left(\frac{R_{IN}}{R_S + R_{IN}} \right) A_V$$

- Can get gain without reconsidering details about components internal to the Amplifier!!!
- Analysis more involved when not unilateral

Amplifier input impedance, output impedance and gain are usually of interest

Why?

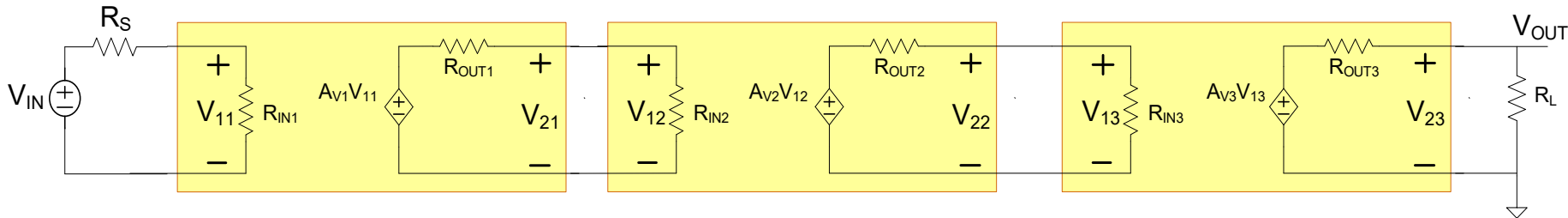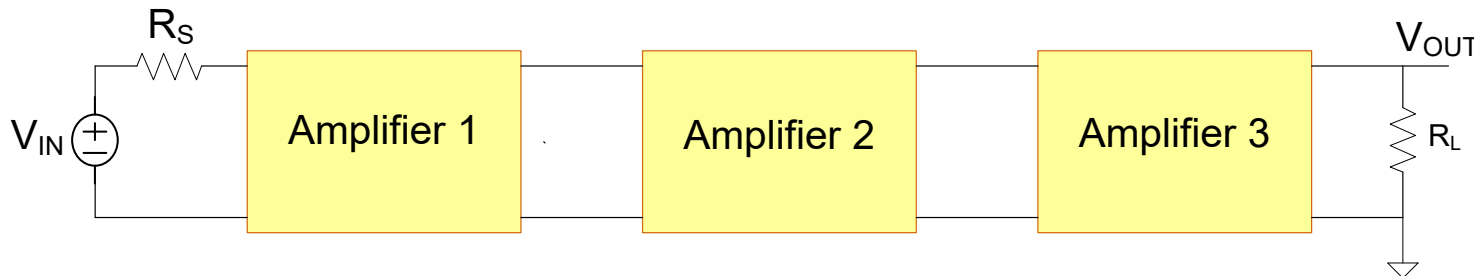Example 2: Assume amplifiers are unilateral




$$V_{OUT} = \left(\frac{R_L}{R_L + R_{OUT3}} \right) A_{V3} \left(\frac{R_{IN3}}{R_{OUT2} + R_{IN3}} \right) A_{V2} \left(\frac{R_{IN2}}{R_{OUT1} + R_{IN2}} \right) A_{V1} \left(\frac{R_{IN1}}{R_S + R_{IN1}} \right) V_{IN}$$

$$A_{VAMP} = \frac{V_{OUT}}{V_{IN}} = \left(\frac{R_L}{R_L + R_{OUT3}} \right) A_{V3} \left(\frac{R_{IN3}}{R_{OUT2} + R_{IN3}} \right) A_{V2} \left(\frac{R_{IN2}}{R_{OUT1} + R_{IN2}} \right) A_{V1} \left(\frac{R_{IN1}}{R_S + R_{IN1}} \right)$$


- Can get gain without reconsidering details about components internal to the Amplifier!!!
- Analysis more involved when not unilateral

Two-port representation of amplifiers

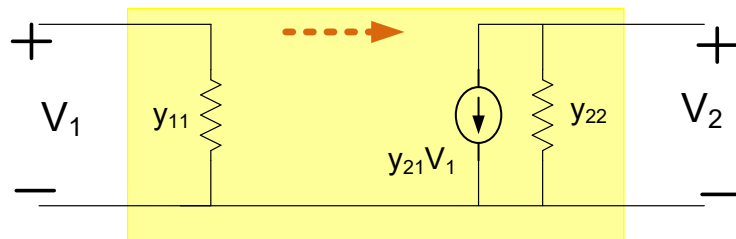- Amplifier often **unilateral** (signal propagates in only one direction: wlog $y_{12}=0$)
- One terminal is often common
- “Amplifier” parameters often used




y parameters

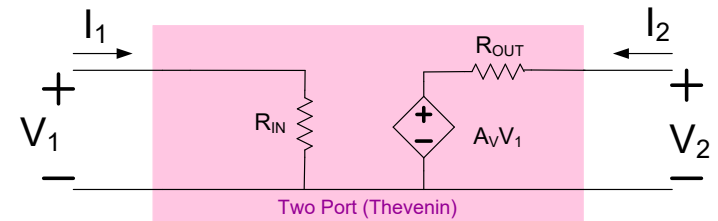


Amplifier parameters

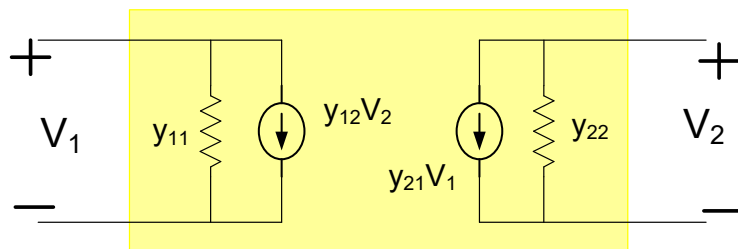- Amplifier parameters can also be used if not **unilateral**
- One terminal is often common




y parameters

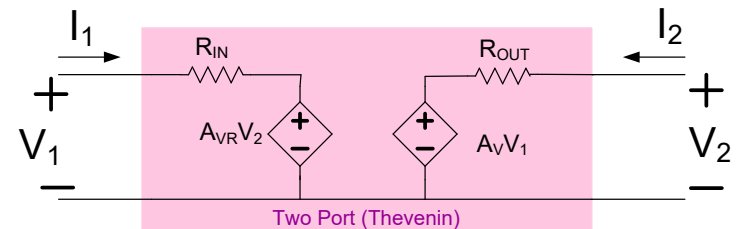

Amplifier parameters

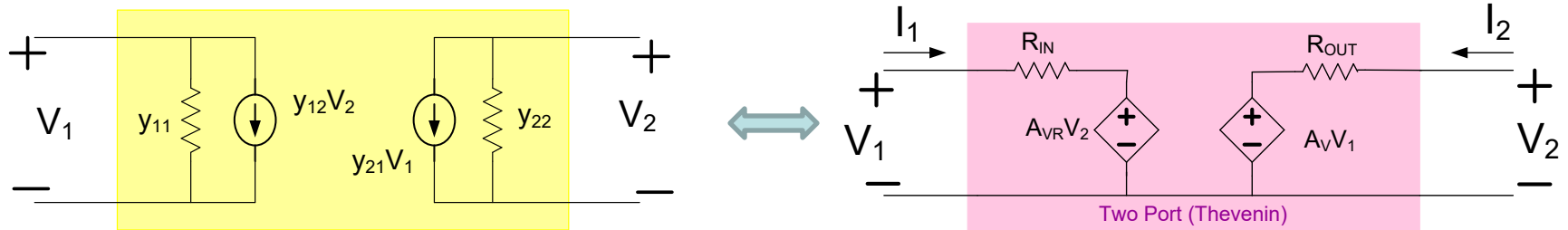Determination of small-signal model parameters:




In the past, we have determined small-signal model parameters of electronic devices from the nonlinear port characteristics

$$\left. \begin{aligned} \mathbf{I}_1 &= \mathbf{f}_1(\mathbf{V}_1, \mathbf{V}_2) \\ \mathbf{I}_2 &= \mathbf{f}_2(\mathbf{V}_1, \mathbf{V}_2) \end{aligned} \right\} \mathbf{y}_{ij} = \left. \frac{\partial \mathbf{f}_i(\mathbf{V}_1, \mathbf{V}_2)}{\partial \mathbf{V}_j} \right|_{\bar{\mathbf{V}} = \bar{\mathbf{V}}_Q}$$

- Will now determine small-signal model parameters for two-port comprised of linear networks (instead of just electronic devices)
- Could go back to the nonlinear models and analyze as we did for electronic devices
- Will follow a different approach (results are identical) that is often much easier

Two-Port Equivalents of Interconnected Two-ports



Example:

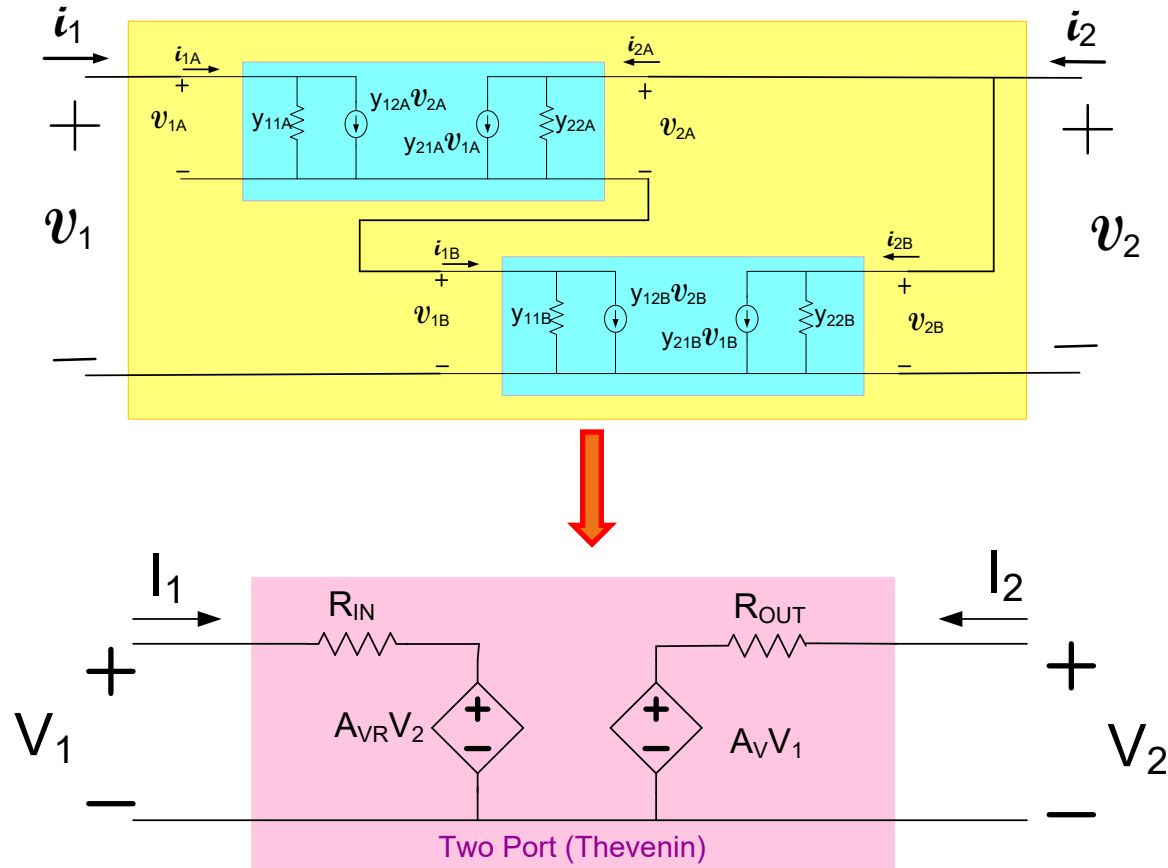


- could obtain two-port in any form
- often obtain equivalent circuit w/o identifying independent variables
- Unilateral iff $A_{VR}=0$ (or if $A_V=0$ though would probably relabel ports)
- Thevenin-Norton transformations can be made on either or both ports

Two-Port Equivalents of Interconnected Two-ports

Example:

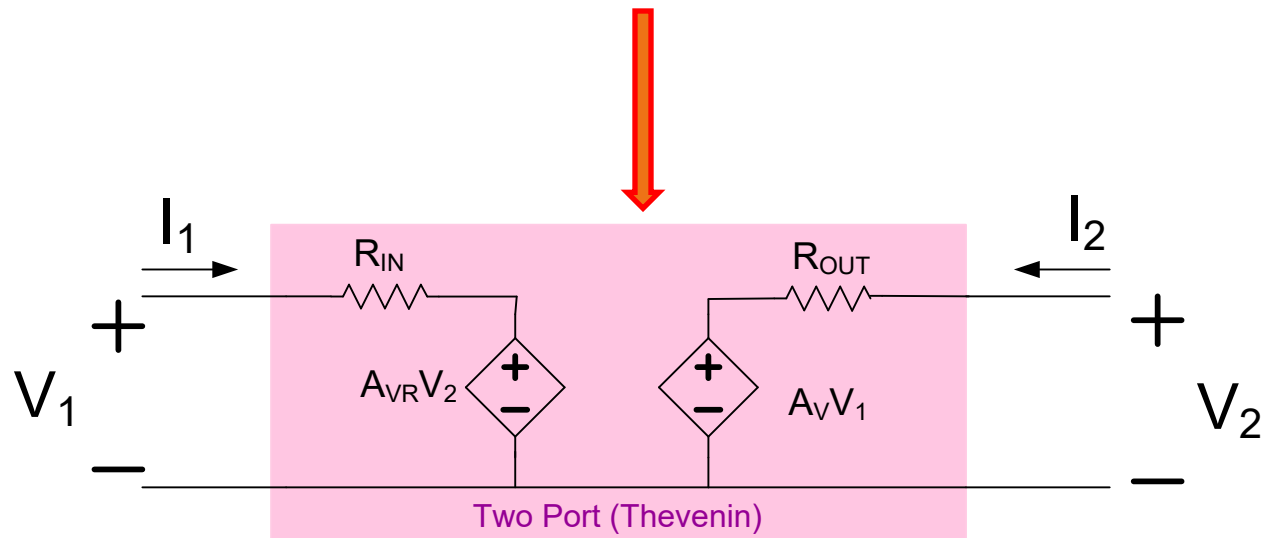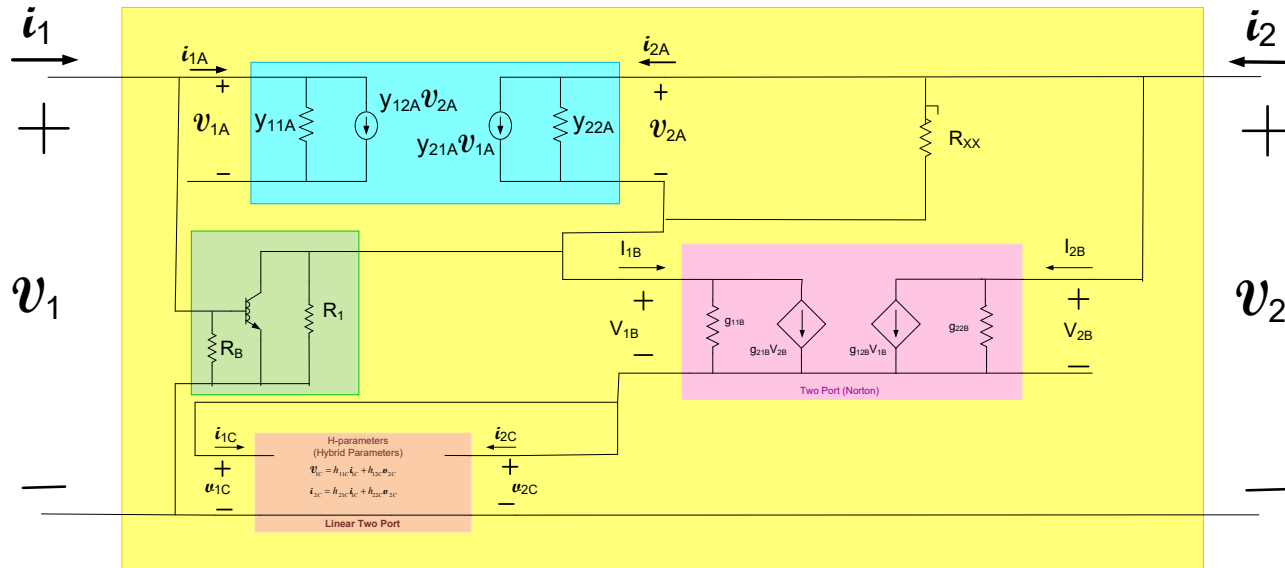

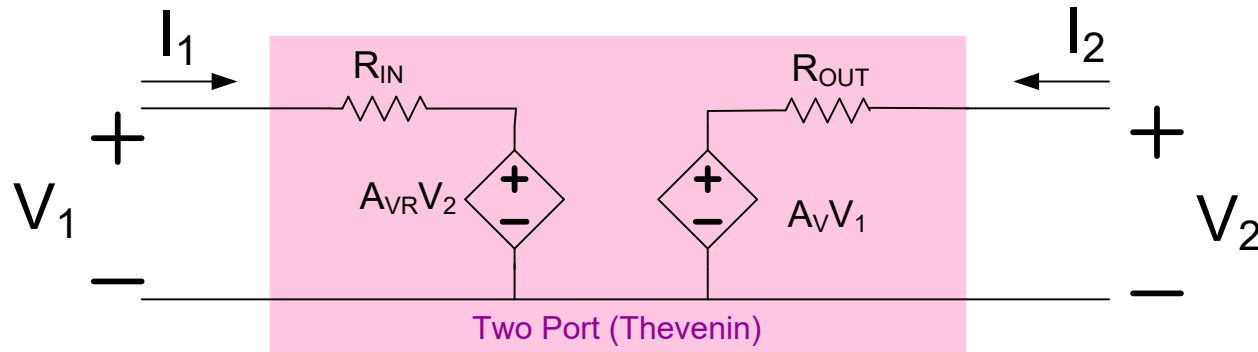Two-Port Equivalents of Interconnected Two-ports



$$v_1 = i_1 R_{in} + A_{VR} v_2$$

$$v_2 = i_2 R_0 + A_{V0} v_1$$


Or equivalently in form where port voltages are the independent variables

$$i_1 = v_1 \left(\frac{1}{R_{in}} \right) + v_2 \left(\frac{-A_{VR}}{R_{in}} \right)$$


$$i_2 = v_1 \left(\frac{-A_{V0}}{R_0} \right) + v_2 \left(\frac{1}{R_0} \right)$$

Determination of two-port small-signal model parameters

(One method will be discussed here)

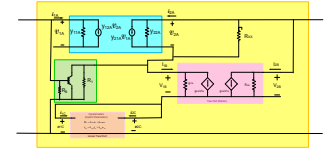

A method of obtaining R_{in}

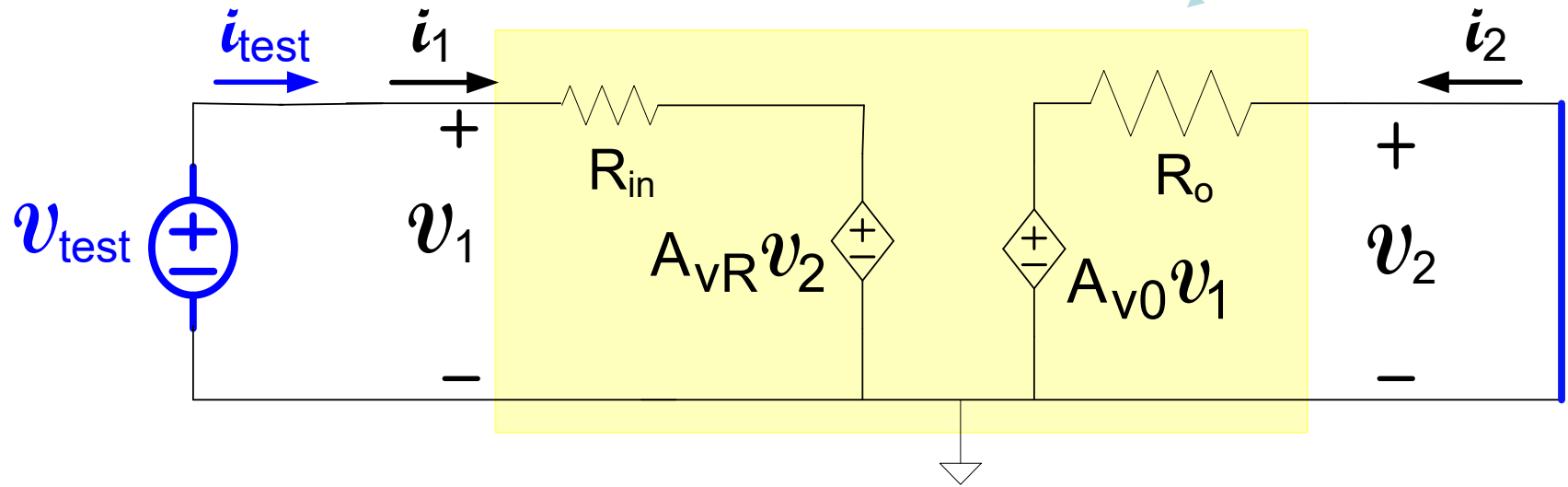


Terminate the output in a (small signal) short-circuit

$$\left. \begin{aligned} i_1 &= v_1 \left(\frac{1}{R_{in}} \right) + v_2 \left(\frac{-A_{VR}}{R_{in}} \right) \\ i_2 &= v_1 \left(\frac{-A_{V0}}{R_0} \right) + v_2 \left(\frac{1}{R_0} \right) \end{aligned} \right\}$$


$$\begin{aligned} v_2 &= 0 \\ v_1 &= v_{test} \\ i_1 &= i_{test} \end{aligned}$$

$$R_{in} = \frac{v_{test}}{i_{test}}$$

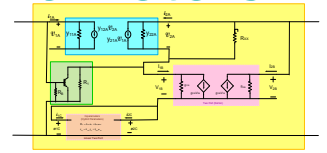Determination of two-port small-signal model parameters



A method of obtaining A_{V0}

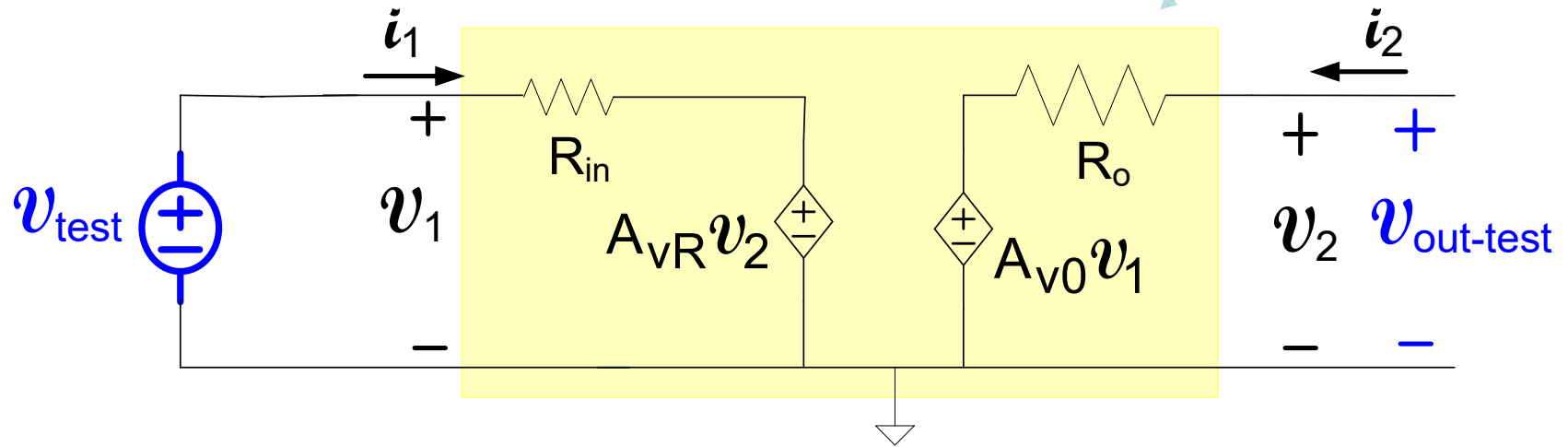


Terminate the output in a (small signal) open-circuit

$$\left. \begin{aligned} i_1 &= v_1 \left(\frac{1}{R_{in}} \right) + v_2 \left(\frac{-A_{VR}}{R_{in}} \right) \\ i_2 &= v_1 \left(\frac{-A_{V0}}{R_o} \right) + v_2 \left(\frac{1}{R_o} \right) \end{aligned} \right\} \begin{array}{l} \xrightarrow{i_2 = 0} \\ v_1 = v_{test} \\ v_2 = v_{out-test} \end{array} \quad A_{V0} = \frac{v_{out-test}}{v_{test}}$$

Determination of two-port small-signal model parameters

A method of obtaining R_0

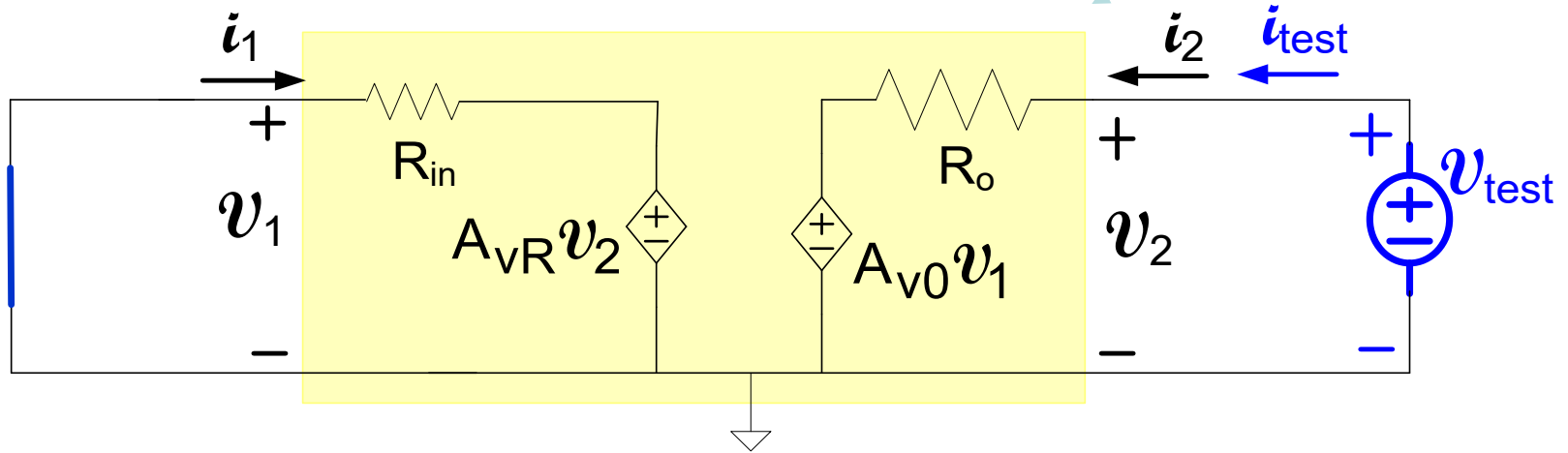


Terminate the input in a (small-signal) short-circuit

$$\left. \begin{aligned} i_1 &= v_1 \left(\frac{1}{R_{in}} \right) + v_2 \left(\frac{-A_{VR}}{R_{in}} \right) \\ i_2 &= v_1 \left(\frac{-A_{V0}}{R_0} \right) + v_2 \left(\frac{1}{R_0} \right) \end{aligned} \right\} \xrightarrow{v_1 = 0} R_0 = \frac{v_{test}}{i_{test}}$$

Determination of two-port small-signal model parameters

A method of obtaining A_{VR}

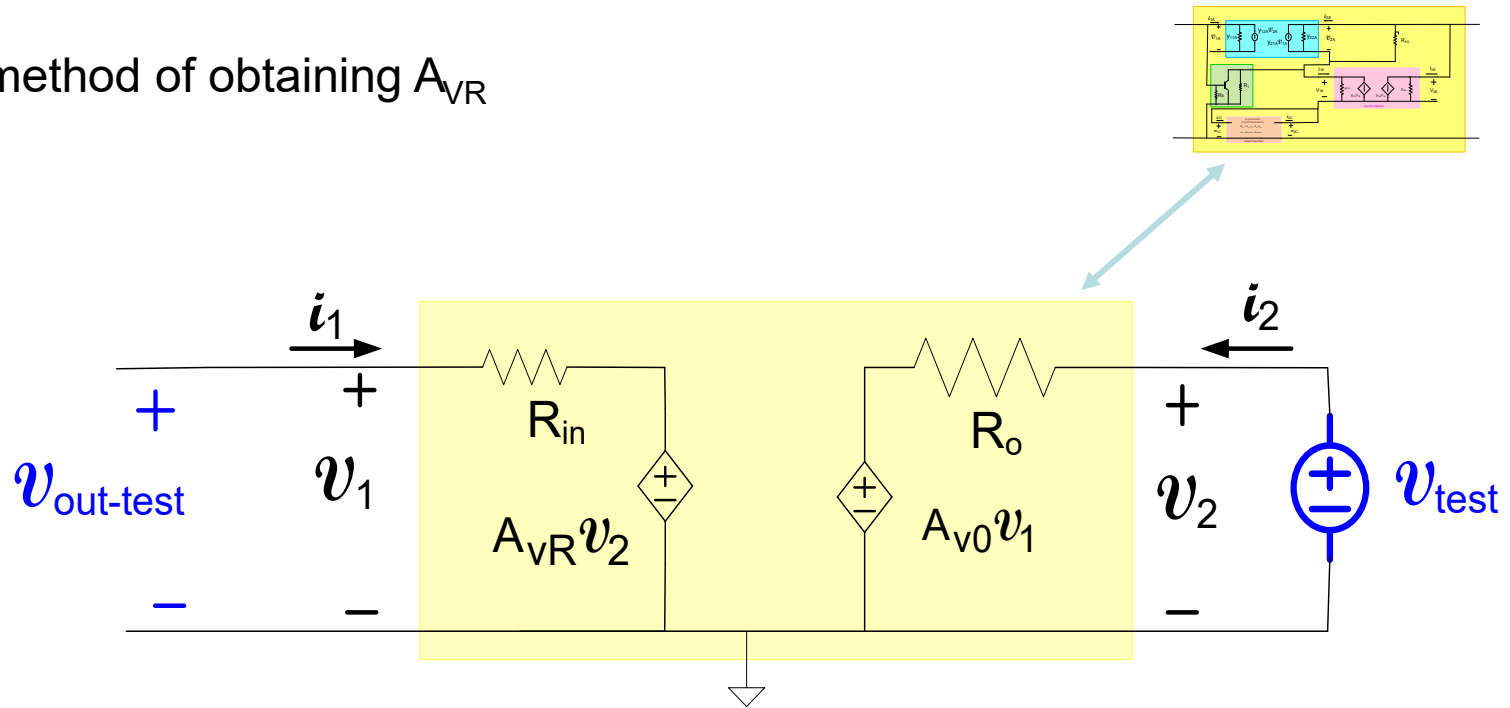

Terminate the input in a (small-signal) open-circuit


$$\left. \begin{aligned} i_1 &= v_1 \left(\frac{1}{R_{in}} \right) - v_2 \left(\frac{A_{VR}}{R_{in}} \right) \\ i_2 &= v_1 \left(\frac{-A_{V0}}{R_0} \right) + v_2 \left(\frac{1}{R_0} \right) \end{aligned} \right\} \xrightarrow{i_1 = 0} A_{VR} = \frac{v_{out-test}}{v_{test}}$$

Determination of Amplifier Two-Port Parameters

- Input and output parameters are obtained in exactly the same way, only distinction is in the notation used for the ports.
- Methods given for obtaining amplifier parameters R_{in} , R_{OUT} and A_V for unilateral networks are a special case of the non-unilateral analysis by observing that $A_{VR}=0$.
- In some cases, other methods for obtaining the amplifier parameters are easier than the “ $V_{TEST} : I_{TEST}$ ” method that was just discussed

Examples

Biassing
Circuit



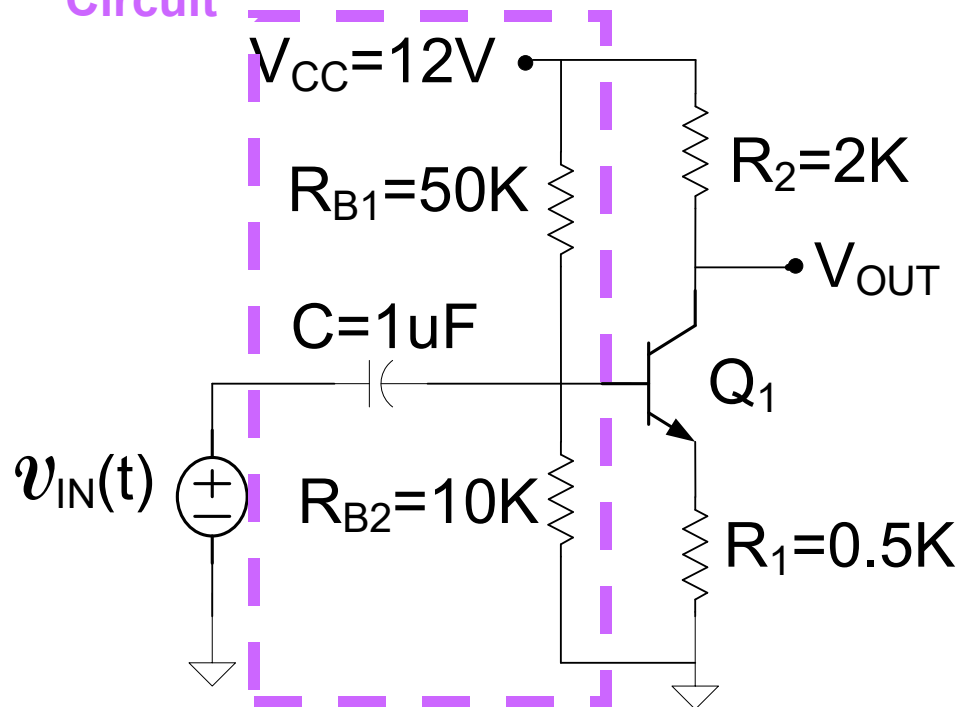


Determine V_{OUTQ} and the SS voltage gain (A_V), assume $\beta=100$

This is a fundamentally different circuit than what we have considered previously !

(A_V is one of the small-signal model parameters for this circuit)



Examples

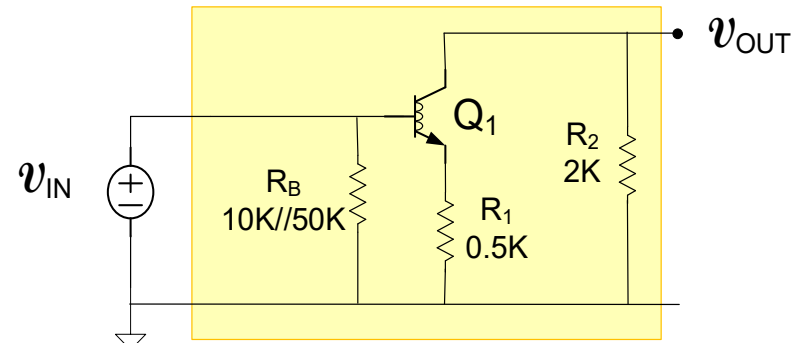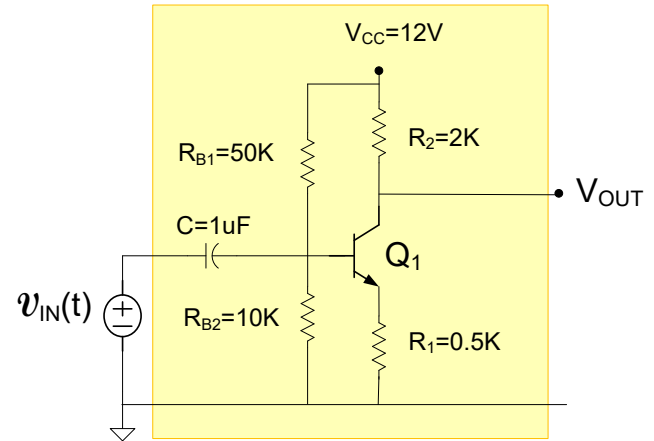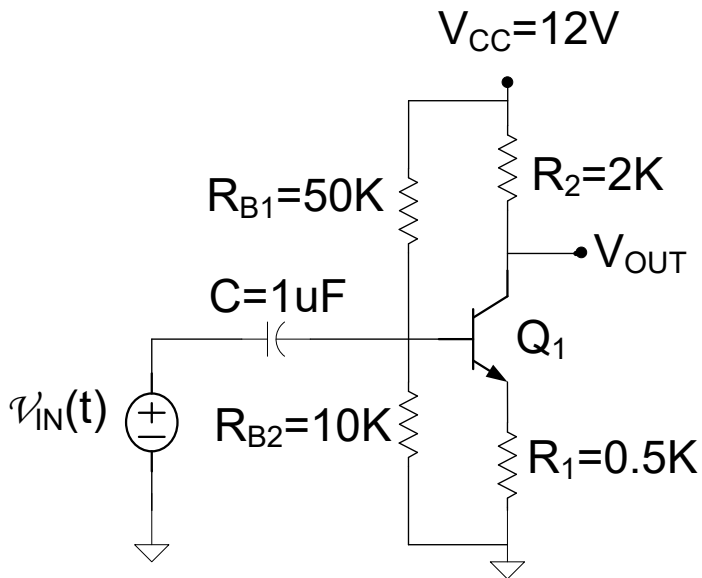

Determine V_{OUTQ} and the SS voltage gain (A_V), assume $\beta=100$


(A_V is one of the small-signal model parameters for this circuit)

Examples

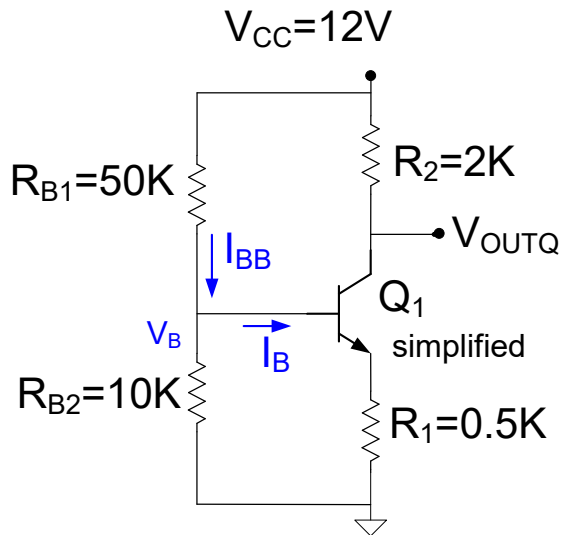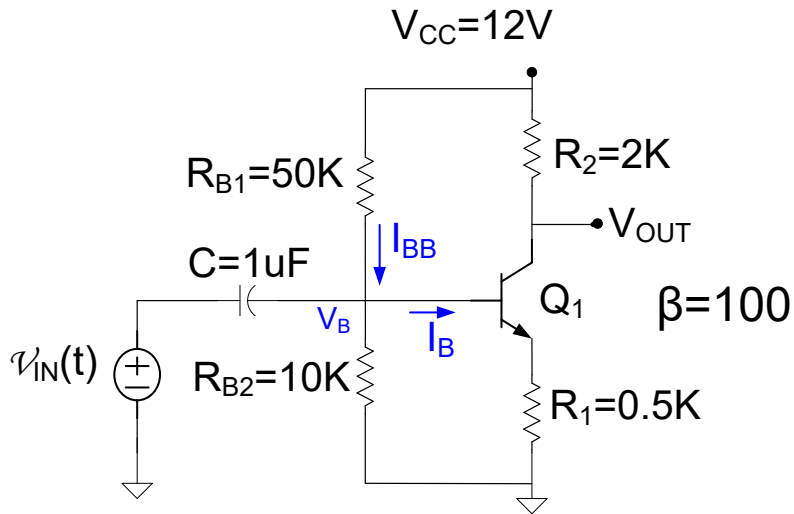

dc equivalent circuit

Determine V_{OUTQ}

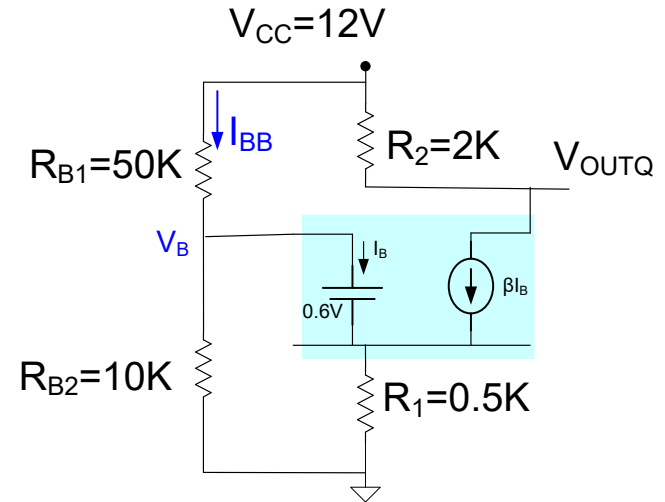

dc equivalent circuit

This circuit is most practical when $I_B \ll I_{BB}$

With this assumption,


$$V_B = \left(\frac{R_{B2}}{R_{B1} + R_{B2}} \right) 12V = 2V$$

$$I_{CQ} = I_{EQ} = \left(\frac{V_B - 0.6V}{R_1} \right) = \frac{1.4V}{.5K} = 2.8mA$$

$$V_{OUTQ} = 12V - I_{CQ} R_1 = 6.4V$$

Note: This Q-point is nearly independent of the characteristics of the nonlinear BJT !

Examples


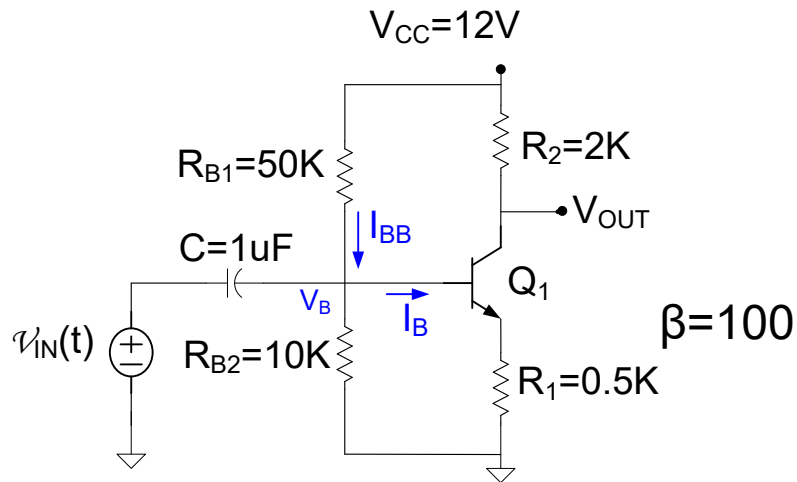


This voltage gain is nearly independent of the characteristics of the nonlinear BJT !

This is a fundamentally different amplifier structure

It can be shown that this is slightly non-unilateral

Determine SS voltage gain

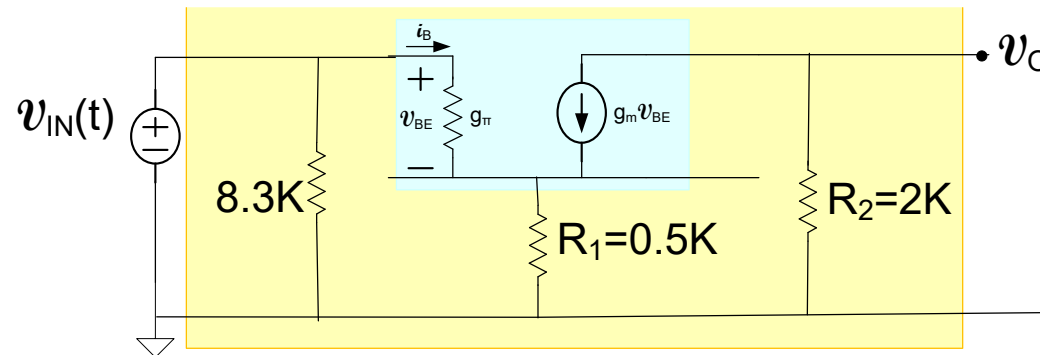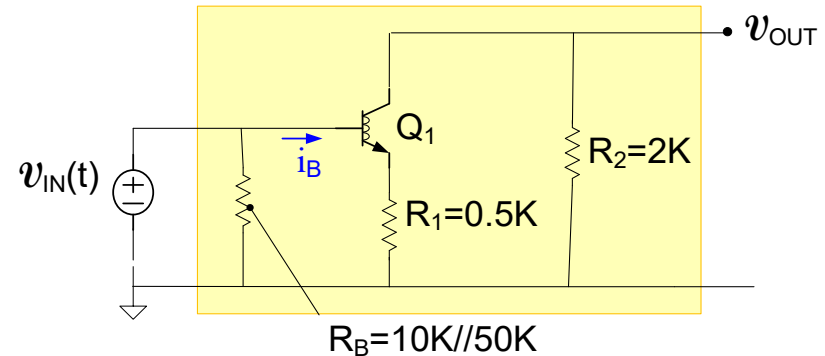

$$v_{OUT} = -g_m v_{BE} R_2$$


$$v_{IN} = v_{BE} + R_1 (v_{BE} [g_\pi + g_m])$$

$$A_V = \frac{-R_2 g_m v_{BE}}{v_{BE} + R_1 (v_{BE} [g_\pi + g_m])} = \frac{-R_2 g_m}{1 + R_1 ([g_\pi + g_m])}$$

$g_m R_1$ typically $\gg 1$

$$A_V \cong \frac{-R_2 g_m}{R_1 g_m} = \frac{-R_2}{R_1} = -4$$

Examples

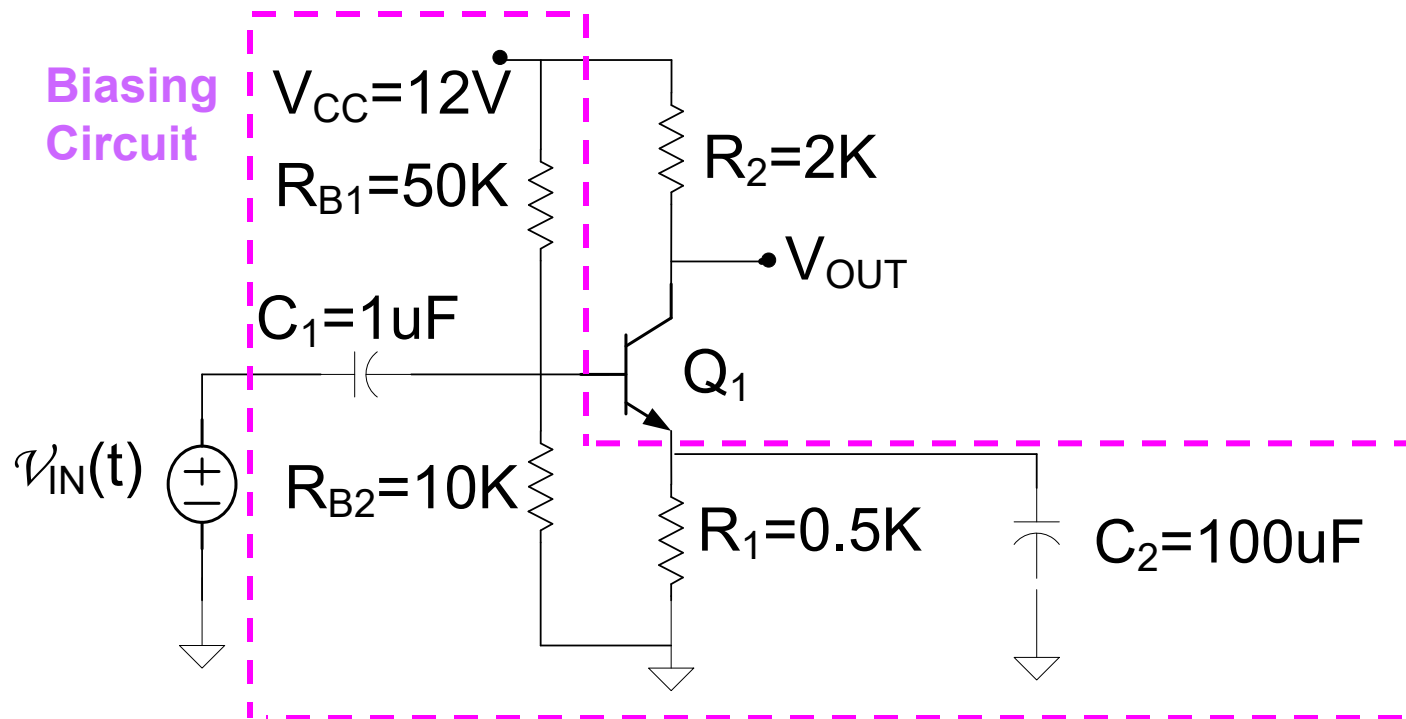

Determine V_{OUTQ} , R_{IN} , R_{OUT} , and the SS voltage gain, and A_{VR} assume $\beta = 100$



Examples

Determine V_{OUTQ} ✓

This is the same as the previous circuit !

$$V_{OUTQ} = 6.4V$$




$$I_{CQ} = \frac{5.6V}{2K} = 2.8mA$$

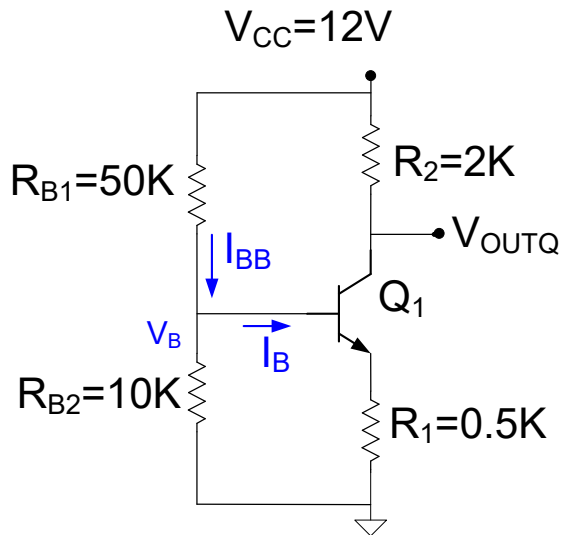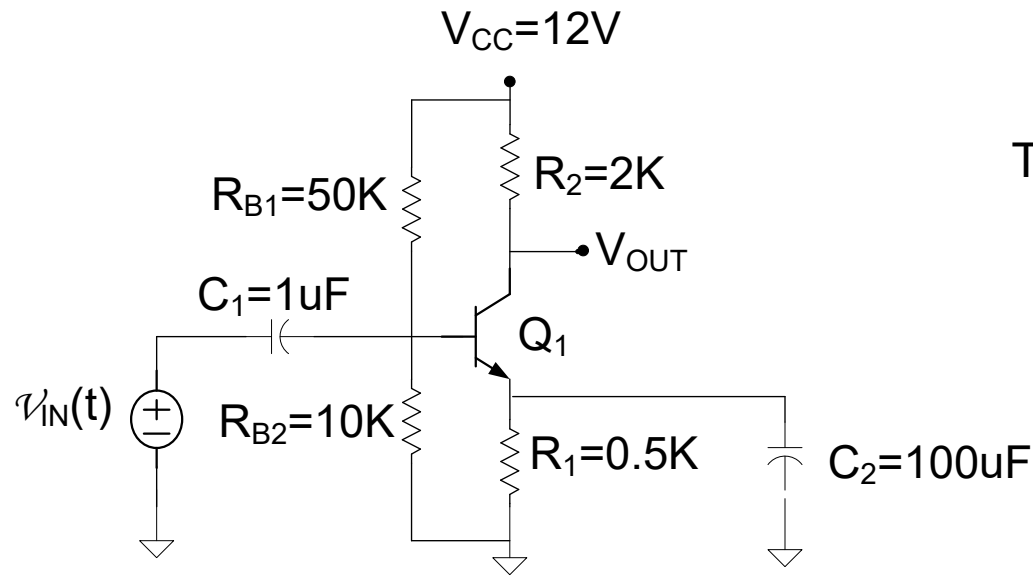

The dc equivalent circuit

Note: This Q-point is nearly independent of the characteristics of the nonlinear BJT !

Examples

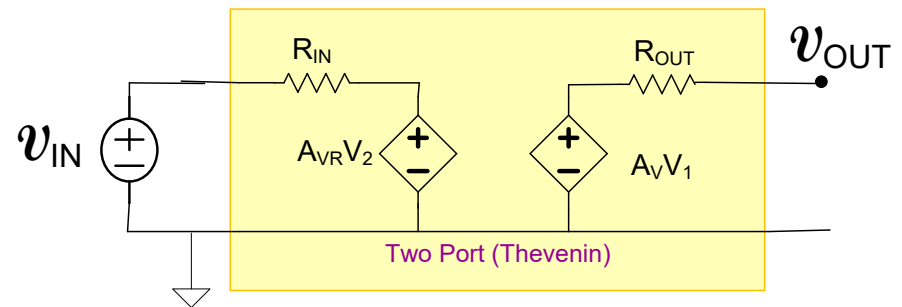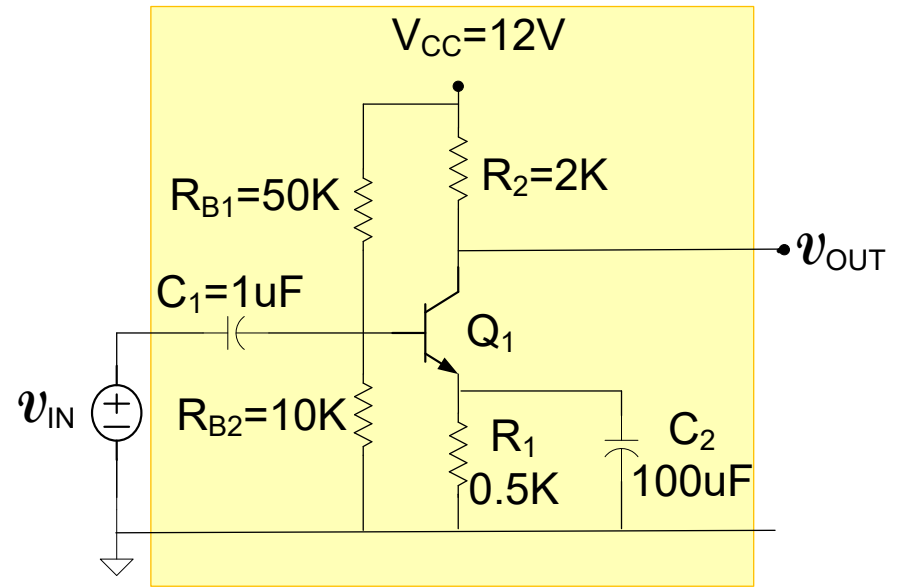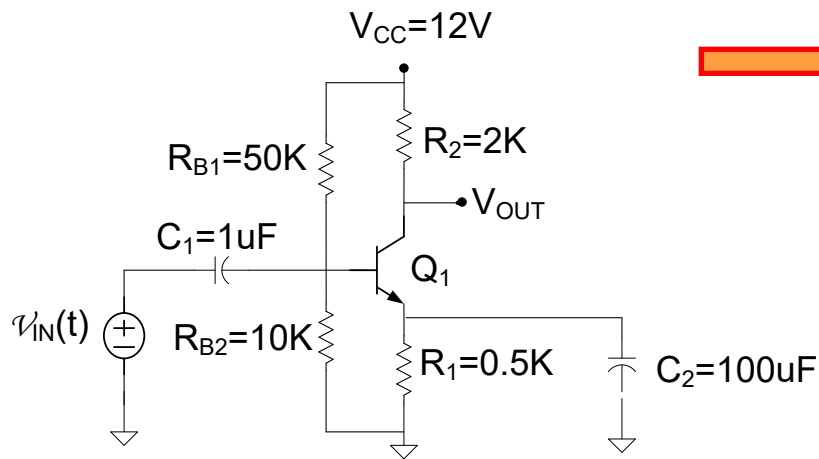


Determine V_{OUTQ} , R_{IN} , R_{OUT} , A_V , and A_{VR} ; assume $\beta=100$

(A_V , R_{IN} , R_{OUT} , and A_{VR} are the small-signal model parameters for this circuit)

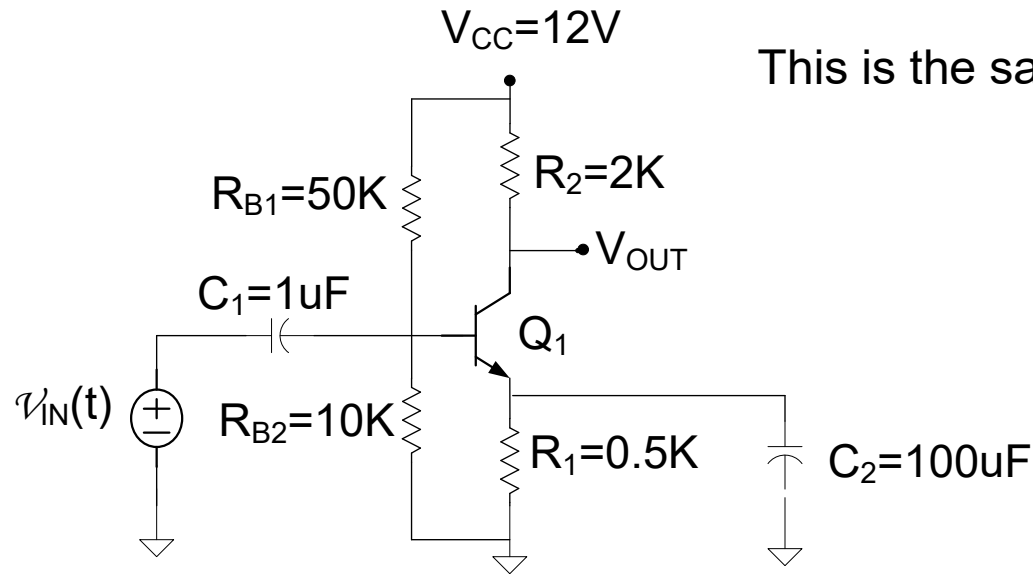Examples


Determine the SS voltage gain A_V

This is the same as another previous-previous circuit !



$$A_V \cong -g_m R_2$$

$$A_V \cong -\frac{I_{CQ} R_2}{V_t}$$

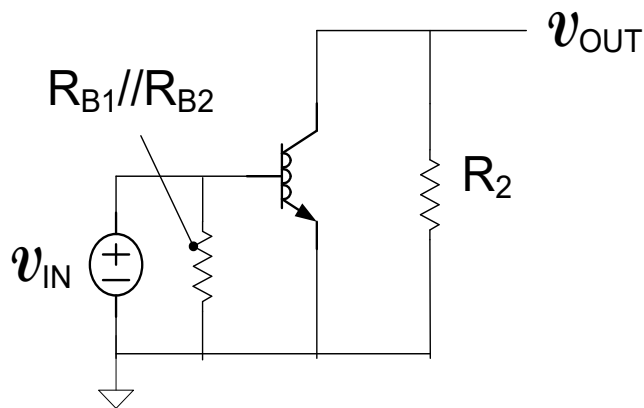


$$A_V \cong -\frac{5.6V}{26mV} = -215$$

The SS equivalent circuit



Note: This Gain is nearly independent of the characteristics of the nonlinear BJT !

Examples

Determination of R_{IN}

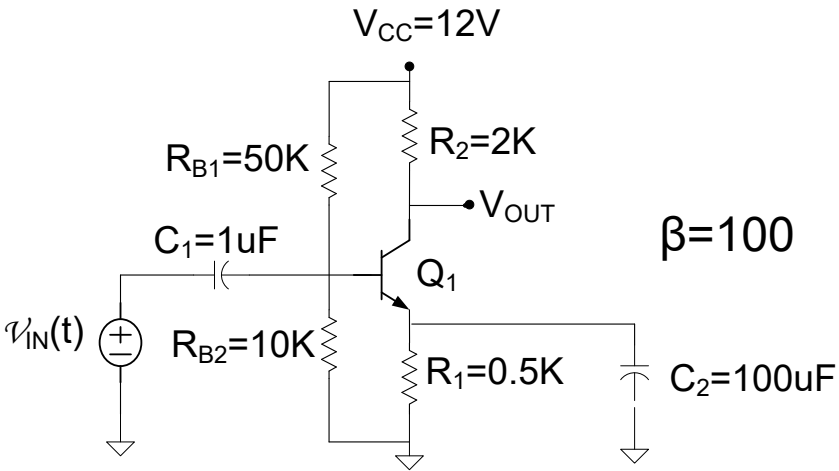

The SS equivalent circuit


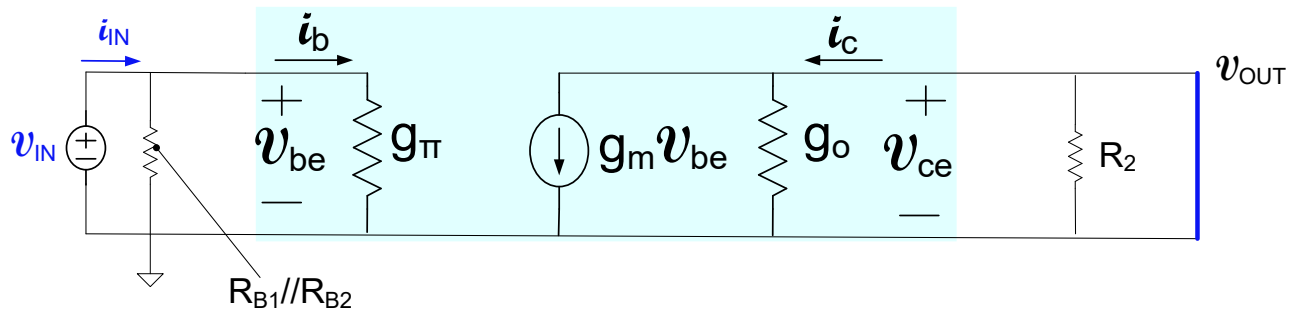
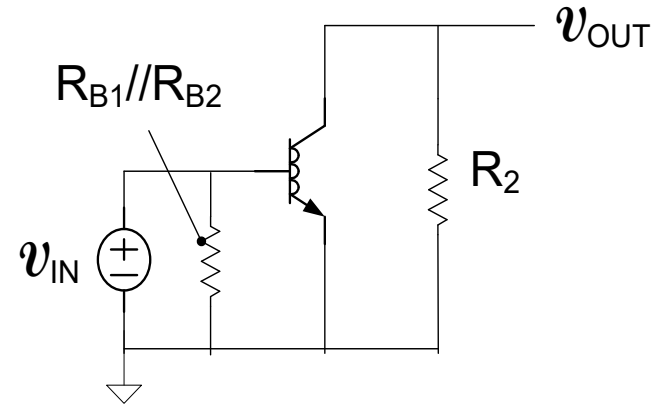


$$R_{IN} = R_{B1} // R_{B2} // r_{\pi} \cong r_{\pi}$$

$$r_{\pi} = \left(\frac{I_{CQ}}{\beta V_t} \right)^{-1} = \left(\frac{2.8\text{mA}}{100 \cdot 26\text{mV}} \right)^{-1} = 928\Omega$$

$$R_{IN} = R_{B1} // R_{B2} // r_{\pi} \cong r_{\pi} = 930\Omega$$

Examples Determination of R_{OUT}

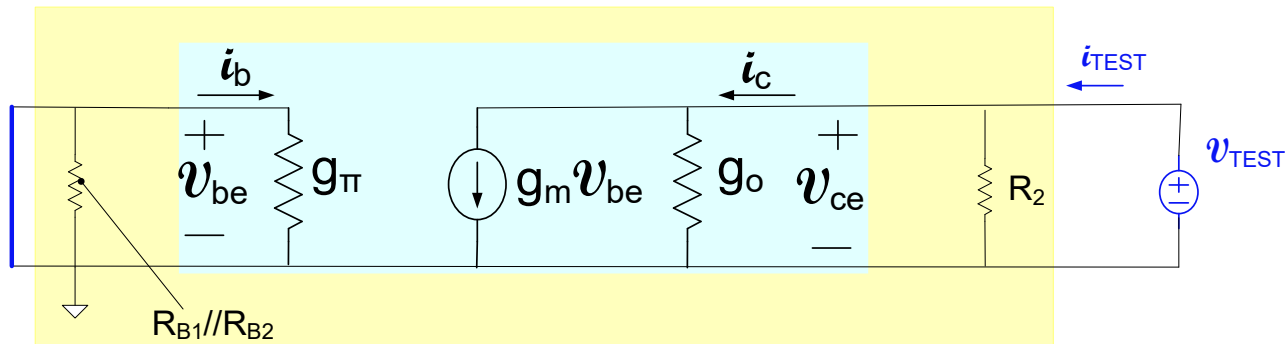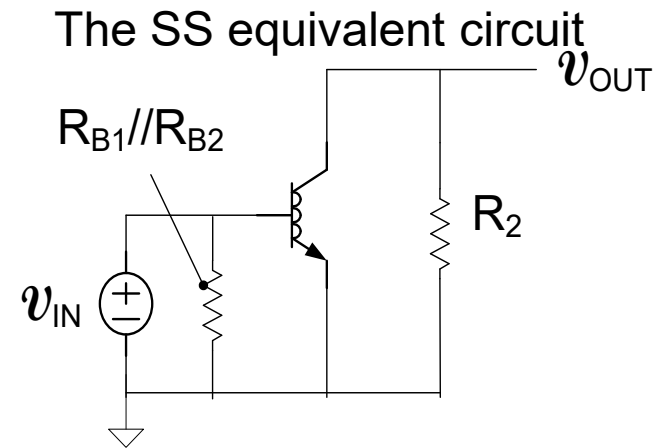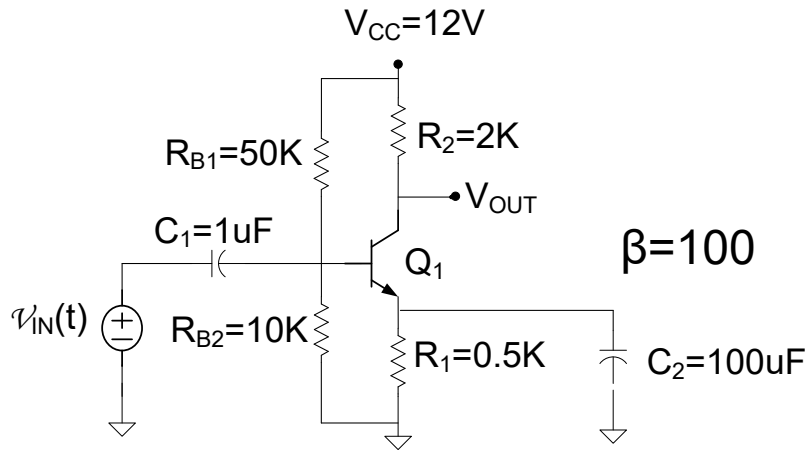


$$R_{OUT} = \frac{v_{TEST}}{i_{TEST}} = R_2 // r_o$$

$$r_o = \left(\frac{I_{CQ}}{V_{AF}} \right)^{-1} = \left(\frac{2.8\text{mA}}{200\text{V}} \right)^{-1} = (1.4\text{E-}5)^{-1} = 71\text{K}\Omega$$



$$R_{OUT} = R_2 // r_o \cong R_2 = 2\text{K}$$

Examples

Determine A_{VR}

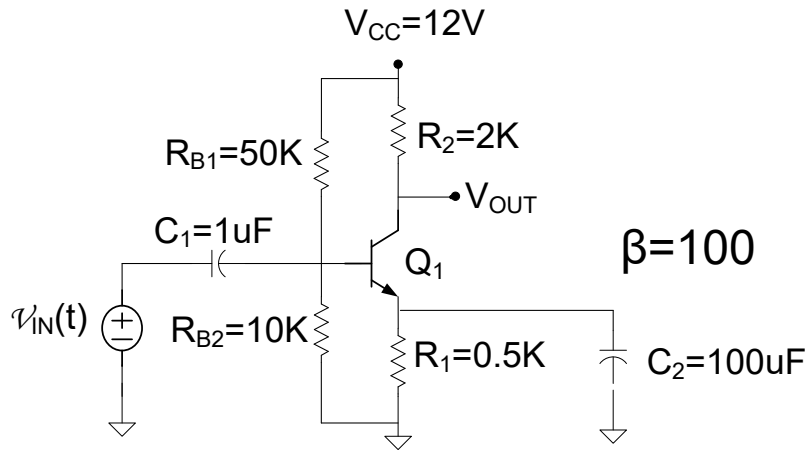



The SS equivalent circuit

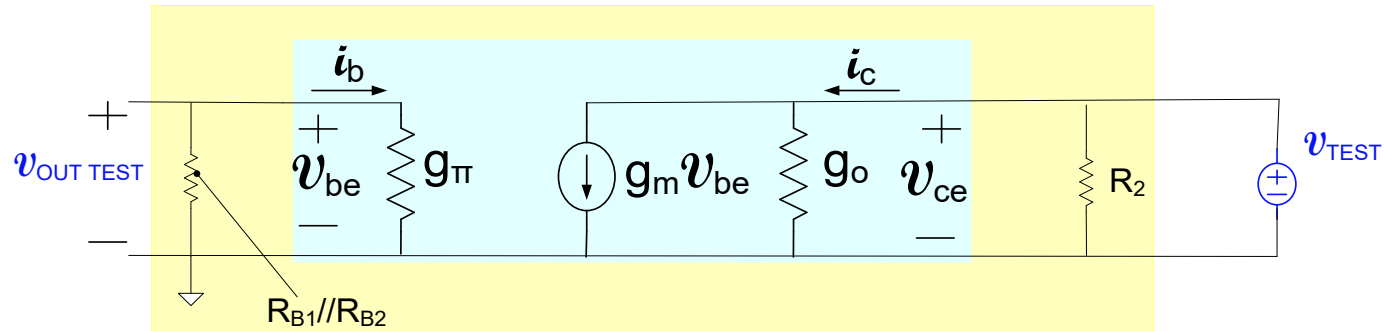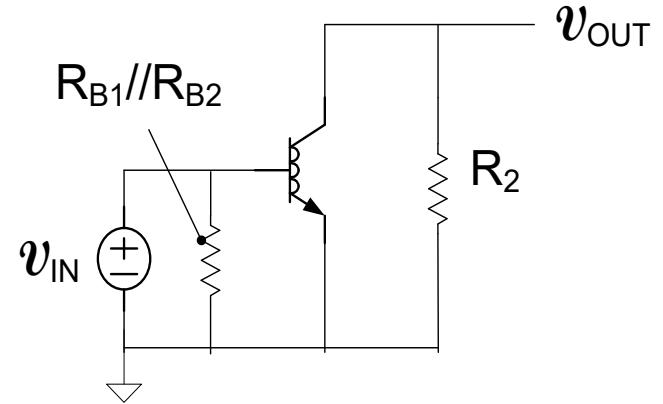

$$v_{OUT TEST} = 0$$

$$A_{VR} = 0$$

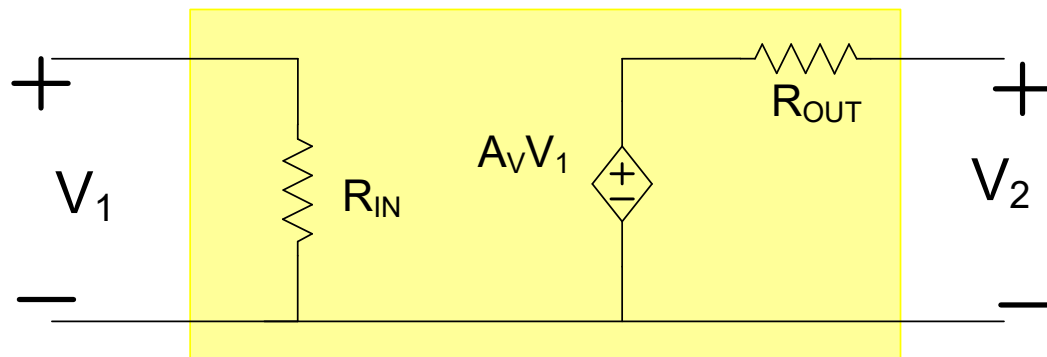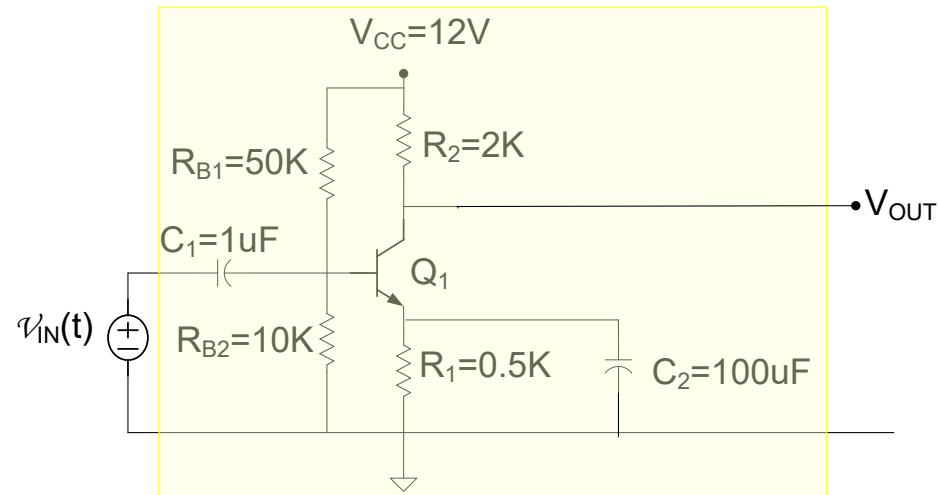Determination of small-signal two-port representation




$$A_V \cong -215$$

$$R_{IN} \cong r_{\pi} = 930\Omega$$


$$R_{OUT} \cong R_2 = 2K$$

This is the same basic amplifier that was considered many times

Relationship with Dependent Sources ?

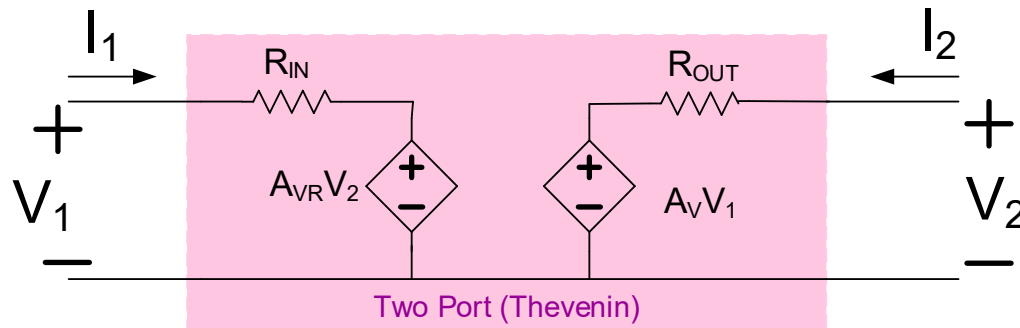


Dependent sources from EE 201

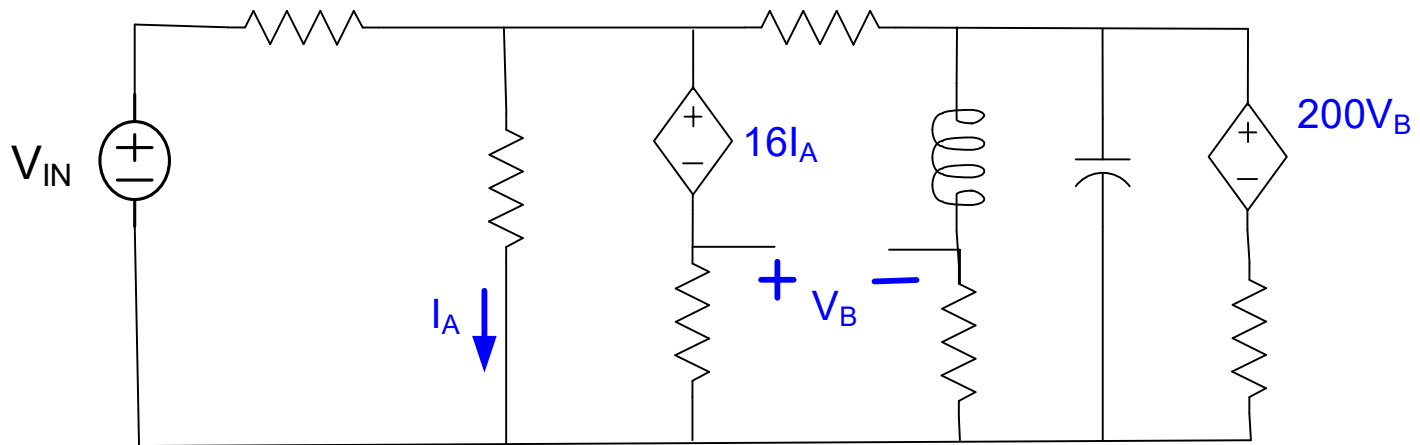

Example showing two dependent sources

Relationship with Dependent Sources ?

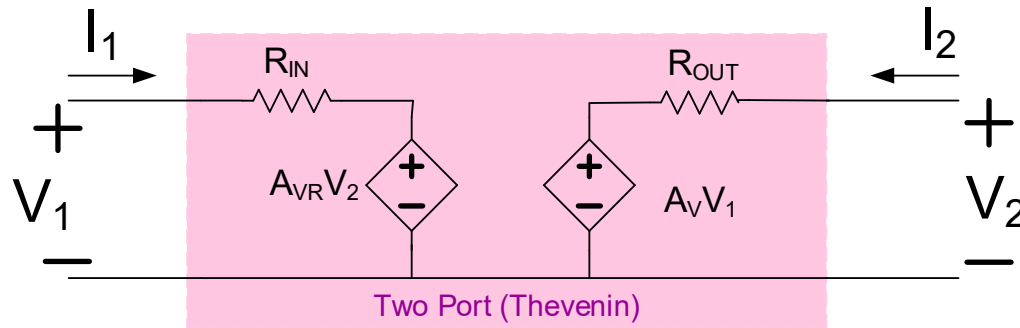

Dependent sources from EE 201

Voltage Amplifier

$$v_s = \mu v_x$$

Voltage Dependent Voltage Source

$$I_s = \alpha v_x$$

Voltage Dependent Current Source

Transconductance Amplifier

Transresistance Amplifier

$$v_s = \rho I_x$$


Current Dependent Voltage Source

$$I_s = \beta I_x$$


Current Dependent Current Source

Current Amplifier

Relationship with Dependent Sources ?

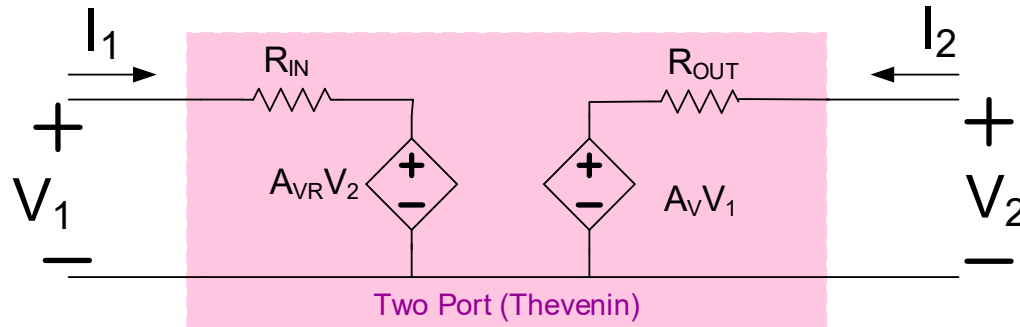


It follows that

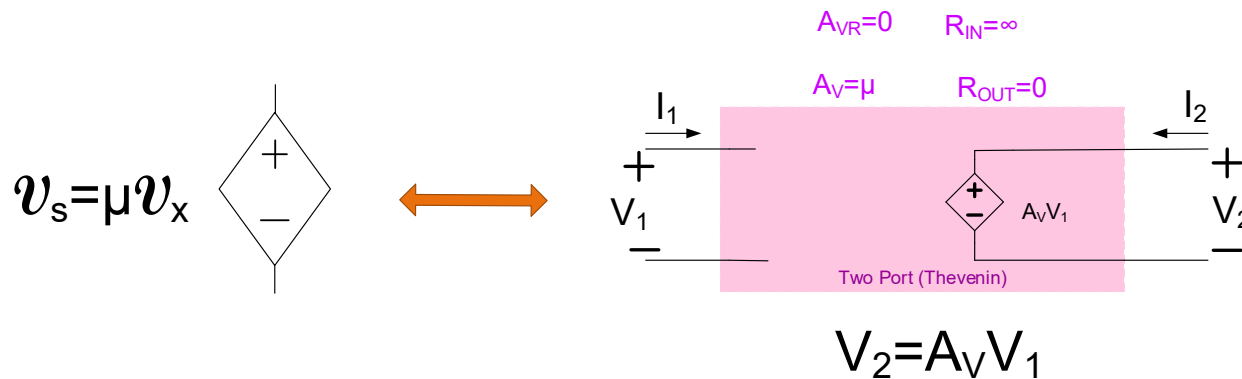


Voltage dependent voltage source is a unilateral floating two-port voltage amplifier with $R_{IN} = \infty$ and $R_{OUT} = 0$

Relationship with Dependent Sources ?

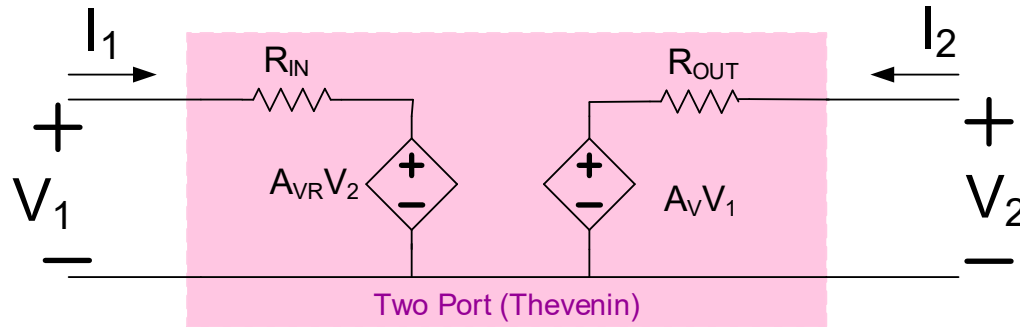


It follows that

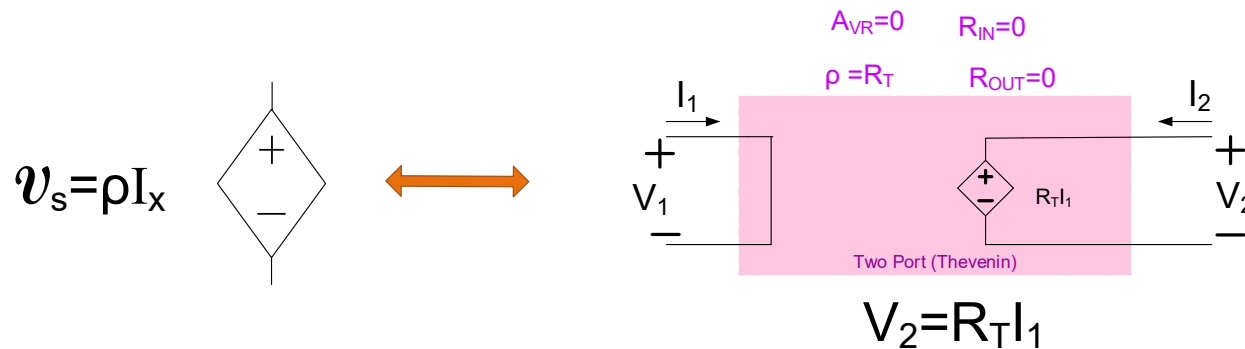


Current dependent voltage source is a unilateral floating two-port transresistance amplifier with $R_{IN}=0$ and $R_{OUT}=0$

Relationship with Dependent Sources ?

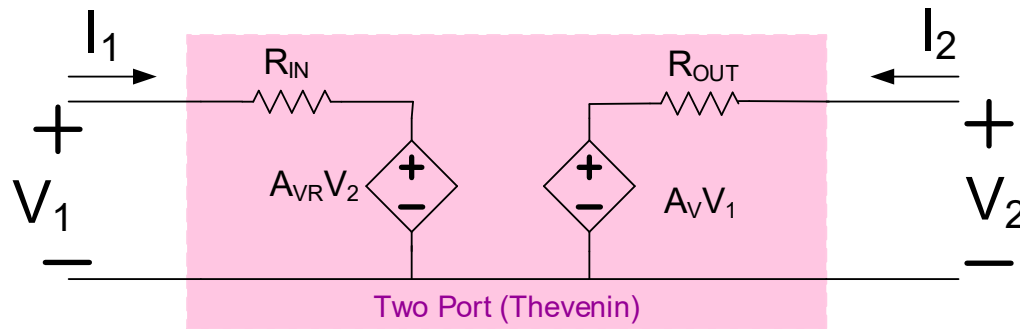


It follows that

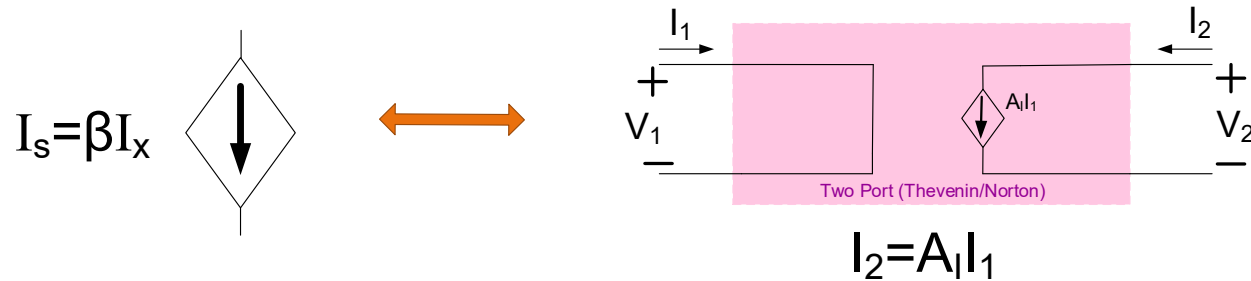


Current dependent current source is a floating unilateral two-port current amplifier with $R_{IN} = 0$ and $R_{OUT} = \infty$

Relationship with Dependent Sources ?


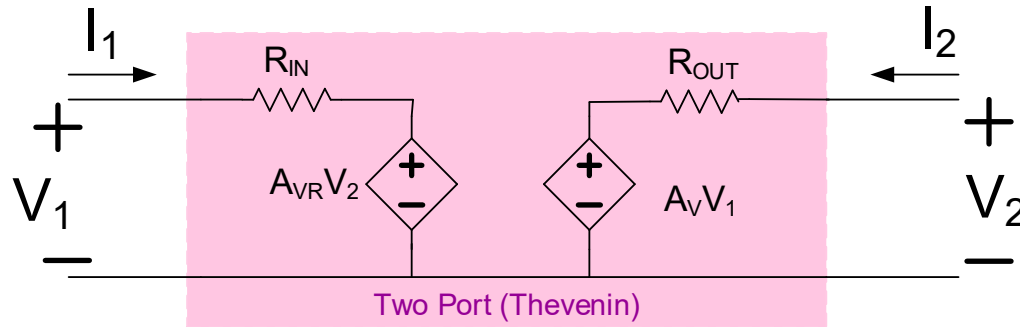


It follows that

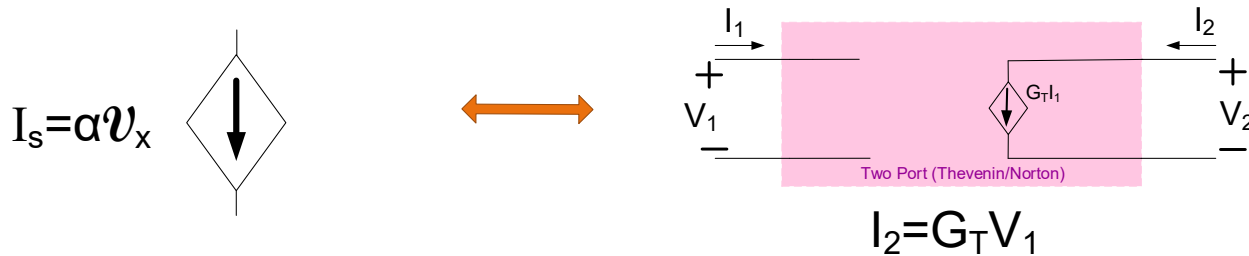

Voltage dependent current source is a floating unilateral two-port transconductance amplifier with $R_{IN} = \infty$ and $R_{OUT} = \infty$

Dependent Sources

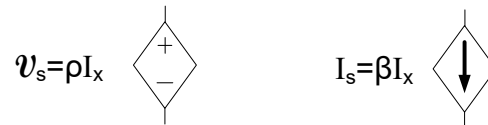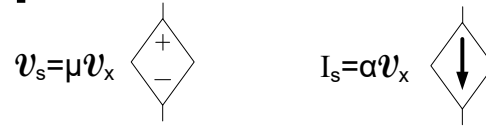

Dependent sources are unilateral two-port amplifiers with ideal input and output impedances

Dependent sources do not exist as basic circuit elements but amplifiers can be designed to perform approximately like a dependent source

- Practical dependent sources typically are not floating on input or output
- One terminal is usually grounded
- Input and output impedances of realistic structures are usually not ideal

Why were “dependent sources” introduced as basic circuit elements instead of two-port amplifiers in the basic circuits courses???

Why was the concept of “dependent sources” not discussed in the basic electronics courses???






Stay Safe and Stay Healthy !

End of Lecture 28



Basic Amplifier Structures

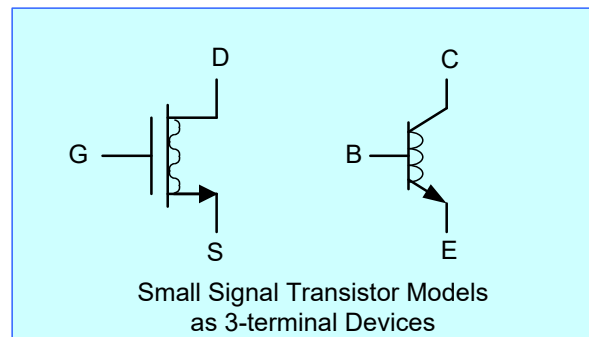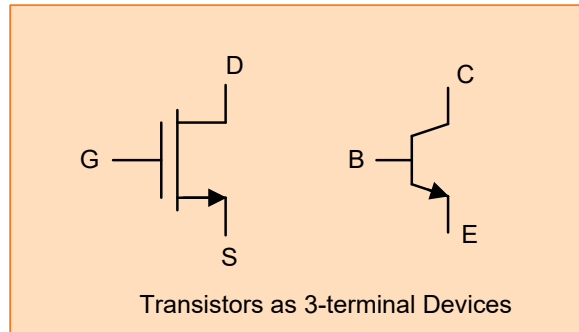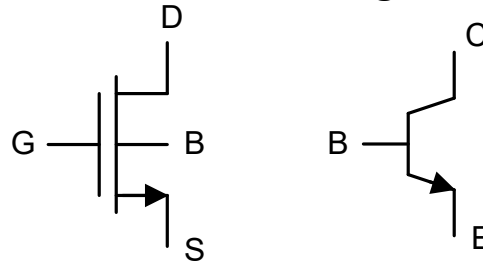- MOS and Bipolar Transistors both have 3 primary terminals
- MOS transistor has a fourth terminal that is generally considered a parasitic terminal



Basic Amplifier Structures

Observation:

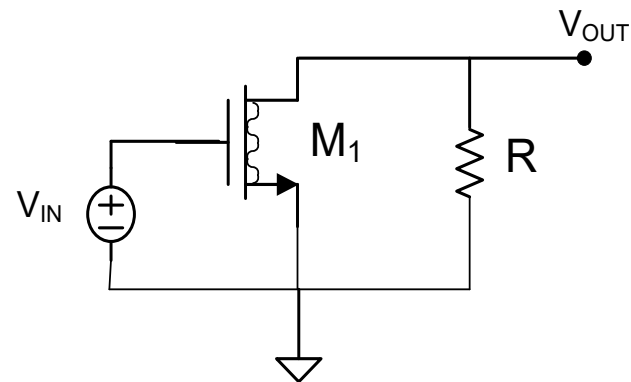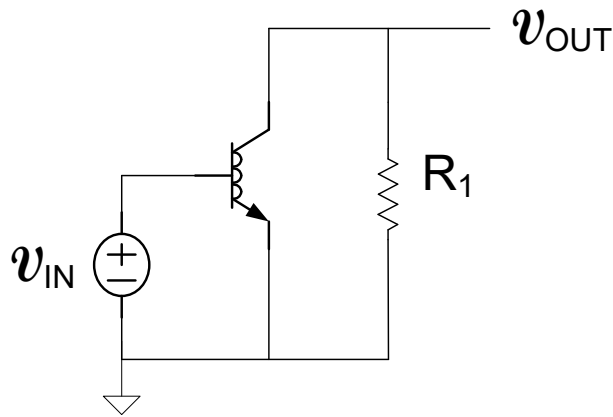

These circuits considered previously have a terminal (emitter or source) common to the input and output in the small-signal equivalent circuit


For BJT, E is common, input on B, output on C

Termed “Common Emitter”

For MOSFET, S is common, input on G, output on D

Termed “Common Source”

Basic Amplifier Structures

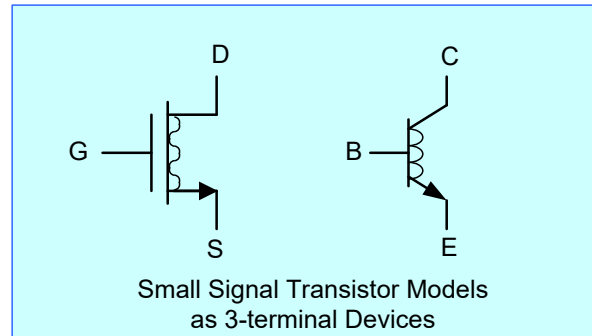


Amplifiers using these devices generally have one terminal common and use remaining terminals as input and output

Since devices are nearly unilateral, designation of input and output terminals is uniquely determined

Three different ways to designate the common terminal

Source or Emitter	termed Common Source or Common Emitter
Gate or Base	termed Common Gate or Common Base
Drain or Collector	termed Common Drain or Common Collector

Basic Amplifier Structures

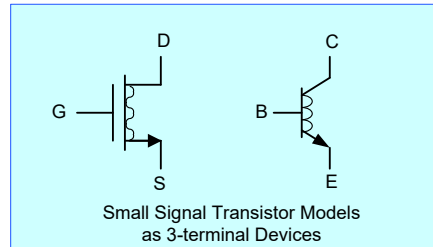

	MOS			BJT		
	Common	Input	Output	Common	Input	Output
Common Source or Common Emitter	S	G	D	E	B	C
Common Gate or Common Base	G	S	D	B	E	C
Common Drain or Common Collector	D	G	S	C	B	E

Identification of Input and Output Terminals is not arbitrary

It will be shown that all 3 of the basic amplifiers are useful !