

# EE 330

## Lecture 33









- High Gain Amplifiers
- Current Sources and Mirrors

# Fall 2024 Exam Schedule

Exam 1	Friday	Sept 27
Exam 2	Friday	October 25
Exam 3	Friday	Nov 22
Final Exam	Monday	Dec 16 12:00 - 2:00 PM

# Review From Previous Lecture

## Basic Amplifier Application Gain Table

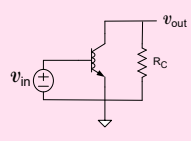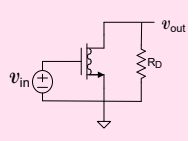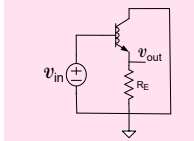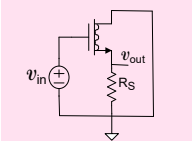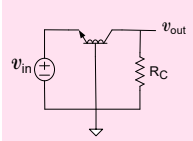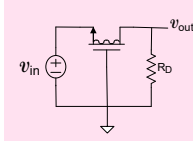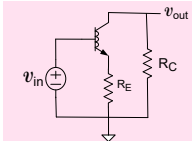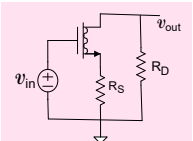	CE/CS		CC/CD		CB/CG		CEwRE/CSwRS	
	BJT	MOS	BJT	MOS	BJT	MOS	BJT	MOS
$A_V$	 $-g_m R_C$ $\frac{I_{CQ} R_C}{V_t}$	 $-\frac{2I_{DQ} R_D}{V_{EB}}$	 $\frac{g_m}{g_m + g_E}$ $\frac{I_{CQ} R_E}{I_{CQ} R_E + V_t}$	 $\frac{2I_{DQ} R_E}{2I_{DQ} R_E + V_{EB}}$	 $g_m R_C$ $\frac{I_{CQ} R_C}{V_t}$	 $\frac{2I_{DQ} R_C}{V_{EB}}$	 $-\frac{R_C}{R_E}$	
$R_{in}$	$r_{\pi}$ $\frac{\beta V_t}{I_{CQ}}$	$\infty$	$r_{\pi} + \beta R_E$ $\beta \left( \frac{V_t}{I_{CQ}} + R_E \right)$	$\infty$	$g_m^{-1}$ $\frac{V_t}{I_{CQ}}$	$\frac{V_{EB}}{2I_{DQ}}$	$r_{\pi} + \beta R_E$ $\beta \left( \frac{V_t}{I_{CQ}} + R_E \right)$	$\infty$
$R_{out}$	$R_C$		$g_m^{-1}$ $\frac{V_t}{I_{CQ}}$	$\frac{V_{EB}}{2I_{DQ}}$	$R_C$		$R_C$	


(not two-port models for the four structures)

Can use these equations only when small signal circuit is EXACTLY like that shown !!

# Summary of Missing Material from Lecture 32


Start Here:

# Basic Amplifier Structures


1. Common Emitter/Common Source
  2. Common Collector/Common Drain
  3. Common Base/Common Gate
  4. Common Emitter with  $R_E$ / Common Source with  $R_S$
  5. Cascode (actually CE:CB or CS:CG cascade)
  6. Darlington (special CC:CE or CD:CS cascade)
- 
- Will be discussed later

The first 4 are most popular

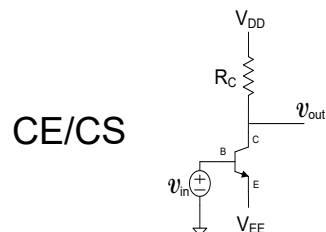
# Basic Amplifier Characteristics Summary



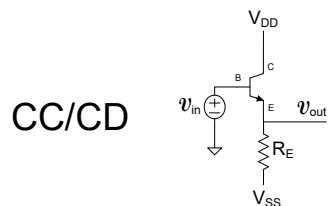
- Large inverting gain
- Moderate input impedance
- Moderate (or high) output impedance
- Widely used as the basic high gain inverting amplifier



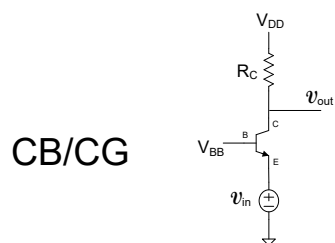- Gain very close to +1 (little less)
- High input impedance for BJT (high for MOS)
- Low output impedance
- Widely used as a buffer




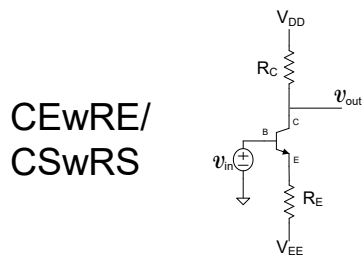- Large noninverting gain
- Low input impedance
- Moderate (or high) output impedance
- Used more as current amplifier or, in conjunction with CD/CS to form two-stage cascode



- Reasonably accurate but somewhat small gain (resistor ratio)
- High input impedance
- Moderate output impedance
- Used when more accurate gain is required


# Cascaded Amplifiers

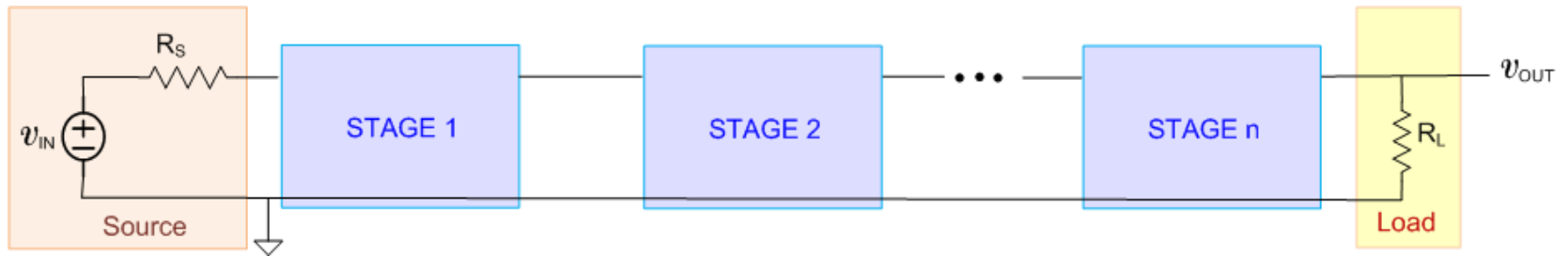

- Amplifier cascading widely used to enhance gain
- Amplifier cascading widely used to enhance other characteristics and/or alter functionality as well  
e.g. ( $R_{IN}$ , BW, Power,  $R_O$ , Linearity, Impedance Conversion.. )


# Cascaded Amplifier Analysis and Operation

## Adjacent Stage Coupling Only

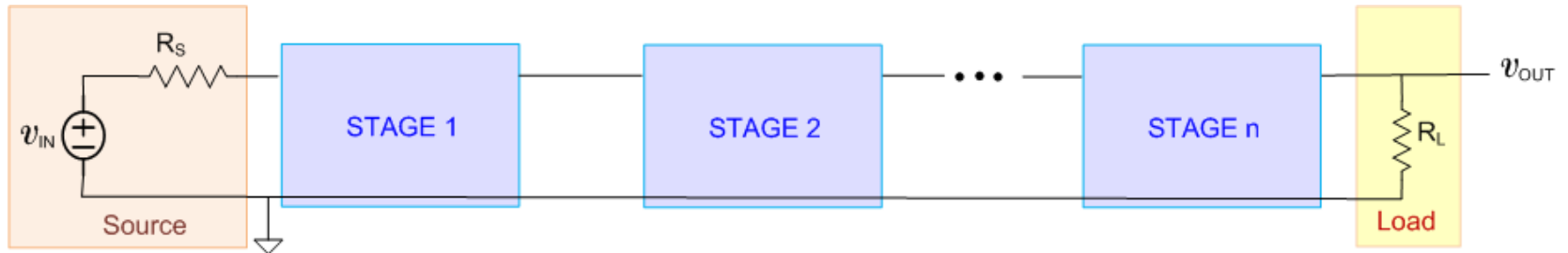

- Systematic Methods of Analysis/Design will be Developed
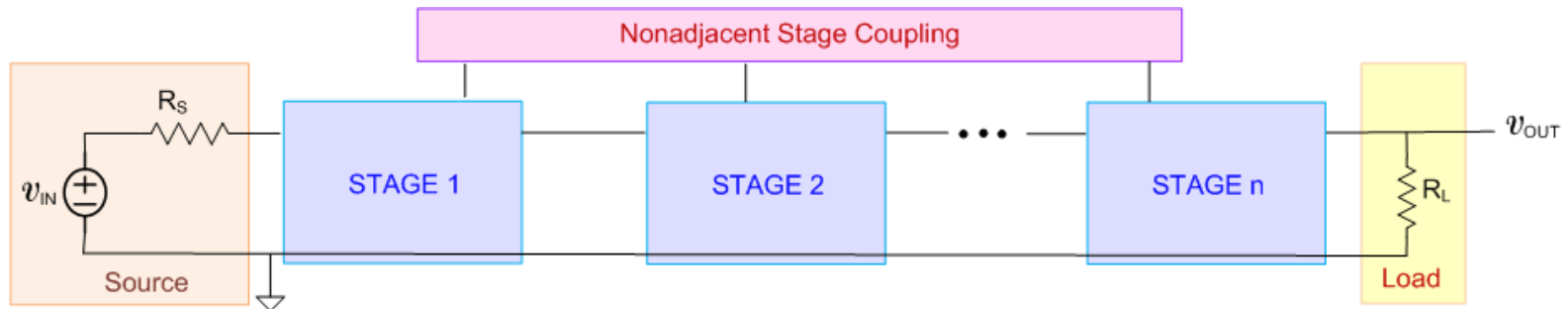
## One or more couplings of nonadjacent stages




- Less Common
- Analysis Generally Much More Involved, Use Basic Circuit Analysis Methods



Repeat from earlier discussions on amplifiers

# Cascaded Amplifier Analysis and Operation

Case 1: All stages Unilateral

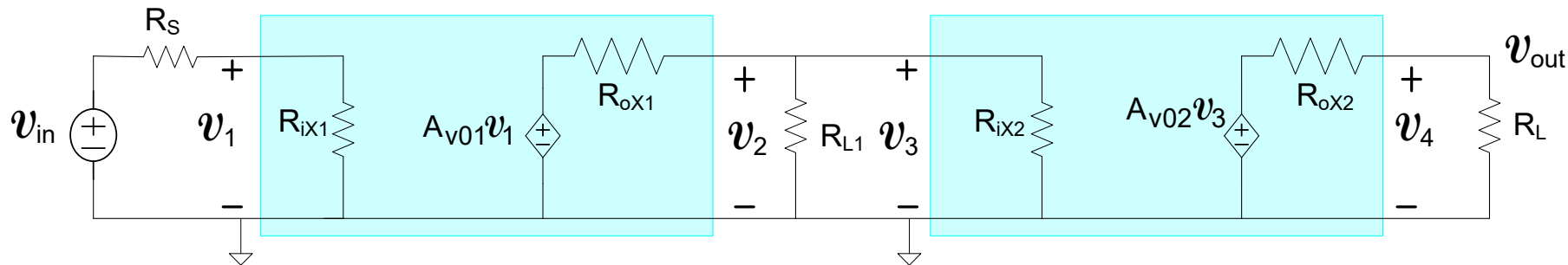


$$A_V = \frac{v_{out}}{v_{in}} = \left( \frac{R_{iX1}}{R_{iX1} + R_S} \right) A_{V01} \left( \frac{R_{L1} // R_{iX2}}{R_{L1} // R_{iX2} + R_{oX1}} \right) A_{V02} \left( \frac{R_L}{R_L + R_{oX2}} \right)$$

**Accounts for all loading between stages !**

# Cascaded Amplifier Analysis and Operation


Case 2: One or more stages are not unilateral

## ➤ Standard two-port cascade

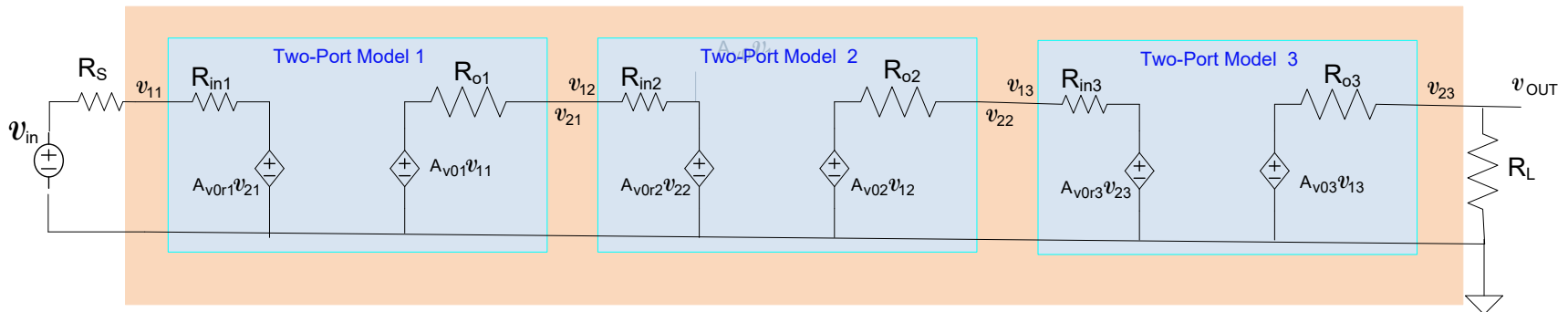

Analysis by creating new two-port of entire amplifier quite tedious because of the reverse-gain elements

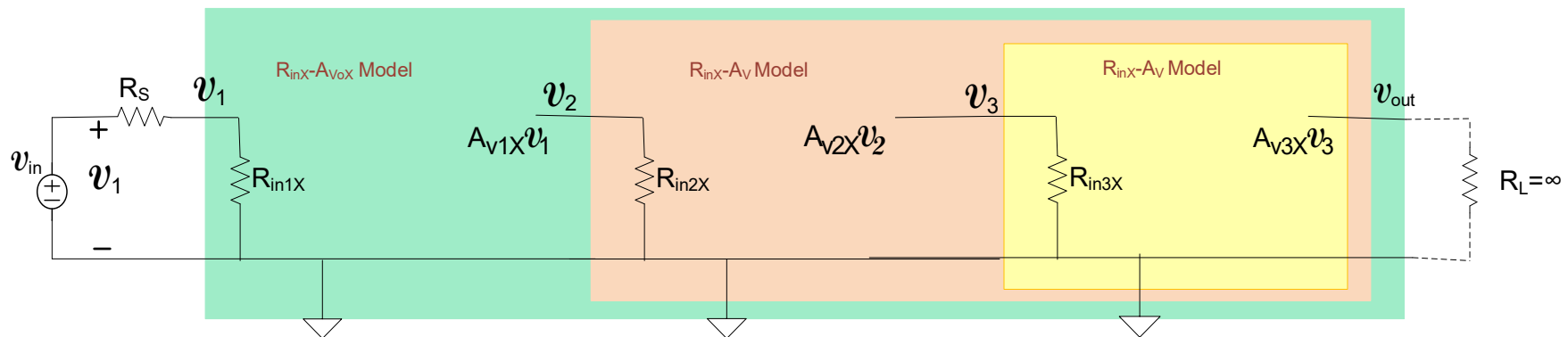
## ➤ Right-to-left nested $R_{inx}$ , $A_{VKX}$ approach



- $R_{inx}$  includes effects of all loading
- $A_{VKX}$  is the voltage ratio from input to output of a stage
- $A_{VKX}$ 's include all loading
- Can not change any loading without recalculating everything!


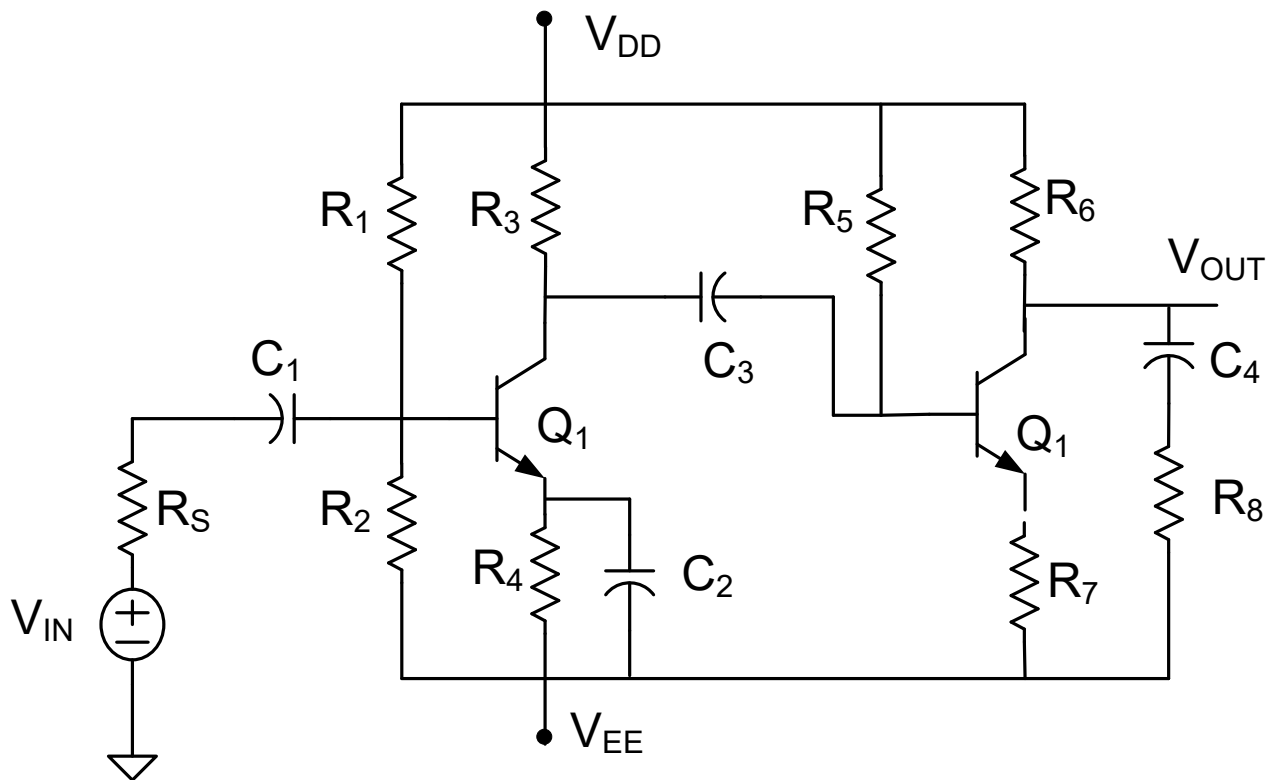
# Example 1:

Determine the voltage gain of the following circuit in terms of the small-signal parameters of the transistors. Assume  $Q_1$  and  $Q_2$  are operating in the Forward Active region and  $C_1 \dots C_4$  are large.



In this form, does not look “EXACTLY” like any of the basic amplifiers !


# Example 1:

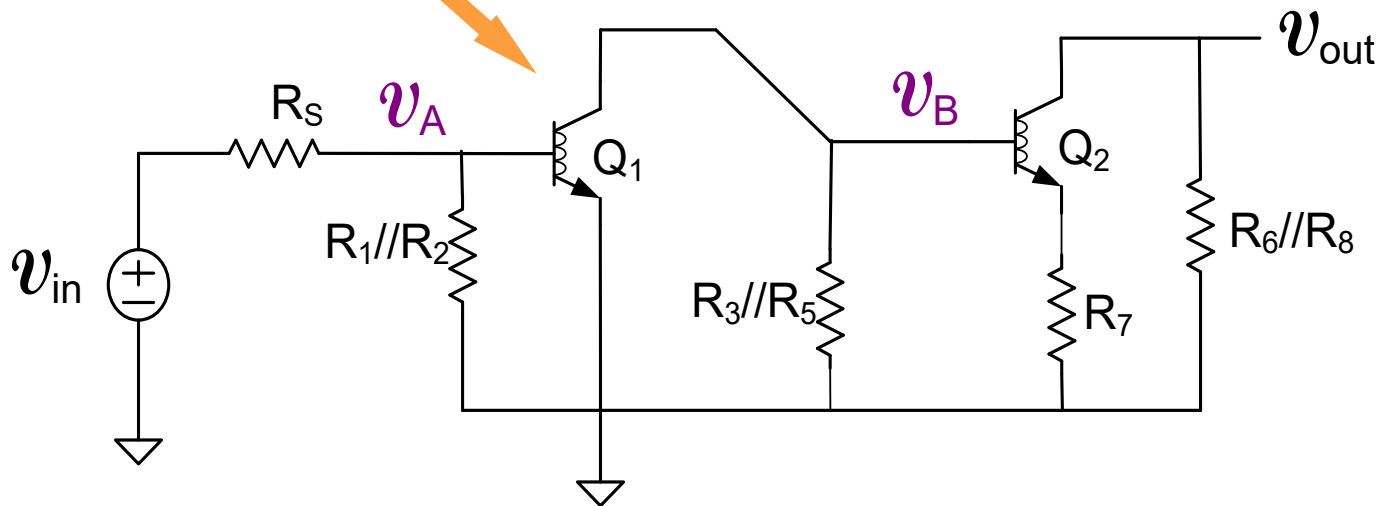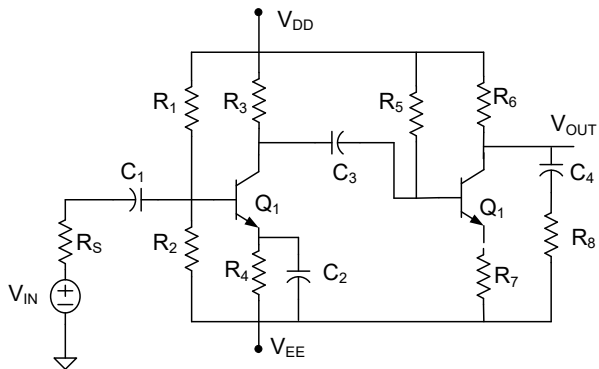

Will calculate  $A_V$  by determining the three ratios (not voltage gains of dependent source):


$$A_V = \frac{v_{out}}{v_{in}} = \frac{v_{out}}{v_B} \frac{v_B}{v_A} \frac{v_A}{v_{in}} = A_{V2} A_{V1} A_{V0}$$

# Example 1:

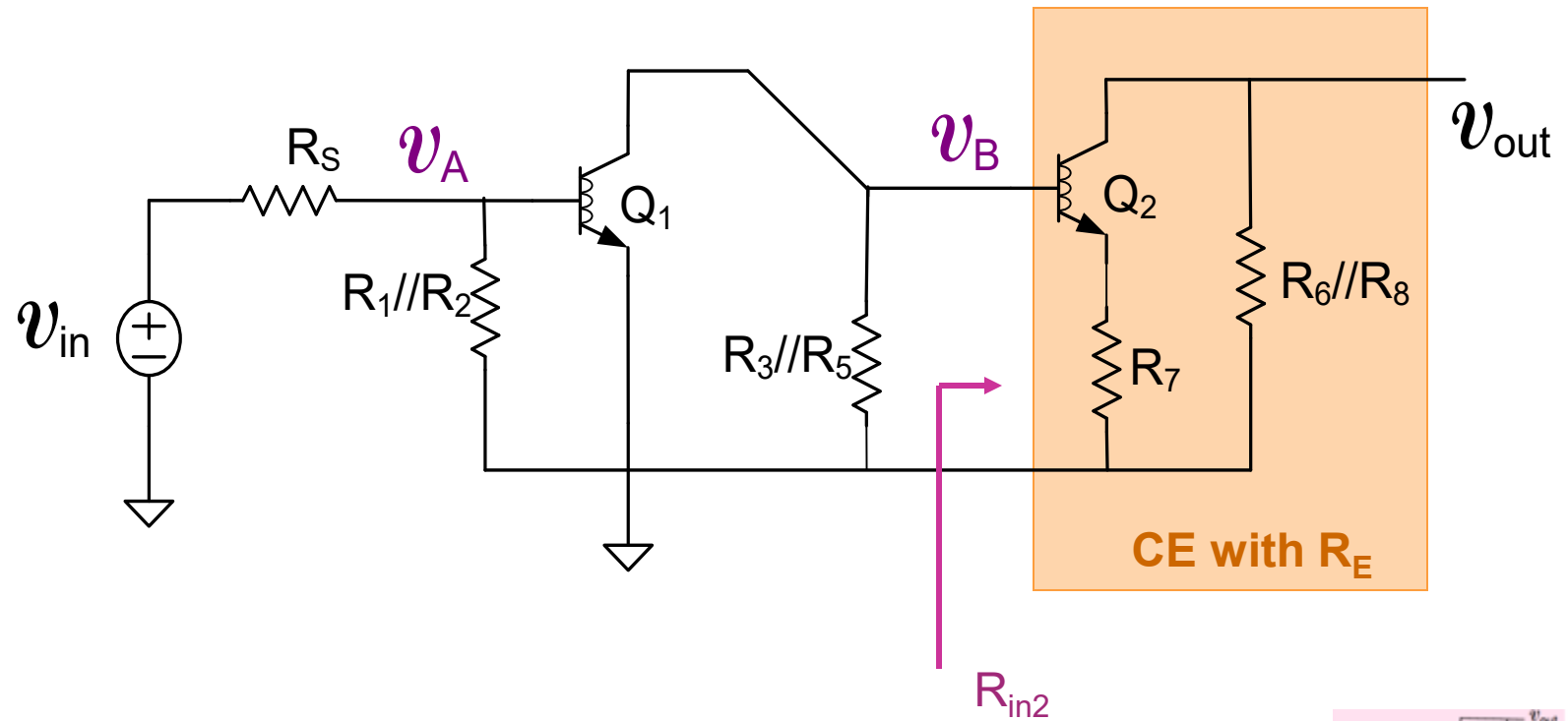


$$A_{V2} = \frac{v_{out}}{v_B} \cong -\frac{R_6 // R_8}{R_7}$$

$$R_{in2} \cong \beta R_7$$

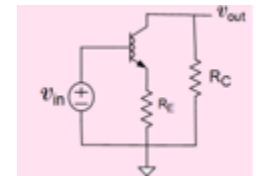


# Example 1:

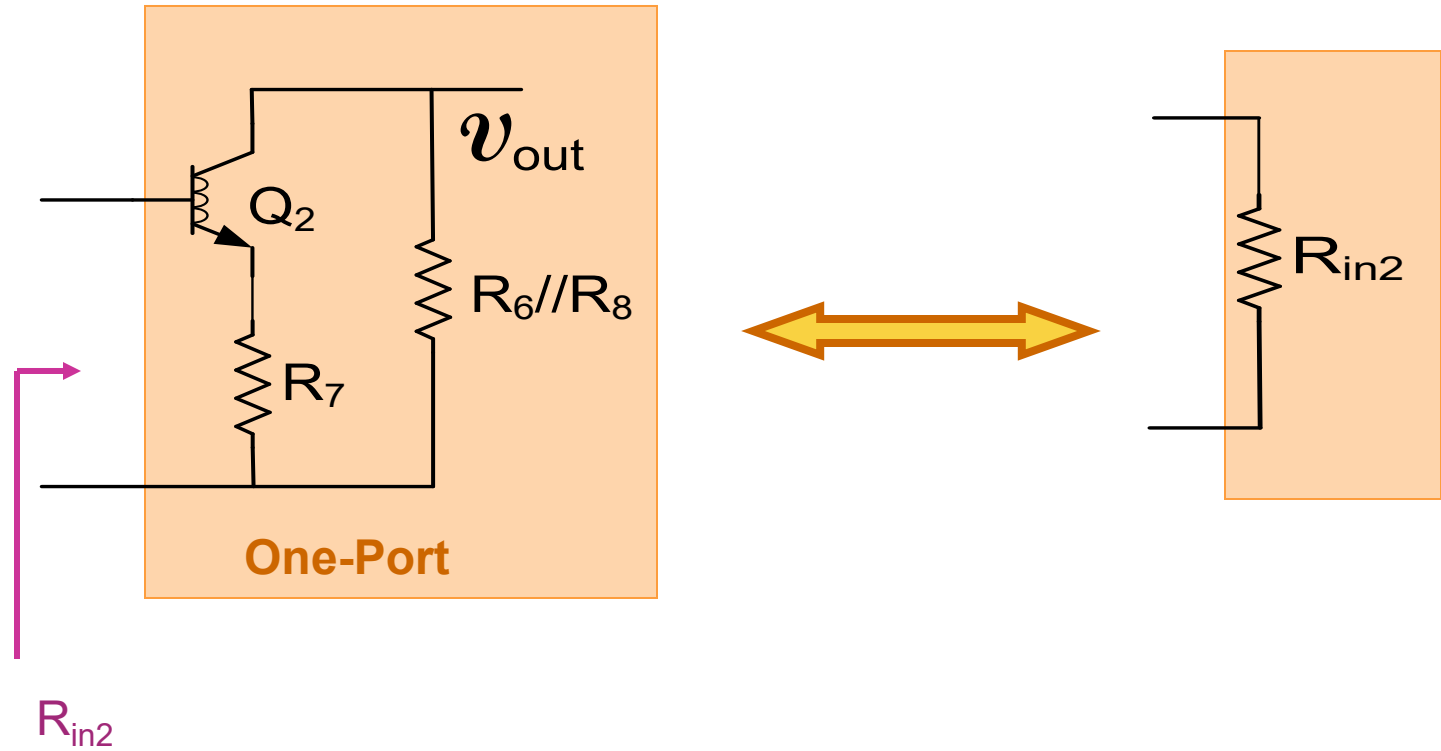

$$R_{in2} \cong \beta R_7$$



# Example 1:

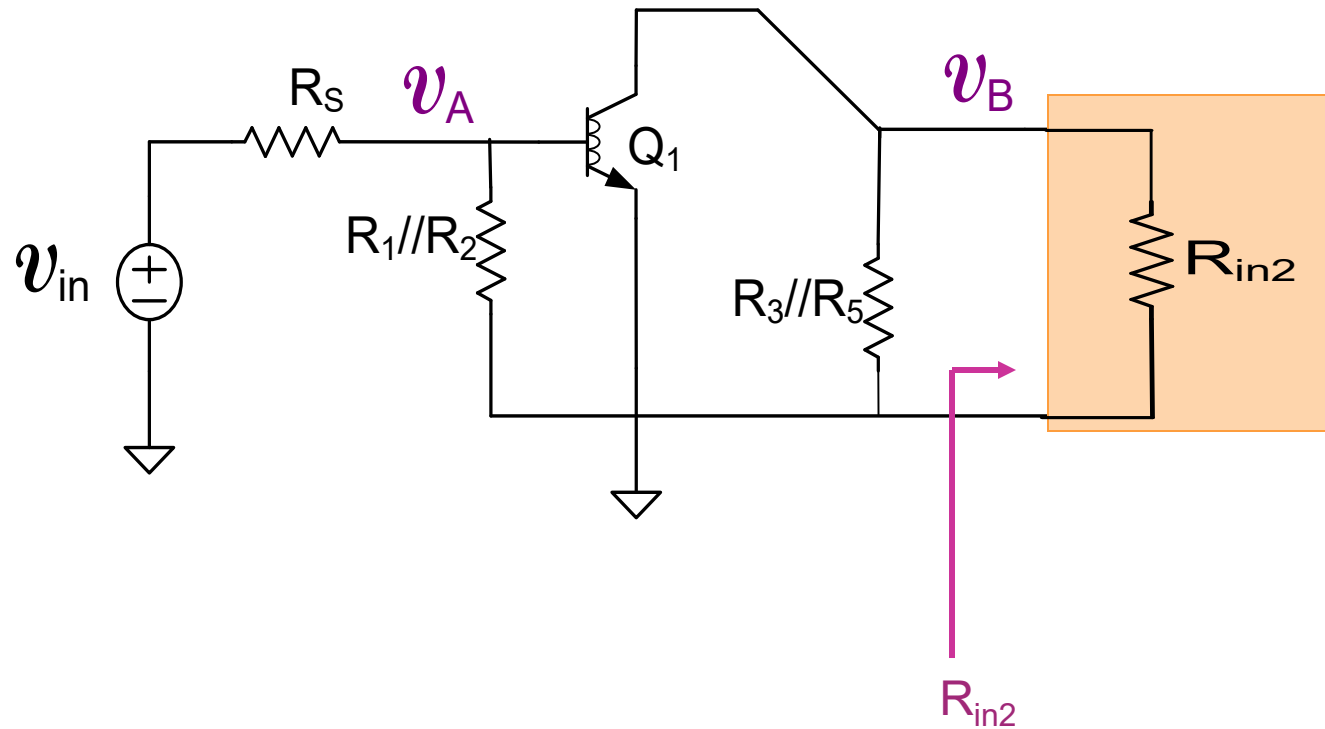

$$A_{V2} = \frac{v_{out}}{v_B} \cong -\frac{R_6 // R_8}{R_7}$$


$$R_{in2} \cong \beta R_7$$

# Example 1:

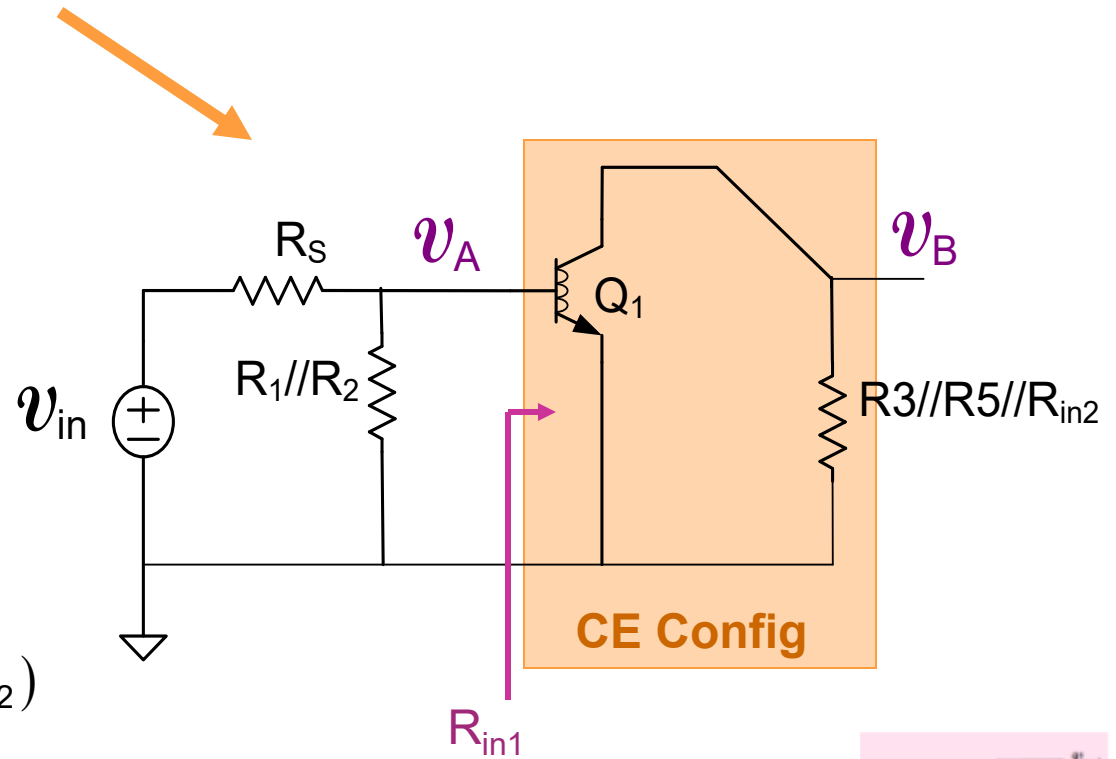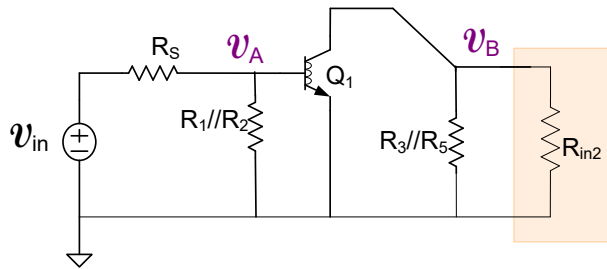


$$A_{V1} = \frac{v_B}{v_A} \cong -g_{m1} (R_3 // R_5 // R_{in2})$$

$$R_{in1} \cong r_{\pi 1}$$

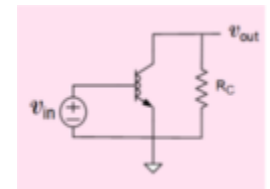




# Example 1:

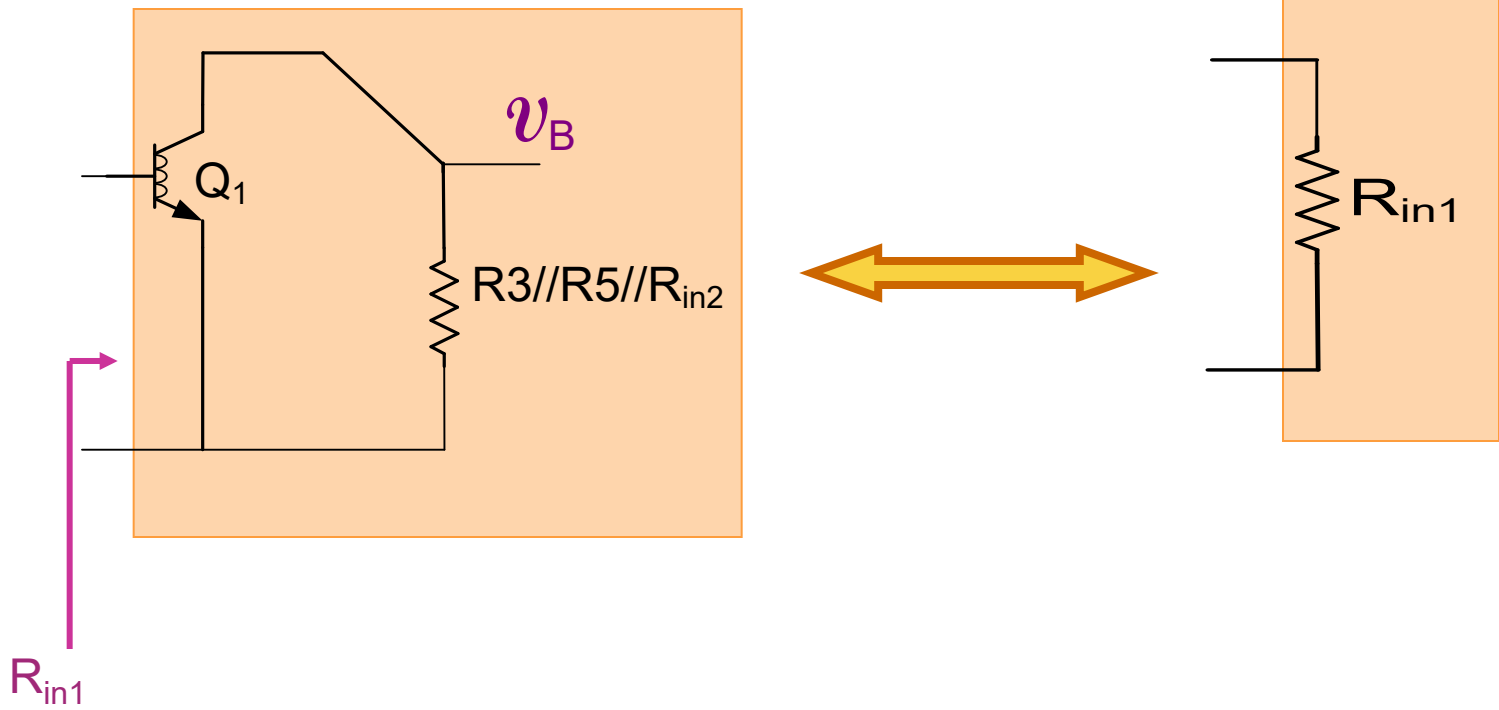


# Example 1:

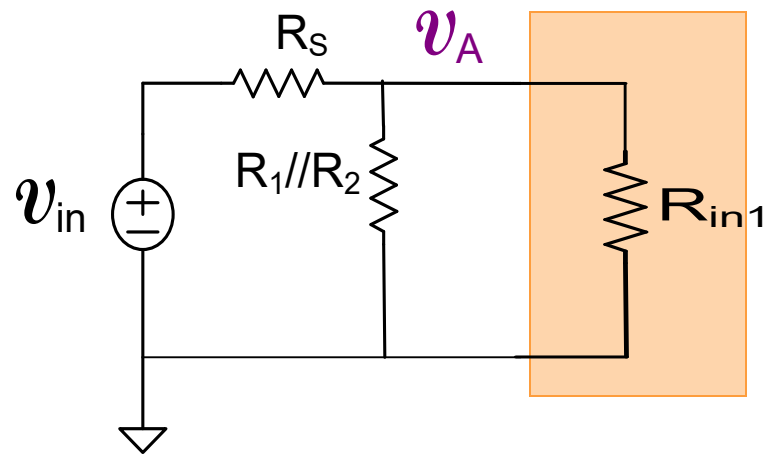

$$A_{v0} = \frac{v_A}{v_{in}} \cong \frac{R_1 // R_2 // R_{in1}}{R_s + R_1 // R_2 // R_{in1}}$$

# Example 1:

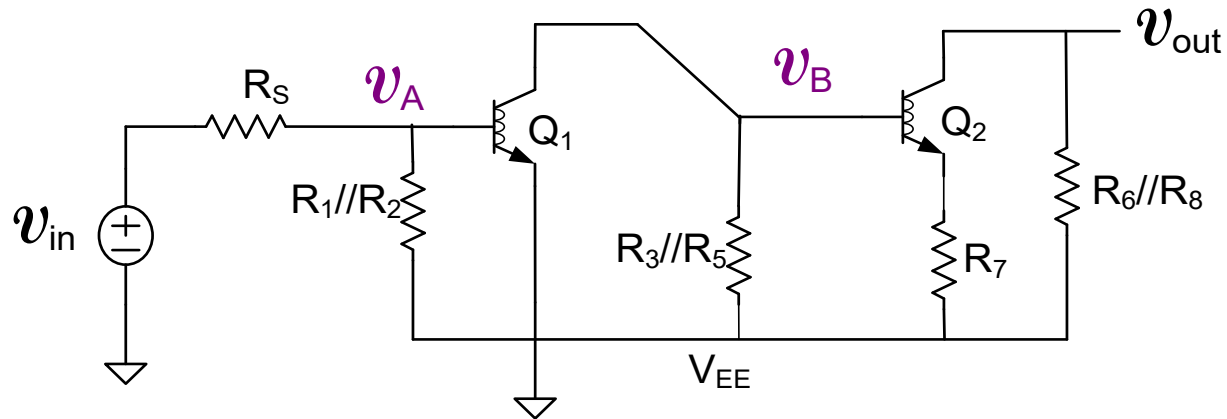

Thus we have

$$A_V = \frac{v_{out}}{v_{in}} = \frac{v_{out}}{v_B} \frac{v_B}{v_A} \frac{v_A}{v_{in}}$$

where

$$\frac{v_{out}}{v_B} \cong -\frac{R_6 // R_8}{R_7}$$


$$\frac{v_B}{v_A} \cong -g_{m1} (R_3 // R_5 // R_{in2})$$

$$R_{in2} \cong \beta R_7$$

$$\frac{v_A}{v_{in}} \cong \frac{R_1 // R_2 // R_{in1}}{R_s + R_1 // R_2 // R_{in1}}$$

$$R_{in1} \cong r_{\pi 1}$$
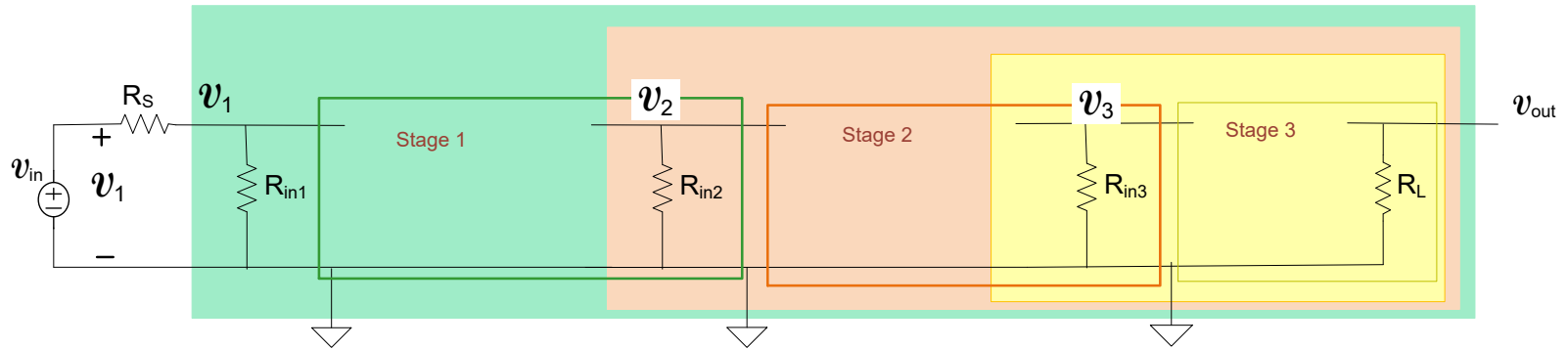
# Formalization of cascade circuit analysis working from load to input: (when stages are unilateral or not unilateral)




$R_{in_k}$  includes effects of all loading  
 Must recalculate if any change in loading  
 Analysis systematic and rather simple


$$\frac{v_{OUT}}{v_{IN}} = \frac{v_1}{v_{IN}} \frac{v_2}{v_1} \frac{v_3}{v_2} \frac{v_{OUT}}{v_3}$$

This was the approach used in analyzing the previous cascaded amplifier

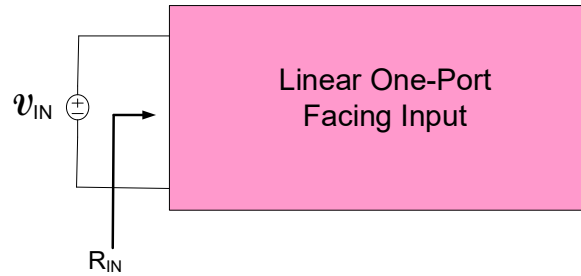
# Review: Small-signal equivalent of a one-port




“Diode-connected transistor”

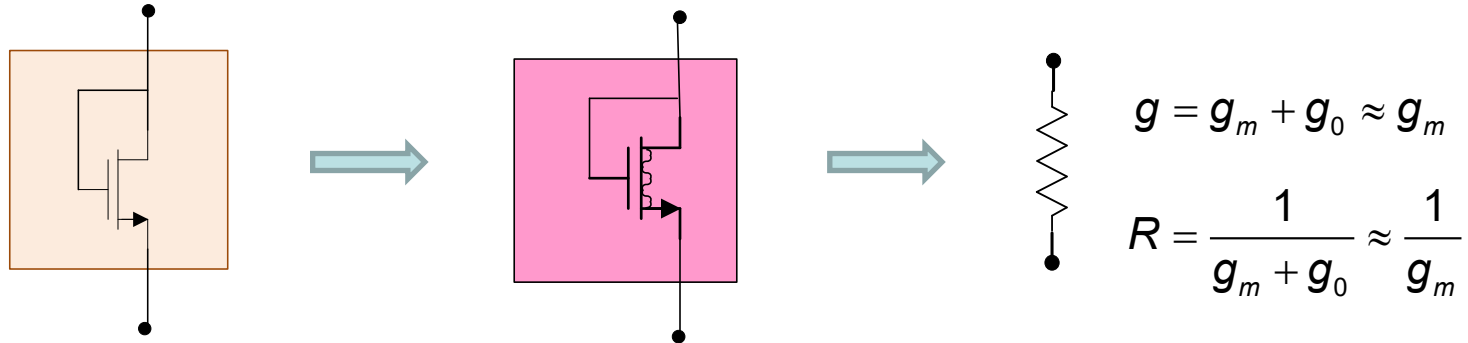


“GS - connected transistor”

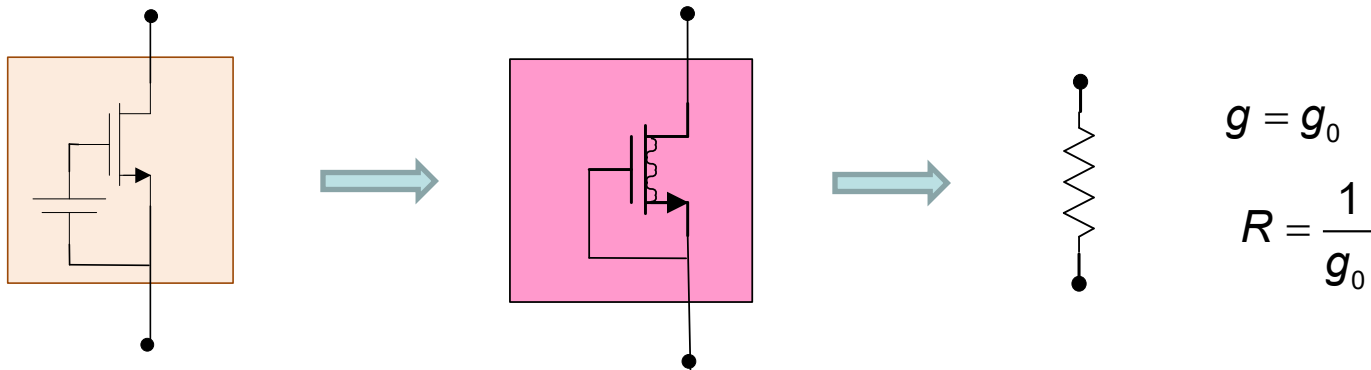

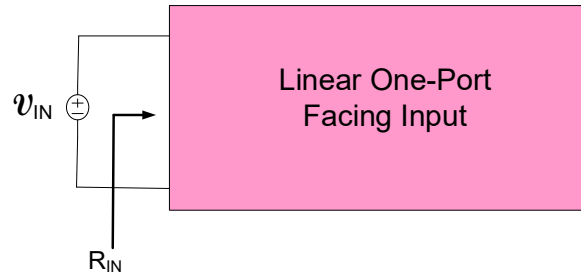
# Review: Small-signal equivalent of a one-port



“Diode-connected transistor”

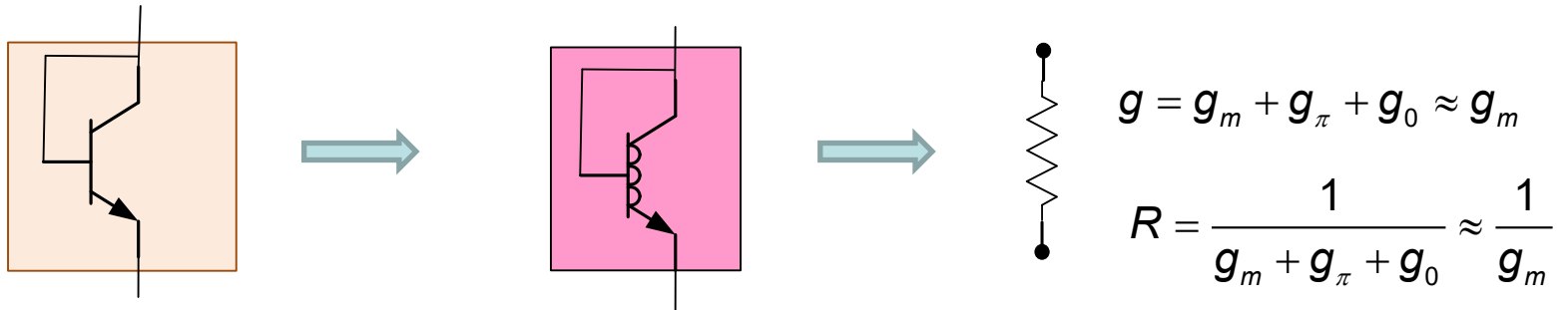


“BE - connected transistor”

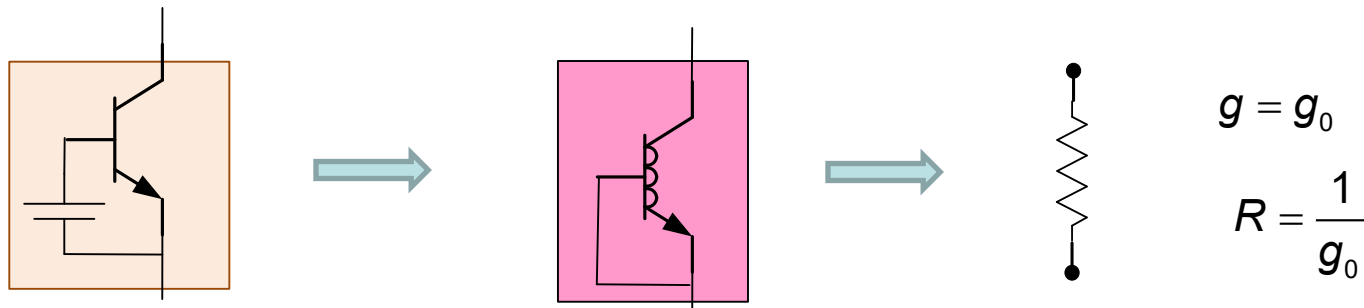


Example 2:  $A_V = \frac{v_{out}}{v_{in}} = ?$

Express in terms of small-signal parameters

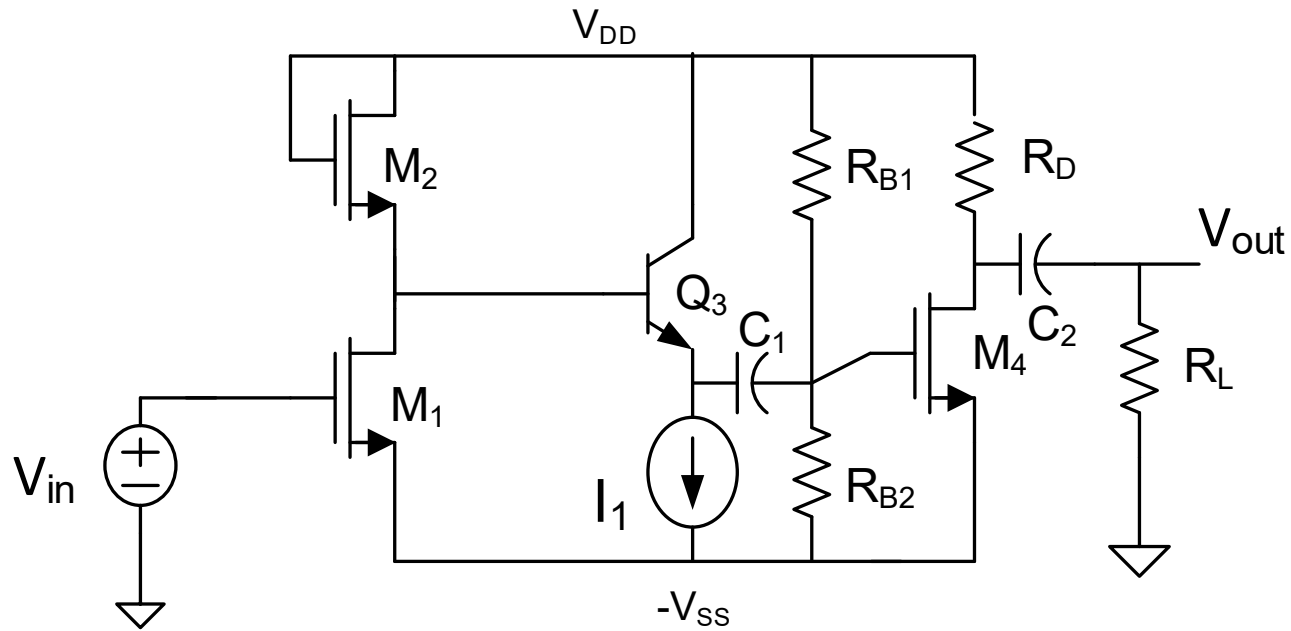


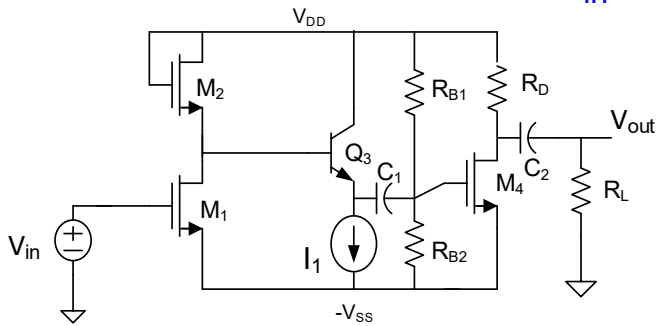Example 2:  $A_V = \frac{v_{out}}{v_{in}} = ?$

Express in terms of small-signal parameters



visualize

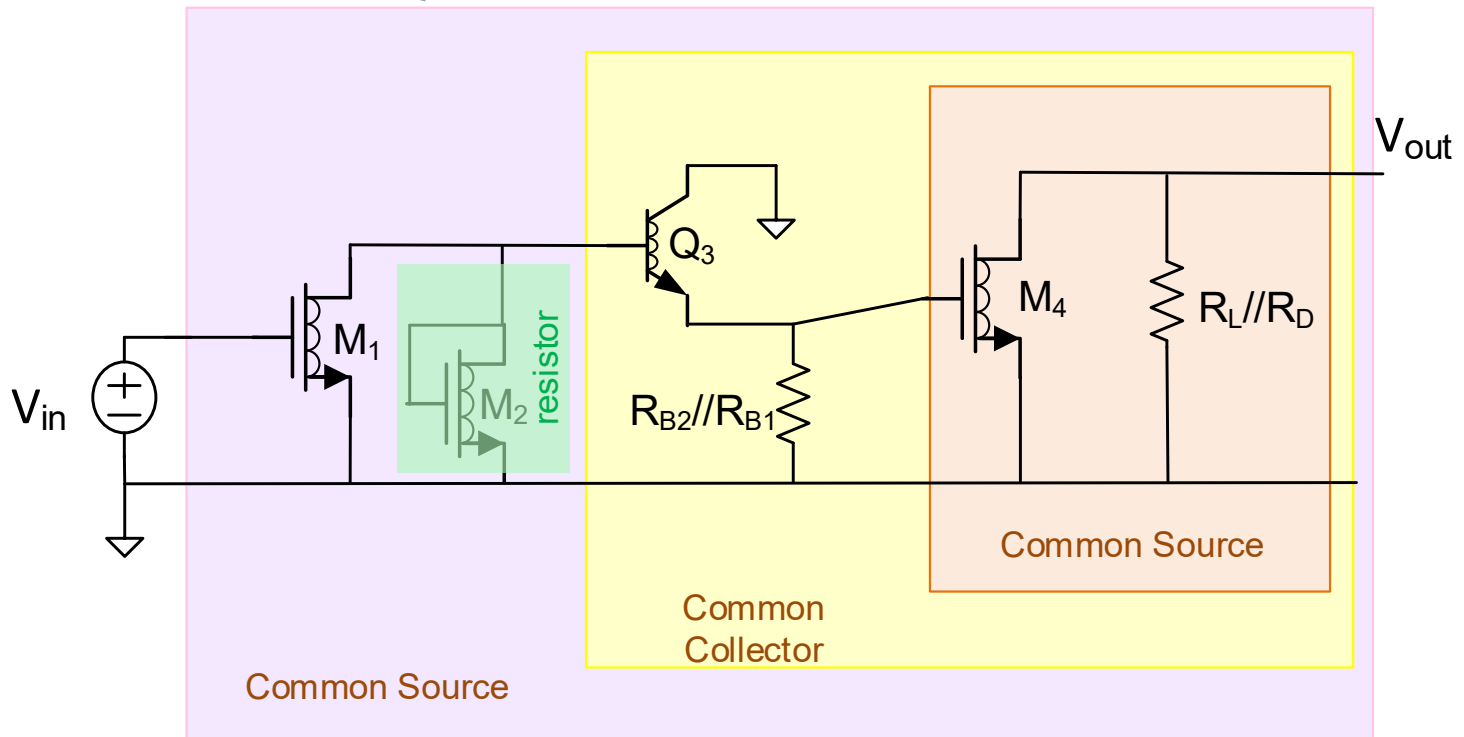



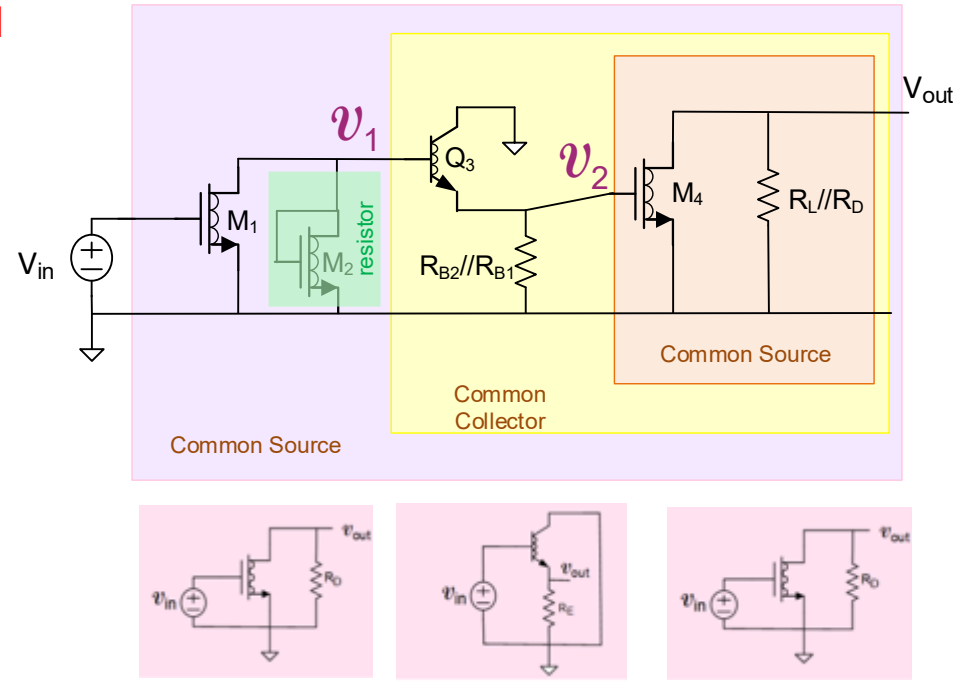
# Example 2: $A_V = \frac{v_{out}}{v_{in}} = ?$

Express in terms of small-signal parameters

Gain Calculation in terms of Small-Signal Parameters



$$\frac{v_{OUT}}{v_2} =$$

$$\frac{v_2}{v_1} =$$

$$\frac{v_1}{v_{in}} =$$


If  $r_{\pi} + \beta(R_{B1} // R_{B2}) \gg 1/g_{m2}$

$$A_V = \frac{v_{out}}{v_2} \frac{v_2}{v_1} \frac{v_1}{v_{in}} \cong \left[ -g_{m4} (R_D // R_L) \right] [1] \left[ \frac{-g_{m1}}{g_{m2}} \right]$$

# Summary of Missing Material from Lecture 32

End Here:

# High-gain BJT amplifier

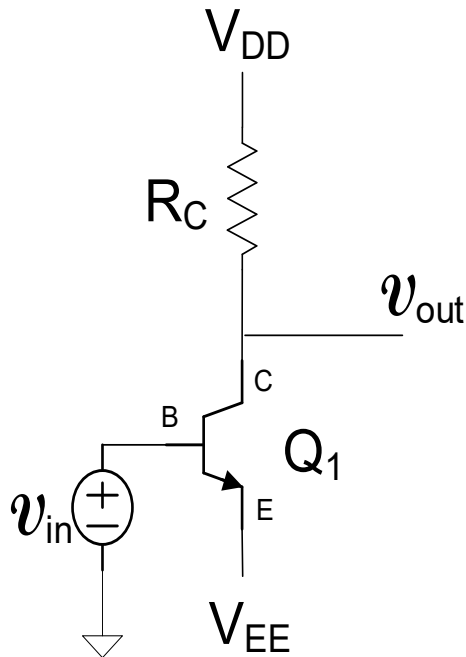

$$A_V = \frac{-g_m}{g_0 + G_C} \cong -g_m R_C$$

To make the gain large, it appears that all one needs to do is make  $R_C$  large !

$$A_V \cong -g_m R_C = \frac{-I_{CQ} R_C}{V_t}$$

But  $V_t$  is fixed at approx 25mV and to keep  $Q_1$  in forward active with large signal swing,  $I_{CQ} R_C < (V_{DD} - V_{EE})/2$

$$|A_V| < \frac{V_{DD} - V_{EE}}{2V_t}$$

If  $V_{DD} - V_{EE} = 5V$ ,

$$|A_V| < \frac{5V}{2 \cdot 25mV} = 100$$

- Gain is practically limited with this supply voltage to around 100
- And in extreme case, limited to about 200 with this supply voltage with very small signal swing

# High-gain MOS amplifier

$$A_V = \frac{-g_m}{g_0 + G_D} \cong -g_m R_D$$

To make the gain large, it appears that all one needs to do is make  $R_D$  large !

$$A_V \cong -g_m R_D = \frac{-2I_{DQ}R_D}{V_{EB}}$$

But  $V_{EB}$  is practically limited to around 100mV and for good signal swing,  $I_{DQ}R_D < (V_{DD} - V_{SS})/2$


$$|A_V| < \frac{V_{DD} - V_{SS}}{V_{EB}}$$

If  $V_{DD} - V_{SS} = 5V$  and  $V_{EB} = 100mV$ ,




$$|A_V| < \frac{5V}{100mV} = 50$$

**Gain is practically limited with this supply voltage to around 50**

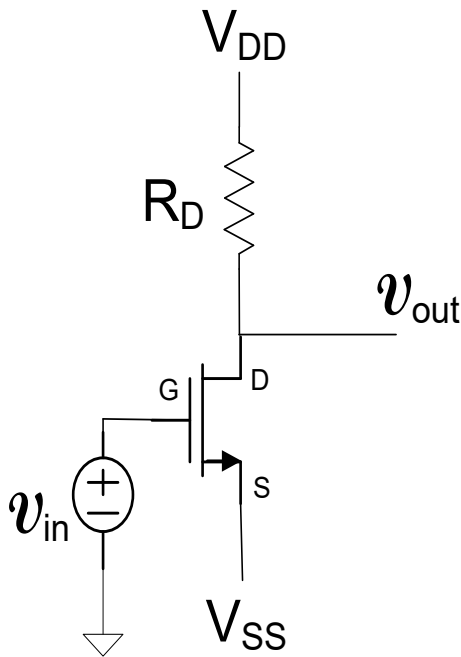**Are these fundamental limits on the gain of the BJT and MOS Amplifiers?**



# High-gain amplifier

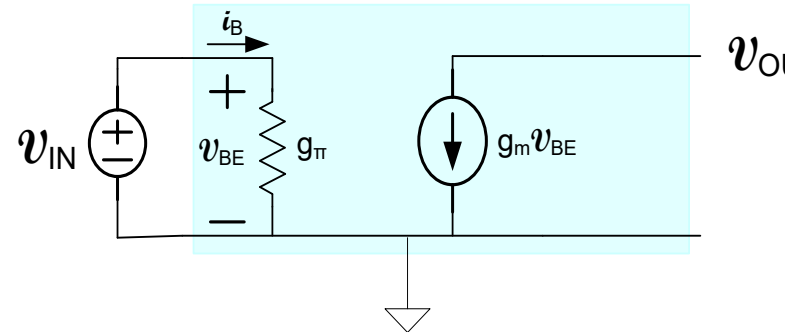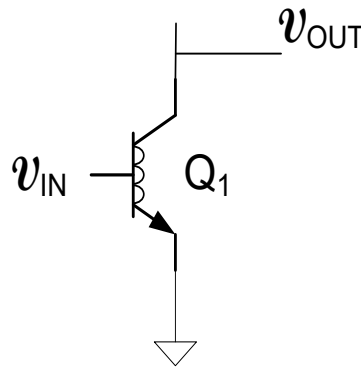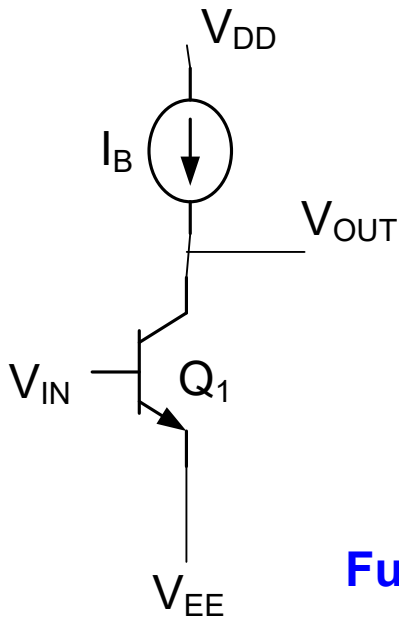

$$A_V = \frac{-g_m}{0} = -\infty$$

**Fundamentally a different circuit**

**Current source is biasing  $Q_1$**

**This gain is very large !**

**Too good to be true !**

**Need better model of BJT and MOS device (but we already have it) !**

# But are current sources really available?




Current Source ???



Keysight  
Technologies...

**\$2,882.00**

Voltage Source

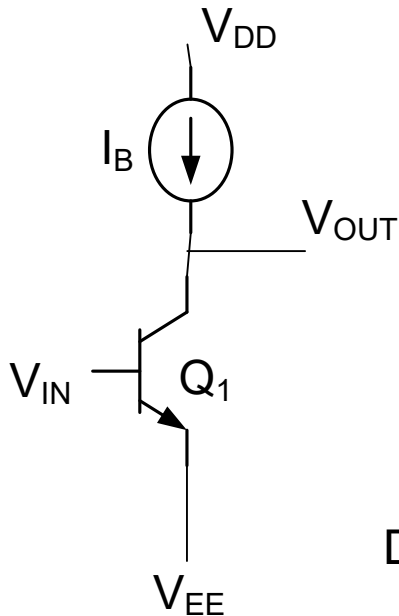




Did you discuss current sources in EE 201?

Did you have any current sources in the EE 201 laboratory?

Did you have any current sources in the EE 230 laboratory?

Do current sources really exist?

# High-gain amplifier

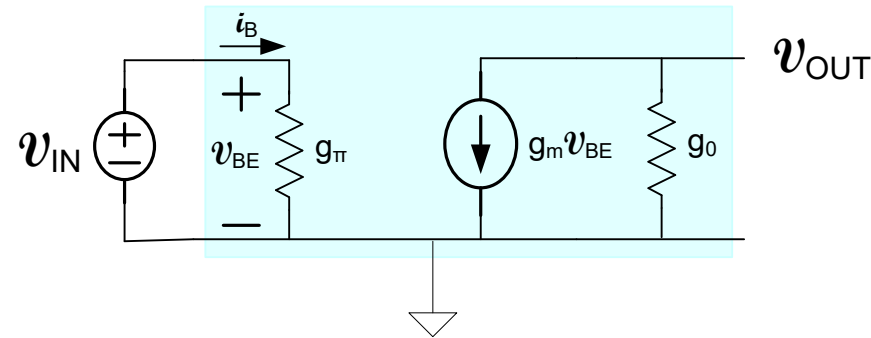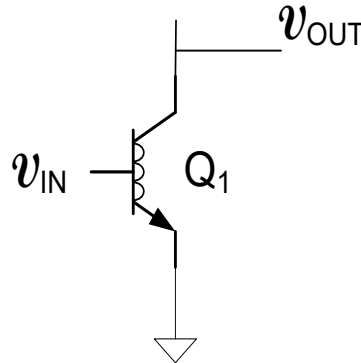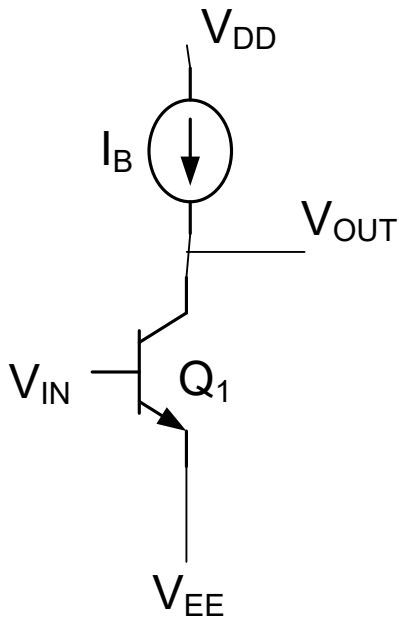

$$A_V = \frac{-g_m}{g_o}$$

$$A_V = \frac{-I_{CQ}}{V_t I_{CQ} / V_{AF}} = -\frac{V_{AF}}{V_t}$$


$$A_V = -\frac{V_{AF}}{V_t} \cong \frac{200V}{25mV} = -8000$$

**This gain is very large (but realistic) !**


**And no design parameters affect the gain**

**But how can we make a current source?**

# High-gain amplifier

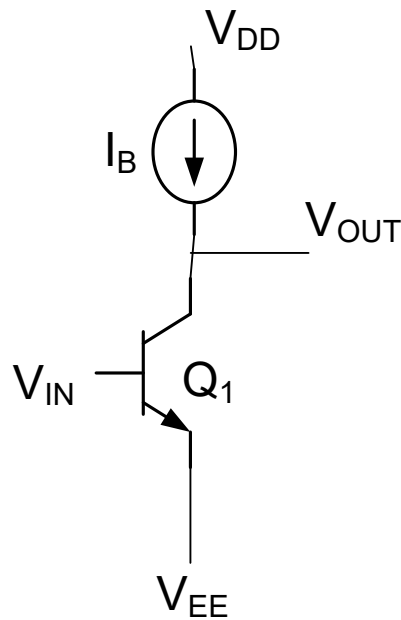

$$A_V \cong -8000$$

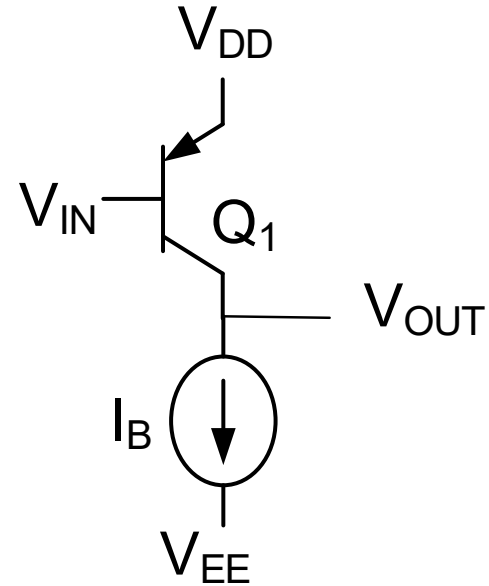


Same gain with both npn and pnp transistors

How can we build the ideal current source?


What is the small-signal model of an actual current source?



# High-gain amplifier

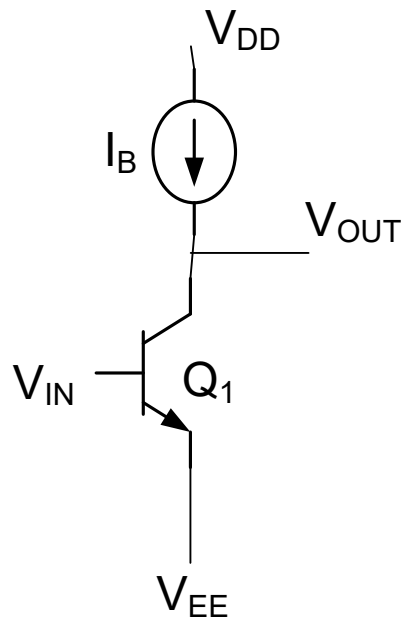

$$A_V \cong -8000$$



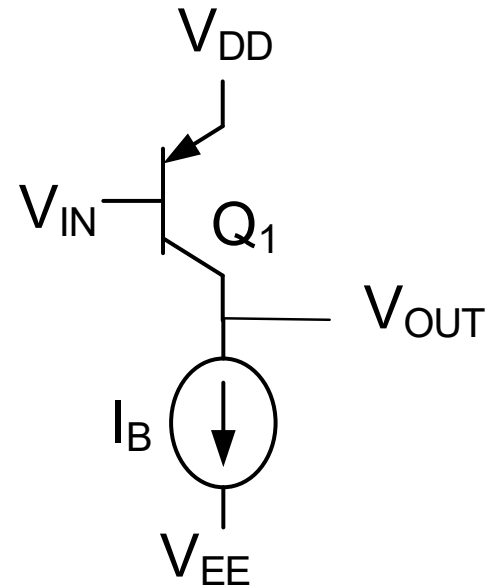


Same gain with both npn and pnp transistors

Will now focus on creating current sources and then return to using these current sources to build high gain amplifiers.

# Simple Current Sources

a “sinking” current source

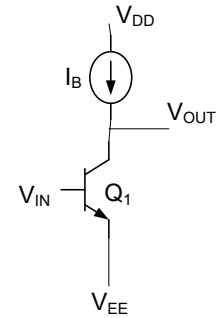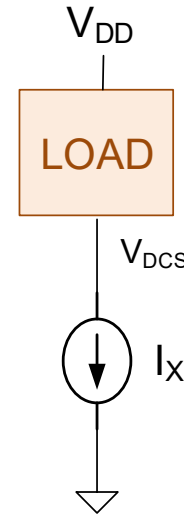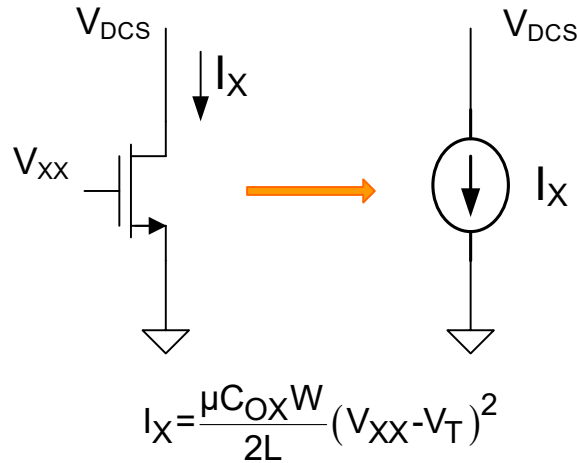

Since  $I_X$  is independent of  $V_{DCS}$ , acts as an ideal current source (with this model)

Termed a “sinking” current source since current is pulled out of the load

If  $V_{XX}$  is available, each dc current source requires only one additional transistor !

Have several methods for generating  $V_{XX}$  from  $V_{DD}$  (see HW problems)



But how good is this current “sink”?

And may not have both MOS and Bipolar devices in most processes!

But for the npn high-gain amplifier considered need a sourcing current

# Simple Current Sources

a “sourcing” current source

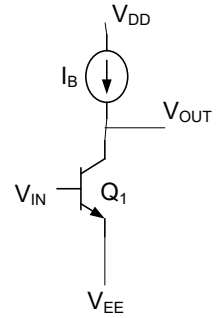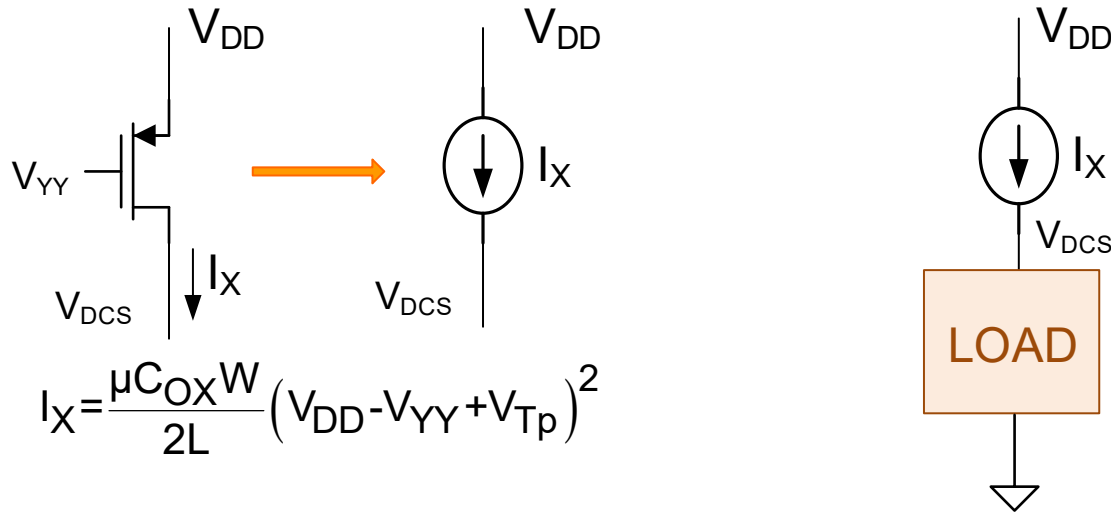

Since  $I_X$  is independent of  $V_{DCS}$ , acts as an ideal current source (with this model)

Termed a “sourcing” current source since pushed into the load

If  $V_{YY}$  is available, each dc current source requires only one additional transistor !



Have several methods for generating  $V_{YY}$  from  $V_{DD}$  (see HW problems)

But how good is this current “source”?

And may not have both MOS and Bipolar devices in most processes!

# Simple Current Sources

a “sinking” current source

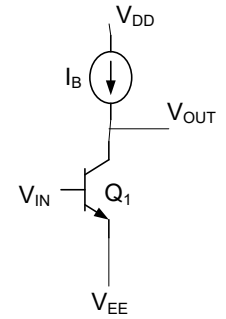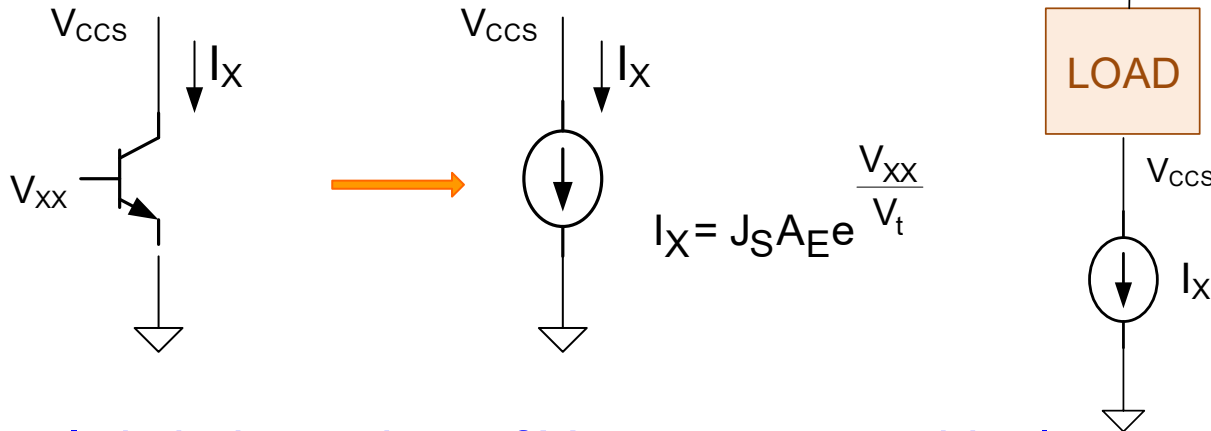

Since  $I_X$  is independent of  $V_{CCS}$ , acts as an ideal current source (with this model)

Termed a “sinking” current source since current is pulled out of the load

If  $V_{XX}$  is available, each dc current source requires only one additional transistor !





Have several methods for generating  $V_{XX}$  from  $V_{DD}$  (see HW problems)

But for the npn high-gain amplifier considered need a sourcing current

But how good is this current “sink”?

# Simple Current Sources

a “sourcing” current source

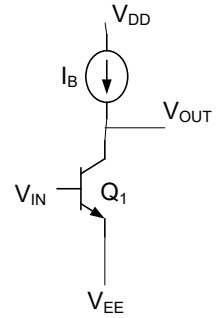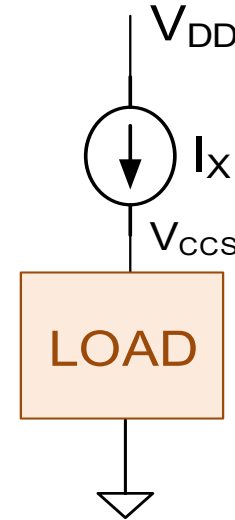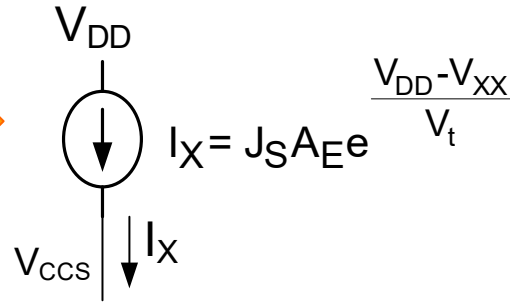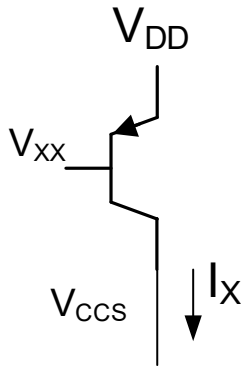

Since  $I_X$  is independent of  $V_{CCS}$ , acts as an ideal current source (with this model)

Termed a “sourcing” current source since pushed into the load

If  $V_{XX}$  is available, each dc current source requires only one additional transistor !


Current highly sensitive to  $V_{XX}$  if generated with dc voltage source

Have several methods for generating  $V_{XX}$  from  $V_{DD}$  (see HW problems)


But how good is this current “source”?

Before addressing the issue of how a current source is designed, will consider another circuit that uses current source biasing

## The Basic Differential Amplifier


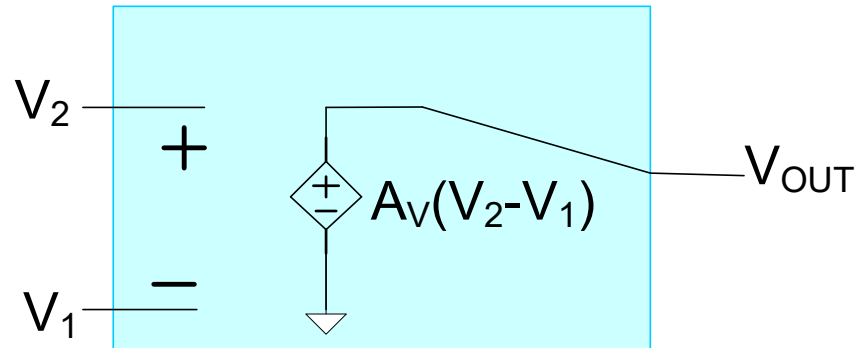


If  $A_V$  is large

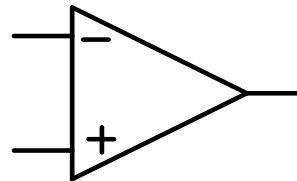

Operational Amplifier (Op Amp)

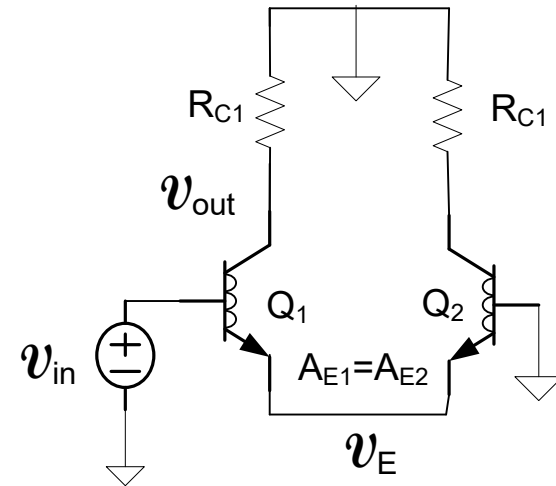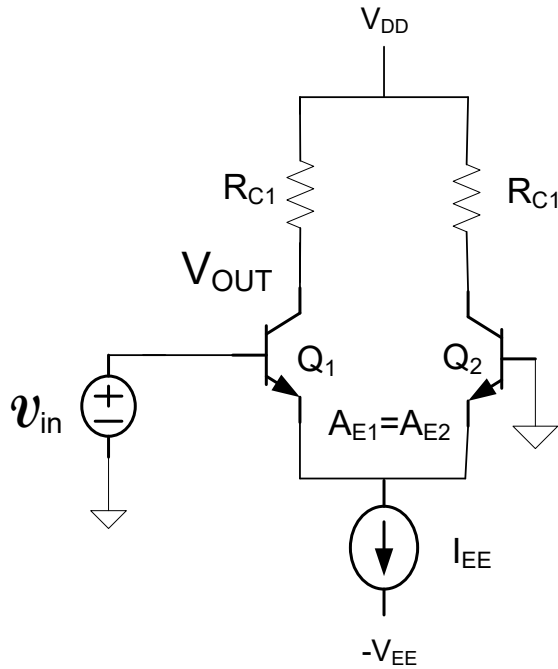
Example: Determine the voltage gain of the following circuit




Since symmetric when  $v_{IN}=0$

$$I_{C1Q} = I_{C2Q} = \frac{I_{EE}}{2}$$
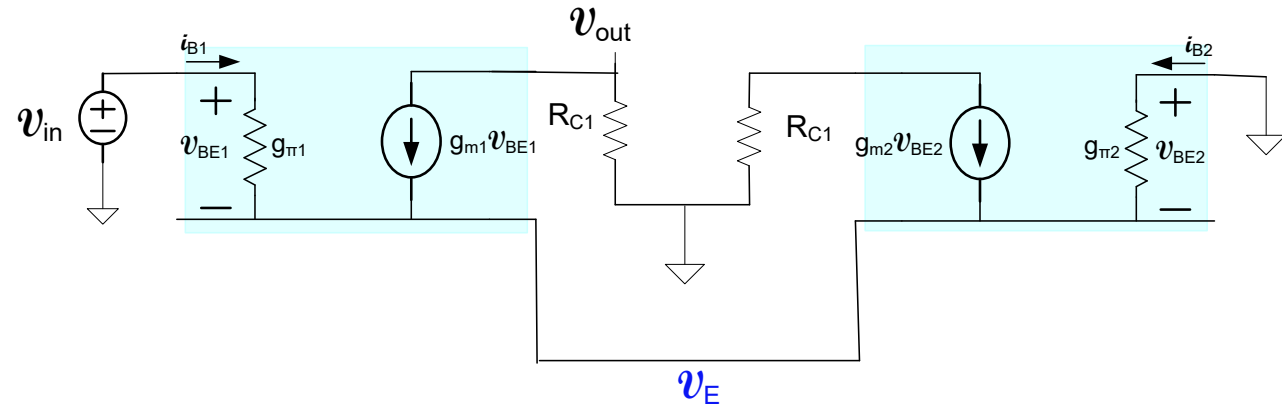
$$g_{m1} = g_{m2} = \frac{I_{EE}}{2V_t}$$



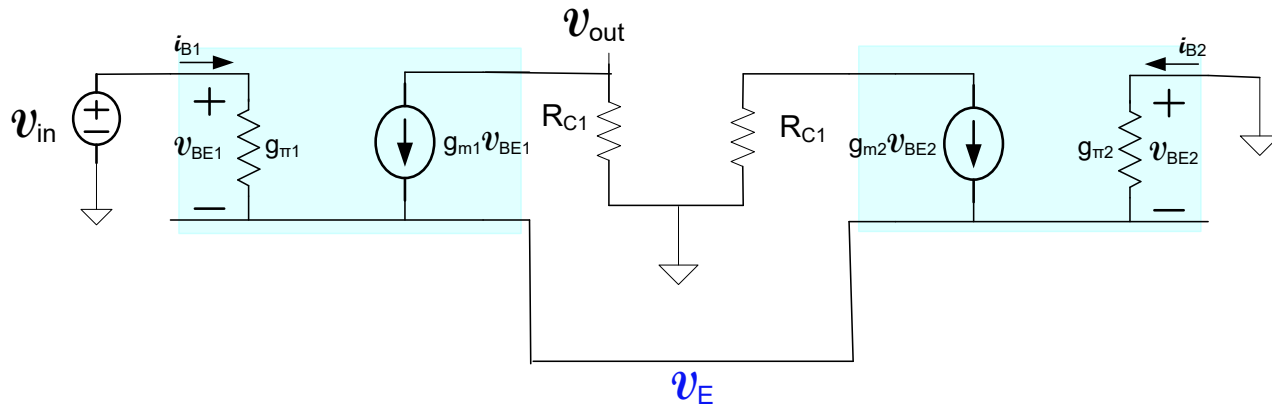Example: Determine the voltage gain of the following circuit



$$v_E (g_{\pi 1} + g_{\pi 1}) = g_{\pi 1} v_{IN} + g_{m1} (v_{IN} - v_E) + g_{m2} (-v_E)$$

$$v_{OUT} = -R_{C1} g_{m1} (v_{IN} - v_E)$$

$$v_E (g_{\pi 1} + g_{\pi 2} + g_{m1} + g_{m2}) = v_{IN} (g_{m1} + g_{\pi 1})$$


$$v_E = \frac{(g_{m1} + g_{\pi 1})}{(g_{\pi 1} + g_{\pi 2} + g_{m1} + g_{m2})} v_{IN}$$

$$v_{OUT} = -R_{C1} g_{m1} v_{IN} \left[ 1 - \frac{(g_{m1} + g_{\pi 1})}{(g_{\pi 1} + g_{\pi 2} + g_{m1} + g_{m2})} \right]$$

$$v_{OUT} = -R_{C1} g_{m1} v_{IN} \left[ \frac{g_{\pi 1} + g_{\pi 2} + g_{m1} + g_{m2} - (g_{m1} + g_{\pi 1})}{(g_{\pi 1} + g_{\pi 2} + g_{m1} + g_{m2})} \right]$$



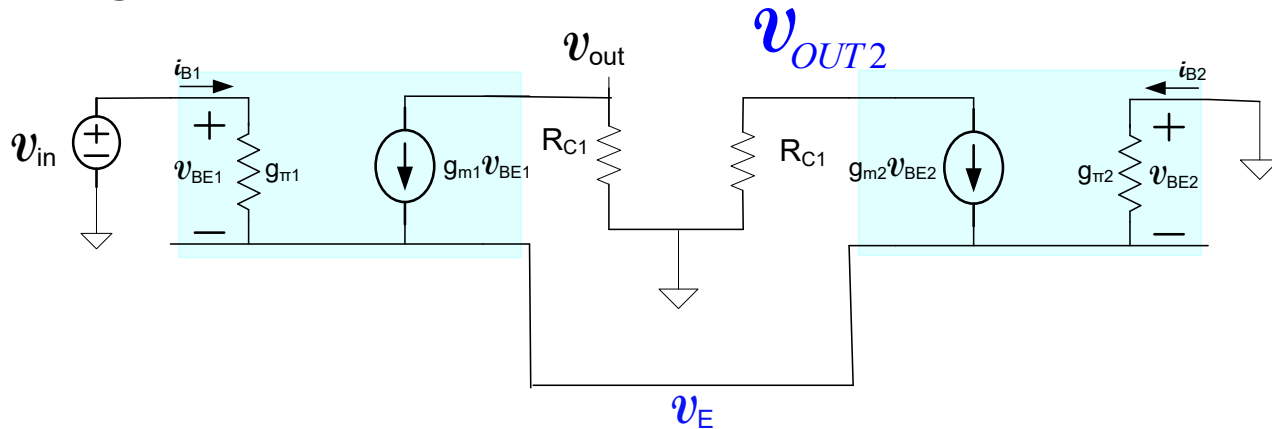Example: Determine the voltage gain of the following circuit




$$v_{OUT} = -R_{C1}g_{m1}v_{IN} \left[ \frac{g_{\pi 1} + g_{\pi 2} + g_{m1} + g_{m2} - (g_{m1} + g_{\pi 1})}{(g_{\pi 1} + g_{\pi 2} + g_{m1} + g_{m2})} \right]$$

$$v_{OUT} \cong -R_{C1}g_{m1}v_{IN} \left[ \frac{g_{m2}}{(g_{m1} + g_{m2})} \right]$$

$$v_{OUT} \cong \left[ \frac{-R_{C1}g_{m1}}{2} \right] v_{IN}$$

$$v_{OUT2} \cong \left[ \frac{R_{C1}g_{m1}}{2} \right] v_{IN}$$

# Differential amplifier


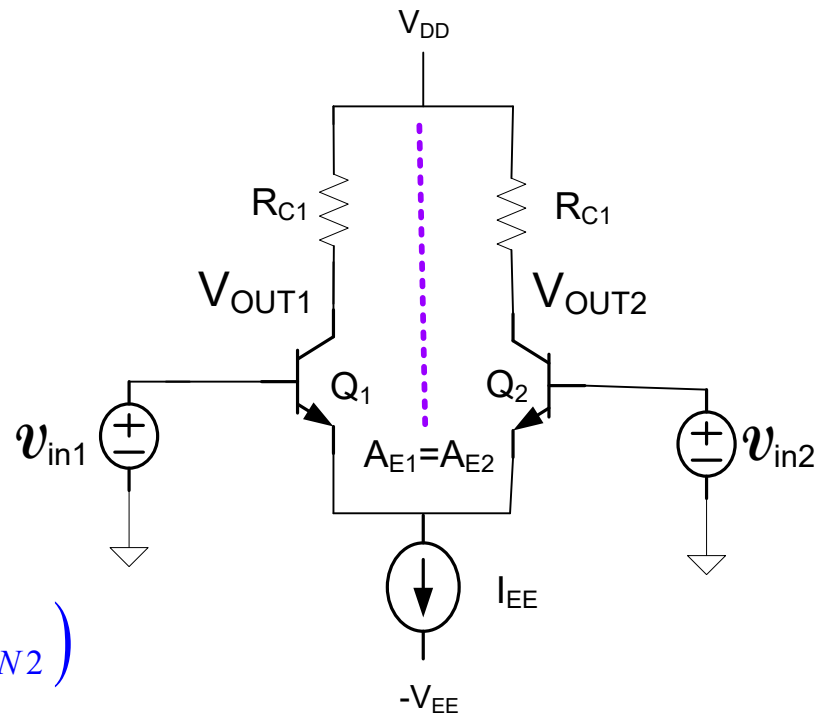


$$v_{OUT1} \cong -\left[\frac{R_{C1}g_{m1}}{2}\right](v_{IN1} - v_{IN2})$$

$$v_{OUT2} \cong \left[\frac{R_{C1}g_{m1}}{2}\right](v_{IN1} - v_{IN2})$$

- Very useful circuit
- This is a basic Op Amp
- Uses a current source and  $V_{DD}$  for biasing (no biasing resistors or caps!)
- But – needs a dc current source !!!!


# Simple Current Sources

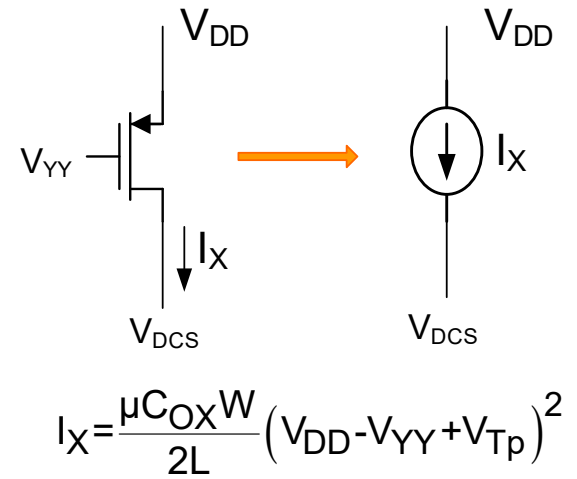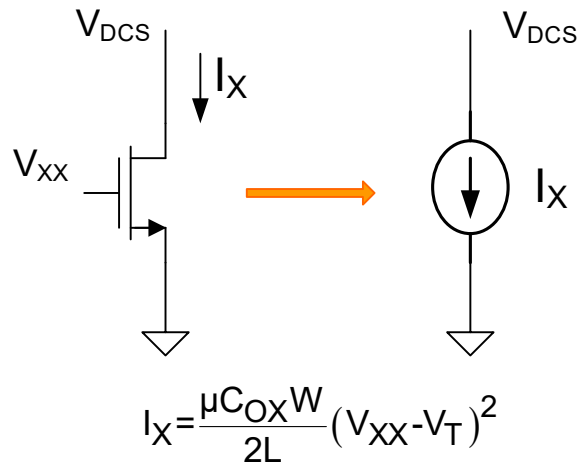

But how good are these current sources?


# Model of dc Current Source

“Reasonable dc Current Source”

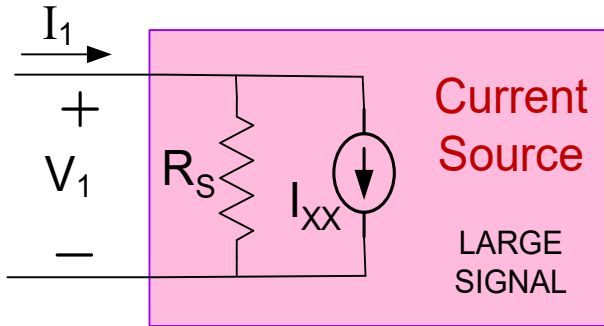


$I_{XX}$  independent of  $V_1$  and  $t$ ,  $R_S$  large

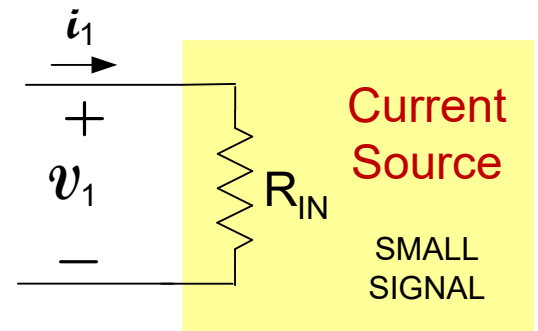Small-signal model of dc current source (since one-port)




want  $R_{IN}$  large

## Ideal dc Current Source

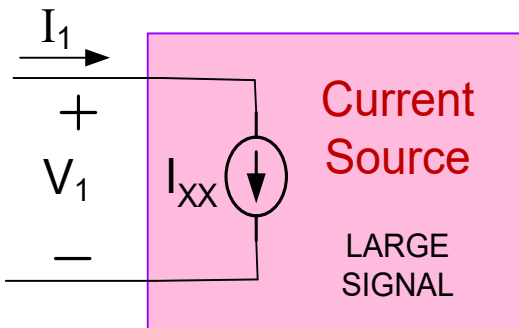

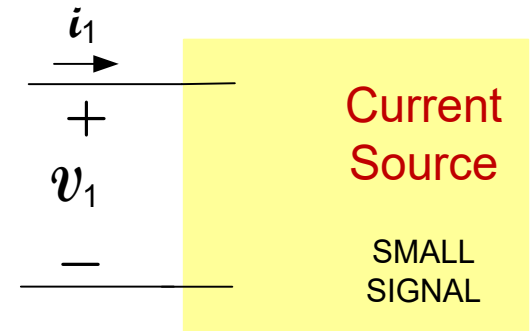
$I_{XX}$  independent of  $V_1$  and  $t$



$R_{IN} = \infty$
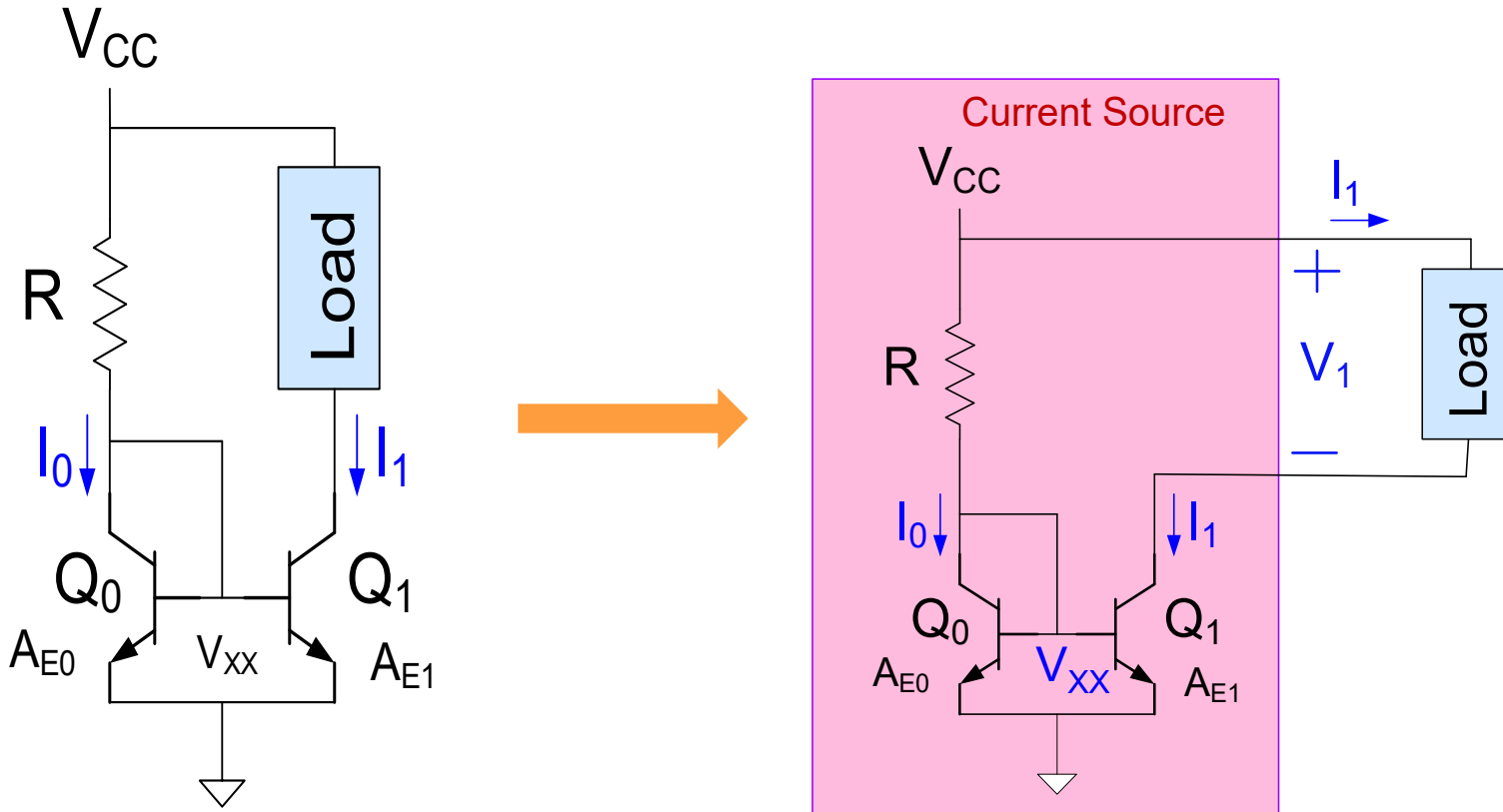
# Current Sources/Mirrors


Will show circuit in red behaves as a current source



$R$  and  $Q_0$  simply generate voltage  $V_{XX}$  in previous circuit

But sensitivity of  $I_1$  is much smaller than using voltage source for generating  $V_{XX}$


# Current Sources/Mirrors

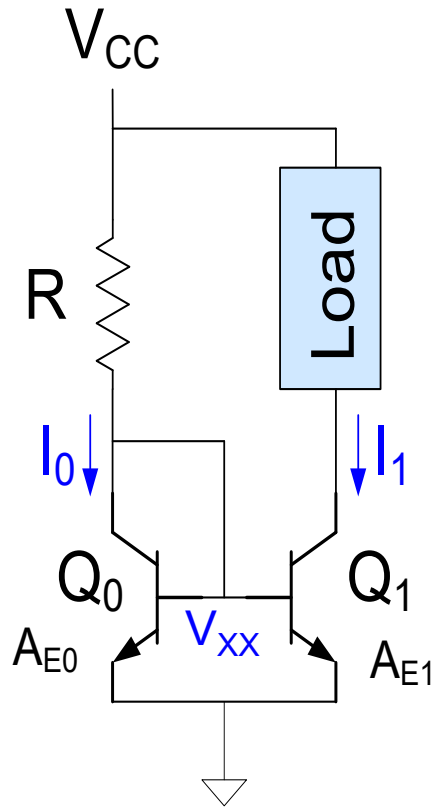

$$I_0 \cong \frac{(V_{CC} - 0.6V)}{R}$$

If the base currents are neglected

# Current Sources/Mirrors

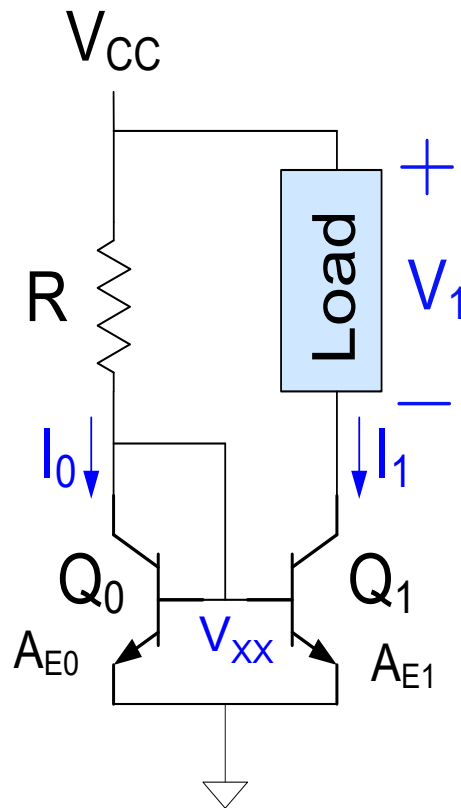

$$I_0 \cong \frac{(V_{CC} - 0.6V)}{R}$$

If the base currents are neglected

$$\left. \begin{aligned} I_0 &= J_S A_{E0} e^{\frac{V_{BE0}}{V_t}} \\ I_1 &= J_S A_{E1} e^{\frac{V_{BE1}}{V_t}} \end{aligned} \right\}$$

since  $V_{BE1} = V_{BE2}$


$$I_1 \cong \left( \frac{A_{E1}}{A_{E0}} \right) I_0 = \left( \frac{A_{E1}}{A_{E0}} \right) \frac{V_{CC} - 0.6V}{R}$$

Note  $I_1$  is not a function of  $V_1$

**Behaves as a current sink ! So is ideal with this model !!**

**And does not require an additional dc voltage source !!!**


# Current Sources/Mirrors

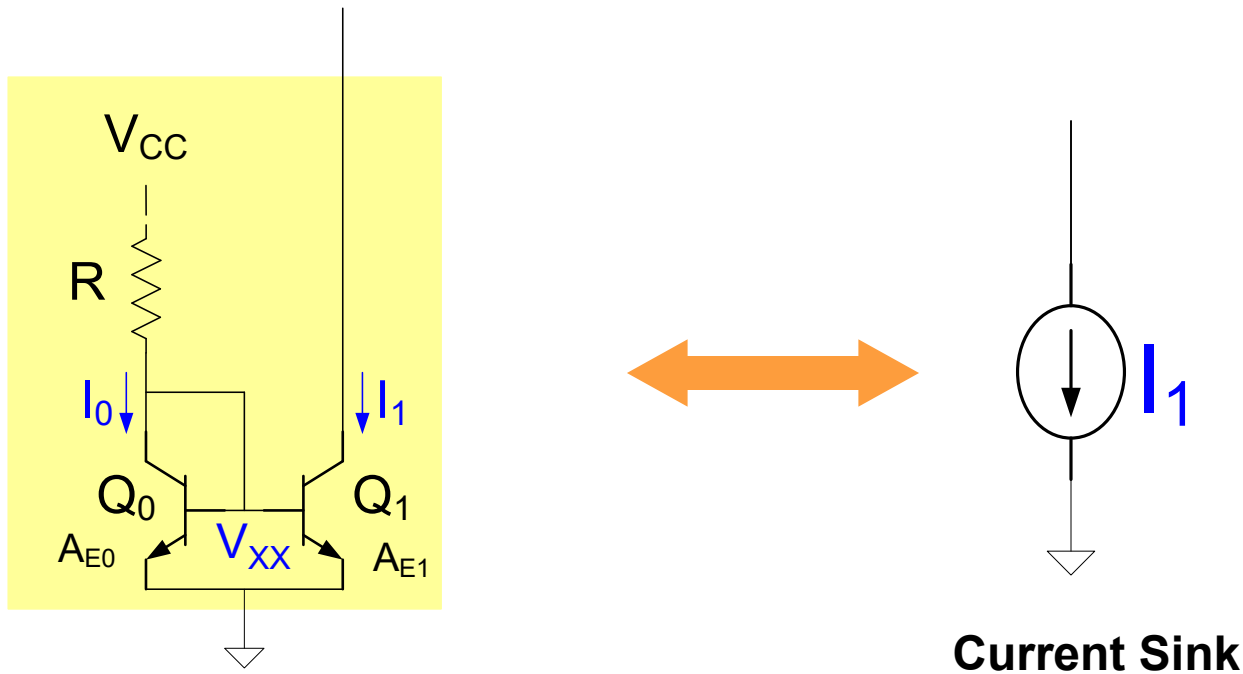

- **Multiple Outputs Possible**
- **Can be built for sourcing or sinking currents**
- **Also useful as a current amplifier**
- **MOS counterparts work very well and are not plagued by base current**




# Current Sources/Mirrors

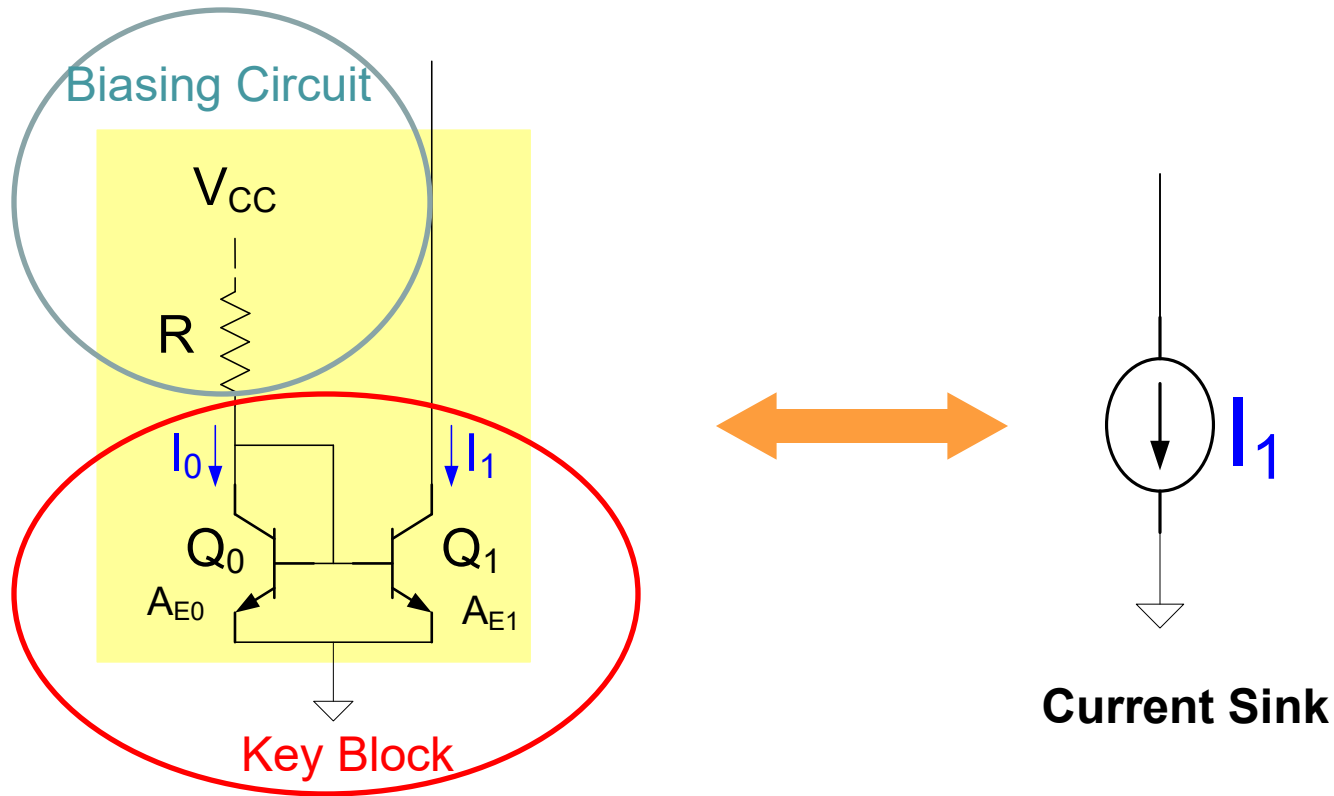

Two ways to look at this circuit:

- $Q_0$  and  $R$  bias  $Q_1$
- $R$  biases the  $Q_0 : Q_1$  block

# Current Sources/Mirrors

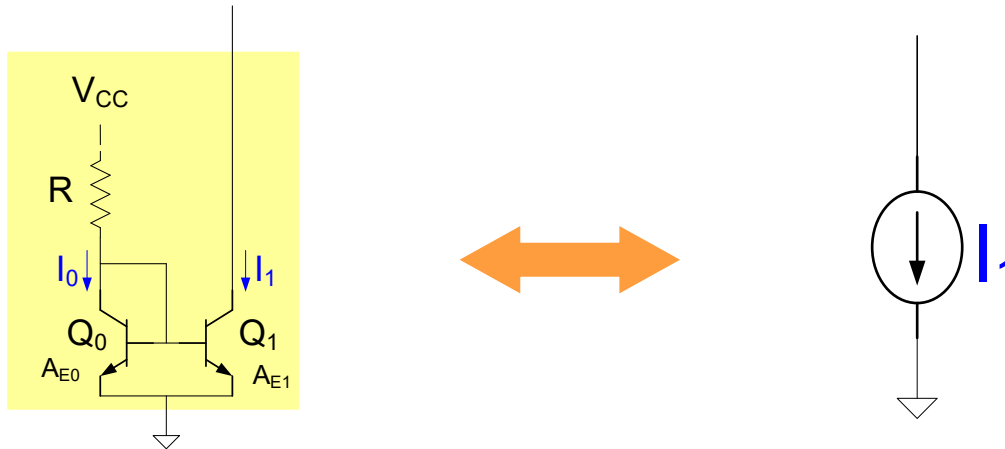

Current Sources are Seldom Available in Basic Laboratories:


Biasing of board-level and discrete electronic circuits is usually done with voltage sources, resistors, and capacitors

Biasing resistors and capacitors are used very sparingly in MOS circuits

Will show on-chip current sources can be very small

Biasing of on-chip circuits is often done with current sources instead of R's and C's

# Current Sources/Mirrors

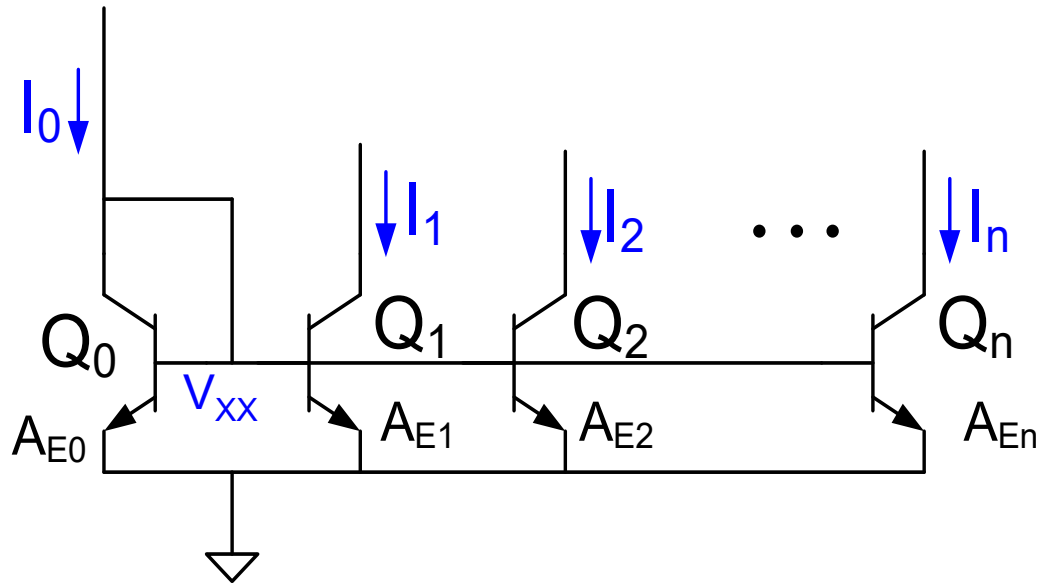


**Multiple-Output Bipolar Current Sink**

**If the base currents are neglected**

$$I_k = \left[ \frac{A_{Ek}}{A_{E0}} \right] I_0$$

# Current Sources/Mirrors

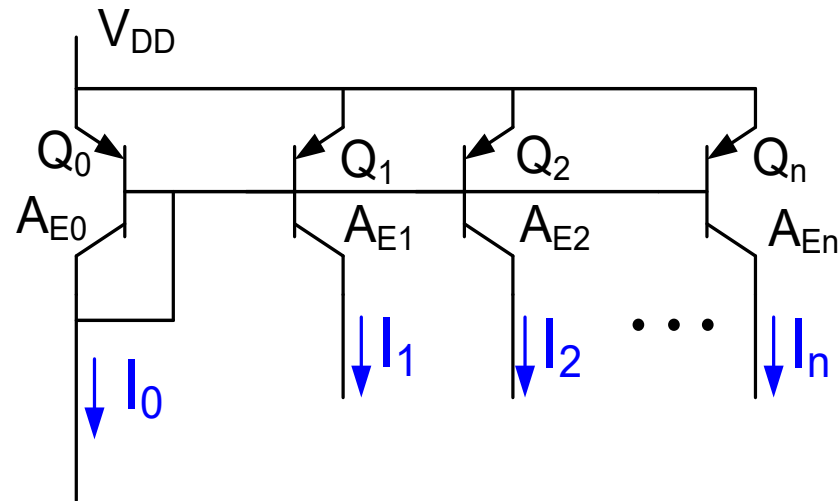


**Multiple-Output Bipolar Current Source**

**If the base currents are neglected**

$$I_k = \left[ \frac{A_{Ek}}{A_{E0}} \right] I_0$$

# Current Sources/Mirrors

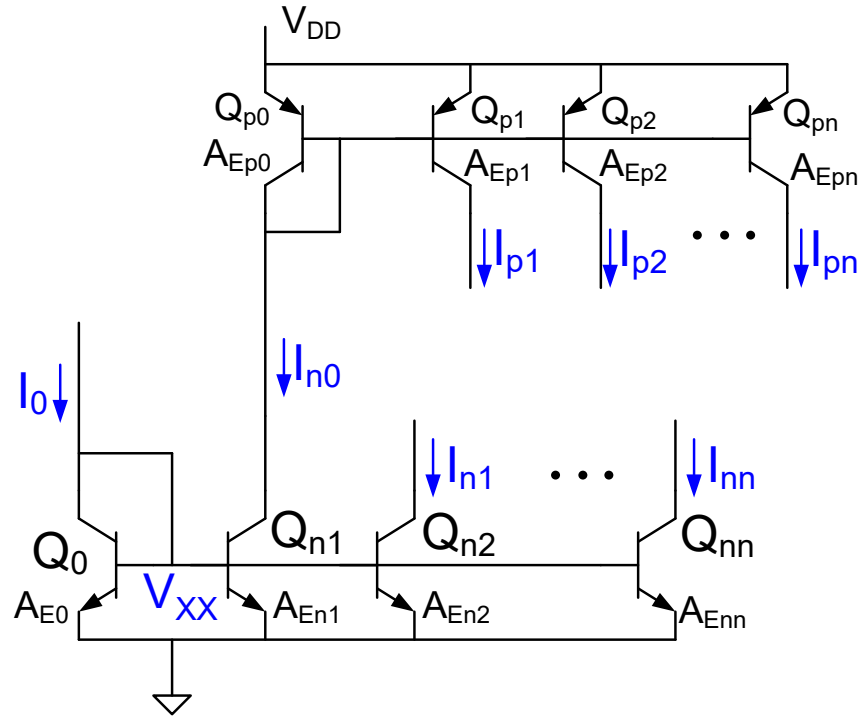


Multiple-Output Bipolar Current Source and Sink

$$I_{nk} = ?$$

$$I_{pk} = ?$$


# Current Sources/Mirrors

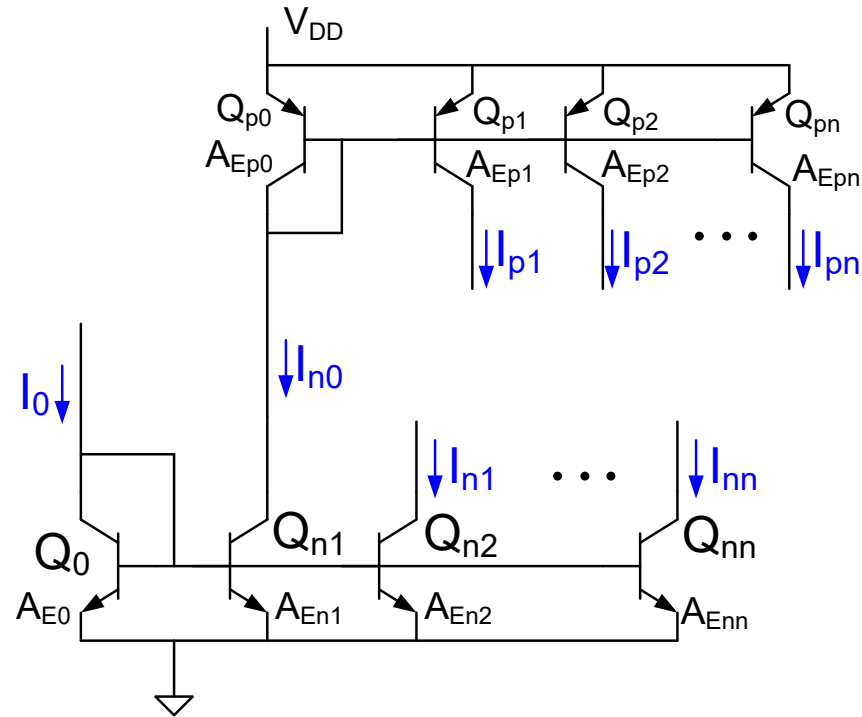

**Multiple-Output Bipolar Current Source and Sink**  
 If the base currents are neglected

$$I_{nk} = \left[ \frac{A_{Enk}}{A_{E0}} \right] I_0 \quad I_{pk} = \left[ \frac{A_{En1}}{A_{E0}} \right] \left[ \frac{A_{Epk}}{A_{Ep0}} \right] I_0$$

# Current Sources/Mirrors

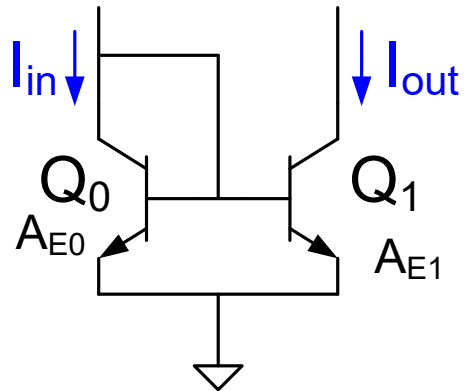


$$I_{out} = \left[ \frac{A_{E1}}{A_{E0}} \right] I_{in}$$

This circuit is termed a “current mirror”

Will re-derive the transfer characteristics of the current mirror assuming  $I_B$  is small compared to  $I_C$

$$\left. \begin{aligned} I_{IN} &= J_S A_{E0} e^{\frac{V_{BE}}{V_t}} \\ I_{OUT} &= J_S A_{E1} e^{\frac{V_{BE}}{V_t}} \end{aligned} \right\} \Rightarrow \frac{I_{OUT}}{I_{IN}} = \frac{J_S A_{E1} e^{\frac{V_{BE}}{V_t}}}{J_S A_{E0} e^{\frac{V_{BE}}{V_t}}} = \frac{A_{E1}}{A_{E0}}$$

# Current Sources/Mirrors

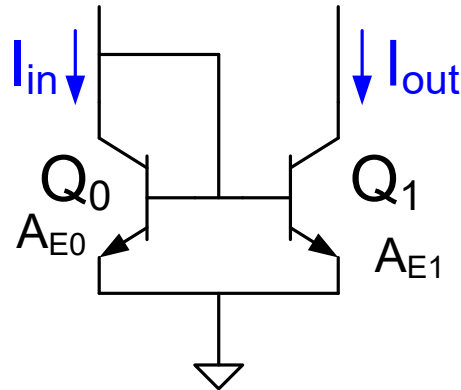

## npn Current Mirror

If the base currents are neglected


$$I_{out} = \left[ \frac{A_{E1}}{A_{E0}} \right] I_{in}$$

- Output current linearly dependent on  $I_{in}$
- Small-signal and large-signal relationships the same since linear
- Serves as a current amplifier
- Widely used circuit

**But  $I_{in}$  must be positive !**



# Current Sources/Mirrors

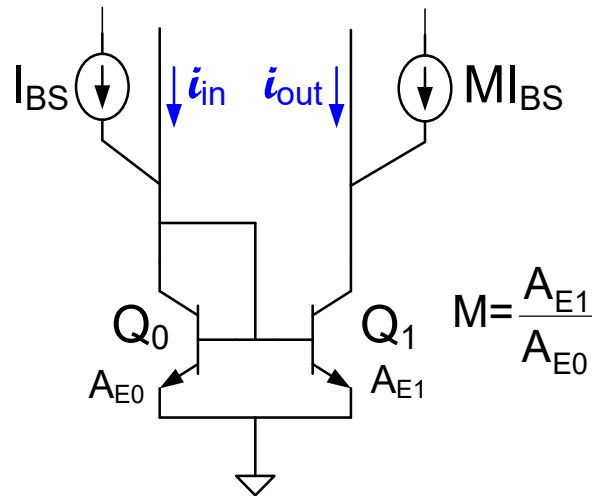

npn current mirror amplifier

$i_{out} = ?$

$$\frac{i_{OUT} + MI_{BS}}{i_{in} + I_{BS}} = M$$


$$i_{OUT} + MI_{BS} = M(i_{in} + I_{BS})$$

$$i_{OUT} + M\cancel{I}_{BS} = M(i_{in} + \cancel{I}_{BS})$$

$$\frac{i_{OUT}}{i_{in}} = M$$

But  $I_{BS} + i_{in} > 0$  !

# Current Sources/Mirrors

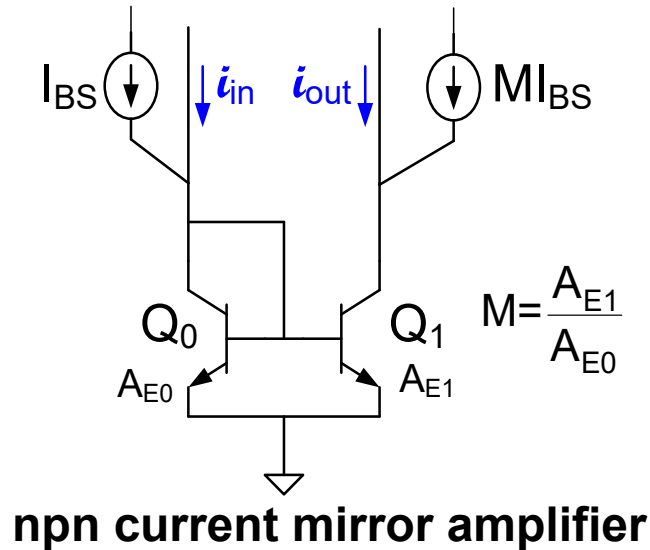


$$i_{\text{out}} = \left[ \frac{A_{E1}}{A_{E0}} \right] i_{\text{in}}$$

Amplifies both positive and negative currents (provided  $i_{\text{IN}} > -I_{\text{BS}}$ )


Current amplifiers are easy to build !!

Current gain can be accurately controlled with appropriate layout !!

# Current Sources/Mirrors

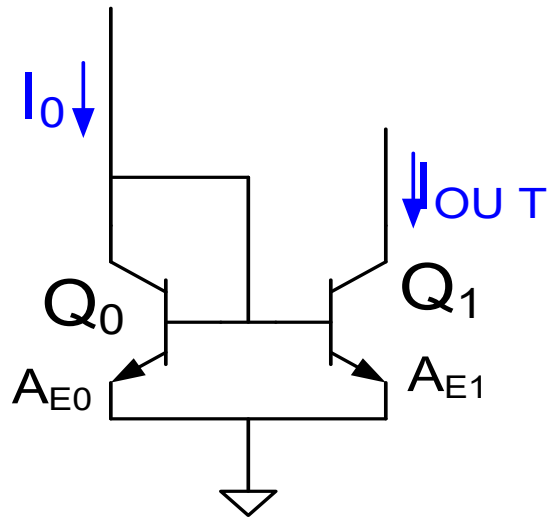


**npn Current Mirror**

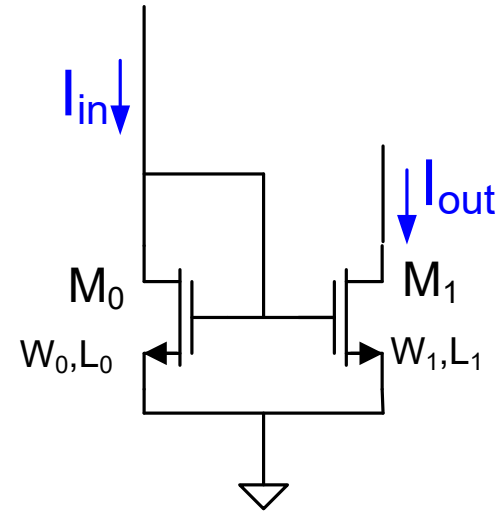

**n-channel Current Mirror**

$$I_{out} = ?$$

# Current Sources/Mirrors

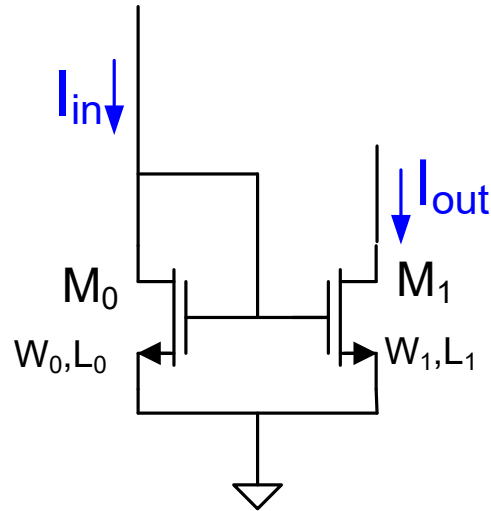

**n-channel Current Mirror**


$$\left. \begin{aligned} I_{in} &= \frac{\mu C_{OX} W_0}{2L_0} (V_{GS0} - V_{T0})^2 \\ I_{out} &= \frac{\mu C_{OX} W_1}{2L_1} (V_{GS1} - V_{T1})^2 \end{aligned} \right\}$$

If process parameters are matched, it follows that

$$I_{out} = \left[ \frac{W_1}{W_0} \frac{L_0}{L_1} \right] I_{in}$$

- Current mirror gain can be accurately controlled !
- Layout is important to get accurate gain (for both MOS and BJT)


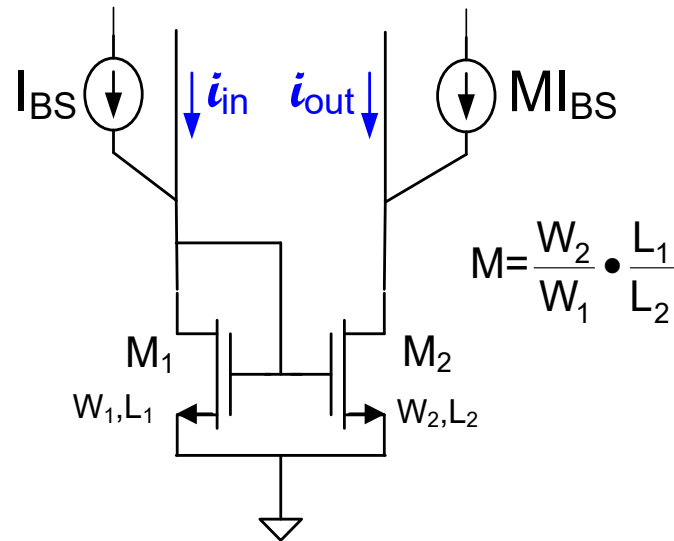
# n-channel current mirror current amplifier



$$i_{\text{out}} = \left[ \frac{W_2}{W_1} \frac{L_1}{L_2} \right] i_{\text{in}}$$

**Amplifies both positive and negative currents**


# Current Sources/Mirrors

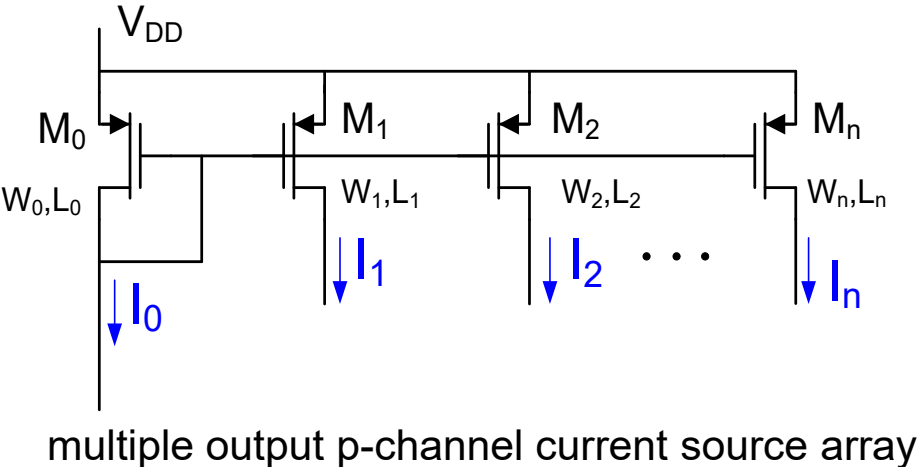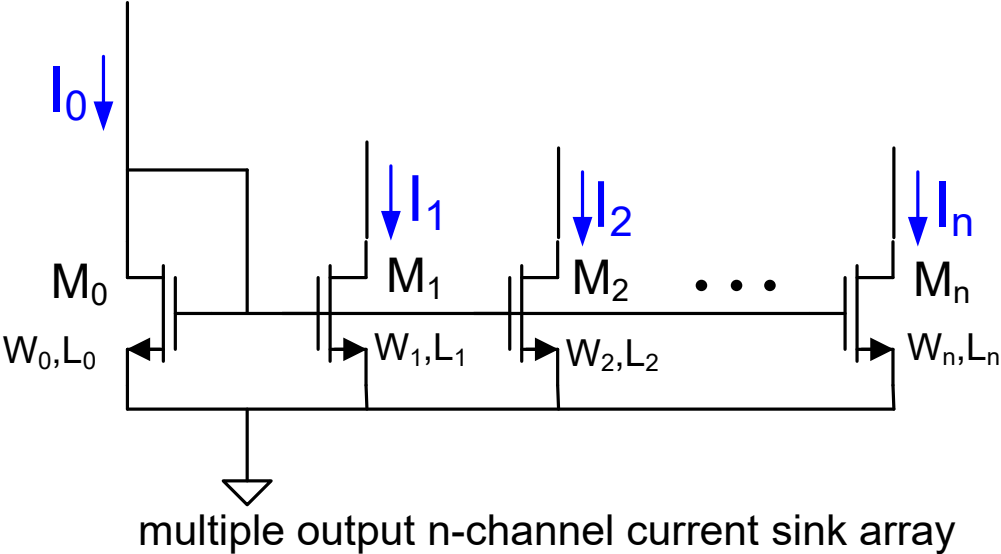

$$I_k = \left[ \frac{W_k L_0}{W_0 L_k} \right] I_0$$
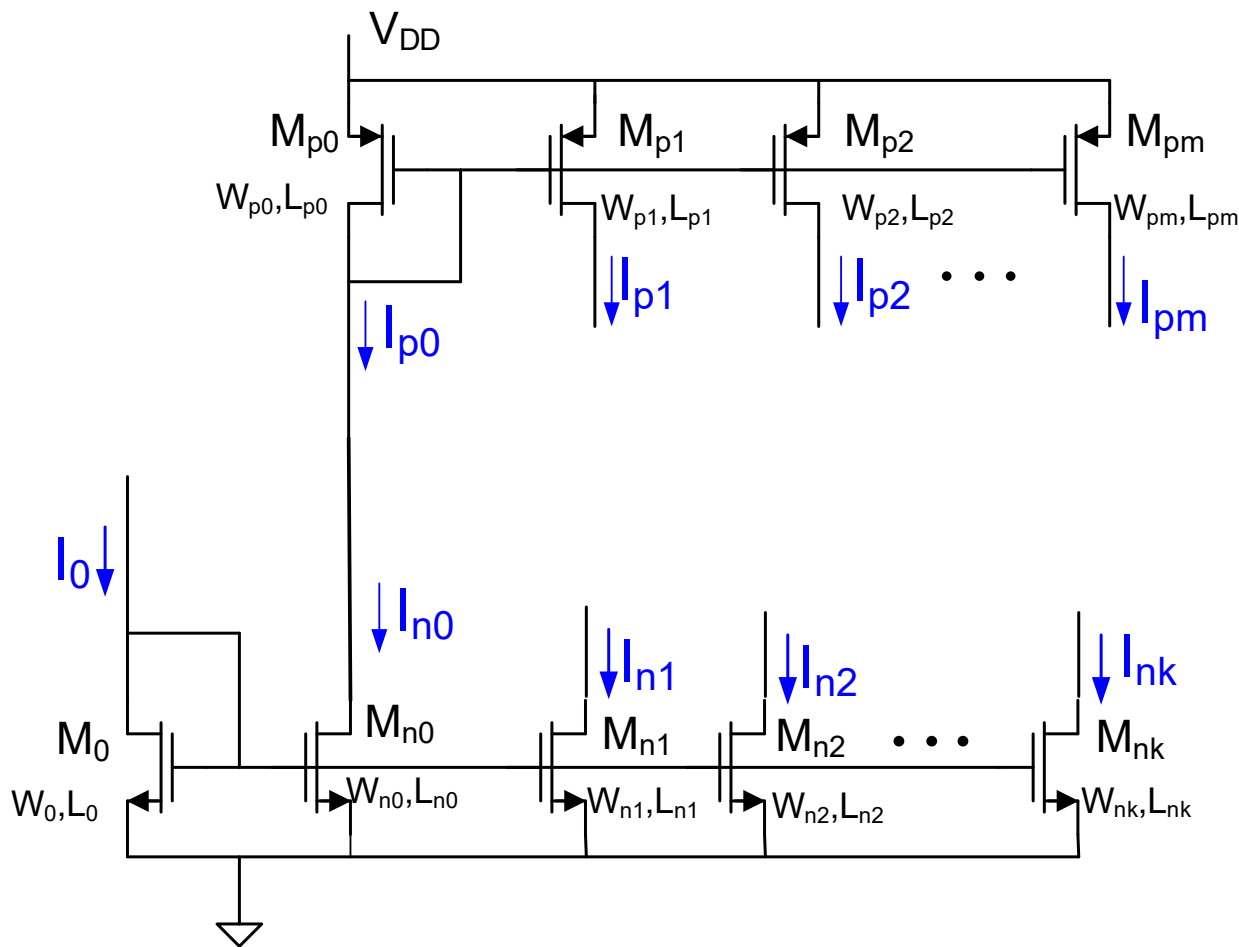
# Current Sources/Mirrors

multiple sourcing and sinking current outputs




$$I_{pj} = \left[ \frac{W_{pj}}{L_{pj}} \cdot \frac{L_{p0}}{W_{p0}} \right] M I_0$$

$$M = \left[ \frac{W_{n0}}{L_{n0j}} \cdot \frac{L_0}{W_0} \right]$$

$$I_{nj} = \left[ \frac{W_{nj}}{L_{nj}} \cdot \frac{L_0}{W_0} \right] I_0$$


m and k may be different  
Often M=1

# Current Sources/Mirrors Summary

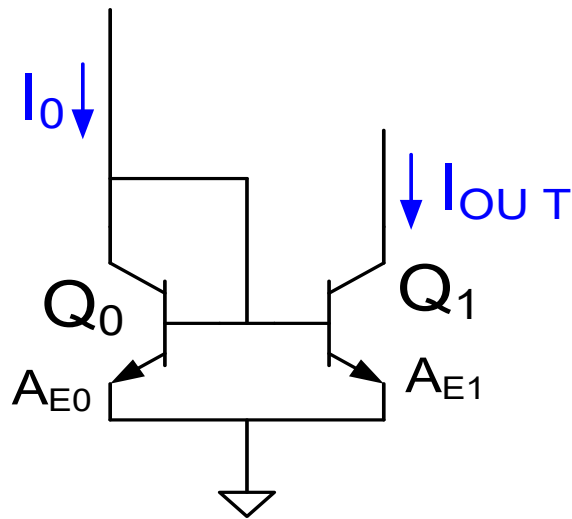

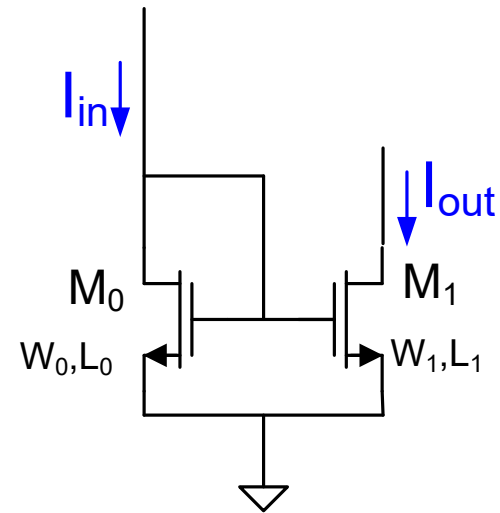**npn Current Mirror**

$$I_{out} = \left[ \frac{A_{E1}}{A_{E0}} \right] I_{in}$$



**n-channel Current Mirror**

$$I_{out} = \left[ \frac{W_1}{W_0} \frac{L_0}{L_1} \right] I_{in}$$

- Current mirror gain can be accurately controlled !
- Layout is important to get accurate gain (for both MOS and BJT)





Stay Safe and Stay Healthy !

End of Lecture 33