

EE 330

Lecture 41

Digital Circuits


Capacitive Loading Effects on Propagation Delay
Overdrive Factors
Propagation Delay With Multiple Levels of Logic

Fall 2024 Exam Schedule

Exam 1	Friday	Sept 27
Exam 2	Friday	October 25
Exam 3	Friday	Nov 22
Final Exam	Monday	Dec 16 12:00 - 2:00
PM		

The Reference Inverter

Reference Inverter

 

Assume $\mu_n/\mu_p=3$

$W_n=W_{MIN}$, $W_p=3W_{MIN}$

$L_n=L_p=L_{MIN}$

In 0.5u proc $t_{REF}=20ps$,
 $C_{REF}=4fF$, $R_{PDREF}=R_{PUREF}=2.5K$

$$R_{PDREF} = R_{PUREF}$$

$$C_{REF} = C_{IN} = 4C_{OX} W_{MIN} L_{MIN}$$

$$R_{PDREF} = \frac{L_{MIN}}{\mu_n C_{OX} W_{MIN} (V_{DD} - V_{Tn})} \stackrel{V_{Tn}=.2V_{DD}}{=} \frac{L_{MIN}}{\mu_n C_{OX} W_{MIN} (0.8V_{DD})}$$

$$t_{HLREF} = t_{LHREF} = R_{PDREF} C_{REF}$$

$$t_{REF} = t_{HLREF} + t_{LHREF} = 2R_{PDREF} C_{REF}$$


(Note: This C_{OX} is somewhat larger than that in the 0.5u ON process)

Device Sizing

Equal Worst-Case Rise/Fall Device Sizing Strategy (and same drive as ref inverter)
 -- (same as $V_{TRIP}=V_{DD}/2$ for worst case delay in typical process considered in example)

Assume $\mu_n/\mu_p=3$ **How many degrees of freedom were available?**

$L_n=L_p=L_{MIN}$

 


INV

$W_n=W_{MIN}, W_p=3W_{MIN}$

$C_{IN}=C_{REF}$

$FI=1$

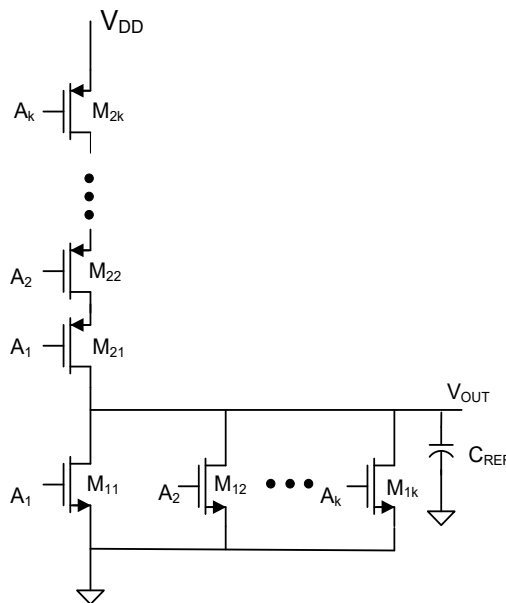


k-input NOR

$W_n=W_{MIN}, W_p=3kW_{MIN}$

$C_{IN}=\left(\frac{3k+1}{4}\right)C_{REF}$

$FI=\left(\frac{3k+1}{4}\right)$

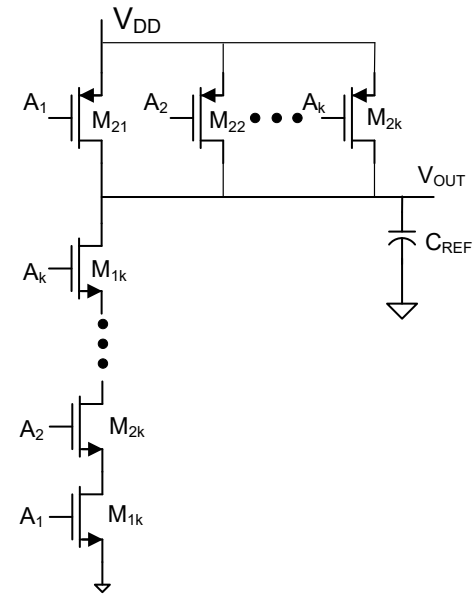

k-input NAND

$W_n=kW_{MIN}, W_p=3W_{MIN}$


$C_{IN}=\left(\frac{3+k}{4}\right)C_{REF}$

$FI=\left(\frac{3+k}{4}\right)$


Device Sizing

Multiple Input Gates:


2-input NOR

 


2-input NAND

 

k-input NOR

 

k-input NAND

 

Equal Worst Case Rise/Fall (and equal to that of ref inverter when driving C_{REF})

$W_n=?$

$W_p=?$

Fastest response (t_{HL} or t_{LH}) = ?

Worst case response (t_{PROP} , usually of most interest)?

Input capacitance (FI) = ?

Minimum Sized (assume driving a load of C_{REF})

$W_n=W_{min}$

$W_p=W_{min}$


Fastest response (t_{HL} or t_{LH}) = ?

Slowest response (t_{HL} or t_{LH}) = ?


Worst case response (t_{PROP} , usually of most interest)?

Input capacitance (FI) = ?

 
Device Sizing – minimum size driving C_{REF}



INV

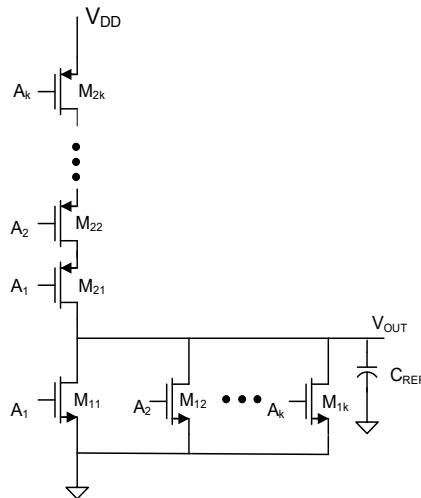

k-input NOR

 

k-input NAND

worst case

$$t_{PROP} = 0.5t_{REF} + \frac{3}{2}t_{REF}$$

$$t_{PROP} = 2t_{REF}$$

$$t_{PROP} = 0.5t_{REF} + \frac{3k}{2}t_{REF}$$

$$t_{PROP} = \left(\frac{3k+1}{2}\right)t_{REF}$$

$$t_{PROP} = \frac{3}{2}t_{REF} + \frac{k}{2}t_{REF}$$

$$t_{PROP} = \frac{3+k}{2}t_{REF}$$

$$\frac{1+3k^2}{2k}t_{REF} \leq t_{PROP} \leq \frac{3k+1}{2}t_{REF}$$

$$\frac{3+k^2}{2k}t_{REF} \leq t_{PROP} \leq \frac{3+k}{2}t_{REF}$$

$$FI = \frac{C_{REF}}{2}$$

$$FI = \frac{C_{REF}}{2}$$

$$FI = \frac{C_{REF}}{2}$$

$$R_{PU} = 3R_{PDREF}$$

$$\frac{R_{PDREF}}{k} \leq R_{PD} \leq R_{PDREF}$$


$$\frac{3R_{PDREF}}{k} \leq R_{PU} \leq 3R_{PDREF}$$

$$R_{PD} = R_{PDREF}$$


$$R_{PU} = 3kR_{PDREF}$$

$$R_{PD} = kR_{PDREF}$$


Device Sizing Summary

 

INV

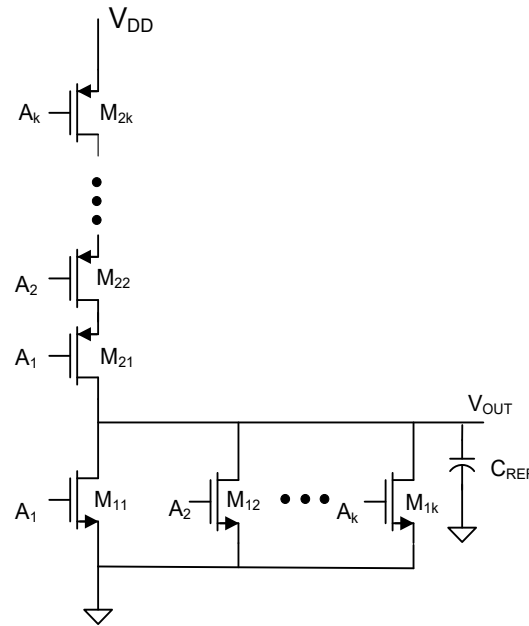

k-input NOR

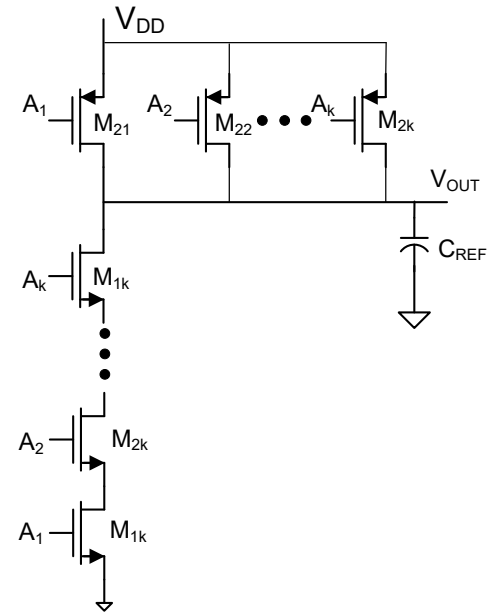

k-input NAND

C_{IN} for N_{AND} gates is considerably smaller than for NOR gates for equal worst-case rise and fall times

C_{IN} for minimum-sized structures is independent of number of inputs and much smaller than C_{IN} for the equal rise/fall time case

R_{PU} gets very large for minimum-sized NOR gate

Digital Circuit Design


- Hierarchical Design
- Basic Logic Gates
- Properties of Logic Families
- Characterization of CMOS Inverter
- Static CMOS Logic Gates
 - Ratio Logic
- Propagation Delay
 - Simple analytical models
 - FI/OD
 - Logical Effort
 - Elmore Delay
- Sizing of Gates
 - The Reference Inverter

- Propagation Delay with Multiple Levels of Logic
 - Optimal driving of Large Capacitive Loads
- Power Dissipation in Logic Circuits
 - Other Logic Styles
 - Array Logic
 - Ring Oscillators

→ **done**

→ **partial**

 Propagation Delay in Multiple-Levels of Logic with Stage Loading



Assume all gates sized for equal worst-case rise/fall times

For n levels of logic between A and F


$$t_{\text{PROP}} = \sum_{k=1}^n t_{\text{PROP}}(k)$$

Remember: t_{prop} is defined to be the worst-case (slowest) propagation delay

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Analysis strategy : Express delays in terms of those of reference inverter

Reference Inverter

 

Assume $\mu_n/\mu_p=3$

$W_n=W_{MIN}$, $W_p=3W_{MIN}$

In 0.5u proc $t_{REF}=20ps$,
 $C_{REF}=4fF$, $R_{PDREF}=2.5K$

$$C_{REF}=C_{IN}=4C_{OX}W_{MIN}L_{MIN}$$

$$FI=1$$


$$R_{PDREF} = \frac{L_{MIN}}{\mu_n C_{OX} W_{MIN} (V_{DD} - V_{Tn})} \stackrel{V_{Tn}=.2V_{DD}}{=} \frac{L_{MIN}}{\mu_n C_{OX} W_{MIN} (0.8V_{DD})}$$

$$t_{REF} = t_{HLREF} + t_{LHREF} = 2R_{PDREF} C_{REF}$$

$$L_n=L_p=L_{MIN}$$


(Note: This C_{OX} is somewhat larger than that in the 0.5u ON process)

 Propagation Delay in Multiple-Levels of Logic with Stage Loading



Assume:

 
- all gates sized for equal worst-case rise/fall times
- all gates sized to have worst-case rise and fall times equal to that of ref inverter when driving C_{REF}



Observe:

- With these assumptions, propagation delay of these gates will be scaled by the ratio of the total load capacitance on each gate to C_{REF}

 Propagation Delay in Multiple-Levels of Logic with Stage Loading



Assume:

- all gates sized for equal worst-case rise/fall times
- all gates sized to have worst case rise and fall times equal to that of ref inverter when driving C_{REF}


Observe:

- Propagation delay of these gates will be scaled by the ratio of the total load capacitance on each gate to C_{REF}

What loading will a gate see?

- Input capacitance to other gates
- Any load capacitors
- Parasitic interconnect capacitances

Propagation Delay with Stage Loading

 

$$t_{REF} = 2R_{PDref} C_{REF}$$

$$C_{REF} = 4C_{OX} W_{MIN} L_{MIN}$$

FI of a capacitor

$$FI_C = \frac{C}{C_{REF}}$$

FI of a gate (input k)

$$FI_G = \frac{C_{INK}}{C_{REF}}$$

FI of an interconnect

$$FI_I = \frac{C_{INI}}{C_{REF}}$$

Overall FI

$$FI = \frac{\sum_{Gates} C_{INGi} + \sum_{Capacitances} C_{INCi} + \sum_{Interconnects} C_{INIi}}{C_{REF}}$$

FI can be expressed either in units of capacitance or normalized to C_{REF}


Most commonly FI is normalized but must determine from context

If gates sized to have same drive as ref inverter

$$t_{prop-k} = t_{REF} \cdot FI_{LOAD-k}$$

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Example

 

Assume all gates sized for equal worst-case rise/fall times

Assume all gate drives are the same as that of reference inverter

Neglect interconnect capacitance, assume load of $10C_{REF}$ on F output

Determine propagation delay from A to F

$$t_{PROP} = \sum_{k=1}^4 t_{PROP-k}$$

$$t_{prop-k} = t_{REF} \cdot FI_{LOAD-k}$$


} →

$$t_{PROP} = t_{REF} \sum_{k=1}^4 FI_{LOAD-k}$$

$$FI_{LOAD-k} = FI_{k+1}$$

$$t_{PROP} = t_{REF} \sum_{k=1}^4 FI_{k+1}$$

 Propagation Delay in Multiple-Levels of Logic with Stage Loading



$$FI_{NOR} = \left(\frac{3k+1}{4}\right) C_{REF}$$

$$FI_{NAND} = \left(\frac{3+k}{4}\right) C_{REF}$$

Assume all gates sized for equal worst-case rise/fall times

Assume all gate drives are the same as that of reference inverter

Neglect interconnect capacitance, assume load of $10C_{REF}$ on F output

Determine propagation delay from A to F

$$t_{PROP} = t_{REF} \sum_{k=1}^4 FI_{k+1}$$

What loading will a gate see?

Derivation:

$$FI_2 = \frac{6}{4} C_{REF}$$


$$FI_3 = C_{REF} + \frac{7}{4} C_{REF}$$

$$FI_4 = \frac{7}{4} C_{REF} + \frac{13}{4} C_{REF}$$

$$FI_{LOAD} = FI_{"5"} = 10C_{REF}$$

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Example

 

Assume all gates sized for equal worst-case rise/fall times

Assume all gate drives are the same as that of reference inverter

Neglect interconnect capacitance, assume load of $10C_{REF}$ on F output

Determine propagation delay from A to F

$$t_{PROP} = t_{REF} \sum_{k=1}^4 FI_{k+1}$$

DERIVATIONS

$$FI_2 = \frac{6}{4} C_{REF}$$

$$FI_3 = C_{REF} + \frac{7}{4} C_{REF}$$

$$FI_4 = \frac{7}{4} C_{REF} + \frac{13}{4} C_{REF}$$

$$FI_5 = 10C_{REF}$$

$$t_{PROP1} = \frac{6}{4} t_{REF}$$

$$t_{PROP2} = \left(1 + \frac{7}{4}\right) t_{REF}$$


$$t_{PROP3} = \left(\frac{7}{4} + \frac{13}{4}\right) t_{REF}$$

$$t_{PROP4} = 10t_{REF}$$

$$t_{PROP} = \sum_{k=1}^n t_{PROP-k} = t_{REF} \sum_{k=1}^n FI_{k+1} = t_{REF} \left(\frac{6}{4} + \frac{11}{4} + \frac{20}{4} + 10 \right) = t_{REF} (19.25)$$

Propagation Delay Through Multiple Stages of Logic with Stage Loading

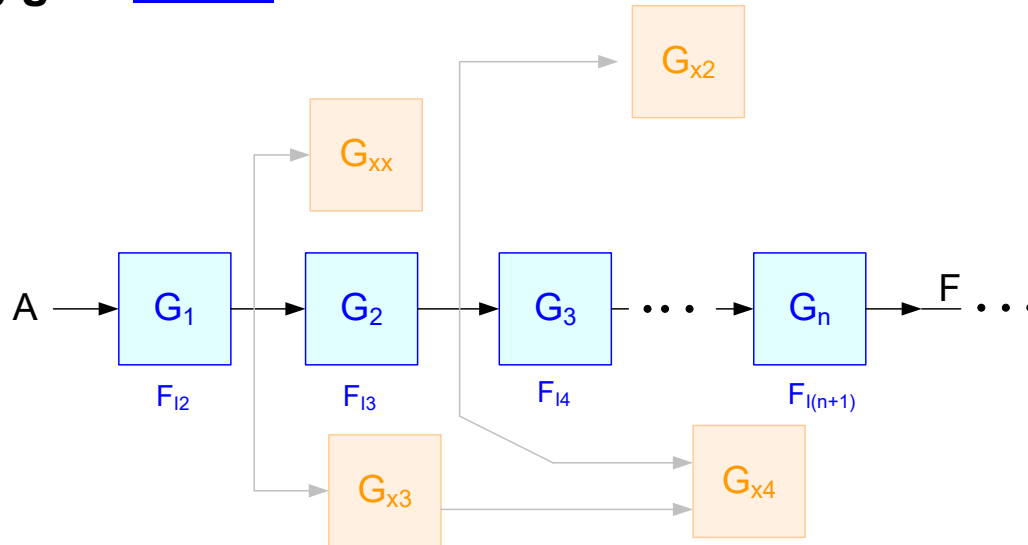(assuming gate drives are all same as that of reference inverter)



Summary:

Identify the gate path from A to F

$$t_{\text{PROP}k} = t_{\text{REF}} F_{I_{k+1}}$$

Propagation delay from A to F:

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n F_{I_{k+1}}$$

This approach is analytically manageable, provides modest accuracy and is “faithful”

Digital Circuit Design


- Hierarchical Design
- Basic Logic Gates
- Properties of Logic Families
- Characterization of CMOS Inverter
- Static CMOS Logic Gates
 - Ratio Logic
- Propagation Delay
 - Simple analytical models
 - FI/OD
 - Logical Effort
 - Elmore Delay
- Sizing of Gates
 - The Reference Inverter

- Propagation Delay with Multiple Levels of Logic
- Optimal driving of Large Capacitive Loads
- Power Dissipation in Logic Circuits
 - Other Logic Styles
 - Array Logic
 - Ring Oscillators

→ **done**

→ **partial**

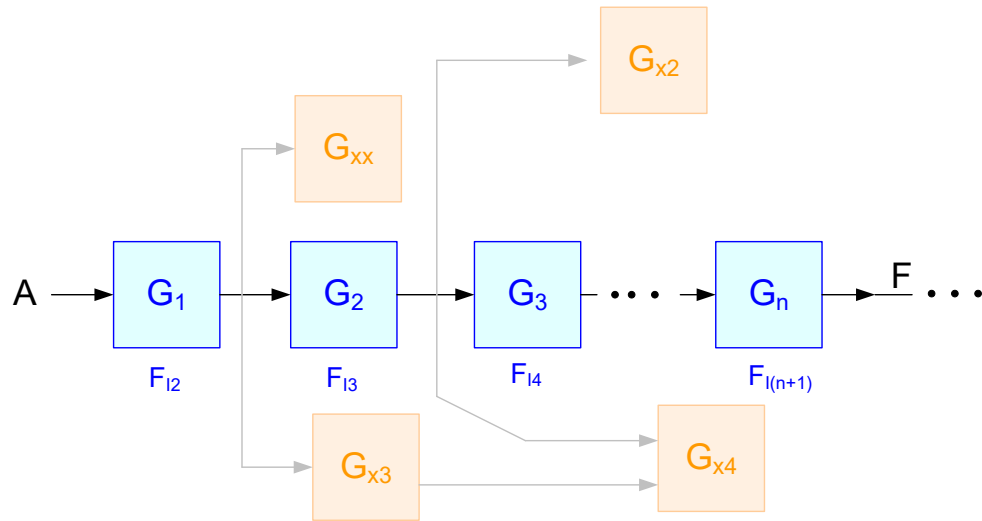What if the propagation delay is too long (or too short)?



Propagation delay from A to F:

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n F_{I_{(k+1)}}$$


$$t_{\text{PROPK}} = t_{\text{REF}} F_{I_{(k+1)}}$$

Recall:


Device Sizing

Multiple Input Gates:


2-input NOR

 


2-input NAND

 

k-input NOR

 

k-input NAND

 

Equal Worst Case Rise/Fall (and equal to that of ref inverter when driving C_{REF})

$W_n = ?$

$W_p = ?$

consider the fine print !

Fastest response (t_{HL} or t_{LH}) = ?

Worst case response (t_{PROP} , usually of most interest)?

Input capacitance (FI) = ?

Minimum Sized (assume driving a load of C_{REF})

$W_n = W_{min}$

$W_p = W_{min}$

Fastest response (t_{HL} or t_{LH}) = ?

Slowest response (t_{HL} or t_{LH}) = ?

Worst case response (t_{PROP} , usually of most interest)?

Input capacitance (FI) = ?

Recall:

Device Sizing

Equal Worst Case Rise/Fall

(and equal to that of ref inverter when driving C_{REF})

Multiple Input Gates: 2-input NOR

(n-channel devices sized same, p-channel devices sized the same)
 Assume $L_n=L_p=L_{min}$ and driving a load of C_{REF}

$W_n=?$


$W_p=?$

Input capacitance = ?

FI=?

$t_{PROP}=?$ (worst case)

DERIVATIONS

 

One degree of freedom was used to satisfy the constraint indicated

$W_n = W_{MIN}$

$W_p = 6W_{MIN}$


Other degree of freedom was used to achieve equal rise and fall times

$$C_{INA} = C_{INB} = C_{OX}W_{MIN}L_{MIN} + 6C_{OX}W_{MIN}L_{MIN} = 7C_{OX}W_{MIN}L_{MIN} = \left(\frac{7}{4}\right)4C_{OX}W_{MIN}L_{MIN} = \left(\frac{7}{4}\right)C_{REF}$$

$$FI = \left(\frac{7}{4}\right)C_{REF} \quad \text{or} \quad FI = \frac{7}{4}$$

$$t_{PROP} = t_{REF} \quad \text{(worst case)}$$

Overdrive Factors

 


Example: Determine t_{prop} in 0.5u process if $C=10pF$ In 0.5u proc $t_{REF}=20ps$,
 $C_{REF}=4fF$, $R_{PDREF}=2.5K$

$$t_{PROP} = t_{REF} \cdot FI = t_{REF} \cdot \frac{10pF}{4fF} = t_{REF} \cdot 2500$$

$$t_{PROP} = 20ps \cdot 2500 = 50nsec$$

Note this is generally considered to be unacceptably long !

Overdrive Factors

 

Scaling widths of ALL devices by constant ($W_{\text{scaled}} = W \times \text{OD}$) will change “drive” capability relative to that of the reference inverter but not change relative value of t_{HL} and t_{LH}

$$R_{\text{PD}} = \frac{L_1}{\mu_n C_{\text{OX}} W_1 (V_{\text{DD}} - V_{\text{Tn}})}$$



$$R_{\text{PDOD}} = \frac{L_1}{\mu_n C_{\text{OX}} [\text{OD} \cdot W_1] (V_{\text{DD}} - V_{\text{Tn}})} = \frac{R_{\text{PD}}}{\text{OD}}$$

$$R_{\text{PU}} = \frac{L_2}{\mu_p C_{\text{OX}} W_2 (V_{\text{DD}} + V_{\text{Tp}})}$$



$$R_{\text{PUOD}} = \frac{L_2}{\mu_p C_{\text{OX}} [\text{OD} \cdot W_2] (V_{\text{DD}} + V_{\text{Tp}})} = \frac{R_{\text{PU}}}{\text{OD}}$$

$$t_{\text{PROP}} = t_{\text{REF}} \cdot \text{Fl}_L \cdot \frac{1}{\text{OD}}$$

Scaling widths of ALL devices by constant will change Fl_{IN} to gate by OD


$$C_{\text{IN}} = C_{\text{OX}} (W_1 L_1 + W_2 L_2)$$



$$C_{\text{INOD}} = C_{\text{OX}} ([\text{OD} \cdot W_1] L_1 + [\text{OD} \cdot W_2] L_2) = \text{OD} \cdot C_{\text{IN}}$$

Overdrive Factors - Summary

(For equal worst-case rise/fall gates)

 

$$W = W_{\text{REF}} \cdot \text{OD}$$

$$R_{\text{PD-OD}} = \frac{R_{\text{PD-REF}}}{\text{OD}}$$



$$R_{\text{PU-OD}} = \frac{R_{\text{PU-REF}}}{\text{OD}}$$

Still equal worst-case rise/fall

$$t_{\text{PROP}} = t_{\text{REF}} \cdot \text{FI}_L \cdot \frac{1}{\text{OD}}$$

$$\text{FI}_{\text{IN}} = \text{OD} \cdot C_{\text{REF}}$$

Overdrive Factors

  

 
Example: Determine t_{prop} in 0.5u process if $C=10\text{pF}$ and $OD=1000$

$$t_{PROP1} = t_{REF} \cdot F_{I_LOAD} \cdot \frac{1}{OD} = t_{REF} \cdot \frac{10 \text{ pF}}{4 \text{ fF}} = t_{REF} \cdot 2500$$

$$t_{PROP2} = t_{REF} \cdot F_{I_LOAD} \cdot \frac{1}{OD} = t_{REF} \cdot \frac{10 \text{ pF}}{4 \text{ fF}} \cdot \frac{1}{1000} = t_{REF} \cdot 2.5$$














Note sizing the inverter with the OD improved delay by a factor of 1000 !

Overdrive Factors



- By definition, the factor by which the W/L of all devices are scaled above those of the reference inverter is termed the overdrive factor, OD
- Scaling widths by overdrive factor **DECREASES** resistance by same factor
- Scaling all widths by a constant does not compromise the symmetry between the rise and fall times (i.e. $t_{HL} = t_{LH}$)
- Judicious use of overdrive can dramatically improve the speed of digital circuits
- Large overdrive factors are often used
- Scaling widths by overdrive factor **INCREASES** input capacitance by same factor - **So is there any net gain in speed?**

Digital Circuit Design

-  Hierarchical Design
-  Basic Logic Gates
-  Properties of Logic Families
-  Characterization of CMOS Inverter
-  Static CMOS Logic Gates
 -  Ratio Logic
-  Propagation Delay
 -  Simple analytical models
 - FI/OD
 - Logical Effort
 - Elmore Delay
-  Sizing of Gates
 -  The Reference Inverter
-  Propagation Delay with Multiple Levels of Logic
-  Optimal driving of Large Capacitive Loads
-  Power Dissipation in Logic Circuits
 - Other Logic Styles
 - Array Logic
 - Ring Oscillators


 **done**

 **partial**


Propagation Delay with Over-drive Capability

 Example


Compare the propagation delays. Assume the OD is 900 in the third case and 30 in the fourth case. Don't worry about the extra inversion at this time.




$$t_{PROP} = 900t_{REF}$$

 
 
$$t_{PROP} = t_{REF} + 900t_{REF} = 901t_{REF}$$



 
$$t_{PROP} = 900t_{REF} + t_{REF} = 901t_{REF}$$



$$t_{PROP} = 30t_{REF} + 30t_{REF} = 60t_{REF}$$

- **Dramatic reduction in t_{PROP} is possible** (input is driving same in all 3 cases)
- **Will later determine what optimal number of stages and sizing is**

 Propagation Delay in Multiple-Levels of Logic with Stage Loading



F_{Ik} denotes the total loading on stage k which is the sum of the F_I of all loading on stage k

Summary: Propagation delay from A to F :

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n \frac{F_{I(k+1)}}{OD_k}$$


Propagation Delay in Multiple-Levels of Logic with Stage Loading

Will consider an example with the five cases

- Equal rise/fall (no overdrive)
- Equal rise/fall with overdrive
- Minimum Sized
- Asymmetric Overdrive
- Combination of equal rise/fall, minimum size and overdrive

Will develop the analysis methods as needed

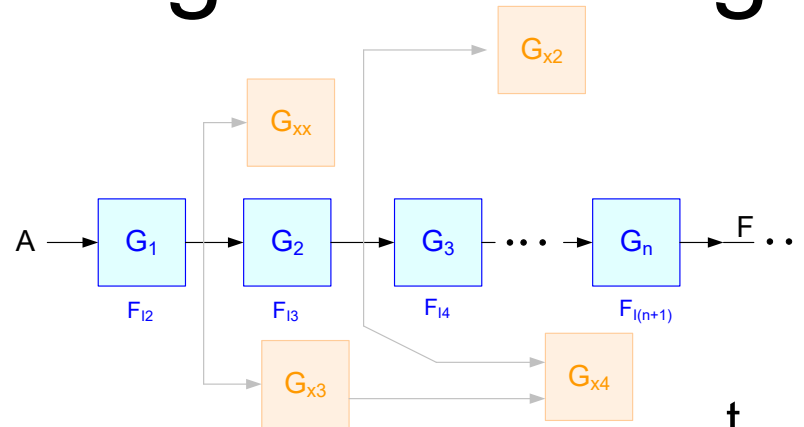Propagation Delay in Multiple-Levels of Logic with Stage Loading



- Equal rise/fall (no overdrive)
- Equal rise/fall with overdrive
- Minimum Sized
- Asymmetric Overdrive
- Combination of equal rise/fall, minimum size and overdrive

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n F_{l(k+1)}$$

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n \frac{F_{l(k+1)}}{\text{OD}_k}$$





$$t_{\text{PROP}} = ?$$

$$t_{\text{PROP}} = ?$$

$$t_{\text{PROP}} = ?$$

Driving Notation

    
- **Equal rise/fall (no overdrive)**
- **Equal rise/fall with overdrive**
- **Minimum Sized**
- **Asymmetric Overdrive**



Notation will be used only if it is not clear from the context what sizing is being used

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Asymmetric Overdrive

 

Recall:


Define the Asymmetric Overdrive Factors of the stage to be the factors by which PU and PD resistors are scaled relative to those of the reference inverter.

$$R_{PDEFF} = \frac{R_{PDREF}}{OD_{HL}}$$

$$R_{PUEFF} = \frac{R_{PUREF}}{OD_{LH}}$$

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Asymmetric Overdrive

 

Recall:

$$t_{\text{PROP}} = t_{\text{LH}} + t_{\text{HL}} = t_{\text{REF}} \frac{F_{\text{IL}}}{\text{OD}}$$

If inverter is not equal rise/fall



$$t_{\text{HL}} = \frac{R_{\text{PDREF}}}{\text{OD}_{\text{HL}}} C_L = \frac{1}{2} t_{\text{REF}} \frac{F_{\text{IL}}}{\text{OD}_{\text{HL}}}$$

$$t_{\text{LH}} = \frac{R_{\text{PUREF}}}{\text{OD}_{\text{LH}}} C_L = \frac{1}{2} t_{\text{REF}} \frac{F_{\text{IL}}}{\text{OD}_{\text{LH}}}$$

$$t_{\text{PROP}} = t_{\text{HL}} + t_{\text{LH}} = \frac{1}{2} t_{\text{REF}} F_{\text{IL}} \left(\frac{1}{\text{OD}_{\text{HL}}} + \frac{1}{\text{OD}_{\text{LH}}} \right)$$


Propagation Delay in Multiple-Levels of Logic with Stage Loading

Asymmetric Overdrive

  

$$t_{PROP} = t_{HL} + t_{LH} = \frac{1}{2} t_{REF} F_{ILOAD} \left(\frac{1}{OD_{HL}} + \frac{1}{OD_{LH}} \right)$$


When propagating through n stages:

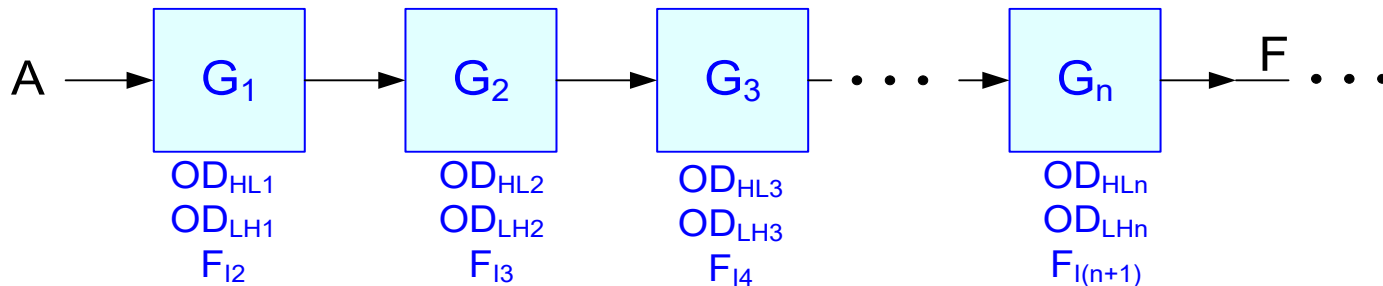

F_{Ik} denotes the total loading on stage k which is the sum of the F_I of all loading on stage k

$$t_{PROP} = t_{REF} \cdot \left(\frac{1}{2} \sum_{k=1}^n F_{I(k+1)} \left(\frac{1}{OD_{HLk}} + \frac{1}{OD_{LHk}} \right) \right)$$

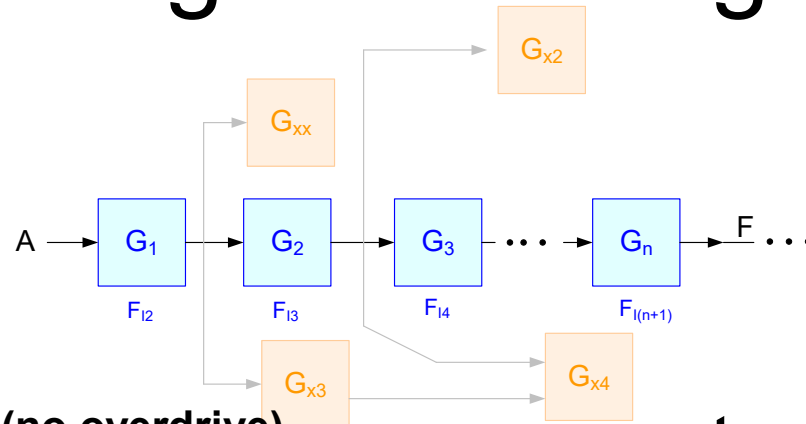Propagation Delay in Multiple-Levels of Logic with Stage Loading



• Equal rise/fall (no overdrive) $t_{\text{PROP}} = ?$


• Equal rise/fall with overdrive $t_{\text{PROP}} = ?$

• Minimum Sized $t_{\text{PROP}} = ?$

• Asymmetric Overdrive $t_{\text{PROP}} = ?$

• Combination of equal rise/fall, minimum size and overdrive $t_{\text{PROP}} = ?$

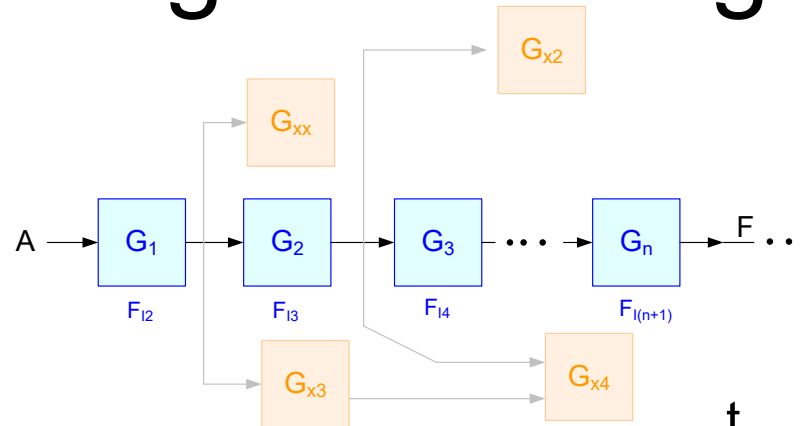Propagation Delay in Multiple-Levels of Logic with Stage Loading



- Equal rise/fall (no overdrive)

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n F_{l(k+1)}$$

- Equal rise/fall with overdrive

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n \frac{F_{l(k+1)}}{\text{OD}_k}$$

- Minimum Sized

$$t_{\text{PROP}} = ?$$


- Asymmetric Overdrive

$$t_{\text{PROP}} = t_{\text{REF}} \cdot \left(\frac{1}{2} \sum_{k=1}^n F_{l(k+1)} \left(\frac{1}{\text{OD}_{\text{HLK}}} + \frac{1}{\text{OD}_{\text{LHK}}} \right) \right)$$

- Combination of equal rise/fall, minimum size and overdrive

$$t_{\text{PROP}} = ?$$

 Propagation Delay in Multiple-Levels of Logic with Stage Loading



- Equal rise/fall (no overdrive)

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n F_{l(k+1)} \quad \checkmark$$

- Equal rise/fall with overdrive

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n \frac{F_{l(k+1)}}{\text{OD}_k}$$

- Minimum Sized

$$t_{\text{PROP}} = ?$$

- Asymmetric Overdrive


$$t_{\text{PROP}} = t_{\text{REF}} \cdot \left(\frac{1}{2} \sum_{k=1}^n F_{l(k+1)} \left(\frac{1}{\text{OD}_{\text{HLk}}} + \frac{1}{\text{OD}_{\text{LHk}}} \right) \right)$$

- Combination of equal rise/fall, minimum size and overdrive

$$t_{\text{PROP}} = ?$$

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Equal rise-fall gates, no overdrive

 

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n F_{l_{k+1}}$$



$$\frac{t_{\text{PROP}}}{t_{\text{REF}}} = \sum_{k=1}^n F_{l_{k+1}}$$

In 0.5u proc $t_{\text{REF}}=20\text{ps}$,
 $C_{\text{REF}}=4\text{fF}$, $R_{\text{PDREF}}=2.5\text{K}$

Propagation Delay in Multiple-Levels of Logic with Stage Loading


Equal rise-fall gates, no overdrive

	Equal Rise/Fall
C_{IN}/C_{REF}	
Inverter	1
NOR	$\frac{3k+1}{4}$
NAND	$\frac{3+k}{4}$
Overdrive	
Inverter	
HL	1
LH	1
NOR	
HL	1
LH	1
NAND	
HL	1
LH	1
t_{PROP}/t_{REF}	$\sum_{k=1}^n F_{(k+1)}$

Equal rise-fall gates, no overdrive

In 0.5u proc $t_{REF}=20ps$,
 $C_{REF}=4fF, R_{PDREF}=2.5K$

 
(Note: This C_{OX} is somewhat larger than that in the 0.5u ON process)



Equal rise-fall gates, no overdrive


In 0.5u proc $t_{REF}=20ps$,
 $C_{REF}=4fF, R_{PDREF}=2.5K$

 (Note: This C_{OX} is somewhat larger than that in the 0.5u ON process)



$$t_{PROP} = 32.5 t_{REF}$$

 How does this propagation delay compare to that required for a propagation of a signal through 5-levels of logic with only reference inverters (load is a ref inverter instead of 50fF as well)?



$$t_{PROP} = 5 t_{REF}$$

Loading can have a dramatic effect on propagation delay



Stay Safe and Stay Healthy !

End of Lecture 41