

# EE 330


## Lecture 7

### Propagation Delay


## Review from Last Time

# MOS Transistor
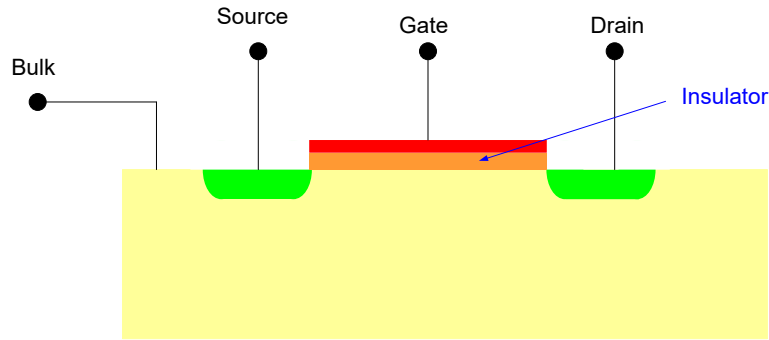
## Qualitative Discussion of n-channel Operation




For  $V_{GS}$  small

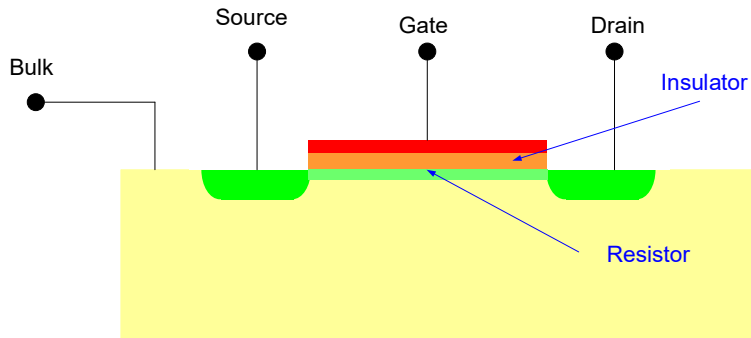

n-channel MOSFET

For  $V_{GS}$  large

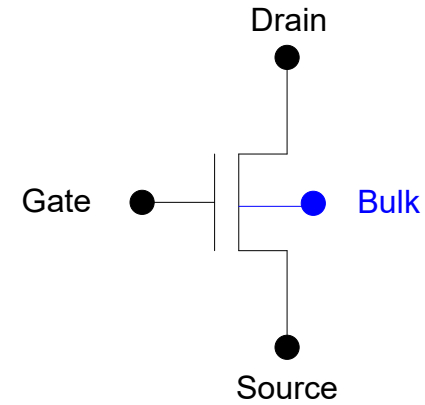- Region under gate termed the “channel”
- When “resistor” is electrically created, region where it resides in channel is termed an “inversion region”




MOSFET actually 4-terminal device

## Review from Last Time


# MOS Transistor
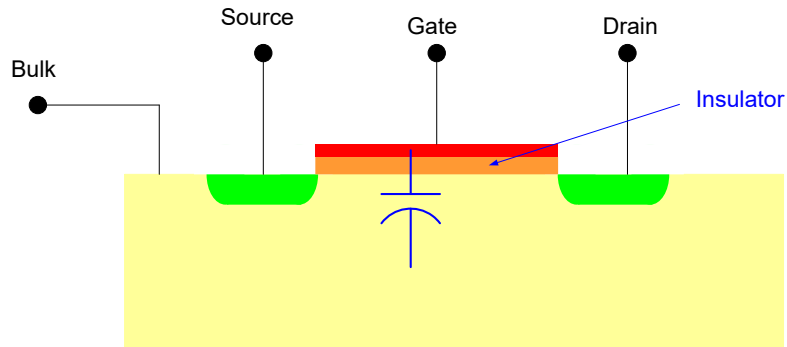
## Qualitative Discussion of n-channel Operation



n-channel MOSFET


For  $V_{GS}$  small

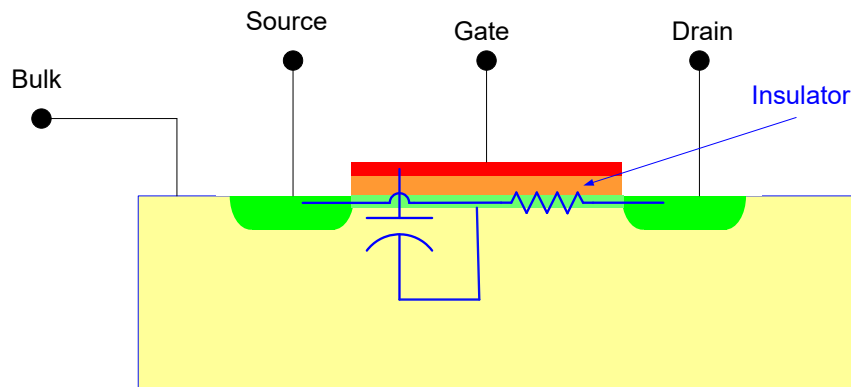

n-channel MOSFET

For  $V_{GS}$  large

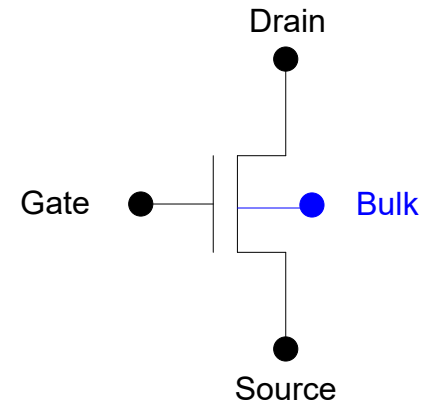
- Electrically created inversion layer forms a “thin “film” resistor
- Capacitance from gate to channel region is distributed
- Lumped capacitance much easier to work with



## Review from Last Time


# MOS Transistor
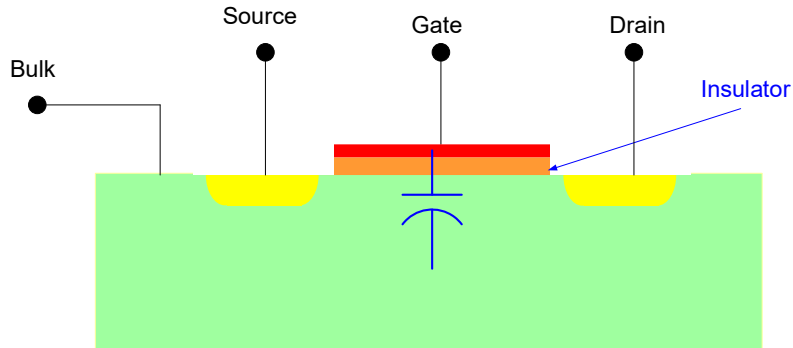
## Qualitative Discussion of p-channel Operation




p-channel MOSFET

For  $|V_{GS}|$  small

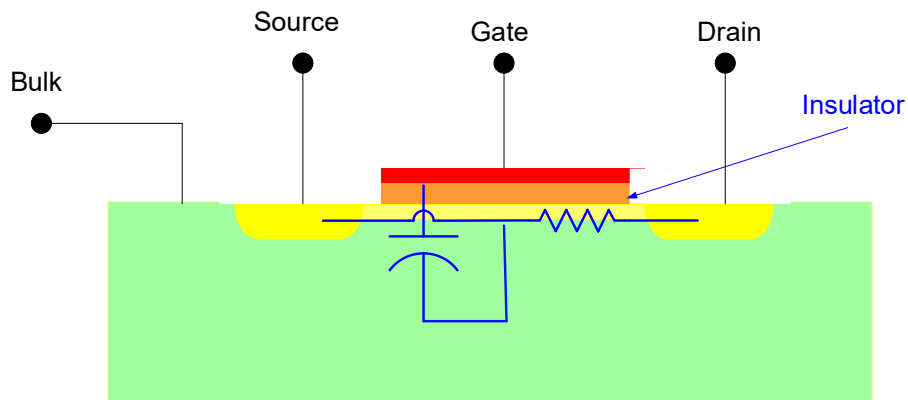

p-channel MOSFET


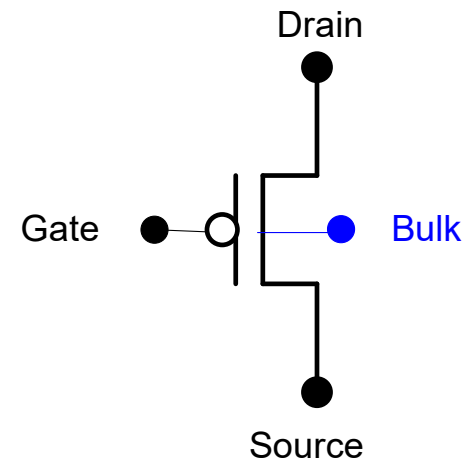


For  $|V_{GS}|$  large

- Electrically created inversion layer forms a “thin “film” resistor
- Capacitance from gate to channel region is distributed
- Lumped capacitance much easier to work with

## Review from Last Time

# Improved Switch-Level Model

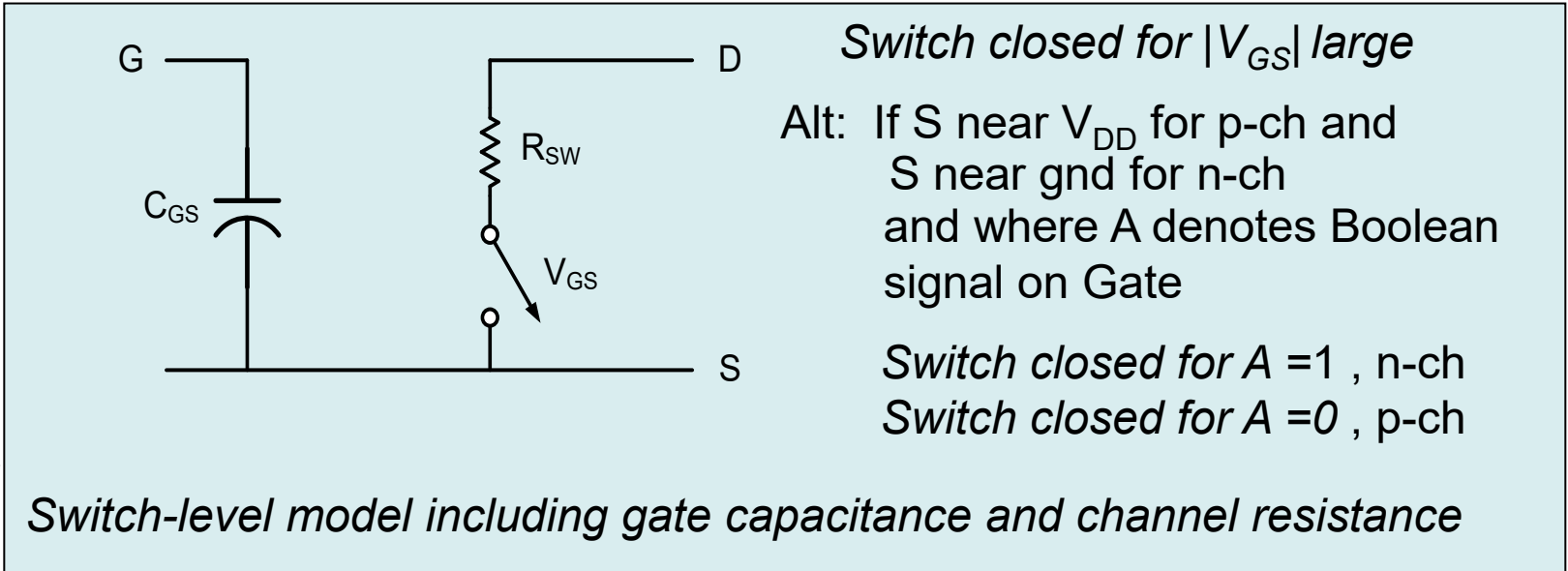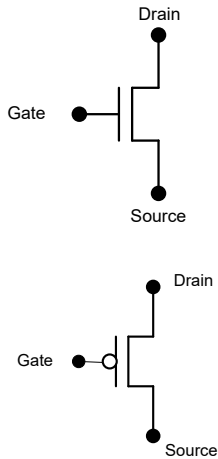

*$C_{GS}$  and  $R_{SW}$  dependent upon device sizes and process*



*For minimum-sized devices in a 0.5u process with  $V_{DD}=5V$*

$$C_{GS} \cong 1.5\text{fF} \quad R_{sw} \cong \left. \begin{array}{l} 2\text{K}\Omega \text{ n-channel} \\ 6\text{K}\Omega \text{ p-channel} \end{array} \right\}$$

*Considerable emphasis will be placed upon device sizing to manage  $C_{GS}$  and  $R_{SW}$*

## Review from Last Time

# Improved Switch-Level Model

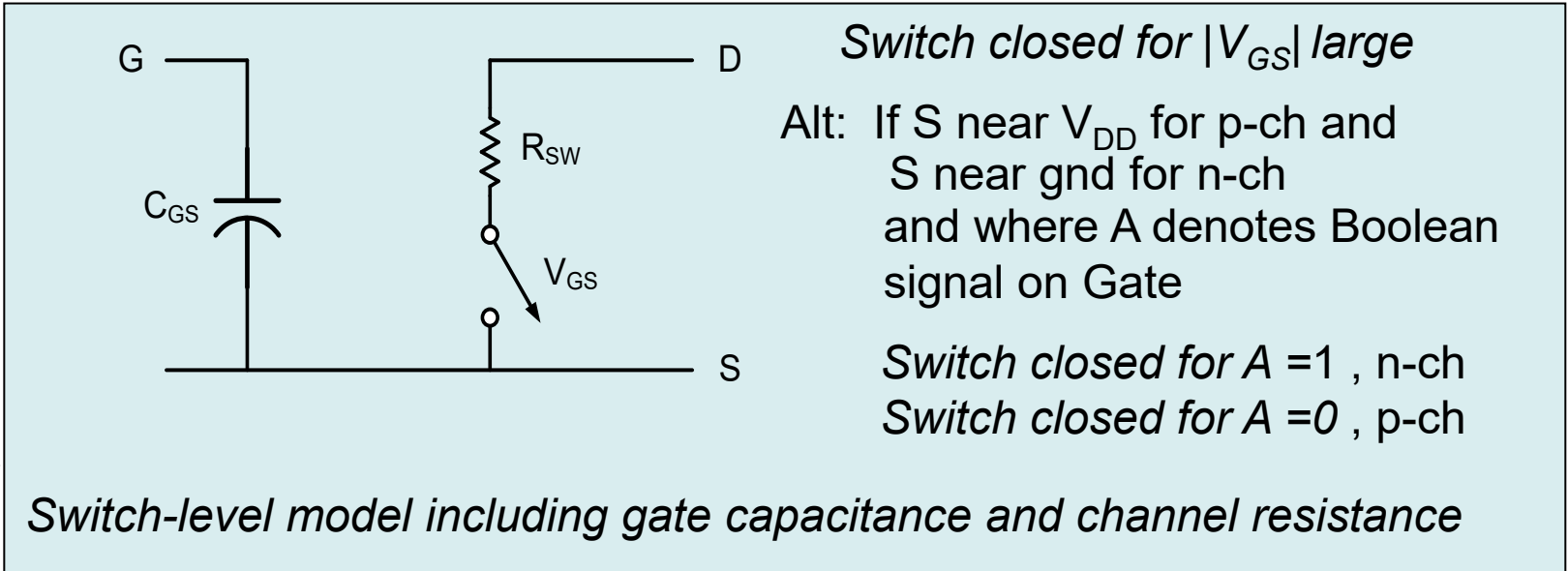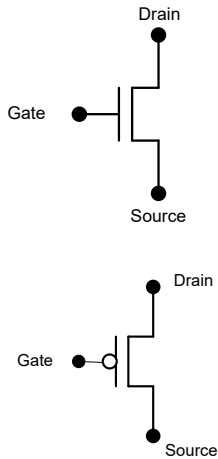

*$C_{GS}$  and  $R_{SW}$  dependent upon device sizes and process*


*Will assume for minimum-sized devices in a 0.18u process with  $V_{DD}=2V$*

$$C_{GS} \cong 1.5\text{fF} \quad R_{sw} \cong \left. \begin{array}{l} 2\text{K}\Omega \text{ n-channel} \\ 6\text{K}\Omega \text{ p-channel} \end{array} \right\}$$

*Considerable emphasis will be placed upon device sizing to manage  $C_{GS}$  and  $R_{SW}$*

Review from Last Time
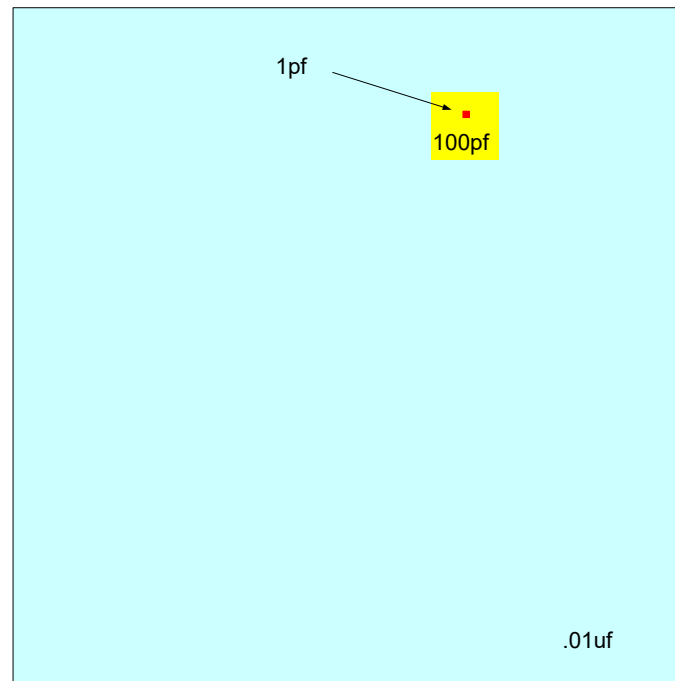
# Is a capacitor of 1.5fF small enough to be neglected?




## From EE 201 Parts Kit

Capacitors (Farads)		
100p	3	
470p	3	
0.001u	3	2
0.0047u	3	2
0.01u	3	
0.047u	3	
0.1u	3	1
0.47u	3	
1u	3	
10u	3	
100u	3	

Area allocations shown to relative scale:

Review from Last Time
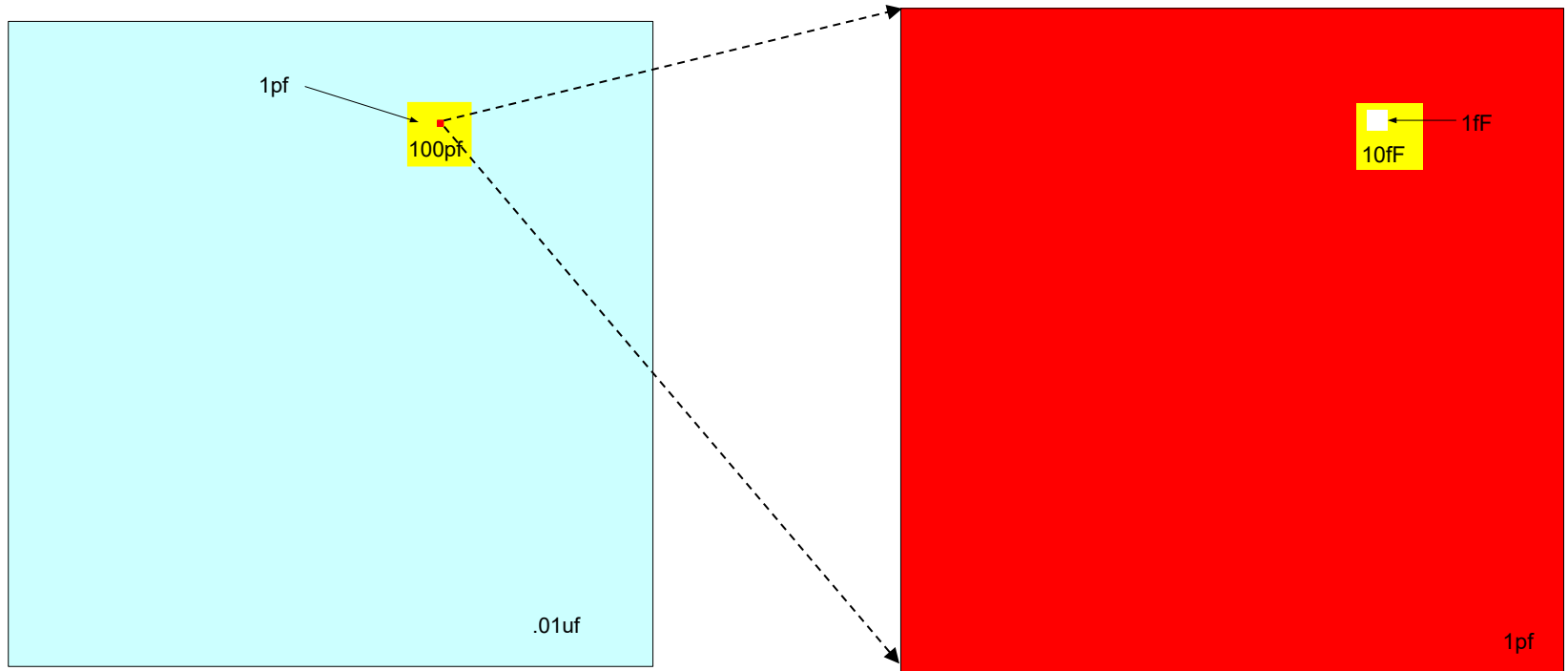
# Is a capacitor of 1.5fF small enough to be neglected?




**Area allocations shown to relative scale:**

- **Not enough information at this point to determine whether this very small capacitance can be neglected**
- **Will answer this important question later**




# Review from Last Time


# Model Summary (for n-channel)

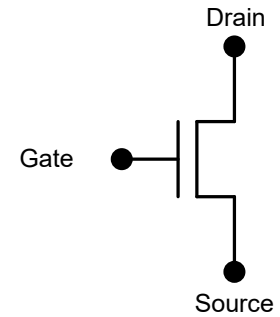

## 1. Switch-Level model

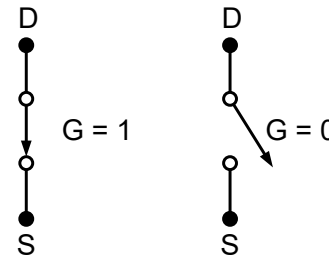

## 2. Improved switch-level model

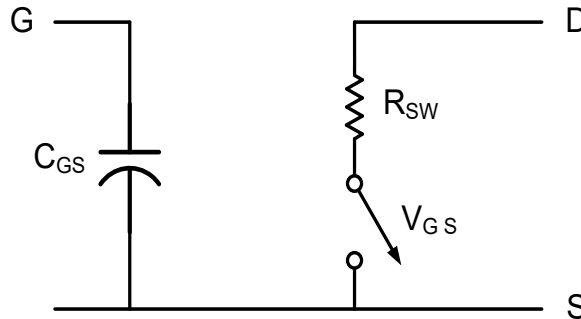


**Switch closed for  $V_{GS} = \text{large}$**   
**Switch open for  $V_{GS} = \text{small}$**


**Other models will be developed later**

# Review from Last Time


# Model Summary (for p-channel)

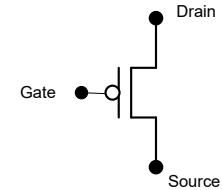

## 1. Switch-Level model

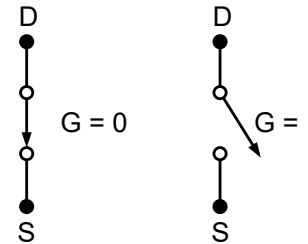

## 2. Improved switch-level model

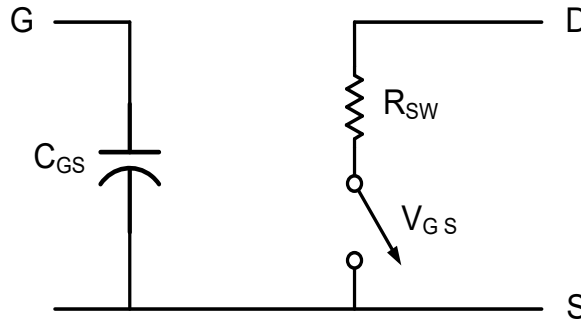

**Switch closed for  $|V_{GS}| = \text{large}$**   
**Switch open for  $|V_{GS}| = \text{small}$**


**Other models will be developed later**

# Propagation Delay

# Example


*What are  $t_{HL}$  and  $t_{LH}$ ?*

*Assume  $V_{DD}=5V$*


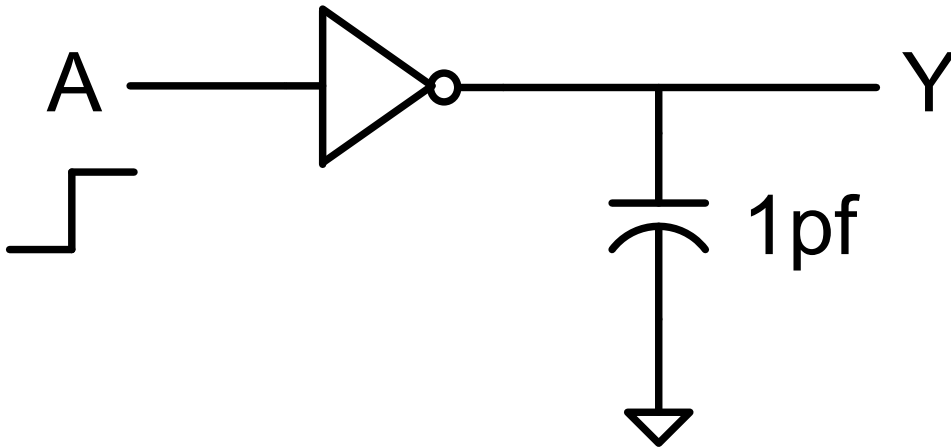


*With basic switch level model ?*


*With improved switch level model ?*

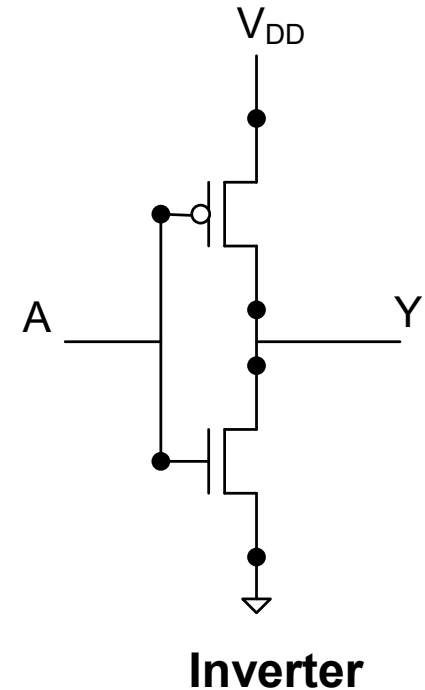

# Example

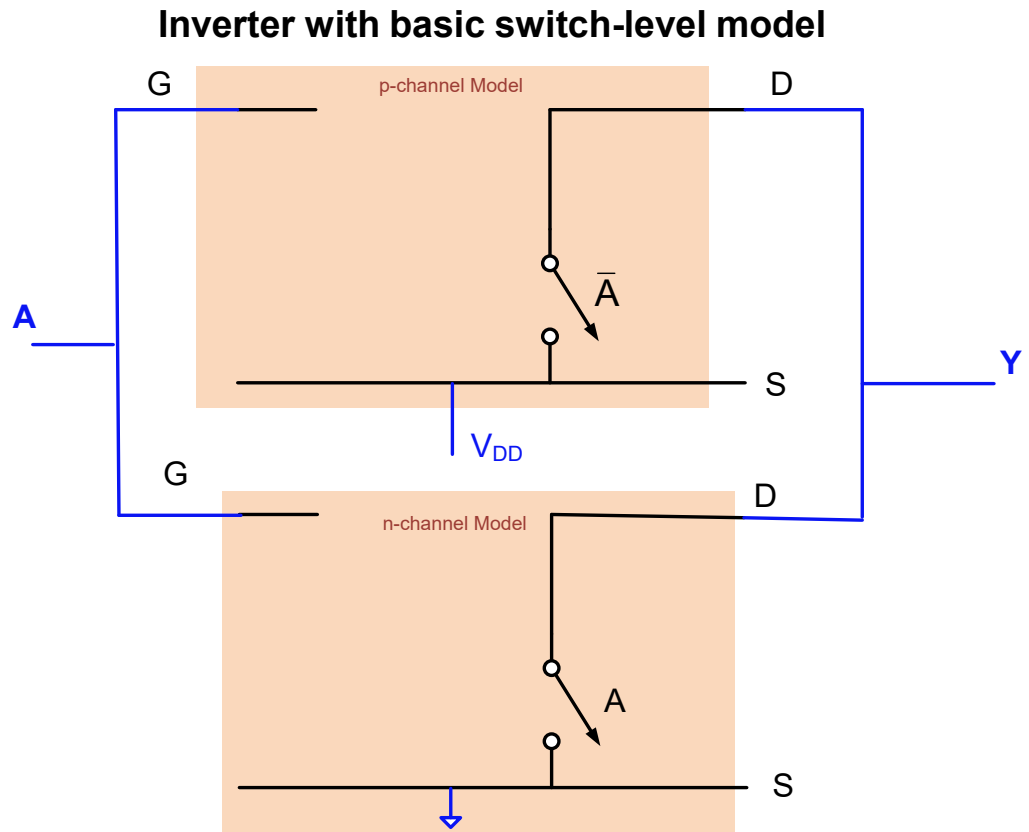
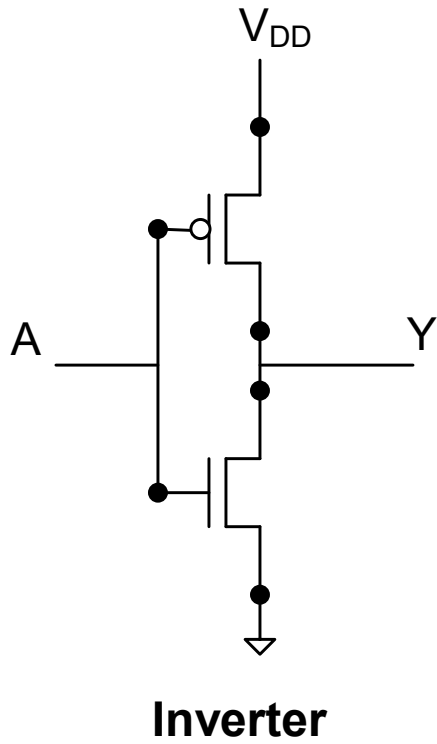

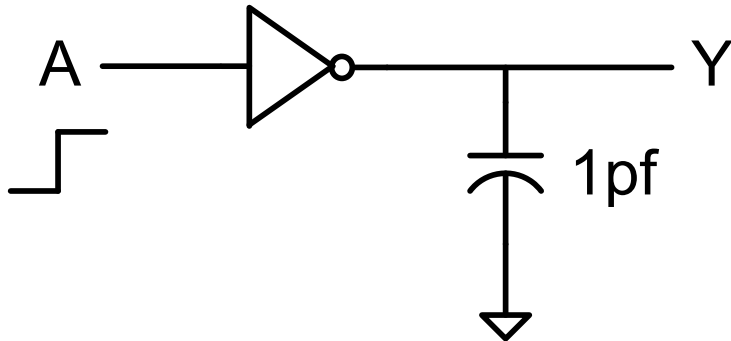
# Example *What are $t_{HL}$ and $t_{LH}$ at output?*



**Assume ideal step at A input**


***With basic switch level model***

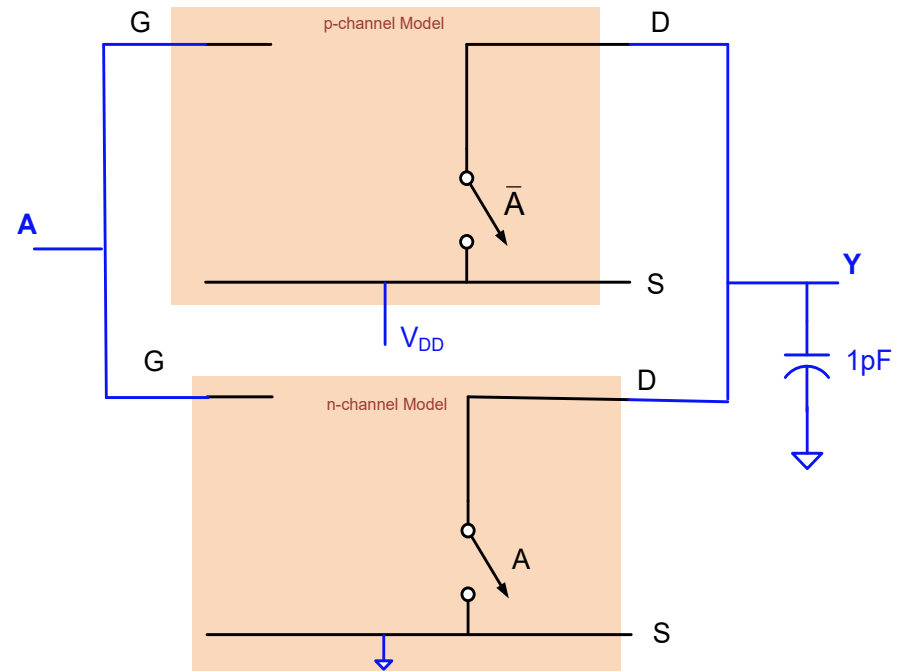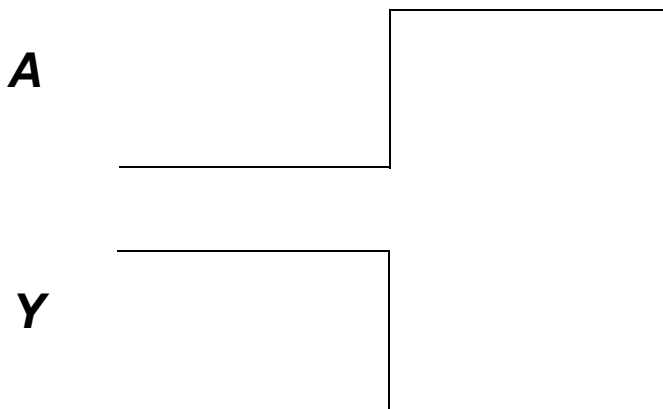


$$t_{HL} = t_{LH} = 0$$
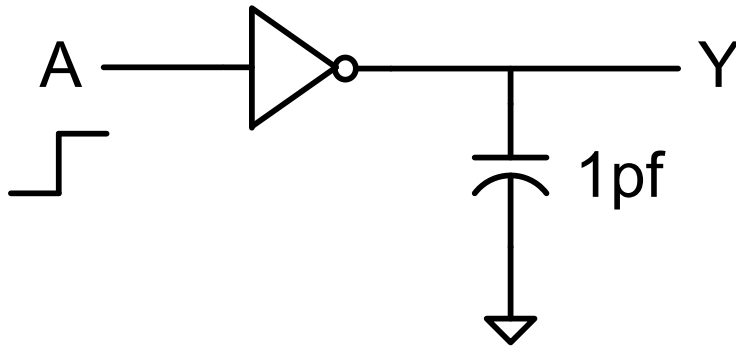
# Example (cont)


*With simple switch-level model*  $t_{HL} = t_{LH} = 0$



*With improved model ?*

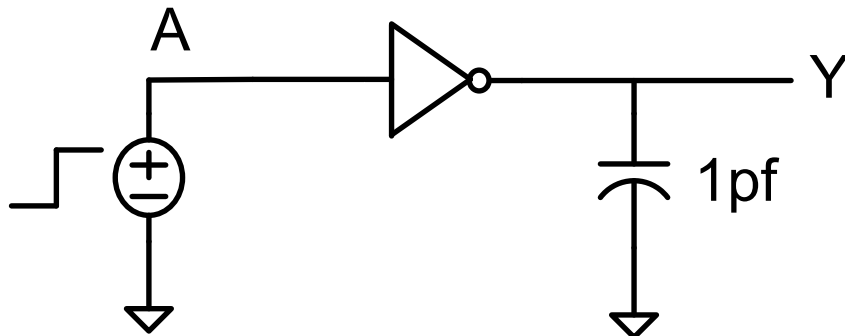



*Inverter Model?*

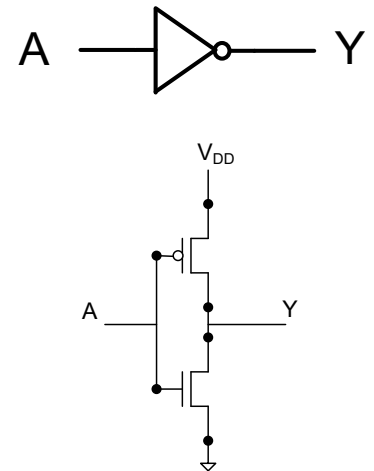


# Example (cont)

## *Inverter with improved model*

### *Inverter Model*

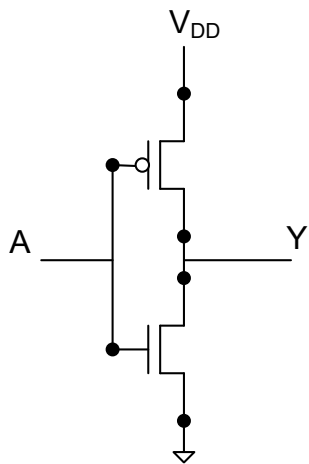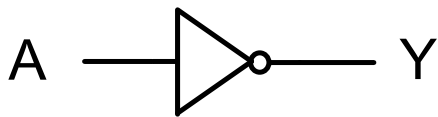



### **Inverter with Improved Model**

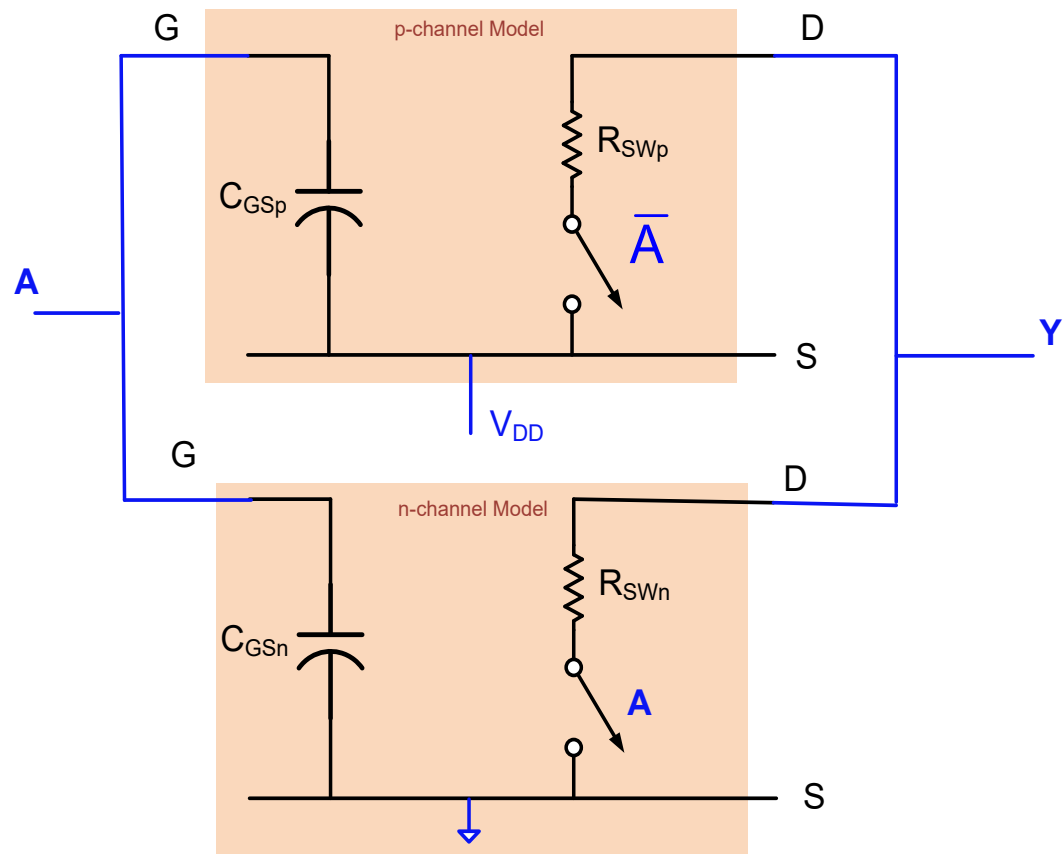




# Example (cont)

With improved model  $t_{HL}=?$

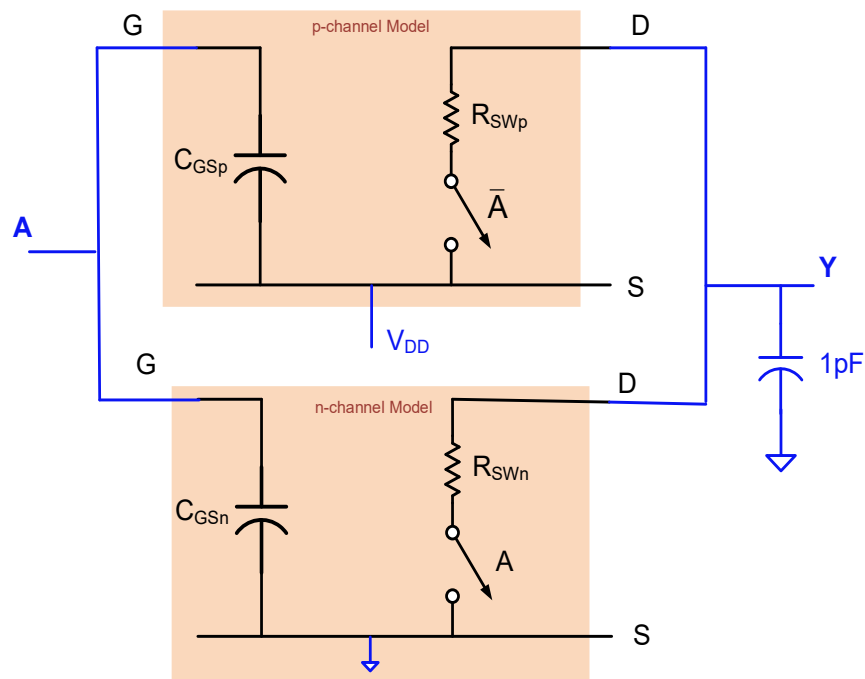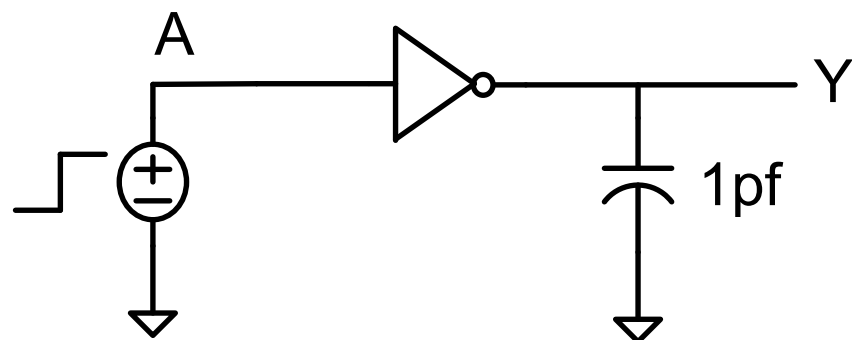

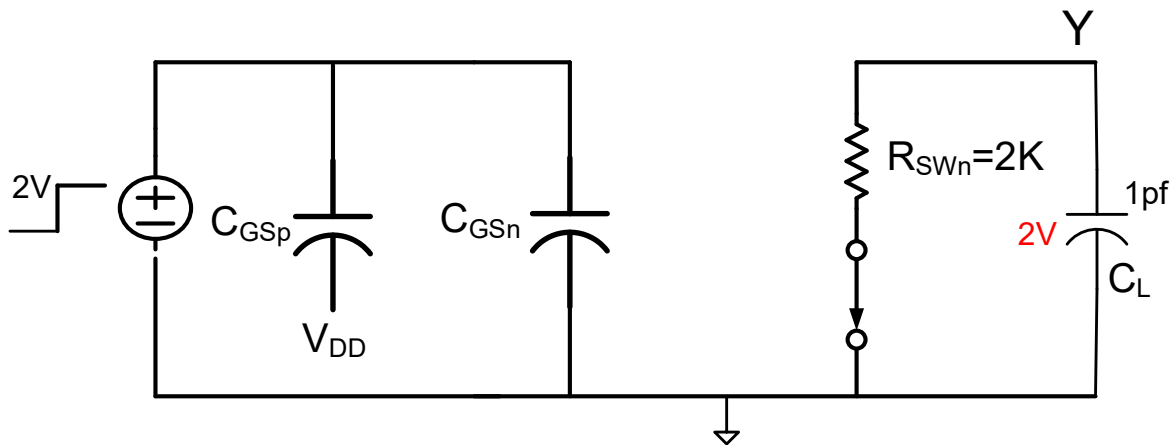To initiate a HL output transition, assume Y has been in the high state for a long time, lower switch closes at time  $t=0$ , and upper switch opens just prior to  $t=0$




2V is the initial condition on  $C_L$

## Example (cont)

*With improved model*

$$t_{HL}=?$$

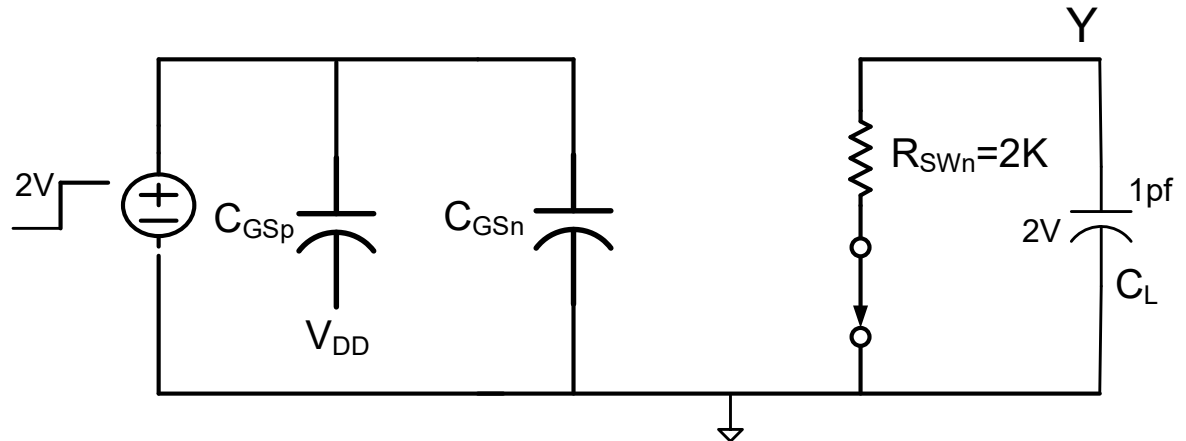

**Recognize circuit (specifically on right) as a first-order RC network**

**Recall: Step response of any first-order network with LHP pole can be written as**

$$y(t) = F + (I - F)e^{-\frac{t}{\tau}}$$


**where  $F$  is the final value,  $I$  is the initial value and  $\tau$  is the time constant of the circuit**

(from Chapter 7 of Nilsson and Riedel)

**For the circuit above,  $F=0$ ,  $I=2$  and  $\tau = R_{SWn} C_L$**

# Example (cont)

*With improved model*

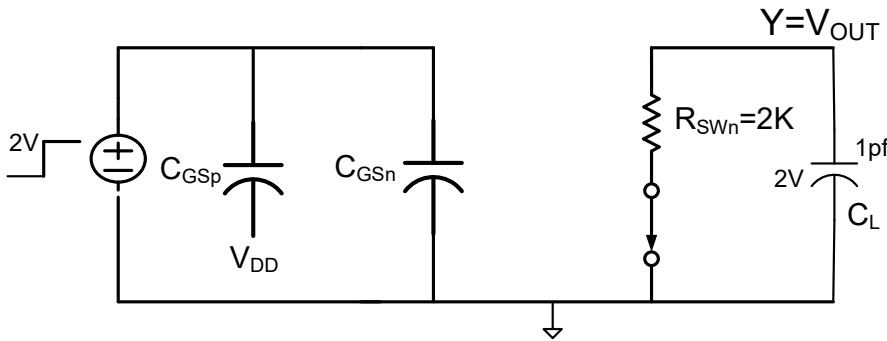


$$t_{HL}=?$$

$$V_{OUT}(t) = F + (I - F)e^{-\frac{t}{\tau}}$$

$$V_{OUT}(t) = 2e^{-\frac{t}{\tau}}$$


$$\tau = R_{SWn} C_L$$

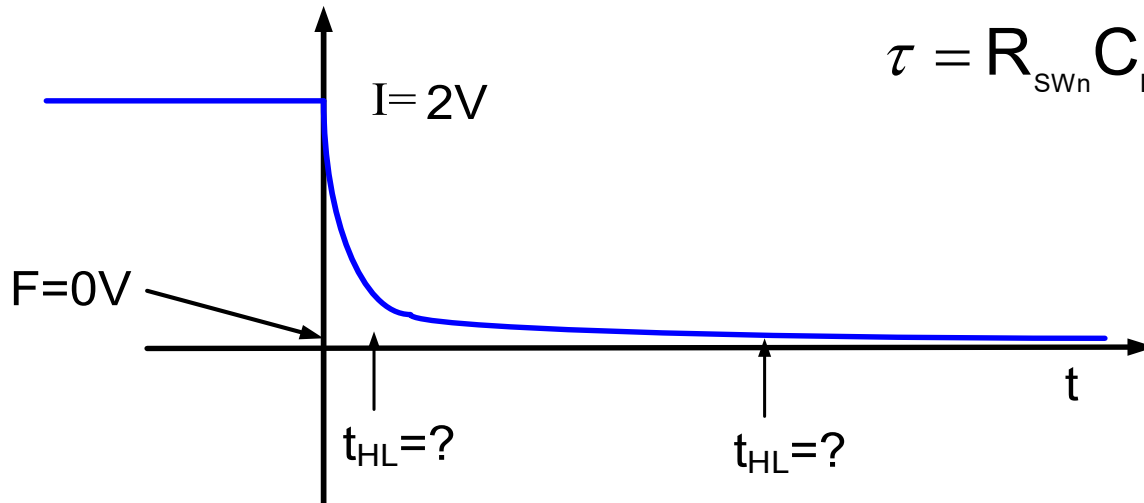

**how is  $t_{HL}$  defined?**

Example (cont)

$t_{HL}=?$

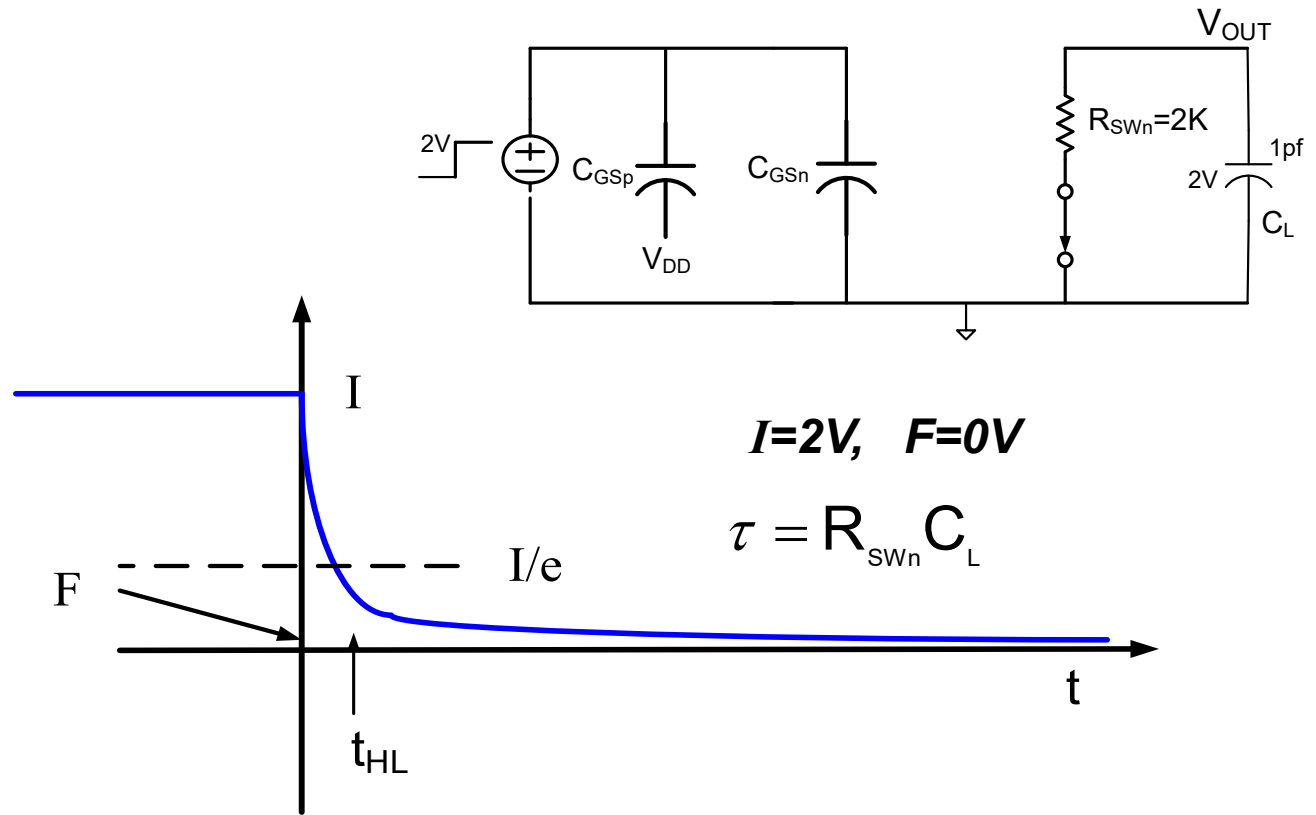

Define  $t_{HL}$  to be the time taken for output to drop to  $I/e$

$$V_{OUT}(t) = F + (I - F)e^{-\frac{t}{\tau}} \quad \longrightarrow \quad \frac{I}{e} = F + (I - F)e^{-\frac{t_{HL}}{\tau}}$$

Is this simply a mathematical definition or does it have some practical significance?

$t_{HL}$  as defined here and as verified by experimental verification has proven useful at analytically predicting response time of circuits

## Example (cont)

*With improved model*

$$\frac{I}{e} = F + (I - F)e^{-\frac{t_{HL}}{\tau}}$$


$$\frac{I}{e} = Ie^{-\frac{t_{HL}}{\tau}}$$

$$\frac{1}{e} = e^{-\frac{t_{HL}}{\tau}}$$

$$t_{HL} = \tau$$





$$t_{HL} = R_{SWn} C_L$$

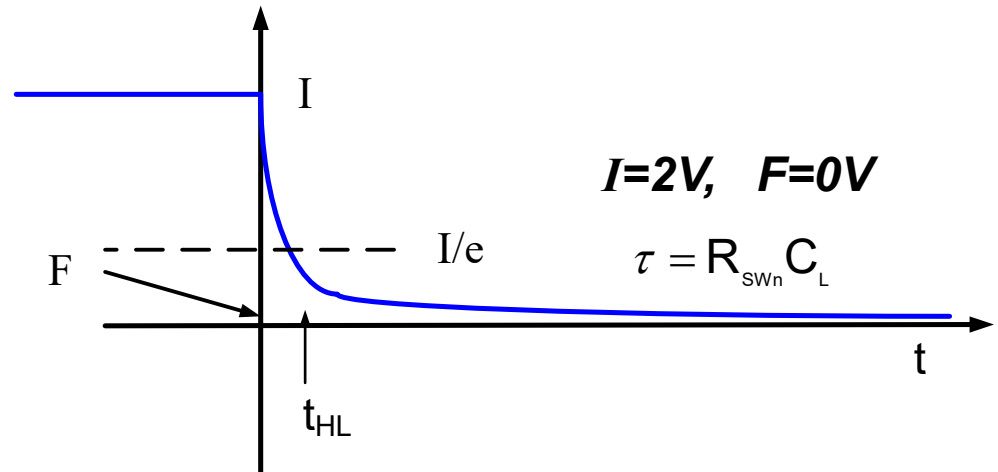


**Both experimental results and accurate computer simulations show that this reasonably accurately predicts how quickly following stages recognize that a logic transition has taken place !!**

# Example (cont)

With improved model  $t_{LH}=?$

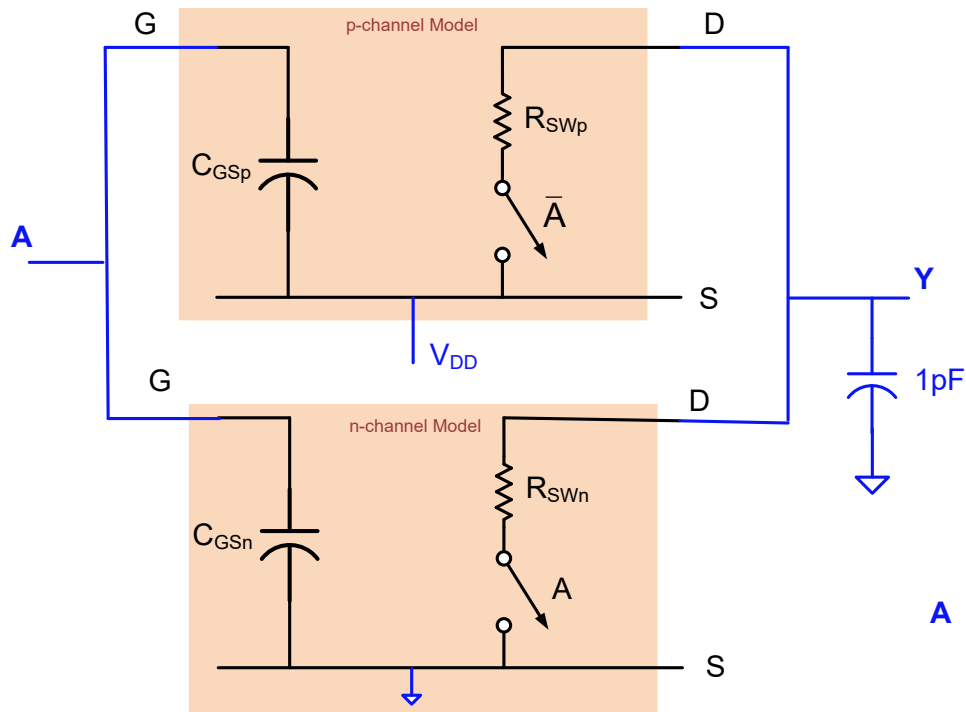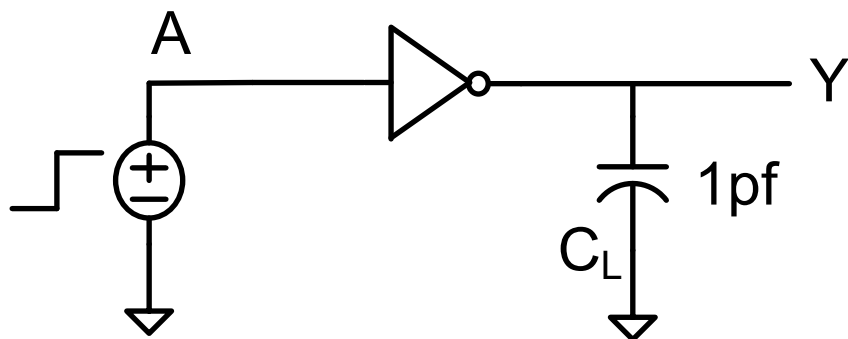

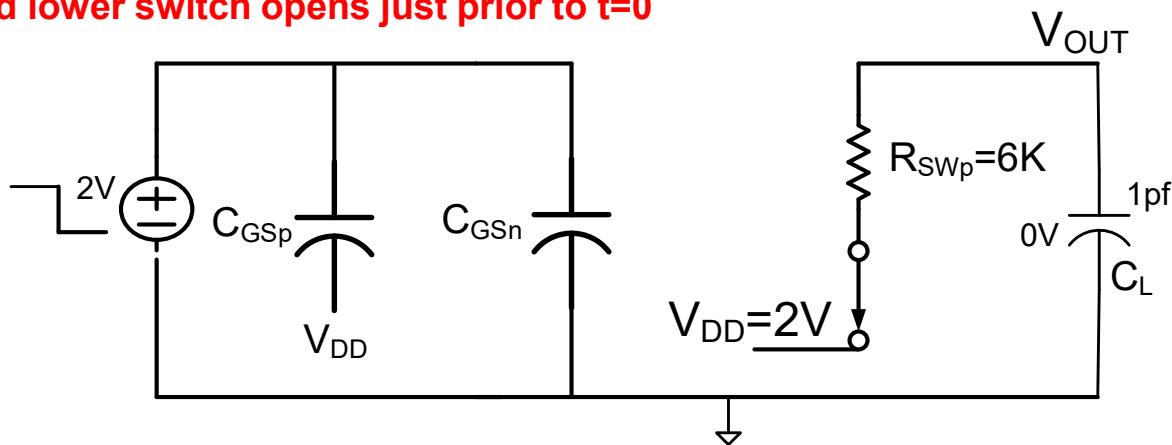
Assume output in low state for a long time and upper switch closes at time  $t=0$  and lower switch opens just prior to  $t=0$



0V is the initial condition on  $C_L$

## Example (cont)

With improved model  $t_{LH}=?$

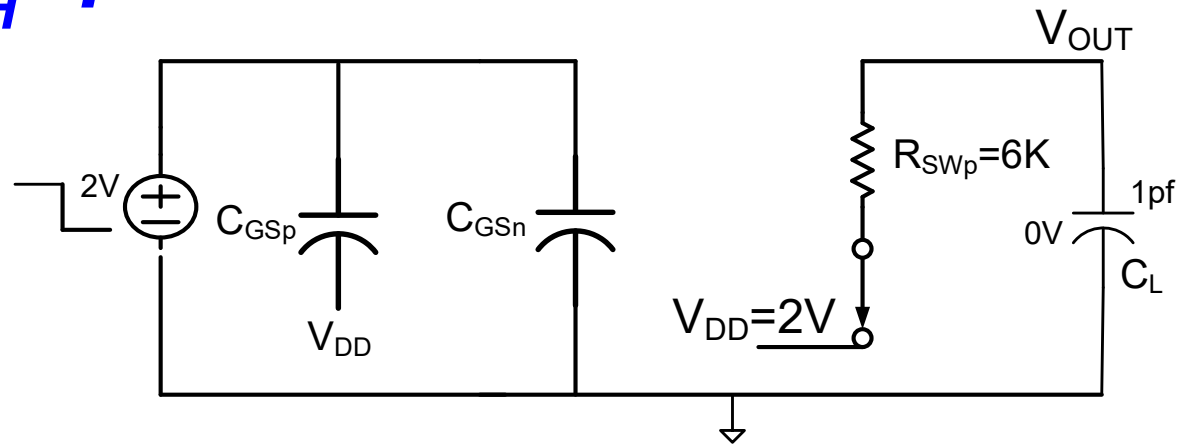


$$y(t) = F + (I - F)e^{-\frac{t}{\tau}}$$

For this circuit (specifically on the right),  $F=2$ ,  $I=0$  and  $\tau = R_{SWp} C_L$

# Example (cont)

*With improved model*

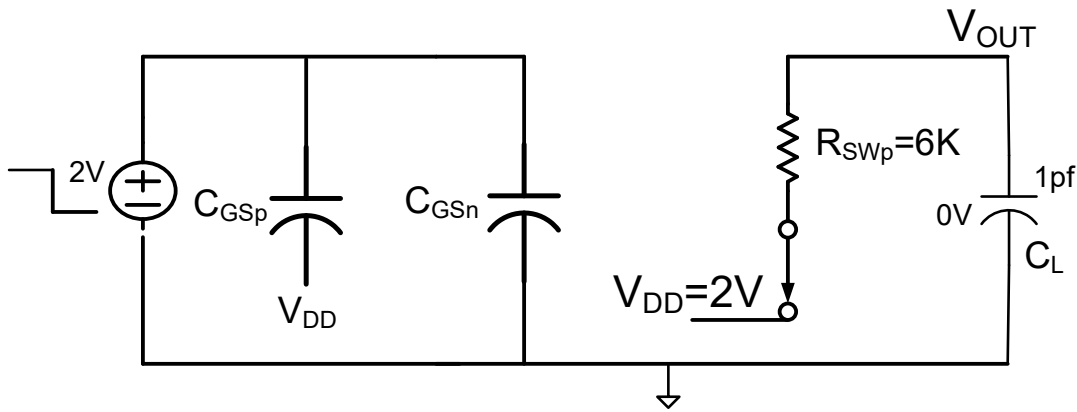


$t_{LH}=?$

$$V_{OUT}(t) = F + (I - F)e^{-\frac{t}{\tau}}$$

$$V_{OUT}(t) = 2\left(1 - e^{-\frac{t}{\tau}}\right)$$

$$\tau = R_{SWp} C_L$$

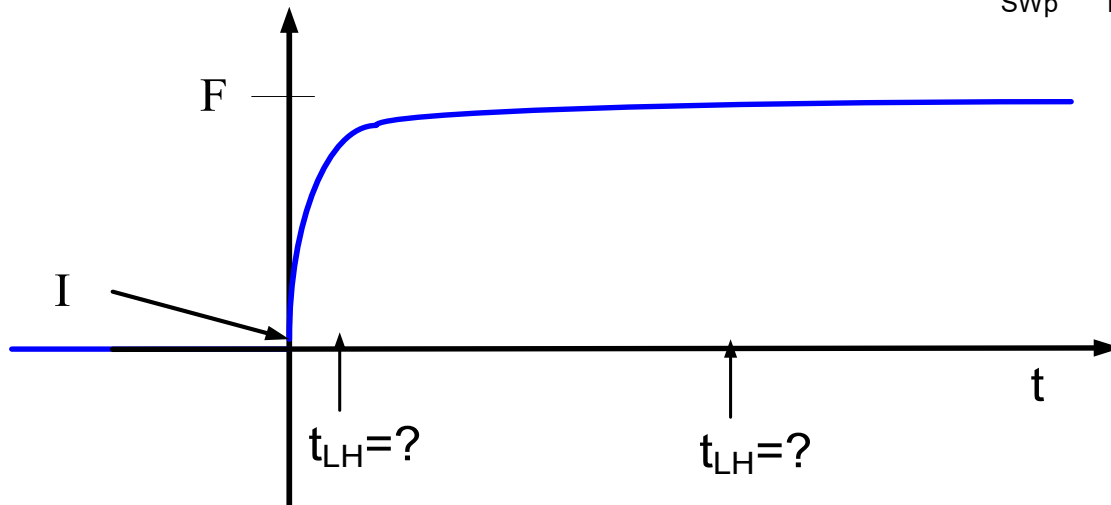

**how is  $t_{LH}$  defined?**





## Example (cont)

With improved model

$t_{LH}=?$

Define  $t_{LH}$  as shown on figure

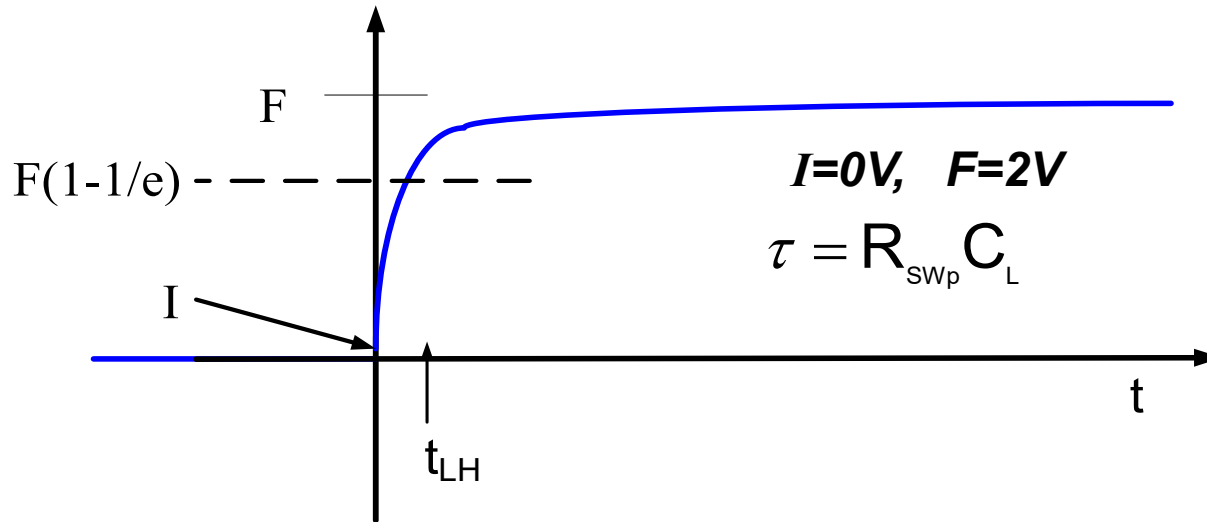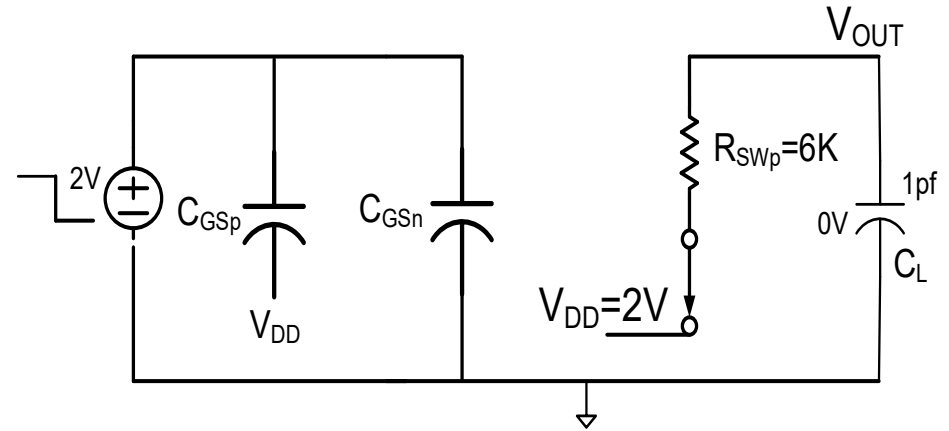

$t_{LH}$  as defined has proven useful for analytically predicting response time of circuits

$$V_{OUT}(t) = F + (I - F)e^{-\frac{t}{\tau}} \quad \longrightarrow \quad F\left(1 - \frac{1}{e}\right) = F + (I - F)e^{-\frac{t_{LH}}{\tau}}$$

## Example (cont)

With improved model

$$t_{LH}=?$$

$$F\left(1 - \frac{1}{e}\right) = F + (I - F)e^{-\frac{t_{LH}}{\tau}}$$


$$F\left(1 - \frac{1}{e}\right) = F + (F)e^{-\frac{t_{LH}}{\tau}}$$

$$1 - \frac{1}{e} = 1 + e^{-\frac{t_{LH}}{\tau}}$$

$$t_{LH} = \tau$$




$$t_{LH} = R_{SWp} C_L$$

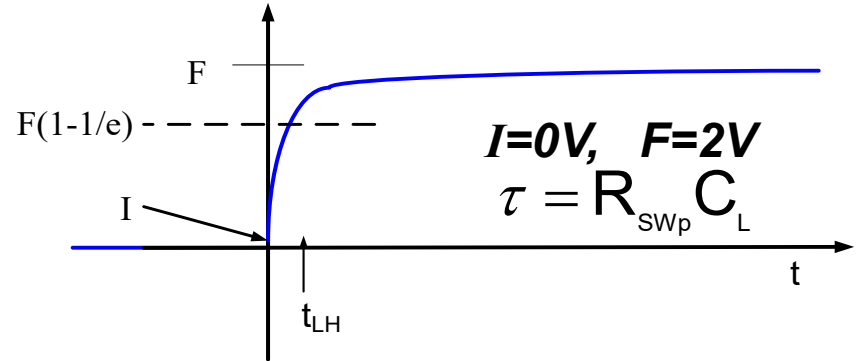

## Example (cont)

*With improved model*

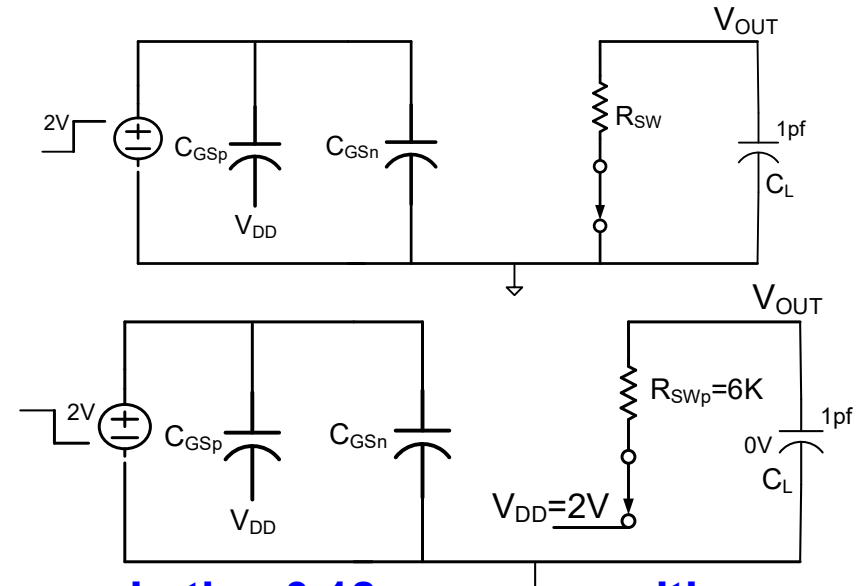

**In the 0.18u process with  
minimum-sized devices**

$$t_{HL} \cong R_{SWn} C_L = 2K \bullet 1pF = 2n \text{ sec}$$


$$t_{LH} \cong R_{SWp} C_L = 6K \bullet 1pF = 6n \text{ sec}$$

***Note this circuit is quite fast !***

***Note that  $t_{HL}$  is much shorter than  $t_{LH}$***

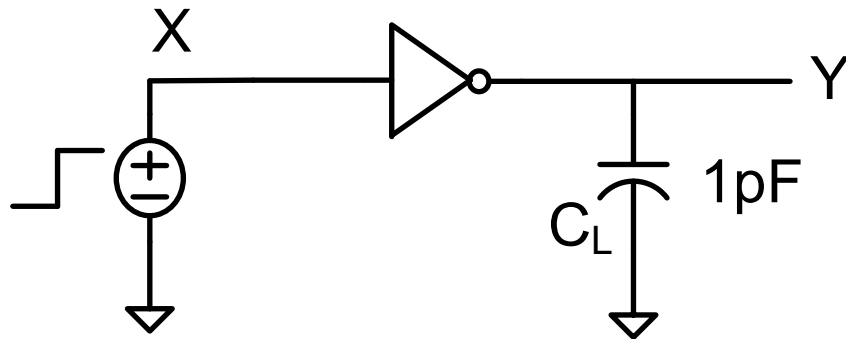***Often  $C_L$  will be even smaller and the circuit will be much faster !!***

Summary: What is the delay of a minimum-sized inverter driving a 1pF load?





In a 0.18μ process

$$t_{HL} \cong R_{SWn} C_L = 2K \bullet 1pF = 2n \text{ sec}$$

$$t_{LH} \cong R_{SWp} C_L = 6K \bullet 1pF = 6n \text{ sec}$$

# Improved switch-level model

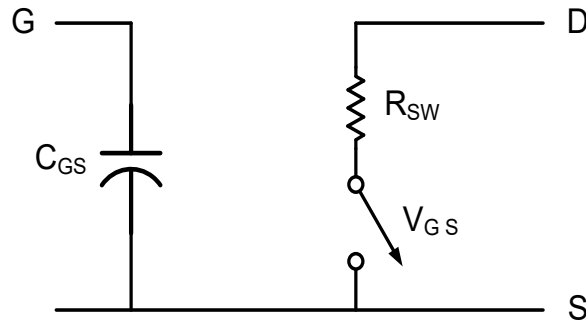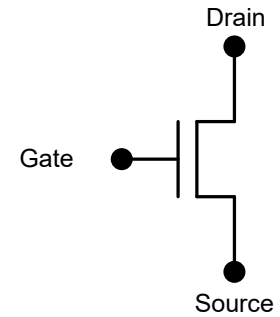

Switch closed for  $V_{GS} = \text{large}$


Switch open for  $V_{GS} = \text{small}$

- Previous example showed why  $R_{SW}$  in the model was important
- But of what use is the  $C_{GS}$  which did not enter the previous calculations?



For minimum-sized devices in a  $0.18\mu$  process

$$C_{GS} \cong 1.5\text{fF} \quad R_{sw} \cong \left. \begin{array}{l} 2\text{K}\Omega \text{ n-channel} \\ 6\text{K}\Omega \text{ p-channel} \end{array} \right\}$$

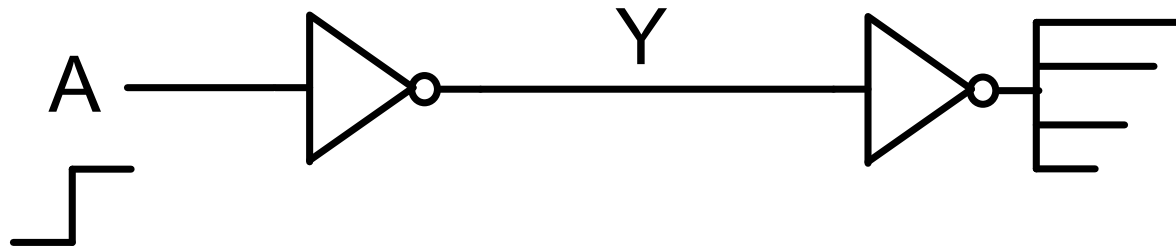
***One gate often drives one or more other gates !***



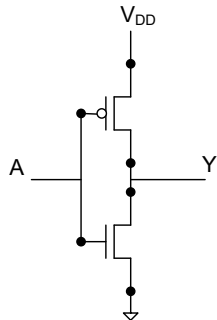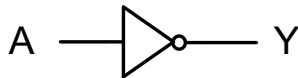***What are  $t_{HL}$  and  $t_{LH}$ ?***




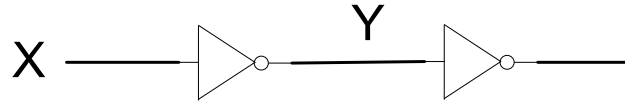Example: What is the delay of a minimum-sized inverter driving another identical device?




Load on first inverter

$C_{GSn}$  and  $C_{GSp}$  both 1.5fF

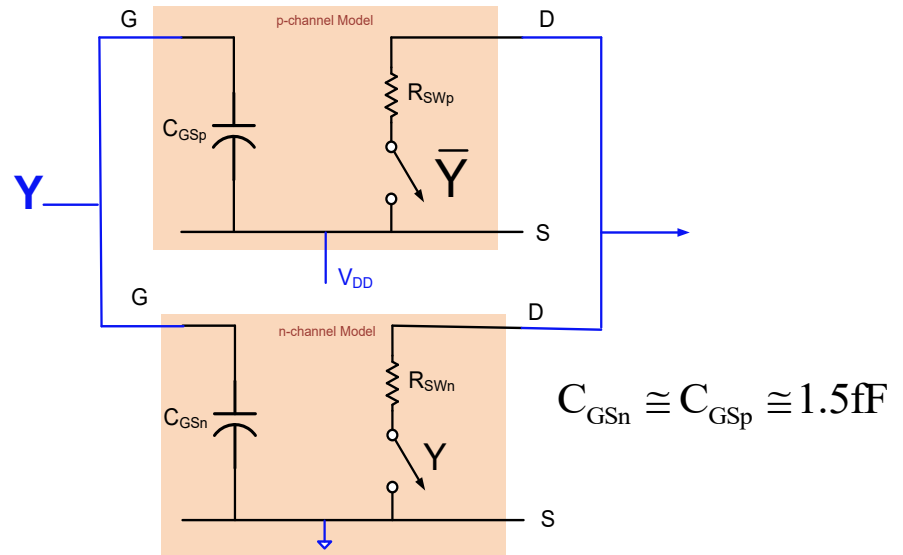


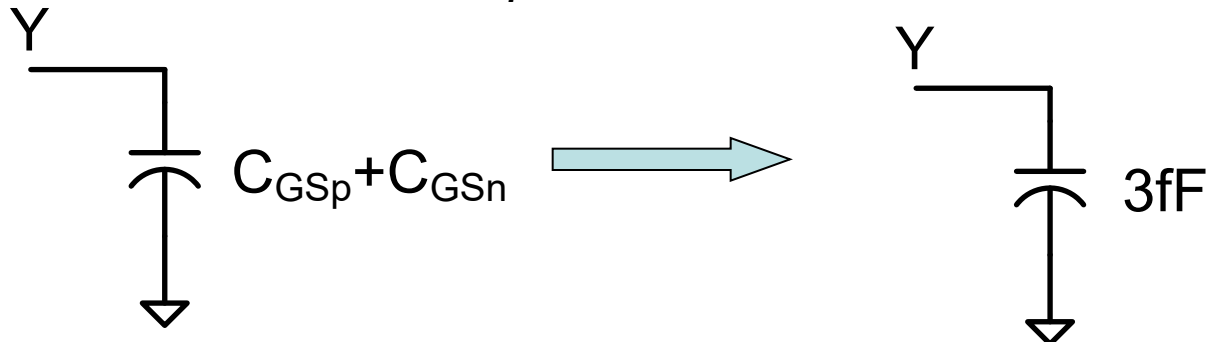Loading effects same whether  $C_{GSp}$  and/or  $C_{GSn}$  connected to  $V_{DD}$  or GND



For convenience, will reference both to ground
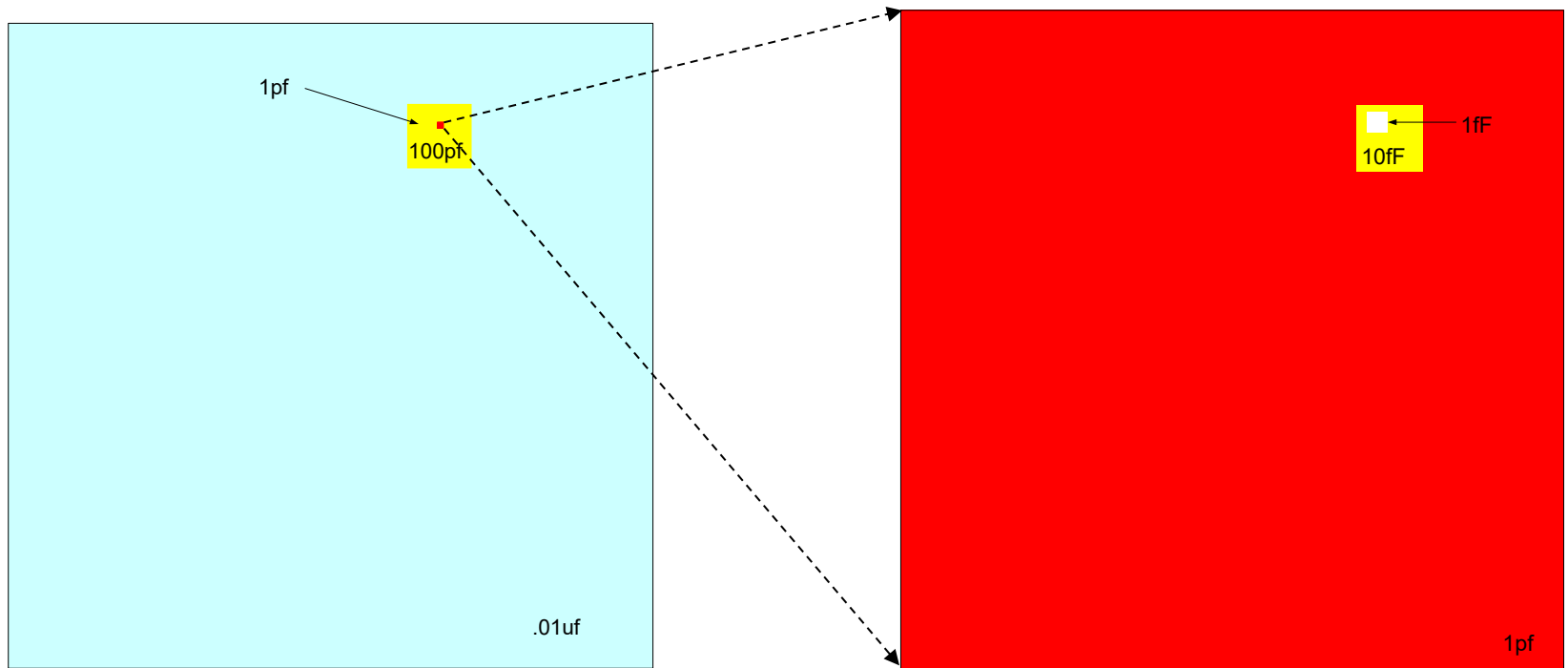
# Is a capacitor of 1.5fF small enough to be neglected?





**Area allocations shown to relative scale:**


- This example will provide insight into the answer of the question



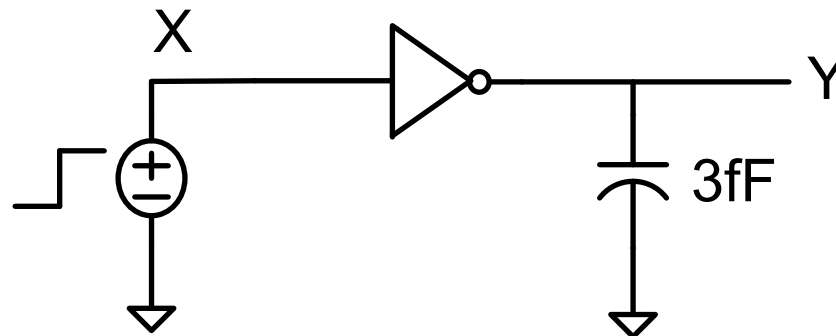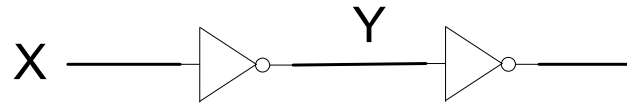Example: What is the delay of a minimum-sized inverter driving another identical device? Assume  $V_{DD}=2V$




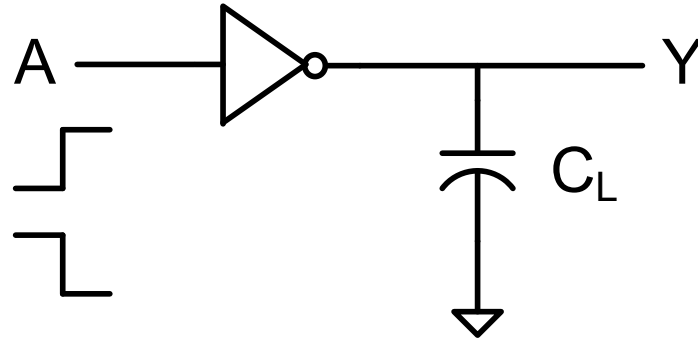
# Generalizing the Previous Analysis to Arbitrary Load



$$t_{HL} \cong R_{SWn} C_L$$

$$t_{LH} \cong R_{SWp} C_L$$

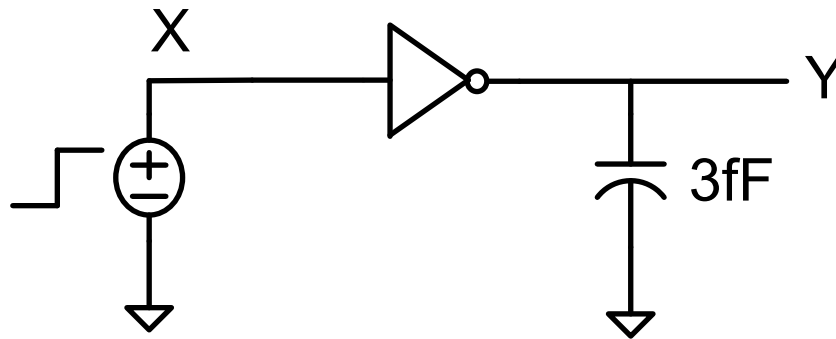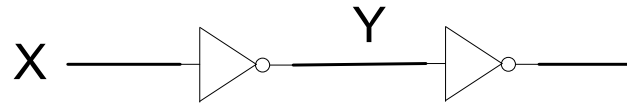Example: What is the delay of a minimum-sized inverter driving another identical device?




$$t_{\text{HL}} \cong R_{\text{SWn}} C_{\text{L}} = 2\text{K} \bullet 3\text{fF} = 6\text{p sec}$$

$$t_{\text{LH}} \cong R_{\text{SWp}} C_{\text{L}} = 6\text{K} \bullet 3\text{fF} = 18\text{p sec}$$

Do gates really operate this fast?

What would be the maximum clock rate for acceptable operation?

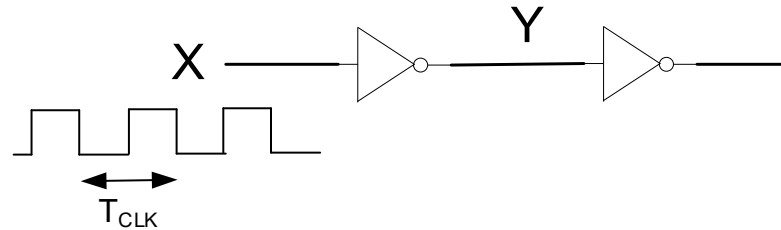Example: What is the delay of a minimum-sized inverter driving another identical device?



$$t_{HL} \cong R_{SWn} C_L = 6 p \text{ sec}$$

$$t_{LH} \cong R_{SWp} C_L = 18 p \text{ sec}$$

What would be the maximum clock rate for acceptable operation?

$$T_{CLK\text{-min}} = t_{HL} + t_{LH}$$



$$f_{CLK\text{-max}} = \frac{1}{T_{CLK\text{-min}}} = \frac{1}{24 \text{ psec}} = 40 \text{ GHz}$$

And much faster in a finer feature process !!

??????

What would be the implications of allowing for 10 levels of logic and 10 loads (FanOut=10)?

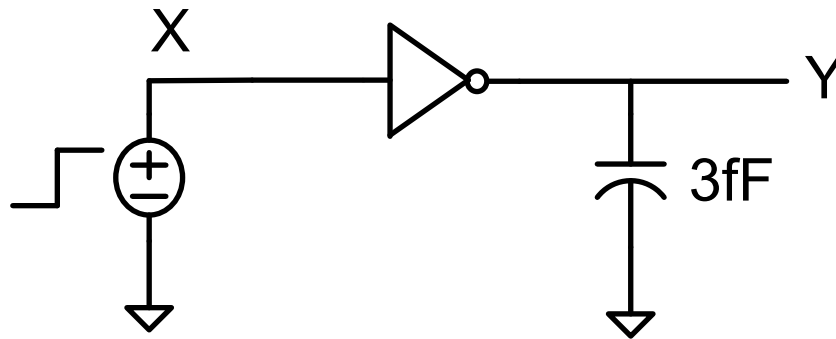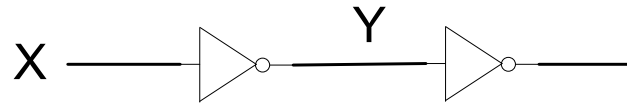Example: What is the delay of a minimum-sized inverter driving another identical device? SUMMARY




$$t_{HL} \cong R_{SWn} C_L = 2K \bullet 3fF = 6p \text{ sec}$$

$$t_{LH} \cong R_{SWp} C_L = 6K \bullet 3fF = 18p \text{ sec}$$

*This is very fast but even the small 1.5fF capacitors are not negligible !  
These capacitors play a key role in determining the speed of a circuit !*

## Response time of logic gates

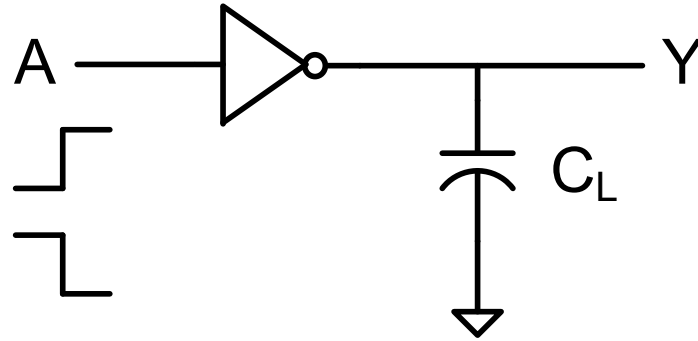

$$t_{HL} \cong R_{SWn} C_L$$

$$t_{LH} \cong R_{SWp} C_L$$


- Logic Circuits can operate very fast
- Extremely small parasitic capacitances play key role in speed of a circuit

# Some Observations about Technology and Politics

Are the larger feature size technologies still used by industry today in the US or abroad?

GlobalData predicts that the Chinese market will play a much smaller role for foreign suppliers by 2030. More than 90% of the chips sold and used worldwide involve low-process production technology.
 
<https://www.investmentmonitor.ai/analysis/china-lead-global-semiconductor-growth-2030#:~:text=Global%20semiconductor%20industry%20revolves%20around,Samsung%20Electronics%20and%20SK%20Hynix.>



Source: SEMI

# Some Observations about Technology and Politics

Sept 2022

<https://technode.com/2021/03/04/where-china-is-investing-in-semiconductors-in-charts/>

China is the world's largest consumer of semiconductors, and the lion's share of revenue from purchasing these chips go to foreign firms. China consumed \$143.4 billion worth of wafers in 2020, and just 5.9% of them were produced by companies headquartered in China.




# The Chips Act of 2022

\$52 billion grant over five years to help grow the domestic semiconductor manufacturing. \$2 billion of which is to explicitly focus on legacy chip production. These chips are essential to the auto industry, the military, and other industries critical to our national security interests.

**By the numbers:** The CHIPS Act directs \$280 billion in spending over the next ten years. The majority—\$200 billion—is for scientific R&D and commercialization. Some \$52.7 billion is for semiconductor manufacturing, R&D, and workforce development, with another \$24 billion worth of tax credits for chip production. There is \$3 billion slated for programs aimed at leading-edge technology and wireless supply chains.

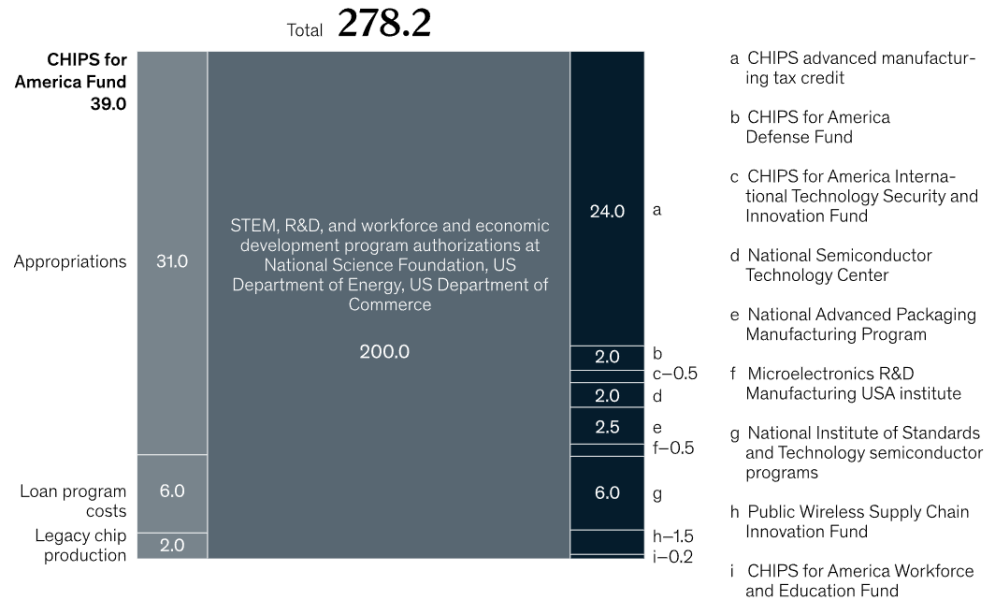**The CHIPS and Science Act of 2022 directs \$280 billion in spending over the next ten years, with the bulk for scientific R&D.**

CHIPS and Science Act funding for 2022–26, \$ billion




Source: Creating Helpful Incentives to Produce Semiconductors (CHIPS) and Science Act of 2022, H.R. 4346, 117th Cong. (2022)

# How do I get CHIPS Act Funding?

Breaking News: The application for wafer manufacturers and suppliers of materials and equipment (e.g., chemicals and tools) was just released. Read the details [here](#).

\$53 billion is available for semiconductor manufacturing and R&D, plus a 25% refundable tax credit for qualified CapEx. See below to discover where your business fits in

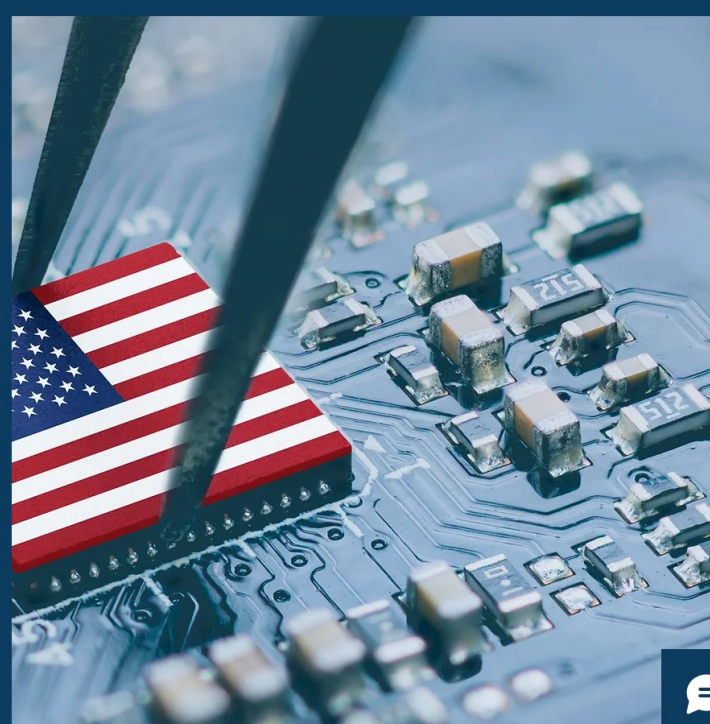Need help? Book an appointment with our professional grant writing team [here](#) or email us: [equity@chipsact.com](mailto:equity@chipsact.com)





# STATE OF THE U.S. SEMICONDUCTOR INDUSTRY

# 20 23



**Stay Safe and Stay Healthy !**

**End of Lecture 7**