

# EE 434


## Lecture 6

Logic Circuits  
Process Technology
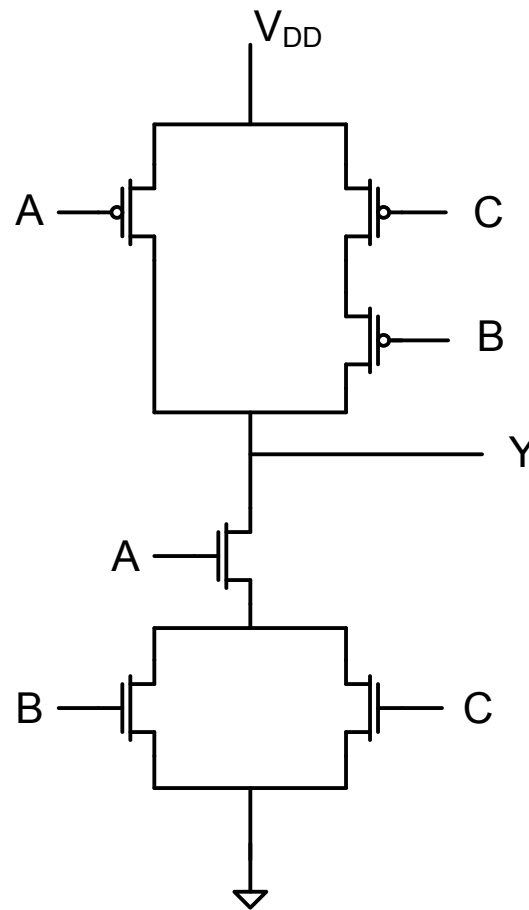
## Quiz 4

A proposed three-input Boolean Gate is shown

- Determine the Boolean output  $Y$
- Is the static power dissipation of this gate zero?  
(use the switch-level model of the MOSFET)



And the number is ....

1            8            7            5            3  
6            9            4            2

**4**

## Quiz 4

A proposed three-input Boolean Gate is shown

- Determine the Boolean output  $Y$
- Is the static power dissipation of this gate zero?  
(use the switch-level model of the MOSFET)

Solution:


- a) From PDN observe

$$Y = \overline{A \cdot (B + C)}$$

In standard Sum of Products form

$$Y = \overline{A} + \overline{B} \cdot \overline{C}$$



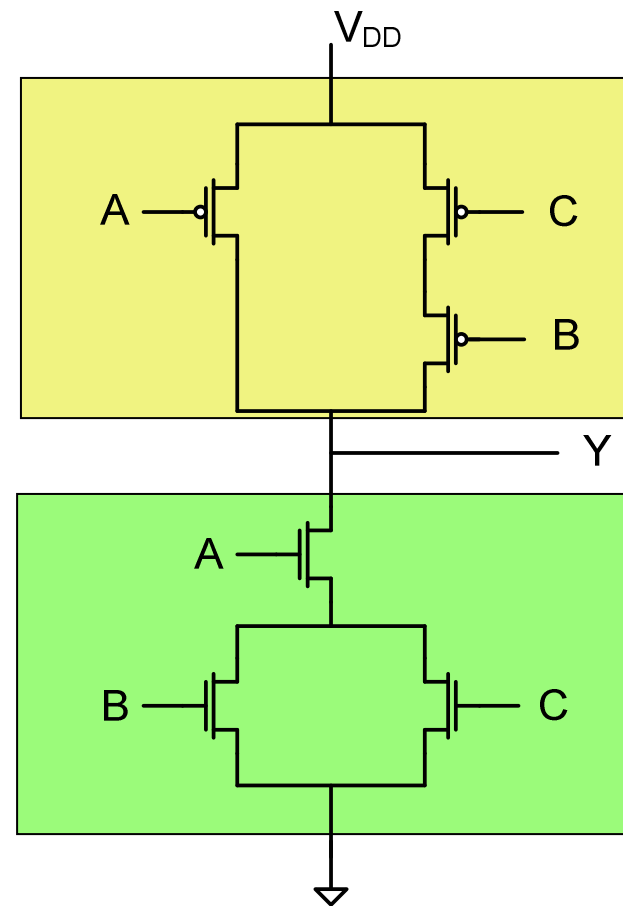
- b) Yes – note PU and PD networks are never both conducting






## Review from Last Time

- Different Logic Design Styles Can Be Used
  - PTL is one style that can offer significant reductions in complexity
  - Signal Degradation and Static Power Dissipation are issues of concern when using PTL
  - Designer is under complete control of circuits that are placed on the silicon
  - Many designs will mix multiple logic design styles
  - New logic design styles are still being proposed and adopted


# Improved Switch-Level Model

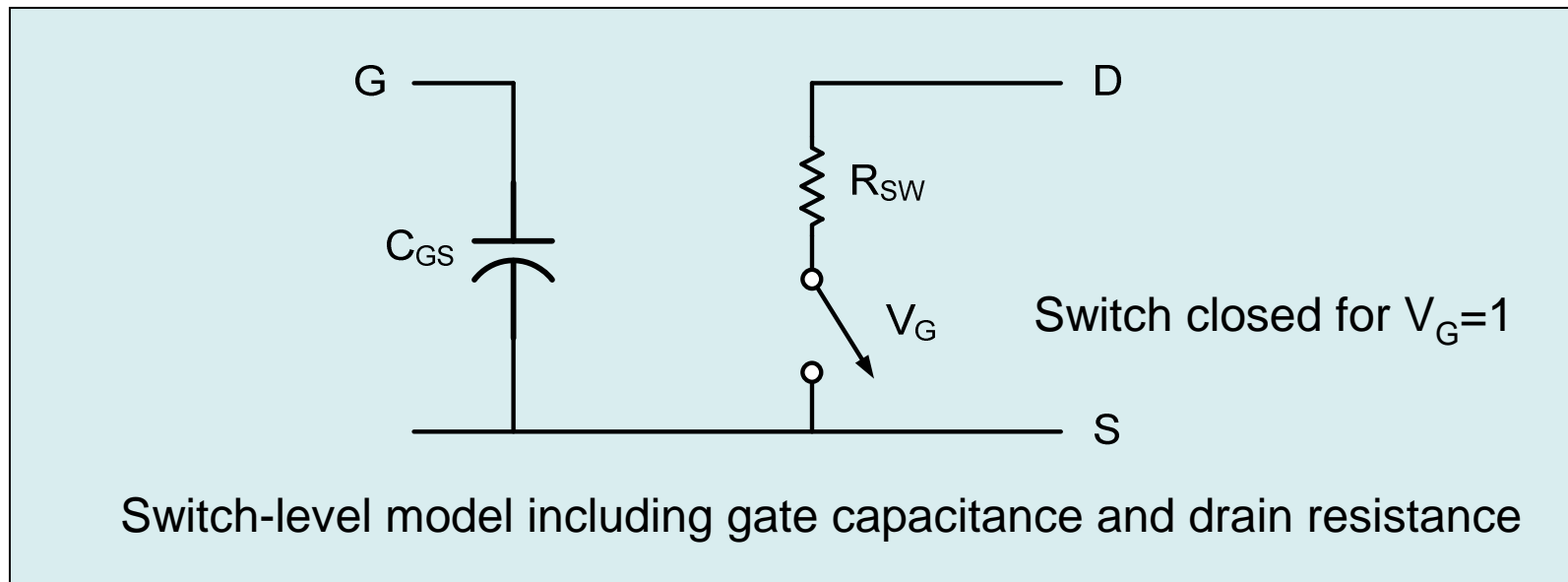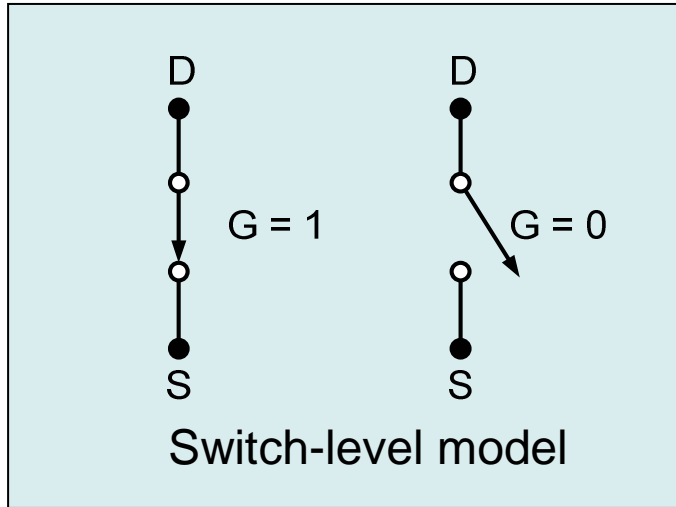 

# Improved Switch-Level Model

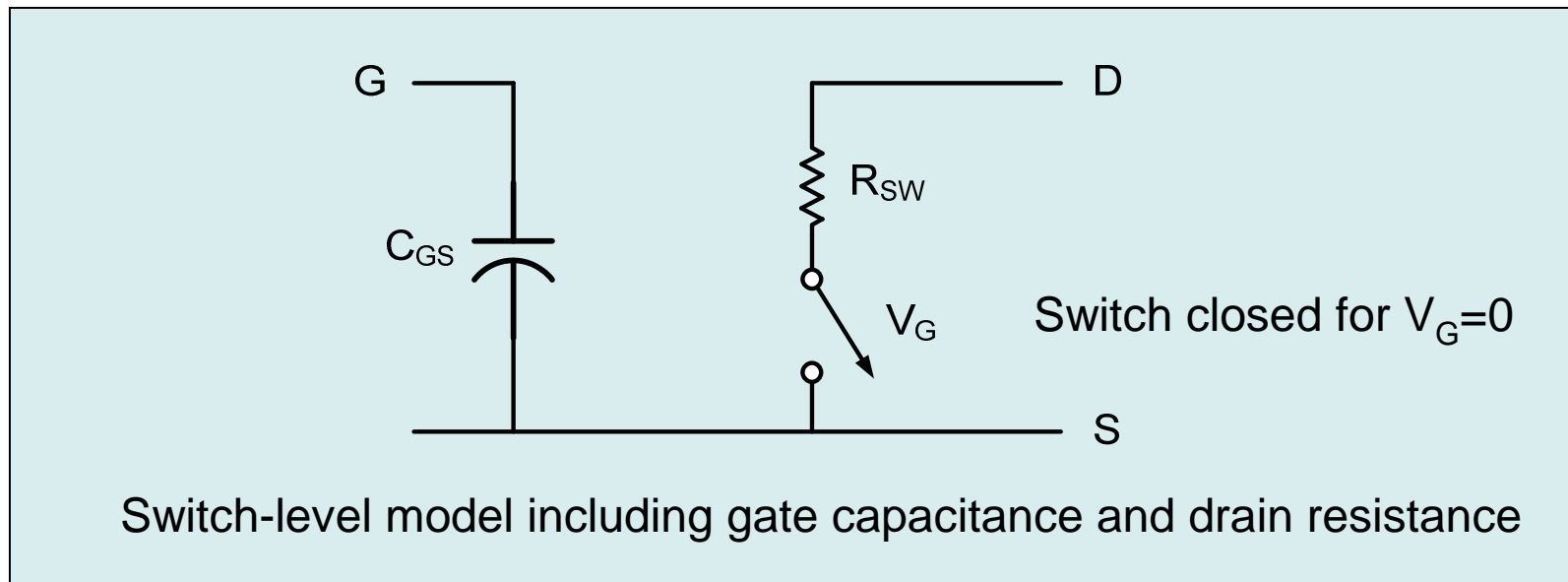  

# Improved Switch-Level Model

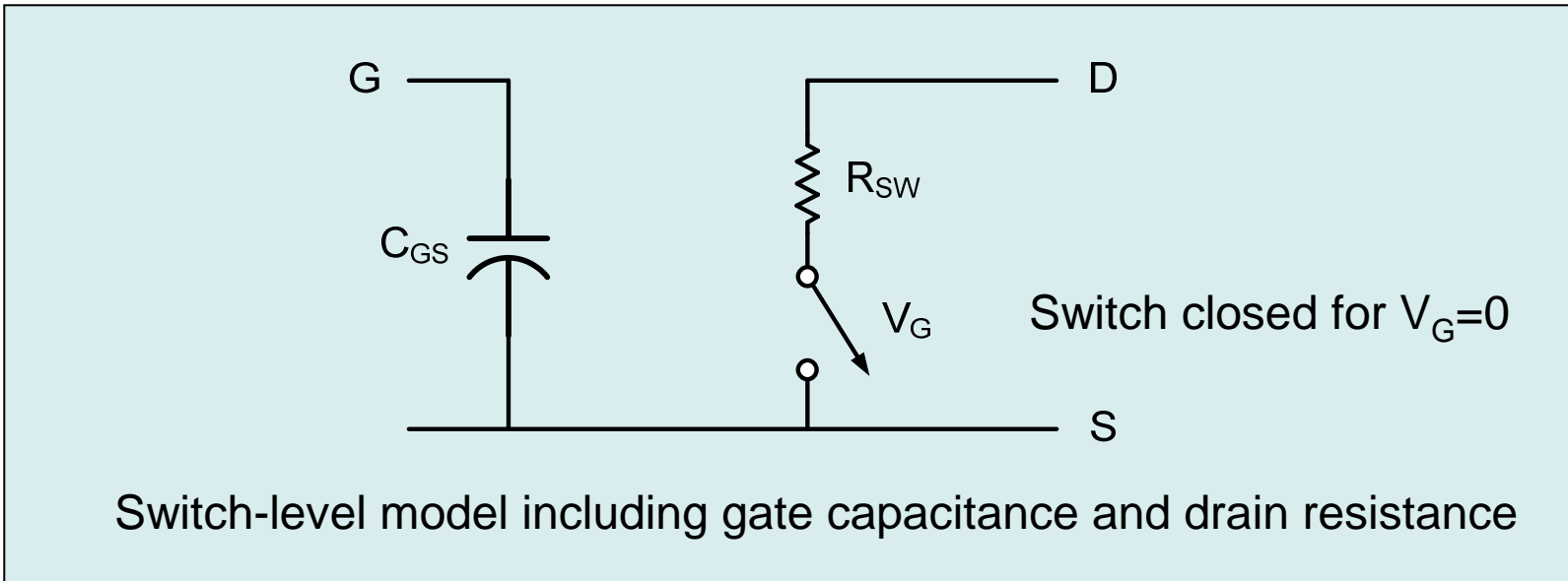

$C_{GS}$  and  $R_{SW}$  dependent upon device sizes and process


For minimum-sized devices in a 0.5u process

$$\mathbf{C_{GS} \cong 1.5fF} \quad \mathbf{R_{sw} \cong \left. \begin{array}{l} 2K\Omega \text{ n-channel} \\ 6K\Omega \text{ p-channel} \end{array} \right\}}$$


Considerable emphasis will be placed upon device sizing to manage  $C_{GS}$  and  $R_{SW}$




# Example

 


With switch level model

 

## Example (cont)


 


With improved model

 


# Example (cont)

With improved model

  

## Example (cont)

With improved model

 

Recognize as a first-order RC network

Recall: Step response of any first-order network with LHP pole can be written as


$$y(t) = F + (I - F)e^{-\frac{t}{\tau}}$$

where  $F$  is the final value,  $I$  is the initial value and  $\tau$  is the time constant of the circuit

For the circuit above,  $F=0$ ,  $I=5$  and  $\tau = R_{SW}C_L$

## Example (cont)

With improved model

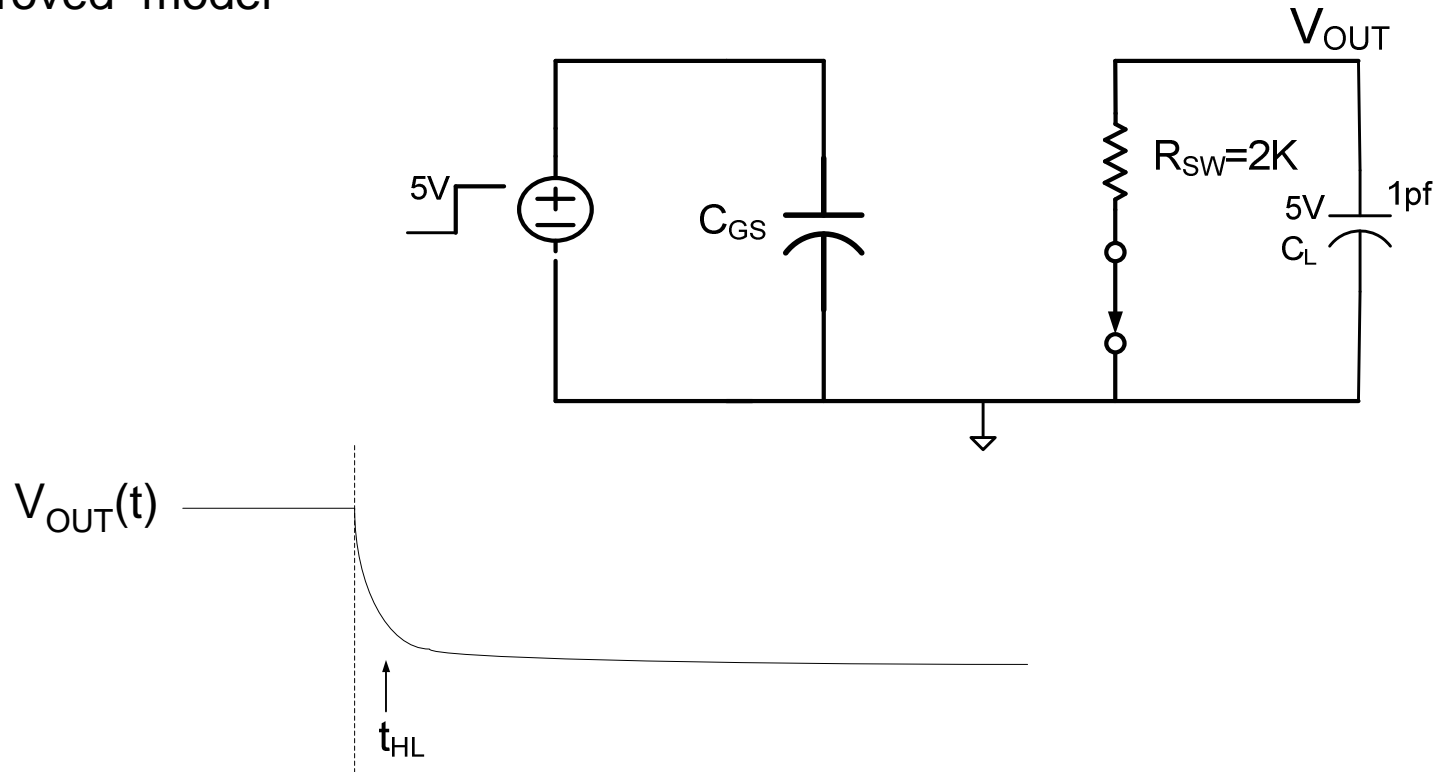


$$t_{HL} \cong R_{SW} C_L = 2K \cdot 1pF = .5E-9 \text{ sec} = .5n \text{ sec}$$

# Stick Diagrams



- It is often necessary to obtain information about placement, interconnect and physical-layer structure
- Stick diagrams are often used for small component-count blocks
- Approximate placement, routing, and area information can be obtained rather quickly with the use of stick diagrams

# Stick Diagrams

 

Additional layers can be added and color conventions are personal

# Stick Diagram

  




A stick diagram is not a layout but gives the basic structure that will be instantiated in the actual layout itself

Modifications can be made much more quickly on a stick diagram than on a layout

Iteration may be needed to come up with a good layout structure



# Stick Diagram

 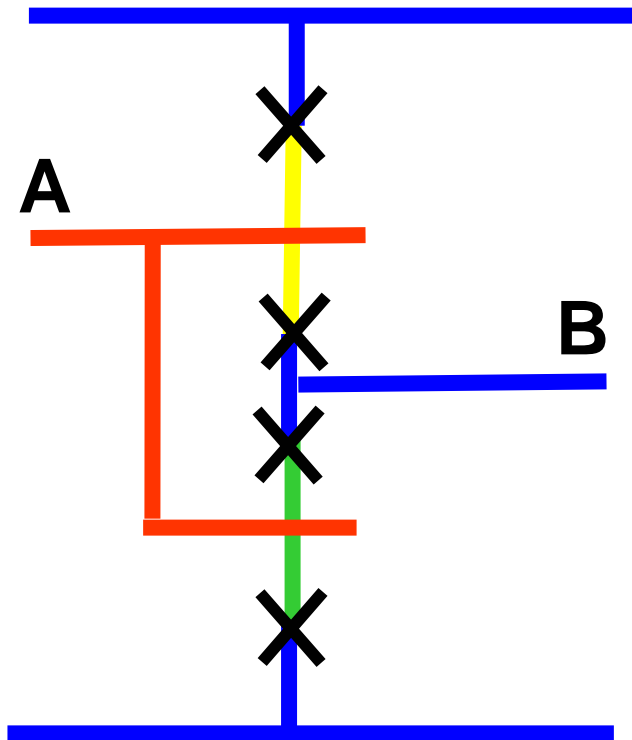 

Alternate Representation