

where, U_1, U_2, U_3 will be chosen as the independent variables

\therefore Modeling problem reduces to finding

f_1, f_2, f_3 such that

$$I_1 = f_1 (U_1, U_2, U_3)$$

$$I_2 = f_2 (U_1, U_2, U_3)$$

$$I_3 = f_3 (U_1, U_2, U_3)$$

$$\binom{6}{3} = \frac{6!}{3!3!} = \frac{6 \cdot 5 \cdot 4}{6} = 20$$

Note: 20.4 = 80 different but equivalent models can be obtained for any 4-terminal device.

$$I_1 = f_1(v_1, v_2, v_3)$$


$$I_2 = f_2(v_1, v_2, v_3)$$

$$I_3 = f_3(v_1, v_2, v_3)$$


Strategy: - Develop multiple models that are useful for classes of applications

- Use as simple of a model as we can get away with

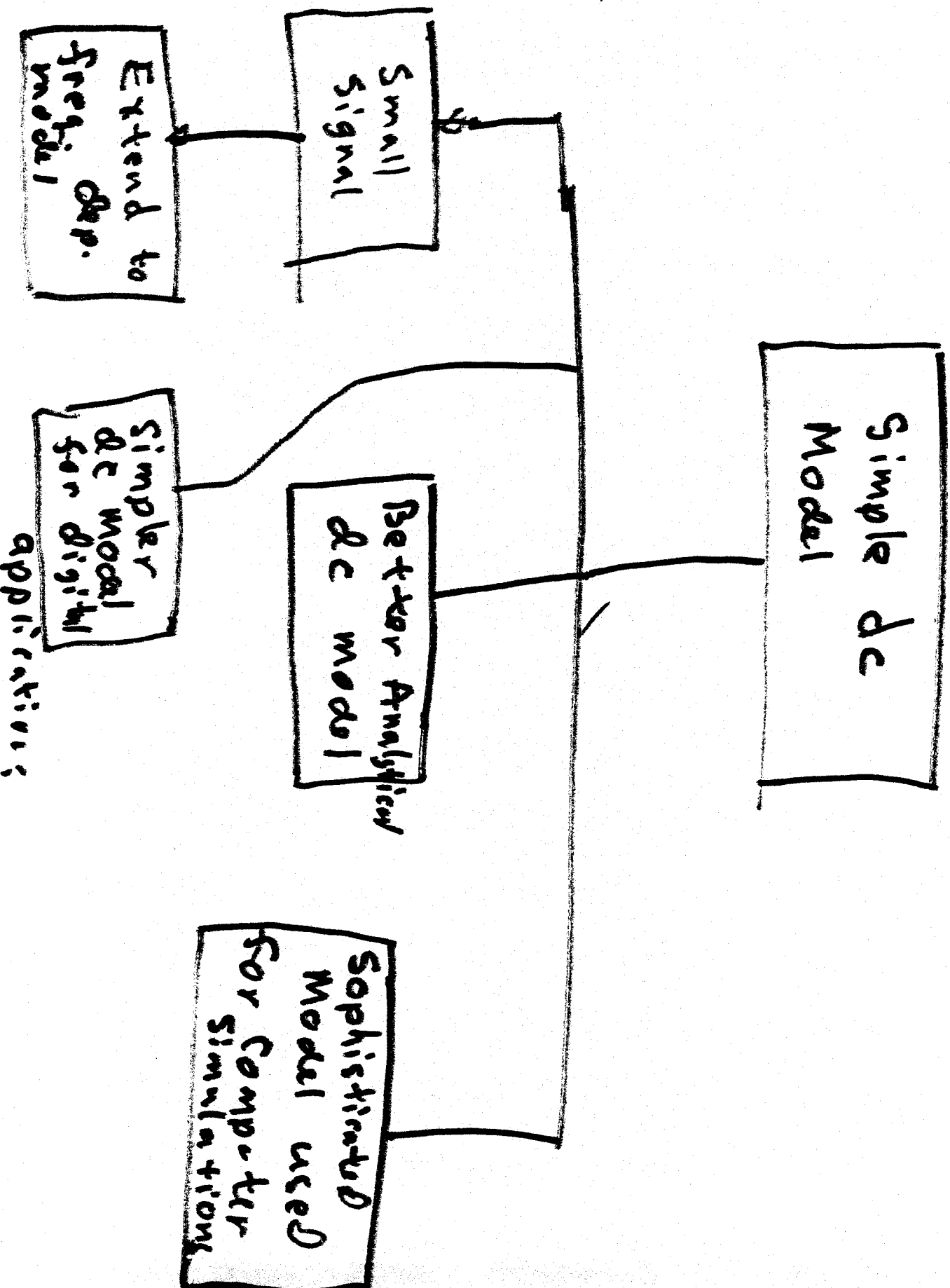- Often must consider a modestly more complicated model to justify a given model.



Small Signal Models

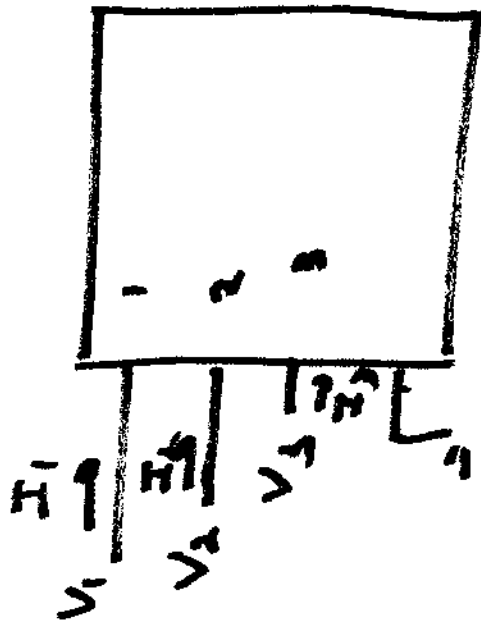

$$I_1 = f_1(v_1, v_2, v_3)$$

$$I_2 = f_2(v_1, v_2, v_3)$$

$$I_3 = f_3(v_1, v_2, v_3)$$

Develop the small signal model at the operating

point (V_{1Q}, V_{2Q}, V_{3Q}) : $\vec{V}_Q =$

$$\begin{bmatrix} V_{1Q} \\ V_{2Q} \\ V_{3Q} \end{bmatrix}$$

$$V = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

$$I = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

5.
Similar exp for $I_2(\vec{v})$ & $I_3(\vec{v})$

$$I_i(\vec{v}) = I_i(\vec{v}_q) + \sum_{k=1}^3 \frac{\partial I_i}{\partial v_k} \Big|_{\vec{v}_q} (v_k - v_{kq}) + \text{H.O.T.}$$

define the small signal quantities by

$$v_1 = v_1 - v_{1q}$$

$$v_2 = v_2 - v_{2q}$$

$$v_3 = v_3 - v_{3q}$$

$$\dot{\lambda}_1 = I_1(\vec{v}) - I_1(\vec{v}_q)$$

$$\dot{\lambda}_2 = I_2(\vec{v}) - I_2(\vec{v}_q)$$

$$\dot{\lambda}_3 = I_3(\vec{v}) - I_3(\vec{v}_q)$$

$$y_{\lambda_i} = \frac{\partial I_i}{\partial v_k} \Big|_{\vec{v}_q}$$

$$\begin{aligned} \dot{v}_1 &= y_{11}v_1 + y_{12}v_2 + y_{13}v_3 \\ \dot{v}_2 &= y_{21}v_1 + y_{22}v_2 + y_{23}v_3 \\ \dot{v}_3 &= y_{31}v_1 + y_{32}v_2 + y_{33}v_3 \end{aligned}$$

Then the model characterized by

$$Y = \begin{bmatrix} y_{11} & y_{12} & y_{13} \\ y_{21} & y_{22} & y_{23} \\ y_{31} & y_{32} & y_{33} \end{bmatrix}$$

the small signal model of the device.

Y =




$$\begin{bmatrix} y_{11} & y_{12} & y_{13} \\ y_{21} & y_{22} & y_{23} \\ y_{31} & y_{32} & y_{33} \end{bmatrix}$$

9 small signal parameters for a 4-term device

4 Small signal parameters for a 3-term device


1 Small signal parameter for a 2-term device

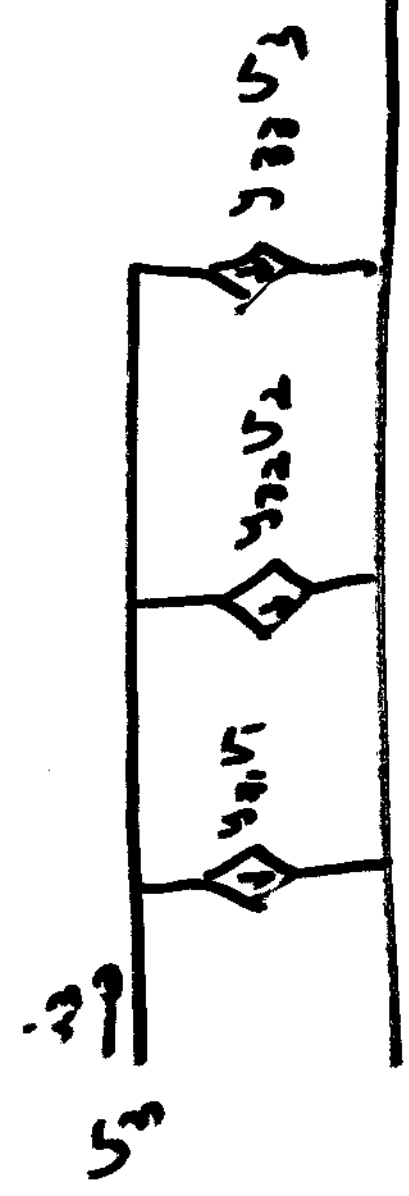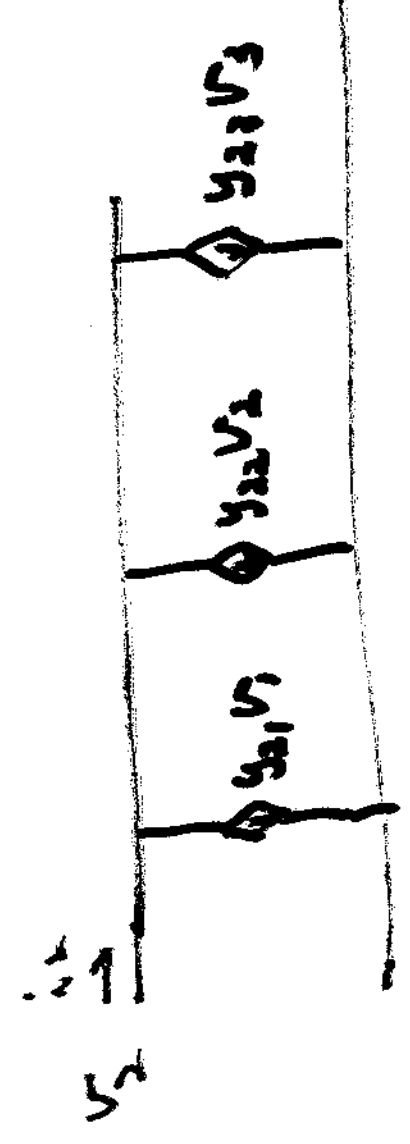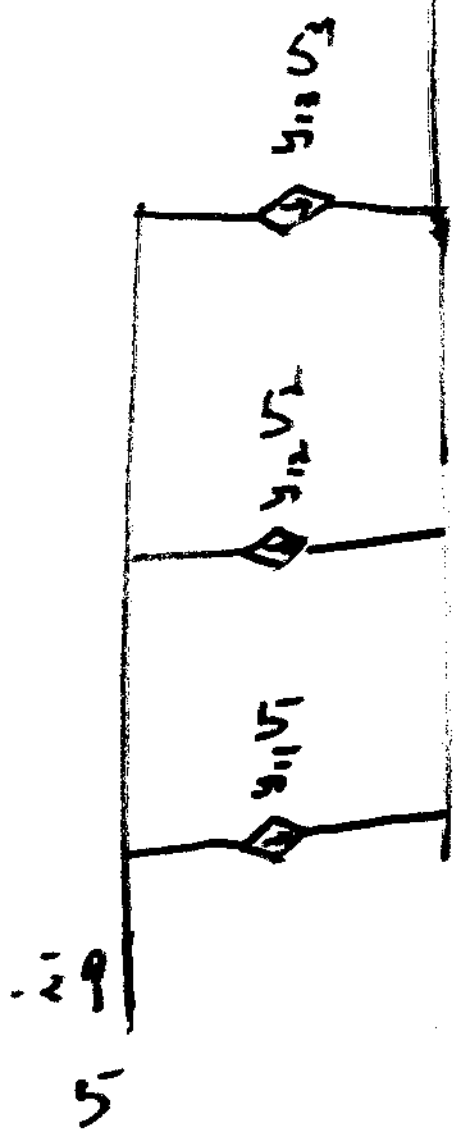Small signal
 ≡ equiv. ckt
 for H-term
 device



9.

Alternate
Eq. Ckt
for
n-term
device

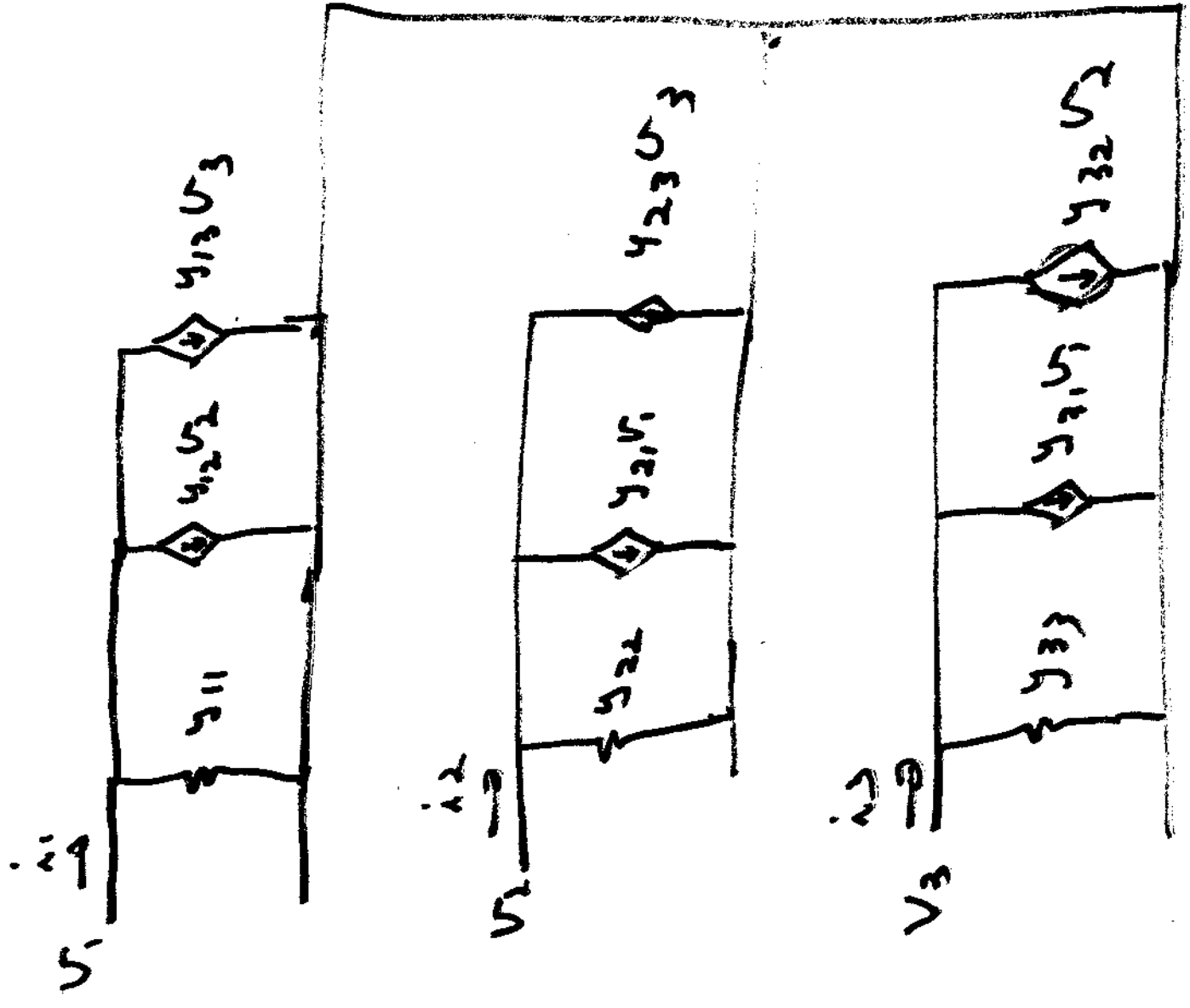


$$i_1 = y_{11}V_1 + y_{12}V_2$$

$$i_2 = y_{21}V_1 + y_{22}V_2$$

Equiv. Ckt

for a

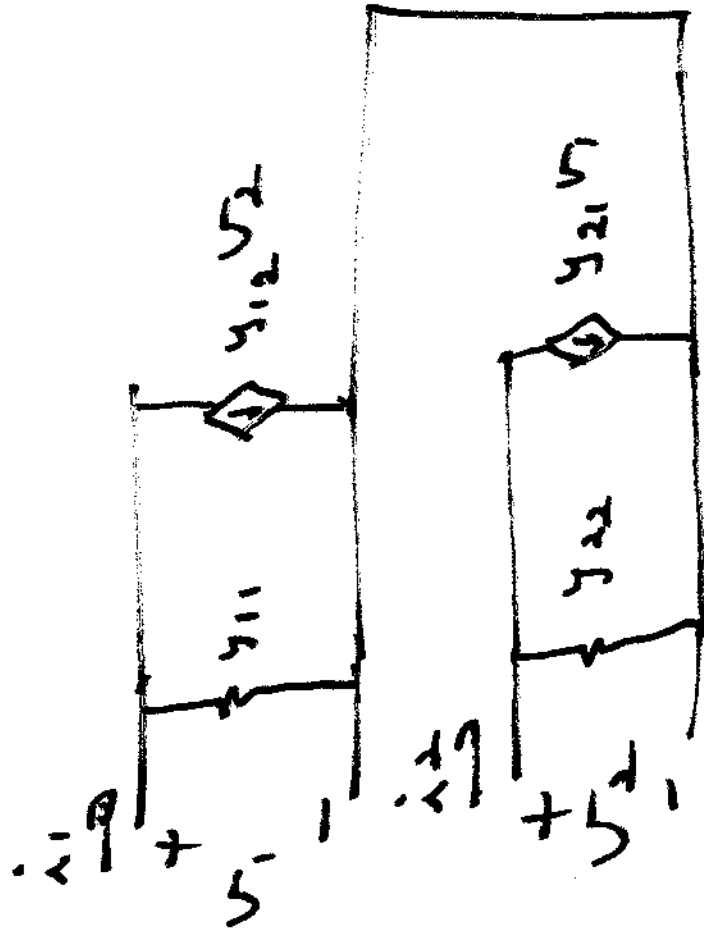3-terminal
device

Note: If the small signal quantities are time-dep, need to characterize them.

Assume all voltages & currents in device are periodic with period T

$$V_{iQ} = \frac{1}{T} \int_{t_1}^{t_1+T} V_i(t) dt$$

$$I_{iQ} = \frac{1}{T} \int_{t_1}^{t_1+T} I_i(t) dt$$

⋮

$$v_1 = v_1 - v_{1q}$$

$$\dot{\lambda}_1 = I_1 - I_{1q}$$

⋮

Example:

$$I_1 = 3V_1 + V_1 V_2^3$$

$$I_2 = V_1 e^{3V_2}$$

Obtain SS model & equiv. ckt at $V_{1Q} = 1V$, $V_{2Q} = 2V$

$$I_{1Q} = I_1(V_Q) = 3V_{1Q} + V_{1Q} V_{2Q}^3 = 3 + 8 = 11A$$

$$I_{2Q} = I_2(V_Q) = (1)e^{3 \cdot 2} = e^6 A$$

$$y_{11} = y_{11} V_1 + y_{12} V_2$$

$$y_{22} = y_{21} V_1 + y_{22} V_2$$

$$y_{11} = \left. \frac{\partial I_1}{\partial V_1} \right|_Q = 3 + V_2^3 \Big|_Q = 3 + 2^3 = 11 \Omega$$

$$y_{12} = \left. \frac{\partial I_1}{\partial V_2} \right|_Q = V_1 3V_2^2 = (1)(3)2^2 = 12 \Omega$$

$$y_{21} = \frac{\partial I_2}{\partial V_1} \Big|_Q = e^{3V_2} \Big|_Q = e^{3 \cdot 2} = e^6$$

$$y_{22} = \frac{\partial I_2}{\partial V_2} \Big|_Q = 3V_1 e^{3V_2} \Big|_Q = 3e^7$$

