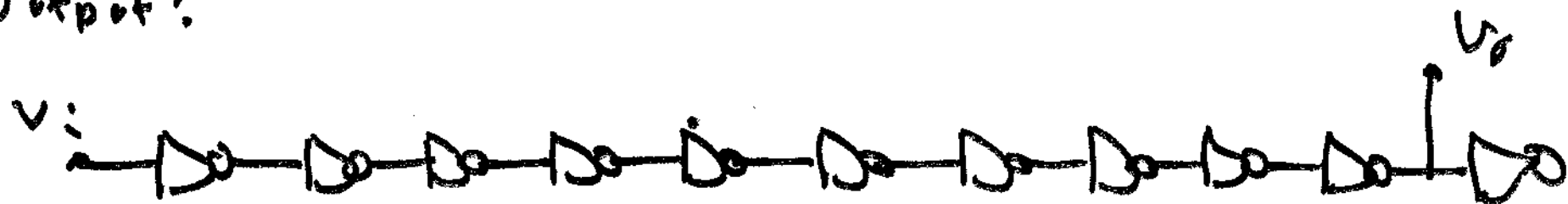


EE 434

Lecture 28

Propagation Delay in Digital
Circuits - Continued





Question: If an inverter drives a cascade of 10 inverters, what delay will be experienced as the signal propagates from the input to the output?






Assume that a transition on a subsequent stage doesn't start until transition is complete on previous stage and subsequent stage transition times are the same as the transition times on the first stage.

$$t_{HL,OA} = 5t_{LH} + 5t_{HL}$$

$$t = \sum_{i=1}^{10} t_i$$

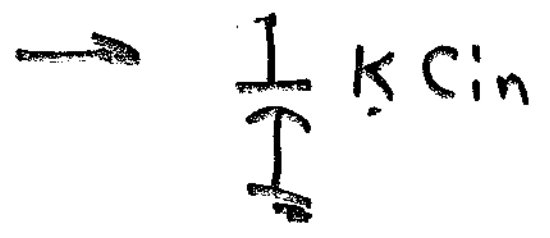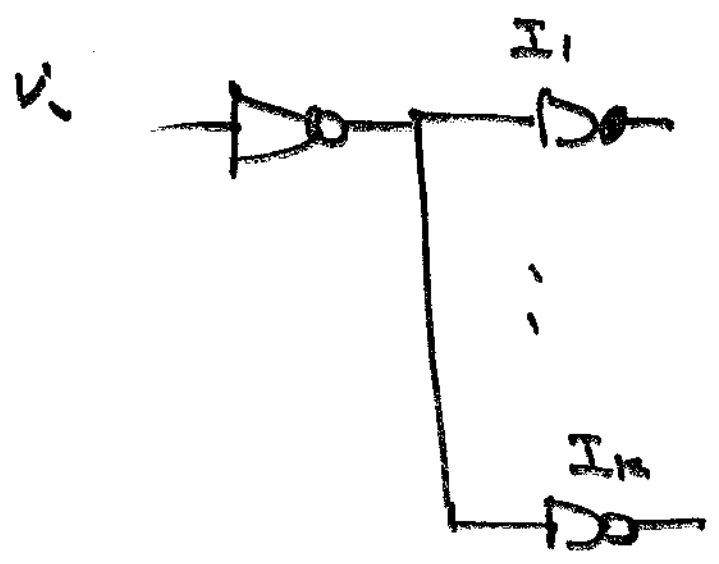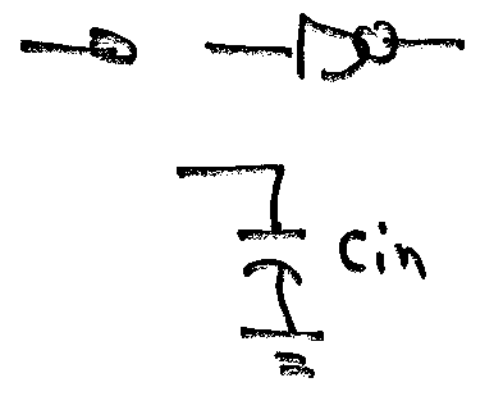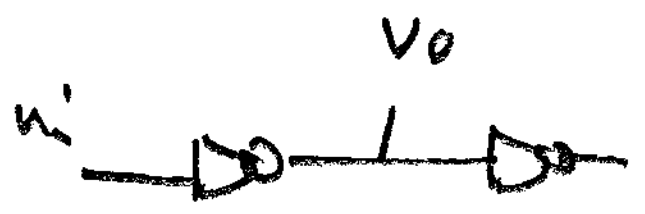

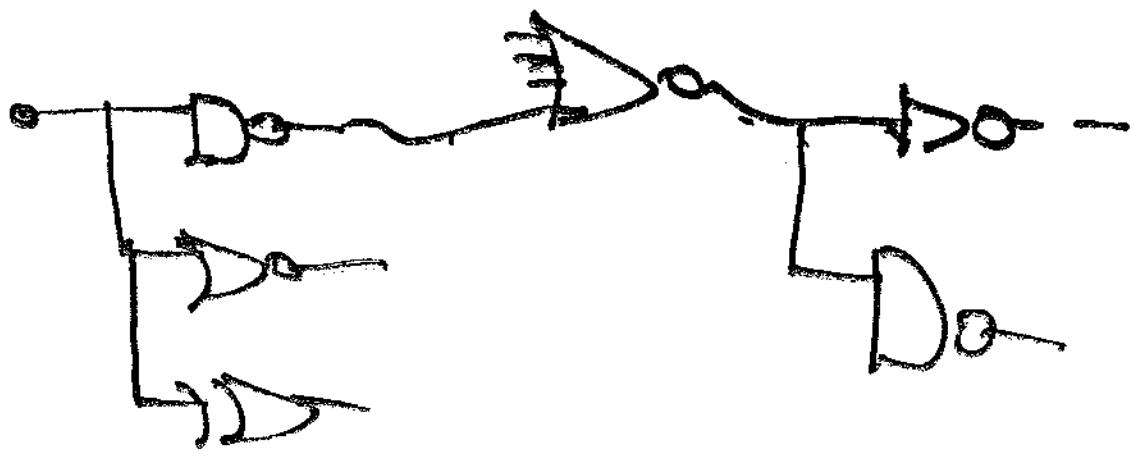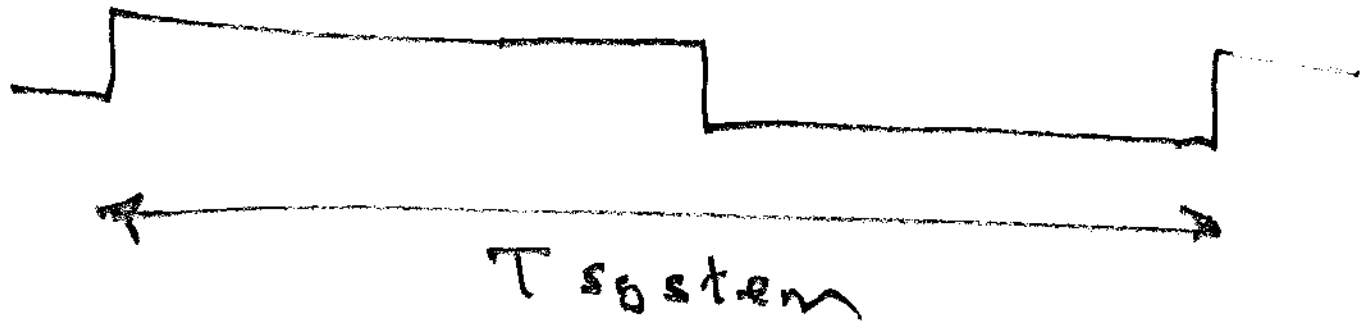

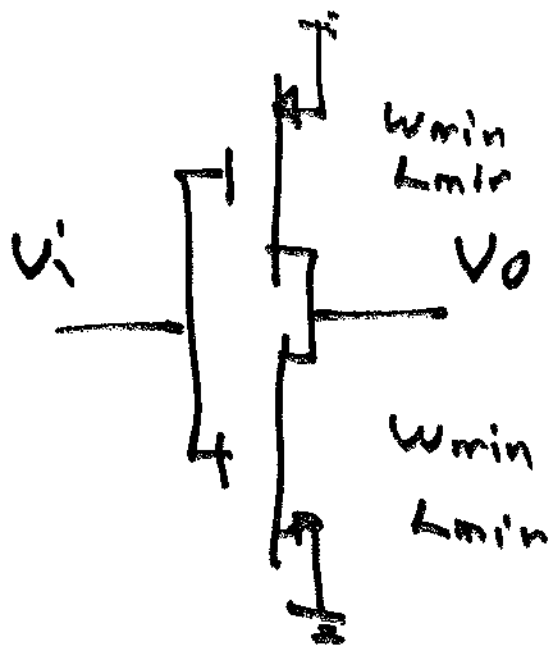


- Establish a reference inverter.
- give propagation data (info) in terms of how an actual gate's propagation relates to that of the reference inverter.

Assume a reference inverter exists.

$$C_{in} = C_{REF}$$


$$t_L = t_{LREF}$$

Consider any gate X_{ink}

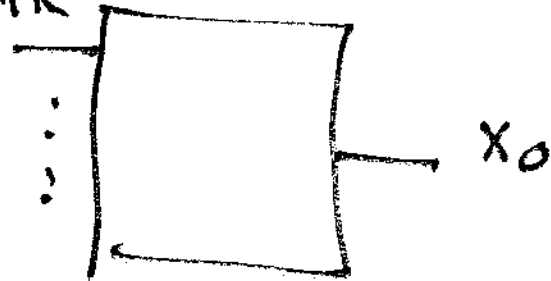


$$F_{an In} = \frac{C_{ink}}{C_{REF}}$$


Example:

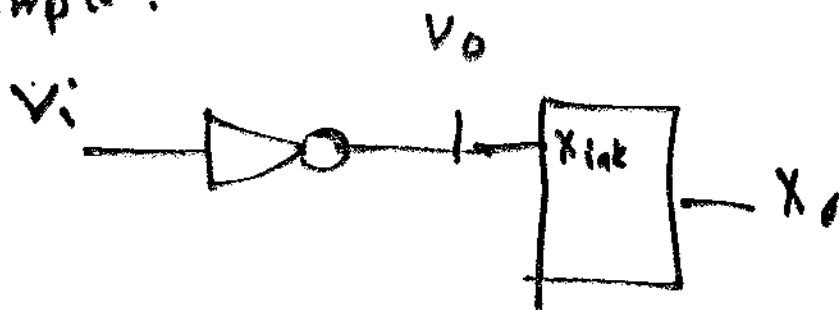

$$t_L = t_{LREF} \cdot F_{an In}$$


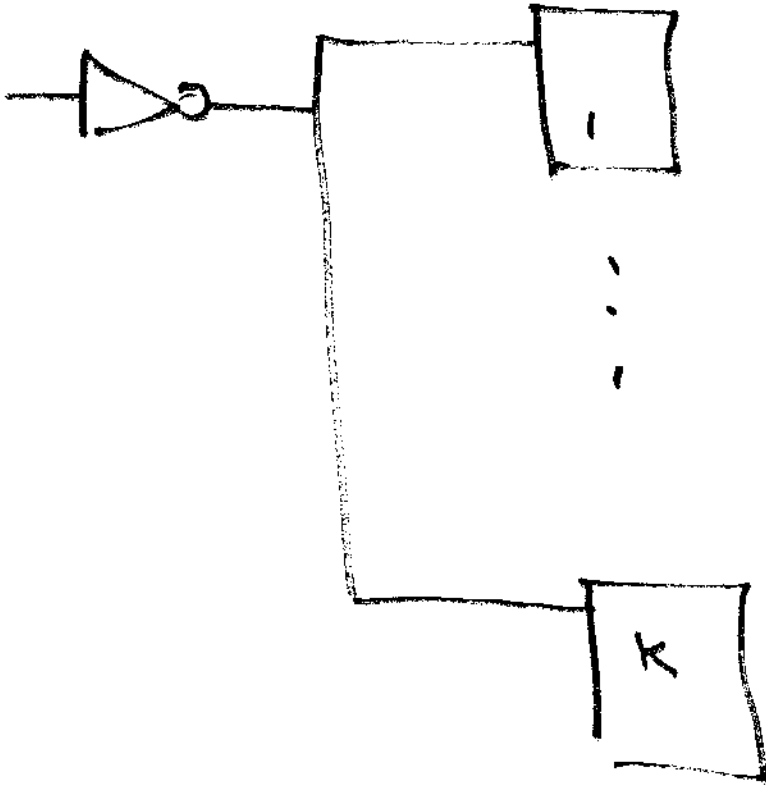

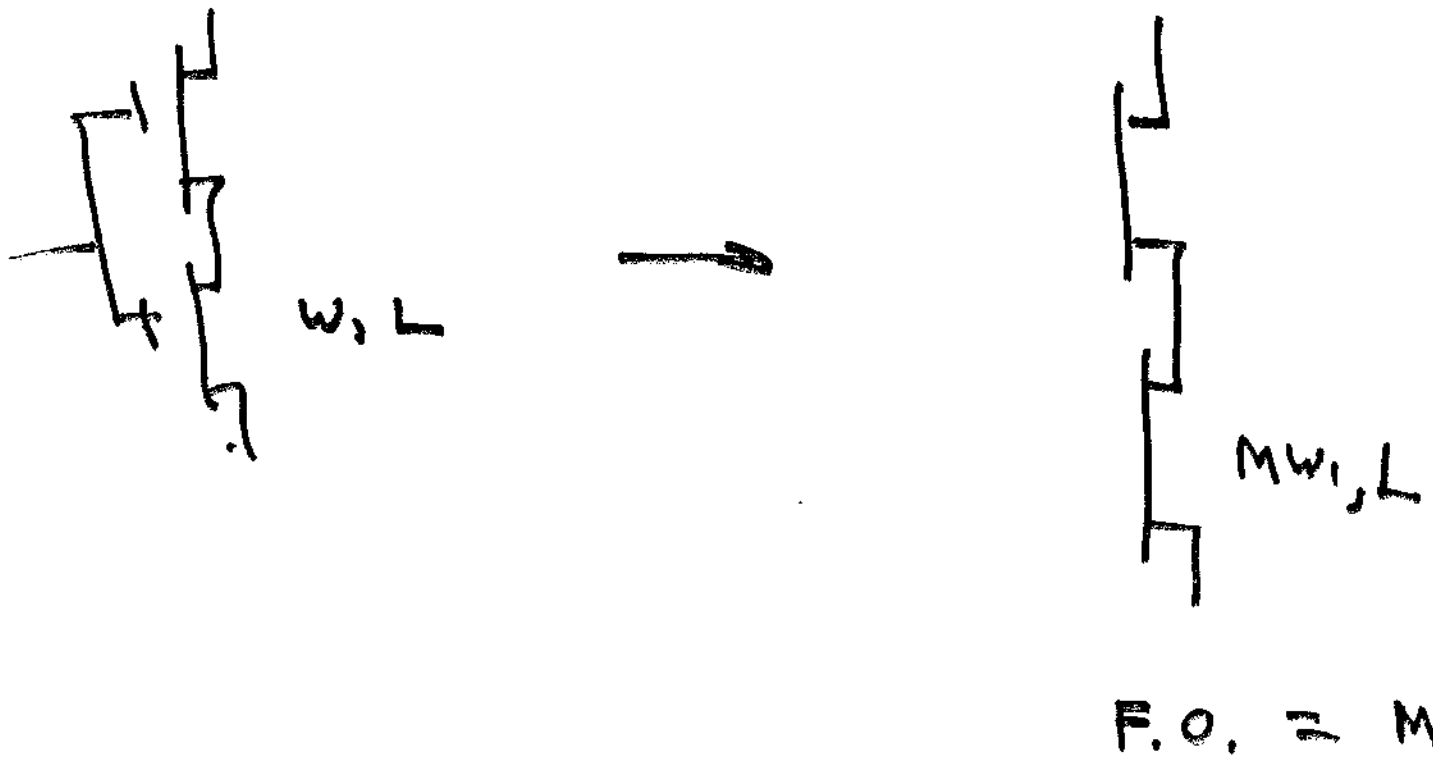
$$\frac{1}{L} = \frac{1}{L_{REF}} \left(\sum_{i=1}^M F I_i \right)$$



If $M > 1$, then the device has a stronger drive capability than the ref. device.

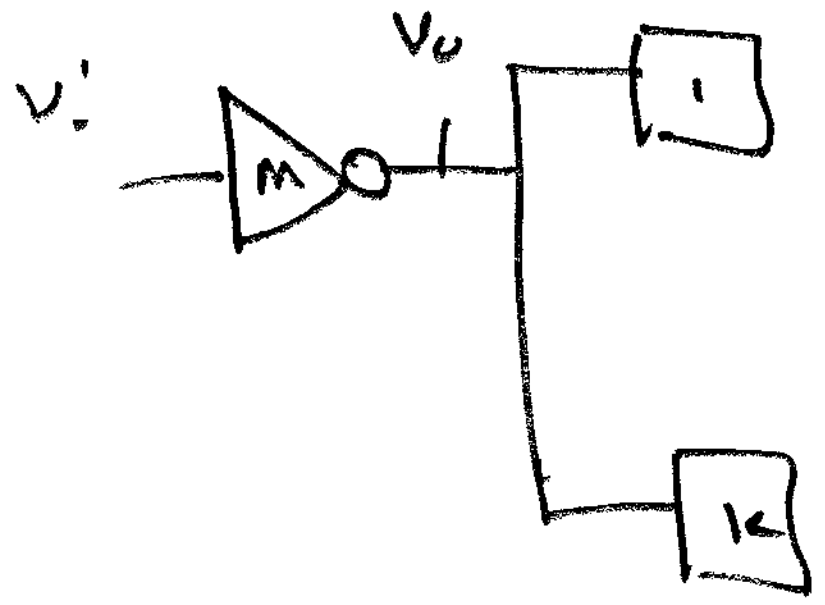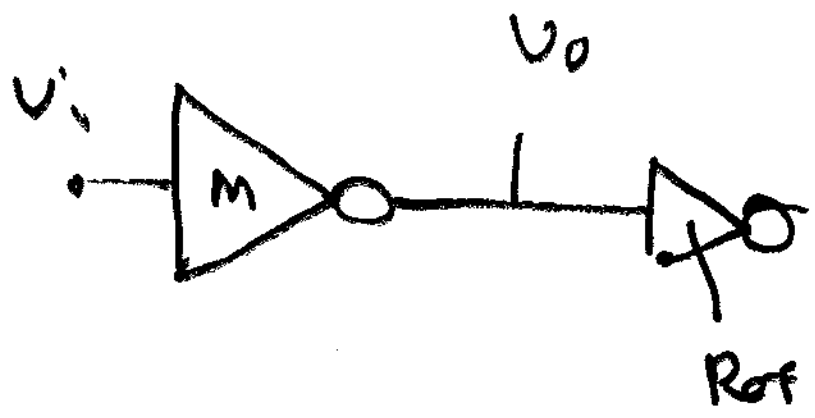If $M < 1$, then the device has a weaker drive capability than the ref. device.



$$k = \frac{t_{REF}}{M}$$

$$k = \frac{t_{REF} \cdot \sum_{i=1}^k \frac{1}{t_{i2}}}{M}$$

EE 434

Lecture 22

~~Timing~~


Delay Calculations

Multiple-Input Gates

Device Sizing

Recall

$$I = (\text{Mult}) I_{REF}$$

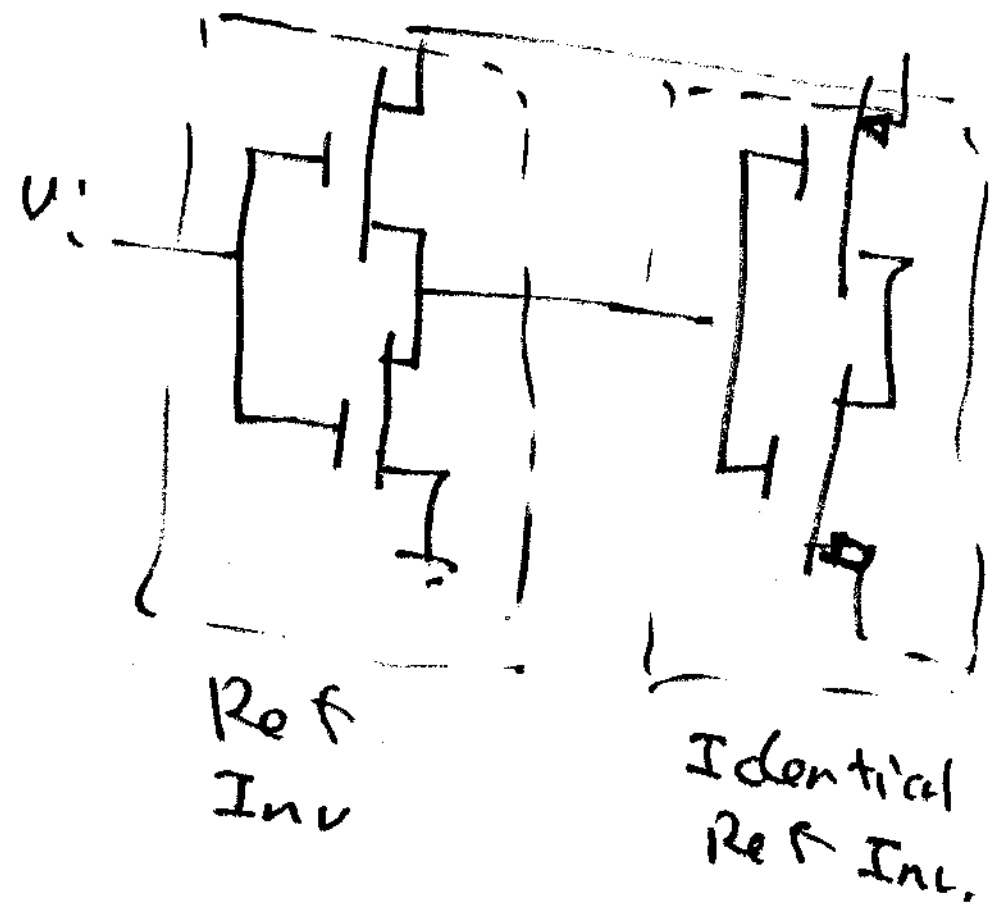

$$I_{REF} = C_{REF} (R_{pu} + R_{pd})$$



L