

EE 434

Lecture 34

Other Logic Styles

Other Logic Design Strategies

Consider an Example! $f = A \oplus B$

- This simple function is one of the small number of "gates" that have two inputs and one output

Gates with 2 inputs, 1 output.

	A	B	C
NAND	0	0	0, 1
NOR	0	1	0, 1
AND	1	0	0, 1
OR	1	1	0, 1
XOR			
XNOR			


∴ Total # of 2 input, 1 output gates is 16

16 - gate

0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	1	1	1
0	0	1	1	0	0	0	1	1
0	1	0	1	0	1	0	0	1
$C=0$	AB	$\bar{A}\bar{B}$	A	$\bar{A}B$	B	$\bar{A}B$ $A\oplus B$	$A+B$	$A+B$

$\overline{A+B}$	$\overline{A\oplus B}$	\bar{B}	\overline{AB}	\bar{A}	\overline{AB}	\overline{AB}	\overline{AB}	$C=1$
1	1	1	1	1	1	1	1	1
0	0	0	0	1	1	1	1	1
0	0	1	1	0	0	1	1	1
0	1	0	1	0	1	0	0	1


$$A \oplus B = A\bar{B} + B\bar{A}$$

 

22 transistors for static CMOS imp.
 5 levels of logic.



$$C = A \oplus B = A\bar{B} + B\bar{A}$$

 

- Pn network & Pn networks never both conducting

- Pn or Pn network is conducting

for Pn network, consider


$$\bar{C} = \overline{A\bar{B} + B\bar{A}}$$

$$= \overline{A\bar{B}} \cdot \overline{B\bar{A}}$$


$$= (\bar{A} + B) \cdot (\bar{B} + A)$$

$$\bar{C} = (\bar{A} + B) \cdot (\bar{B} + A)$$
 
$$= \bar{A}\bar{B} + \bar{A}A + B\bar{B} + AB$$
$$= \bar{A}\bar{B} + AB$$



8 transistors

 

8 transistor c


↙ 4 trans. for pd function
 ↘ 4 trans for variable comp. function.

$$C = \bar{A}B + A\bar{B}$$

for p-channel devices



$$C = A\bar{B} + \bar{A}B$$

 


8 transistors

4 trans for pu


4 trans for var. comp
 
$$\begin{aligned} A\bar{B} + \bar{A}B + A\bar{A} + B\bar{B} &= \\ \bar{A}(A+B) + \bar{B}(A+B) &= \\ (\bar{A} + \bar{B})(A+B) &= \end{aligned}$$



Another Alternative.


pu network : $A\bar{B} + B\bar{A}$

 


transistors : 2

Another Pull-Down Network.

$$\bar{C} = \bar{A}\bar{B} + AB$$

 

~~6~~ 4 - transistors

 

- 3-transistor implementation

- when V_o is high

a) V_o is not quite V_{DD}

b) $P_{\text{STATIC}} = V_{DD} I$

- when V_o is low


V_o is zero



$P_{\text{STATIC}} = 0$

Often the necessity of implementing a function in SOP form when many input variables are present exists

Often necessary to implement a function in POS form where there are many input variables.

Consider the multiple-input NOR gate. :

 

  

Pseudo-NMOS Logic

- ratioed logic

$$- P_{\text{STATIC}} = \begin{cases} 0 & \text{when } V_o \text{ high} \\ V_{DD} \cdot I & \text{when } V_o \text{ low} \end{cases}$$

Styles of Logic

- Standard CMOS
- Complex Logic Gates
- Pass Transistor Logic
- Pseudo NMOS
- Dynamic or Domino Logic