
 


EE 434

Lecture 41


Array Logic

 - Sea of Gates
- Mask Programmable ROM
- FPGA




- If more inputs are needed
can use multiple cells
- waste is common
 - both within a cell
 - within the array

Basic Sea of Gates Structure

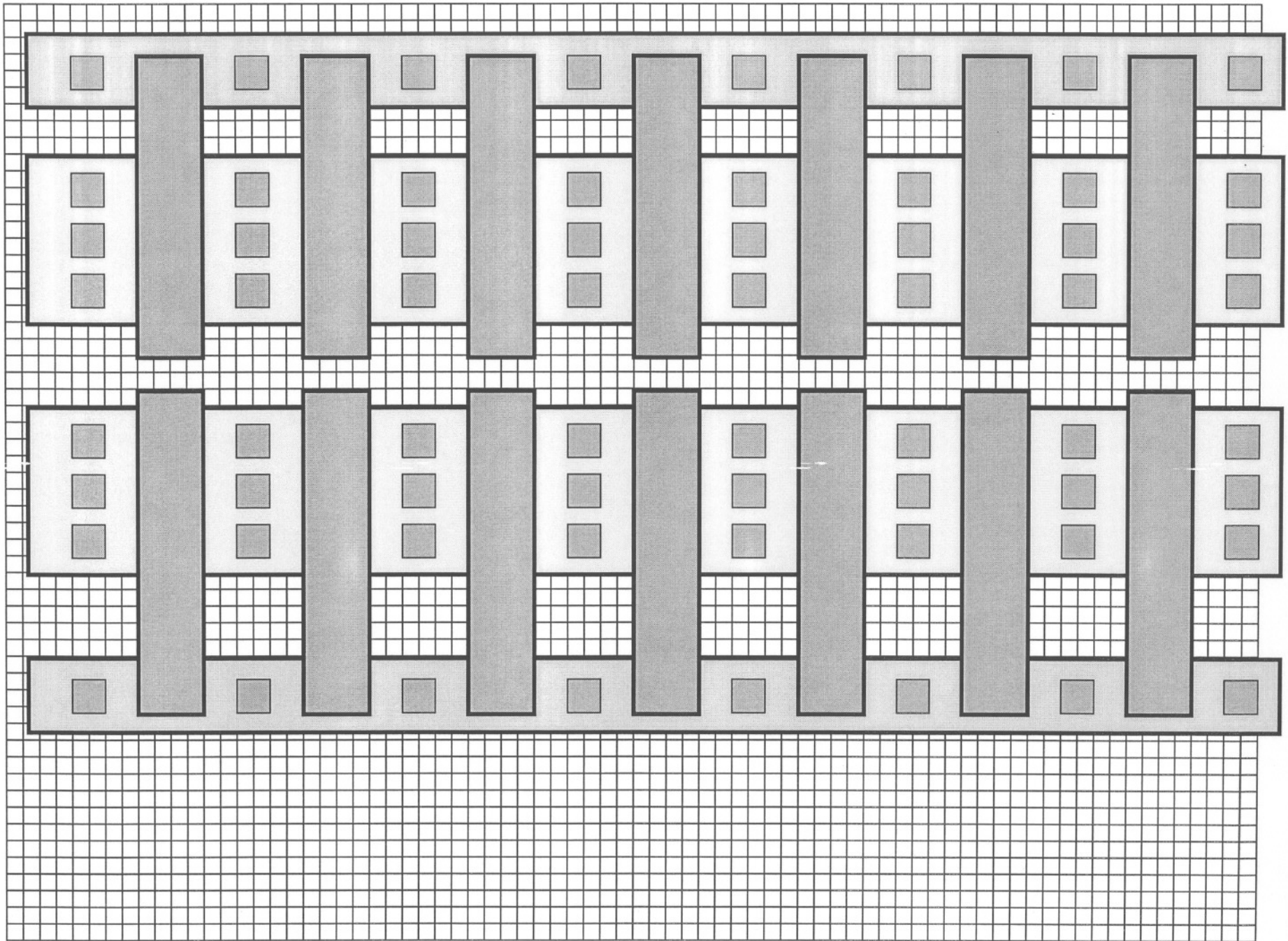


 Sea of Gates Partitioning to Realize Array of Small Gates



- Simply need to add contacts to partition array
- Logic implemented in same way as Gate Arrays
- May be less wasted sites since partitions can be used to create desired size of gates

Mask Programmable ROM

 

- Single transistor for each bit 😊
- Read Only 😊
- transistor site reserved at all intersections

 


FIG 11-57 Pseudo-nMOS PLA schematic

To read, take Row L high and present column outputs to sense amp.

- Cap. on column lines is large and can cause cell contents to be overwritten!
- To circumvent this problem, precharge column lines to V_{TRIP}

Field Programmable Gate Arrays

Major players :

Xilinx

Altera

Actel



comparable
in size



Much
Smaller



- Some are one-time programmable
- Some can be repeatedly reprogrammed


Memory in FPGAs

- 1) SRAM / EPROM support or E²PROM support
- 2) EPROM
or E²PROM
- 3) Anti-fuses
- 4) Fuses (Least Popular)

Must be able to interconnect "gates"
and program the gates

Fuse :

  

 


If transistors are used to route the current, how do we keep the transistors from burning out?
 → size width & interconnect appropriately

Limitations

- 1) Transistors for prog. current are too large
- 2) one-time use
- 3) damages material above & has regrowth

Antifuse

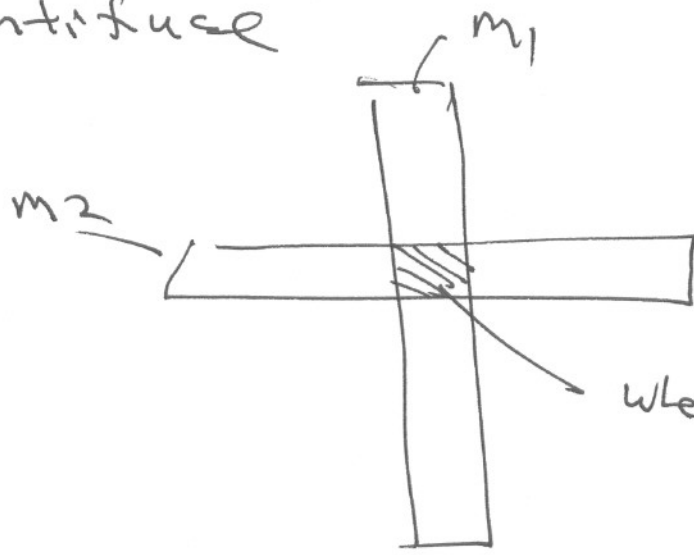

When heated up, Resistance Drops a lot.

— widely used at Altera

Limitations

- 1) Single-tile programmable
- 2) Specialized processing step