

EE 434

Lecture 21


MOS Amplifiers
Bipolar Devices

Quiz 13

The quiescent voltage across the 25K resistor in the circuit shown was measured to be 3V.

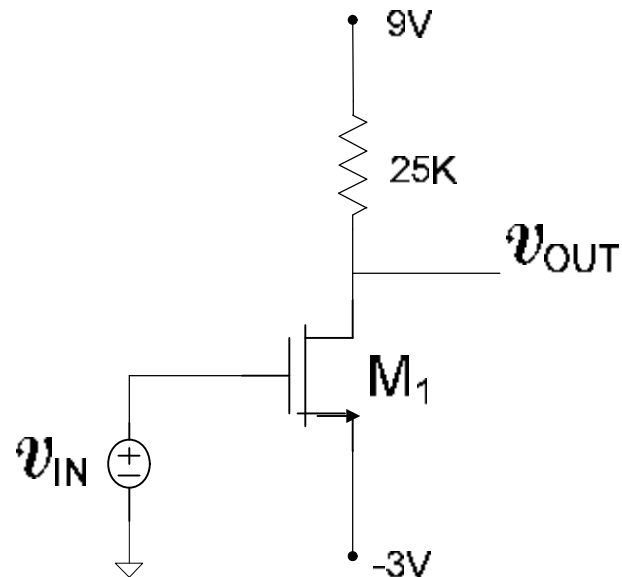- 1) Determine the quiescent output voltage
- 2) Determine the small signal voltage gain

Assume M_1 is manufactured in a process with $\mu C_{OX}=100\mu A/V^2$ and $V_T=1V$.



And the number is

1 8 7 5 3
6 9 4 2

And the number is

1 8 7 5 3
6 9 4 2

1

Quiz 13


The quiescent voltage across the 25K resistor in the circuit shown was measured to be 3V.

- 1) Determine the quiescent output voltage
- 2) Determine the small signal voltage gain

Assume M_1 is manufactured in a process with $\mu C_{OX}=100\mu A/V^2$ and $V_T=1V$.

Solution:

$$V_{OQ} = V_{DD} - I_{DQ} R_D = 9V - 3V = 6V$$

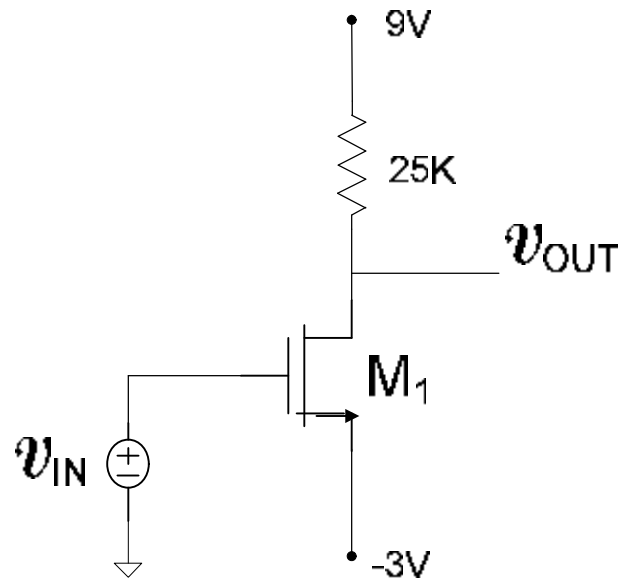

Quiz 13


The quiescent voltage across the 25K resistor in the circuit shown was measured to be 3V.

- 1) Determine the quiescent output voltage
- 2) Determine the small signal voltage gain

Assume M_1 is manufactured in a process with $\mu C_{OX}=100\mu A/V^2$ and $V_T=1V$.

Solution:

$$A_V = g_M R_D = -\frac{2 I_{DQ} R_L}{V_{EB}}$$

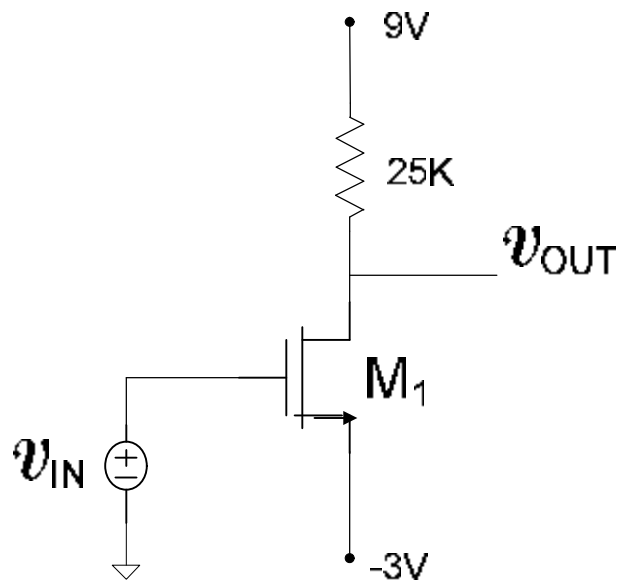

Quiz 13


The quiescent voltage across the 25K resistor in the circuit shown was measured to be 3V.

- 1) Determine the quiescent output voltage
- 2) Determine the small signal voltage gain



Assume M_1 is manufactured in a process with $\mu C_{OX}=100\mu A/V^2$ and $V_T=1V$.

Solution:
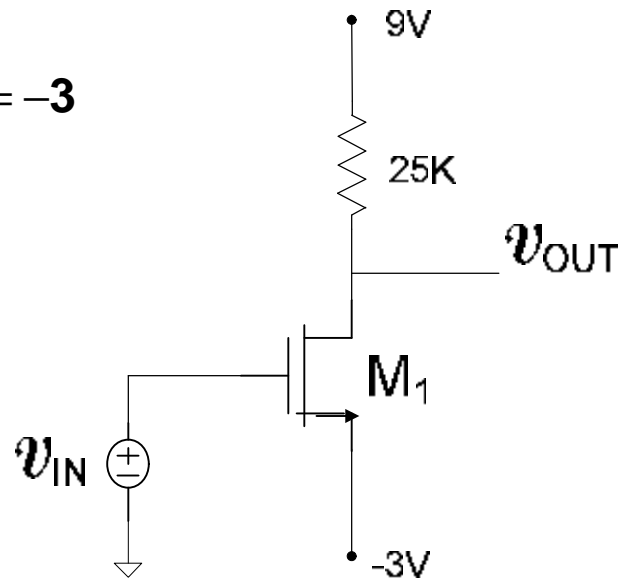
$$A_V = g_M R_D = -\frac{2 I_{DQ} R_L}{V_{EB}} = -\frac{2 \cdot 3V}{3V - 1V} = -3$$



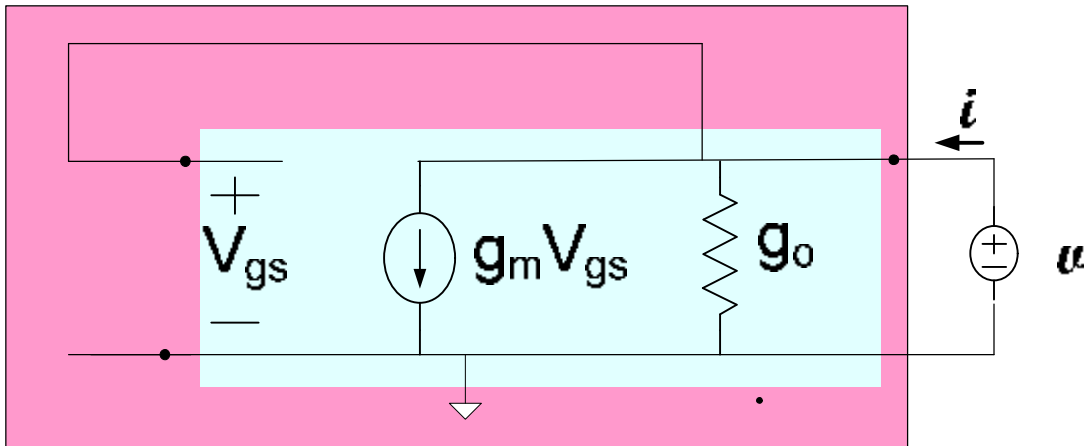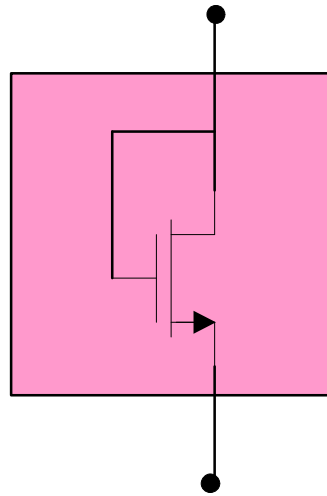Example: Determine the small signal equivalent for the following device.
 Assume M_1 operating in the saturation region




$$i = g_0 V + g_m V$$



$$G_{EQ} = \frac{i}{V} = g_0 + g_m \cong g_m$$

MOS Amplifier



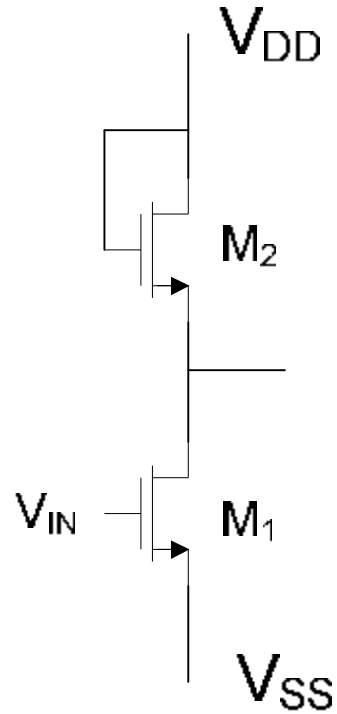
Determine the small signal voltage gain for the following circuit.
Assume M_1 and M_2 operating in the saturation region



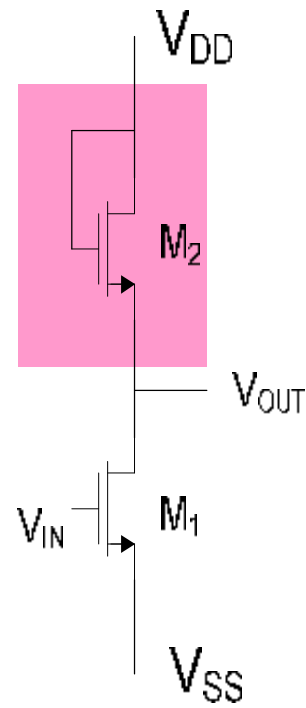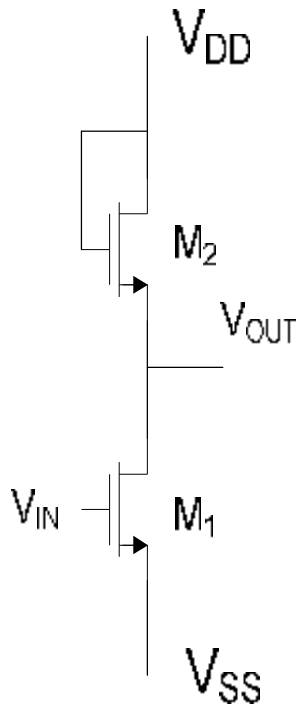MOS Amplifier Determine the small signal voltage gain for the following circuit. Assume M_1 and M_2 operating in the saturation region




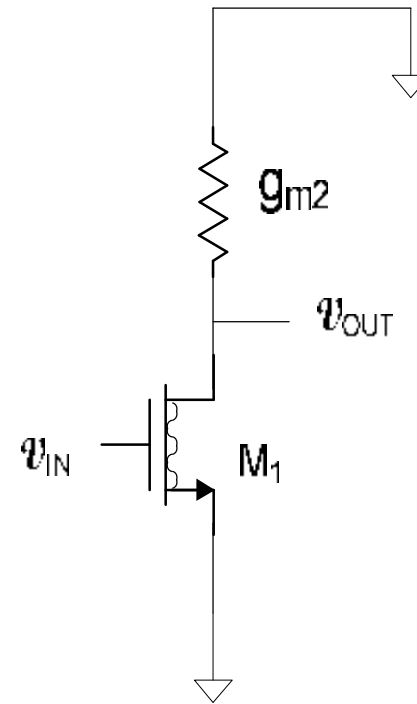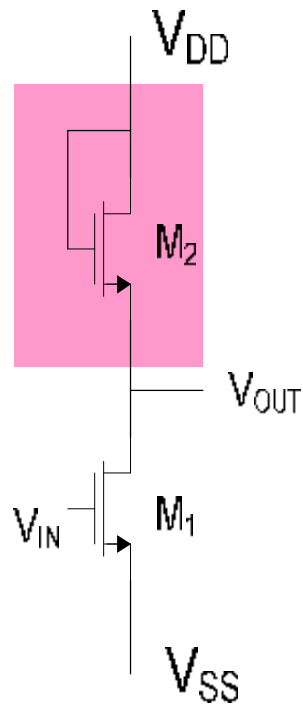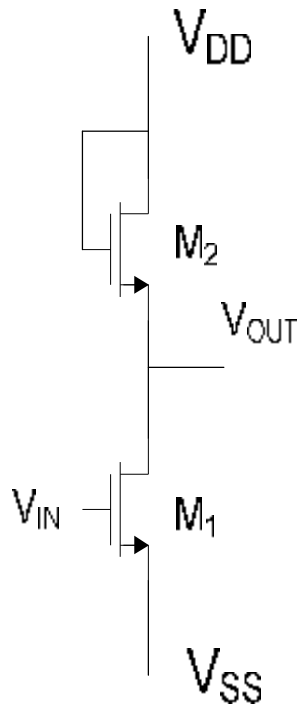MOS Amplifier Determine the small signal voltage gain for the following circuit. Assume M_1 and M_2 operating in the saturation region



$$A_v = -\frac{g_{m1}}{g_{m2}}$$

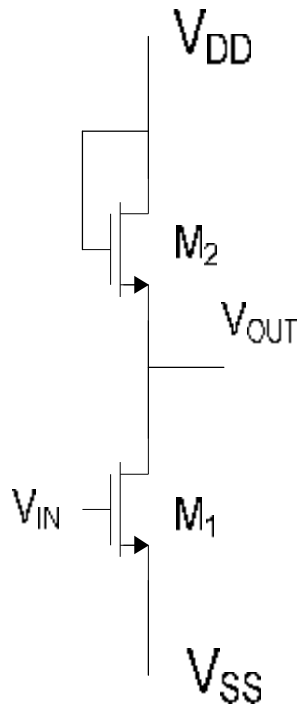
MOS Amplifier Determine the small signal voltage gain for the following circuit. Assume M_1 and M_2 operating in the saturation region



$$A_V = -\frac{g_{m1}}{g_{m2}}$$

$$A_V = -\frac{\sqrt{2m_1 C_{OX1} \frac{W_1}{L_1} I_{DQ1}}}{\sqrt{2m_2 C_{OX2} \frac{W_2}{L_2} I_{DQ2}}}$$

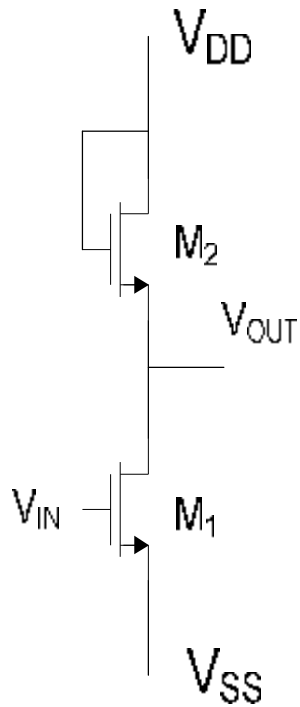MOS Amplifier Determine the small signal voltage gain for the following circuit.
 Assume M_1 and M_2 operating in the saturation region




$$A_V = - \frac{g_{m1}}{g_{m2}}$$

$$A_V = - \frac{\sqrt{\cancel{2m_1} C_{OX1} \frac{W_1}{L_1} \cancel{I_{DQ1}}}}{\sqrt{\cancel{2m_2} C_{OX2} \frac{W_2}{L_2} \cancel{I_{DQ2}}}}$$

$$A_V = \sqrt{\frac{W_1 L_2}{W_2 L_1}}$$

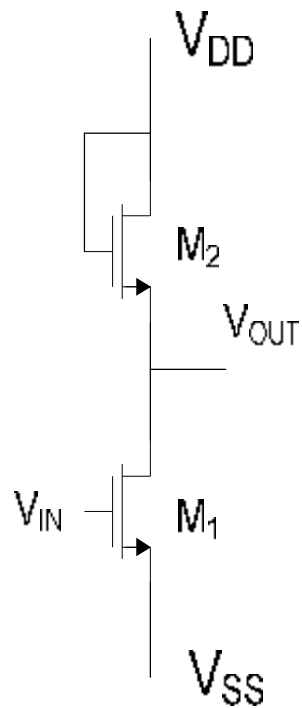MOS Amplifier Determine the small signal voltage gain for the following circuit.
 Assume M_1 and M_2 operating in the saturation region



$$A_V = -\frac{g_{m1}}{g_{m2}}$$

$$A_V = -\frac{\sqrt{\cancel{2m_1} C_{OX1} \frac{W_1}{L_1} \cancel{I_{DQ1}}}}{\sqrt{\cancel{2m_2} C_{OX2} \frac{W_2}{L_2} \cancel{I_{DQ2}}}}$$

$$A_V = \sqrt{\frac{W_1 L_2}{W_2 L_1}}$$


Accurate gain control

Nearly independent of process parameters

Can also show (but not from ss analysis) that this is quite very linear !

MOS Amplifier Determine the small signal voltage gain for the following circuit.
Assume M_1 and M_2 operating in the saturation region

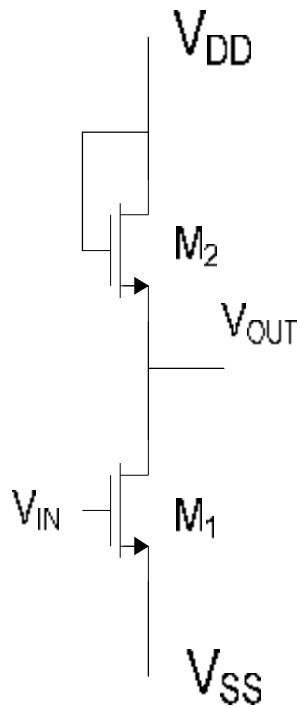Linearity of this common-source amplifier



$$I_{D1} \cong \mu_1 C_{OX1} \frac{W_1}{2L_1} (V_{IN} - V_{T1})^2$$

$$I_{D2} \cong \mu_2 C_{OX2} \frac{W_2}{2L_2} (V_{DD} - V_{OUT} - V_{T2})^2$$


$$I_{D1} = I_{D2} \Rightarrow \mu_1 C_{OX1} \frac{W_1}{2L_1} (V_{IN} - V_{T1})^2 \cong \mu_2 C_{OX2} \frac{W_2}{2L_2} (V_{DD} - V_{OUT} - V_{T2})^2$$

Taking the square root of both sides of this eqn, obtain

$$V_{OUT} = -\sqrt{\frac{W_1}{W_2} \frac{L_2}{L_1}} V_{IN} + V_{DD} + \sqrt{\frac{W_1}{W_2} \frac{L_2}{L_1}} V_{T1} - V_{T2}$$

MOS Amplifier Determine the small signal voltage gain for the following circuit.
 Assume M_1 and M_2 operating in the saturation region

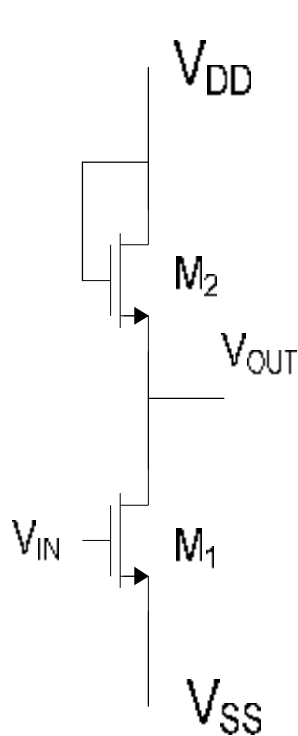Linearity of this common-source amplifier



$$V_{OUT} = -\sqrt{\frac{W_1 L_2}{W_2 L_1}} V_{IN} + V_{DD} + \sqrt{\frac{W_1 L_2}{W_2 L_1}} V_{T1} - V_{T2}$$

Appears to be perfectly linear


Have neglected bulk effect for M_2 which introduces small nonlinearity

Have also neglected λ effects which introduce some more nonlinearity

Dependent upon square-law model which may not be good enough

Overall, good linearity and accurate control of gain but not perfect

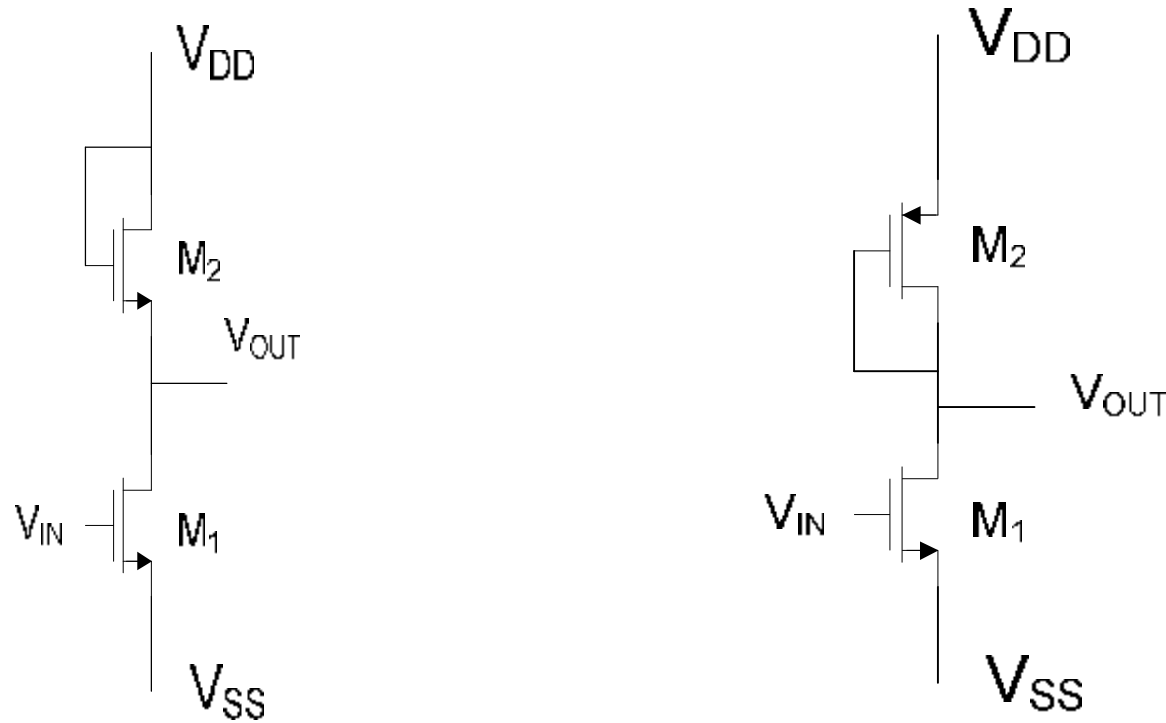
MOS Amplifier Determine the small signal voltage gain for the following circuit.
 Assume M_1 and M_2 operating in the saturation region



How do these two amplifiers compare?

$$A_V = - \frac{\sqrt{\cancel{2} m_1 C_{OX1} \frac{W_1}{L_1} \cancel{I_{DQ1}}}}{\sqrt{\cancel{2} m_2 C_{OX2} \frac{W_2}{L_2} \cancel{I_{DQ2}}}} \cong \sqrt{\frac{m_1}{m_2} \frac{W_1}{W_2} \frac{L_2}{L_1}}$$

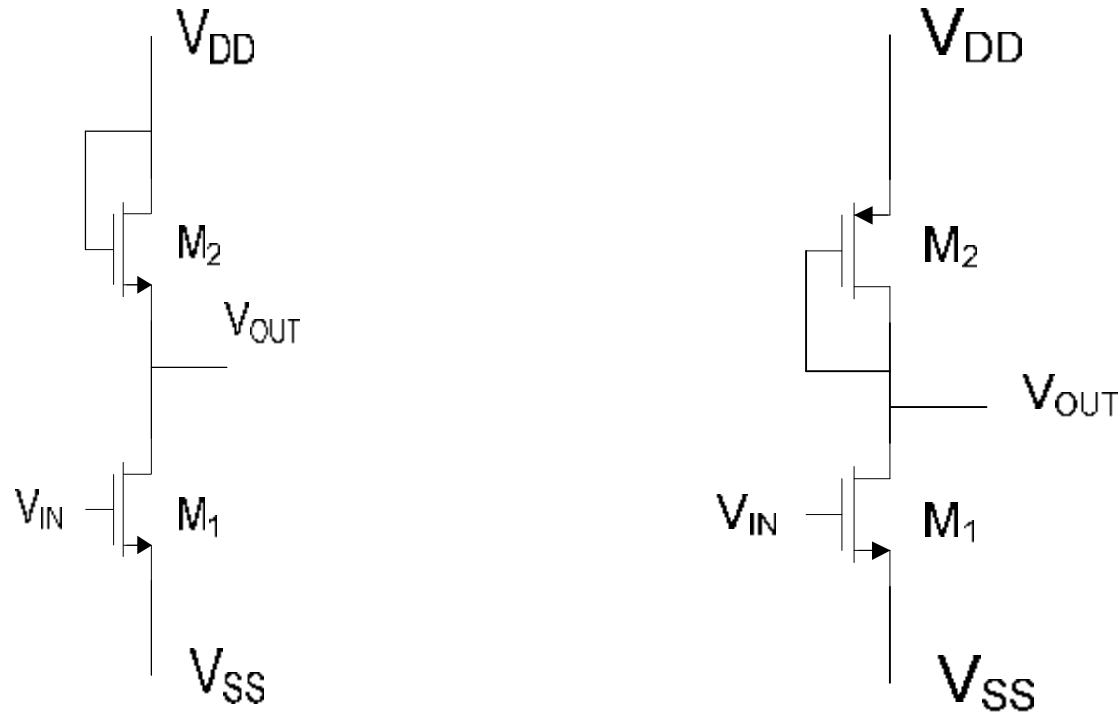MOS Amplifier Determine the small signal voltage gain for the following circuit.
Assume M_1 and M_2 operating in the saturation region



How do these two amplifiers compare?


g_{mb} effects are removed for one on right !

Gain can not be as accurately controlled


Bipolar Junction Transistors

- Operation
- Modeling


Carriers in Doped Semiconductors

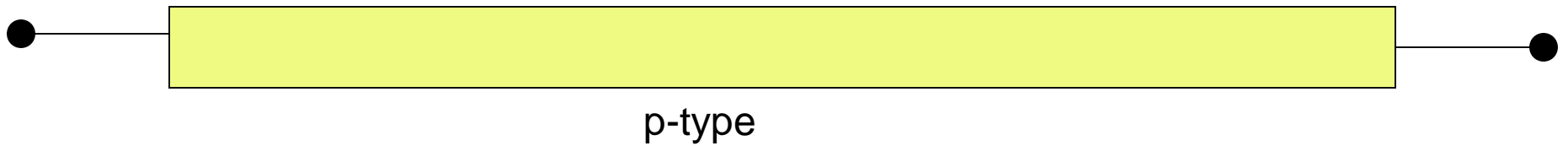

Carriers in Doped Semiconductors

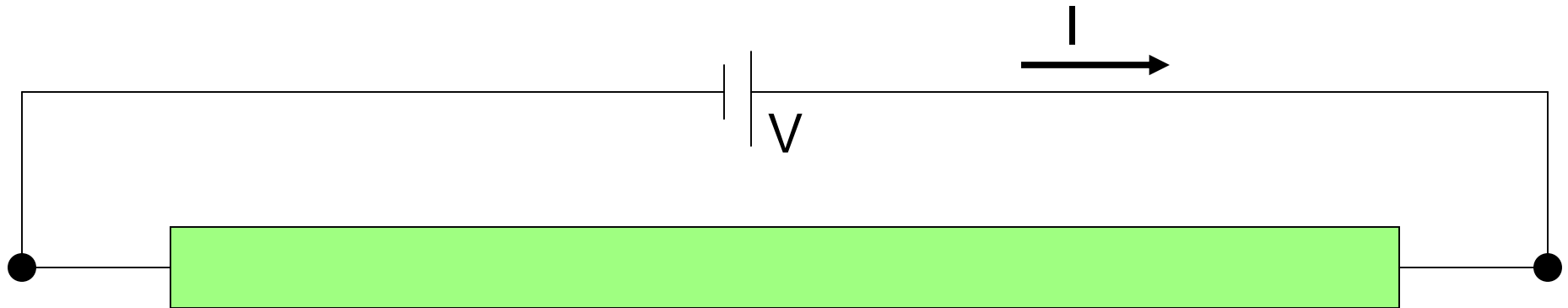

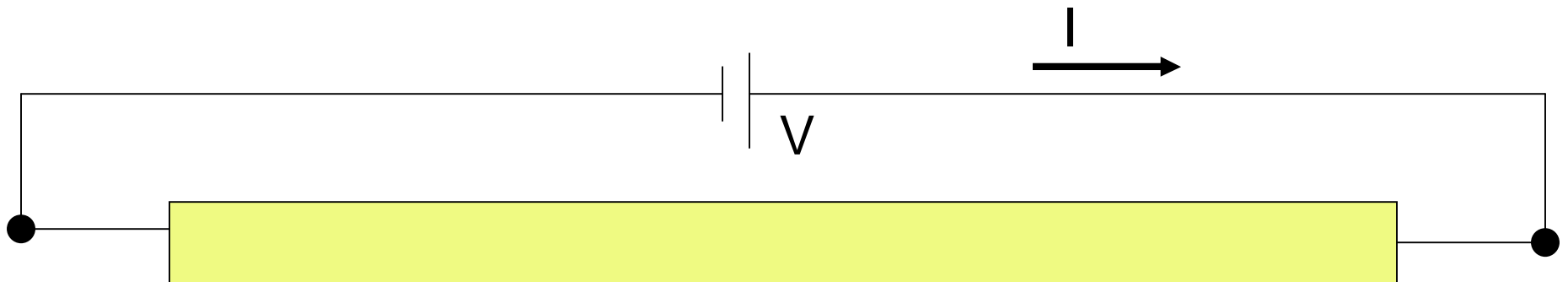Current carriers are dominantly electrons
Small number of holes are short-term carriers




Current carriers are dominantly holes
Small number of electrons are short-term carriers

Carriers in Doped Semiconductors

	Majority Carriers	Minority Carriers
n-type	electrons	holes
p-type	holes	electrons


Carriers in MOS Transistors

Consider n-channel MOSFET

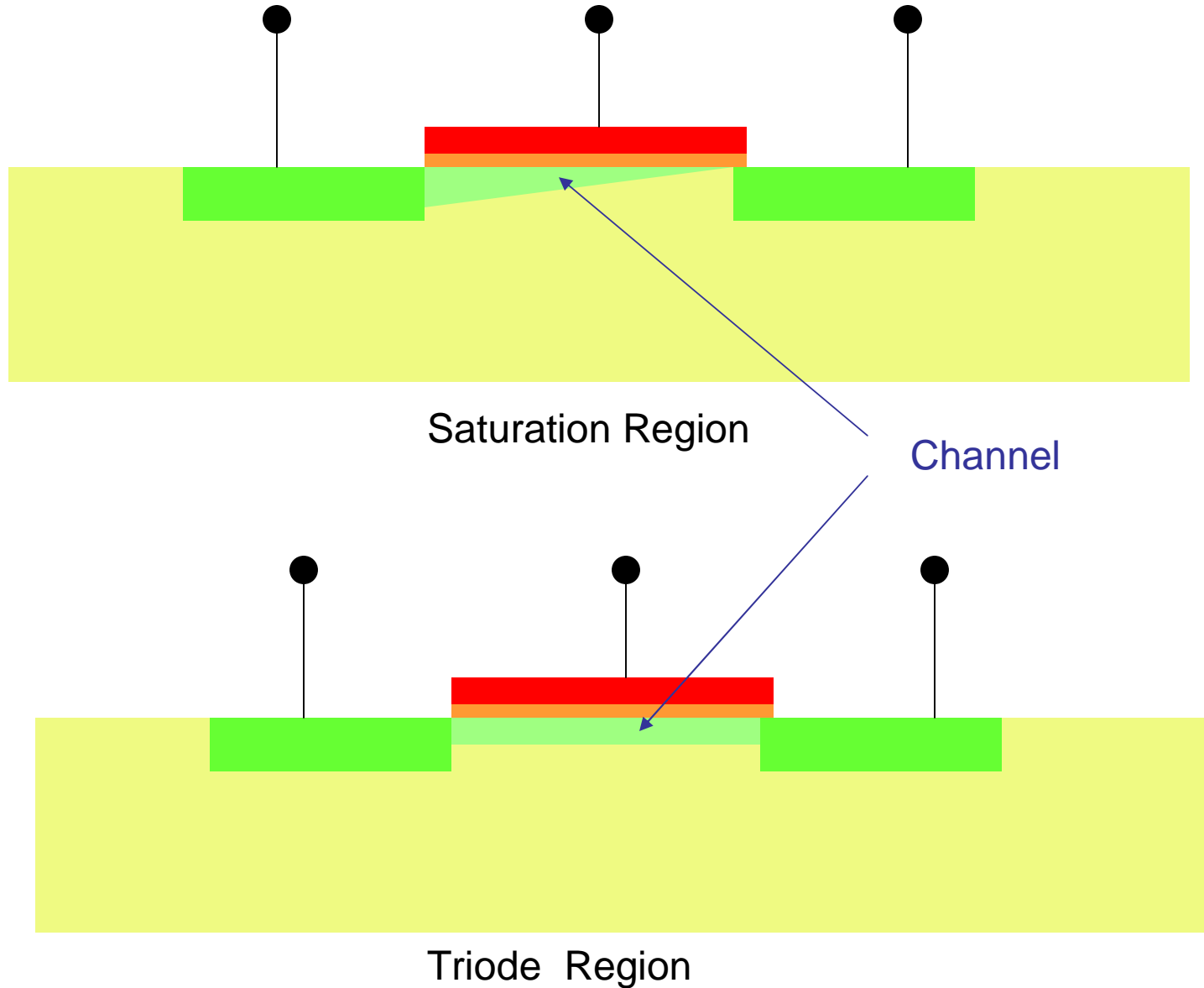


Carriers in MOS Transistors

Consider n-channel MOSFET

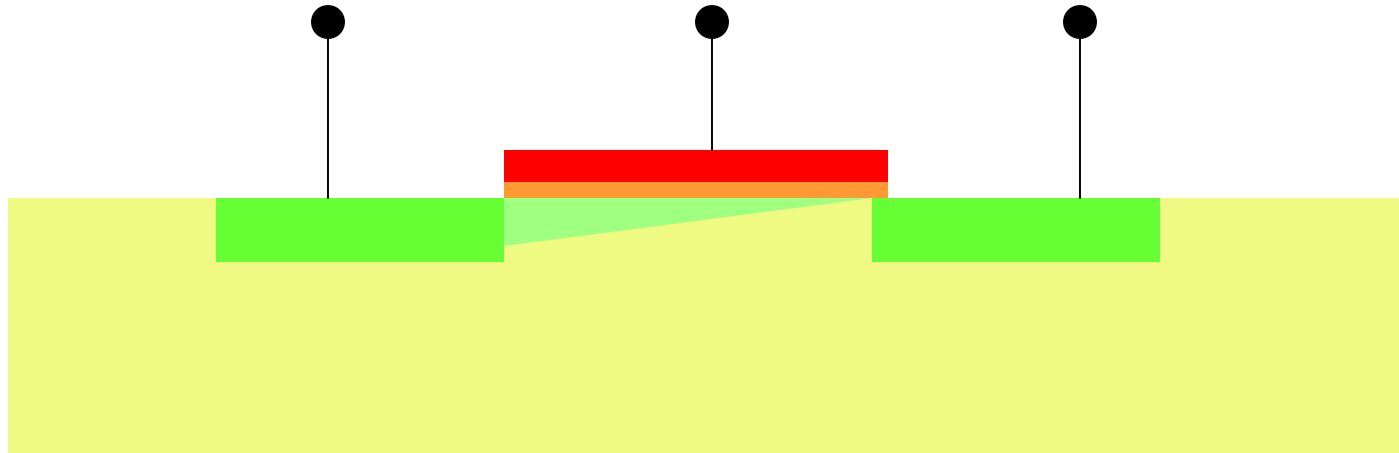

Saturation Region

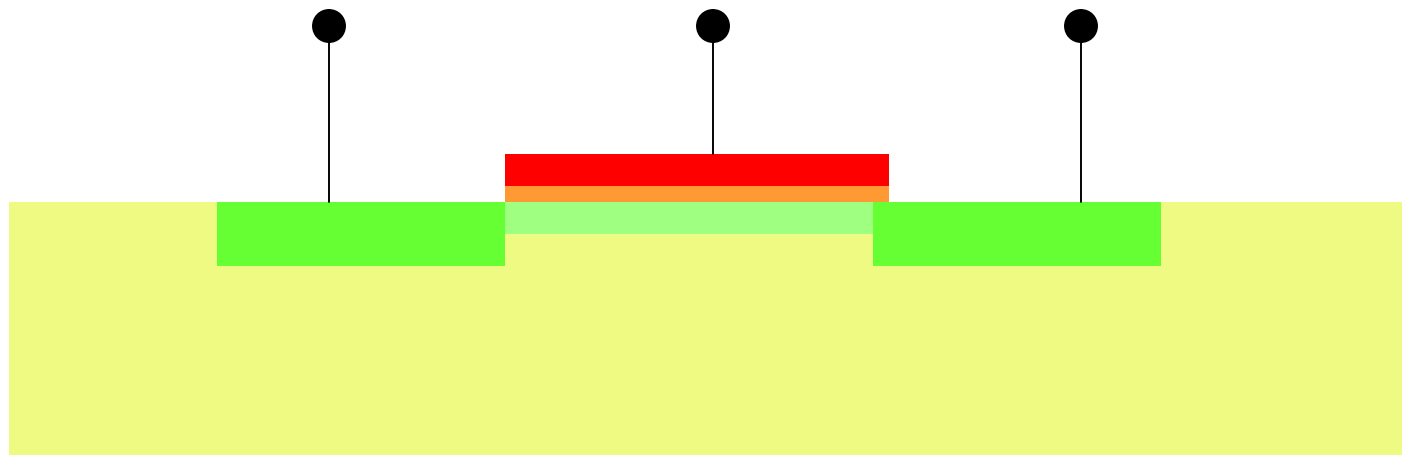


Triode Region

Carriers in electrically induced n-channel are electrons


Carriers in MOS Transistors

Consider p-channel MOSFET

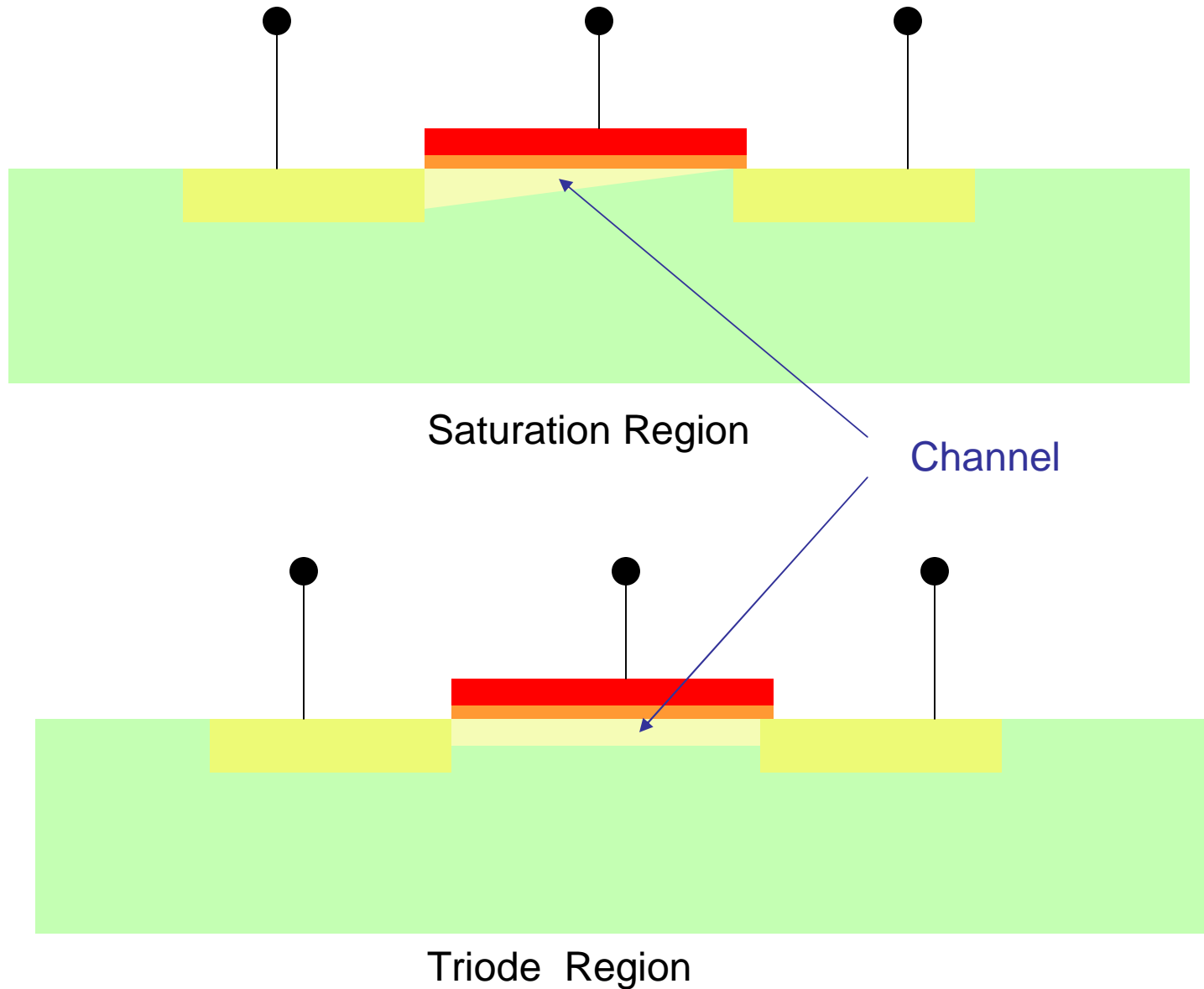


Carriers in MOS Transistors

Consider p-channel MOSFET

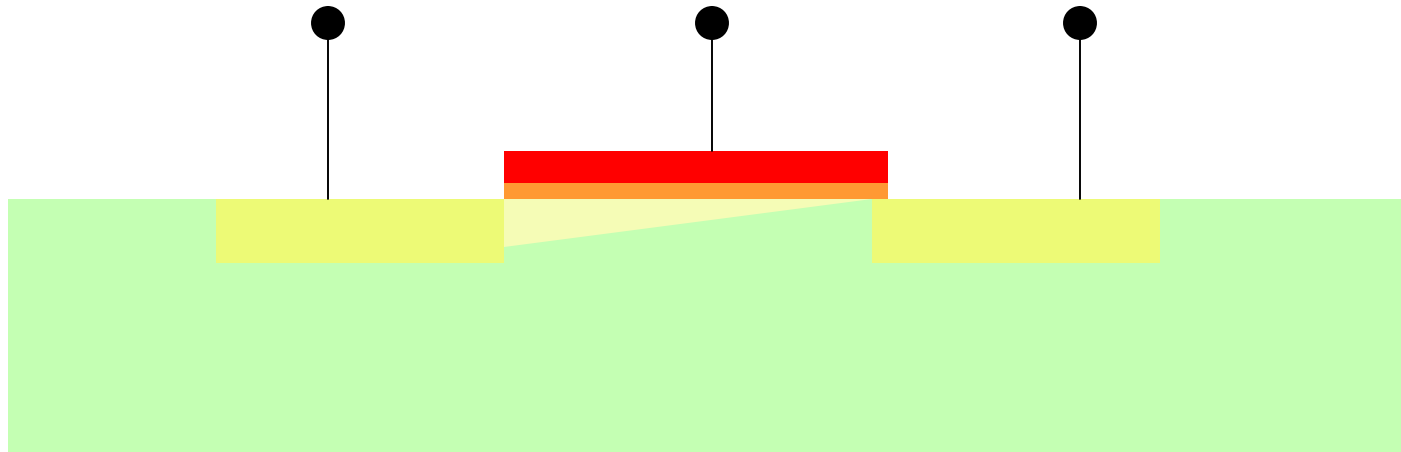





Saturation Region

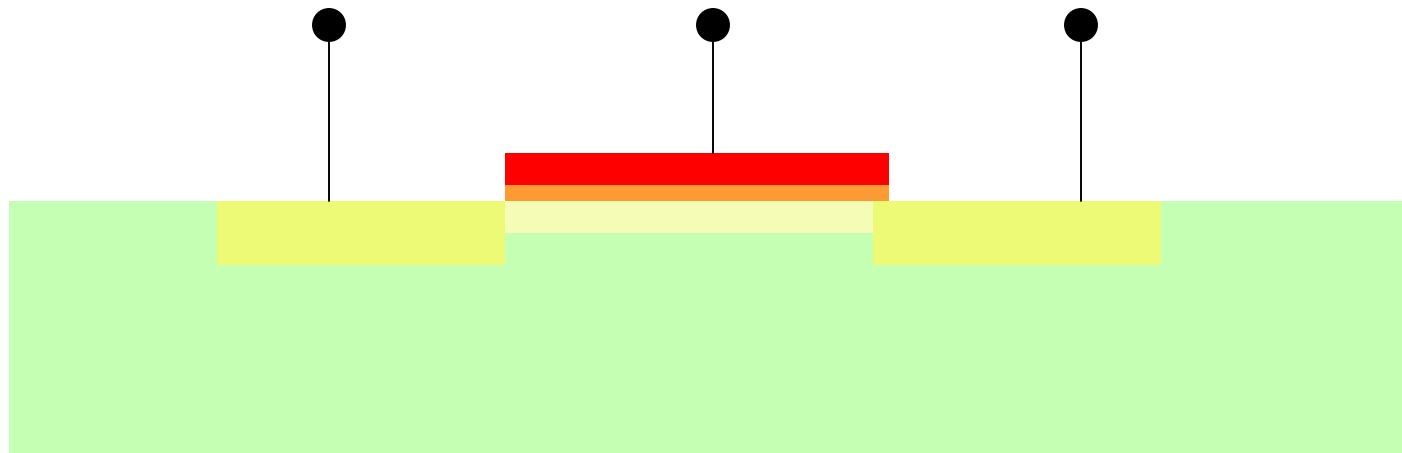

Triode Region


Carriers in electrically induced p-channel are holes

Carriers in MOS Transistors

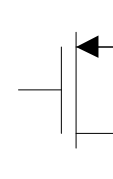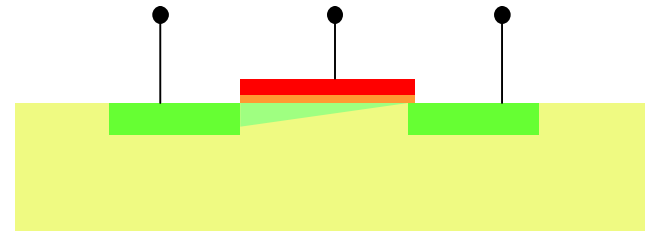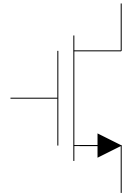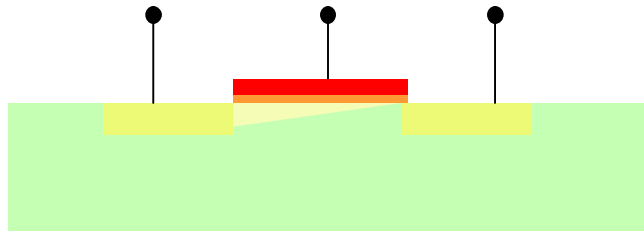


Carriers in channel of MOS transistors are Majority carriers


Bipolar Transistors

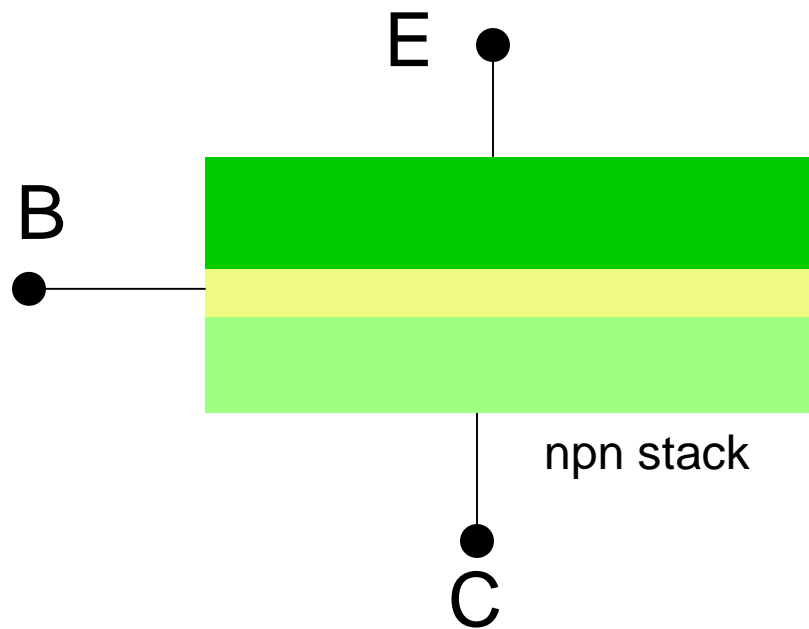


npn stack

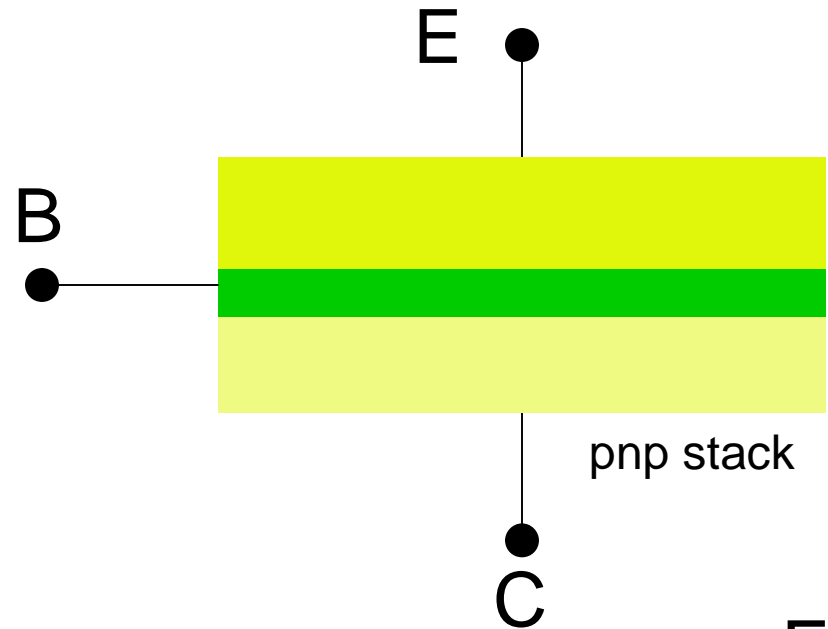

pnp stack

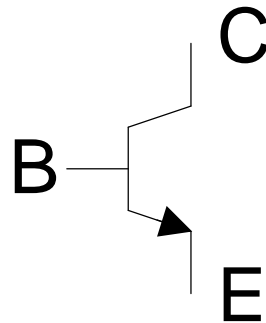


npn transistor

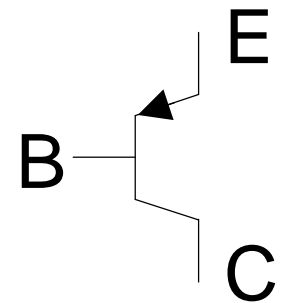


pnp transistor

With proper doping and device sizing these form Bipolar Transistors


Bipolar Transistors

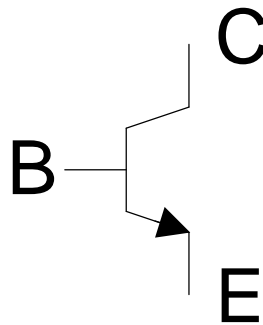


npn transistor

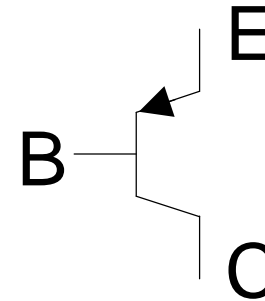

pnp transistor

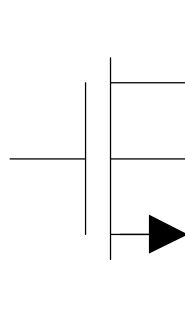

n-channel MOSFET

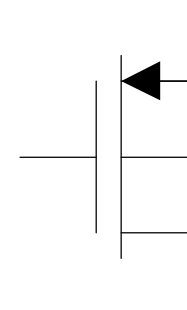


p-channel MOSFET

In contrast to a MOSFET which has 4 terminals, a BJT only has 3 terminals

Bipolar Operation

Consider npn transistor

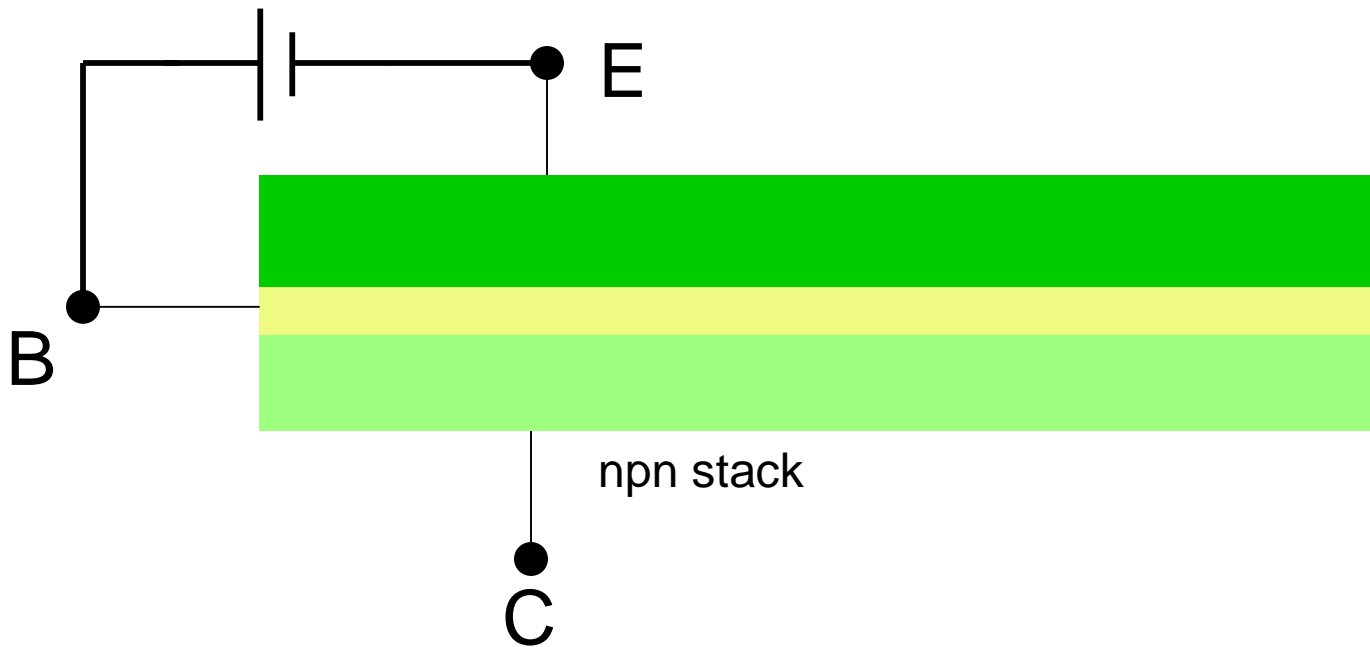

Under **forward bias** current flow into base and out of emitter

Current flow is governed by the diode equation

Carriers in emitter are electrons (majority carriers)


When electrons pass into the base they become minority carriers

Quickly recombine with holes to create holes base region

Dominant current flow in base is holes (majority carriers)

Bipolar Operation

Consider npn transistor

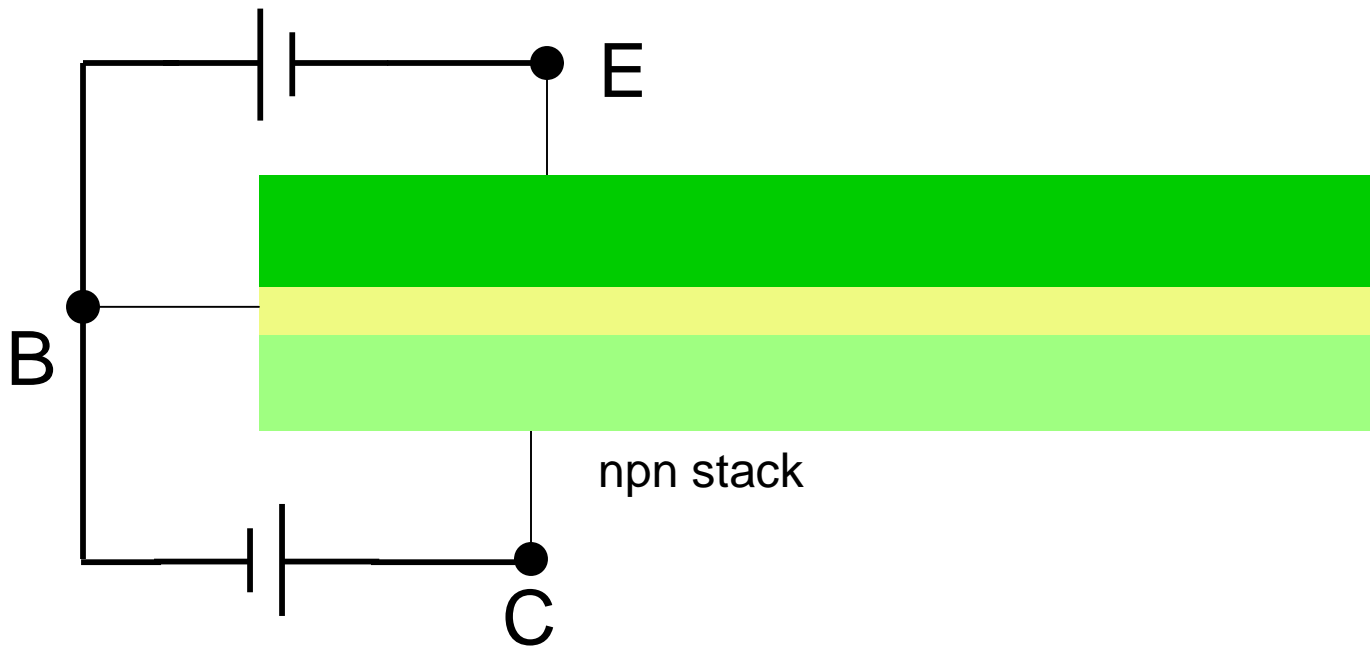

Under forward BE bias and reverse BC bias current flows into base region


Carriers in emitter are electrons (majority carriers)

When electrons pass into the base they become minority carriers

When minority carriers are present in the base they can be attracted to collector

Bipolar Operation


Consider npn transistor

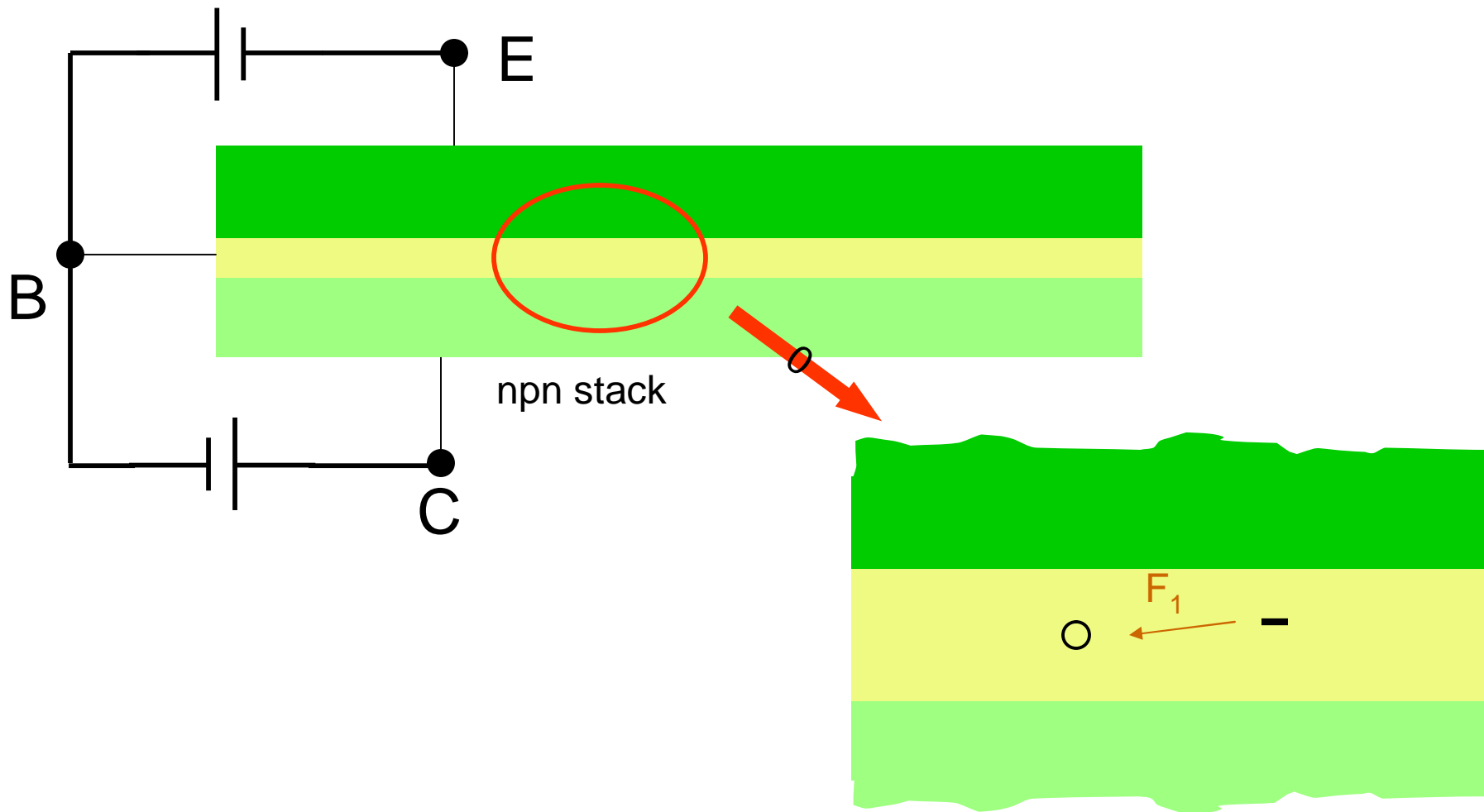

If no force on electron is applied by collector, electron will contribute to base current

Bipolar Operation

Consider npn transistor

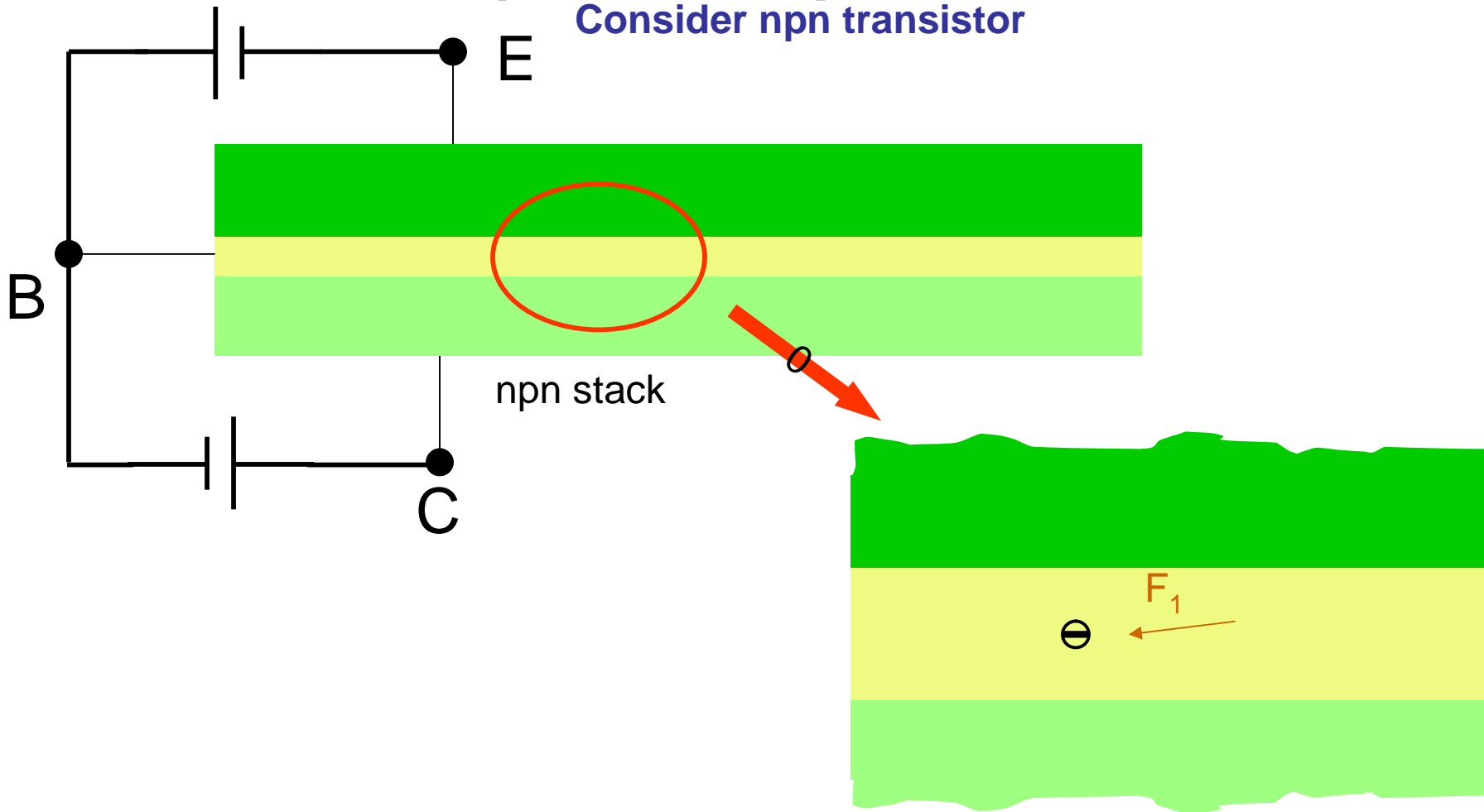


If no force on electron is applied by collector, electron will contribute to base current

Electron will recombine with a hole so dominant current flow in base will be by majority carriers

Bipolar Operation


Consider npn transistor

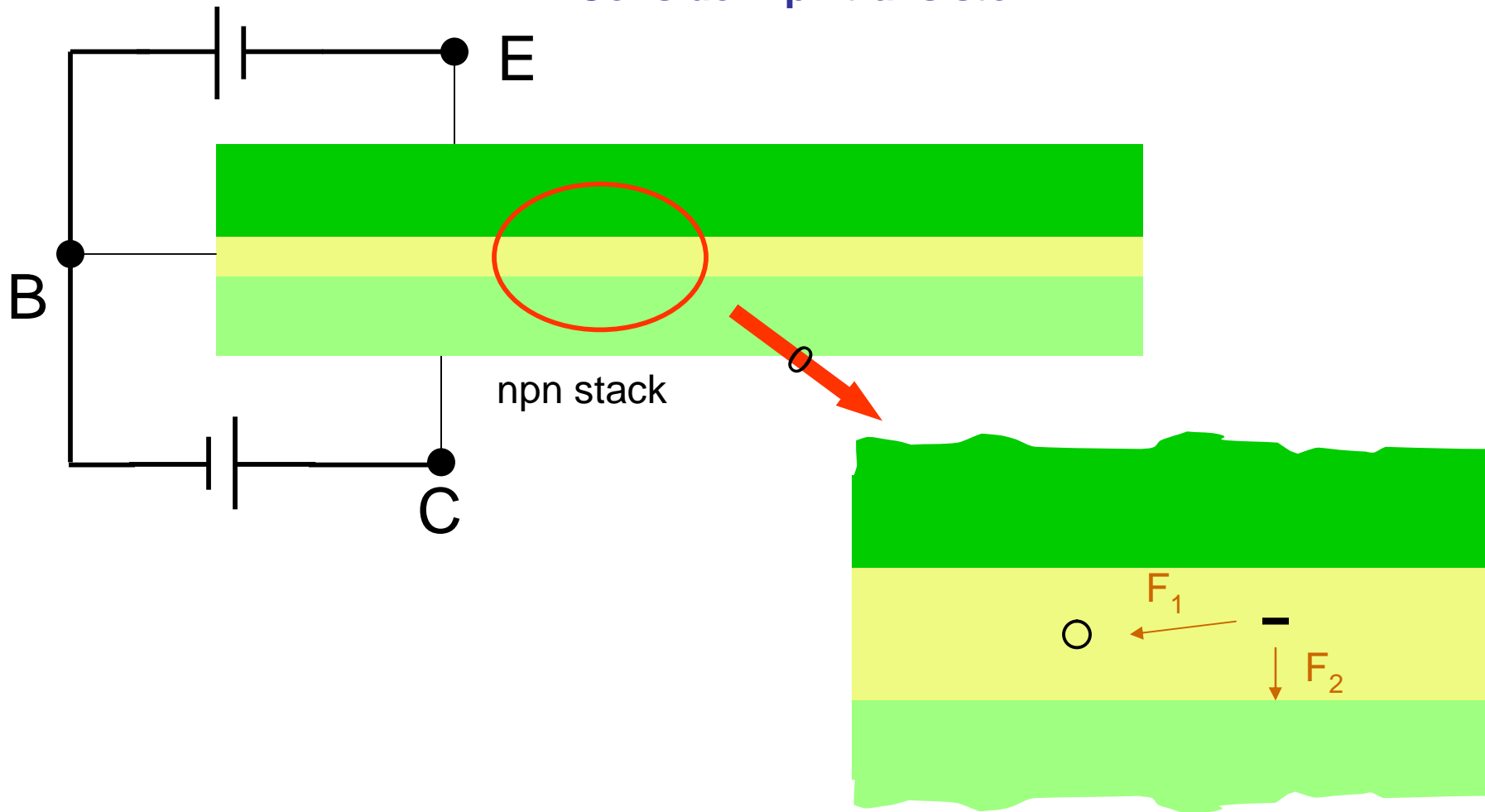

When minority carriers are present in the base they can be attracted to collector with reverse-bias of BC junction and can move across BC junction

Bipolar Operation

Consider npn transistor

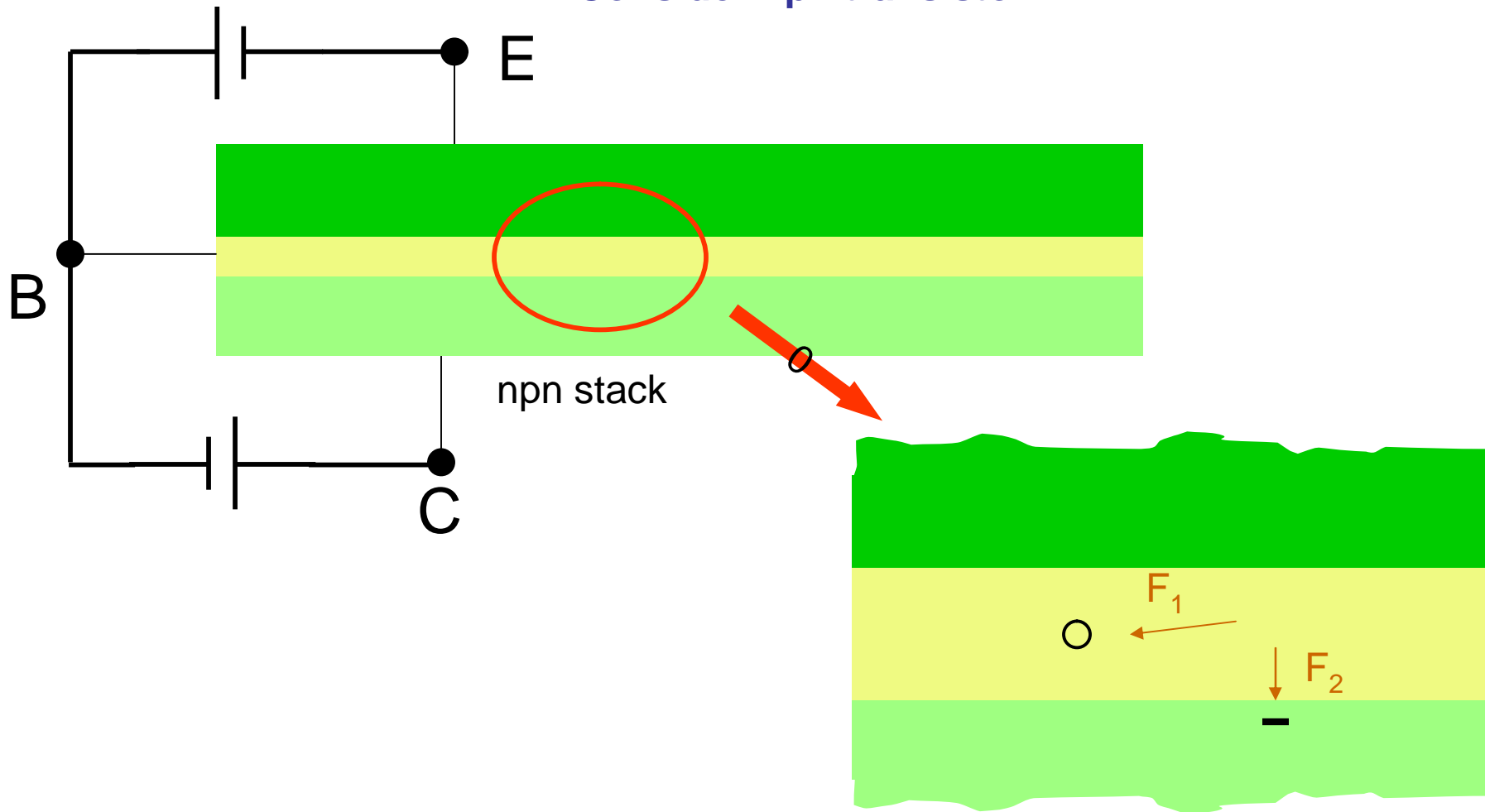


When minority carriers are present in the base they can be attracted to collector with reverse-bias of BC junction and can move across BC junction

Will contribute to collector current flow as majority carriers

Bipolar Operation


Consider npn transistor

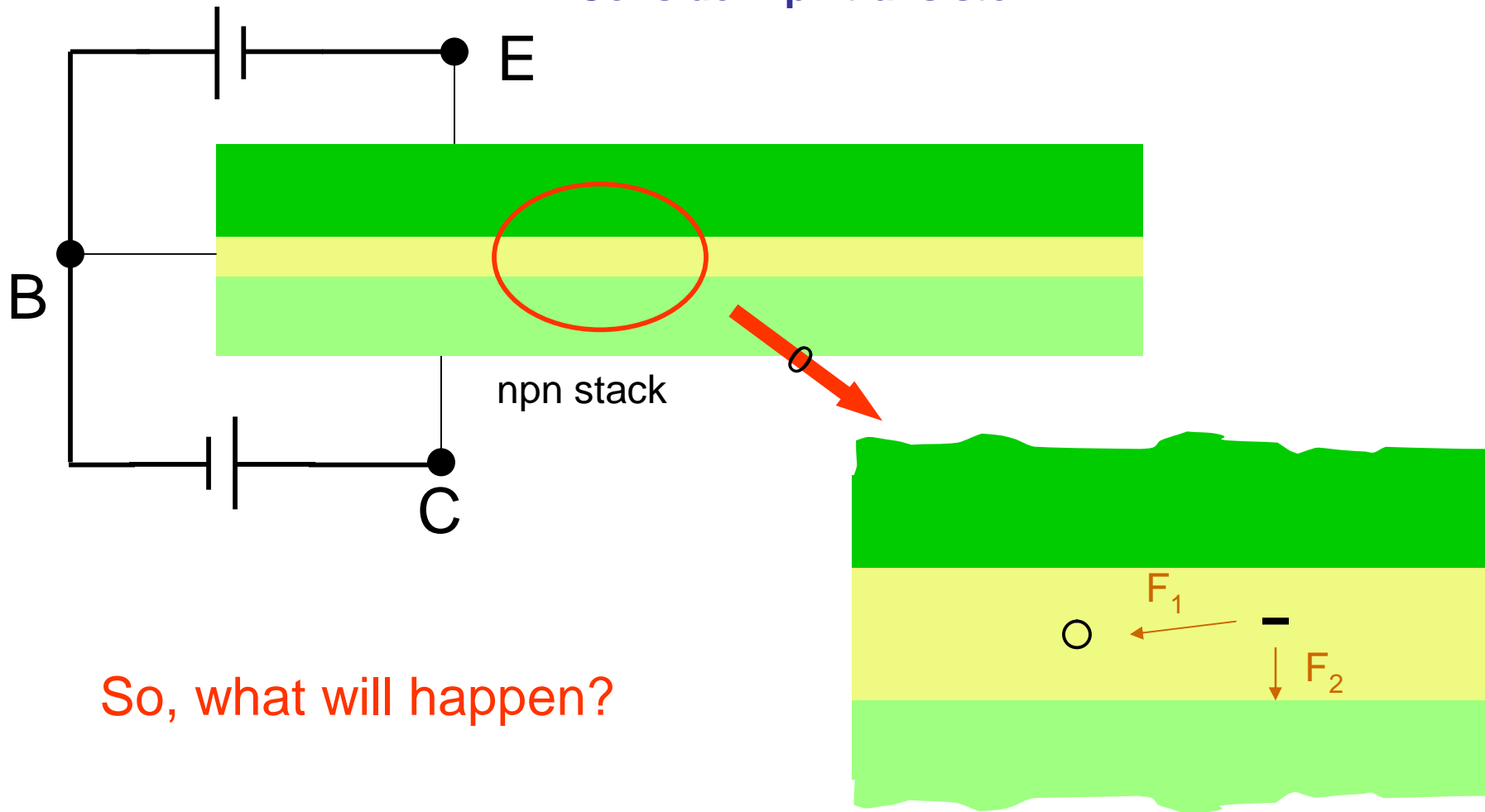

So, what will happen?

Bipolar Operation

Consider npn transistor

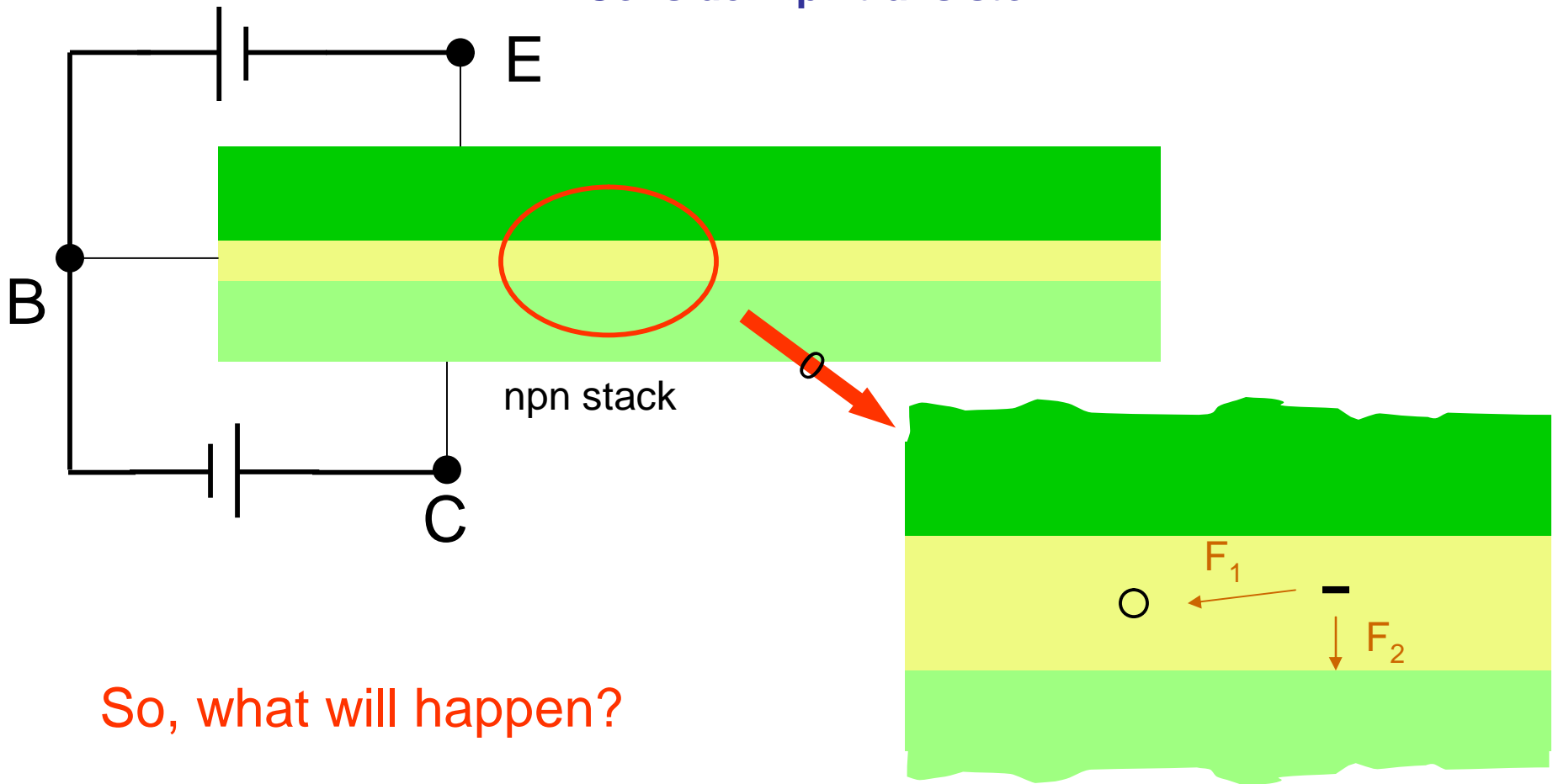


So, what will happen?

Some will recombine with holes and contribute to base current and some will be attracted across BC junction and contribute to collector

Size and thickness of base region and relative doping levels will play key role in percent of minority carriers injected into base contributing to collector current

Bipolar Operation

Consider npn transistor

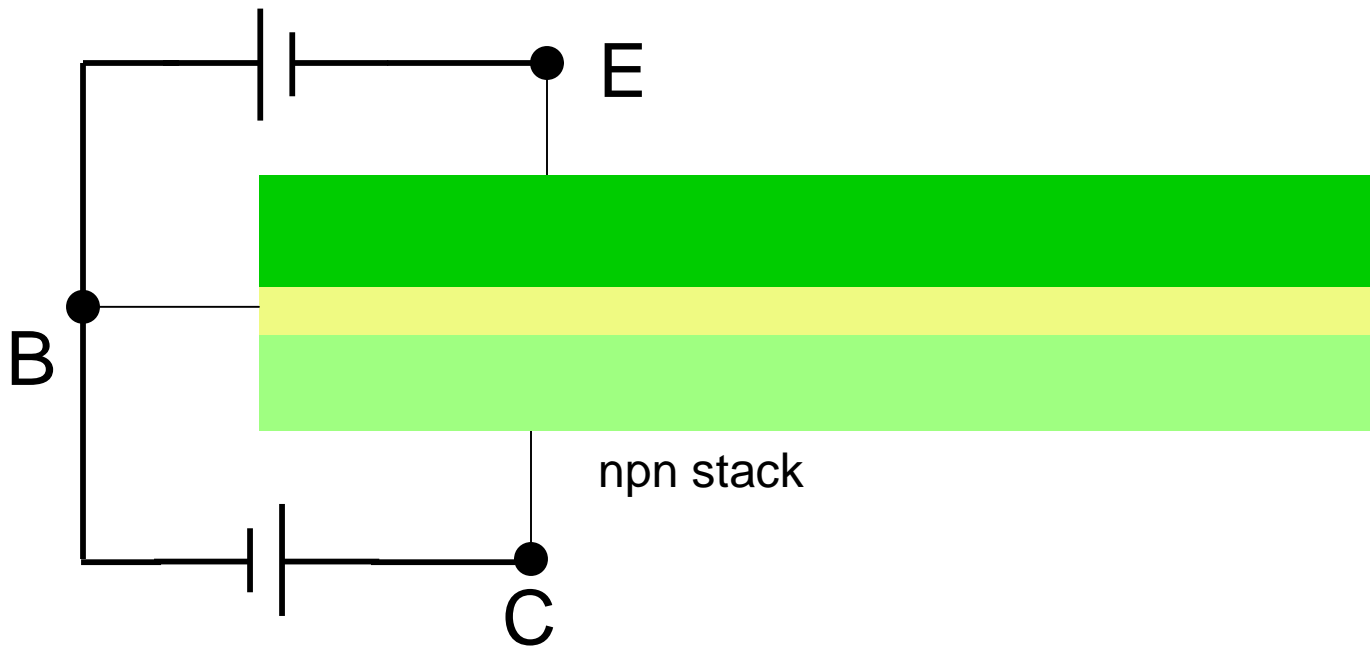

Under forward BE bias and reverse BC bias current flows into base region

Carriers in emitter are electrons (majority carriers)

When electrons pass into the base they become minority carriers


When minority carriers are present in the base they can be attracted to collector

Minority carriers either recombine with holes and contribute to base current

or are attracted into collector region and contribute to collector current

Bipolar Operation

Consider npn transistor

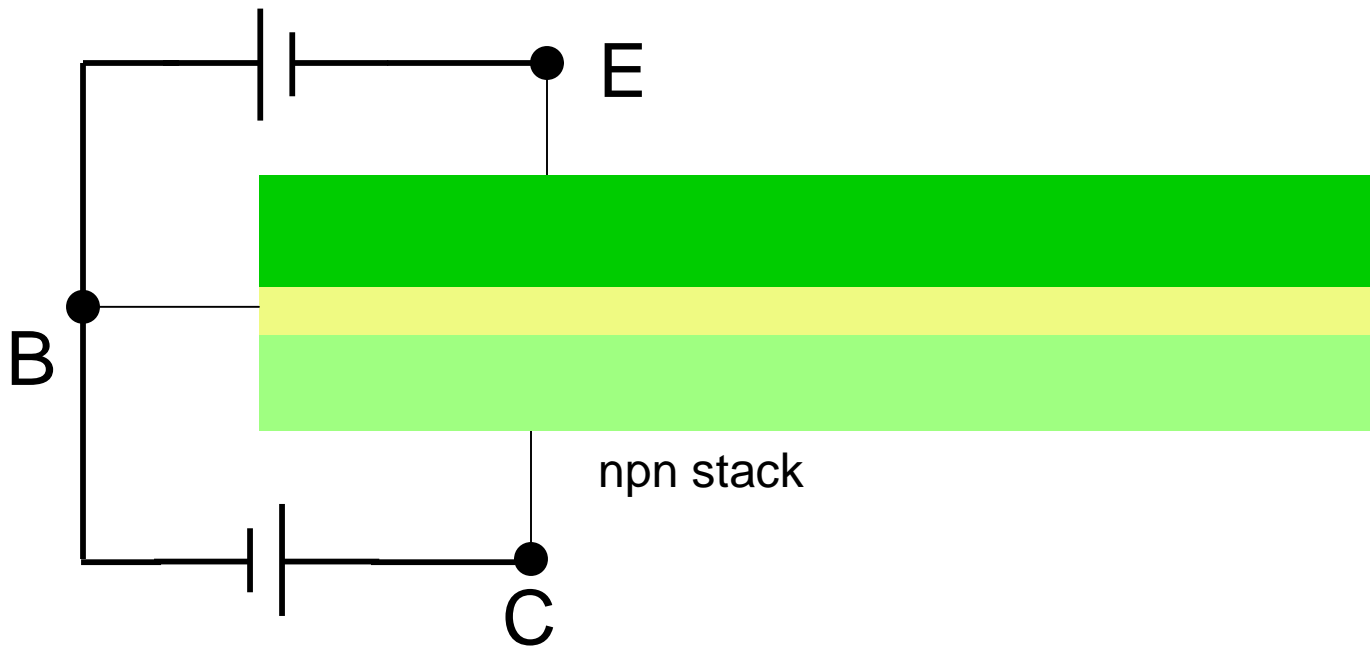

Under forward BE bias and reverse BC bias current flows into base region


Efficiency at which minority carriers injected into base region and contribute to collector current is termed α

α is always less than 1 but for a good transistor, it is very close to 1

For good transistors $.99 < \alpha < .999$

Making the base region very thin makes α large

Bipolar Transistors

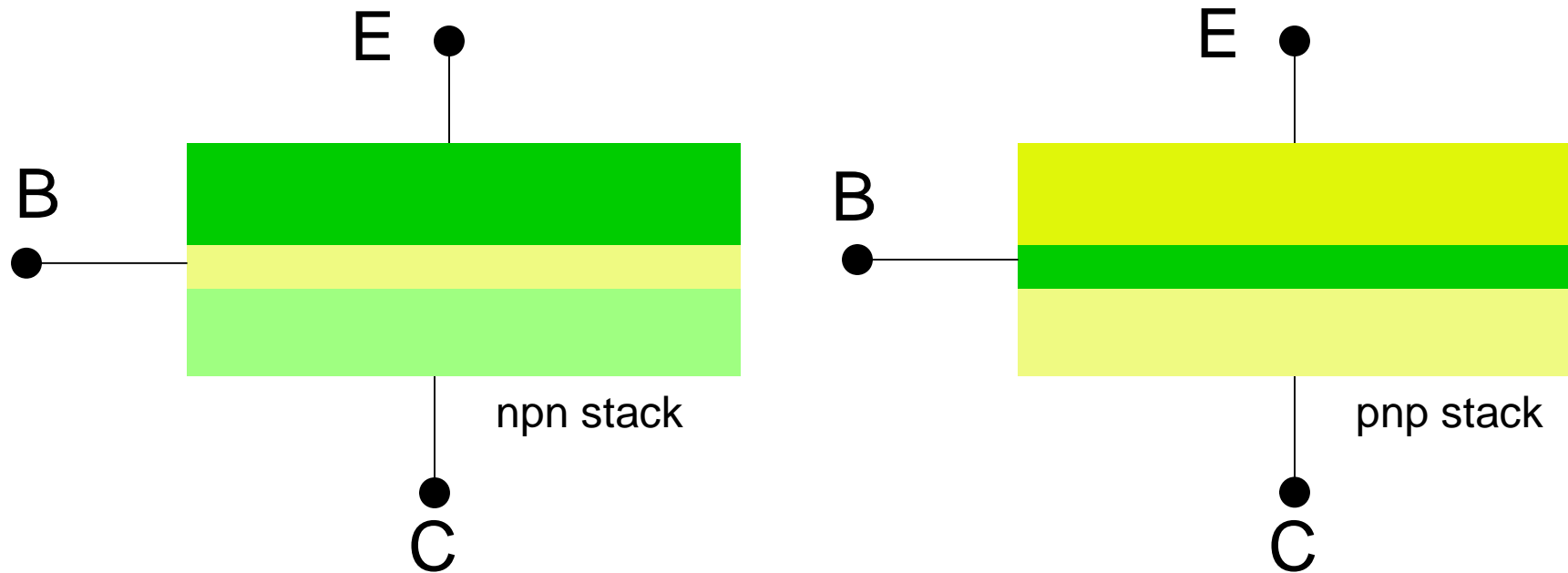


principle of operation of pnp and npn transistors are the same

minority carriers in base of pnp are holes

npn usually have modestly superior properties because mobility of electrons is larger than mobility of holes



Bipolar Operation

Consider npn transistor

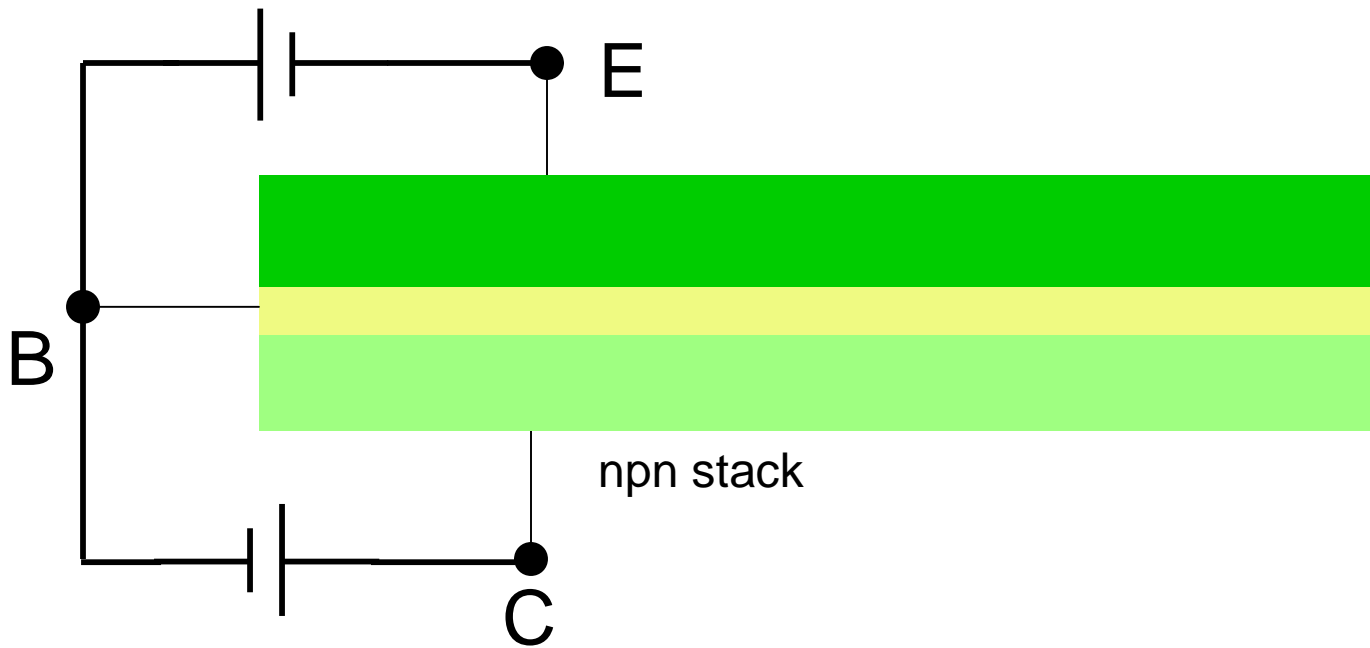

In contrast to MOS devices where current flow in channel is by majority carriers, current flow in the critical base region of bipolar transistors is by minority carriers

Bipolar Operation

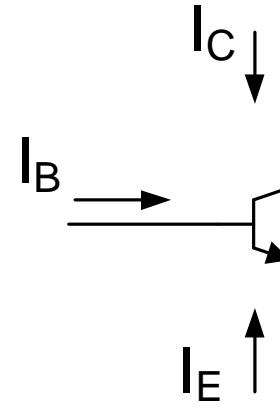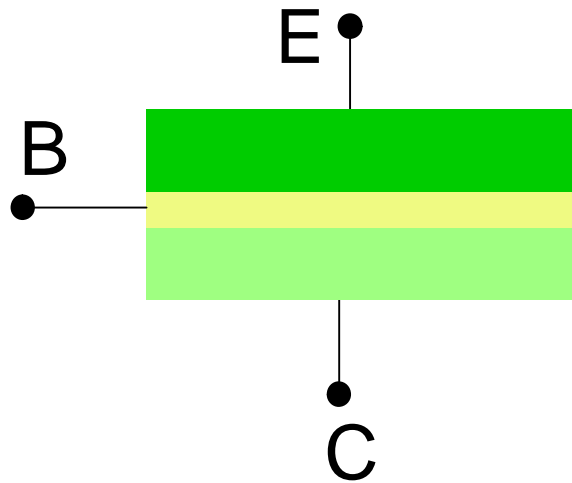

$$\left. \begin{aligned} I_C + I_B &= -I_E \\ I_C &= -\alpha I_E \end{aligned} \right\}$$

$$I_C = \frac{a}{1-a} I_B$$

$$b \stackrel{\text{defn}}{=} \frac{a}{1-a}$$


$$I_C = b I_B$$

β is typically very large

often $50 < \beta < 999$

$$I_C = \beta I_B$$

Bipolar Operation

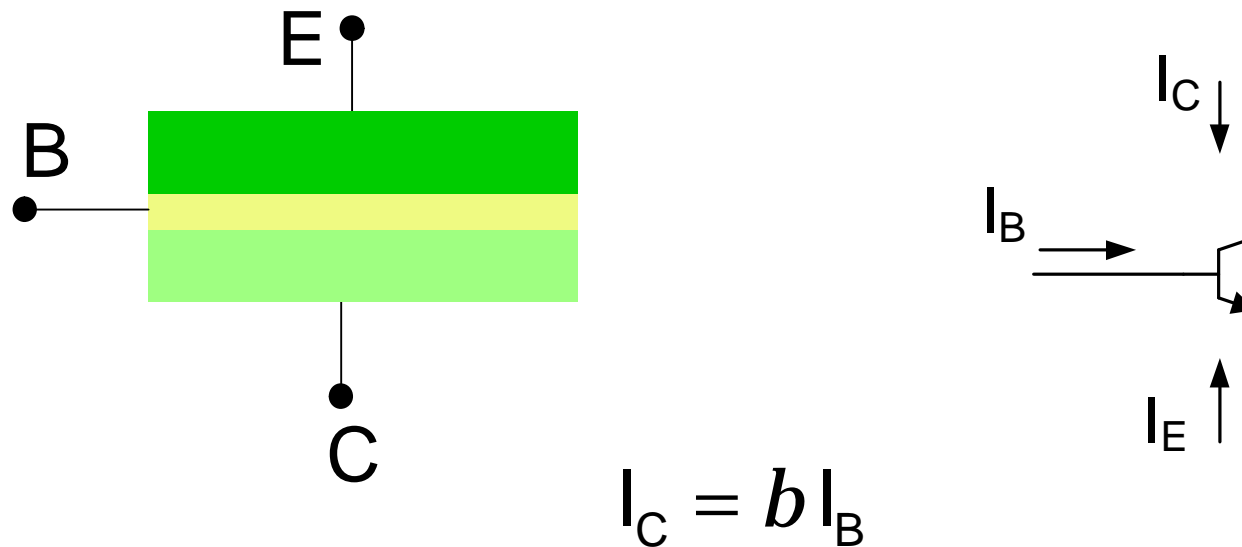

β is typically very large

Bipolar transistor can be thought of a current amplifier with a large current gain



In contrast, MOS transistor is inherently a transconductance amplifier

Current flow in base is governed by the diode equation $I_B = \tilde{I}_S e^{\frac{V_{BE}}{V_t}}$

Collector current thus varies exponentially with V_{BE} $I_C = \beta \tilde{I}_S e^{\frac{V_{BE}}{V_t}}$

$$I_C = \beta I_B$$

Bipolar Operation

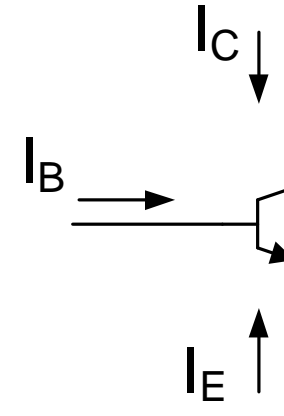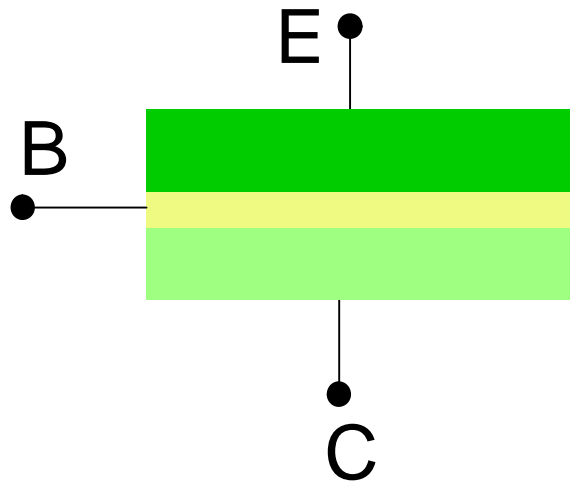

$$I_C = \beta I_B$$

β is typically very large

Collector current thus varies exponentially with V_{BE}

$$I_C = \beta \tilde{I}_S e^{\frac{V_{BE}}{V_t}}$$

This exponential relationship (in contrast to the square-law relationship for the MOSFET) provides a very large gain for the BJT and this property is very useful for many applications !!