

EE 434

Lecture 28

- BJT Models for Computer Simulation
- Basic Linear Applications

Review from last time


Model on junction capacitance

$$C_j = \begin{cases} \frac{C_{j0} A}{\left(1 - \frac{V_{FB}}{\phi_B}\right)^n} \\ 2^n C_{j0} A \left[ \frac{2n V_{FB}}{\phi_B} + (1-n) \right] \end{cases}$$

$$V_{FB} < \frac{\phi_B}{n}$$

$$V_{FB} > \frac{\phi_B}{n}$$

Review from last time

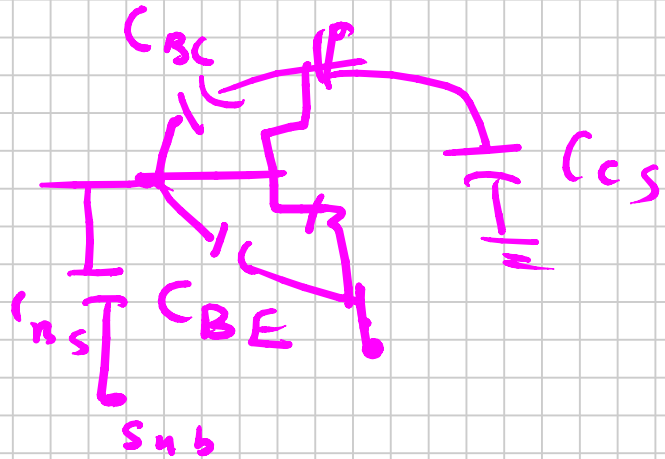

$$C_{BE} = C_{BEJ} + \tau_F g_m$$

$$C_{AC} = \tau_F \frac{I_{CQ}}{kT/e}$$

# Model of BJT for computer simulations

## MOS

- Process Description
- Geometric Parameter Description

## BJT



- Model for a reference device
  - often for several reference devices
- Device scale factor ( $A_E/A_{ER}$ )

$$I_{CR} \approx J_S A_{ER} e^{V_{BE}/V_T}$$

$$I_C = J_S \times A_{ER} e^{V_{BE}/V_T}$$

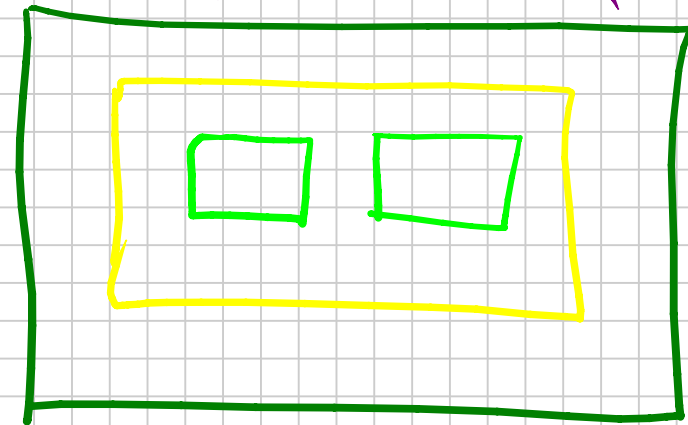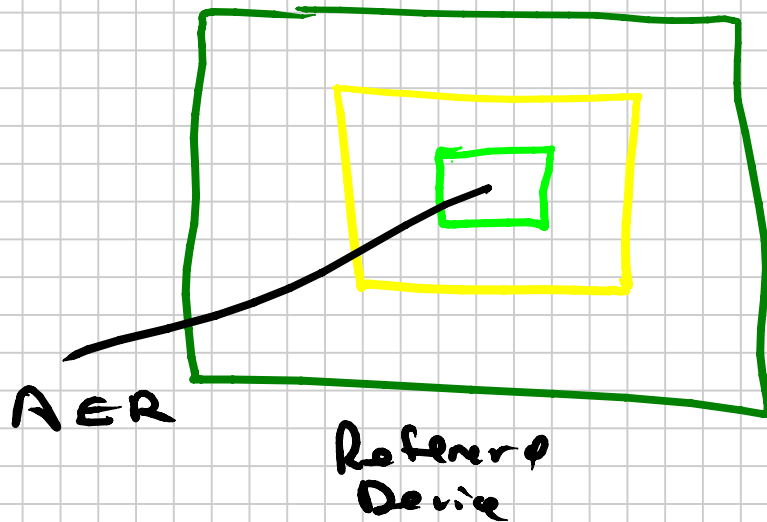
## Issues with this approach:

- all caps are assumed to be part of the model of the reference device
- Base area and collector Area may not scale equally.




Device of interest
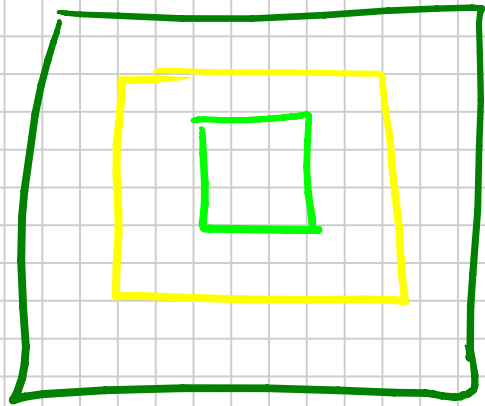
$$A_E = 2 A_{ER}$$
$$A_B \neq 2 A_{BR}$$
$$A_C \neq 2 A_{CR}$$



$\frac{1}{2} A_{ER}$

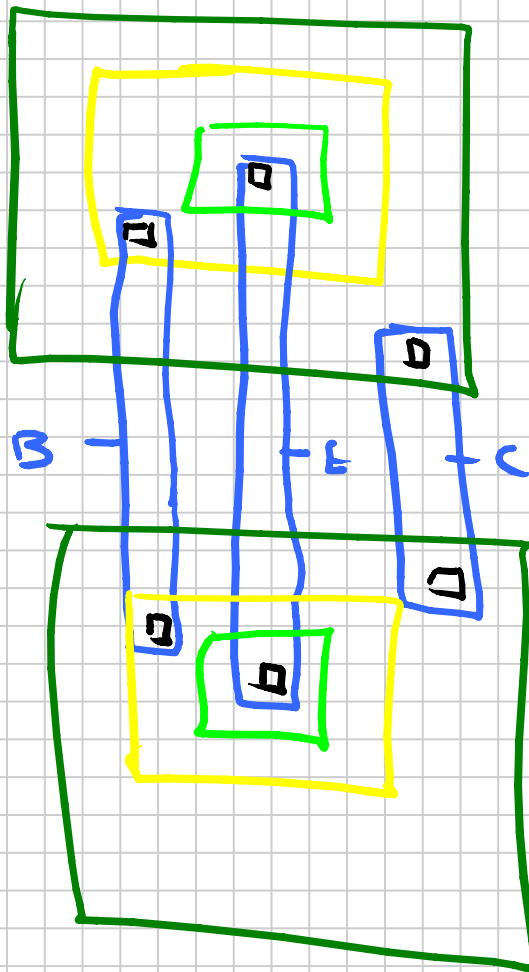





$A_E = 2A_{ER}$

This scaling is not necessarily attractive because area may be considerably larger than that required to simply change  $A_E$  and then make modest changes in  $A_B, A_C$

---

Often see a large number of specific binocular transistors with various layouts and with various  $A_E$ . Designers simply use parallel combination of these devices rather than simply scaling  $A_E$
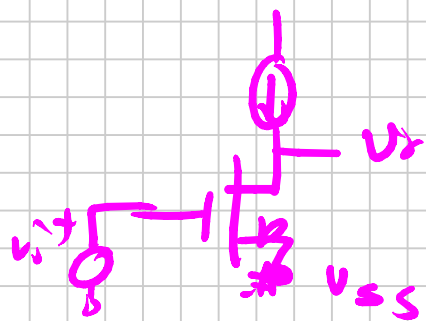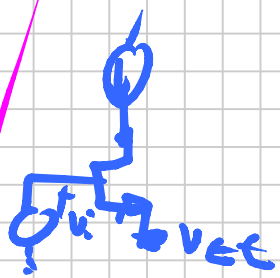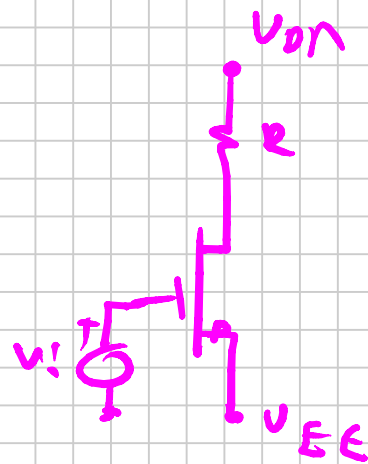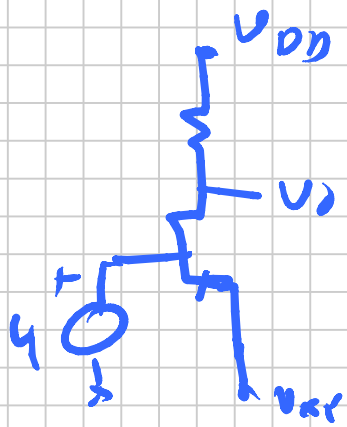
# Basic Linear Applications (MOS & Bipolar Devices)




- Large gains
- $A_{MOS} \ll A_{BJT}$
- Current source was used for biasing



- Whereas in discrete design, current sources are expensive with limited use, in linear integrated design current sources are very inexpensive and widely used.

## Current Source Design

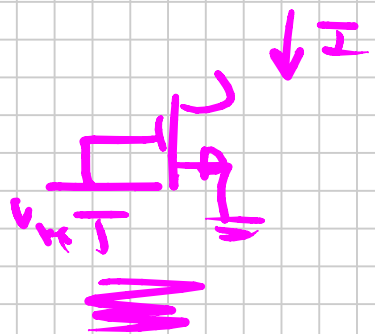


If  $\lambda = 0$

$$I \approx \frac{\mu_0 C_{ox} W}{2L} (V_{DD} - V_T)^2$$

- $I$  is nearly constant

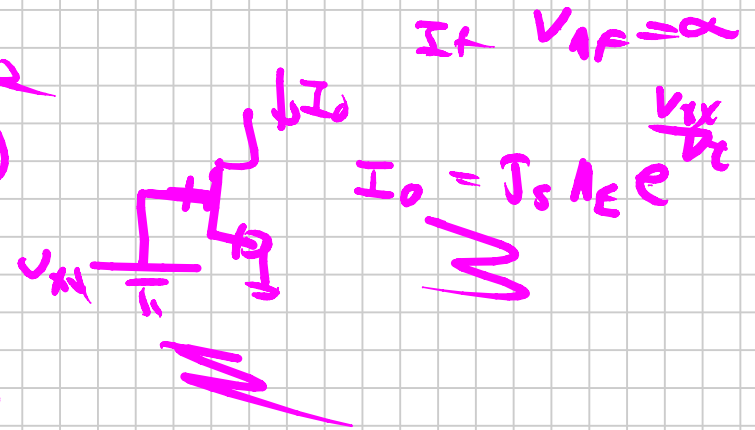
- This simple 1-transistor circuit behaves as a current source



If  $V_{AF} = \alpha$

$$I_0 = I_s A_E e^{\frac{V_{DD}}{V_T}}$$

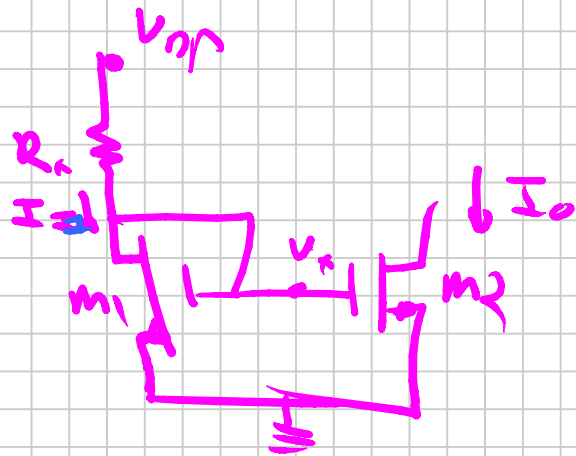Assume  $M_2$  in saturation, neglect  $\lambda$  effects



$$I_o = \frac{\mu C_{ox} W_2}{2L_2} (V_x - V_T)^2$$

$$I_x = \frac{\mu C_{ox} W_1}{2L_1} (V_x - V_T)^2$$


$$\therefore \frac{I_o}{I_x} = \frac{W_2 L_1}{W_1 L_2}$$

$$\text{or } I_o = \left[ \frac{W_2 L_1}{W_1 L_2} \right] I_x$$

- It behaves as a current amplifier with gain  $\frac{W_2 L_1}{W_1 L_2}$
- If  $I_x$  is a constant, this behaves as a current source!

• Since  $\frac{W_1}{W_2}, \frac{L_2}{L_1}$  can be accurately controlled,

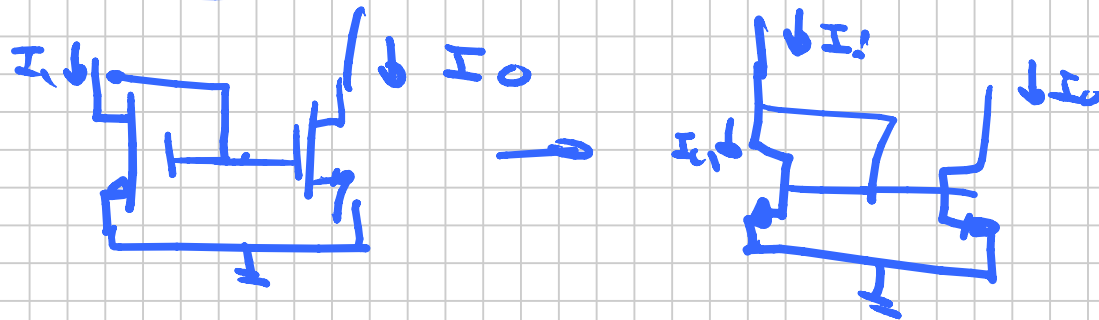the gain of the current amplifier is quite accurate  
(i.e. does not change much with process variations or temp).



If  $\beta$  is very large

$$V_{AF} = \infty$$

$$I_{c1} \approx I_b$$


$$I_{c1} = J_s A_{E1} e^{\frac{V_{BE1}}{V_T}}$$

$$I_{c2} = J_s A_{E2} e^{\frac{V_{BE2}}{V_T}}$$

$$\therefore \frac{I_{c2}}{I_{c1}} = \frac{A_{E2}}{A_{E1}}$$

- serves as a current amplifier
- $A_{E2}/A_{E1}$  is precisely controllable

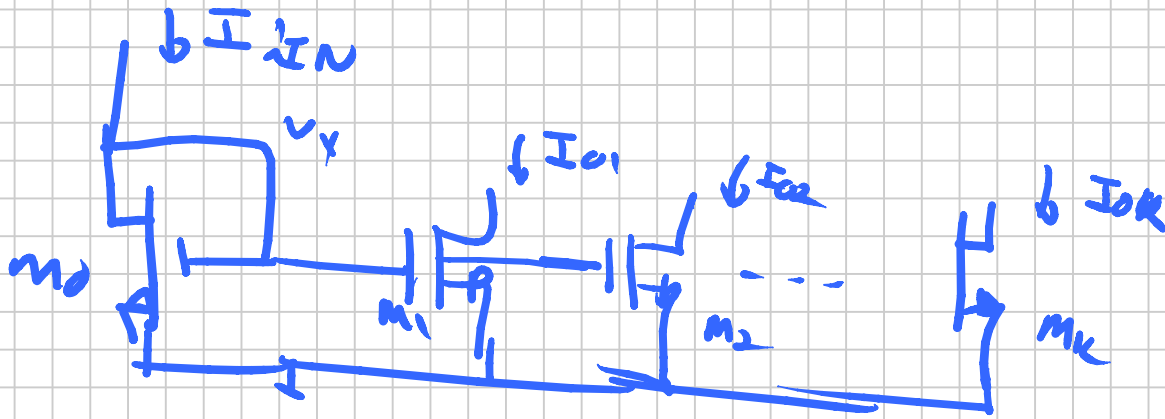Many current sources are often required for building CMOS ICs



$$I_{IN} = \frac{\mu_0 C_{ox} W}{2L} (V_x - V_T)^2$$

$$I_{OK} = \frac{\mu_0 C_{ox} W_K}{2L_K} (V_x - V_T)^2$$

$$I_{OK} \approx I_{IN} \left( \frac{W_K}{W_I} \right) \left( \frac{L_I}{L_K} \right)$$

If  $I_{IN}$  is a dc current, multiple output currents proportional to  $I_{IN}$  can be obtained readily!


# Bipolar Current Sources



$$I_{Oj} = \frac{\beta_{Ej}}{\beta_{E0}} I_1$$

Examples all provided similarly circuits



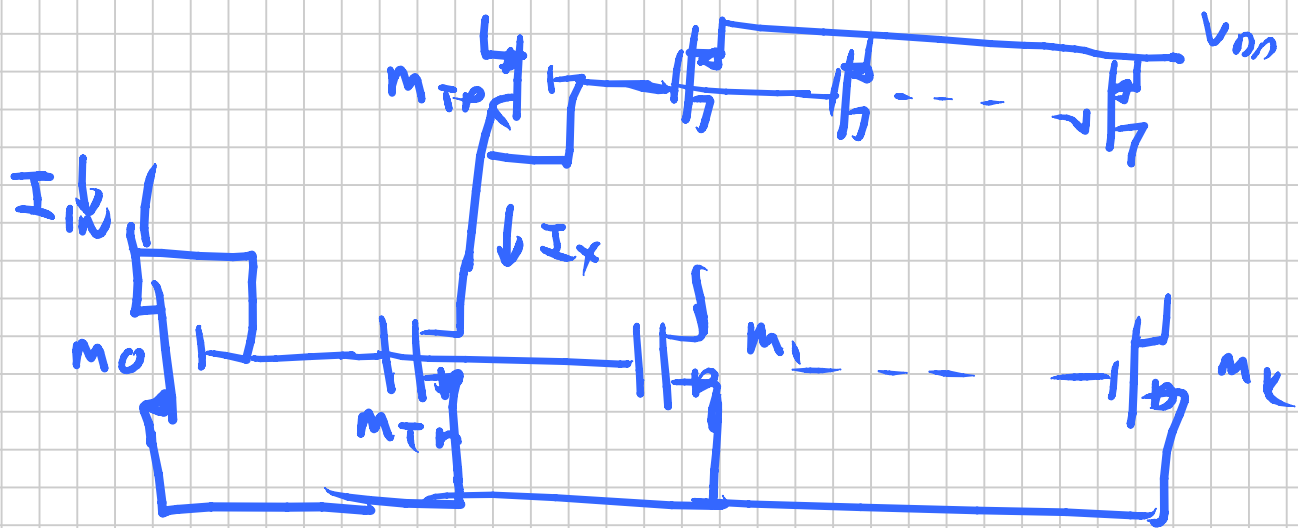

$$I_X = \frac{A_{EI}}{A_{EO}} I_1$$

$$I_{OTK} = \frac{A_{EI}}{A_{EO}} \frac{A_{EK}}{A_{ETP}} I_1$$

∴ - this circuit provides both sourcing and sinking current outputs  
 - require one additional transistor for each additional output