 


EE 434
Lecture 33
Logic Design





Review from last time:

Ask the inverter how it will interpret logic levels





$$V_H = ?$$

$$V_L = ?$$

    

Review from last time:




The two-inverter loop

  

Standard 6-transistor SRAM Cell

Review from last time:

Observation

   

V_H and V_L obtained from the inverter pair transfer characteristics

V_{TRIP} can be obtained from either the inverter or the inverter pair transfer characteristics

Review from last time:

Logic Family Characteristics



What properties of an inverter are necessary for it to be useful for building a two-level logic family

The inverter-pair transfer characteristics must have three unique intersection points with the $V'_{\text{OUT}} = V_{\text{IN}}$ line

What are the logic levels for a given inverter of for a given logic family?

The two extreme intersection points of the inverter-pair transfer characteristics with the $V'_{\text{OUT}} = V_{\text{IN}}$ line

  Transfer characteristics of the static CMOS inverter



Transfer characteristics of the static CMOS inverter

(Neglect effects)

Case 1 M_1 triode, M_2 cutoff

$$I_{D1} = \mu_n C_{oxn} \frac{W_1}{L_1} \left(V_{IN} - V_{Tn} - \frac{V_{OUT}}{2} \right) V_{OUT}$$

$$I_{D2} = 0$$

Equating I_{D1} and $-I_{D2}$ we obtain:

$$0 = \mu_n C_{oxn} \frac{W_1}{L_1} \left(V_{IN} - V_{Tn} - \frac{V_{OUT}}{2} \right) V_{OUT}$$

It can be shown that the first solution will not verify, thus

$$V_{OUT} = 0$$

valid for:


$$V_{GS1} \geq V_{Tn}$$

thus, valid for:

$$V_{IN} \geq V_{Tn}$$

$$V_{DS1} < V_{GS1} - V_{Tn}$$

$$V_{GS2} \geq V_{Tp}$$

 

$$V_{OUT} < V_{IN} - V_{Tn}$$


$$V_{IN} - V_{DD} \geq V_{Tp}$$

Transfer characteristics of the static CMOS inverter

(Neglect effects)

Case 1 M_1 triode, M_2 cutoff

$$V_{\text{OUT}} = 0$$

 


Transfer characteristics of the static CMOS inverter

(Neglect effects)

Case 1 M_1 triode, M_2 cutoff


$$V_{\text{OUT}} = 0$$

 

Transfer characteristics of the static CMOS inverter

(Neglect effects)


Partial solution:

 

Transfer characteristics of the static CMOS inverter

(Neglect effects)

Case 2 M_1 triode, M_2 sat

 

Transfer characteristics of the static CMOS inverter

(Neglect effects)

Case 2 M_1 triode, M_2 sat

$$I_{D1} = \mu_n C_{OxN} \frac{W_1}{L_1} \left(V_{IN} - V_{Tn} - \frac{V_{OUT}}{2} \right) V_{OUT}$$

$$I_{D2} = -\frac{\mu_p C_{OxP}}{2} \frac{W_2}{L_2} (V_{IN} - V_{DD} - V_{Tp})^2$$

Equating I_{D1} and $-I_{D2}$ we obtain:


$$\frac{\mu_p C_{OxP}}{2} \frac{W_2}{L_2} (V_{IN} - V_{DD} - V_{Tp})^2 = \mu_n C_{OxN} \frac{W_1}{L_1} \left(V_{IN} - V_{Tn} - \frac{V_{OUT}}{2} \right) V_{OUT}$$

valid for:

$$V_{GS1} \geq V_{Tn} \quad V_{DS1} < V_{GS1} - V_{Tn} \quad V_{GS2} \leq V_{Tp} \quad V_{DS2} \leq V_{GS2} - V_{Tp}$$

thus, valid for:

 
$$V_{IN} \geq V_{Tn} \quad V_{OUT} < V_{IN} - V_{Tn} \quad V_{IN} - V_{DD} \leq V_{Tp} \quad V_{OUT} - V_{DD} \leq V_{IN} - V_{DD} - V_{Tp}$$



Transfer characteristics of the static CMOS inverter

(Neglect effects)


Case 2 M_1 triode, M_2 sat

 

Transfer characteristics of the static CMOS inverter


(Neglect effects)

Case 2 M_1 triode, M_2 sat

 

Transfer characteristics of the static CMOS inverter


Partial solution:

 

Transfer characteristics of the static CMOS inverter

(Neglect effects)

Case 3 M_1 sat, M_2 sat

 

Transfer characteristics of the static CMOS inverter

(Neglect effects)

Case 3 M_1 sat, M_2 sat

$$I_{D1} = \frac{\mu_n C_{OXn}}{2} \frac{W_1}{L_1} (V_{IN} - V_{Tn})^2$$

$$I_{D2} = \frac{\mu_p C_{OXp}}{2} \frac{W_2}{L_2} (V_{IN} - V_{DD} - V_{Tp})^2$$

Equating I_{D1} and $-I_{D2}$ we obtain:


$$\frac{\mu_p C_{OXp}}{2} \frac{W_2}{L_2} (V_{IN} - V_{DD} - V_{Tp})^2 = \frac{\mu_n C_{OXn}}{2} \frac{W_1}{L_1} (V_{IN} - V_{Tn})^2$$

Which can be rewritten as:

$$\sqrt{\frac{\mu_p C_{OXp}}{2} \frac{W_2}{L_2}} (V_{DD} + V_{Tp} - V_{IN}) = \sqrt{\frac{\mu_n C_{OXn}}{2} \frac{W_1}{L_1}} (V_{IN} - V_{Tn})$$

Which can be simplified to:
 
$$V_{IN} = \frac{(V_{Tn}) \sqrt{\frac{\mu_n C_{OXn}}{2} \frac{W_1}{L_1}} + (V_{DD} + V_{Tp}) \sqrt{\frac{\mu_p C_{OXp}}{2} \frac{W_2}{L_2}}}{\sqrt{\frac{\mu_n C_{OXn}}{2} \frac{W_1}{L_1}} + \sqrt{\frac{\mu_p C_{OXp}}{2} \frac{W_2}{L_2}}}$$



This is a vertical line

Transfer characteristics of the static CMOS inverter

(Neglect effects)

Case 3 M_1 sat, M_2 sat

$$V_{IN} = \frac{(V_{Tn}) \sqrt{\frac{\mu_n C_{Ox_n}}{2} \frac{W_1}{L_1}} + (V_{DD} + V_{Tp}) \sqrt{\frac{\mu_p C_{Ox_p}}{2} \frac{W_2}{L_2}}}{\sqrt{\frac{\mu_n C_{Ox_n}}{2} \frac{W_1}{L_1}} + \sqrt{\frac{\mu_p C_{Ox_p}}{2} \frac{W_2}{L_2}}}$$

Since $C_{Ox_n} \approx C_{Ox_p} = C_{Ox}$ this can be simplified to:

$$V_{IN} = \frac{(V_{Tn}) \sqrt{\frac{W_1}{L_1}} + (V_{DD} + V_{Tp}) \sqrt{\frac{\mu_p W_2}{\mu_n L_2}}}{\sqrt{\frac{W_1}{L_1}} + \sqrt{\frac{\mu_p W_2}{\mu_n L_2}}}$$

valid for:

$$V_{GS1} \geq V_{Tn}$$

$$V_{DS1} \geq V_{GS1} - V_{Tn}$$

$$V_{GS2} \leq V_{Tp}$$

$$V_{DS2} \leq V_{GS2} - V_{T2}$$


thus, valid for:

$$V_{IN} \geq V_{Tn}$$

$$V_{OUT} \geq V_{IN} - V_{Tn}$$

$$V_{IN} - V_{DD} \leq V_{Tp}$$

 
$$V_{OUT} - V_{DD} \leq V_{IN} - V_{DD} - V_{Tp}$$



Transfer characteristics of the static CMOS inverter

(Neglect effects)


Case 3 M_1 sat, M_2 sat

 

Transfer characteristics of the static CMOS inverter

(Neglect effects)


Partial solution:

 

Transfer characteristics of the static CMOS inverter

(Neglect effects)


Case 3 M_1 sat, M_2 sat

 

Transfer characteristics of the static CMOS inverter

(Neglect effects)

Case 4 M_1 sat, M_2 triode

 

Transfer characteristics of the static CMOS inverter

(Neglect effects)

Case 4 M_1 sat, M_2 triode

$$I_{D1} = \frac{\mu_n C_{OxN}}{2} \frac{W_1}{L_1} (V_{IN} - V_{Tn})^2$$

$$I_{D2} = -\mu_p C_{OxP} \frac{W_2}{L_2} \left(V_{IN} - V_{DD} - V_{Tp} - \frac{V_{OUT} - V_{DD}}{2} \right) \bullet (V_{OUT} - V_{DD})$$

Equating I_{D1} and $-I_{D2}$ we obtain:


$$\frac{\mu_n C_{OxN}}{2} \frac{W_1}{L_1} (V_{IN} - V_{Tn})^2 = \mu_p C_{OxP} \frac{W_2}{L_2} \left(V_{IN} - V_{DD} - V_{Tp} - \frac{V_{OUT} - V_{DD}}{2} \right) \bullet (V_{OUT} - V_{DD})$$

valid for:

$$V_{GS1} \geq V_{Tn} \quad V_{DS1} \geq V_{GS1} - V_{Tn} \quad V_{GS2} \leq V_{Tp} \quad V_{DS2} > V_{GS2} - V_{Tp}$$

thus, valid for:

 
$$V_{IN} \geq V_{Tn} \quad V_{OUT} \geq V_{IN} - V_{Tn} \quad V_{IN} - V_{DD} \leq V_{Tp} \quad V_{OUT} - V_{DD} > V_{IN} - V_{DD} - V_{Tp}$$



Transfer characteristics of the static CMOS inverter

(Neglect effects)


Case 4 M_1 sat, M_2 triode

 

Transfer characteristics of the static CMOS inverter

(Neglect effects)


Case 4 M_1 sat, M_2 triode

 

Transfer characteristics of the static CMOS inverter

(Neglect effects)


Partial solution:

 

Transfer characteristics of the static CMOS inverter

(Neglect effects)

Case 4 M_1 cutoff, M_2 triode

 

Transfer characteristics of the static CMOS inverter

(Neglect effects)

Case 5 M_1 cutoff, M_2 triode

$$I_{D1} = 0$$

$$I_{D2} = -\mu_p C_{OxP} \frac{W_2}{L_2} \left(V_{IN} - V_{DD} - V_{Tp} - \frac{V_{OUT} - V_{DD}}{2} \right) \bullet (V_{OUT} - V_{DD})$$

Equating I_{D1} and $-I_{D2}$ we obtain:

$$\mu_p C_{OxP} \frac{W_2}{L_2} \left(V_{IN} - V_{DD} - V_{Tp} - \frac{V_{OUT} - V_{DD}}{2} \right) \bullet (V_{OUT} - V_{DD}) = 0$$

valid for:

$$V_{GS1} < V_{Tn}$$

$$V_{GS2} \leq V_{Tp}$$


$$V_{DS2} > V_{GS2} - V_{T2}$$

thus, valid for:

$$V_{IN} < V_{Tn}$$

$$V_{IN} - V_{DD} \leq V_{Tp}$$

 
$$V_{OUT} - V_{DD} > V_{IN} - V_{DD} - V_{Tp}$$



Transfer characteristics of the static CMOS inverter

(Neglect effects)


Case 5 M_1 cutoff, M_2 triode

 

Transfer characteristics of the static CMOS inverter


(Neglect effects)

Case 5 M_1 cutoff, M_2 triode

 


Transfer characteristics of the static CMOS inverter

(Neglect effects)

 


Transfer characteristics of the static CMOS inverter

(Neglect effects)

 

Transfer characteristics of the static CMOS inverter




(Neglect effects)

 


From Case 3 analysis:

$$V_{IN} = \frac{(V_{Tn}) + (V_{DD} + V_{Tp}) \sqrt{\frac{\mu_p}{\mu_n} \frac{W_2}{W_1} \frac{L_1}{L_2}}}{1 + \sqrt{\frac{\mu_p}{\mu_n} \frac{W_2}{W_1} \frac{L_1}{L_2}}}$$

   Inverter Transfer Characteristics of Inverter Pair



 Extension of Basic CMOS Inverter to Multiple-Input Gates




| A | B | Y |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |


Truth Table

Performs as a 2-input NOR Gate

 Can be easily extended to an n-input NOR Gate



 Extension of Basic CMOS Inverter to Multiple-Input Gates




| A | B | Y |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |



Truth Table

Performs as a 2-input NAND Gate

 Can be easily extended to an n-input NAND Gate






Static CMOS Logic Family

  


Observe PUN is p-channel, PDN is n-channel

Static CMOS Logic Family

   


n-channel PDN and p-channel PUN

General Logic Family

 


p-channel PUN
n-channel PDN

 


Arbitrary PUN
and PDN


Other CMOS Logic Families

 

Enhancement
Load NMOS


 


Enhancement Load
Pseudo-NMOS

 




Depletion
Load NMOS

Other CMOS Logic Families

  


- High and low swings are reduced
- Response time is slow on LH output transitions
- Static Power Dissipation Large when V_{OUT} is low
- Very economical process
- Termed “ratio logic”
- Compact layout (no wells !)

Other CMOS Logic Families

   


- Multiple-input gates require single transistor for each additional input
- Still useful if many inputs are required (static power does not increase with k)

Other CMOS Logic Families


 


Enhancement Load
Pseudo-NMOS

 





- High and low swings are reduced
- Response time is slow on LH output transitions
- Static Power Dissipation Large when V_{OUT} is low
- Termed “ratio” logic

Other CMOS Logic Families

  


- $V_{TD} < 0$
- Low swing is reduced
 - Static Power Dissipation Large when V_{OUT} is low
 - Very economical process
 - Termed “ratio” logic
 - Compact layout (no wells !)
 - Dominant MOS logic until about 1985
 - Depletion device not available in most processes today

Other CMOS Logic Families

    



- Reduced $V_H - V_L$
- Device sizing critical for even basic operation
- Shallow slope at V_{TRIP}

Other CMOS Logic Families

 


- Reduced $V_H - V_L$
- Device sizing critical for even basic operation
- Shallow slope at V_{TRIP}

Other CMOS Logic Families

  

- Reduced $V_H - V_L$
- Device sizing critical for even basic operation
- Shallow slope at V_{TRIP}

 Static Power Dissipation in Static CMOS Family



When V_{OUT} is Low, $I_{D1}=0$

When V_{OUT} is High, $I_{D2}=0$

Thus, $P_{STATIC}=0$

This is a key property of the static CMOS Logic Family and is the major reason Static CMOS Logic is so dominant


It can be shown that this zero static power dissipation property can be preserved if the PUN is comprised of n-channel devices, the PDN is comprised of n-channel devices and they are never both driven into the conducting states at the same time

Static Power Dissipation in Ratio Logic Families

 Example:

Assume $V_{DD}=5V$

$V_T=1V$, $C_{OX}=10^{-4}A/V^2$, $W_1/L_1=1$ and M_2 sized so that $V_L=V_{Th}$



Observe:

$$V_H = V_{DD} - V_{Th}$$

If $V_{IN}=V_H$, $V_{OUT}=V_L$ so

$$I_{D1} = \frac{\mu C_{ox} W_1}{L_1} \left(V_{GS1} - V_T - \frac{V_{DS1}}{2} \right) V_{DS1}$$

$$I_{D1} = 10^{-4} \left(5 - 1 - 1 - \frac{1}{2} \right) \bullet 1 = 0.25mA$$


$$P_L = (5V)(0.25mA) = 1.25mW$$

Static Power Dissipation in Ratio Logic Families

 Example:

Assume $V_{DD}=5V$

$V_T=1V$, $C_{OX}=10^{-4}A/V^2$, $W_1/L_1=1$ and M_2 sized so that $V_L=V_{Th}$



$$P_L = (5V)(0.25mA) = 1.25mW$$


If a circuit has 100,000 gates and half of them are in the $V_{OUT}=V_L$ state, the static power dissipation will be

Static Power Dissipation in Ratio Logic Families

 Example:

Assume $V_{DD}=5V$

$V_T=1V$, $C_{OX}=10^{-4}A/V^2$, $W_1/L_1=1$ and M_2 sized so that $V_L=V_{Th}$




$$P_L = (5V)(0.25mA) = 1.25mW$$

If a circuit has 100,000 gates and half of them are in the $V_{OUT}=V_L$ state, the static power dissipation will be

$$P_{STATIC} = \frac{1}{2} 10^5 \bullet 1.25mW = \mathbf{62.5W}$$


This power dissipation is way too high and would be even larger in circuits with 100 million or more gates – the level of integration common in SoC circuits today

Propagation Delay in Static CMOS Family

 

Switch-level model of Static CMOS
inverter (neglecting diffusion parasitics)

Propagation Delay in Static CMOS Family

 

Switch-level model of Static CMOS inverter (neglecting diffusion parasitics)