

EE 434

Lecture 35⁶


~~Device Sizing~~

Propagation Delay in Logic Circuits

Review from last time

Device Sizing

Sizing Strategies

 

- Minimum Size
- Fixed V_{TRIP}
- Equal rise-fall times
(equal worst-case rise and fall times)
- Minimum power dissipation
- Minimum time required to drive a given load
- Minimum input capacitance

4 design variables $\{W_1, W_2, L_1, L_2\}$

Invariably will select $L_1 = L_2 = L_{MIN}$

2 degrees of freedom $\{W_1, W_2\}$


Review from last time

Device Sizing

Equal Rise/Fall Device Sizing Strategy

-- (same as $V_{TRIP}=V_{DD}/2$ in typical process considered in example)

Assume $\mu_n/\mu_p=3$ $L_n=L_p=L_{MIN}$

 

$$W_n=W_{MIN}, \quad W_p=3W_n$$

$$C_{IN}=C_{OX} (W_{MIN}L_{MIN}+3W_{MIN}L_{MIN}) = 4C_{OX} W_{MIN}L_{MIN}$$

$$V_{OUT} \quad t_{HL}=t_{LH}=\frac{1}{R_{PD}C_L}$$


$$t_{PROP}=t_{HL}+t_{LH}=\frac{2}{R_{PD}C_L}$$

Review from last time

Device Sizing

The reference inverter

 Assume $\mu_n/\mu_p=3$ $L_n=L_p=L_{MIN}$ $W_n=W_{MIN}$, $W_p=3W_n$




$$C_{REF} = C_{IN} = 4C_{OX} W_{MIN} L_{MIN}$$

$$t_{PROP} = t_{HL} + t_{LH} = \frac{2}{R_{PD} C_L}$$

Review from last time

Device Sizing

 The reference inverter pair Assume $\mu_n/\mu_p=3$ $L_n=L_p=L_{MIN}$ $W_n=W_{MIN}$, $W_p=3W_n$



$$C_{REF} = 4C_{OX} W_{MIN} L_{MIN}$$

$$C_{L1} = C_{REF} = 4C_{OX} W_{MIN} L_{MIN}$$

$$R_{PDREF} = \frac{L_{MIN}}{\mu_n C_{OX} W_{MIN} (V_{DD} - V_{Tn})} \stackrel{V_{Tn}=.2V_{DD}}{=} \frac{L_{MIN}}{\mu_n C_{OX} W_{MIN} (0.8V_{DD})}$$

$$t_{REF} = t_{HLREF} + t_{LHREF} = \frac{2}{R_{PDREF} C_{REF}}$$

$$C_{IN} = C_{REF} = 4C_{OX} W_{MIN} L_{MIN}$$


Review from last time

Device Sizing

Equal Rise/Fall Device Sizing Strategy

-- (same as $V_{TRIP} = V_{DD}/2$ in typical process considered in example)

 
Assume $\mu_n/\mu_p = 3$ $L_n = L_p = L_{MIN}$



INV

$$W_n = W_{MIN}, W_p = 3W_{MIN}$$


$$C_{IN} = C_{REF}$$

 

k-input NOR

$$W_n = W_{MIN}, W_p = 3kW_{MIN}$$
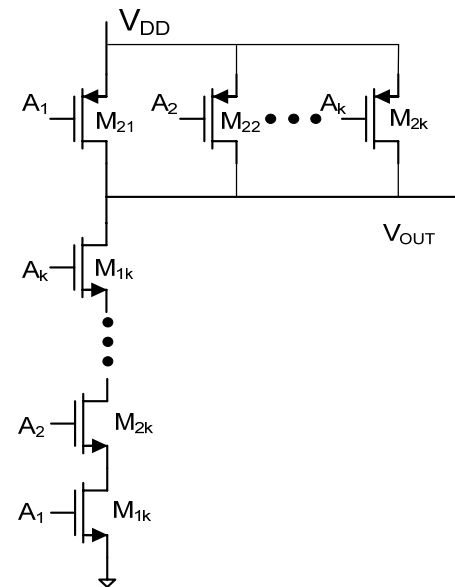
$$C_{IN} = \left(\frac{3k+1}{4} \right) C_{REF}$$






k-input NAND

$$W_n = kW_{MIN}, W_p = 3W_{MIN}$$

$$C_{IN} = \left(\frac{3+k}{4} \right) C_{REF}$$

Review from last time

Device Sizing

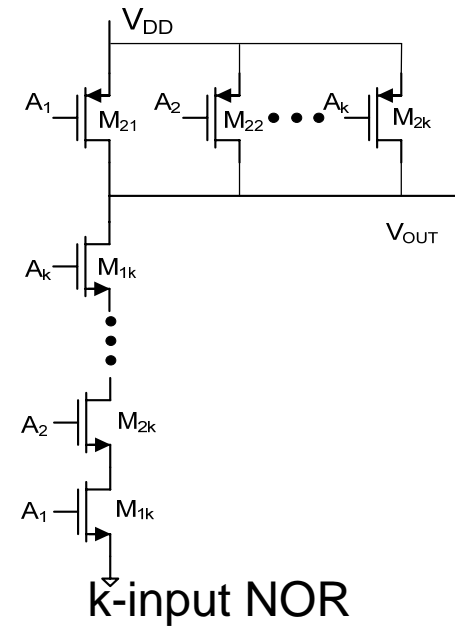  

C_{IN} for N_{AND} gates is considerably smaller than for NOR gates for equal worst-case rise and fall times


C_{IN} for minimum-sized structures is independent of number of inputs and much smaller than C_{IN} for the equal rise/fall time case

or P_{PD}
 R_{PU} gets very large for minimum-sized NOR gate

$$\frac{C_{REF}}{2}$$

Propagation Delay in Multiple-Levels of Logic with Stage Loading

 Analysis strategy : Express delays in terms of those of reference inverter



$$C_{REF} = C_{IN} = \underline{4C_{OX} W_{MIN} L_{MIN}}$$


$$R_{PDREF} = \frac{L_{MIN}}{\mu_n C_{OX} W_{MIN} (V_{DD} - V_{Tn})} \stackrel{V_{Tn} = .2V_{DD}}{=} \frac{L_{MIN}}{\mu_n C_{OX} W_{MIN} (0.8V_{DD})}$$

$$t_{REF} = t_{HLREF} + t_{LHREF} = \frac{2}{R_{PDREF} C_{REF}}$$

Assume $\mu_n/\mu_p=3$ $L_n=L_p=L_{MIN}$

$W_n=W_{MIN}$, $W_p=3W_{MIN}$

 Propagation Delay in Multiple-Levels of Logic with Stage Loading



$$F_{IL} = \frac{C_L}{C_{REF}}$$

⇒


$$t_{HL} = R_{PD} C_L = (R_{PD} C_{REF}) F_{IL}$$

$$t_{LH} = t_{HL}$$

$$t_{PROP} = t_{HL} + t_{LH} = \underbrace{2 R_{PD} C_{REF}} F_{IL}$$

$$t_{PROP} = (t_{REF}) F_{IL}$$

 Propagation Delay in Multiple-Levels of Logic with Stage Loading



Assume m is even

$$t_{HL} = t_{LHm} + t_{HLm-1} + t_{LHm-2} + \dots + t_{HL1}$$

$$t_{LH} = t_{HLm} + t_{LHm-1} + \dots + t_{LH1}$$

\therefore


$$t_{PROP} = t_{HL} + t_{LH} = (t_{LHm} + t_{HLm}) + (t_{LHm-1} + t_{HLm-1}) + \dots + t_{HL1} + t_{LH1}$$

$$t_{PROP} = \sum_{i=1}^m t_{PROP_i}$$

If m stages are identical & all reference inputs,

$$t_{PROP} = m t_{REF}$$

 
Propagation Delay in Multiple-Levels of Logic with Stage Loading



$$t_{PROP} = (t_{REF} \cdot FI_2) + t_{REF} \cdot FI_3 + \dots + t_{REF} \cdot FI_m$$
$$t_{PROP} = \sum_{i=2}^m t_{REF} \cdot FI_i$$


Propagation Delay in Multiple-Levels of Logic with Stage Loading

Overdrive (assume equal rise/fall)

 

$$C_L = 10^4 C_{REF} \quad (\sim 20 \text{ pF})$$
 
$$t_{PROP} = t_{REF} \cdot F_{IL} = 10^4 t_{REF}$$



$$w_n = k w_{n1}$$

$$w_p = 3k w_{n1}$$

$$R_{pd} = \frac{R_{pdREF}}{k}$$

$$\therefore t_{prop} = \frac{1}{R_{pd} C_L} = \frac{1}{\frac{1}{k} (R_{pdREF} C_L)} = \frac{t_{REF}}{k}$$

if $k = 10^4$, $t_{PROP} = t_{REF} \frac{1}{10^4} = t_{REF}$

OD = factor by which the widths 10^4 are increased


beyond those of ref inverter

Propagation Delay in Multiple-Levels of Logic with Stage Loading

an OD factor of K will decrease
the delay by a factor of K !



 but: may have a problem driving
the inverter with a large OD



$$t_{PROP} = t_{REF} \cdot FI_2 + \frac{t_{REF} \cdot FI}{OD} \quad \text{IF} \quad FI = 10^4$$

$$OD = 10^4$$

$$= 10^4 t_{REF} + t_{REF}$$


$$= t_{REF} (1 + 10^4)$$

slight increase
in prop. delay



Propagation Delay in Multiple-Levels of Logic with Stage Loading


Consider

 

$$t_{PROP} = t_1 + t_2 + t_3$$

$$= (t_{REF}) F I_2 + \frac{t_{REF} 10^4}{10^2} + t_{REF} \frac{10 I_3}{100}$$

$$= t_{REF} (100 + 100 + 1)$$

 

$$t_{PROP} = 200 t_{REF}$$

$$t_{PROP} = 201 t_{REF} \quad \text{decrease from } 10^6 t_{REF}$$

Dramatic Reduction in prop. delay

OD can speed up logic if appropriately used

Propagation Delay in Multiple-Levels of Logic with Stage Loading

- What is the optimal way to drive a given load C_L ?


- How many stages?

- How much OD on each stage

- Extremely big w/L ratios caused when very large OD

- but almost always justifiable when speed limitations are present

Logic with varying OD , multiple levels

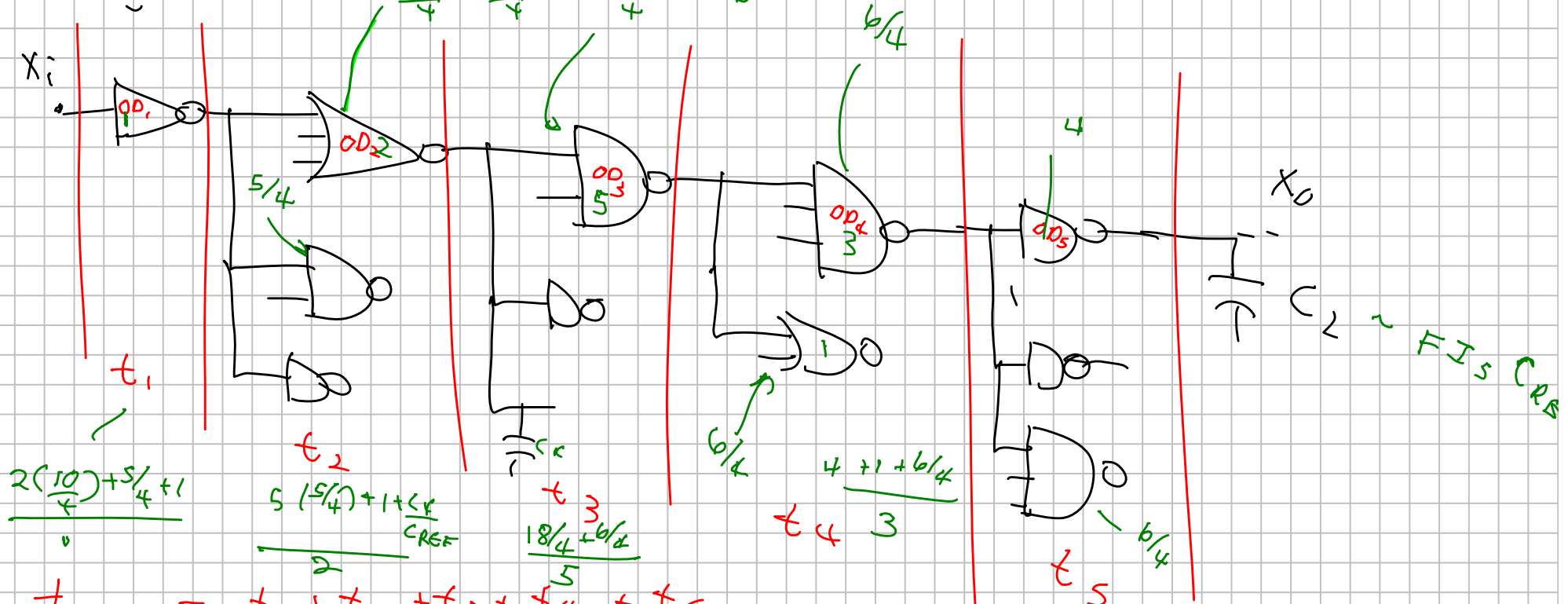

$$\frac{2(\frac{10}{4}) + \frac{5}{4} + 1}{0}$$

$$\frac{5(\frac{5}{4}) + 1 + C_{REF}}{2}$$

$$\frac{18/4 + 6/4}{5}$$

$$\frac{4 + 1 + 6/4}{3}$$

$$\frac{FI_5}{4}$$

$$t_{PROP} = t_1 + t_2 + t_3 + t_4 + t_5$$

$$= t_{REF} \frac{FI_2}{OD_1} + t_{REF} \frac{FI_3}{OD_2} + t_{REF} \frac{FI_4}{OD_3} + \dots$$

$$t_{PROP} = t_{REF} \sum_{i=1}^m \frac{FI_{i+1}}{OD_i}$$

Elmore Delay

OD sizing for NAND & NOR Gates.

— For an OD of h on a NAND or NOR Gate
(assuming equal rise/fall times)

• scale all widths by h