

EE 434

Lecture 38


Propagation Delay in Logic Circuits

Power Dissipation

Review from last time

Propagation Delay in Multiple-Levels of Logic with Stage Loading

 Analysis strategy : Express delays in terms of those of reference inverter



Reference Inverter

$$C_{REF} = C_{IN} = 4C_{OX} W_{MIN} L_{MIN}$$

$$R_{PDREF} = \frac{L_{MIN}}{\mu_n C_{OX} W_{MIN} (V_{DD} - V_{Tn})} \stackrel{V_{Tn} = .2V_{DD}}{=} \frac{L_{MIN}}{\mu_n C_{OX} W_{MIN} (0.8V_{DD})}$$

$$t_{REF} = t_{HLREF} + t_{LHREF} = \frac{2}{R_{PDREF} C_{REF}}$$


Assume $\mu_n/\mu_p=3$ $L_n=L_p=L_{MIN}$

$W_n=W_{MIN}$, $W_p=3W_{MIN}$

Review from last time

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Capacitive Loading

 

Define the Fan In loading on the stage to be the total capacitive load on the stage normalized to C_{REF}

$$F_{IL} = \frac{C_L}{C_{REF}}$$

If inverter sized for equal rise/fall

$$t_{HL} = t_{LH} = R_{PD} C_L = R_{PD} C_{REF} F_{IL}$$

$$t_{PROP} = t_{LH} + t_{HL} = 2 R_{PD} C_{REF} F_{IL}$$


If inverter is the reference inverter

$$t_{PROP} = t_{REF} F_{IL}$$

Review from last time

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Overdrive

 

Define the Overdrive Factor of the stage to be the factor by which PU and PD resistors are scaled relative to those of the reference inverter.

$$R_{PDEFF} = \frac{R_{PDREF}}{OD_{HL}}$$

$$R_{PUEFF} = \frac{R_{PUREF}}{OD_{LH}}$$

If inverter sized for equal rise/fall, $OD_{HL} = OD_{LH} = OD$


$$t_{HL} = t_{LH} = \frac{R_{PDREF}}{OD} C_L = R_{PDREF} C_{REF} \frac{F_{IL}}{OD}$$

$$t_{PROP} = t_{LH} + t_{HL} = t_{REF} \frac{F_{IL}}{OD}$$

OD may be larger or smaller than 1

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Overdrive

 

$$t_{PROP} = t_{LH} + t_{HL} = t_{REF} \frac{F_{IL}}{OD}$$

If inverter is not equal rise/fall


$$t_{HL} = \frac{R_{PDREF}}{OD_{HL}} C_L = \frac{1}{2} t_{REF} \frac{F_{IL}}{OD_{HL}}$$

$$t_{LH} = \frac{R_{PUREF}}{OD_{LH}} C_L = \frac{1}{2} t_{REF} \frac{F_{IL}}{OD_{LH}}$$


$$t_{PROP} = t_{HL} + t_{LH} = \frac{1}{2} t_{REF} F_{IL} \left(\frac{1}{OD_{HL}} + \frac{1}{OD_{LH}} \right)$$

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Overdrive Notation

 


Equal Rise/Fall with overdrive OD

 


Rise/Fall may be different with overdrive OD_{HL} and OD_{LH}

Examples

 


Equal Rise/Fall with overdrive of 8

 

If $W_n = W_{MIN}$, minimum sized inverter

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Example:

 

$$t_{\text{PROP}} = t_{\text{LH}} + t_{\text{HL}} = t_{\text{REF}} \frac{F_{\text{IL}}}{\text{OD}}$$

If inverter is not equal rise/fall

$$t_{\text{HL}} = \frac{R_{\text{PDREF}}}{\text{OD}_{\text{HL}}} C_L = \frac{1}{2} t_{\text{REF}} \frac{F_{\text{IL}}}{\text{OD}_{\text{HL}}}$$

$$t_{\text{LH}} = \frac{R_{\text{PUREF}}}{\text{OD}_{\text{LH}}} C_L = \frac{1}{2} t_{\text{REF}} \frac{F_{\text{IL}}}{\text{OD}_{\text{LH}}}$$


$$t_{\text{PROP}} = t_{\text{HL}} + t_{\text{LH}} = \frac{1}{2} t_{\text{REF}} F_{\text{IL}} \left(\frac{1}{\text{OD}_{\text{HL}}} + \frac{1}{\text{OD}_{\text{LH}}} \right)$$



Review from last time

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Equal rise-fall gates, no overdrive

 


$$t_{REF} = 2t_{HL_{REF}}$$

$$t_{PROP} = t_{REF} \sum_{k=1}^n F_{k+1}$$

Review from last time

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Equal rise-fall gates, no overdrive

 


$$t_{\text{REF}} = 2t_{\text{HLREF}}$$

$$t_{\text{PROP}} = t_{\text{REF}} \sum_{k=1}^n F_{k+1}$$

Review from last time

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Equal rise-fall gates, with overdrive

 

$$t_{REF} = 2t_{HL_{REF}}$$


$$t_{PROP} = t_{REF} \sum_{k=1}^n \frac{F_{l_{k+1}}}{OD_k}$$



Review from last time



Propagation Delay in Multiple-Levels of Logic with Stage Loading

 Nonequal rise-fall gates, with *overdrive*




$$t_{\text{PROP}} = \frac{t_{\text{REF}}}{2} \sum_{k=1}^n F_{l_{k+1}} \left(\frac{1}{\text{OD}_{\text{HLk}}} + \frac{1}{\text{OD}_{\text{LHk}}} \right)$$

Optimal Driving of Capacitive Loads

  

Minimum at $\theta=e$ but shallow inflection point for $2 < \theta < 3$

Optimal Driving of Capacitive Loads

 


Optimal number of stages is $\ln(C_L/C_{REF})$

Practically pick $\theta=2$ or 2.5 or 3 to obtain near optimal performance

$$t_{PROP} \approx n\theta$$

these drivers
used on-chip as
well to drive capacitive buses or large
numbers of gates

Optimal Driving of Capacitive Loads

 

Optimal number of stages is $\ln(C_L/C_{REF})$

Practically pick $\theta=2$ or 2.5 or 3 to obtain near optimal performance

$$t_{PROP} \approx n\theta$$

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Delay calculations with logical effort approach

g = ratio of input capacitance of the gate to the input capacitance of an inverter that can deliver the same output current
— logic effort

$$g = \frac{C_{in}}{\widetilde{C}_{inv}} = \frac{C_{in}}{C_{REF} OD_k}$$

h = electrical effort to be ratio of load capacitance to input capacitance of a gate

$$h = \frac{C_L}{C_{in}}$$

Propagation Delay in Multiple-Levels of Logic with Stage Loading

Delay calculations with logical effort approach

$$\begin{aligned}
 t_{LE} &= gh \\
 &= \frac{C_{in}}{C_{inv}} \cdot \frac{C_L}{C_{in}} \\
 &= \frac{C_{in}}{OD \cdot C_{REF}} \cdot \frac{FI_L C_{REF}}{C_{in}}
 \end{aligned}$$




$$t_{LE} = \frac{FI_{k+1}}{OD_k}$$

$$t_{PROP} = t_{REF} \left(\sum_{i=1}^m t_{LE_i} \right) = t_{REF} \sum_{i=1}^m \frac{FI_{k+1}}{OD_k}$$




Propagation Delay in Multiple-Levels of Logic with Stage Loading

   ~~Delay calculations with logical effort approach~~ Elmore Delay



😊 easy to model as ladder network

 😞 solution is messy if $m = 2$
really messy if $m > 2$



$$t_{\text{DELAY}} = R_1 C_1 + (R_1 + R_2) C_2 + (R_1 + R_2 + R_3) C_3 + (R_1 + R_2 + R_3 + R_4) C_4$$

approx solution to a 4th order differential equation

$$t_{\text{DELAY}} \approx \sum_{i=1}^n \sum_{j=1}^m R_i C_j$$

Note error in text





Is there a problem associated with neglecting stage coupling in delay calculations for logic circuits we have used?

- Gates actually do decouple between stages so existing approximations are quite good.

Ring Oscillators


Recall

  


- unstable as linear circuit at V_{CRIP}

- Bistable Nonlinear Circuit

 ↳
RHP real axis pole provides
this property!




Oscillator

 

$$C = C_{in} + C_{D,FF}$$

Ring Oscillator

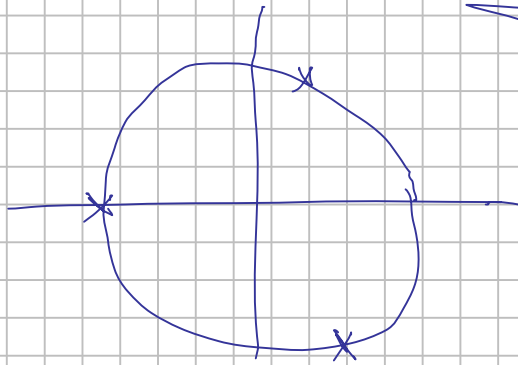


$$T_{osc} = 3 t_{PROP}$$

$$\therefore f_{osc} = \frac{1}{3 t_{PROP}}$$

Good sinusoidal oscillator





 




$$n = 3!$$

$$f_{osc} = \frac{1}{(n) t_{PROP}}$$

- n is a prime number

  

  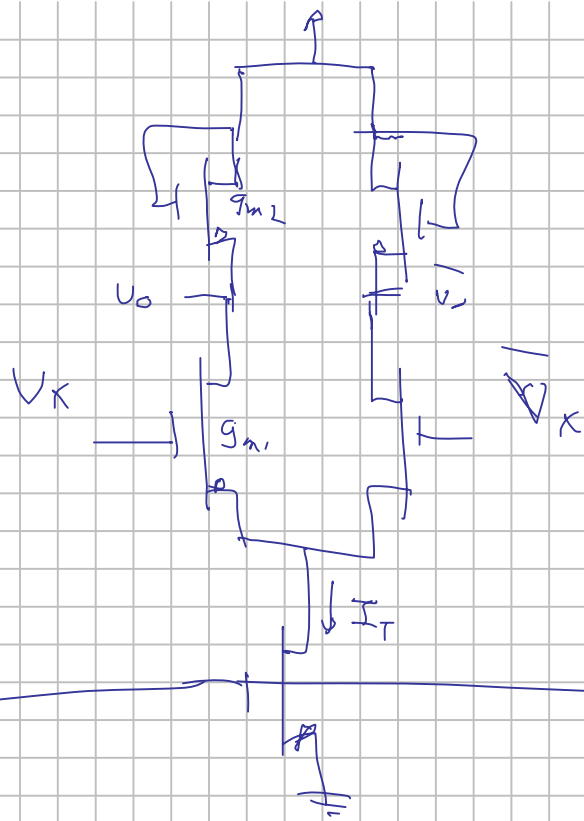- apply output to a binary counter for practical freq. reduction



$$t_{delay} \approx \frac{C_L}{g_{m1}}$$

$$g_m = f(I_T)$$

VCO with wide adj range

odd # stages (prime)

