

# EE 434

## Lecture 5

Improved Device Model  
Stick Diagrams  
Technology Files

## Quiz 3

How many transistors are required to realize the function

$$F = \overline{A} \cdot \overline{B} + \overline{A} \cdot C$$

in a basic CMOS process if static NAND and NOR gates are used? Assume A, B and C are available.

And the number is ....

1            8            7            5            3  
6            9            4            2

9


## Quiz 3

How many transistors are required to realize the function

$$F = \overline{A \cdot B} + \overline{A} \cdot C$$

in a basic CMOS process if static NAND and NOR gates are used? Assume A, B and C are available.

**Solution:**

 

**20 transistors and 5 levels of logic**

## Quiz 3

How many transistors are required to realize the function


$$F = \overline{\overline{A} \cdot \overline{B}} + \overline{A} \cdot C$$

in a basic CMOS process if static NAND and NOR gates are used? Assume A, B and C are available.

**Solution (alternative):** From basic Boolean Manipulations

$$F = \overline{\overline{A} \cdot \overline{B}} + \overline{A} \cdot C = \overline{A} + B + \overline{A} \cdot C$$
 
$$F = \overline{A} \cdot (1 + C) + B = \overline{A} + B$$



**8 transistors and 3 levels of logic**

## Quiz 3

How many transistors are required to realize the function

$$F = \overline{\overline{A} \cdot \overline{B}} + \overline{A} \cdot C$$


in a basic CMOS process if static NAND and NOR gates are used? Assume A, B and C are available.

**Solution (alternative):**

From basic Boolean Manipulations

$$F = \overline{\overline{A} \cdot (1 + C)} + B = \overline{\overline{A} + B}$$
 
$$F = \overline{\overline{\overline{\overline{A} + B}}} = \overline{\overline{A} \cdot \overline{B}}$$



**6 transistors and 2 levels of logic**

## Review from Last Time




- Simple model of MOSFET was developed
  - hierarchical model structure will be developed
  - generally use simplest model that can be justified
- Simple CMOS gates were introduced
  - Zero power dissipation
  - Rail to Rail Swings
  - Infinitely Fast
  - Simple model may not give sufficiently accurate insight relating to these properties

## Review from Last Time




- Different Logic Design Styles Often Used on an Integrated Circuit
  - PTL is one style that can offer significant reductions in complexity
  - Signal Degradation and Static Power Dissipation are issues of concern when using PTL
  - Designer is under complete control of circuits that are placed on the silicon
  - Many designs will mix multiple logic design styles
  - New logic design styles are still being proposed and adopted




# Improved Switch-Level Model

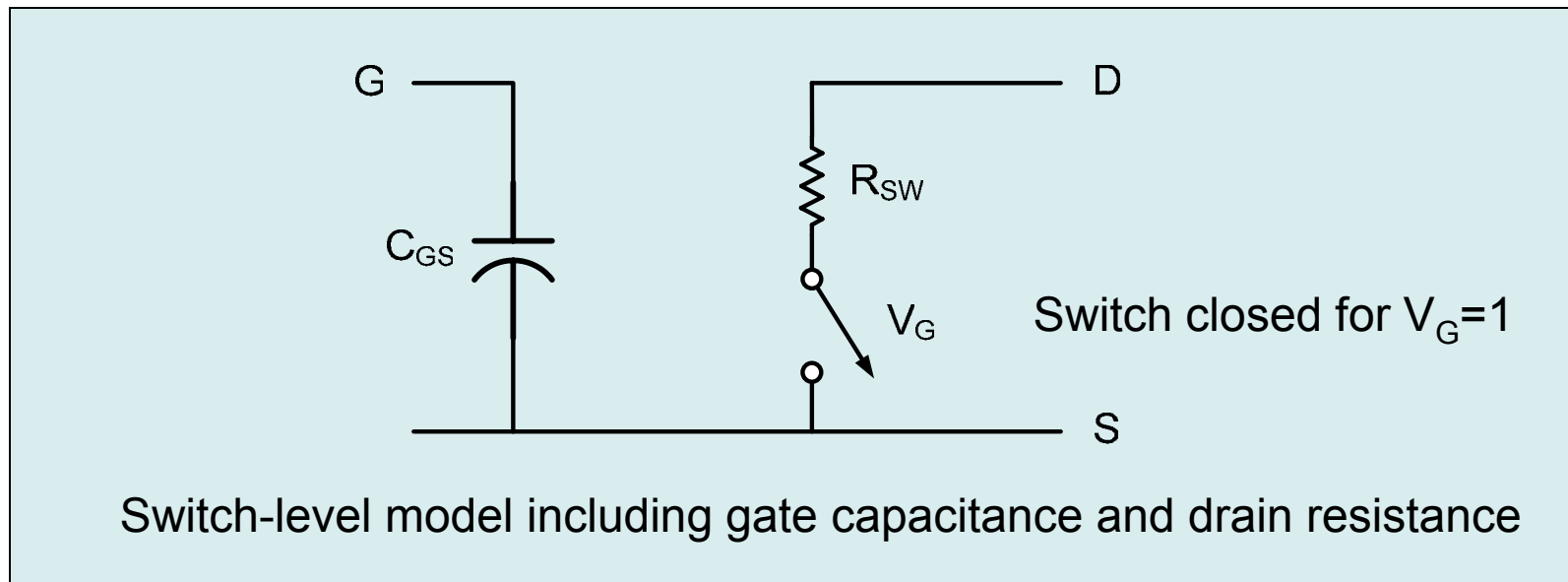  

# Improved Switch-Level Model

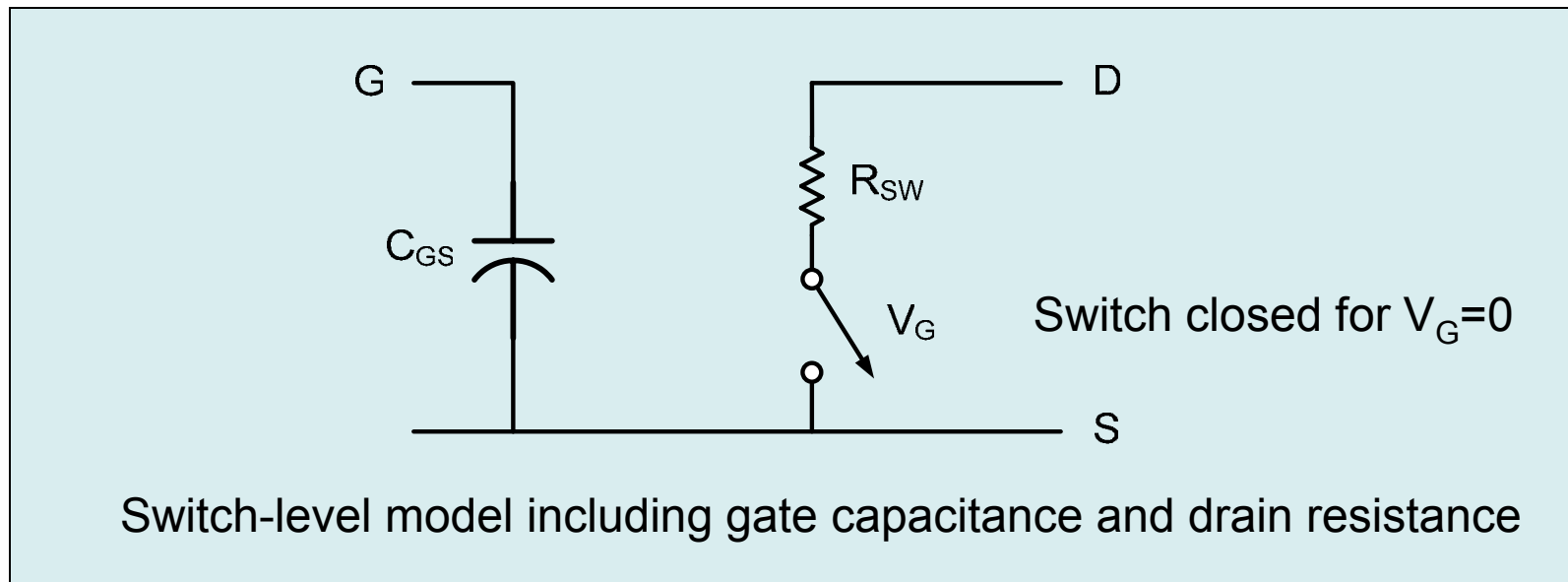  

# Improved Switch-Level Model

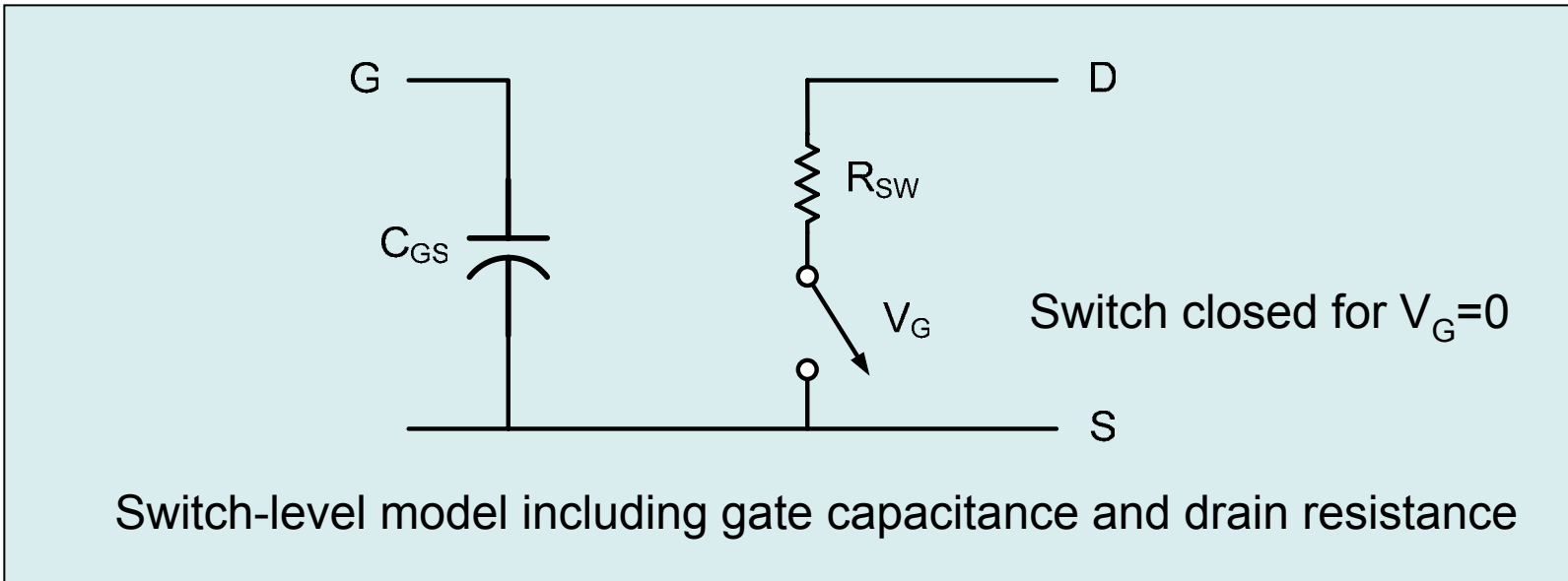


$C_{GS}$  and  $R_{SW}$  dependent upon device sizes and process

For minimum-sized devices in a 0.5 $\mu$  process


$$\mathbf{C_{GS} \cong 1.5fF} \quad \mathbf{R_{sw} \cong \left. \begin{array}{l} 2K\Omega \text{ n-channel} \\ 6K\Omega \text{ p-channel} \end{array} \right\}}$$

Considerable emphasis will be placed upon device sizing to manage  $C_{GS}$  and  $R_{SW}$


# Example

 


With switch level model

 

## Example (cont)


 


With improved model

 


# Example (cont)

With improved model

  

## Example (cont)

With improved model

 

Recognize as a first-order RC network

Recall: Step response of any first-order network with LHP pole can be written as


$$y(t) = F + (I - F)e^{-\frac{t}{\tau}}$$

where  $F$  is the final value,  $I$  is the initial value and  $\tau$  is the time constant of the circuit

For the circuit above,  $F=0$ ,  $I=5$  and  $\tau = R_{SW}C_L$

## Example (cont)

With improved model

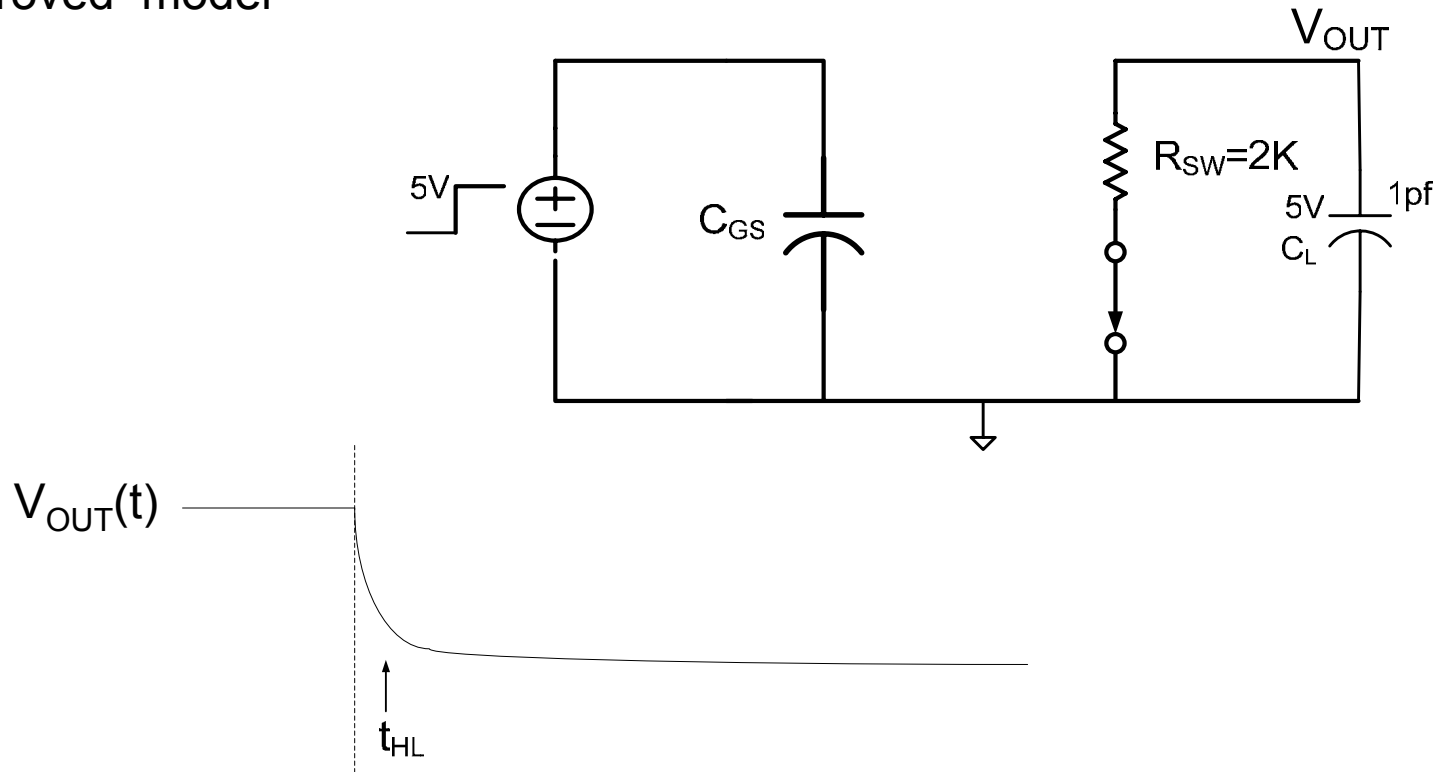


$$t_{HL} \cong \frac{1}{R_{SW} C_L} = \frac{1}{2K \cdot 1pF} = .5E-9 \text{ sec} = .5n \text{ sec}$$



# Stick Diagrams



- It is often necessary to obtain information about placement, interconnect and physical-layer structure
- Stick diagrams are often used for small component-count blocks
- Approximate placement, routing, and area information can be obtained rather quickly with the use of stick diagrams

# Stick Diagrams

 

Additional layers can be added and color conventions are personal

# Stick Diagram


 
 


A stick diagram is not a layout but gives the basic structure that will be instantiated in the actual layout itself

Modifications can be made much more quickly on a stick diagram than on a layout

Iteration may be needed to come up with a good layout structure

# Stick Diagram

   

Alternate Representation

# Technology Files

# Technology Files

- Provide Information About Process
  - Process Flow (Fabrication Technology)
  - Model Parameters
  - Design Rules
- Serve as Interface Between Design Engineer and Process Engineer
- Insist on getting information that is deemed important for a design
  - Limited information available in academia
  - Foundries often sensitive to who gets access to information
  - Customer success and satisfaction is critical to foundries

# Technology Files



- **Process Flow (Fabrication Technology)** (will finish discussion next week)
- **Model Parameters** (will discuss in detail after device models are introduced)
- **Design Rules**

# Design Rules





  

- Give minimum feature sizes, spacing, and other constraints that are acceptable in a process
- Very large number of devices can be reliably made with the design rules of a process
- Yield and performance unpredictable and often low if rules are violated
- Compatible with design rule checker in integrated toolsets




# Design Rules – consider transistors



 
## Layer Map

-  p-active
-  n-active
-  Poly 1
-  Metal 1
-  n-well
-  contact




Layout

 

Layout

**Layout always represented in a top view in two dimensions**






# Design Rules

 

**Design rules give minimum feature sizes and spacings**



**Designers generally do layouts to minimize size of circuit subject to design rule constraints (because yield, cost, and performance usually improve)**

# Design Rules – consider transistors

     



- Bulk connection needed
- Single bulk connection can often be used for several (many) transistors

# Design Rules – consider transistors

  


 
 
## Layer Map

- p-active
- n-active
- Poly 1
- Metal 1
- n-well
- contact



- **Bulk connection needed**
- **Single bulk connection can often be used for several (many) transistors if they share the same well**

# Design Rules (example)

 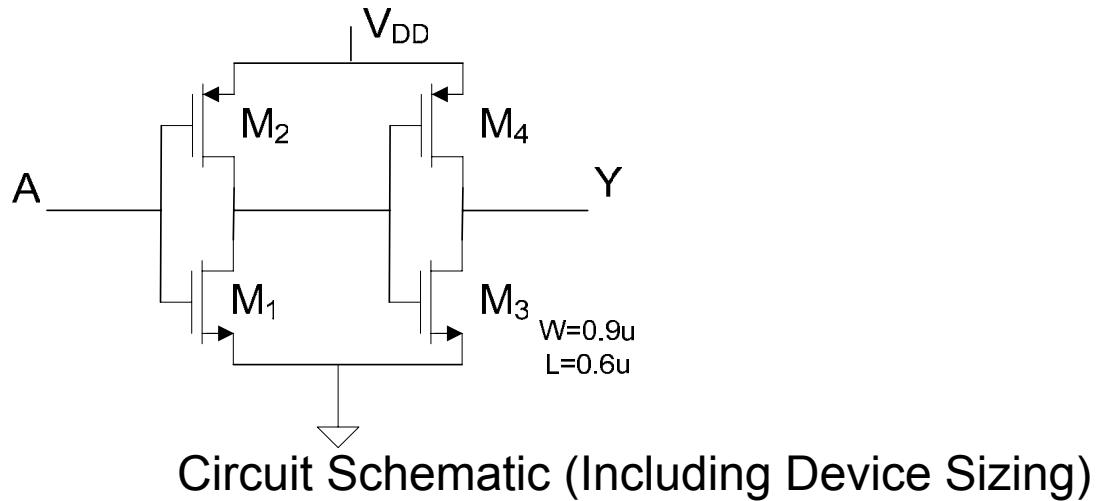 

**End of Lecture 5**