

EE 434


Lecture 4~~3~~

Other Logic Styles

- Static CMOS Logic
- Complex Logic Gates
-  Pass Transistor Logic
-  Pseudo-NMOS
-  Dynamic Logic

Review from last time

Complex Logic Gates

 

Implement \bar{F} in PD Network with n-channel devices

Implement F in PU Network with p-channel devices with complimented variables

Preserves rail-to-rail signal swing

No static power dissipation



At most two levels of logic

Often significant reduction in device count and delay

Review from last time

Pass Transistor Logic

Example:

  

$$F=A \cdot B$$

Low device count implementation of non inverting function (can be dramatic)

Logic Swing not rail to rail

Static power dissipation not 0 when F high


R_{LG} may be unacceptably large

Slow t_{LH}

Signal degradation can occur when multiple levels of logic are used



Review from last time

Pass Transistor Logic

 


Physical Size of R_{LG} too large

Methods of implementing R_{LG}

  


Review from last time

Pass Transistor Logic

 

Signal degradation

 

No signal degradation

Signal degradation may occur with PTL

- Can intermix n-channel and p-channel devices to reduce/eliminate the signal degradation problem
- Can add static CMOS buffers to restore signals provided too much signal degradation has not occurred

Other Logic Styles

Static CMOS Logic





Complex Logic Gates

 Pass Transistor Logic


Pseudo-NMOS

Dynamic Logic



Pass Transistor Logic Gates

    


Pass Transistor Logic Gates

 


$$F=A \cdot B$$

  



$$F=A \cdot B$$

 


Pass Transistor Logic Gates

 


$$F = \overline{A \cdot B}$$

  



$$F = \overline{A + B}$$

 


Pass Transistor Logic Gates

 




$$F = A + B$$

  


$$F = \overline{A + B}$$

 




Pass Transistor Logic Gates

   

$$F = A \oplus B$$

 


Pass Transistor Logic Gates

   


- Observe all PTL gates discussed so far were of this form
- PU network can contain a mixture of n-channel and p-channel devices
- Any of the PU networks used for complex logic gates could also be used in PTL

Pass Transistor Logic Gates


 


- PTL gates could also be designed with logic in PD network
- PD network can contain a mixture of n-channel and p-channel devices
- Any of the PD networks used in complex logic gates could be used in PTL

Pass Transistor Logic Gates

 

As an example:

  

Other Logic Styles

Static CMOS Logic

Complex Logic Gates


Pass Transistor Logic

Pseudo-NMOS



Dynamic Logic



Dynamic Logic

 

Observations:

- PU network major contributor to dynamic power dissipation
- PU network for complex logic gates requires large devices for good t_{LH}
- PU network requires large area for n-wells
- PU and PD network duplicate logic function


Dynamic Logic

  

Question:

Is it possible to eliminate PU Network and still maintain signal swing and zero static power dissipation of complex logic gate approaches?

Dynamic Logic

 


Basic Dynamic Logic Gate

Precharges F to V_{DD} when C_{LK} is low (precharge state)

when C_{LK} is high (evaluate state) discharges C_H only if PD network conducts

C_H (hold capacitor) can be simply parasitic capacitances on node F

Dynamic Logic

 


Basic Dynamic Logic Gate

Positive Attributes:

- ✓ • Potential for substantial decrease in dynamic power dissipation
- ✓ • Zero Static Power Dissipation
- ✓ • Excellent speed
- ✓ • Reduced area

Dynamic Logic

 


Negative Attributes:

- Output valid only during evaluate state
- Requires Clock
- Can not be placed in a static hold state
- Premature discharge can occur with cascaded logic (potential stopper !)

Dynamic Logic

Premature discharge example:

 

When G is precharged high and is to go Low ($A=B=1$) on the evaluate state F should be a 1 but may be prematurely discharged while G is high

Alternatively, if A or B are to be 1 but come from another gate where they were low initially, there may be a delay for becoming 1 thus keeping G high even longer thus prematurely discharging F