

$$a) t_{REF} \left( \frac{FI_2}{OD_1} + \frac{FI_3}{OD_2} + \frac{FI_4}{OD_3} \right) \quad \text{NOR: } \frac{3 \cdot 2 + 1}{4}$$

$$FI_2 = 8 \left( \frac{1}{4} \right) + 2 + 1$$

$$OD_1 = 3$$

$$FI_3 = 6 \left( \frac{10}{4} \right) + 2 \left( \frac{13}{4} \right)$$

$$OD_2 = 1$$

$$FI_4 = \frac{C_L}{C_{REF}} = \frac{160 \text{ fF}}{2 \text{ fF}}$$

$$OD_3 = 2$$

$$1.34 \text{ nsec}$$

$$(t_{REF} = 67.1)$$

$$b) \frac{t_{REF}}{2} \left[ FI_2 \left( \frac{1}{OD_{1HL}} + \frac{1}{OD_{1LH}} \right) + FI_3 \left( \frac{1}{OD_{2HL}} + \frac{1}{OD_{2LH}} \right) + FI_4 \left( \frac{1}{OD_{3HL}} + \frac{1}{OD_{3LH}} \right) \right]$$

$$FI_2 = 3/2$$

$$OD_{1HL} = 1$$

$$OD_{2HL} = 1$$

$$OD_{3HL} = 1$$

$$FI_3 = 1$$

$$OD_{1LH} = 1/2$$


$$OD_{2LH} = 1/3$$

$$OD_{3LH} = 1/2$$

$$FI_4 = \frac{160}{2}$$

$$532 t_{REF} = 10.6 \text{ nsec}$$

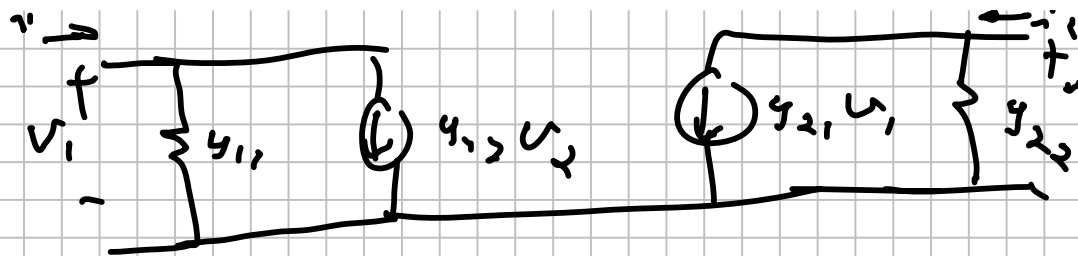a)  $I_1 = 2V_1 + 4V_2^2$   
 $I_2 = 8V_1^2 + .25V_2$




$y_{11} = \frac{\partial I_1}{\partial V_1} \Big|_Q = 2$

$y_{12} = \frac{\partial I_1}{\partial V_2} \Big|_Q = 8V_2 \Big|_Q = 16$

$y_{21} = \frac{\partial I_2}{\partial V_1} \Big|_Q = 24V_1^2 \Big|_Q = 24$




$y_{22} = \frac{\partial I_2}{\partial V_2} \Big|_Q = 1/4$

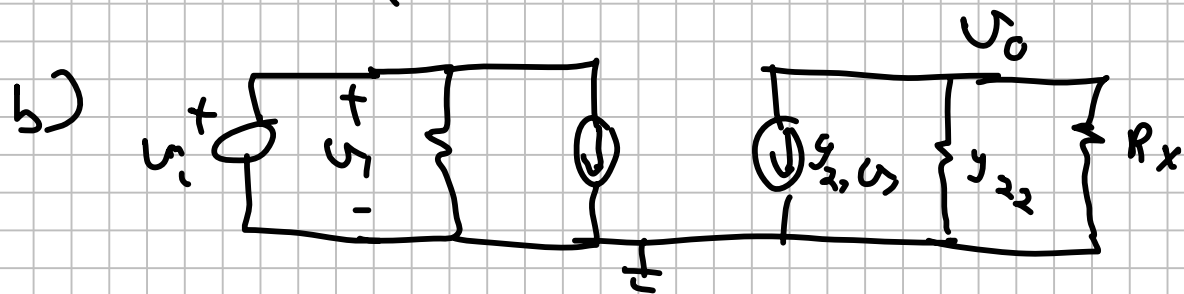

$A_v = \frac{-y_{21}}{y_{22} + 1/R_x} = -12$

$V_{OQ} = 3V$

Problem 3

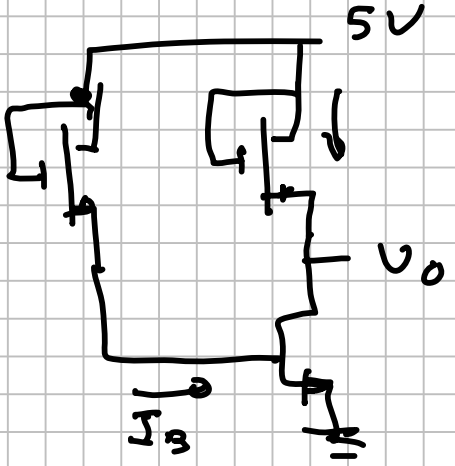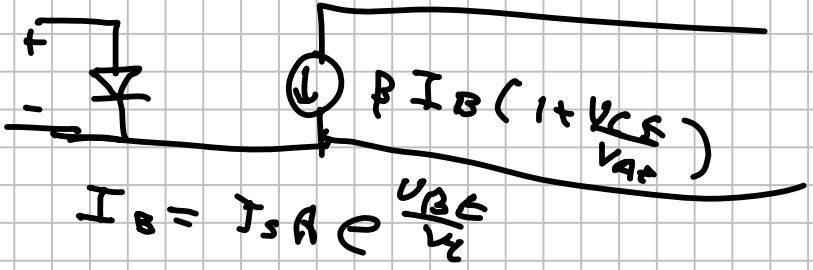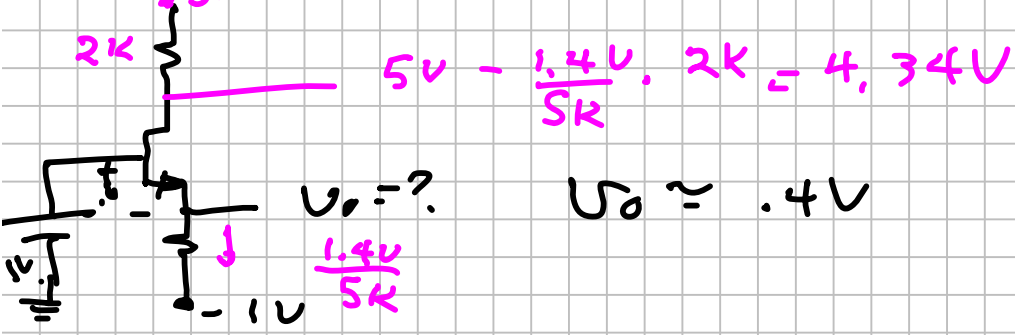

$$I_c = \frac{\mu C_{ox} W_2}{2L_2} (5 - U_o - V_T)^2$$


$$I_B = \frac{\mu C_{ox} W_1}{2L_1} (5 - .6 - V_T)^2 \approx 16 \mu A$$

$U_o = 2.68V$

$$I_c = \beta I_B = 1.6 mA$$

$$I_c = I_s A e^{\frac{V_{BE}}{V_T}}$$

can not assume  $V_{BE} = .6V$

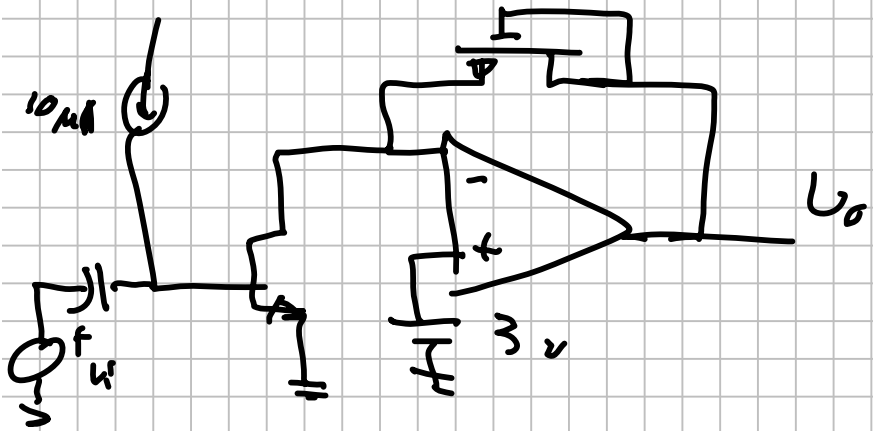

$$U_o = 3V + U_{GS}$$


$$I_D = \beta I_{0\mu A} = 1mA$$

$$1mA = \frac{\mu C_{ox} k W}{2L} (V_{GS} - V_T)^2$$

$$V_{GS} = 2.5V$$

$$\therefore U_o = 5.5V$$

A.

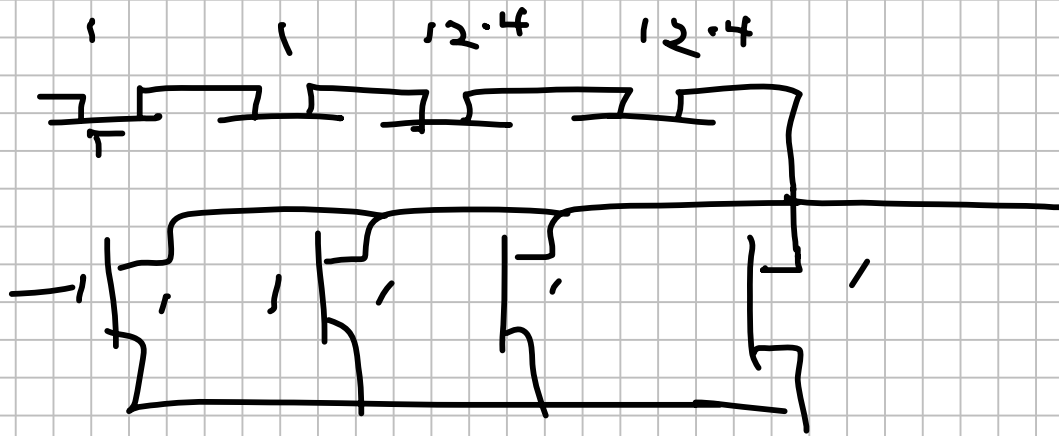


$$\frac{k+3}{f}$$

$$w_c p_n = R_{po} (98) (8) \left( \frac{12.4}{4} \right) C_{REF}$$

$$p_e = R_{po} (8) \frac{7}{4} C_{REF}$$
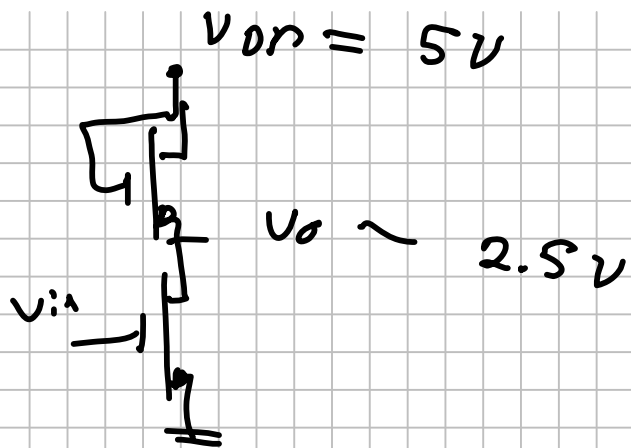
$$\left( \frac{1}{2} \right) \left( \frac{C_{REF}}{4} (8) \frac{7}{4} C_{REF} \right)$$



$$\frac{\mu C_{ox} W_1}{2L_1} (V_{in} - V_T)^2 = \frac{\mu C_{ox} W_2}{2L_2} (5 - v_o - V_T)^2$$

$$V_{in} = V_T + \frac{L_1}{L_2} (V_{DD} - v_o - V_T)$$