


Instructions: This is an open-book, open-notes exam. It is due at 11:59 p.m. on Monday May 9. The solutions should be slid under the office door of the course instructor, 2133 Coover. On those problems that need technology parameters, assume you are working in a $0.5\mu\text{m}$ CMOS process with key parameters $\mu_n C_{OX}=100\mu\text{A}/\text{v}^2$, $\mu_p C_{OX}=30\mu\text{A}/\text{v}^2$, $V_{TNO}=0.8\text{V}$, $V_{TPO}= - 0.8\text{V}$, $C_{OX}=2\text{fF}/\mu^2$, $\lambda =0.01\text{v}^{-1}$, $\gamma = 0$, $C_{dbot} = 0.5\text{fF}/\mu^2$, and $C_{bdsw} = 2.5\text{fF}/\mu$.

All work is to be individual with no discussion with anyone else (except as specified below), no posting of the exam questions, and no use of any other source for obtaining the solutions of the problems. You may make unlimited use of WEB resources for obtaining technical information. You may consult the designated instructor of the course or the designated Teaching Assistant if you have questions. You will be expected to certify that you comply with the honor system by signing the following statement.

I certify that I completed this exam in compliance with the honor system described above
_____ (signature).


Problem 1 Consider the DAC circuit shown below.

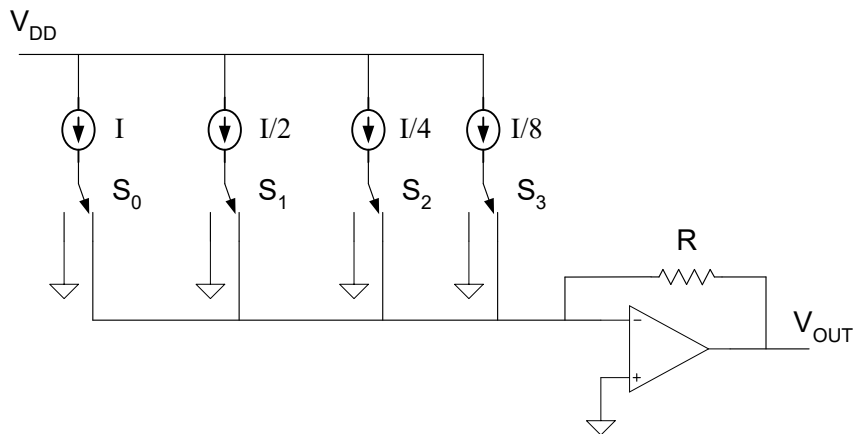- a) Derive an expression for the output voltage as a function of the Boolean inputs S_0, S_1, S_2 and S_3 .
- b) If the current source above S_0 is 10% below the nominal value and all other current sources are equal to their nominal values, determine the INL of this DAC.



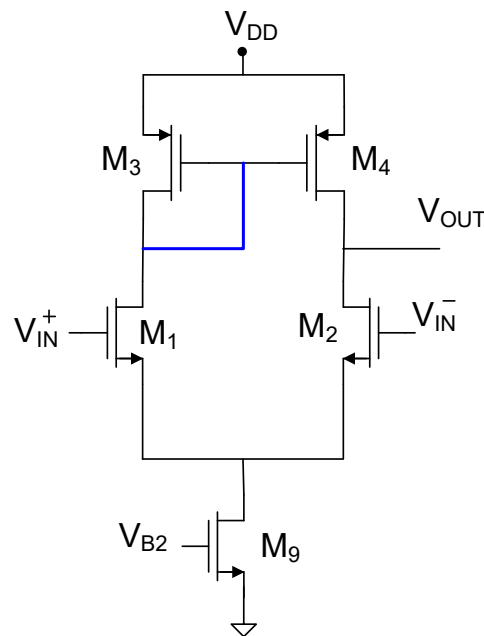Problem 2 Assume in your new job you were told that a previous engineer who worked for the company had designed a 5T op amp in the $0.5\mu\text{m}$ process (process parameters given in instructions of this exam) and that you were to first obtain the circuit schematic and then modify the design for a new project. But when you went to the design document on file, the only design information that was provided by the previous engineer was a note that the magnitude of all of the excess bias voltages were the same and that the op amp was to operate with a supply voltage of 5V . There were also some rudimentary test results included. When a differential step input of $20\mu\text{V}$ was applied to the open-loop amplifier, a step on the output of 10mV was observed and that when a 1nF capacitor was placed on the output and a large step was applied to the differential input, it took $2\mu\text{s}$ for the voltage across the load capacitor to increase from 2V to 3V .


- What is the power dissipation of the op amp?
- What is the GB of the op amp?
- What is W_1/L_1 ?
- What is V_{B2} ?



Problem 3 A 12-bit string DAC has an INL of 11 LSB. Determine the ENOB from an INL perspective.

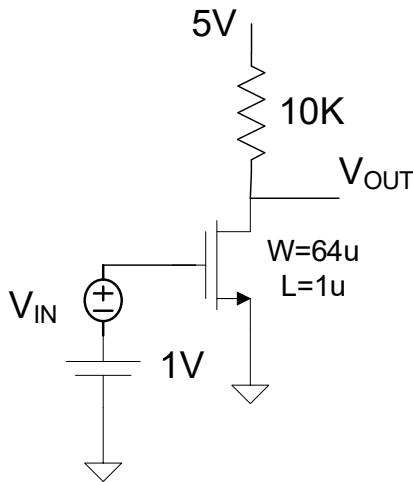
Problem 4 Consider the following circuit where $V_{IN} = 0.05\sqrt{2} \sin(2000\pi t)$

- Determine V_{OUT} .
- Determine the RMS output noise voltage at $T=300K$ in the interval from dc to 10KHz. Include only the thermal noise in the load resistor and in the transistor in this calculation.
- Determine the signal to noise ratio (SNR) at the output where the noise is that in the interval determined in part b)



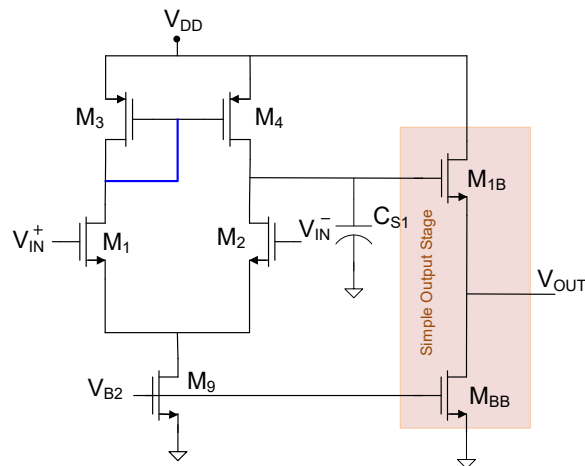
Problem 5 Consider the following amplifier which includes a simple output stage. Assume $V_{DD}=5V$, $C_{S1}=2pF$, and the circuit was designed so that all transistors have $V_{EB}=0.25V$. Further assume the total power dissipation is 10mW and that is split evenly between the differential stage and the output stage.

- Determine W_1/L_1
- Determine W_{1B}/L_{1B}
- What is the maximum output signal swing?



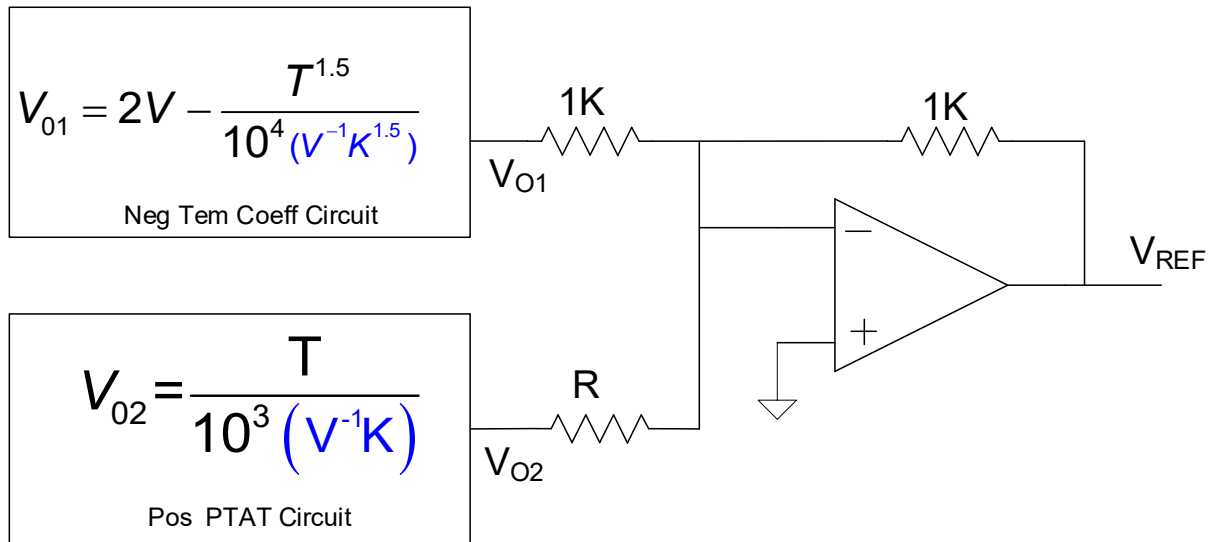Problem 6 The circuit shown has been proposed as a voltage reference. It has two temperature sensors, one with a positive temperature coefficient and the other with a negative temperature coefficient. (The two boxes on the left are assumed to be voltage sources with zero output impedance and output voltages given by the equations shown in the figure.)

- Determine R so that the temperature coefficient of V_{REF} is 0 at $T=300K$.
- With the value of R determined in part a), what is the maximum deviation in V_{REF} from the value output at 300K for $250K < T < 350K$?




Problem 7 A periodic signal was applied to a DAC and the output was sampled 4096 times at 1msec spacings over precisely 11 periods of the output. A DFT using the FFT was used to obtain the DFT of the sampled sequence. The magnitude of the first 120 terms, expressed in DB, are given on the following page. All remaining terms were smaller than -95dB.


- What is the magnitude of the signal?
- What was the frequency of the signal?
- What is the SFDR?
- What is the THD?

Index Number	Mag (dB)	Index Number	Mag (dB)	Index Number	Mag (dB)
1	-97.23	41	-99.21	81	-99.21
2	-98.4	42	-97.43	82	-97.43
3	-96.3	43	-95.61	83	-95.61
4	-99.21	44	-97.4	84	-97.4
5	-97.43	45	-97.23	85	-97.23
6	-95.61	46	-98.2	86	-98.2
7	-97.4	47	-99.4	87	-99.4
8	-97.23	48	-98.78	88	-98.78
9	-98.2	49	-99.21	89	-97.23
10	-99.4	50	-97.43	90	-99.21
11	-98.78	51	-95.61	91	-97.43
12	4.001	52	-97.4	92	-95.61
13	-96.3	53	-97.23	93	-97.4
14	-99.21	54	-98.2	94	-97.23
15	-97.43	55	-99.4	95	-98.2
16	-95.61	56	-98.78	96	-99.4
17	-97.4	57	-97.23	97	-98.78
18	-97.23	58	-98.4	98	-97.23
19	-98.2	59	-96.3	99	-98.4
20	-99.4	60	-99.21	100	-96.3
21	-98.78	61	-97.43	101	-99.21
22	-97.23	62	-95.61	102	-97.43
23	-57.2	63	-97.4	103	-95.61
24	-96.3	64	-98.78	104	-97.4
25	-99.21	65	-98.83	105	-98.78
26	-97.43	66	-96.3	106	-98.3
27	-95.61	67	-99.21	107	-96.3
28	-97.4	68	-97.23	108	-99.21
29	-98.78	69	-98.4	109	-97.43
30	-98.3	70	-96.3	110	-95.61
31	-96.3	71	-99.21	111	-97.4
32	-99.21	72	-97.43	112	-97.23
33	-97.43	73	-95.61	113	-97.23
34	-60.9	74	-97.4	114	-98.4
35	-97.4	75	-98.78	115	-96.3
36	-97.23	76	-98.3	116	-99.21
37	-98.2	77	-96.3	117	-97.43
38	-99.4	78	-99.21	118	-95.61
39	-98.78	79	-97.43	119	-97.4
40	-97.23	80	-95.61	120	-98.78

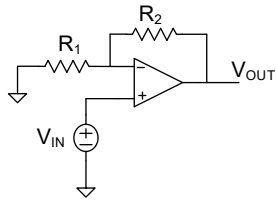
Problem 8 Operational amplifiers are often compensated for an acceptably transient response or gain peaking when connected in a standard feedback configuration such as shown in part (a) below. The consumer often uses the amplifier in other configurations. Shown below are four different amplifier structures. Assume that in all cases the resistors are chosen so that the dc gain is 100. Assume the op amp has been designed so that it has a dc gain of 100,000 and a pole at 10 rad/sec. Analytically compare the 3dB bandwidth and the amplifier poles of the following four circuits assuming the same op amp is used in all four cases. Comment on the relative performance of the four different finite gain amplifiers.




(a)

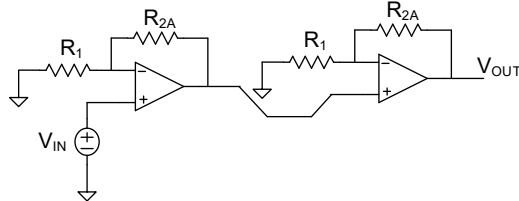

(b)

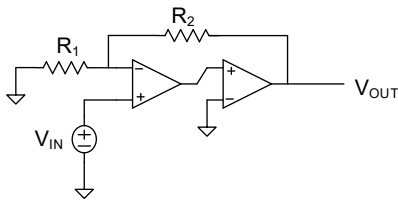



(c)

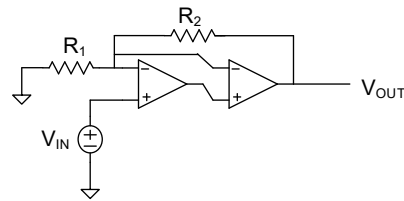

(d)

Problem 9 Two operational amplifiers are shown below. Assume the standard symmetry properties in both structures.

- Compare the dc voltage gain (differential output voltage divided by the differential input voltage) of the two amplifiers in terms of the small-signal model parameters.
- If the lengths of all devices are the same and $W_5=0.9W_3$, compare the dc voltage gain of the two amplifiers in terms of the natural design parameters.
- Compare the power dissipation of the two amplifiers assuming the devices in the left circuit are sized identically to those in the right circuit.

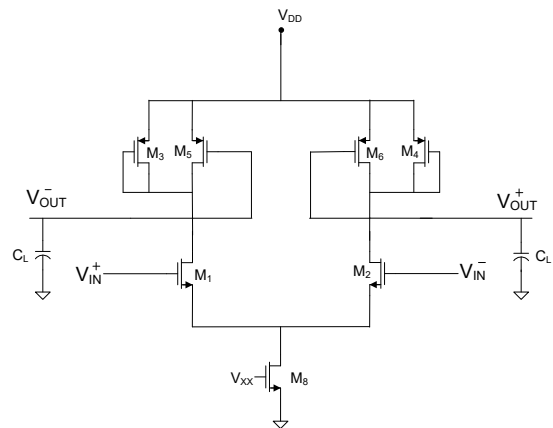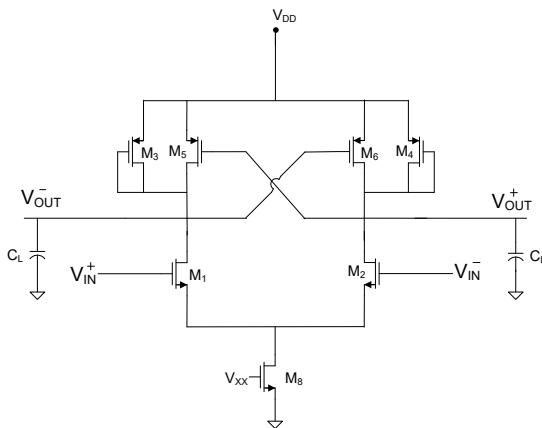

Problem 10

Answer the following questions.

- a) In a hybrid DAC architecture, the input is often partitioned into an MSB part and a LSB part. The MSB part of the input is often used as the input to a thermometer coded DAC and the LSB part of the input is often used as the input to a binary-coded DAC. What is the major reason this approach is often used?

- b) In the bandgap circuits discussed in class, the ratio of the currents in the two diodes was kept constant independent of temperature. Why was this done?

- c) What layout strategy is used to eliminate the effects of linear gradients in device parameters?

- d) It was observed that a rapidly switched capacitor behaves as a resistor. Though this relationship was observed by Maxwell in the late 1800's, it was little more than an academic curiosity at the time. But in the late 1970's two important properties of circuits that used switched capacitors to implement resistors were recognized. What were those two important properties?

- e) Miller compensation of an op amp was a major breakthrough but strict Miller compensation results in a zero on the positive real axis and this is undesirable. What simple circuit modification is often used to move the RHP zero to the negative real axis where performance of the circuit can actually be improved?

- f) When compensating an op amp, dominant pole compensation is often used to move the pole on the output of the first stage to a very low frequency. Why is it not advantageous to also move the pole on the second stage to a lower frequency?

- g) Switching currents on and off in a current-steering DAC causes large glitches on the output and long settling times to turn on and off the current sources. What strategy is used to dramatically reduce the glitches and settling time in current steering DACs?