


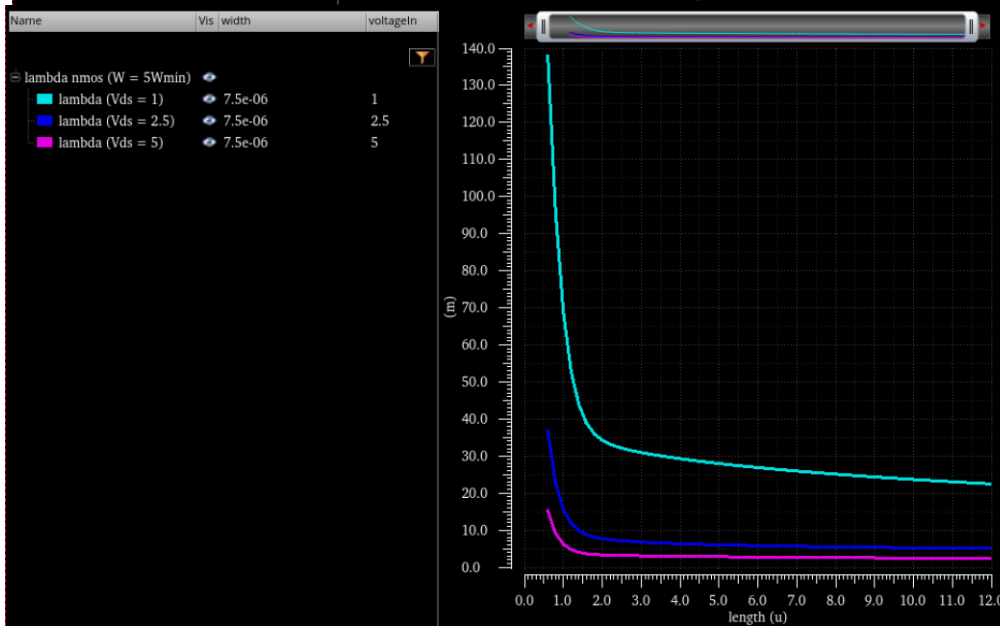


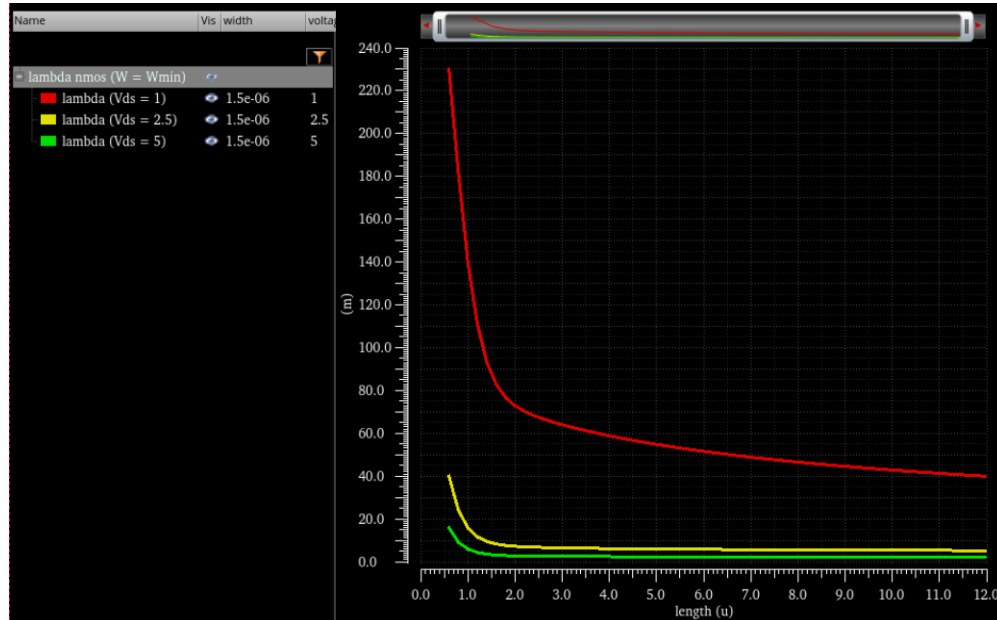
EE 435
 Homework 4 Solutions
 Spring 2024
 Problem 1 & 2
 NMOS



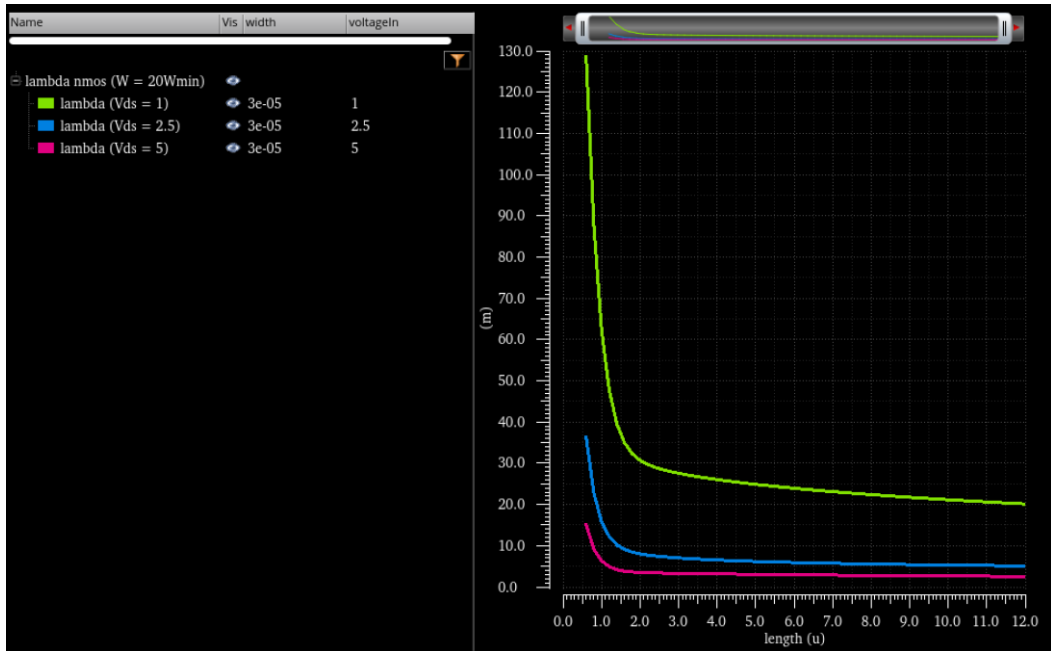

PMOS

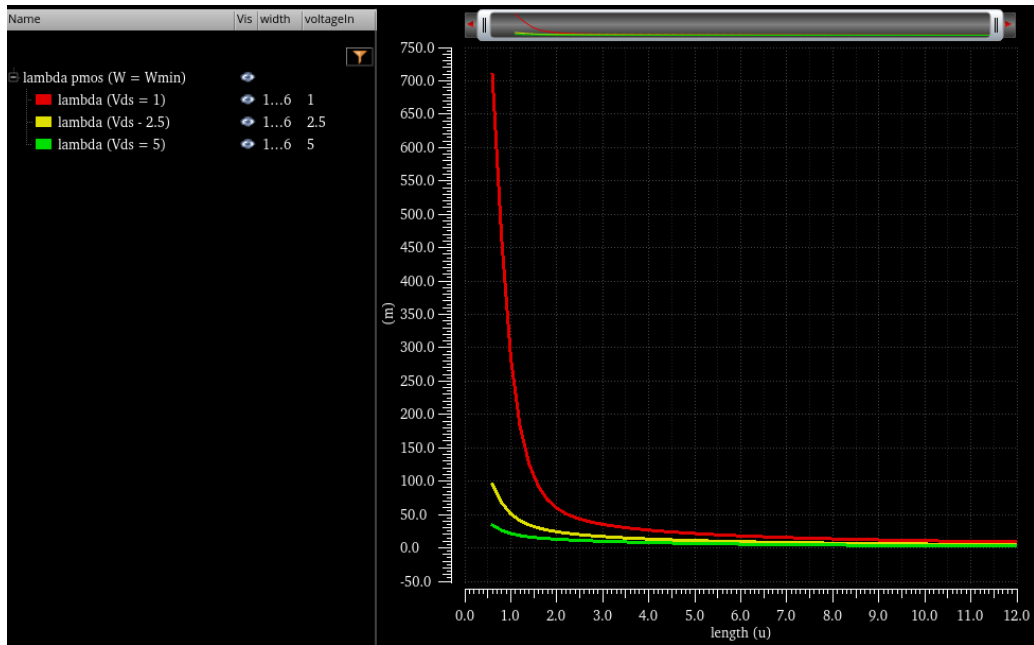

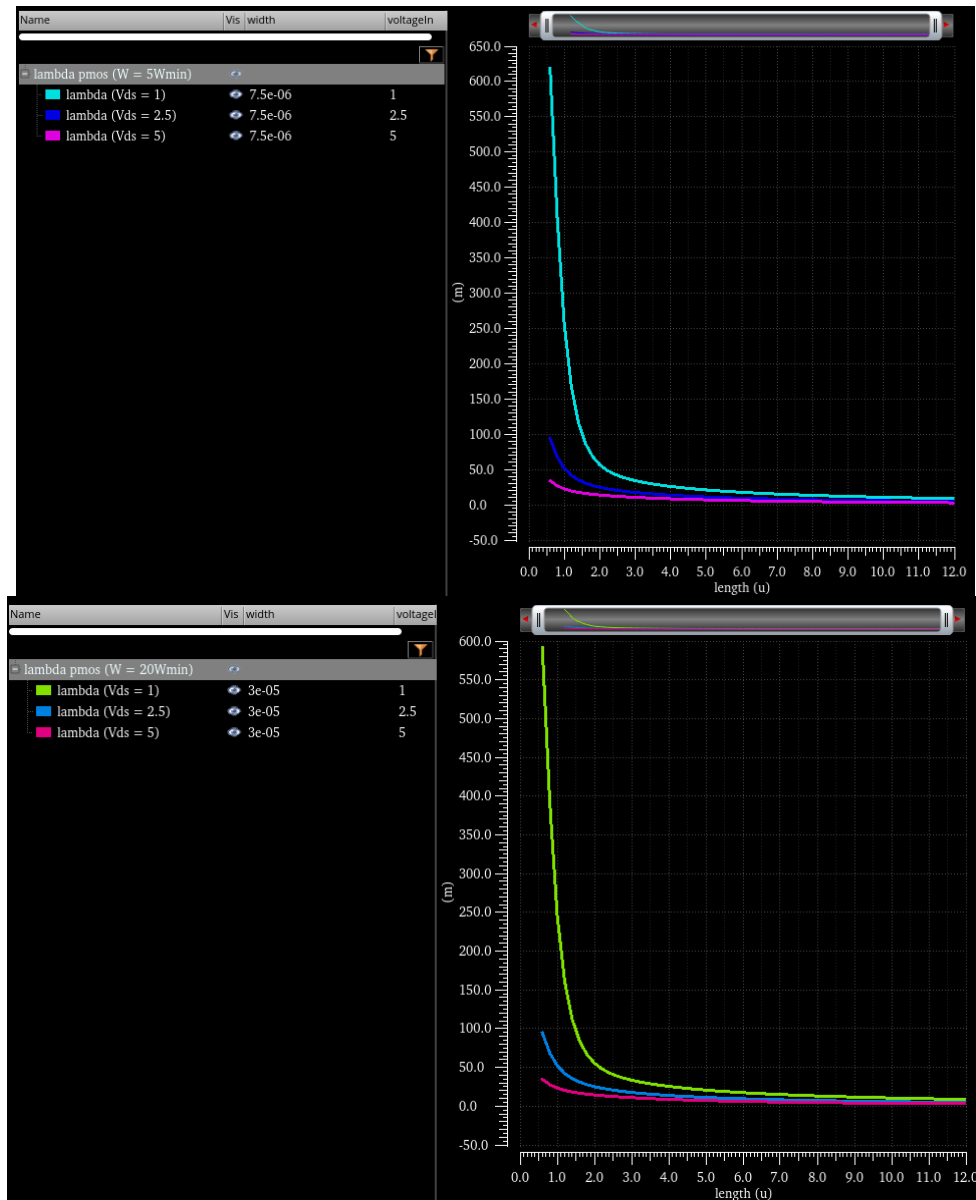

Problem 3

Part A

The current through M1 is $\frac{P}{V_{DD}-V_{SS}} * \frac{1}{2} = 83.33 \mu\text{A}$. So we can find W_1 as foll

$$W_1 = \frac{2IL}{\mu C_{ox} V_{EB}^2} = \frac{2 * 83.3 \mu * 2 \mu}{112.8 \mu * 0.2^2} = 73.84 \mu\text{m}$$

Part B

We know that $V_{EB1} = V_{GS} - V_{Tn} = 0.2\text{V}$. Quiescently, $V_G = 0\text{V}$. So:

$$V_G - V_S - V_{Tn} = -V_S - 0.79\text{V} = 0.2 \rightarrow V_S = -0.99\text{V}$$

Part C

Create an expression for V_{OUT} divided by V_{IN} :

$$g_{m1}V_{IN} = V_{OUT} \left(sC_1 + \frac{1}{R_1} \right)$$

$$A(s) = \frac{g_{m1}}{sC_1 + 1/R_1}$$


Part D

Start by finding the DC gain:

$$A_0 = g_m R_1 = \frac{2 * 83.33 \mu A}{0.2} * 50 k\Omega = 41.665_{10} = 32.39 dB$$

Now find the corner frequency:
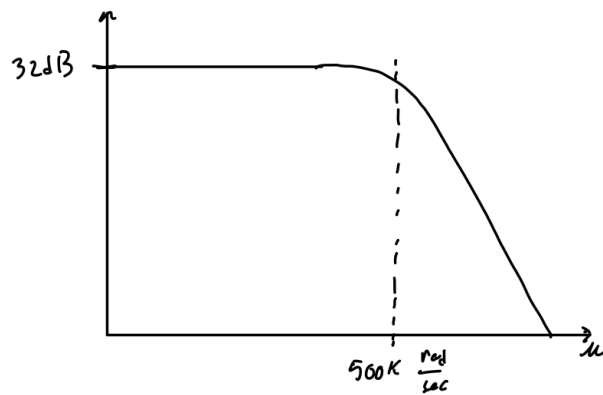
$$sC_1 + \frac{1}{R_0} = 0 \rightarrow s = -\frac{1}{R_1 C_1} = 500 k \text{ rad/sec}$$



Part E

As found in Part D, the 3dB bandwidth is $500 k \text{ rad/sec}$.

Part F

Increasing the power increases the gain-bandwidth, but not the bandwidth. The bandwidth is only dependent on R_1 and C_1 .

Problem 4

Part A

Pole spread, k , is defined simply to be p_2/p_1 . The open-loop amplifier has poles located at $p_2 = 10^4 \text{ rad/sec}$ and $p_1 = 5 \text{ rad/sec}$. The pole spread is then:

$$k = \frac{10^4}{5} = 2000$$

Part B

Begin by finding the amplifier's closed loop transfer function:

$$\begin{aligned} A_{CL}(s) &= \frac{A(s)}{1 + \beta A(s)} = \frac{\frac{10^9}{(s+5)(s+10^4)}}{1 + \frac{\beta 10^9}{(s+5)(s+10^4)}} = \frac{10^9}{(s+5)(s+10^4) + 10^9 \beta} \\ &= \frac{10^9}{s^2 + s(10005) + 50000 + \beta 10^9} \end{aligned}$$

Let $\beta = 0.1$:

$$A_{CL}(s) = \frac{10^9}{s^2 + s(10005) + 50000 + 10^8}$$

To find the pole Q , it is easiest to recall the following standard form:

$$D(s) = s^2 + \frac{p}{Q}s + p^2$$

We can use this to solve for Q :

$$\begin{aligned} p &= \sqrt{50000 + 10^8} \\ \frac{p}{Q} &= \frac{\sqrt{50000 + 10^8}}{Q} = 10005 \rightarrow Q = 0.99975 \end{aligned}$$

Part C

To find overshoot, ζ , start by finding the pole Q again with the new β .

$$\begin{aligned} A_{CL}(s) &= \frac{10^9}{s^2 + s(10005) + 50000 + 5 * 10^8} \\ p &= \sqrt{50000 + 5 * 10^8} \\ \frac{p}{Q} &= \frac{\sqrt{50000 + 5 * 10^8}}{Q} = 10005 \rightarrow Q = 2.235 \end{aligned}$$

Now recall that $\zeta = \frac{1}{2Q}$.

$$\zeta = \frac{1}{2Q} = \frac{1}{4.47} = 0.22$$

Part D

Per Lecture 13, slide 12, to avoid ringing in the step response the pole Q should be $\frac{1}{2}$. We can then work backward to figure out what β gives this pole Q :

$$\frac{p}{Q} = \frac{\sqrt{50000 + \beta 10^9}}{1/2} = 10005 \rightarrow \beta = 0.0249$$

The maximum closed-loop DC gain is $\frac{1}{\beta} = 40$.

Part E

If we assume that the DC gain of the open-loop amplifier is not changed by adjusting the location of p_1 (as stated by the problem), then we can assume A_0 will continue being $20k V/V$. To achieve an optimal response with no ringing, we want a pole spread equal to $4\beta A_0$ (Lecture 13, Slide 12). In our case, $\beta = 1$ and $A_0 = 20kV/V$. So, we need a pole spread of $80k$.

If p_2 remains at 10^4 rad/sec , we can find p_1 easily:

$$k = 80k = \frac{p_2}{p_1} = \frac{10^4}{p_1} \rightarrow p_1 = \frac{10^4}{80k} = 0.125 \text{ rad/sec}$$

The minimal adjustment is then $5 - 0.125 = 4.875 \text{ rad/sec}$.

Problem 5

Part A

Begin by figuring out how much current flows through each branch of the amplifier. Let I_{BRANCH} be the current through the left- and right-most branches ($M_5, M_6, M_8,$ and M_9) and I_{TAIL} be the current through the middle branch (M_7).

The total power consumption of the amplifier structure is given to be $10mW$. The net current is then $I_{NET} = \frac{10mW}{2V} = 5mA$.

Because M_{35} and M_{46} are both given to be 20, we can find the branch and tail current:

$$\begin{aligned} I_{TAIL} + 2I_{BRANCH} &= 5mA \\ I_{TAIL} + 2\left(20 * \frac{I_{TAIL}}{2}\right) &= 5mA \\ I_{TAIL} + 20I_{TAIL} &= 5mA \\ I_{TAIL} &= 238\mu A \\ I_{BRANCH} &= \frac{20I_{TAIL}}{2} = 2.38mA \end{aligned}$$

If I know the V_{EB} and drain current of each MOSFET, I can find the device size easily using the square-law equation for a MOSFET in saturation. Use the process parameters given at the top of the homework. That gives the below results:

Device	W/L
M_1 & M_2	105.77
M_3 & M_4	320.53
M_5 & M_6	6410.77
M_7	211.55
M_8 & M_9	2115.55

Part B

By inspection:

$$A_0 = -\frac{Mg_{m1}}{g_{o6} + g_{o8}}$$

$$GBW = \frac{g_{m1}}{C_L}$$

Recalling that $g_m = \frac{2I_{DQ}}{V_{EB}}$ and $g_o \approx \lambda I_{DQ}$:

$$g_{m1} = \frac{20 * 2 \frac{238\mu A}{2}}{0.15} = 31.72m$$

$$g_{o6} = g_{o8} \approx 0.01V^{-1}I_{BRANCH} = 23.8\mu\Omega^{-1}$$

$$A_0 = -\frac{31.72m}{47.6\mu} = -666 = 56.4dB$$

$$GBW = \frac{31.72m}{10pF} = 3.172G \frac{rad}{sec} = 504.83MHz$$

Part B

$$g_{MEQ} = M * g_{m1} = M * \frac{2I_{DQ}}{V_{EB}} = 20 * 2 * \frac{238\mu A}{0.15} = 31.73mS$$

Problem 6

Part A

Let the positive input to the g_{m2} OTA be V_x . Start by defining two equations for the currents at V_x and V_{OUT} :

$$(V_x - V_{IN})sC_1 + g_{m1}V_{OUT} = 0$$

$$V_{OUT}sC_2 - g_{m2}(V_x - V_{OUT}) = 0$$

Solve the first equation for V_x :

$$V_x sC_1 - V_{IN}sC_1 - g_{m1}V_{OUT} = 0 \rightarrow V_x = \frac{V_{IN}sC_1 - g_{m1}V_{OUT}}{sC_1}$$

Substitute into the second equation:


$$V_{OUT}sC_2 - g_{m2}\left(\frac{V_{IN}sC_1 - g_{m1}V_{OUT}}{sC_1} - V_{OUT}\right) = 0$$

$$V_{OUT}\left(sC_2 + \frac{g_{m2}g_{m1}}{sC_1} + g_{m2}\right) = V_{IN}(g_{m2})$$

$$V_{OUT}\left(\frac{s^2C_1C_2 + g_{m2}g_{m1} + g_{m2}sC_1}{sC_1}\right) = g_{m2}V_{IN}$$

$$\frac{V_{OUT}}{V_{IN}} = T(s) = \frac{sC_1g_{m2}}{s^2C_1C_2 + g_{m2}sC_1 + g_{m2}g_{m1}}$$

Part B

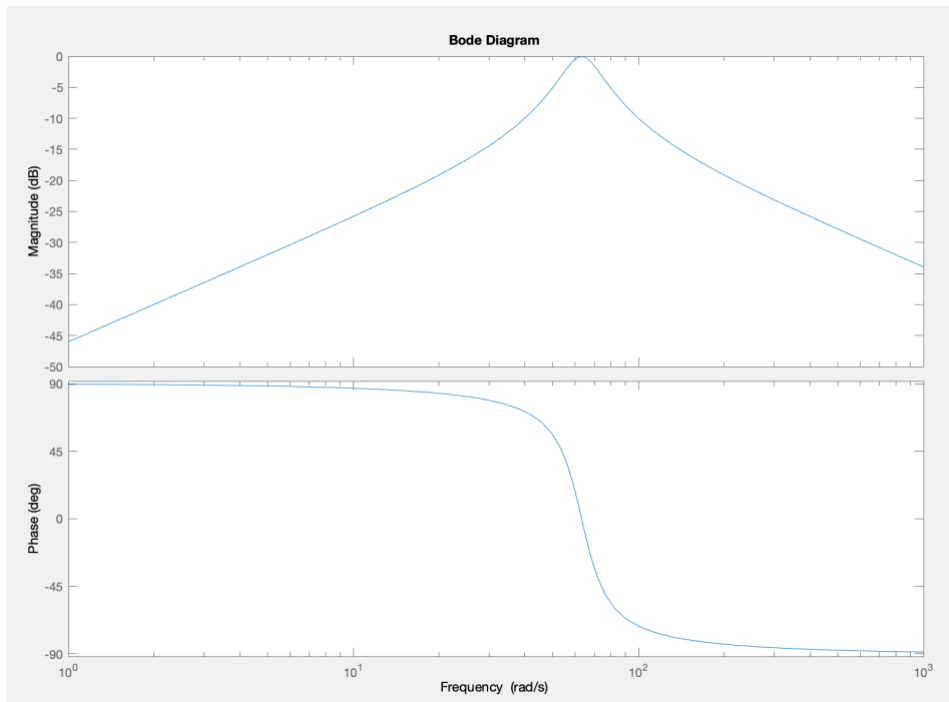

$$g_{m1}$$
$$g_{00} = g_{06}$$

Solution:

a) $V_{B2}-V_{SS}=V_{THn}+V_{EB}$ Thus $V_{B2}=V_{SS}+V_{THn}+V_{EB} = (-1.2+0.5+0.1)V = -0.6V$. By the same argument, $V_{B3} = -0.6V$.

b) For all transistors, $I_D = \frac{\mu C_{OX} W}{2L} V_{EB}^2$. Thus $\frac{W}{L} = \frac{2I_D}{\mu C_{OX} V_{EB}^2}$. Since 1mW is dissipated in each stage and since the total supply voltage is 2.4V, it follows that $I_7=I_{D6}=0.417mA$ and $I_{D1}=0.209 mA$. It thus follows that $W1/L1=139$, $W3/L3=417$, $W7/L7=278$, $W5/L5=834$ and $W6/L6=278$.

$$c) A_0 = \frac{4}{(\lambda_n + \lambda_p)^2 V_{EB1} V_{EB5}} = \frac{4}{.02^2 0.1^2} = 10^6$$

d)

$$C_C = \frac{C_L 2\theta(1-\theta)\beta}{Q^2} \frac{V_{EB1}|V_{EB5}|}{(V_{EB1}2\theta-\beta|V_{EB5}|(1-\theta))^2}$$

With $\theta=0.5$, it follows that and $C_L=100fF$, it follows that $C_C=24.7fF$

e) $g_{m5}=2I_{DQ5}/V_{EB}$ $I_{DQ5} * 2.4V = 1mW$ so $I_{DQ5}=0.42mA$
thus $g_{m5}=8.4E-3 AV^{-1}$