

# EE 435

## Lecture 20

### Linearity in Operational Amplifiers -- The differential pairs

# Lecture 19 executive summary

Thank You Robert

## Assessing open loop gain:

- Break the loop at input or output (for voltage series, current series, break loop at output and measure  $v_{out}$ ; for current-shunt and voltage-shunt measure  $i_{out}$ )
- Test bench for  $A_{V0}$  should use a test network that does not affect open loop gain as the  $\beta$  network could be unstable

## Gain enhancement strategies:

- Change excitation by decreasing the denominator and/or increasing numerator of  $A_{V0}$  which almost doubles gain and GB by including  $g_m$  of the counterpart circuit in the numerator
- Drive counterpart circuit with  $-V_{out}$ , DC gain now subtracts  $g_{MCC}$  from denominator of CC


## Regenerative Feedback:

- Gain can be made arbitrarily large by selecting  $g_{mP1}$  correctly; GB does not degrade
- Cross coupling outputs in a differential structure has the same effect as using two amplifiers
- Infinite DC gain when  $g_{mp1} = g_{of1} + g_{op1}$
- If  $g_{mp1} > g_{of1} + g_{op1}$  the amp will be unstable because the pole will be in the RHP
- Feedback amp is usually stable even if open loop amp is unstable because the numerator of  $A_v$  doesn't change signs when the constant changes signs
- feedback performance can actually be enhanced if the open-loop amplifier is unstable because the right half plane pole has better settling time

## Alternative positive feedback amplifier

- requires precise matching of  $g_{m4}$  to  $(g_{o2} + g_{o4} + g_{o6})$  for good gain enhancement, which is difficult to do
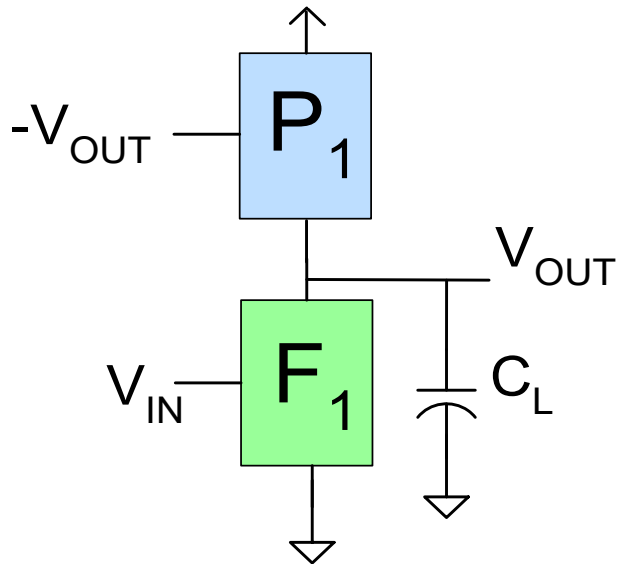
# Gain Enhancement with Regenerative Feedback



$$A_{V0} = \frac{-g_{mF1}}{sC_L + g_{oF1} + g_{oP1} - g_{mP1}}$$

$$A_{V0} = \frac{g_{mF1}}{g_{oF1} + g_{oP1} - g_{mP1}}$$

$$BW = \frac{g_{oF1} + g_{oP1} - g_{mP1}}{C_L}$$

$$GB = \frac{g_{mF1}}{C_L}$$



The gain can be made arbitrarily large by selecting  $g_{mP1}$  appropriately



The GB does not degrade !

But - can we easily build circuits with this property?
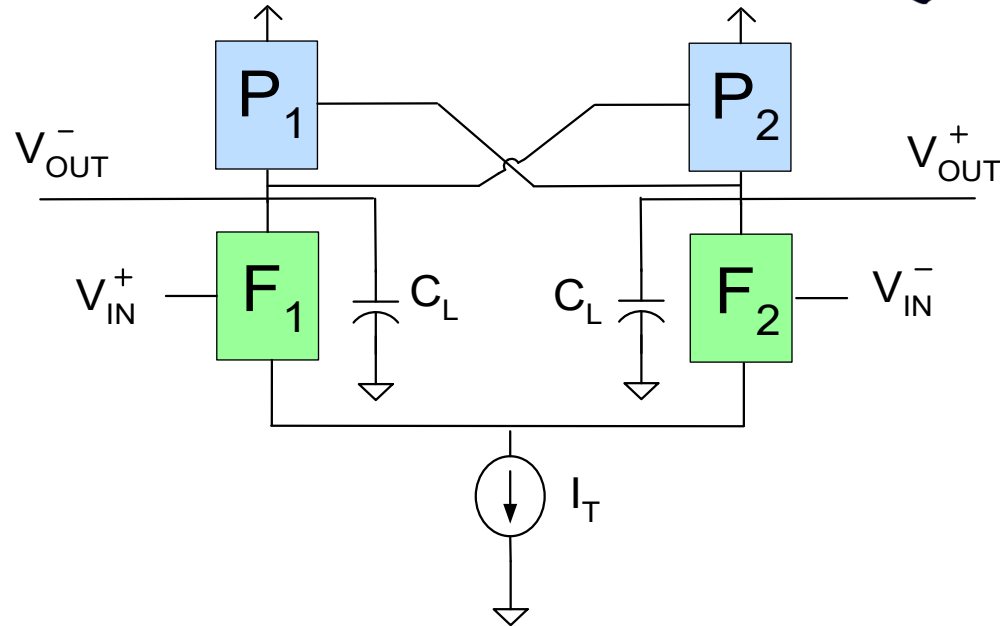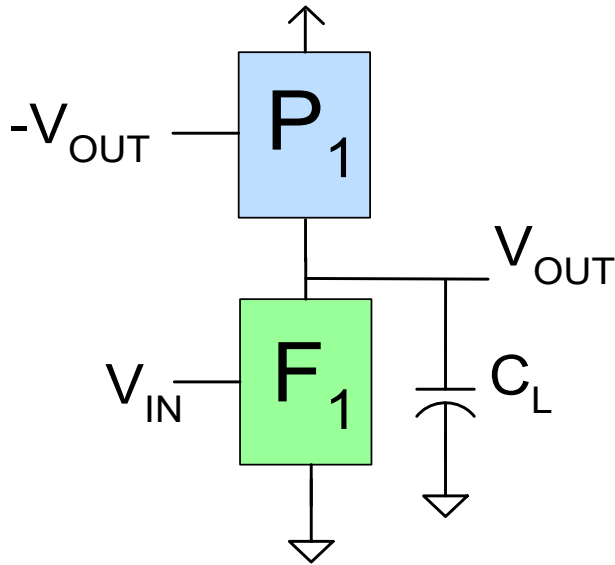
# Gain Enhancement with Regenerative Feedback



But - can we easily build circuits with this property?




Review from last lecture . . . . .

But – the inverting amplifier may be more difficult to build than the op amp itself!

**YES – simply by cross-coupling the outputs in a fully differential structure**
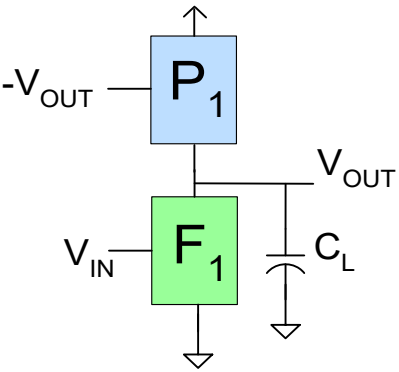
# Gain Enhancement with Regenerative Feedback




It can be shown that the feedback amplifier is usually stable even if the open-loop Op amp is unstable



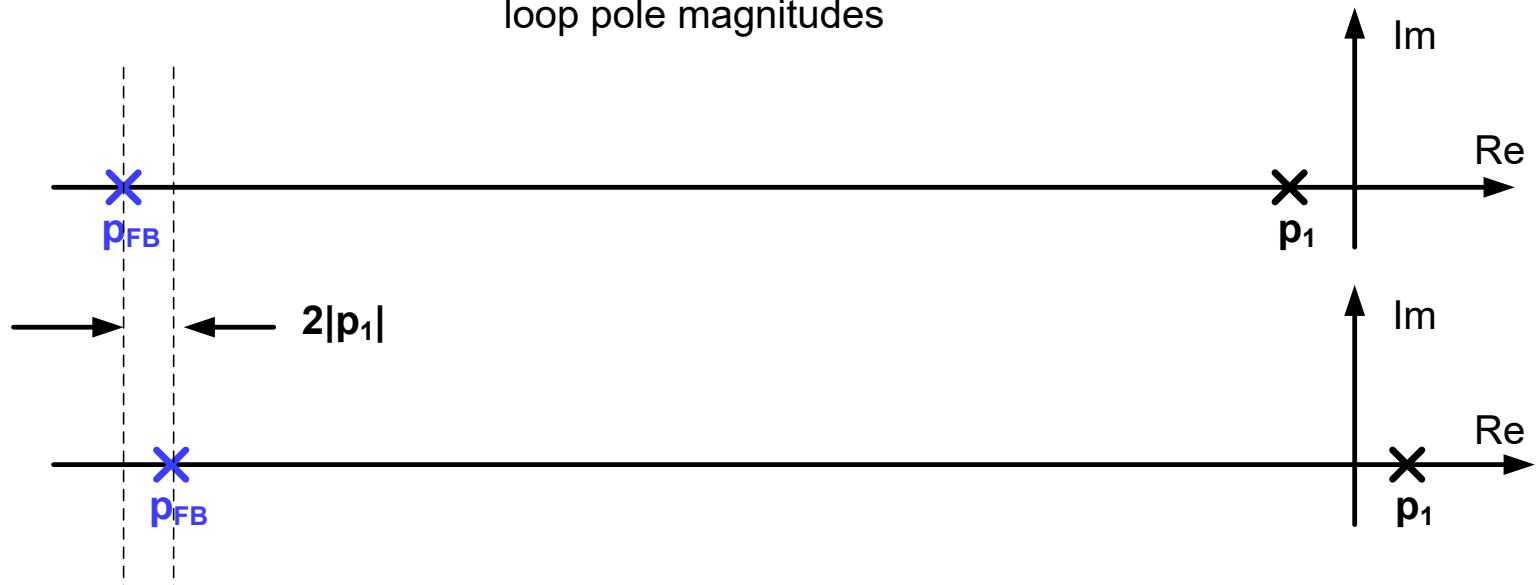**How?**

$$p_{FB} = \begin{cases} -\tilde{p}_1 (1 + \beta A_{V0}) = p_1 (1 + \beta A_{V0}) & \text{for } p_1 < 0 \\ -\tilde{p}_1 (1 - \beta A_{V0}) = p_1 (1 - \beta A_{V0}) & \text{for } p_1 > 0 \end{cases}$$

Open-Loop and Closed-Loop Pole Plot for equal open-loop pole magnitudes




# Gain Enhancement with Regenerative

## Feedback

The feedback performance can actually be enhanced if the open-loop amplifier is unstable

Why?

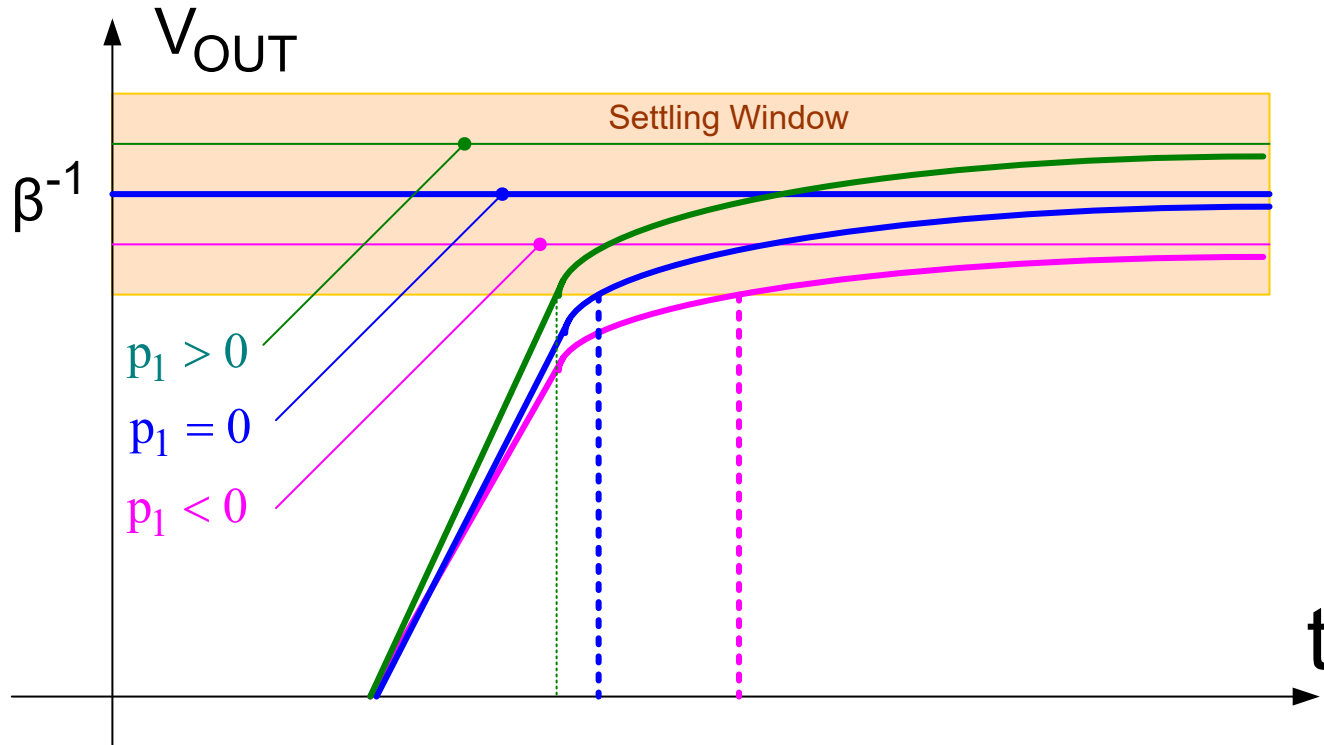

- Time required to get in settling window can be reduced with RHP pole
- But, if pole is too far in RHP, response will exit top of window

# Up to this point all analysis of the op amp has focused on small-signal gain characteristics

Linearity of the amplifier does play a role in linearity and spectral performance of feedback amplifiers

Linearity is of major concern when the op amp is used open-loop such as in OTA applications

A major source of linearity is often associated with the differential input pair

Will consider linearity of the input differential pairs

# Signal Swing and Linearity


Signal swing identifies range over which signals can be applied and still maintain operation of devices in desired region of operation

Some subset of the signal swing range will be quite linear

Often that subset is close to the entire signal swing range




# Signal Swing and Linearity

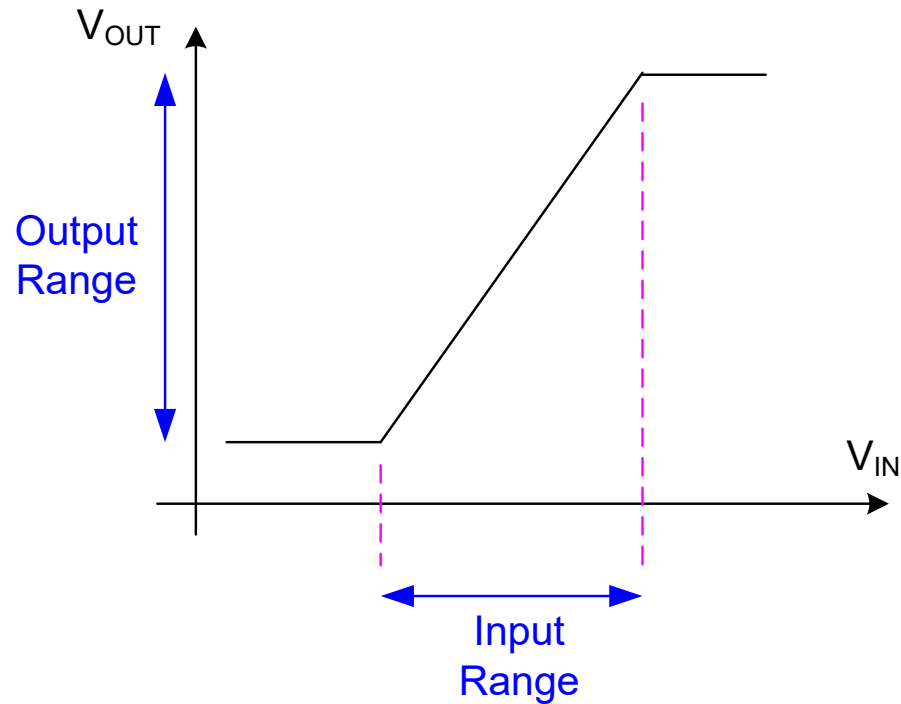

Ideal Scenario:

Completely Linear over Input and Output Range



# Signal Swing and Linearity

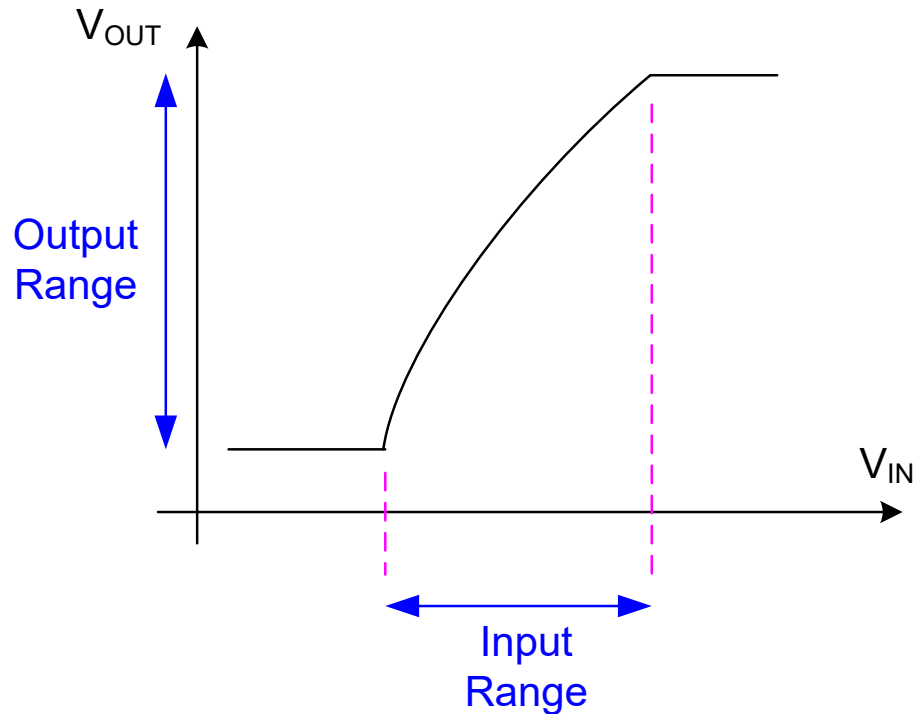


Realistic Scenario:

- Modest Nonlinearity throughout Input Range
- But operation will be quite linear over subset of this range

# Signal Swing and Linearity

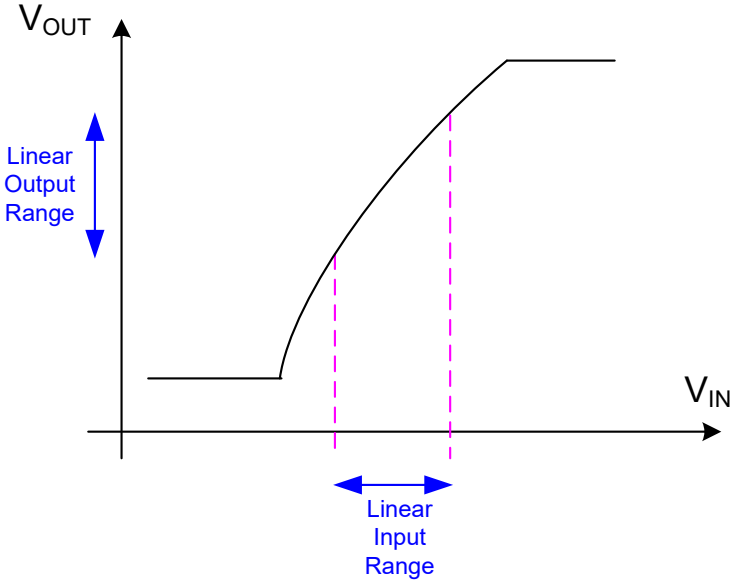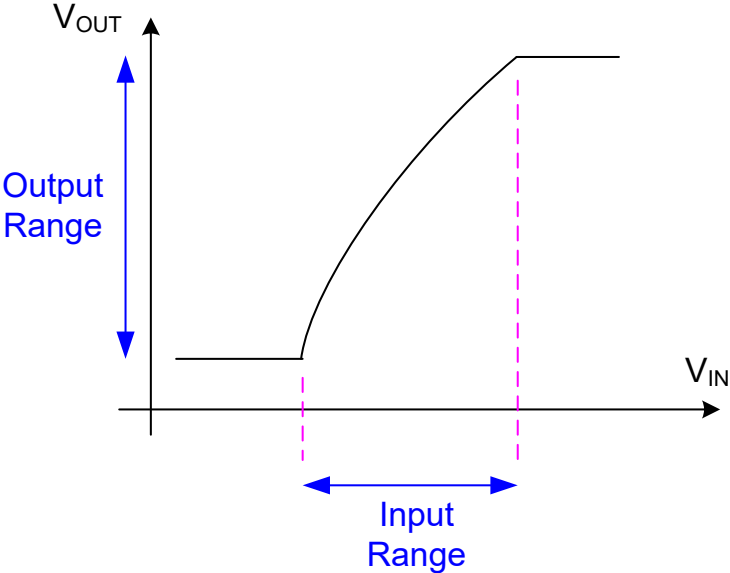


# Linearity of Amplifiers

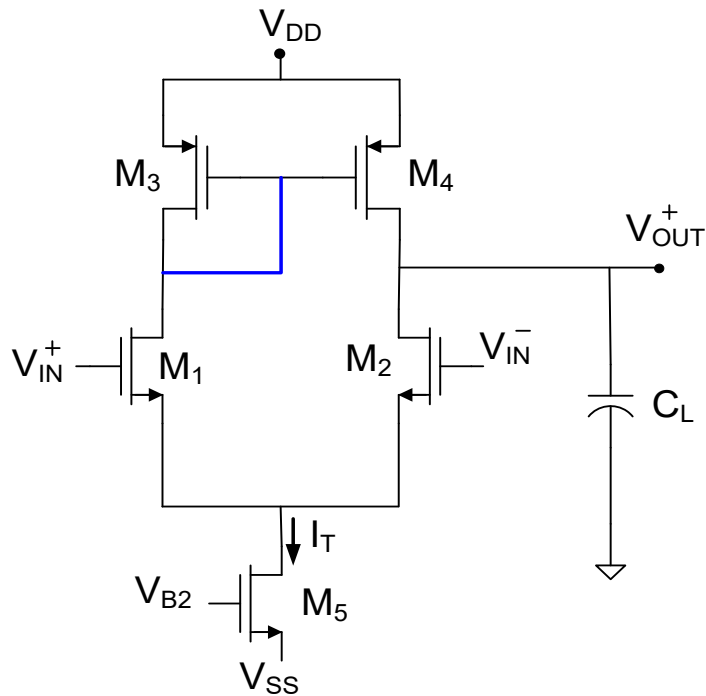

Single-Stage

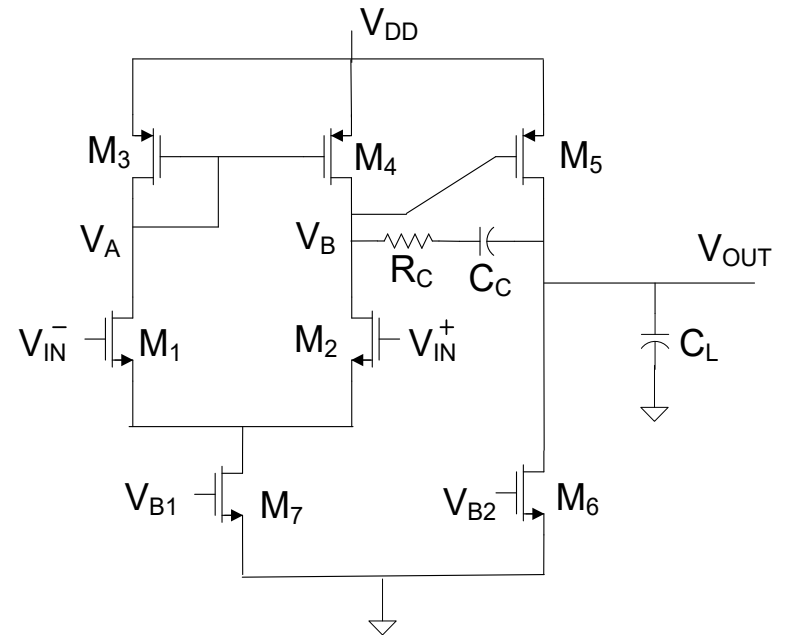
Linearity of differential pair of major concern




Two-Stage

Linearity of common-source amplifier is of major concern (since signals so small at output of differential pair)

# Differential Input Pairs

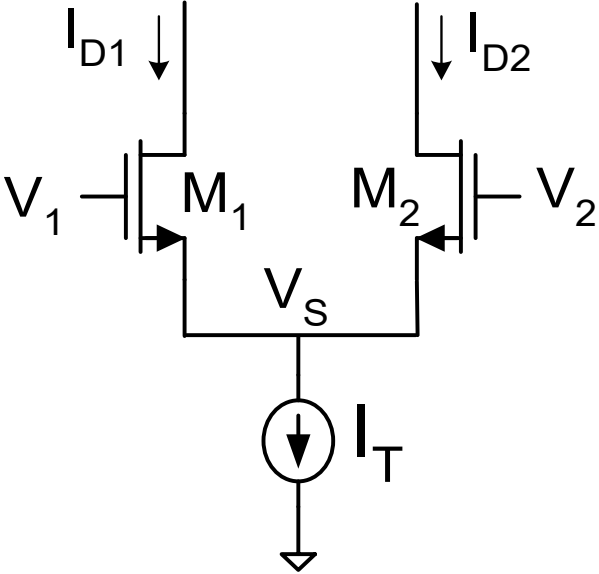


MOS Differential Pair

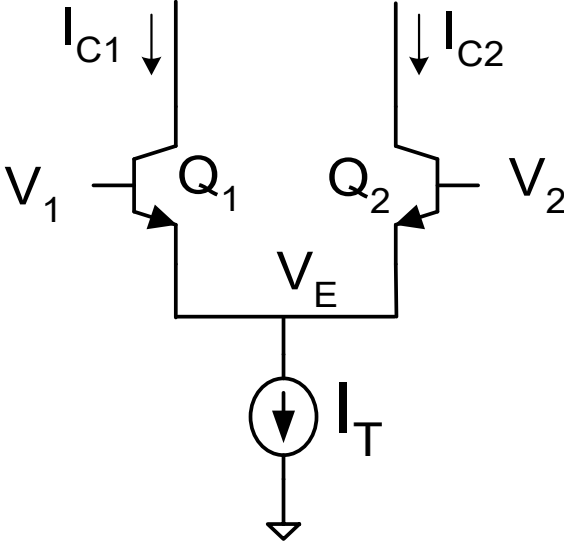

Bipolar Differential Pair

# MOS Differential Pair

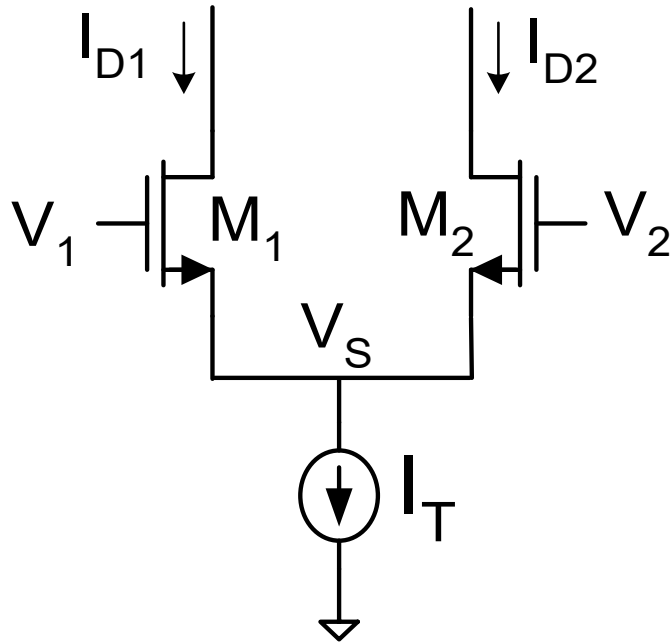

$$I_{D1} = \frac{\mu C_{OX} W}{2L} (V_1 - V_S - V_T)^2$$

$$I_{D2} = \frac{\mu C_{OX} W}{2L} (V_2 - V_S - V_T)^2$$

$$I_{D1} + I_{D2} = I_T$$

$$\pm \sqrt{I_{D1}} \sqrt{\frac{2L}{\mu C_{OX} W}} = V_1 - V_S - V_T$$

$$\pm \sqrt{I_{D2}} \sqrt{\frac{2L}{\mu C_{OX} W}} = V_2 - V_S - V_T$$



$$V_d = V_2 - V_1$$

$$V_d = \pm \sqrt{\frac{2L}{\mu C_{OX} W}} (\sqrt{I_T - I_{D1}} - \sqrt{I_{D1}})$$

$$V_d = \pm \sqrt{\frac{2L}{\mu C_{OX} W}} (\sqrt{I_{D2}} - \sqrt{I_T - I_{D2}})$$
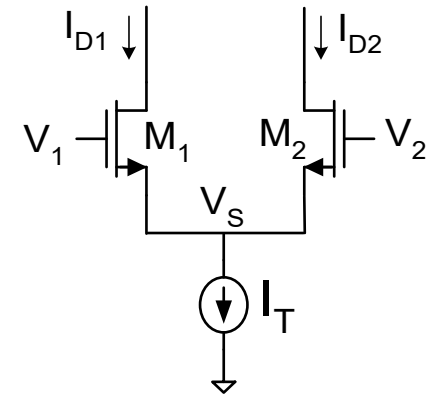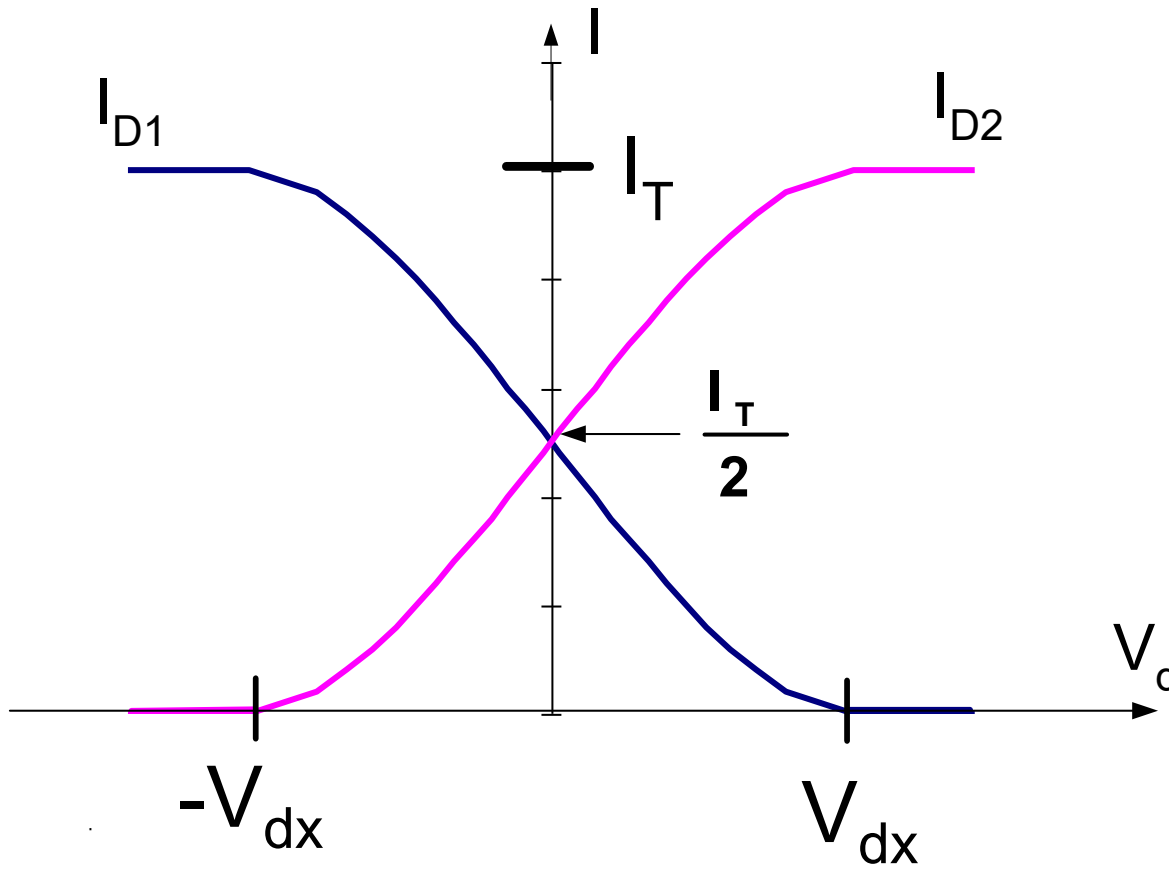
# Transfer Characteristics of MOS Differential Pair


$$V_d = \pm \sqrt{\frac{2L}{\mu C_{ox} W}} \left( \sqrt{I_{D2}} - \sqrt{I_T - I_{D2}} \right)$$


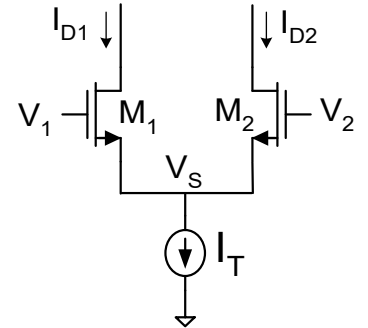
# MOS Differential Pair

$$V_d = \pm \sqrt{\frac{2L}{\mu C_{OX} W}} \left( \sqrt{I_T - I_{D1}} - \sqrt{I_{D1}} \right)$$

$$V_d = \pm \sqrt{\frac{2L}{\mu C_{OX} W}} \left( \sqrt{I_{D2}} - \sqrt{I_T - I_{D2}} \right)$$



What values of  $V_d$  will cause all of the current to be steered to the left or the right ?



Setting  $I_{D1}=0$  obtain:

$$V_{dx} = \pm \sqrt{\frac{2L}{\mu C_{OX} W}} \left( \sqrt{I_T} \right)$$



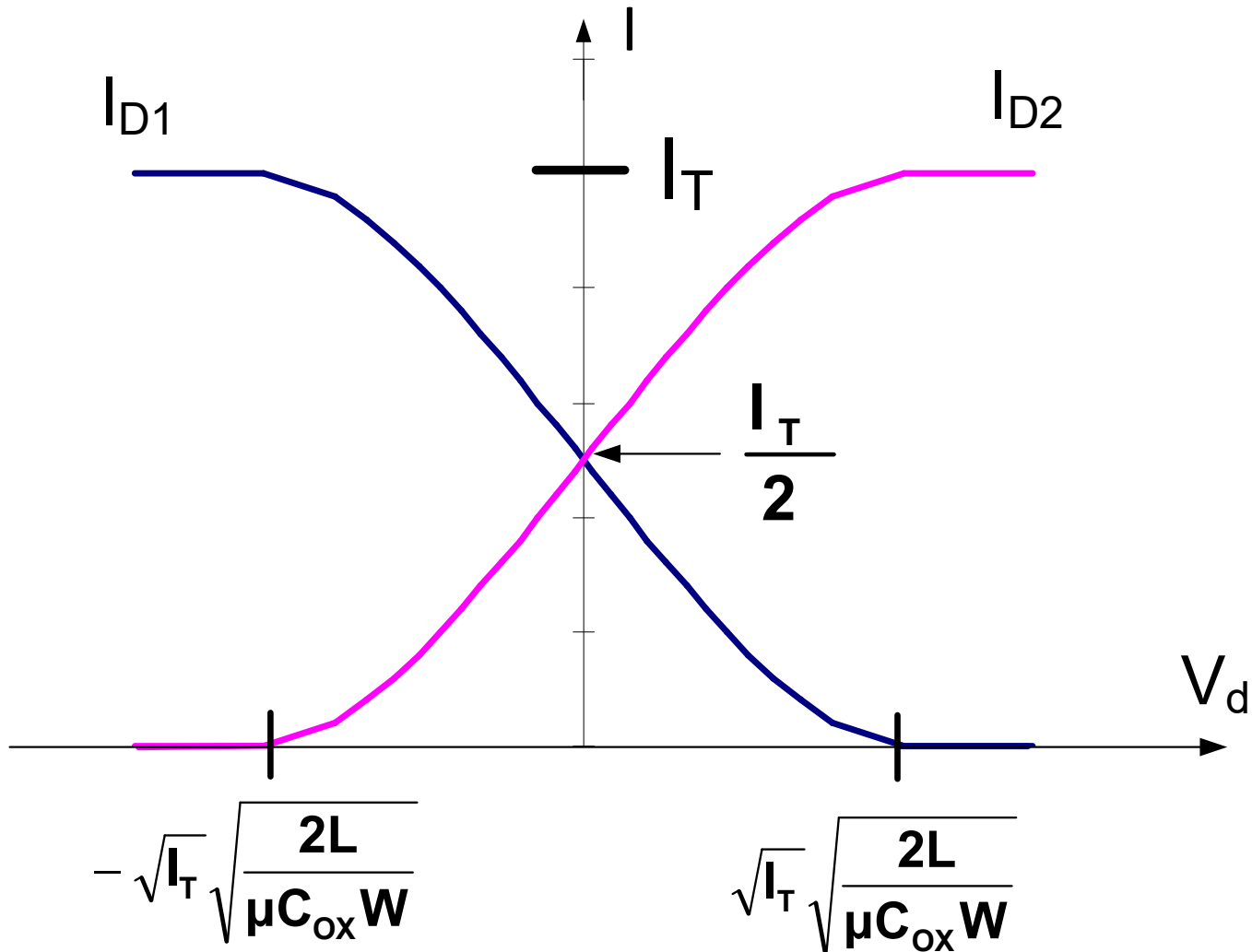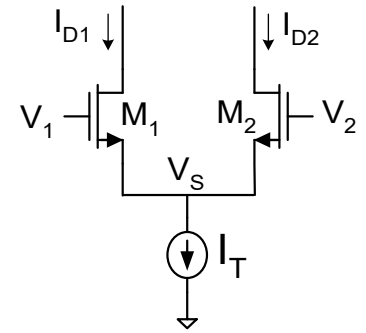
# Transfer Characteristics of MOS Differential Pair

$$V_d = \sqrt{\frac{2L}{\mu C_{ox} W}} \left( \sqrt{I_{D2}} - \sqrt{I_T - I_{D2}} \right)$$



## Q-point Calculations

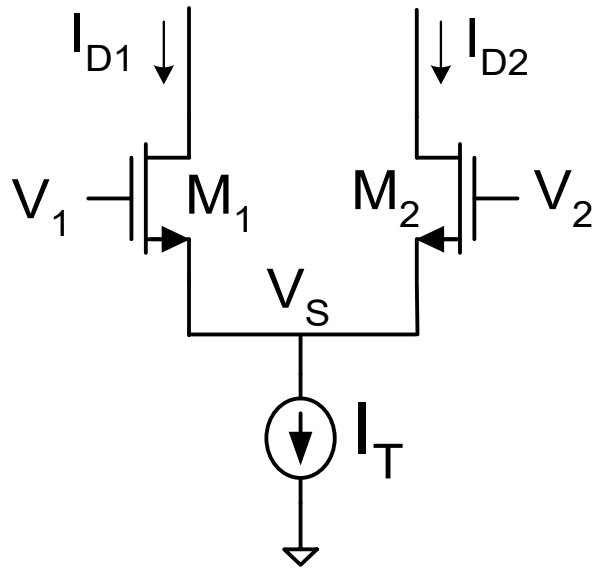

$$V_{dx} = \pm \sqrt{\frac{2L}{\mu C_{ox} W}} (\sqrt{I_T})$$

- Have naturally expressed  $V_{dx}$  in natural parameter domain
- This expression does not provide good insight into actual swing

From device model:

$$\frac{I_T}{2} = \frac{\mu C_{ox} W}{2L} (V_{EB})^2$$





$$V_{EB} = \sqrt{I_T} \sqrt{\frac{L}{\mu C_{ox} W}}$$

Observe !!

$$V_{dx} = \pm \sqrt{2} V_{EB}$$
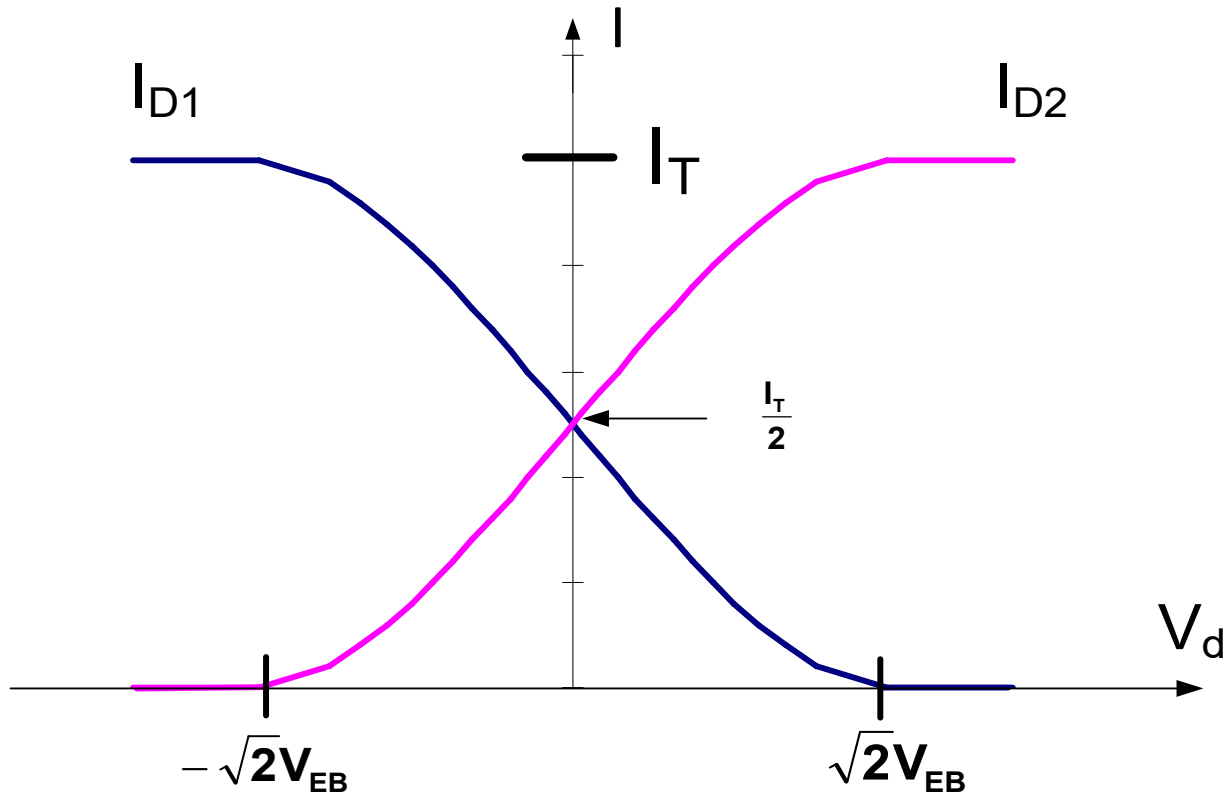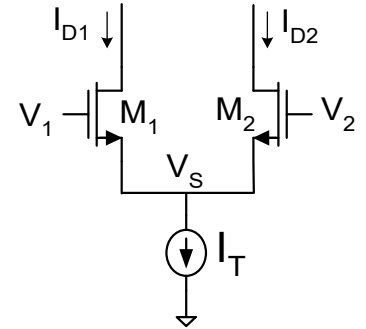
# Transfer Characteristics of MOS Differential Pair


$$V_d = \sqrt{\frac{2L}{\mu C_{ox} W}} \left( \sqrt{I_{D2}} - \sqrt{I_T - I_{D2}} \right)$$




$V_{EB}$  affects linearity

How linear is the amplifier ?

# How linear is the amplifier ?

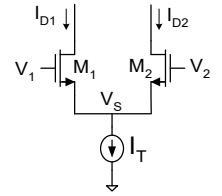

$$I = mV_d + h$$

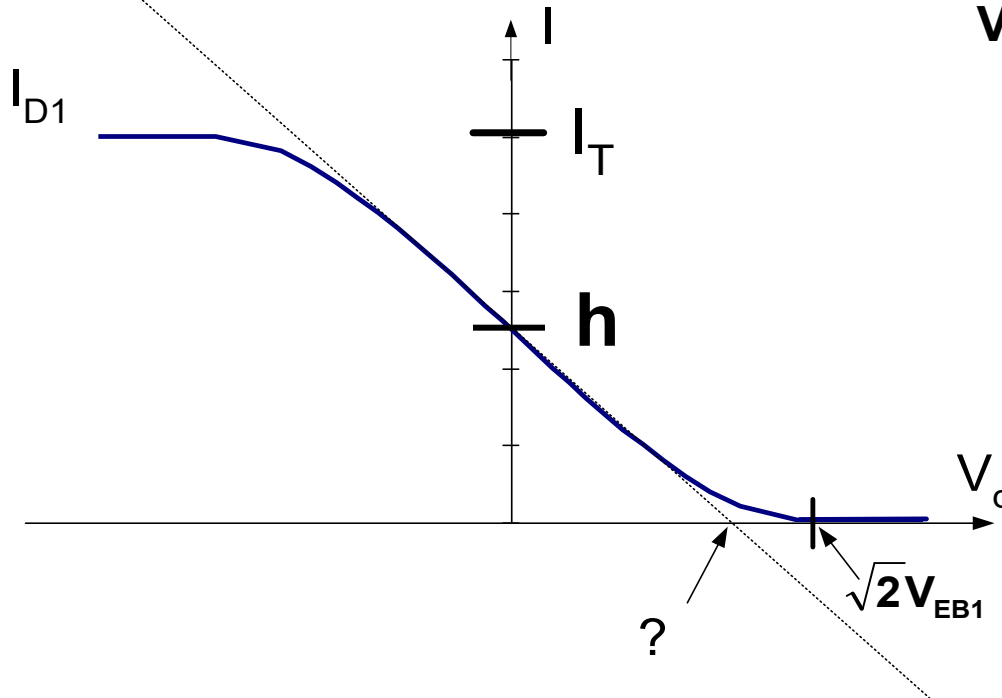

$$V_d = \sqrt{\frac{2L}{\mu C_{ox} W}} \left( \sqrt{I_T - I_{D1}} - \sqrt{I_{D1}} \right)$$

Consider the fit line:

$$I = mV_d + h$$

When  $V_d=0$ ,  $I=I_T/2$ , thus



$$h = \frac{I_T}{2}$$

$$V_{dint} = -\frac{h}{m} = -\frac{I_T}{2m}$$

$$m = \left. \frac{\partial I_{D1}}{\partial V_d} \right|_{Q-pt}$$

$$Q-pt = (0, h)$$

# How linear is the amplifier ?

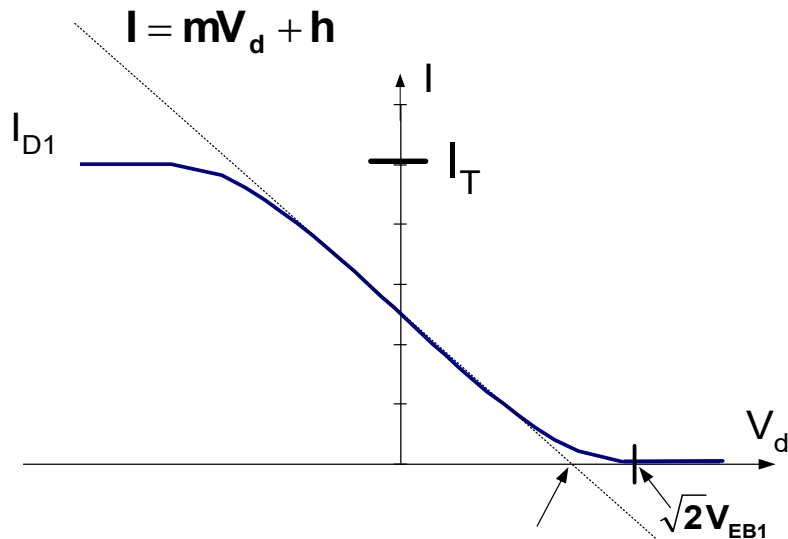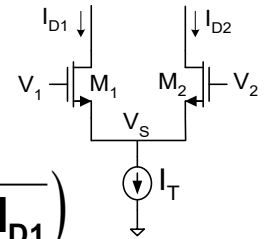

$$V_{dint} = -\frac{I_T}{2m} = V_{EB1}$$

$$V_{dint} = -\frac{h}{m} = -\frac{I_T}{2m}$$

Thus fit line is:

$$I = -\frac{I_T}{2V_{EB1}} V_d + \frac{I_T}{2}$$

$$V_d = \sqrt{\frac{2L}{\mu C_{ox} W}} \left( \sqrt{I_T - I_{D1}} - \sqrt{I_{D1}} \right)$$

$$m = \left. \frac{\partial I_{D1}}{\partial V_d} \right|_{Q-pt}$$

$$\frac{\partial V_d}{\partial I_{D1}} = \sqrt{\frac{2L}{\mu C_{ox} W}} \left( \frac{1}{2} (I_T - I_{D1})^{-1/2} (-1) - \frac{1}{2} (I_{D1})^{-1/2} \right) \Bigg|_{Q-point}$$



$$\frac{\partial V_d}{\partial I_{D1}} = -2 \sqrt{\frac{L}{\mu C_{ox} W}} \sqrt{\frac{1}{I_T}}$$

$$\sqrt{\frac{L}{\mu C_{ox} W}} = \frac{V_{EB1}}{\sqrt{I_T}}$$

$$\frac{\partial V_d}{\partial I_{D1}} = -2 \frac{V_{EB1}}{I_T}$$

$$m = \left. \frac{\partial I_{D1}}{\partial V_d} \right|_{Q-pt} = -\frac{I_T}{2V_{EB1}}$$



# How linear is the amplifier ?

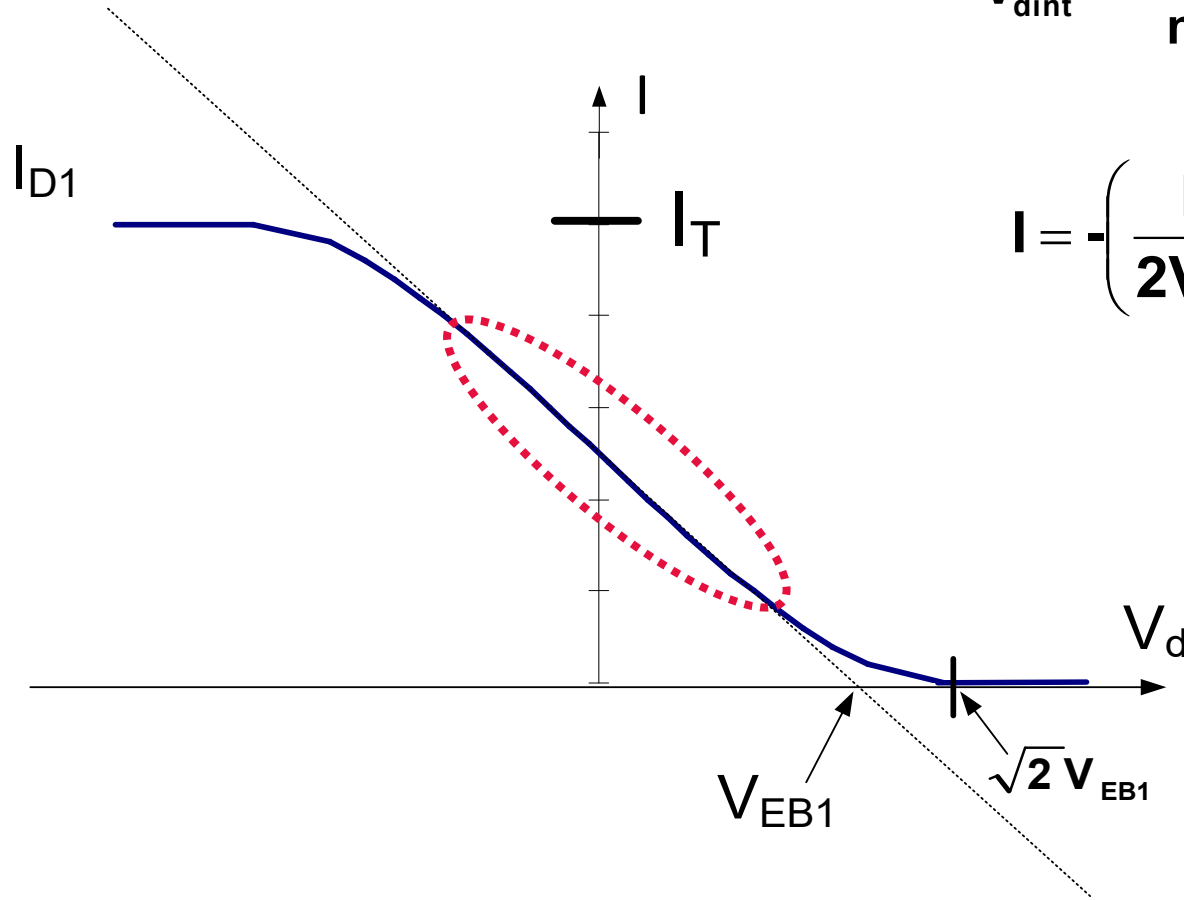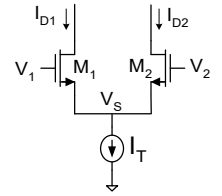

$$V_{dint} = -\frac{h}{m} = -\frac{I_T}{2m} = V_{EB1}$$

$$I = -\left(\frac{I_T}{2V_{EB1}}\right)V_d + \frac{I_T}{2}$$



# How linear is the amplifier ?

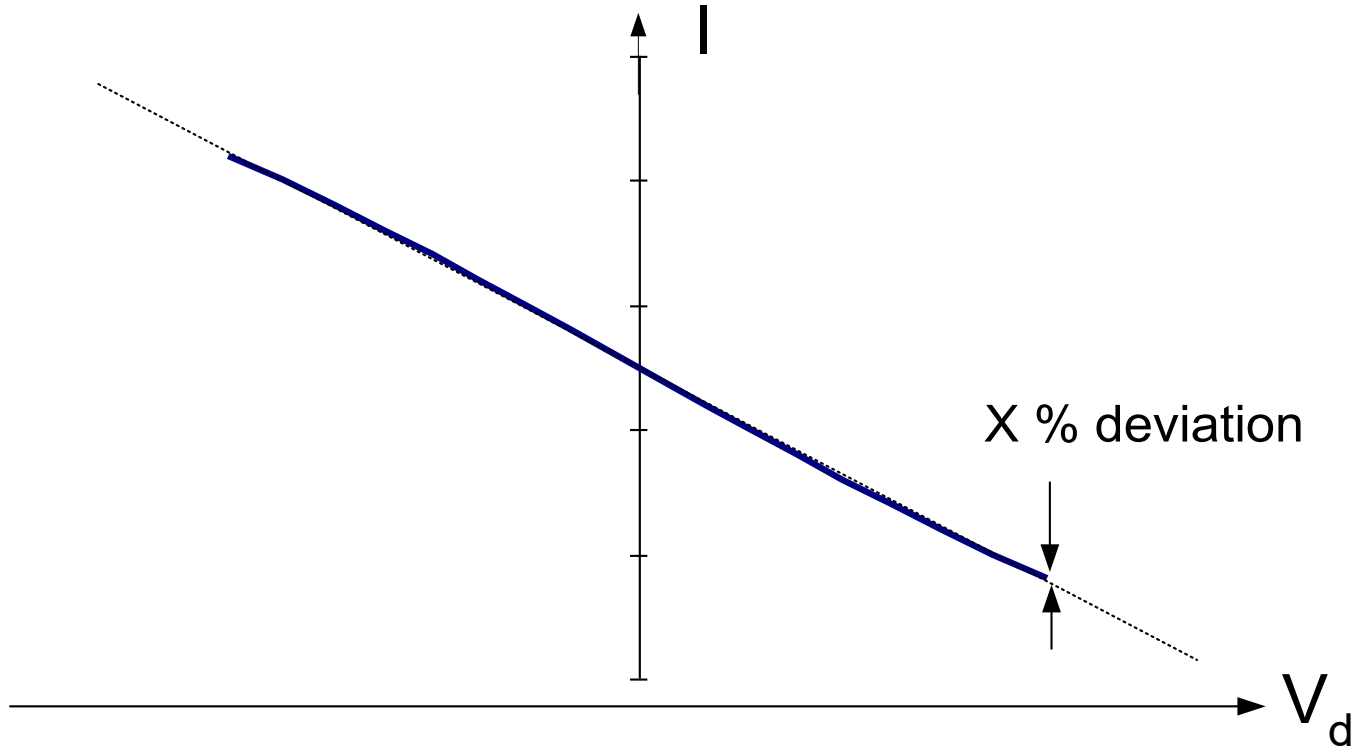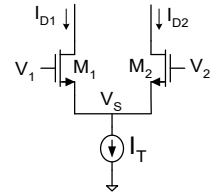

It can be shown that a 1% deviation from the straight line occurs at

$$V_d \cong \frac{V_{EB}}{3} \quad \text{and a 0.1% variation occurs at} \quad V_d \cong \frac{V_{EB}}{10}$$



# How linear is the amplifier ?

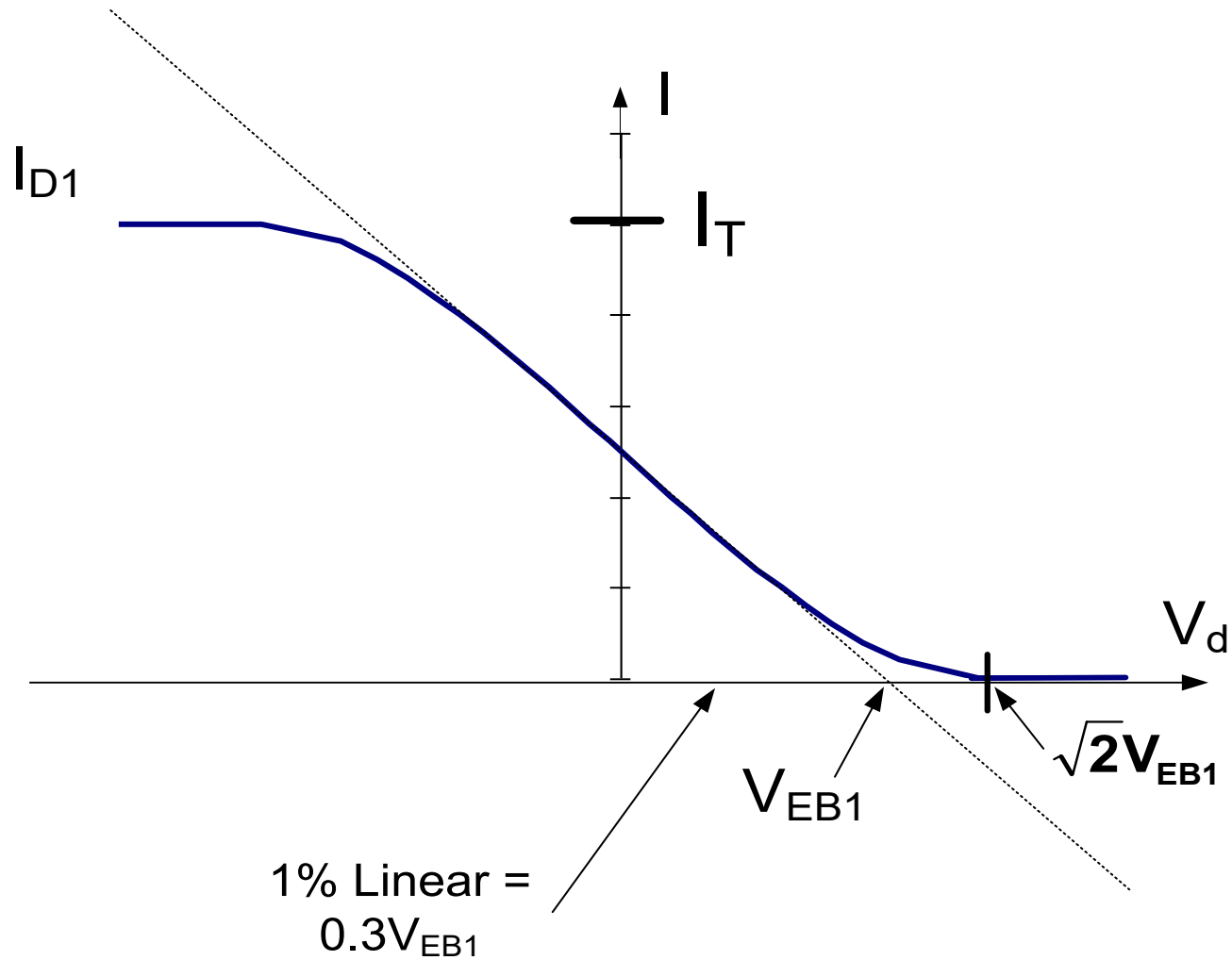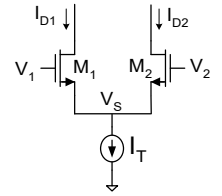



# How linear is the amplifier ?

Deviation from Linear

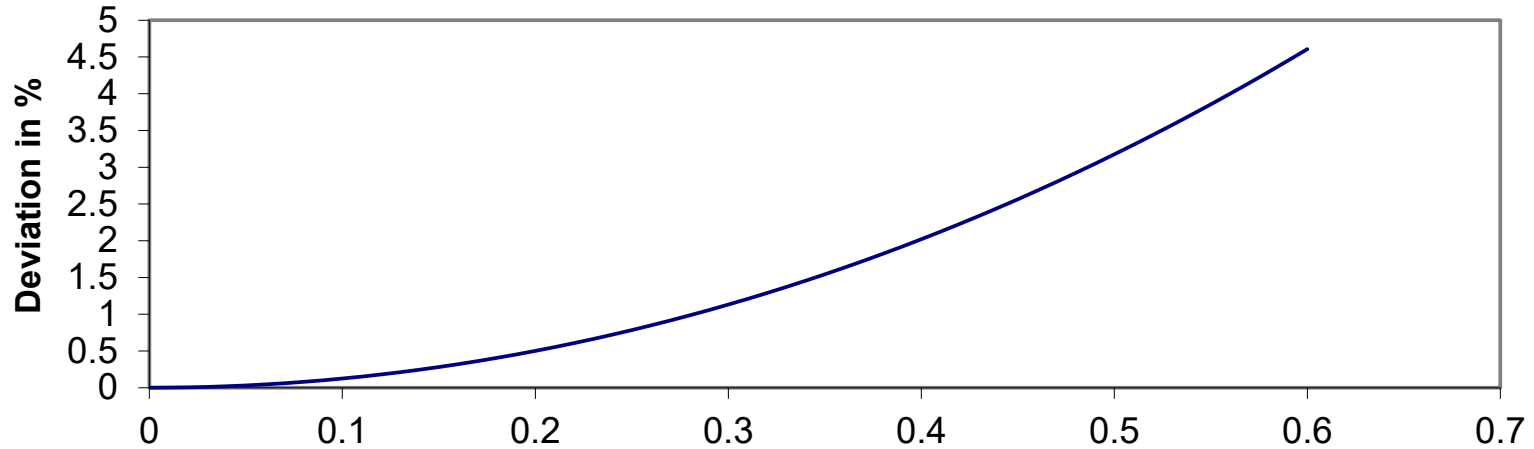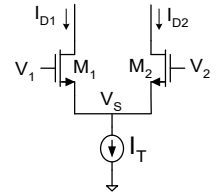

Vd/VEB					
Vd/VEB	$\theta$	Vd/VEB	$\theta$	Vd/VEB	$\theta$
0.02	0.005	0.22	0.607	0.42	2.23
0.04	0.020	0.24	0.723	0.44	2.45
0.06	0.045	0.26	0.849	0.46	2.68
0.08	0.080	0.28	0.985	0.48	2.92
0.1	0.125	0.3	1.13	0.5	3.18
0.12	0.180	0.32	1.29	0.52	3.44
0.14	0.245	0.34	1.46	0.54	3.71
0.16	0.321	0.36	1.63	0.56	4.00
0.18	0.406	0.38	1.82	0.58	4.30
0.2	0.501	0.4	2.02	0.6	4.61


# How linear is the amplifier ?

Distortion in the differential pair is another useful metric for characterizing linearity of  $I_{D1}$  and  $I_{D2}$  with sinusoidal differential excitation

Consider again the differential pair and assume excited differentially with

$$V_2 = \frac{V_d}{2} \quad V_1 = -\frac{V_d}{2}$$

and assume  $V_d = V_m \sin(\omega t)$

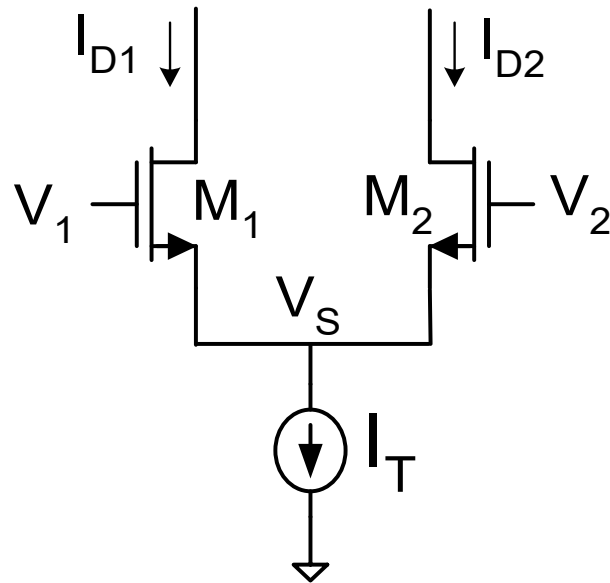

$$V_d = V_2 - V_1$$

Recall:

$$V_d = \sqrt{\frac{2L}{\mu C_{OX} W}} \left( \sqrt{I_{D2}} - \sqrt{I_T - I_{D2}} \right)$$

Define (strictly for notational convenience)

$$\theta = \frac{\mu C_{OX} W}{2L}$$


Thus can express as

$$\sqrt{\theta} V_d = \sqrt{I_{D2}} - \sqrt{I_T - I_{D2}}$$
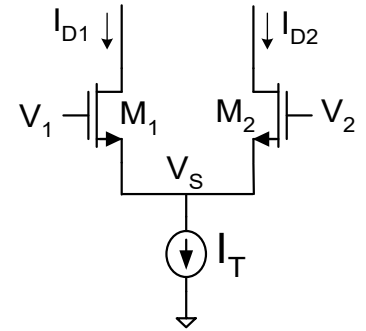
# How linear is the amplifier ?

$$V_d = V_m \sin(\omega t) \quad \theta = \frac{\mu C_{OX} W}{2L}$$

$$\sqrt{\theta} V_d = \sqrt{I_{D2}} - \sqrt{I_T - I_{D2}}$$



Squaring, regrouping, and squaring we obtain

$$\theta V_d^2 = I_{D2} + (I_T - I_{D2}) - 2\sqrt{I_{D2}} \sqrt{I_T - I_{D2}}$$

$$\theta V_d^2 = I_T - 2\sqrt{I_{D2}} \sqrt{I_T - I_{D2}}$$


$$(\theta V_d^2 - I_T)^2 = 4I_{D2} (I_T - I_{D2})$$

This latter equation can be expressed as a second-order polynomial in  $I_{D2}$  as

$$I_{D2}^2 - I_{D2} I_T + \left( \frac{\theta V_d^2 - I_T}{2} \right)^2 = 0$$
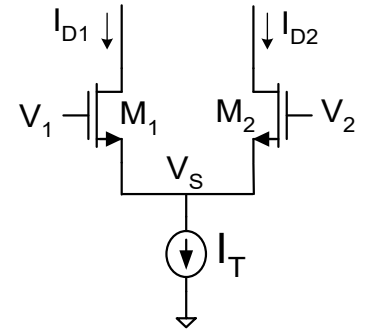
# How linear is the amplifier ?

and assume  $V_d = V_m \sin(\omega t)$        $\theta = \frac{\mu C_{ox} W}{2L}$



$$I_{D2}^2 - I_{D2} I_T + \left( \frac{\theta V_d^2 - I_T}{2} \right)^2 = 0$$

Solving, we obtain

$$I_{D2} = \frac{I_T}{2} + \sqrt{\left( \frac{I_T}{2} \right)^2 - \left( \frac{\theta V_d^2 - I_T}{2} \right)^2}$$

$$I_{D2} = \frac{I_T}{2} + \sqrt{\left( \frac{I_T}{2} \right)^2 - \left( \frac{\theta V_d^2}{2} \right)^2 - \left( \frac{I_T}{2} \right)^2 + \frac{\theta I_T}{2} V_d^2}$$

$$I_{D2} = \frac{I_T}{2} + \sqrt{\frac{\theta I_T}{2} V_d^2 - \left( \frac{\theta V_d^2}{2} \right)^2}$$

# How linear is the amplifier ?

and assume  $V_d = V_m \sin(\omega t)$        $\theta = \frac{\mu C_{ox} W}{2L}$

$$I_{D2} = \frac{I_T}{2} + \sqrt{\frac{\theta I_T}{2} V_d^2 - \left(\frac{\theta V_d^2}{2}\right)^2}$$

This can be expressed as

$$I_{D2} = \frac{I_T}{2} + V_d \sqrt{\frac{\theta I_T}{2}} \sqrt{1 - V_d^2 \frac{\theta}{2I_T}}$$


Recall for x small

$$\sqrt{1-x} \cong 1 - \frac{x}{2} - \frac{x^2}{8} + \dots$$

Using a Truncated Taylor's series, we obtain:


$$I_{D2} \cong \frac{I_T}{2} + V_d \sqrt{\frac{\theta I_T}{2}} \left( 1 - V_d^2 \frac{\theta}{4I_T} \right)$$

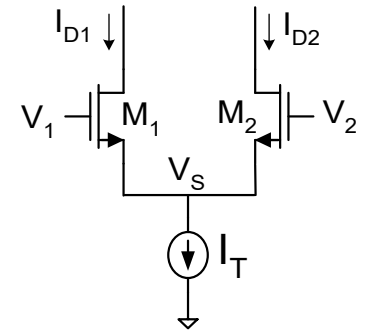Note this has no second-order term thus the dominant distortion when  $V_d = V_m \sin(\omega t)$  will be due to the third-order term


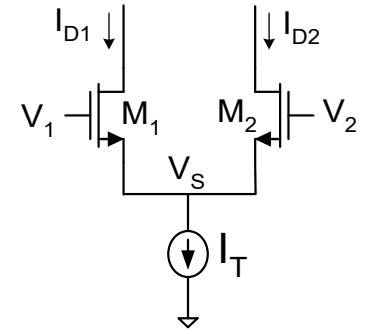
# How linear is the amplifier ?

$$I_{D2} \approx \frac{I_T}{2} + V_d \sqrt{\frac{\theta I_T}{2}} \left( 1 - V_d^2 \frac{\theta}{4I_T} \right) \quad \theta = \frac{\mu C_{ox} W}{2L}$$



Substituting in  $V_d = V_m \sin(\omega t)$

$$I_{D2} \approx \frac{I_T}{2} + V_m \sin(\omega t) \sqrt{\frac{\theta I_T}{2}} \left( 1 - V_m^2 \sin^2(\omega t) \frac{\theta}{4I_T} \right)$$

$$I_{D2} \approx \frac{I_T}{2} + \left[ V_m \sqrt{\frac{\theta I_T}{2}} \right] \sin(\omega t) - \left[ V_m^3 \frac{\theta^{\frac{3}{2}}}{4\sqrt{2}\sqrt{I_T}} \right] \sin^3(\omega t)$$

$$\sin^3(\omega t) = \frac{3}{4} \sin(\omega t) - \frac{1}{4} \sin(3\omega t)$$


$$I_{D2} \approx \frac{I_T}{2} + \left[ V_m \sqrt{\frac{\theta I_T}{2}} \right] \sin(\omega t) - \left[ V_m^3 \frac{\theta^{\frac{3}{2}}}{4\sqrt{2}\sqrt{I_T}} \right] \left[ \frac{3}{4} \sin(\omega t) - \frac{1}{4} \sin(3\omega t) \right]$$

$$I_{D2} \approx \frac{I_T}{2} + \left[ V_m \sqrt{\frac{\theta I_T}{2}} - V_m^3 \frac{3\theta^{\frac{3}{2}}}{16\sqrt{2}\sqrt{I_T}} \right] \sin(\omega t) + \left[ V_m^3 \frac{\theta^{\frac{3}{2}}}{16\sqrt{2}\sqrt{I_T}} \right] \sin(3\omega t)$$

# How linear is the amplifier ?

$$I_{D2} \approx \frac{I_T}{2} + V_d \sqrt{\frac{\theta I_T}{2}} \left( 1 - V_d^2 \frac{\theta}{4I_T} \right)$$

$$\theta = \frac{\mu C_{OX} W}{2L}$$

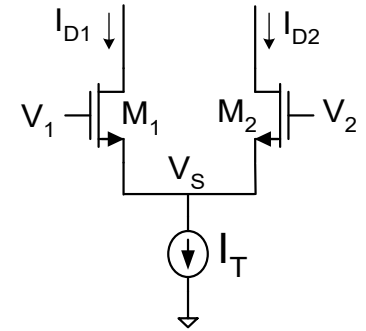


$$I_{D2} \approx \frac{I_T}{2} + \left[ V_m \sqrt{\frac{\theta I_T}{2}} - V_m^3 \frac{3\theta^{\frac{3}{2}}}{16\sqrt{2}\sqrt{I_T}} \right] \sin(\omega t) + \left[ V_m^3 \frac{\theta^{\frac{3}{2}}}{16\sqrt{2}\sqrt{I_T}} \right] [\sin(3\omega t)]$$

Note this has no second-order harmonic term thus the dominant distortion when  $V_d = V_m \sin(\omega t)$  will be due to the third-order harmonic

$$I_{D2} \approx a_0 + a_1 \sin(\omega t) + a_3 (3\omega t)$$

$$a_1 = \left[ V_m \sqrt{\frac{\theta I_T}{2}} - V_m^3 \frac{3\theta^{\frac{3}{2}}}{16\sqrt{2}\sqrt{I_T}} \right] \quad a_3 = \left[ \frac{\theta^{\frac{3}{2}}}{16\sqrt{2}\sqrt{I_T}} \right] V_m^3$$

# How linear is the amplifier ?

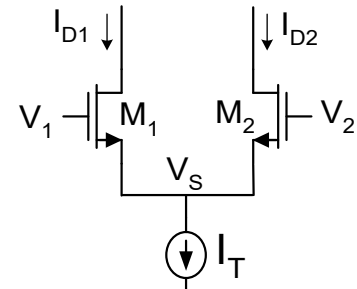

$$I_{D2} \approx a_0 + a_1 \sin(\omega t) + a_3 \sin(3\omega t)$$

$$THD = 20 \log \left( \frac{\sqrt{\sum_{k=2}^{\infty} a_k^2}}{a_1} \right)$$

$$a_1 = \left[ V_m \sqrt{\frac{\theta I_T}{2}} - V_m^3 \frac{3\theta^2}{16\sqrt{2}\sqrt{I_T}} \right] \quad a_3 = \left[ \frac{\theta^2}{16\sqrt{2}\sqrt{I_T}} \right] V_m^3$$

For low distortion want THD a large negative number

Substituting in we obtain

$$THD = 20 \log \left( \frac{\frac{\theta^2}{16\sqrt{2}\sqrt{I_T}} V_m^3}{V_m \sqrt{\frac{\theta I_T}{2}} - V_m^3 \frac{3\theta^2}{16\sqrt{2}\sqrt{I_T}}} \right) \quad \text{where} \quad \theta = \frac{\mu C_{OX} W}{2L}$$


This expression gives little insight.

Consider expression in the practical parameter domain:

$$I_T = \frac{\mu C_{OX} W}{L} V_{EB1}^2$$



# How linear is the amplifier ?

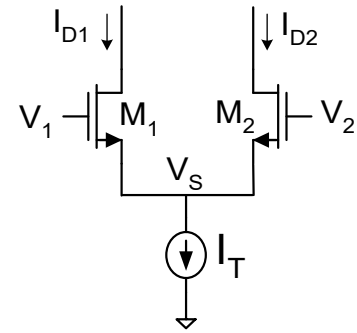

$$I_{D2} \approx a_0 + a_1 \sin(\omega t) + a_3 \sin(3\omega t)$$

$$\text{THD} = 20 \log \left( \frac{\frac{\theta^{\frac{3}{2}}}{16\sqrt{2}\sqrt{I_T}} V_m^3}{V_m \sqrt{\frac{\theta I_T}{2}} - V_m^3 \frac{3\theta^{\frac{3}{2}}}{16\sqrt{2}\sqrt{I_T}}} \right)$$

$$\theta = \frac{\mu C_{OX} W}{2L}$$

$$I_T = \frac{\mu C_{OX} W}{L} V_{EB1}^2$$


Eliminating  $I_T$  and  $\theta$ , we obtain

$$\text{THD} = -20 \log \left( 32 \left( \frac{V_{EB1}}{V_m} \right)^2 - 3 \right)$$

$V_m / V_{EB1}$	THD (dB)
2.5	-6.52672
1	-29.248
0.5	-41.9382
0.25	-54.1344
0.1	-70.0949
0.05	-82.1422
0.025	-94.1849
0.01	-110.103

Thus to minimize THD, want  $V_{EB}$  large and  $V_m$  small

# Bipolar Differential Pair

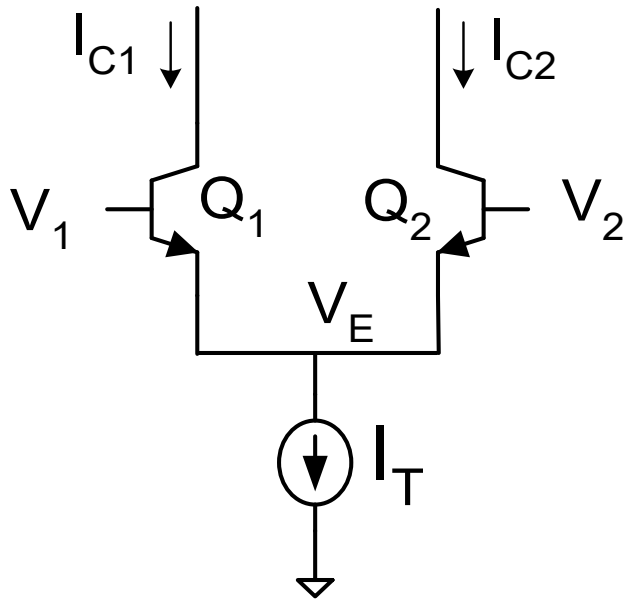

$$\left. \begin{aligned} I_{C1} &= J_S A_{E1} e^{\frac{V_1 - V_E}{V_t}} \\ I_{C2} &= J_S A_{E2} e^{\frac{V_2 - V_E}{V_t}} \\ I_{C1} + I_{C2} &= I_T \end{aligned} \right\}$$


$$V_1 = V_E + V_t \ln \left( \frac{I_{C1}}{J_S A_{E1}} \right)$$

$$V_2 = V_E + V_t \ln \left( \frac{I_{C2}}{J_S A_{E2}} \right)$$

$$V_d = V_2 - V_1$$

$$V_d = V_t \left( \ln \left( \frac{I_{C2}}{J_S A_{E2}} \right) - \ln \left( \frac{I_{C1}}{J_S A_{E1}} \right) \right) = V_t \ln \left( \frac{I_{C2}}{I_{C1}} \right)^{A_{E1} - A_{E2}}$$

# Bipolar Differential Pair

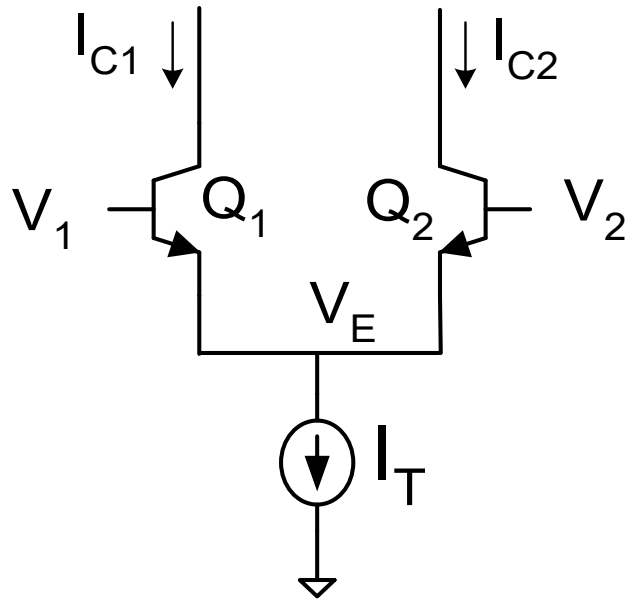

$$V_d = V_2 - V_1$$

$$V_d = V_t \left( \ln \left( \frac{I_{C2}}{J_S A_{E2}} \right) - \ln \left( \frac{I_{C1}}{J_S A_{E1}} \right) \right) \stackrel{A_{E1} = A_{E2}}{=} V_t \ln \left( \frac{I_{C2}}{I_{C1}} \right)$$

$$V_d = V_t \ln \left( \frac{I_T - I_{C1}}{I_{C1}} \right)$$

$$V_d = V_t \ln \left( \frac{I_{C2}}{I_T - I_{C2}} \right)$$



At  $I_{C1} = I_{C2} = I_T/2$ ,  $V_d = 0$

As  $I_{C1}$  approaches 0,  $V_d$  approaches infinity

As  $I_{C1}$  approaches  $I_T$ ,  $V_d$  approaches minus infinity

Transition much steeper than for MOS case
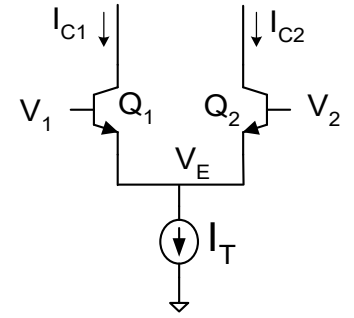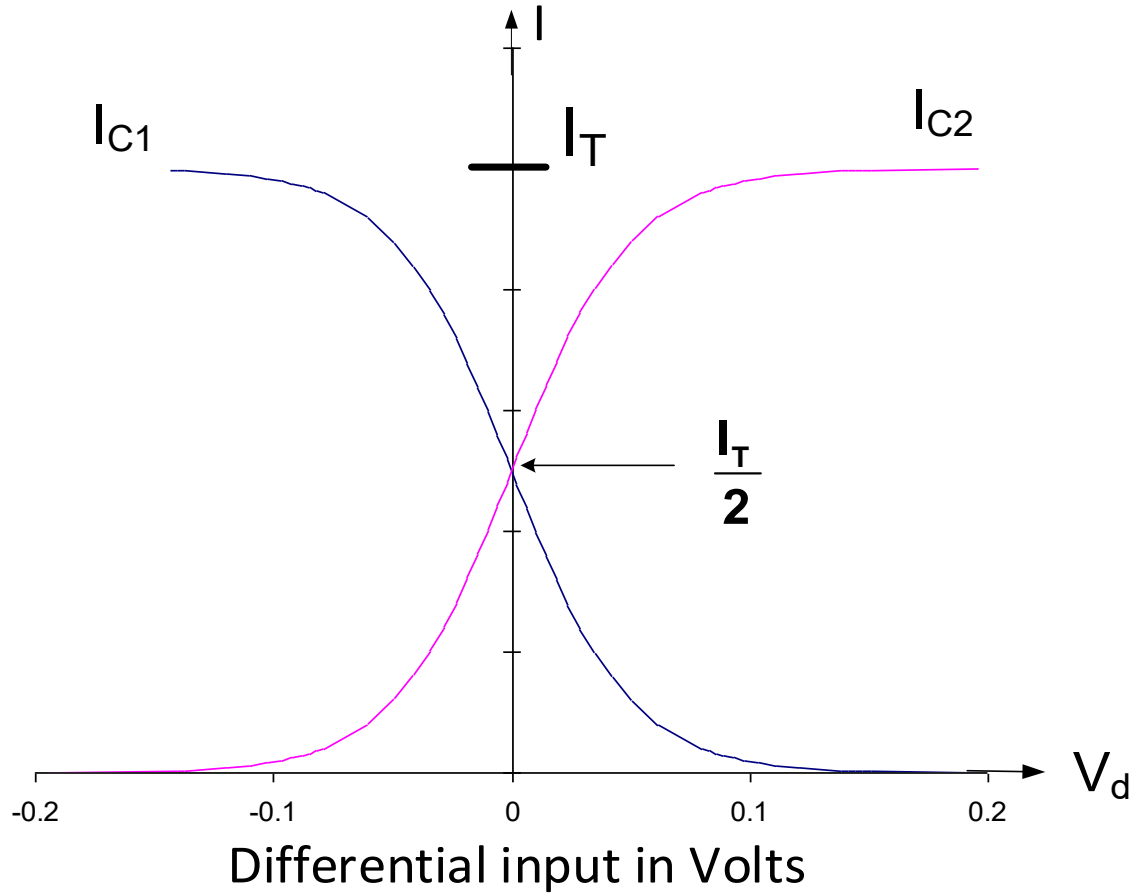
# Transfer Characteristics of Bipolar Differential Pair





$$V_d = V_t \ln \left( \frac{I_T - I_{C1}}{I_{C1}} \right)$$

Transition much steeper than for MOS case  
Asymptotic Convergence to 0 and  $I_T$

# Signal Swing and Linearity of Bipolar Differential Pair

$$I_{FIT} = mV_d + h$$

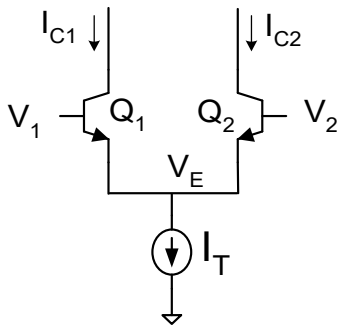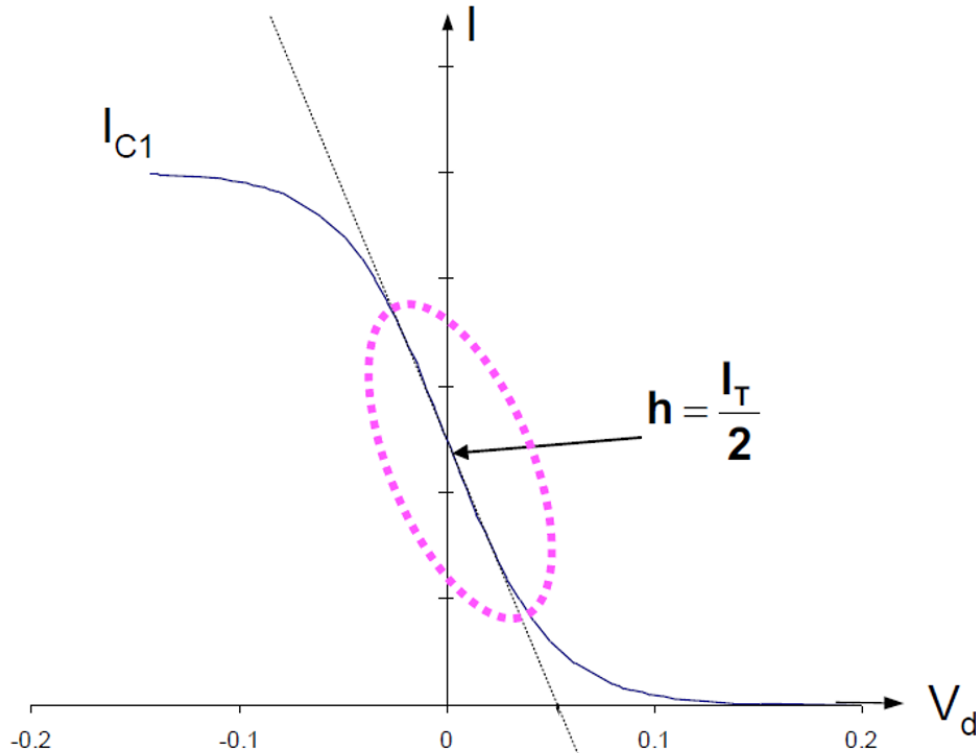

$$V_{dint} = -\frac{h}{m} = ?$$

$$V_d = V_t \ln \left( \frac{I_T - I_{C1}}{I_{C1}} \right)$$

$$m = \left. \frac{\partial I_{C1}}{\partial V_d} \right|_{Q\text{-point}}$$

$$Q\text{-pt} = (0, h)$$


$$\left. \frac{\partial V_d}{\partial I_{C1}} \right|_{Q\text{-point}} = -V_t \left. \frac{I_T}{I_{C1}(I_T - I_{C1})} \right|_{I_{C1} = \frac{I_T}{2}}$$

$$\left. \frac{\partial V_d}{\partial I_{C1}} \right|_{Q\text{-point}} = -\frac{4V_t}{I_T}$$


$$I_{FIT} = -\frac{I_T}{4V_t} V_d + \frac{I_T}{2}$$

$$V_{dint} = -\frac{h}{m} = 2V_t$$

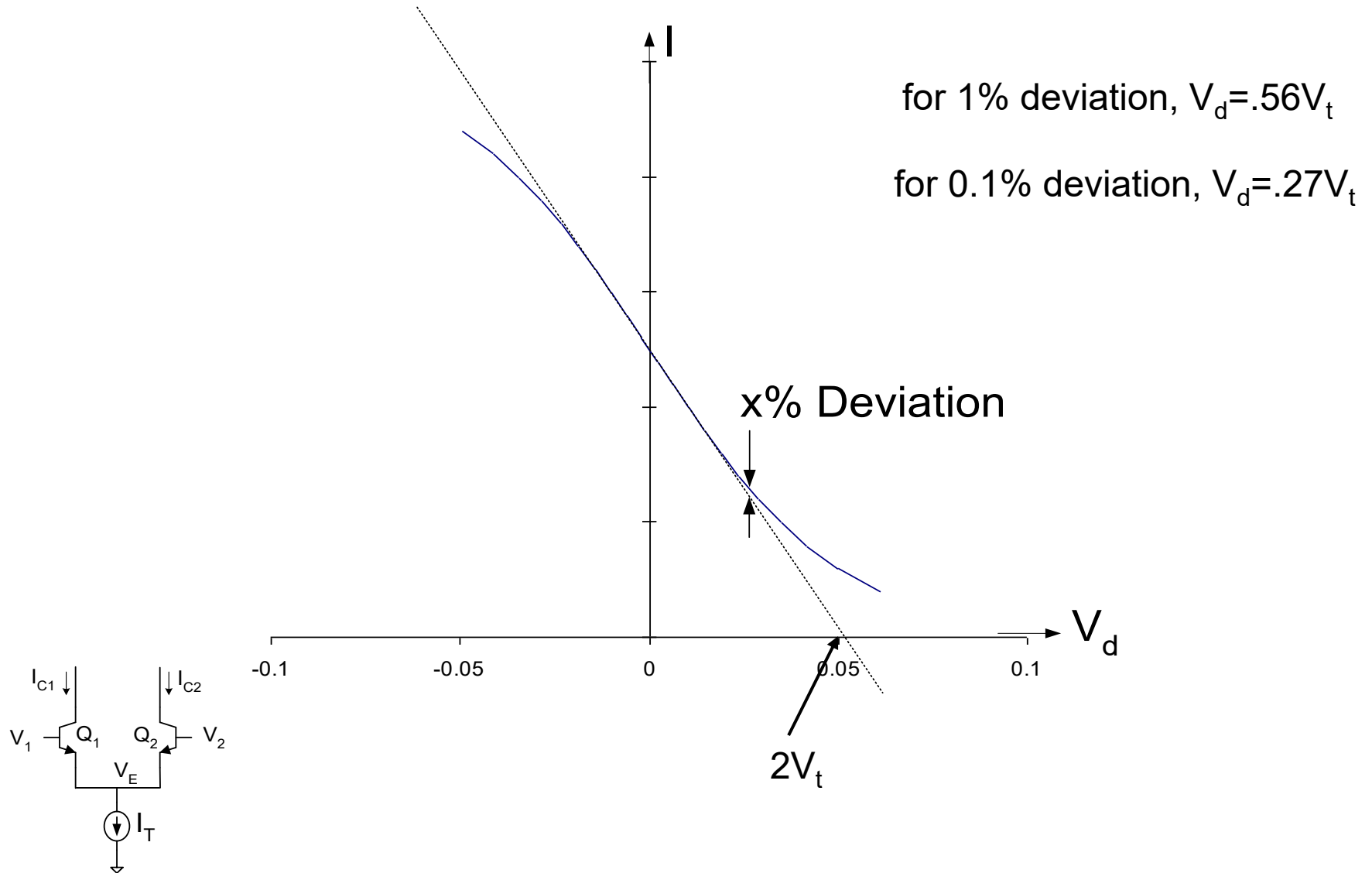
# Signal Swing and Linearity of Bipolar Differential Pair


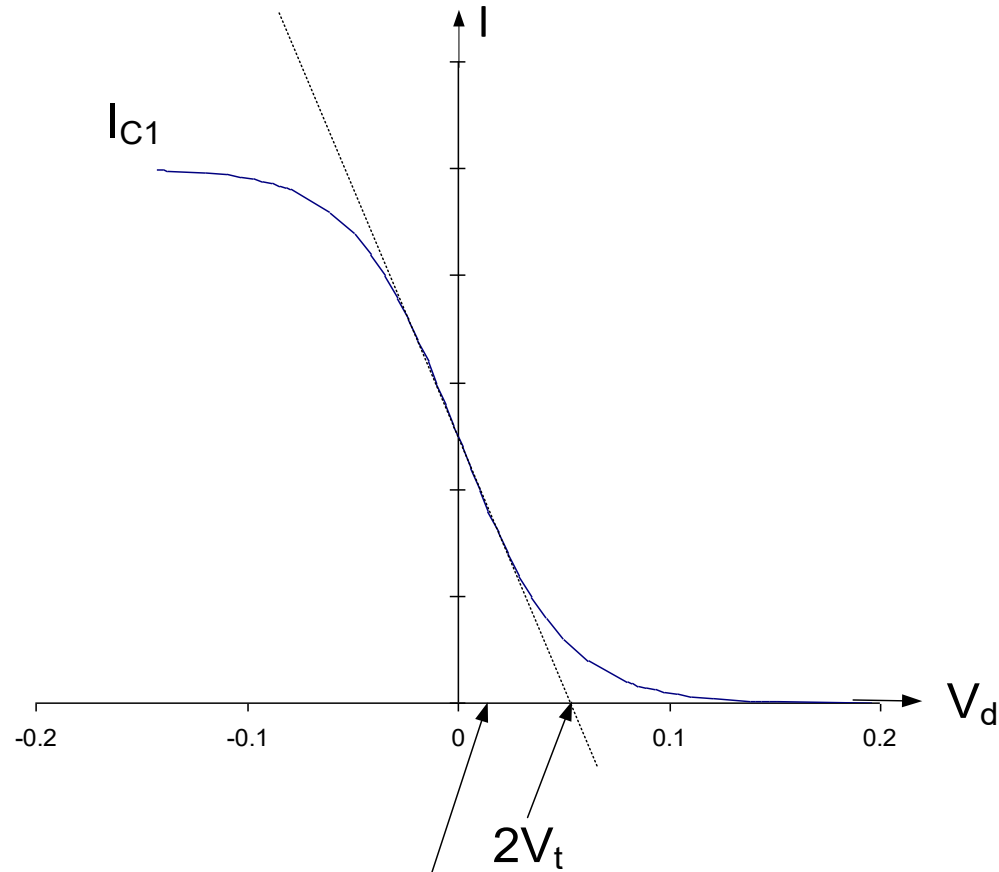
# Signal Swing and Linearity of Bipolar Differential Pair



1% linear =  $.56V_t$

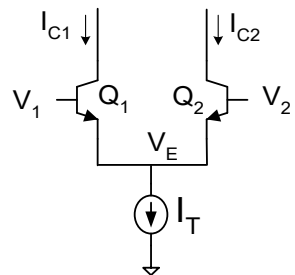

Note  $V_d$  axis intercept for BJT pair typically much smaller than for MOS pair ( $V_{EB}$ ) but designer has no control of intercept for BJT pair


# How linear is the amplifier ?

Distortion in the differential pair is another useful metric for characterizing linearity of  $I_{C1}$  and  $I_{C2}$  with sinusoidal differential excitation

Consider again the differential pair and assume excited differentially with

$$V_2 = \frac{V_d}{2} \quad V_1 = -\frac{V_d}{2}$$

and assume  $V_d = V_m \sin(\omega t)$

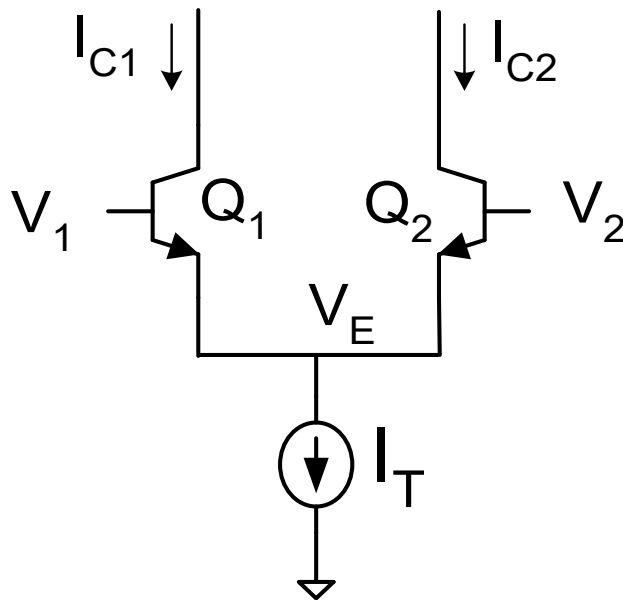

$$V_d = V_2 - V_1$$

Recall:

$$V_d = V_t \ln \left( \frac{I_T - I_{C1}}{I_{C1}} \right)$$


Thus can express as

$$e^{\frac{V_d}{V_t}} = \frac{I_T - I_{C1}}{I_{C1}}$$

$$I_{C1} = I_T \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-1}$$



# How linear is the amplifier ?

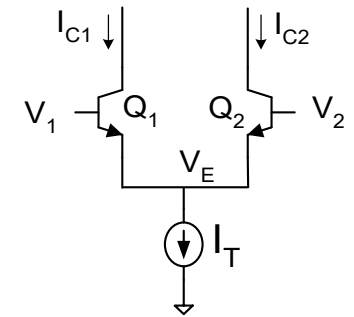


$$I_{C1} = I_T \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-1}$$

$$V_d = V_m \sin(\omega t)$$

Consider a Taylor's Series Expansion

$$I_{C1} = I_{C1}|_{V_d=0} + \left. \frac{\partial I_{C1}}{\partial V_d} \right|_{V_d=0} V_d + \frac{1}{2!} \left. \frac{\partial^2 I_{C1}}{\partial V_d^2} \right|_{V_d=0} V_d^2 + \frac{1}{3!} \left. \frac{\partial^3 I_{C1}}{\partial V_d^3} \right|_{V_d=0} V_d^3 + H.O.T$$

# How linear is the amplifier ?

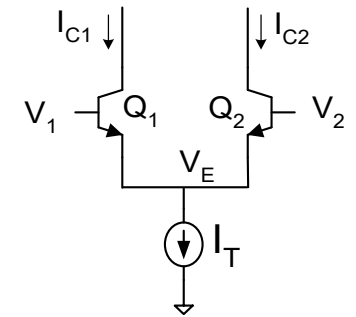

$$I_{C1} = I_T \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-1} \quad V_d = V_m \sin(\omega t)$$

$$I_{C1} = I_{C1}|_{V_d=0} + \left. \frac{\partial I_{C1}}{\partial V_d} \right|_{V_d=0} V_d + \frac{1}{2!} \left. \frac{\partial^2 I_{C1}}{\partial V_d^2} \right|_{V_d=0} V_d^2 + \frac{1}{3!} \left. \frac{\partial^3 I_{C1}}{\partial V_d^3} \right|_{V_d=0} V_d^3 + H.O.T$$

$$\frac{\partial I_{C1}}{\partial V_d} = -\frac{I_T}{V_t} \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-2} e^{\frac{V_d}{V_t}}$$


$$\frac{\partial^2 I_{C1}}{\partial V_d^2} = -\frac{I_T}{V_t} \left[ \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-2} e^{\frac{V_d}{V_t}} \frac{1}{V_t} - 2 e^{\frac{V_d}{V_t}} \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-3} e^{\frac{V_d}{V_t}} \frac{1}{V_t} \right]$$

$$\frac{\partial^2 I_{C1}}{\partial V_d^2} = -\frac{I_T}{V_t^2} \left[ \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-2} e^{\frac{V_d}{V_t}} - 2 e^{\frac{2V_d}{V_t}} \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-3} \right]$$

$$\frac{\partial^3 I_{C1}}{\partial V_d^3} = -\frac{I_T}{V_t^2} \left[ \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-2} e^{\frac{V_d}{V_t}} \frac{1}{V_t} - 2 e^{\frac{V_d}{V_t}} \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-3} e^{\frac{V_d}{V_t}} \frac{1}{V_t} + 6 e^{\frac{2V_d}{V_t}} \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-4} e^{\frac{V_d}{V_t}} \frac{1}{V_t} - 2 e^{\frac{2V_d}{V_t}} \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-3} \frac{2}{V_t} \right]$$

$$\frac{\partial^3 I_{C1}}{\partial V_d^3} = -\frac{I_T}{V_t^3} \left[ \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-2} e^{\frac{V_d}{V_t}} - 2 e^{\frac{2V_d}{V_t}} \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-3} + 6 e^{\frac{3V_d}{V_t}} \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-4} - 4 e^{\frac{2V_d}{V_t}} \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-3} \right]$$

# How linear is the amplifier ?

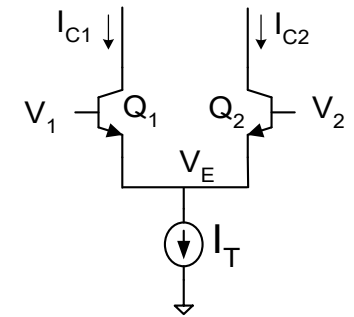

$$V_d = V_m \sin(\omega t)$$

$$I_{C1} = I_{C1}|_{V_d=0} + \left. \frac{\partial I_{C1}}{\partial V_d} \right|_{V_d=0} V_d + \frac{1}{2!} \left. \frac{\partial^2 I_{C1}}{\partial V_d^2} \right|_{V_d=0} V_d^2 + \frac{1}{3!} \left. \frac{\partial^3 I_{C1}}{\partial V_d^3} \right|_{V_d=0} V_d^3 + H.O.T$$

$$\left. \frac{\partial I_{C1}}{\partial V_d} \right|_{V_d=0} = -\frac{I_T}{V_t} \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-2} e^{\frac{V_d}{V_t}} \Big|_{V_d=0} = -\frac{I_T}{V_t} (2)^{-2} = -\frac{I_T}{4V_t}$$

$$\left. \frac{\partial^2 I_{C1}}{\partial V_d^2} \right|_{V_d=0} = -\frac{I_T}{V_t^2} \left[ \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-2} e^{\frac{V_d}{V_t}} - 2 e^{\frac{2V_d}{V_t}} \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-3} \right] \Big|_{V_d=0} = -\frac{I_T}{V_t^2} [(2)^{-2} - 2(2)^{-3}] = 0$$


$$\left. \frac{\partial^3 I_{C1}}{\partial V_d^3} \right|_{V_d=0} = -\frac{I_T}{V_t^3} \left[ \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-2} e^{\frac{V_d}{V_t}} - 2e^{\frac{2V_d}{V_t}} \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-3} + 6e^{\frac{3V_d}{V_t}} \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-4} - 4e^{\frac{2V_d}{V_t}} \left( 1 + e^{\frac{V_d}{V_t}} \right)^{-3} \right] \Big|_{V_d=0} = -\frac{I_T}{V_t^3} [(2)^{-2} - 2(2)^{-3} + 6(2)^{-4} - 4(2)^{-3}] = \frac{I_T}{8V_t^3}$$

$$\left. \frac{\partial I_{C1}}{\partial V_d} \right|_{V_d=0} = -\frac{I_T}{4V_t}$$

$$\left. \frac{\partial^2 I_{C1}}{\partial V_d^2} \right|_{V_d=0} = 0$$

$$\left. \frac{\partial^3 I_{C1}}{\partial V_d^3} \right|_{V_d=0} = \frac{I_T}{8V_t^3}$$

# How linear is the amplifier ?

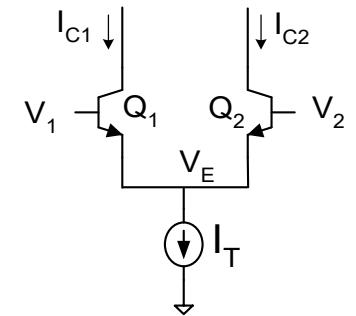

$$V_d = V_m \sin(\omega t)$$

$$I_{C1} = I_{C1}|_{V_d=0} + \left. \frac{\partial I_{C1}}{\partial V_d} \right|_{V_d=0} V_d + \frac{1}{2!} \left. \frac{\partial^2 I_{C1}}{\partial V_d^2} \right|_{V_d=0} V_d^2 + \frac{1}{3!} \left. \frac{\partial^3 I_{C1}}{\partial V_d^3} \right|_{V_d=0} V_d^3 + H.O.T$$


$$\left. \frac{\partial I_{C1}}{\partial V_d} \right|_{V_d=0} = -\frac{I_T}{4V_t} \quad \left. \frac{\partial^2 I_{C1}}{\partial V_d^2} \right|_{V_d=0} = 0 \quad \left. \frac{\partial^3 I_{C1}}{\partial V_d^3} \right|_{V_d=0} = \frac{I_T}{8V_t^3}$$

$$I_{C1} \cong \frac{I_T}{2} - \frac{I_T}{4V_t} V_d + \frac{I_T}{48V_t^3} V_d^3$$

$$I_{C1} \cong \frac{I_T}{2} - \frac{I_T}{4V_t} V_m \sin(\omega t) + \frac{I_T}{48V_t^3} V_m^3 \sin^3(\omega t)$$

$$\sin^3(\omega t) = \frac{3}{4} \sin(\omega t) - \frac{1}{4} \sin(3\omega t)$$

# How linear is the amplifier ?

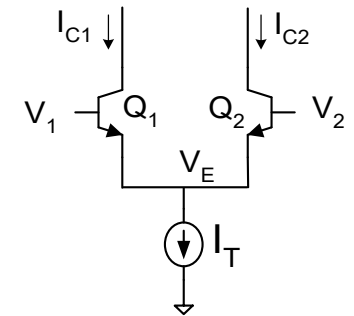

$$V_d = V_m \sin(\omega t)$$

$$I_{C1} = I_{C1}|_{V_d=0} + \left. \frac{\partial I_{C1}}{\partial V_d} \right|_{V_d=0} V_d + \frac{1}{2!} \left. \frac{\partial^2 I_{C1}}{\partial V_d^2} \right|_{V_d=0} V_d^2 + \frac{1}{3!} \left. \frac{\partial^3 I_{C1}}{\partial V_d^3} \right|_{V_d=0} V_d^3 + H.O.T$$

$$I_{C1} \cong \frac{I_T}{2} - \frac{I_T}{4V_t} V_m \sin(\omega t) + \frac{I_T}{48V_t^3} V_m^3 \left[ \frac{3}{4} \sin(\omega t) - \frac{1}{4} \sin(3\omega t) \right]$$

$$I_{C1} \cong \frac{I_T}{2} + \left[ \frac{3I_T}{4 \bullet 48V_t^3} V_m^3 - \frac{I_T}{4V_t} V_m \right] \sin(\omega t) - \frac{I_T}{4 \bullet 48V_t^3} V_m^3 \sin(3\omega t)$$

Thus:


$$THD = 20 \log \left( \frac{V_m^2}{[48V_t^2 - 3V_m^2]} \right)$$

or, equivalently


$$THD = -20 \log \left( 48 \left( \frac{V_t}{V_m} \right)^2 - 3 \right)$$

$V_m / V_t$	THD (dB)
2.5	-13.4049
1	-33.0643
0.5	-45.5292
0.25	-57.6732
0.1	-73.6194
0.05	-85.6647
0.025	-97.7069
0.01	-113.625
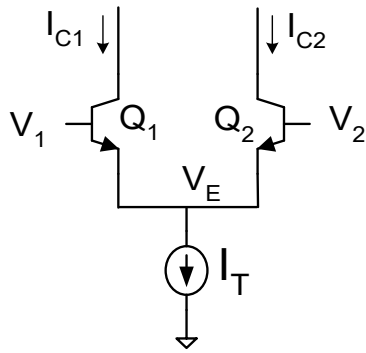
# Comparison of Distortion in BJT and MOSFET Pairs



$$V_d = V_m \sin(\omega t)$$




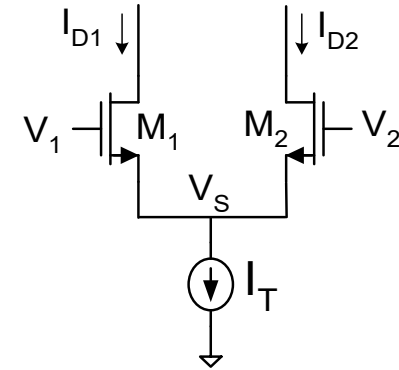


$$\text{THD} = -20 \log \left( 48 \left( \frac{V_t}{V_m} \right)^2 - 3 \right)$$

$$\text{THD} = -20 \log \left( 32 \left( \frac{V_{EB1}}{V_m} \right)^2 - 3 \right)$$

$V_m / V_t$	THD (dB)	$V_m / V_{EB1}$	THD (dB)
2.5	-13.4049	2.5	-6.52672
1	-33.0643	1	-29.248
0.5	-45.5292	0.5	-41.9382
0.25	-57.6732	0.25	-54.1344
0.1	-73.6194	0.1	-70.0949
0.05	-85.6647	0.05	-82.1422
0.025	-97.7069	0.025	-94.1849
0.01	-113.625	0.01	-110.103
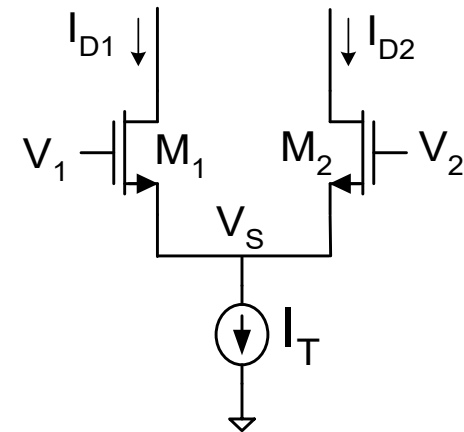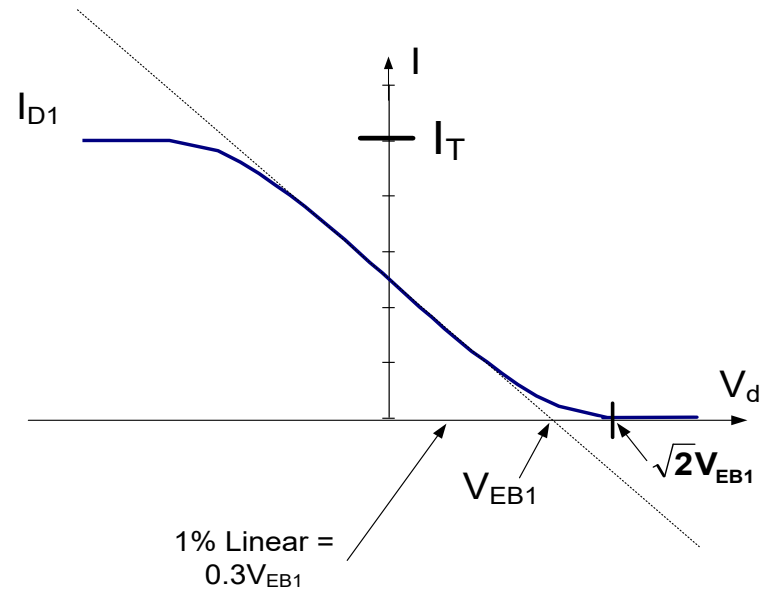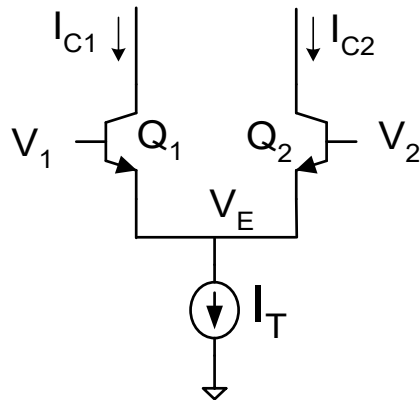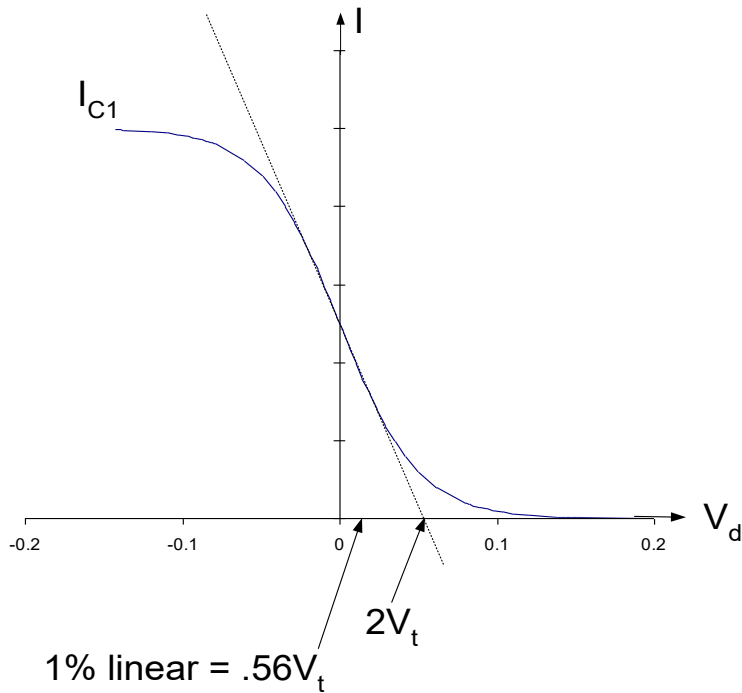
# Linearity and Signal Swing Comparison of Bipolar/MOS Differential Pair



Have completed linearity analysis but must now look at the implications



Stay Safe and Stay Healthy !



End of Lecture 20