

EE 435

Lecture 3


Design Space Exploration

with applications to single-stage amplifier design


Systematic Strategies for Designing and Analyzing Op Amps

Review from last lecture:

Single-ended Op Amp Inverting Amplifier

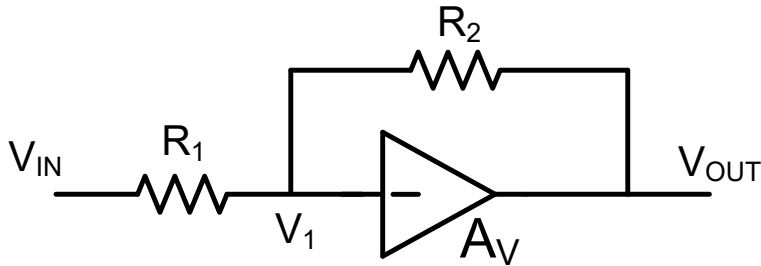
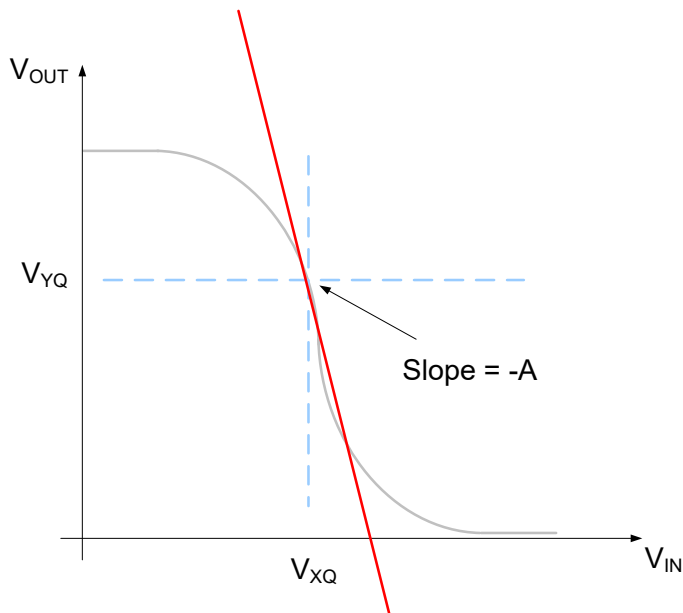
$$\left. \begin{aligned} V_O &= (-A)(V_1 - V_{XQ}) + V_{YQ} \\ V_1 &= \frac{R_1}{R_1 + R_2} V_O + \frac{R_2}{R_1 + R_2} V_{IN} \end{aligned} \right\}$$



Summary:


$$V_O = -\frac{R_2}{R_1} V_{iss} + V_{XQ} + \frac{R_2}{R_1} (V_{XQ} - V_{inQ})$$

What type of circuits have the transfer characteristic shown?

Review from last lecture:

Single-stage single-input low-gain op amp

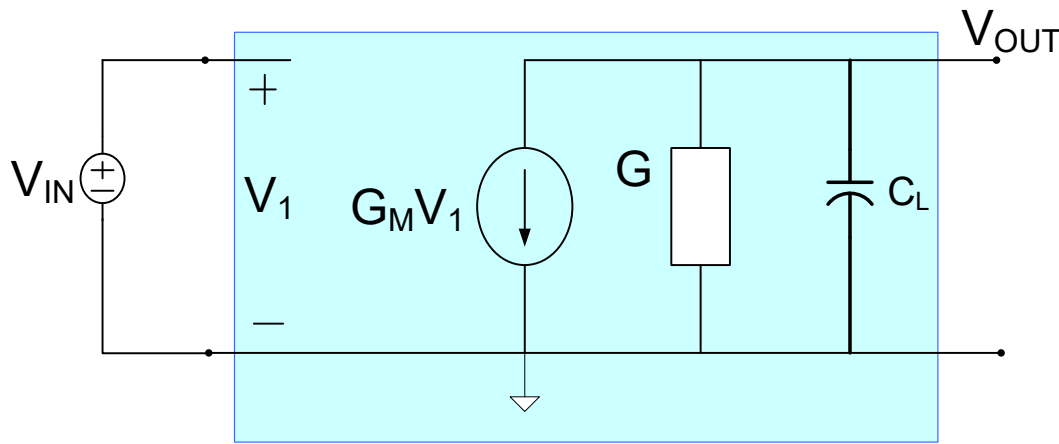(unilateral with infinite input impedance and one capacitor)




$$A_V = \frac{-G_M}{sC_L + G}$$

$$A_{V0} = \frac{-G_M}{G}$$

$$BW = \frac{G}{C_L}$$
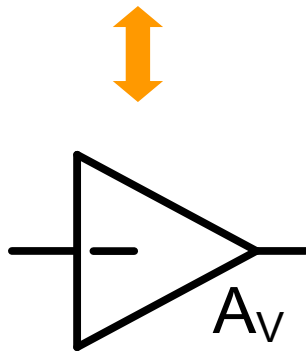
$$GB = \left(\frac{G_M}{G}\right) \left(\frac{G}{C_L}\right) = \frac{G_M}{C_L}$$



GB and A_{V0} are two of the most important parameters in an op amp

Review from last lecture:

How do we design an amplifier with a given architecture in general or this architecture in particular?

What is the design space?

Generally V_{SS} , V_{DD} , C_L (and possibly V_{OUTQ}) will be fixed

Must determine $\{W_1, L_1, I_{DQ} \text{ and } V_{INQ}\}$

Thus there are 4 design variables

But W_1 and L_1 appear as a ratio in almost all performance characteristics of interest


and I_{DQ} is related to V_{INQ} , W_1 and L_1
(this is a constraint)

Thus the design space generally has only two independent variables or **two degrees of freedom**

$$\left\{ \frac{W_1}{L_1}, I_{DQ} \right\}$$

Thus design or "synthesis" with this architecture involves exploring the two-dimensional design space
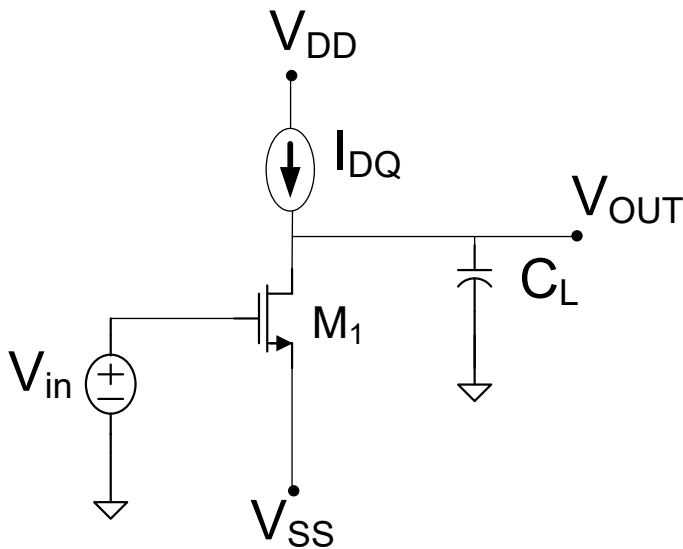
$$\left\{ \frac{W_1}{L_1}, I_{DQ} \right\}$$



Review from last lecture:

How do we design an amplifier with a given architecture ?

1. Determine the design space
2. Identify the constraints
3. Determine the entire set of unknown variables and the Degrees of Freedom
4. Determine an appropriate parameter domain
5. Explore the resultant design space with the identified number of Degrees of Freedom

Review from last lecture:

Parameter Domains for Characterizing Amplifier Performance

Degrees of Freedom: 2

Small signal parameter domain : $\{g_m, g_0\}$

$$A_{V0} = \frac{-g_m}{g_0} \quad GB = \frac{g_m}{C_L}$$

Natural design parameter domain:

$$\left\{ \frac{W}{L}, I_{DQ} \right\}$$

$$A_{V0} = \left[\frac{\sqrt{2\mu C_{OX}}}{\lambda} \right] \left[\frac{\sqrt{\frac{W}{L}}}{\sqrt{I_{DQ}}} \right] \quad GB = \left[\frac{\sqrt{2\mu C_{OX}}}{C_L} \right] \left[\sqrt{\frac{W}{L}} \sqrt{I_{DQ}} \right]$$

Alternate parameter domain:

$$\{P, V_{EB}\}$$

$$A_{V0} = \left[\frac{2}{\lambda} \right] \left[\frac{1}{V_{EB}} \right]$$

$$GB = \left[\frac{2}{V_{DD} C_L} \right] \left[\frac{P}{V_{EB}} \right]$$

Process Dependent

Review from last lecture:

Parameter Domains for Characterizing Amplifier Performance

Degrees of Freedom: 2

Small signal parameter domain : $\{g_m, g_0\}$

$$A_{v0} = \frac{-g_m}{g_0} \qquad GB = \frac{g_m}{C_L}$$

Natural design parameter domain: $\left\{ \frac{W}{L}, I_{DQ} \right\}$

$$A_{v0} = \left[\frac{\sqrt{2\mu C_{OX}}}{\lambda} \right] \frac{\sqrt{\frac{W}{L}}}{\sqrt{I_{DQ}}} \qquad GB = \left[\frac{\sqrt{2\mu C_{OX}}}{C_L} \right] \sqrt{\frac{W}{L}} \sqrt{I_{DQ}}$$

Alternate parameter domain:

$\{P, V_{EB}\}$

$$A_{v0} = \left[\frac{2}{\lambda} \right] \left[\frac{1}{V_{EB}} \right] \qquad GB = \left[\frac{2}{V_{DD} C_L} \right] \left[\frac{P}{V_{EB}} \right]$$

Architecture Dependent

Review from last lecture:

Parameter Domains for Characterizing Amplifier Performance

Degrees of Freedom: 2

Small signal parameter domain :

$$\{g_m, g_0\}$$

$$A_{V0} = \frac{-g_m}{g_0}$$

$$GB = \frac{g_m}{C_L}$$

Natural design parameter domain:

$$\left\{ \frac{W}{L}, I_{DQ} \right\}$$

$$A_{V0} = \left[\frac{\sqrt{2\mu C_{OX}}}{\lambda} \right] \frac{\sqrt{\frac{W}{L}}}{\sqrt{I_{DQ}}}$$

$$GB = \left[\frac{\sqrt{2\mu C_{OX}}}{C_L} \right] \sqrt{\frac{W}{L}} \sqrt{I_{DQ}}$$

Alternate parameter domain:

$$\{P, V_{EB}\}$$

$$A_{V0} = \left[\frac{2}{\lambda} \right] \left[\frac{1}{V_{EB}} \right]$$

$$GB = \left[\frac{2}{V_{DD} C_L} \right] \left[\frac{P}{V_{EB}} \right]$$

- Alternate parameter domain gives considerable insight into design
- Easy to map from alternate parameter domain to natural parameter domain
- Alternate parameter domain provides modest parameter decoupling
- $A_{V0} \left[\frac{\lambda}{2} \right]$ and $GB \left[\frac{V_{DD} C_L}{2} \right]$ figures of merit for comparing architectures


Review from last lecture:

Design With the Basic Amplifier Structure

Consider basic op amp structure

Alternate parameter domain: $\{P, V_{EB}\}$

Degrees of Freedom: 2

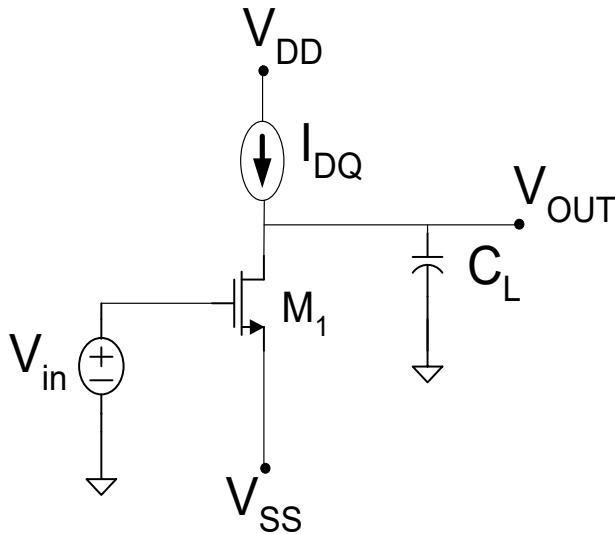

$$A_{V0} = \left[\frac{2}{\lambda} \right] \left[\frac{1}{V_{EB}} \right]$$

$$GB = \left[\frac{2}{V_{DD} C_L} \right] \left[\frac{P}{V_{EB}} \right]$$

$$I_{DQ} = \frac{P}{V_{DD}}$$

$$\frac{W}{L} = \frac{P}{V_{DD} \mu C_{OX} V_{EB}^2}$$

$$V_{INQ} = V_{SS} + V_T + \sqrt{I_{DQ} \frac{2}{\mu C_{OX}} \frac{L}{W}}$$

But what if the design requirement dictates that $V_{INQ}=0$?

Question: How can one meet two or more performance requirements with one design degree of freedom with this circuit?

Degrees of Freedom: 1

Luck or Can't

How do we design an amplifier with a given architecture ?

1. Determine the design space
2. Identify the constraints
3. Determine the entire set of unknown variables and the Degrees of Freedom
4. Determine an appropriate parameter domain




5. Explore the resultant design space with the identified number of Degrees of Freedom

Design Space Exploration

Question: How does the GB of the single-stage amplifier common-source amplifier change with bias current?

$$GB = \frac{g_m}{C_L} \quad \longrightarrow \quad GB = \left[\frac{2}{C_L} \right] \left[\frac{I_{DQ}}{V_{EB}} \right]$$

GB increases linearly with I_{DQ}

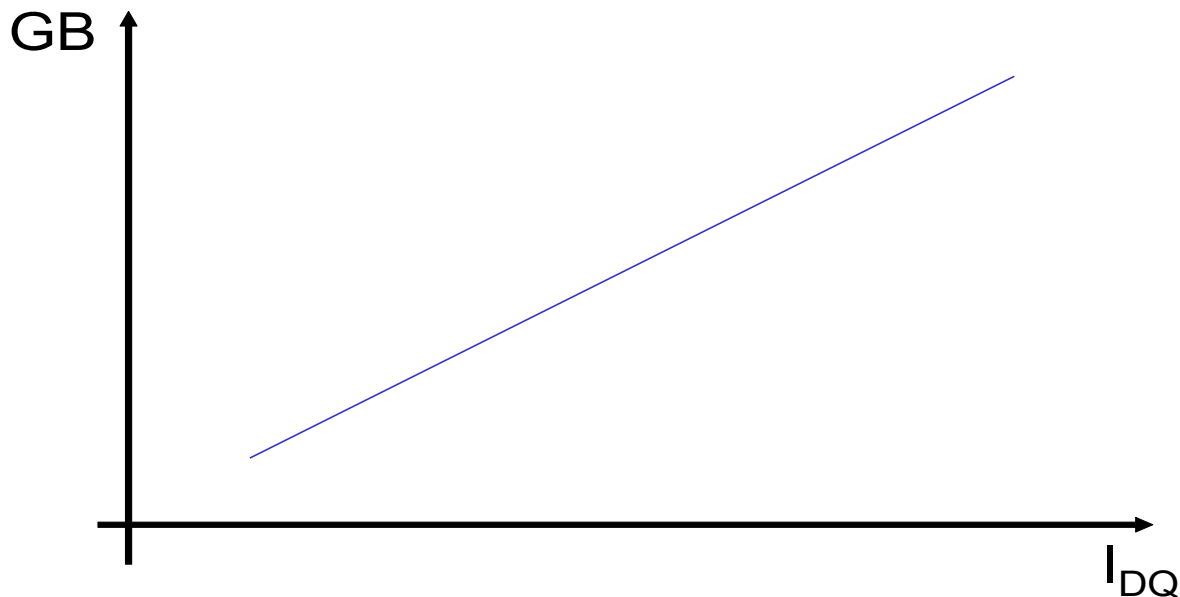


Design Space Exploration

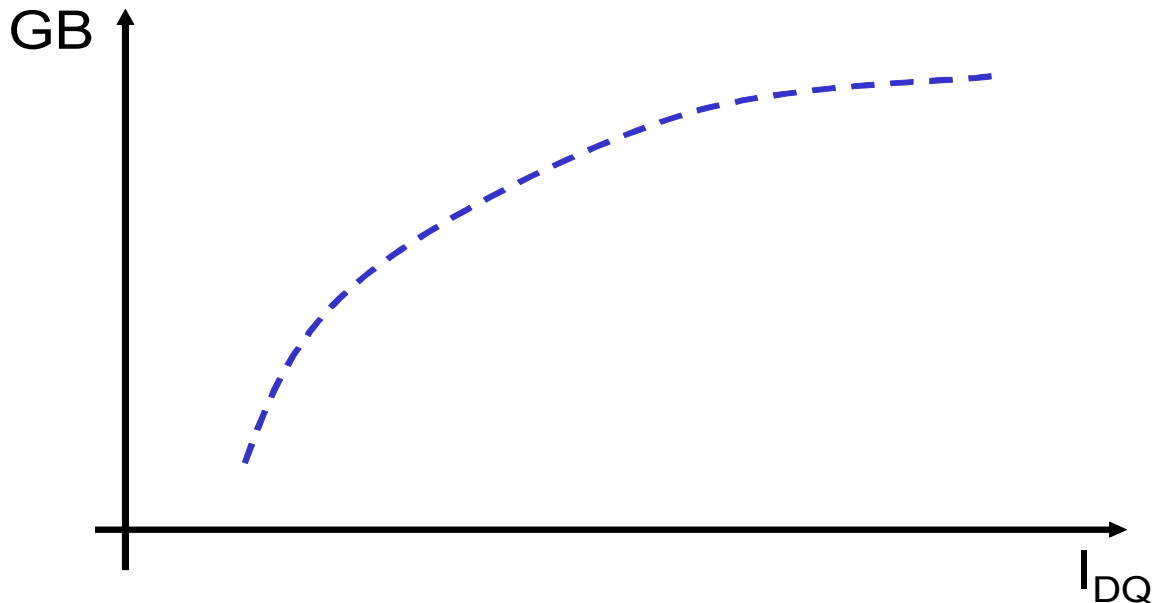Question: How does the GB of the single-stage amplifier change with bias current?

$$GB = \left[\frac{\sqrt{2\mu C_{OX}}}{C_L} \right] \left[\sqrt{\frac{W}{L}} \sqrt{I_{DQ}} \right]$$

GB increases with the square root of I_{DQ}




Design Space Exploration

Question: How does the GB of the single-stage amplifier change with bias current?

$$GB = \left[\frac{2}{V_{DD} C_L} \right] \left[\frac{P}{V_{EB}} \right]$$

GB independent of I_{DQ}

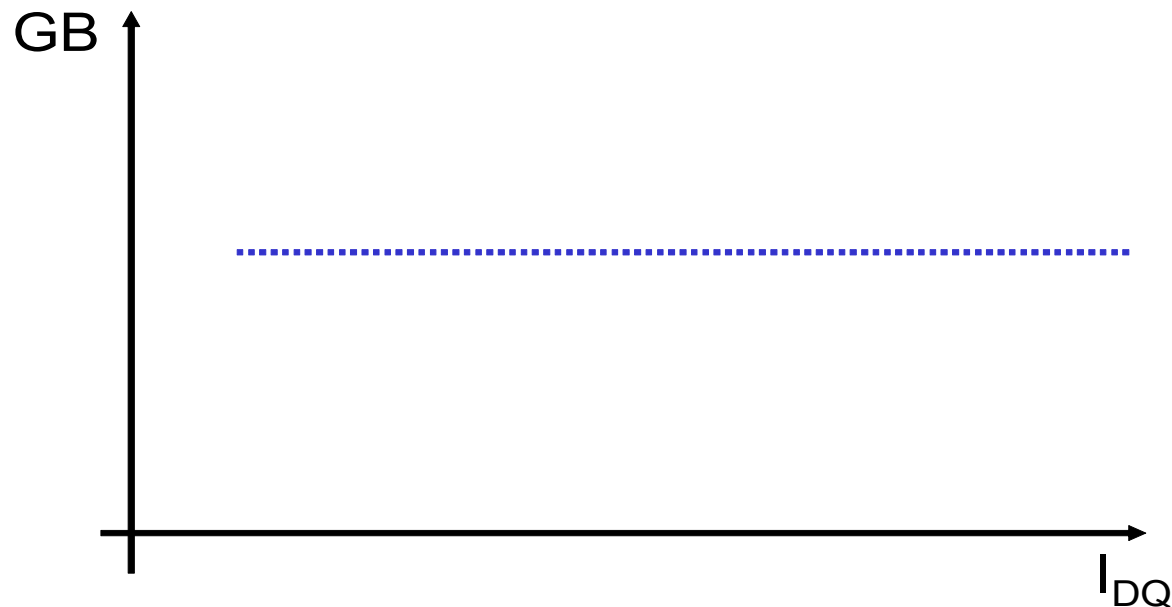


Design Space Exploration

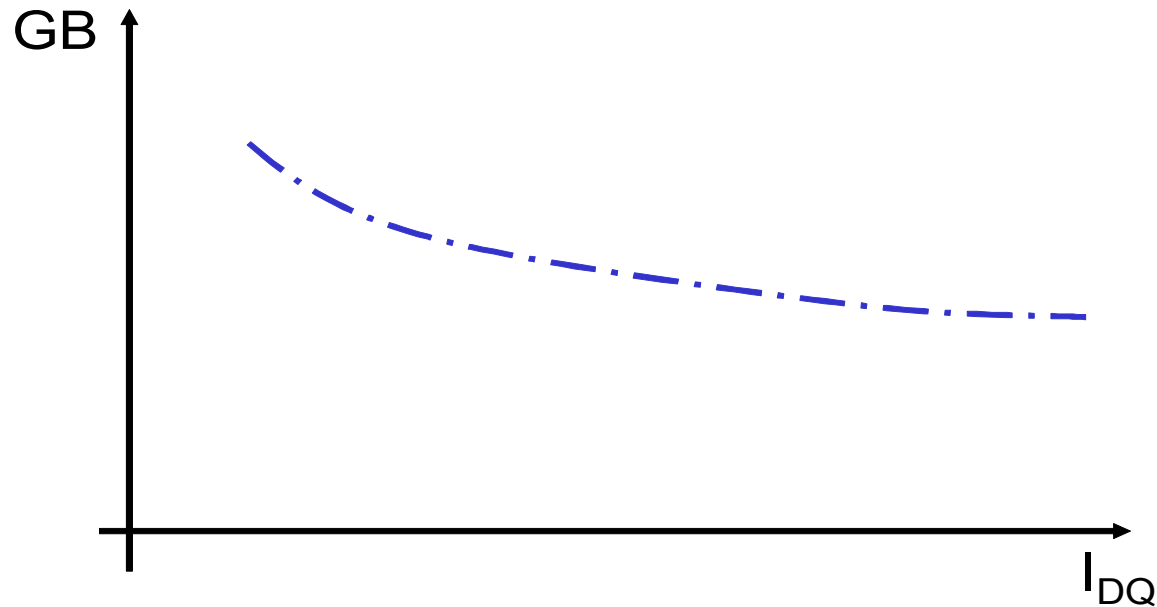Question: How does the GB of the single-stage amplifier change with bias current?

$$GB = \frac{1}{\sqrt{I_{DQ}}} \frac{P}{C_L} \sqrt{\frac{2\mu C_{OX} W}{L}}$$

GB decreases with the reciprocal of the square root of I_{DQ}




Design Space Exploration

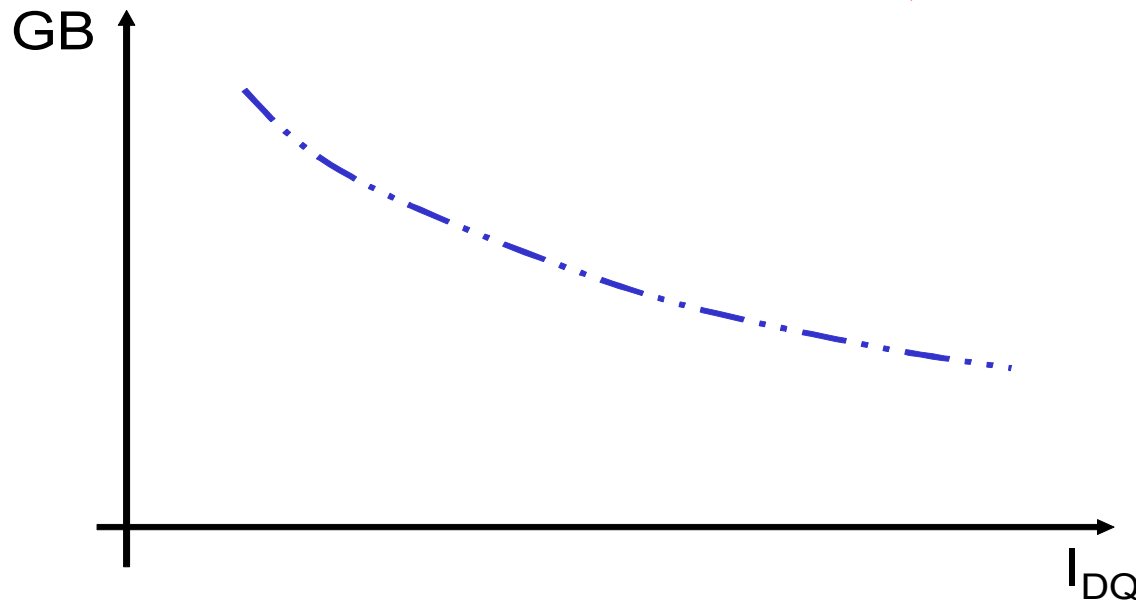Question: How does the GB of the single-stage amplifier change with bias current?

$$GB = \frac{\sqrt{\frac{2\mu C_{OX} WP^3}{LV_{DD}}}}{I_{DQ} C_L}$$

GB decreases with the reciprocal of I_{DQ}



Design Space Exploration

Question: How does the GB of the single-stage amplifier change with bias current?

$$GB = \left[\frac{2}{C_L} \right] \left[\frac{I_{DQ}}{V_{EB}} \right] \quad \longrightarrow \quad \text{Increases Linearly}$$

$$GB = \left[\frac{\sqrt{2\mu C_{OX}}}{C_L} \right] \left[\sqrt{\frac{W}{L}} \sqrt{I_{DQ}} \right] \quad \longrightarrow \quad \text{Increases Quadratically}$$


$$GB = \left[\frac{2}{V_{DD} C_L} \right] \left[\frac{P}{V_{EB}} \right] \quad \longrightarrow \quad \text{Independent of } I_{DQ}$$

$$GB = \frac{1}{\sqrt{I_{DQ}}} \frac{P}{C_L} \sqrt{\frac{2\mu C_{OX} W}{L}} \quad \longrightarrow \quad \text{Decreases Quadratically}$$

$$GB = \frac{\sqrt{\frac{2\mu C_{OX} W P^3}{L V_{DD}}}}{I_{DQ} C_L} \quad \longrightarrow \quad \text{Decreases Linearly}$$

It depends upon how the design space is explored !!!

Design Space Exploration

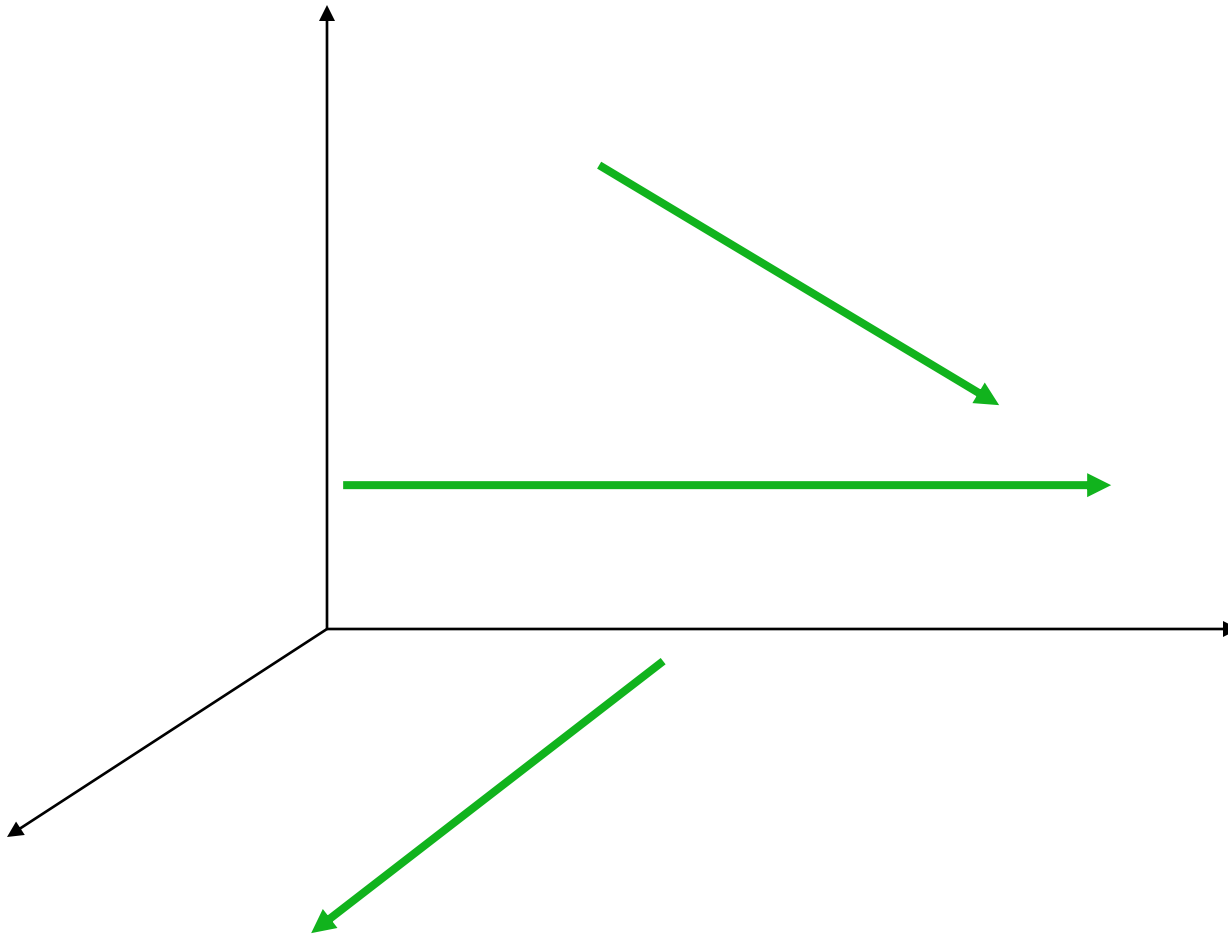

Different trajectories through a design space

Design Space Exploration

Issue becomes more involved for amplifiers or circuits with more than one transistor

Choice of design parameters can have major impact on insight into design

Size of parameter domain should agree with the number of degrees of freedom

Affects of any parameter on performance whether it be in the identified parameter domain or not is strongly dependent on how design space is explored

Small signal and natural parameter domains give little insight into design or performance

Design Space Exploration

Question: How does the A_{V0} of the single-stage amplifier change with V_{EB} ?

$$A_{V0} = \left[\frac{2}{\lambda} \right] \left[\frac{1}{V_{EB}} \right]$$

A_{V0} decreases with the reciprocal of V_{EB}

Even though there are 2 degrees of freedom, the dependence of A_{V0} on V_{EB} is unambiguous

Question: How does the A_{V0} of the single-stage amplifier change with P ?

A_{V0} is independent of P if V_{EB} is fixed

Even though there are 2 degrees of freedom, the dependence of A_{V0} on P is unambiguous provided A_{V0} is fixed

Design Space Exploration

Question: How does the GB of the single-stage amplifier change with P?

$$GB = \left[\frac{2}{V_{DD} C_L} \right] \left[\frac{P}{V_{EB}} \right]$$

GB increases linearly with P ?

This is essentially the same question of how GB varies with I_{DQ}

Answer depends on how V_{EB} changes



GB increases linearly with P provided the A_{V0} is fixed ?

This answer is unambiguous since fixing A_{V0} fixes V_{EB}

Often in situations where the dc gain requirements are fixed and this necessitates a very unfavorable tradeoff between GB and power in this structure since P is a critical “resource” in most applications !

Single-Stage Low-Gain Op Amps


- Single-ended input

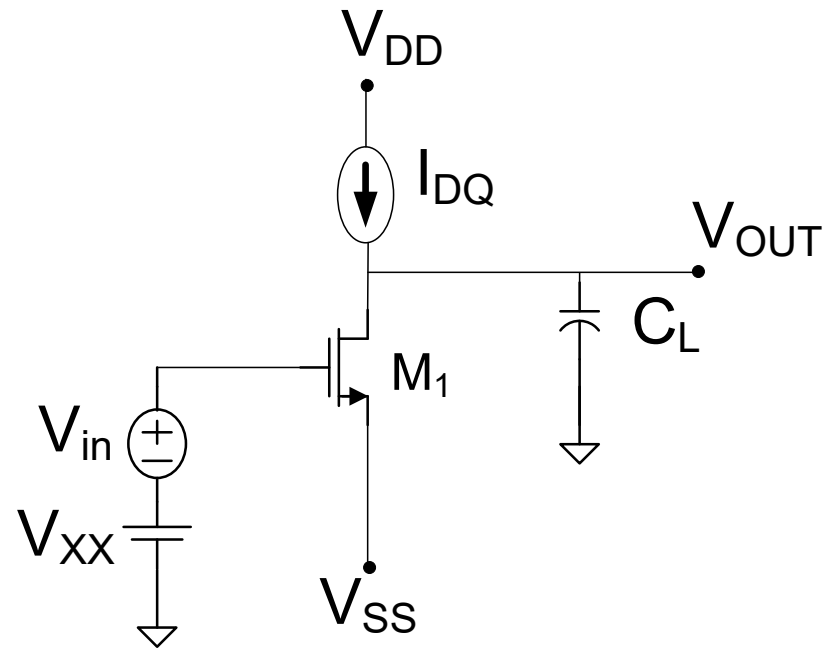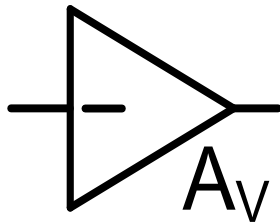

Basic single-stage op amp

Single-Stage Low-Gain Op Amps

- Single-ended input

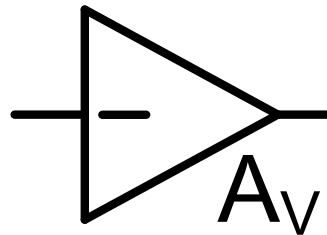

Observations:

- This circuit often known as a common source amplifier
- Gain in the 30dB to 45dB range
- Inherently a transconductance amplifier since output impedance is high
- Voltage gain is ratio of transconductance gain to output conductance
- Critical to know degrees of freedom in design and know how to systematically explore design space
- Alternative parameter domain much more useful for design than small-signal domain or natural domain
- Performance of differential circuits will be obtained by inspection from those of the single-ended structures

Review

- Multiple parameter domains can be used to characterize and explore a design space
- Performance characteristics of interest take on many different forms depending upon how design space is characterized
- Critical to identify the real number of degrees of freedom in design space (mathematical degrees of freedom minus the number of constraints)
- Performance characteristics often can be expressed as product of a process dependent term and an architecture dependent term
 - Facilitates comparison of different architectures
- Choice of characterization parameters can make a major difference on how hard it is to explore a design space


Review

- Design space is often a high-dimensional system with many local extrema (minimums or maximums)
- Be careful about drawing conclusions about how any parameter individually affects system performance because its affect will depend upon how the design space is explored

Design Space for Single-Stage Op Amp

$$GB = \left[\frac{2}{V_{DD}C_L} \right] \left[\frac{P}{V_{EB}} \right]$$

Plot of $GB_N = \frac{P}{V_{EB}}$

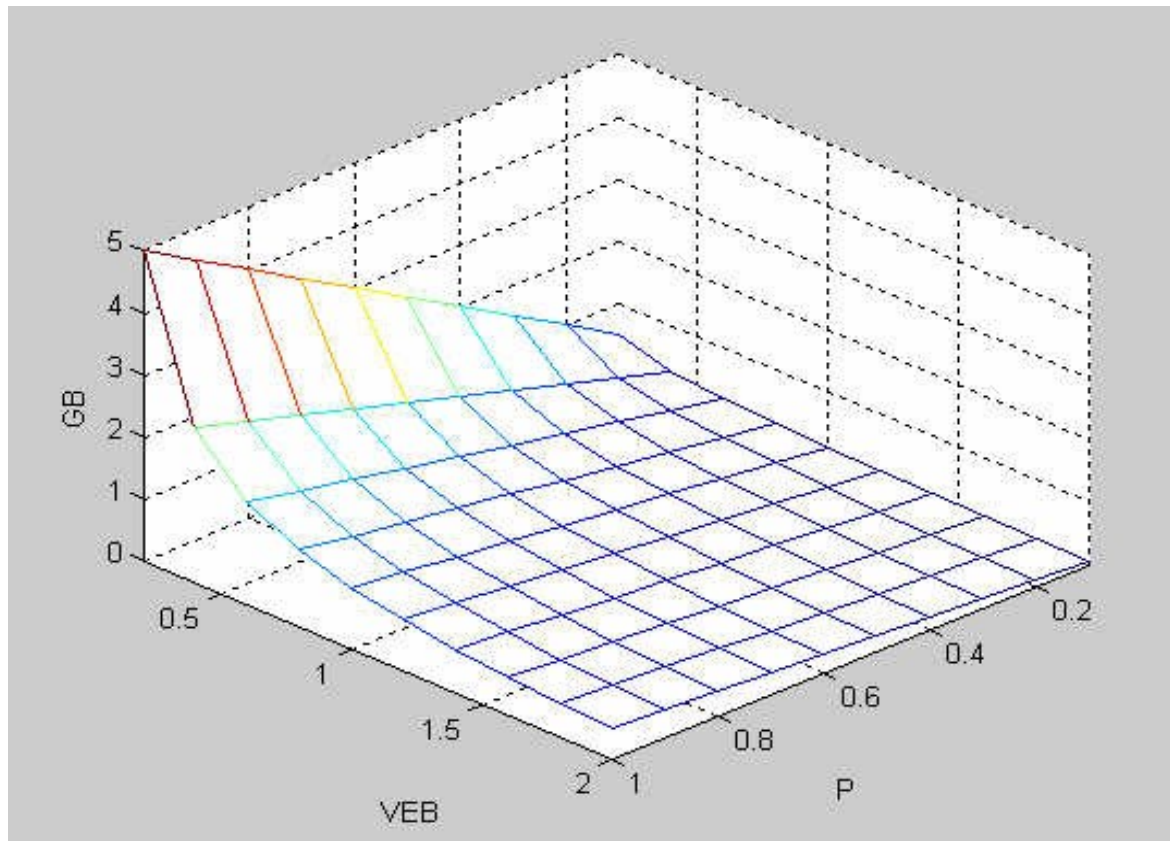


Can we say that GB increases linearly with P ?

Design Space for Single-Stage Op Amp

$$GB = \left[\frac{2}{V_{DD}C_L} \right] \left[\frac{P}{V_{EB}} \right]$$

Plot of $GB_N = \frac{P}{V_{EB}}$

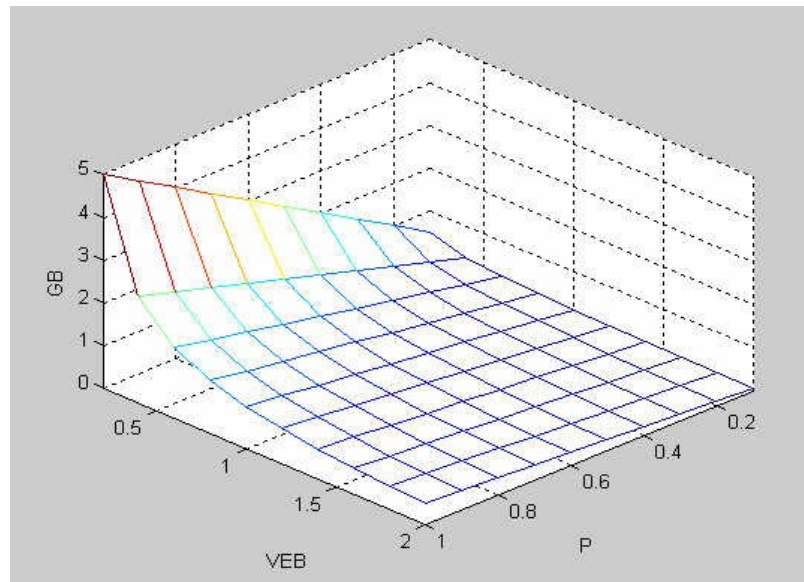

Can we say that GB increases linearly with P ?

Can we say that GB increases linearly with P if A_V is fixed?

Where we are at:

Basic Op Amp Design

- Fundamental Amplifier Design Issues





- Single-Stage Low Gain Op Amps
- Single-Stage High Gain Op Amps
- Two-Stage Op Amp
- Other Basic Gain Enhancement Approaches


Where we are at:

Single-Stage Low-Gain Op Amps

- Single-ended input

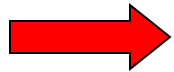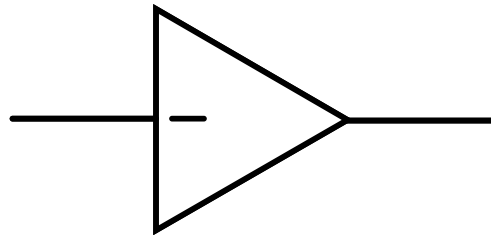

- Differential Input

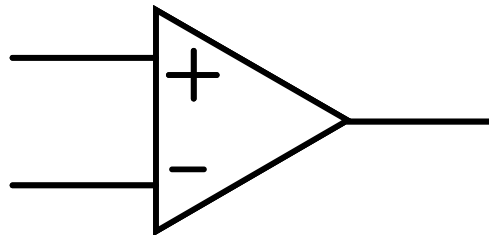

(Symbol does not distinguish between different amplifier types)

Differential Input Low Gain Op Amps

Will Next Show That :

- Differential input op amps can be readily obtained from single-ended op amps
- Performance characteristics of differential op amps can be directly determined from those of the single-ended counterparts


Systematic strategies for designing and analyzing op amps

- Analytical expressions for even simple op amps can become very complicated if brute force analysis techniques are used
- Considerable insight into both performance and design can be obtained from a systematic strategy for design and analysis of op amps
- Most authors present operational amplifiers from an “appear and analyze” approach

A systematic strategy for designing and analyzing op amps will now be developed

Symmetric Networks

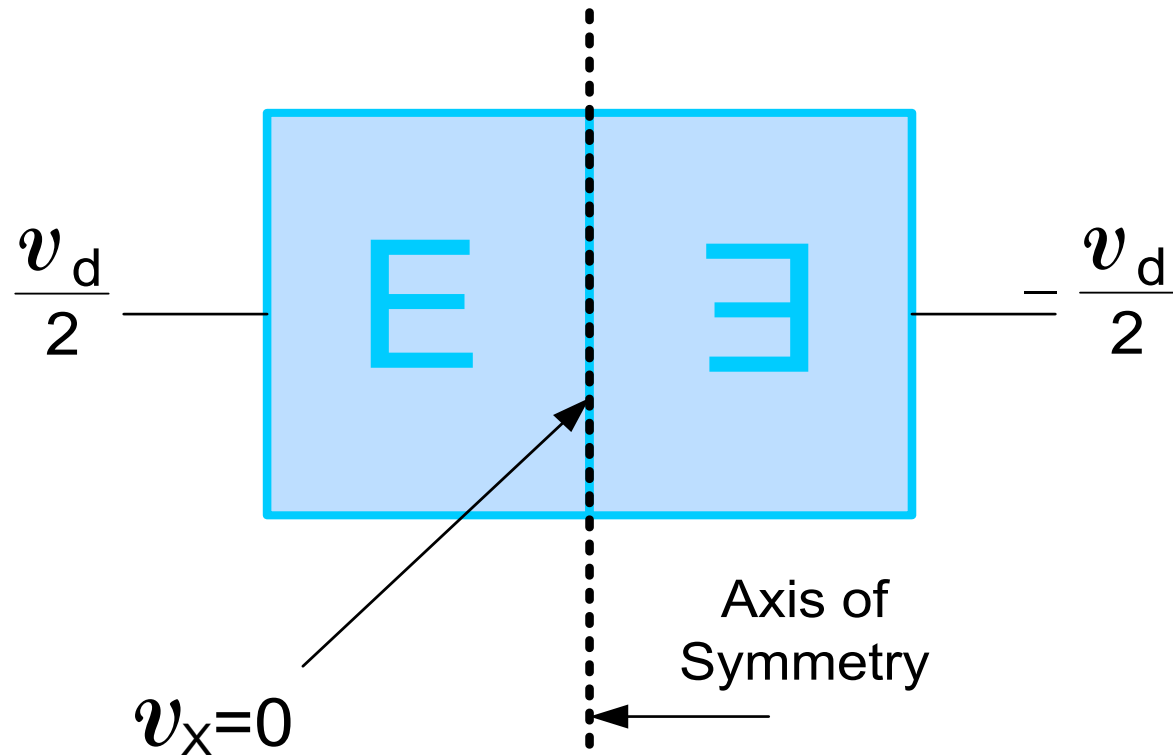Theorem: If a linear network is symmetric, then for all differential symmetric excitations, the small signal voltage is zero at all points on the axis of symmetry.









Counterpart Networks


Definition: The counterpart network of a network is obtained by replacing all n-channel devices with p-channel devices, replacing all p-channel devices with n-channel devices, replacing V_{SS} biases with V_{DD} biases, and replacing all V_{DD} biases with V_{SS} biases.

Counterpart Networks

Example:

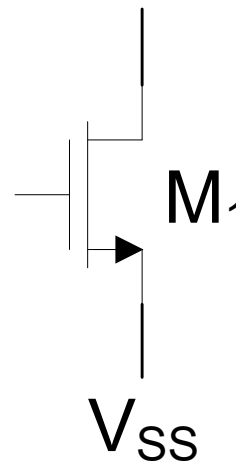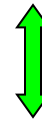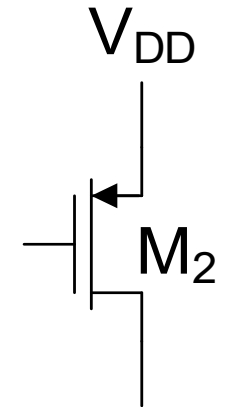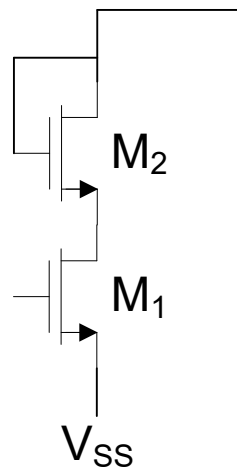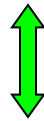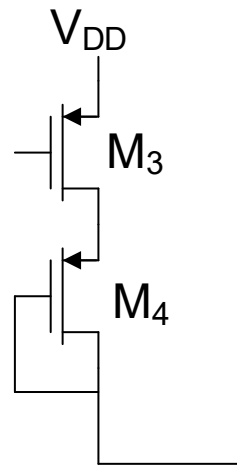

Counterpart Networks

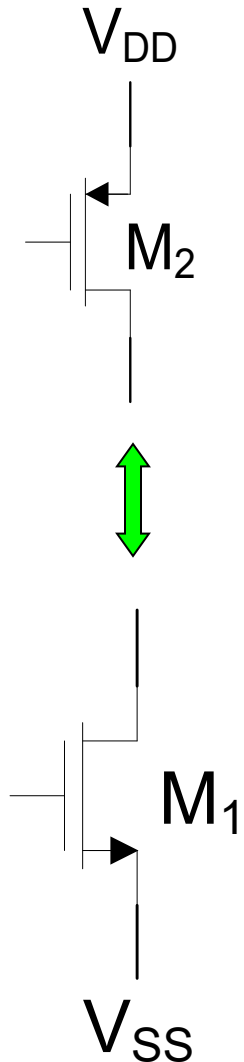

the counterpart network is unique


the counterpart of the counterpart is the original network

Counterpart Networks


Theorem: The parametric expressions for all small-signal characteristics¹, such as voltage gain, output impedance, and transconductance of a network and its counterpart network are the same.

¹when expressed in the small-signal parameter domain


Terminology and Notation

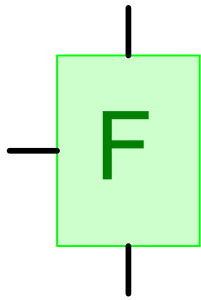


Quarter Circuit

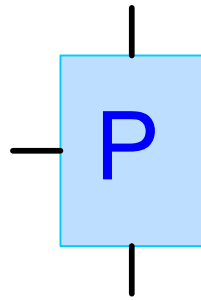


Counterpart Circuit

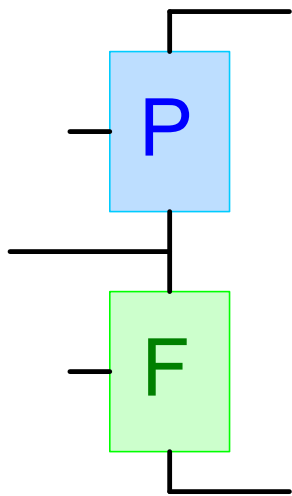

Half Circuit

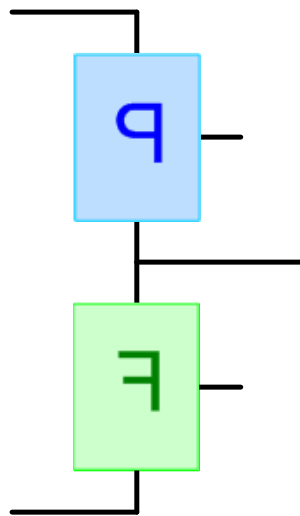

“Reflected Image”
Half Circuit

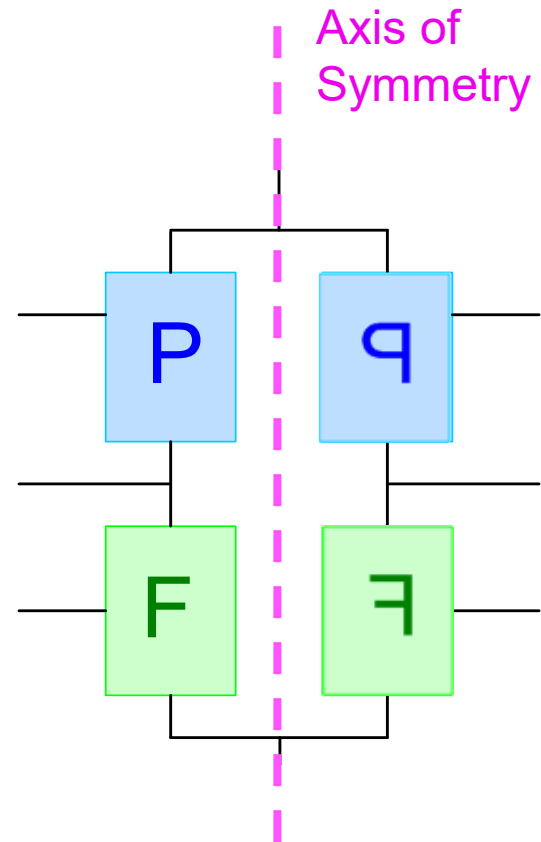


Symmetric Circuit


Reflected Image Half-circuit is identical to half-circuit, just drawn differently

Synthesis of fully-differential op amps from symmetric networks and counterpart networks

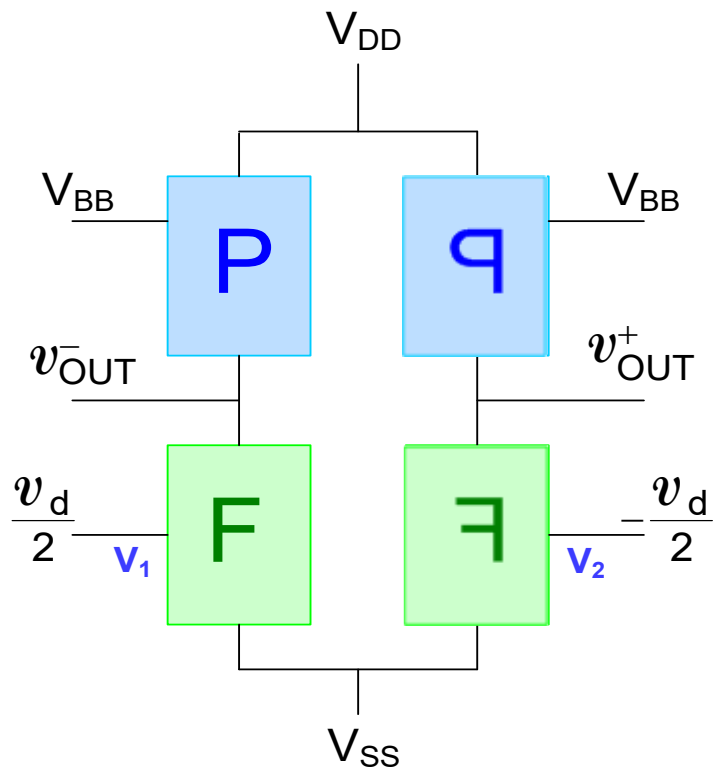
Theorem: If F is any network with a single input and P is its counterpart network, then the following circuits are fully differential circuits --- “op amps”.




$$V_d = V_1 - V_2$$

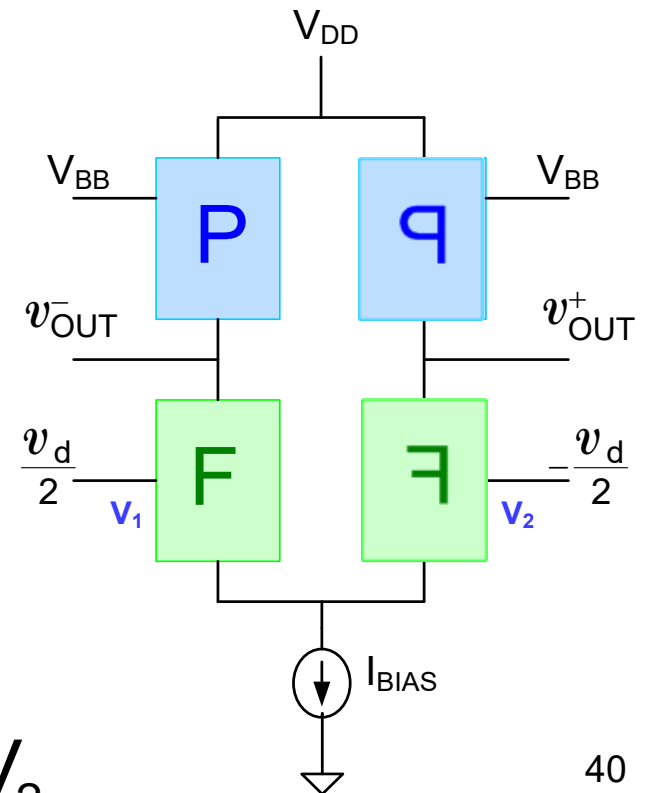

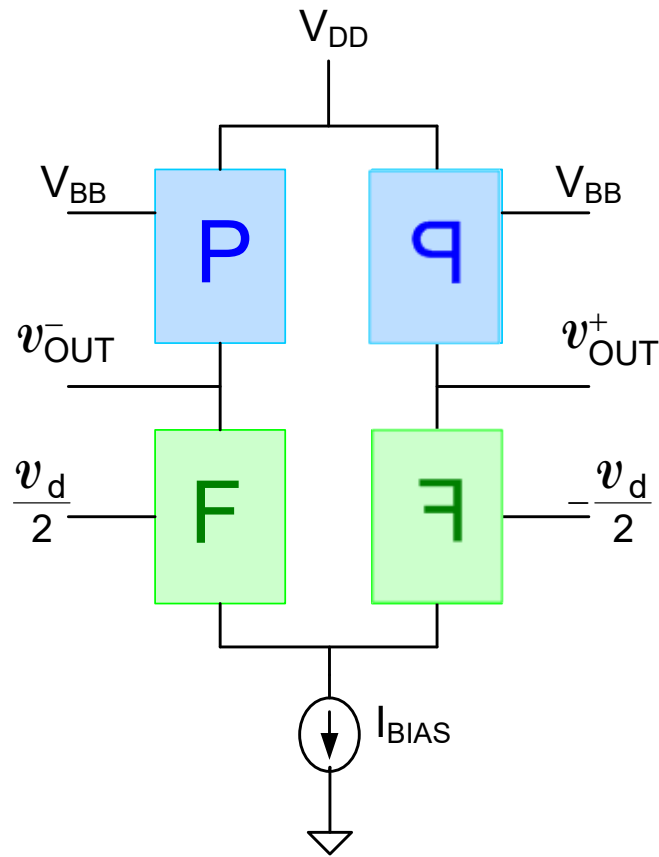
Synthesis of fully-differential op amps from symmetric networks and counterpart networks




$$v_d = V_1 - V_2$$

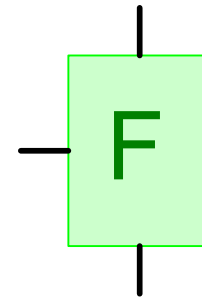


Quarter Circuit

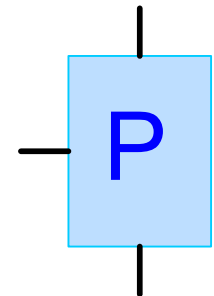

Counterpart Circuit

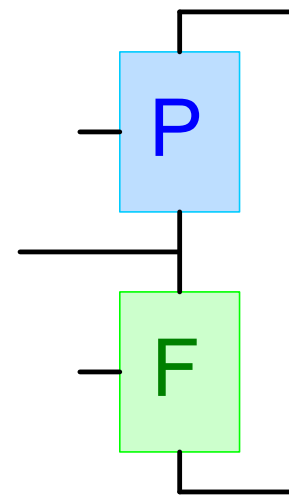


Half Circuit

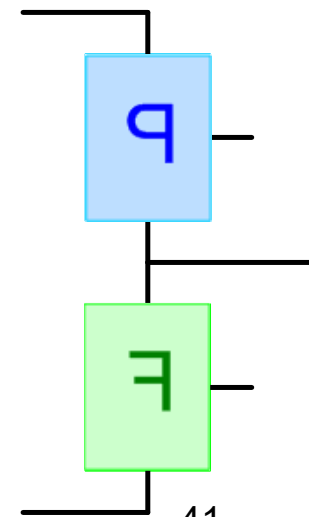


Reflected Image Half Circuit

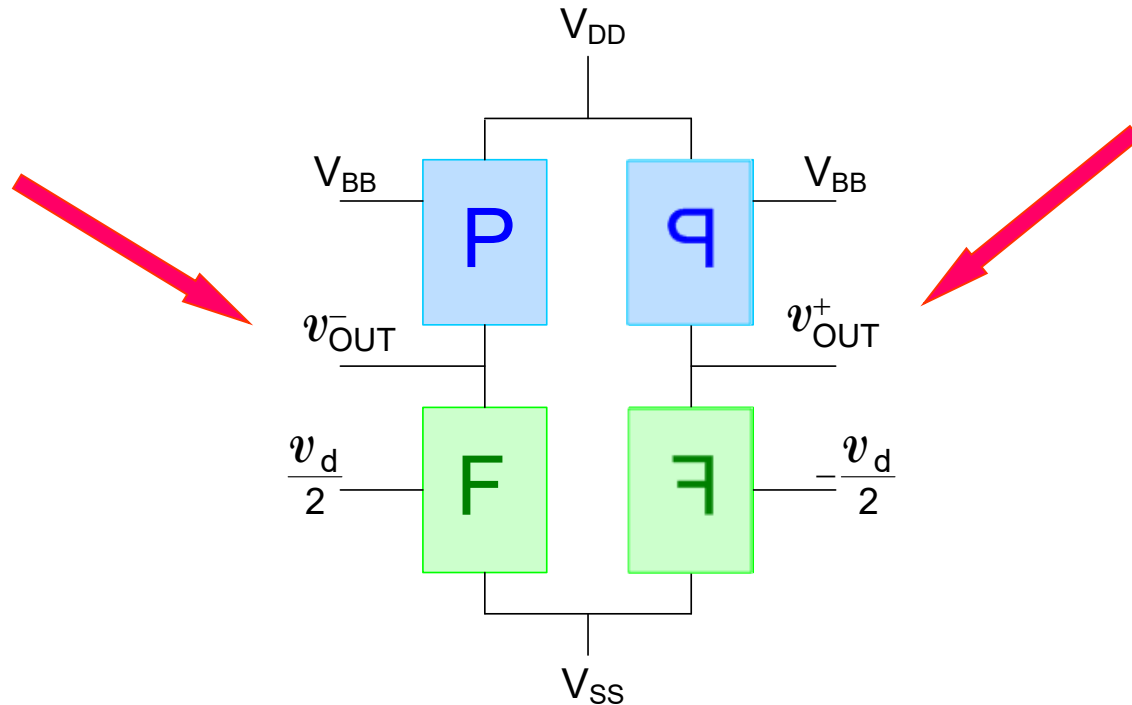Synthesis of fully-differential op amps from symmetric networks and counterpart networks



What do we do with the extra output ?

What do we do with the extra output ?

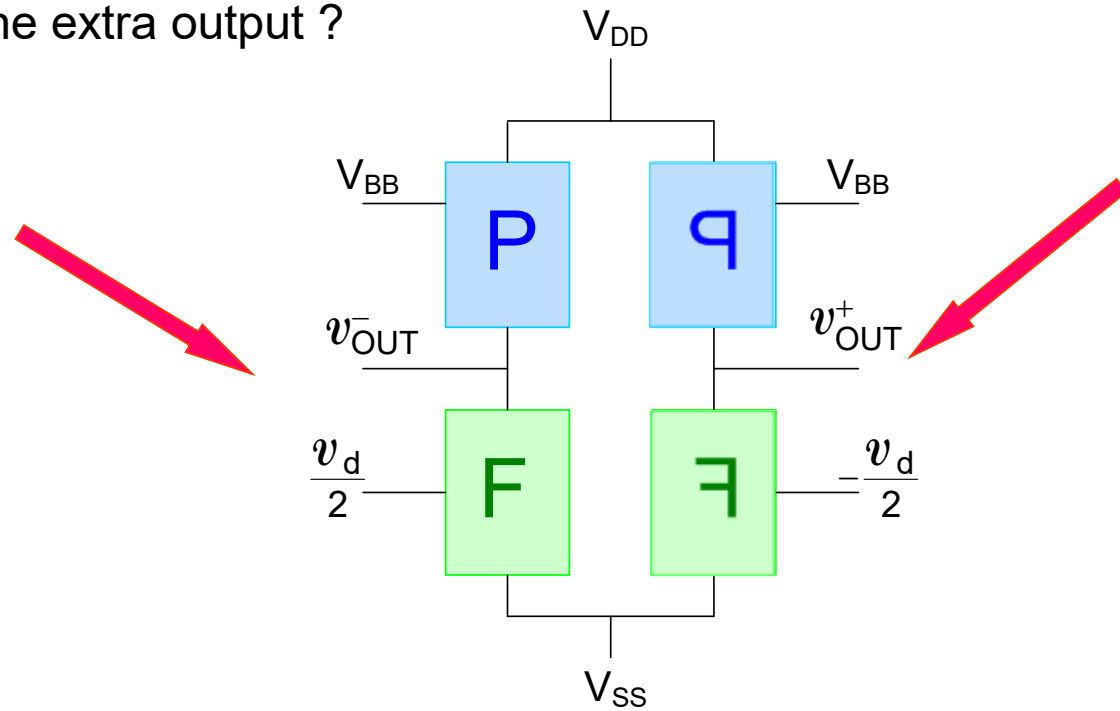


Use it or ignore it !!




Synthesis of fully-differential op amps from symmetric networks and counterpart networks

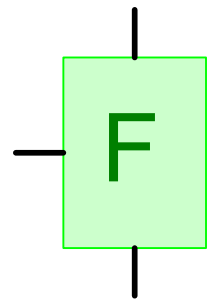A fully differential op amp can be derived from any quarter circuit by combining it with its counterpart to obtain a half-circuit, combining two half-circuits to form a differential symmetric circuit and then biasing the symmetric differential circuit with a current source on the axis of symmetry.



Quarter Circuit

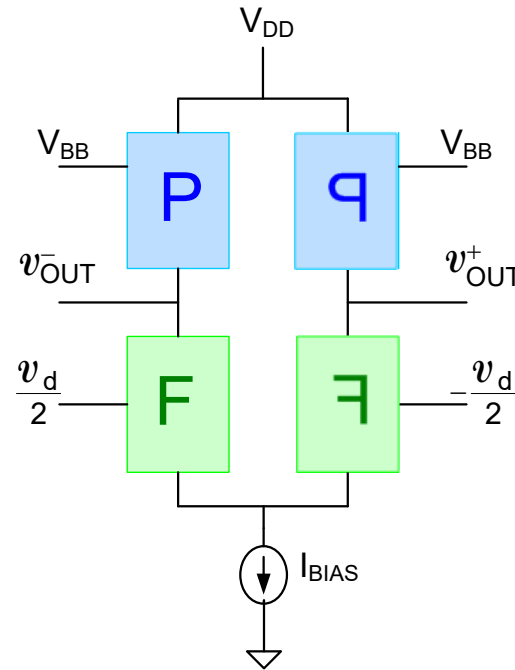


Further, most of the properties of the operational amplifier can be obtained by inspection, from those of the quarter circuit.

Synthesis of fully-differential op amps from symmetric networks and counterpart networks

A fully differential op amp can be derived from any quarter circuit by combining it with its counterpart to obtain a half-circuit, combining two half-circuits to form a differential symmetric circuit and then biasing the symmetric differential circuit with a current source on the axis of symmetry.

Further, most of the properties of the operational amplifier can be obtained by inspection, from those of the quarter circuit.

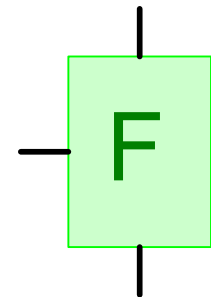Implications: Much Op Amp design can be reduced to designing much simpler quarter-circuits where it is much easier to get insight into circuit performance





**Quarter
Circuit**

- Fully Differential Single-Stage Amplifier
 - – General Differential Analysis
 - 5T Op Amp from simple quarter circuit
 - Biasing with CMFB circuit
 - Common-mode and differential-mode analysis
 - Common Mode Gain
 - Overall Transfer Characteristics
- Design of 5T Op Amp
- Slew Rate

Characterization of Quarter Circuit

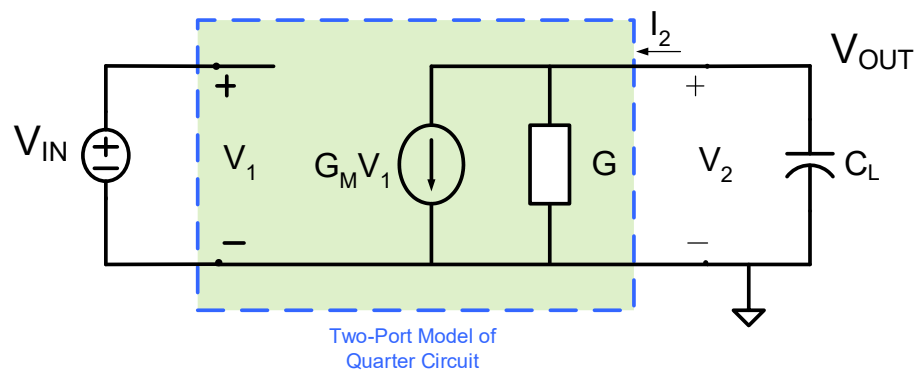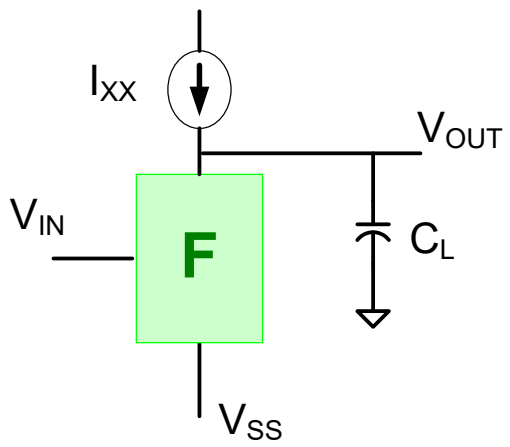If the input impedance is infinite and circuit is unilateral, the two-port network only has two characterizing parameters : G_M and G



$$\left. \begin{aligned} \mathbf{V}_{OUT}(\mathbf{G} + \mathbf{sC}_L) + \mathbf{G}_M \mathbf{V}_1 &= \mathbf{0} \\ \mathbf{V}_{IN} &= \mathbf{V}_1 \end{aligned} \right\}$$






$$\mathbf{A}_{VQC}(\mathbf{s}) = \frac{-\mathbf{G}_M}{\mathbf{sC}_L + \mathbf{G}}$$

$$\mathbf{A}_{voqc} = -\frac{\mathbf{G}_M}{\mathbf{G}}$$


$$\mathbf{BW} = \frac{\mathbf{G}}{\mathbf{C}_L}$$

$$\mathbf{GB} = \frac{\mathbf{G}_M}{\mathbf{C}_L}$$

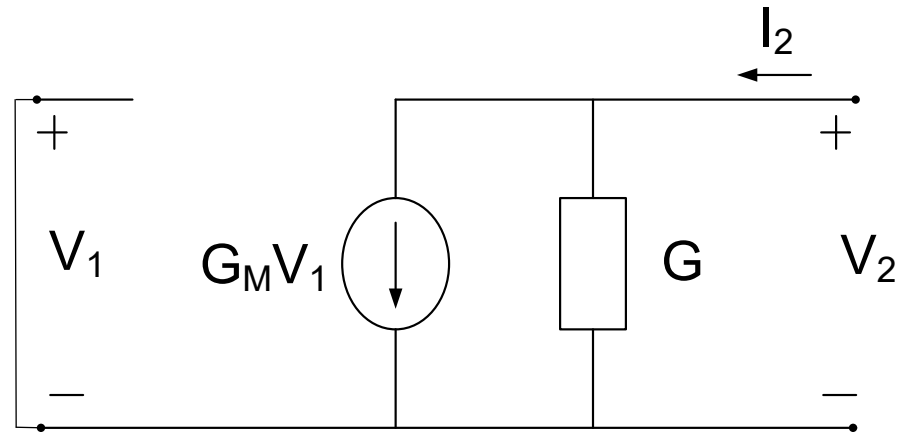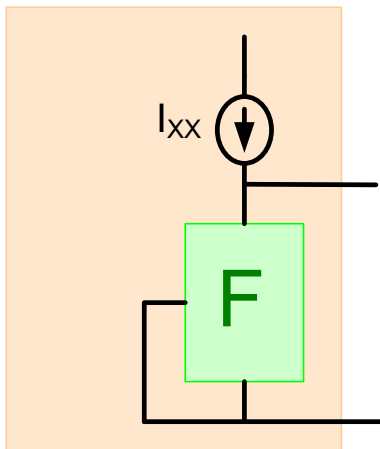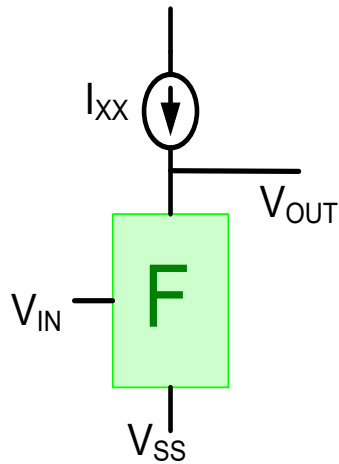Characterization of Quarter Circuit (or Counterpart Circuit) with input port terminated in small-signal short circuit



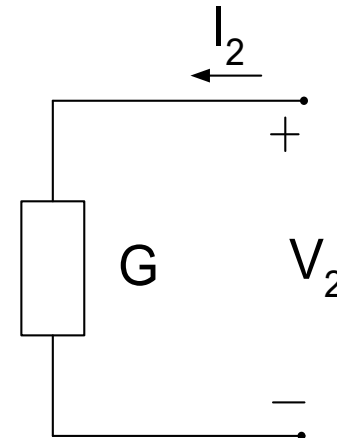
If the input port of a two-port has an ac short, then the two-port reduces to a one-port characterized by the conductance G




Determination of op amp characteristics from quarter circuit characteristics

-- The "differential" gain --

$$A_{VQC}(s) = \frac{-G_M}{sC_L + G}$$

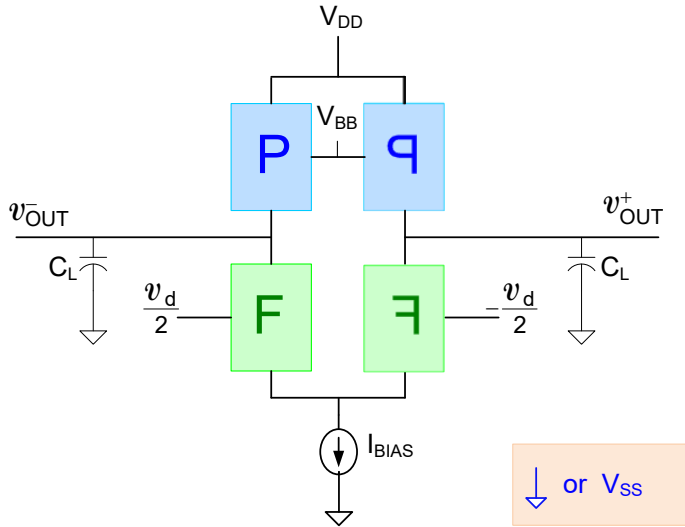

Small signal differential half-circuit

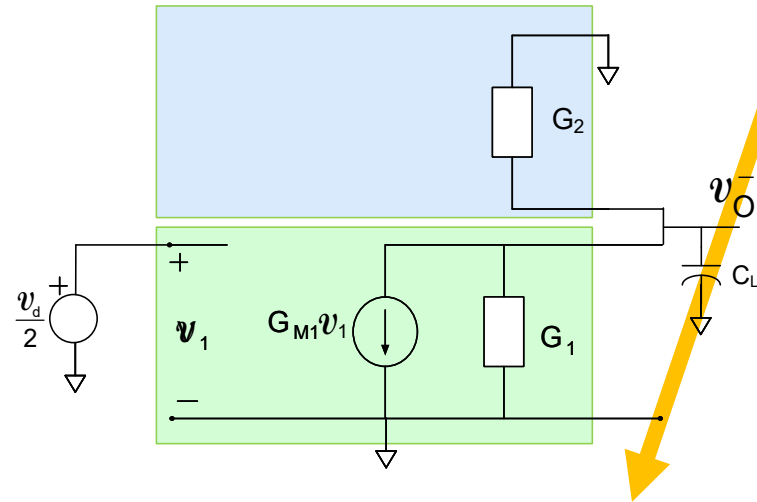

Derivation:
from KCL and KVL:

$$\left. \begin{aligned} v_o^- (G_1 + G_2 + sC_L) + G_{M1}v_1 &= 0 \\ v_1 &= \frac{v_d}{2} \end{aligned} \right\} \Rightarrow$$


$$A_V = \frac{v_o^-}{v_d} = \frac{-\frac{G_{M1}}{2}}{sC_L + G_1 + G_2}$$

Note: Factor of 2 reduction of differential gain since only half of the differential input is applied to the half-circuit

Note: More reduction of gain since denominator increases

Determination of op amp characteristics from quarter circuit characteristics

-- The "differential" gain --

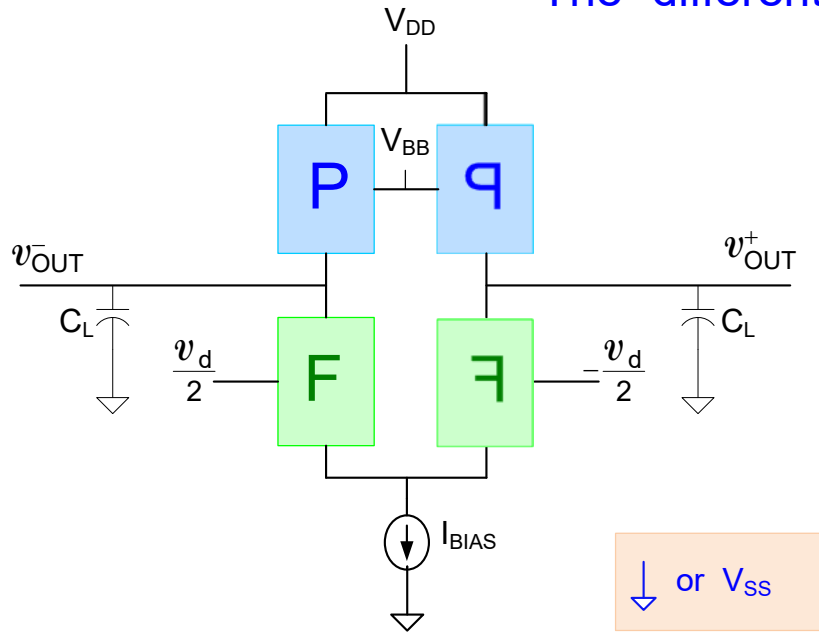


$$A_V = \frac{v_o^-}{v_d} = \frac{-\frac{G_{M1}}{2}}{sC_L + G_1 + G_2}$$



$A_{VO}=?$
 $BW=?$
 $GB=?$

Small signal differential half-circuit

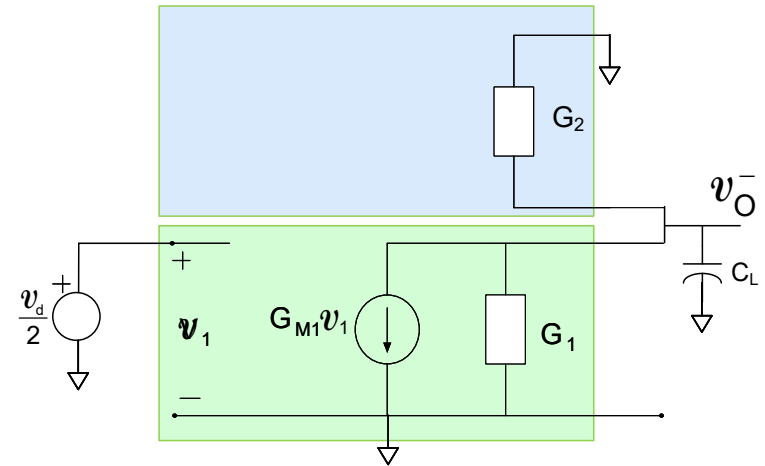

$$A_{VO} = \frac{-G_{M1}}{2(G_1 + G_2)}$$


$$BW = \frac{G_1 + G_2}{C_L}$$

$$GB = \frac{G_{M1}}{2C_L}$$

Determination of op amp characteristics from quarter circuit characteristics


-- The "differential" gain --

Small signal Quarter Circuit

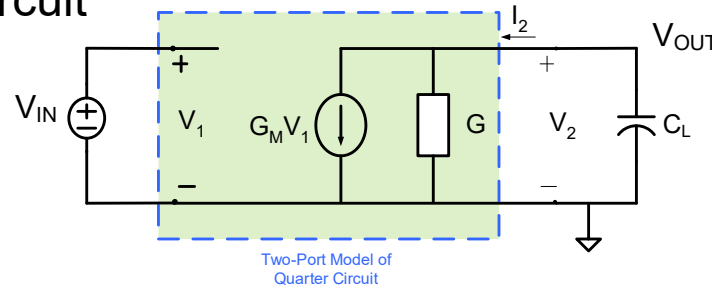

$$A_{VQC}(s) = \frac{-G_M}{sC_L + G}$$

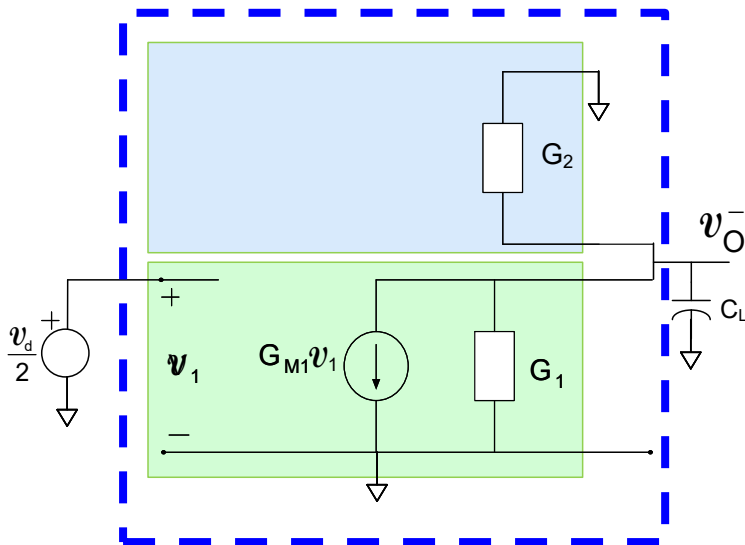
Small signal differential half-circuit (repeated from last slide)



$$A_V = \frac{v_o^-}{v_d} = \frac{-\frac{G_{M1}}{2}}{sC_L + G_1 + G_2}$$

$$G_M = \frac{G_{M1}}{2}$$

$$G = G_1 + G_2$$

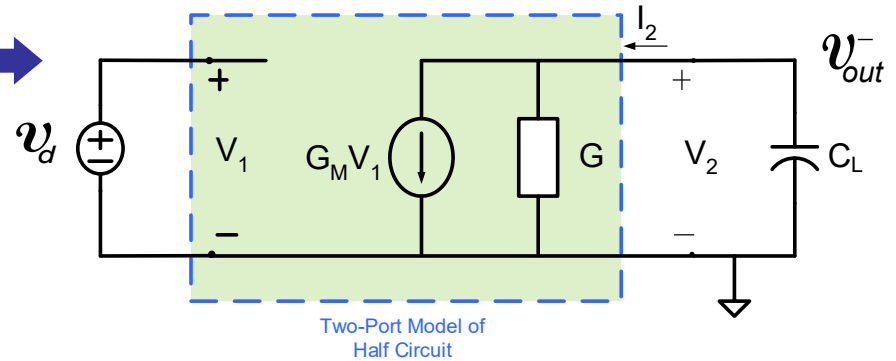


$$A_{VHC}(s) = \frac{-G_M}{sC_L + G}$$

Determination of op amp characteristics from quarter circuit characteristics


-- The "differential" gain --

Small signal Quarter Circuit

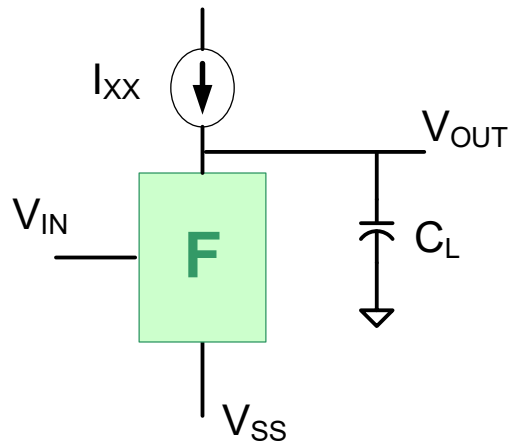

$$A_{VQC}(s) = \frac{-G_M}{sC_L + G}$$

Small signal differential amplifier

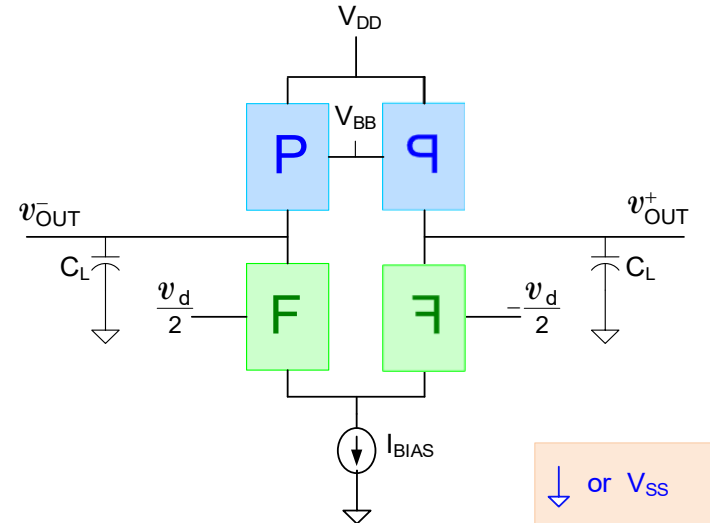


$$A_V = \frac{v_o^-}{v_d} = \frac{-\frac{G_{M1}}{2}}{sC_L + G_1 + G_2}$$



Determination of op amp characteristics from quarter circuit characteristics

-- The "differential" gain --

Small signal Quarter Circuit

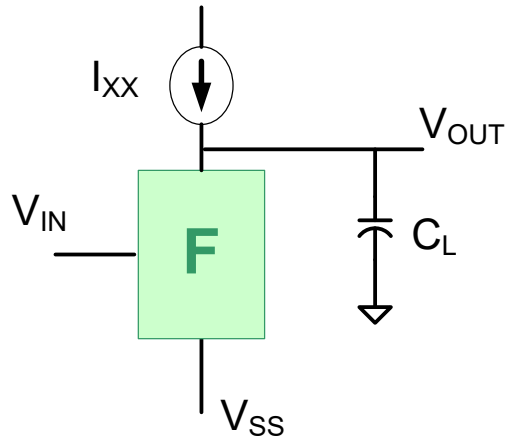


$$A_{voqc} = -\frac{G_M}{G}$$

$$BW = \frac{G}{C_L}$$

$$GB = \frac{G_M}{C_L} \longleftrightarrow$$

Small signal differential amplifier

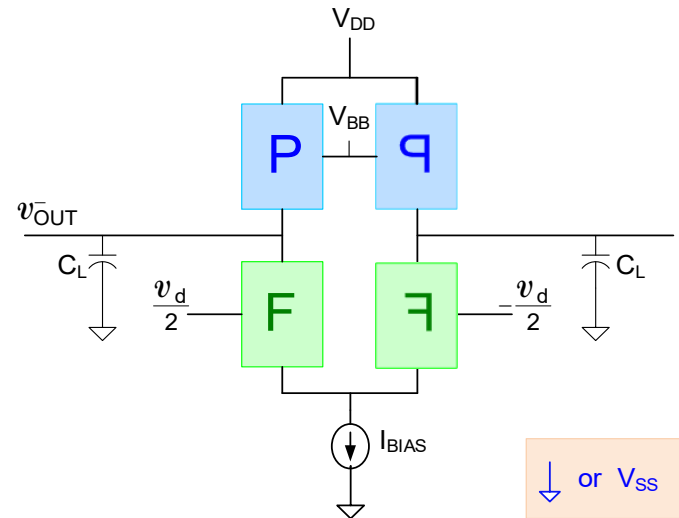

$$A_{V0} = \frac{v_{OUT}^-}{v_d} = \frac{-G_{M1}}{2(G_1 + G_2)}$$

$$BW = \frac{G_1 + G_2}{C_L}$$

$$GB = \frac{G_{M1}}{2C_L}$$

Note: Factor of 4 reduction of gain if $G_1=G_2$ (this often occurs)



Note: Factor of 2 increase of BW if $G_1=G_2$ (this often occurs)

Note: Factor of 2 reduction of GB if $G_1=G_2$ (this often occurs)

Remember this is applicable to ANY quarter circuit !

Comparison of Tail Voltage and Tail Current Source Structures

-- The "differential" gain --

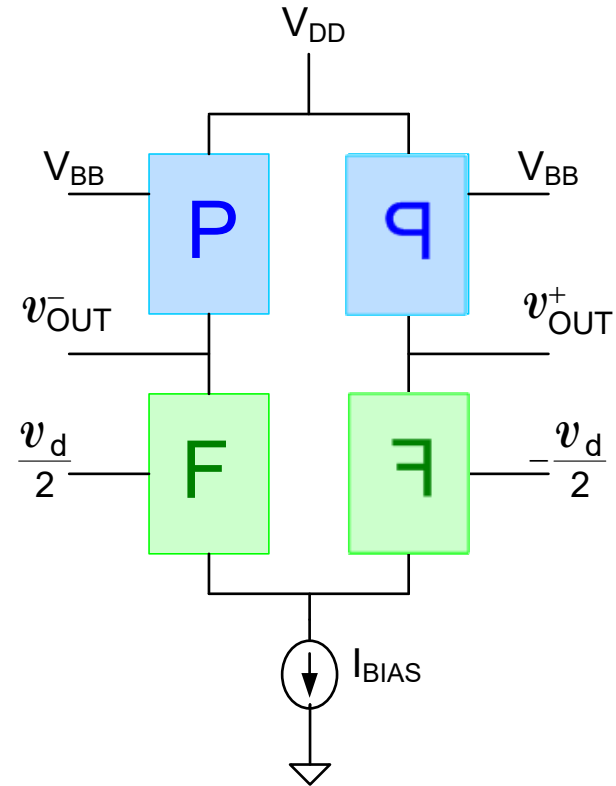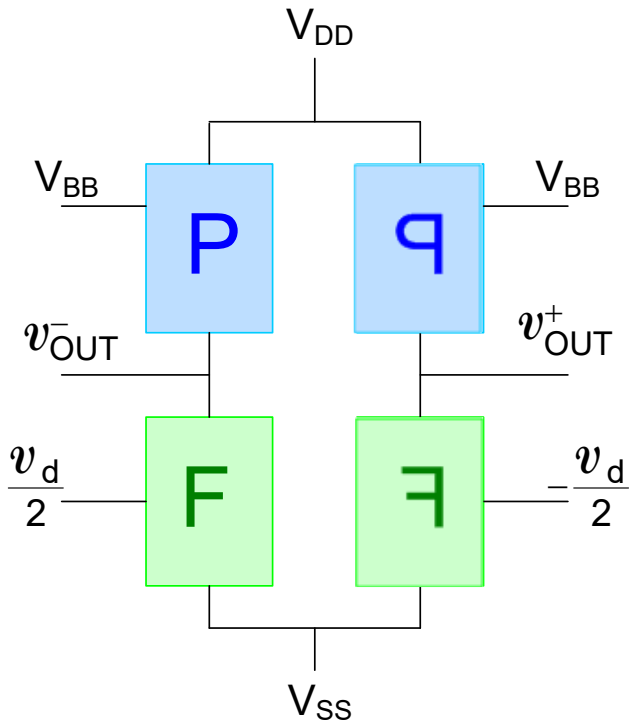



Small signal half-circuits are identical so differential voltage gains, BW, and GB are all the same

Biasing Issues for Differential Amplifier


- Tail voltage bias not suitable for large common-mode (CM) input range but does offer good output swing
- Tail current bias provides good CM input range but at the expense of a modest reduction in output signal swing

Differential Output Amplifiers

-- The "differential" gain --

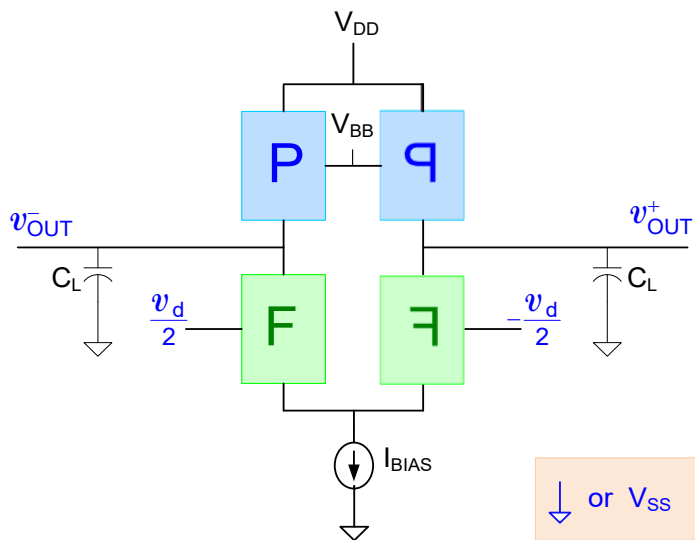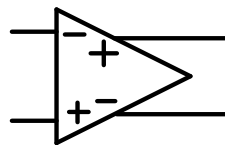


Single-Ended Outputs

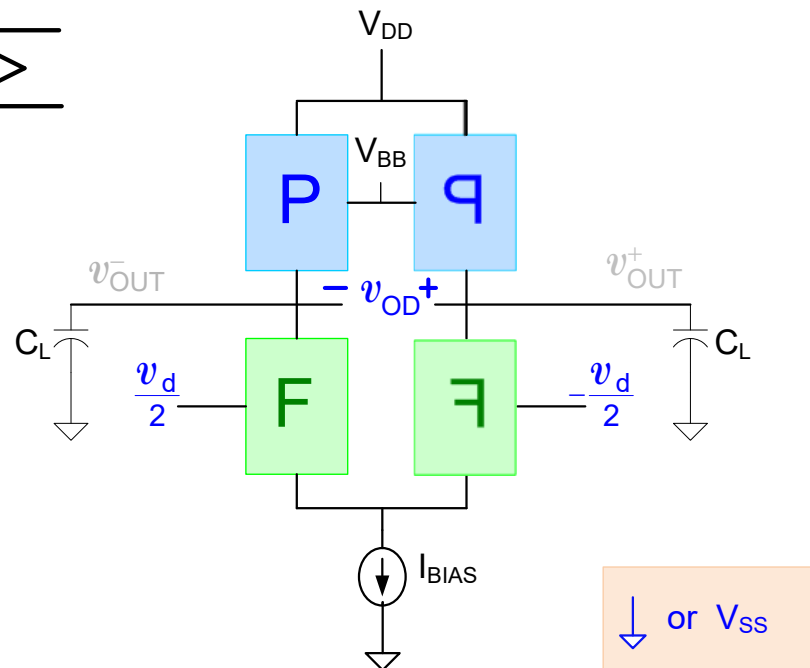

Differential Output


Theorem: For a symmetric circuit with symmetric outputs and differential excitations:

- Differential Voltage Gain Double that of Single-Ended Structure
- BW is the same
- GB Doubles for the Differential Output Structure

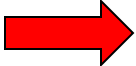
- Fully Differential Single-Stage Amplifier
 - General Differential Analysis
 -  – 5T Op Amp from simple quarter circuit
 - Biasing with CMFB circuit
 - Common-mode and differential-mode analysis
 - Common Mode Gain
 - Overall Transfer Characteristics
- Design of 5T Op Amp
- Slew Rate

Applications of Quarter-Circuit Concept to Op Amp Design

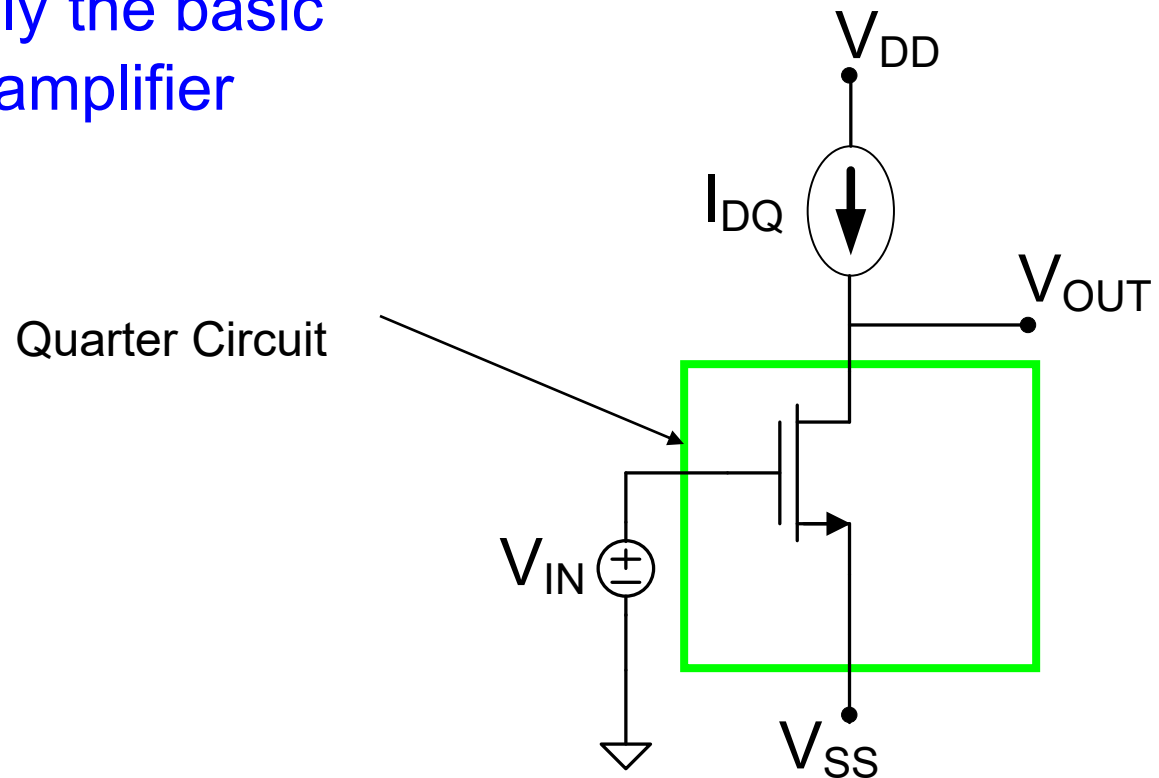
consider initially the basic single-ended amplifier



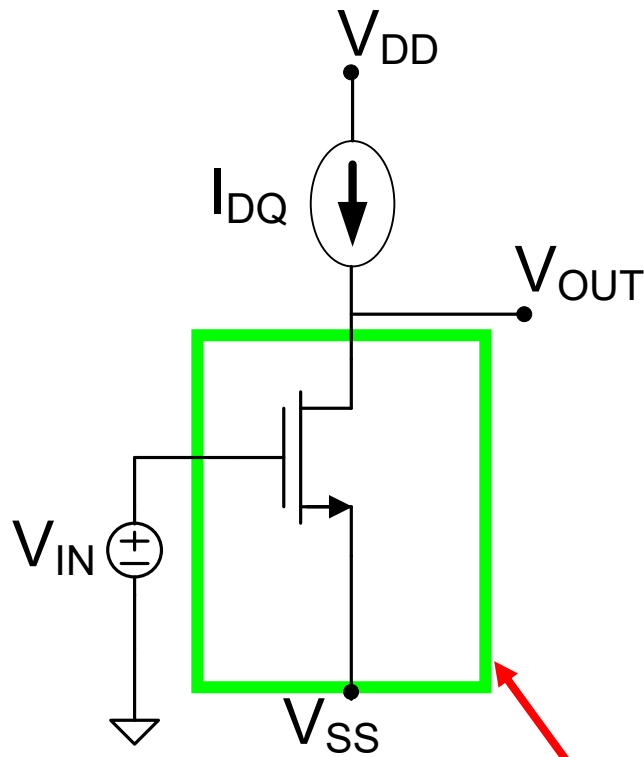Single-stage single-input low-gain op amp




Basic Structure

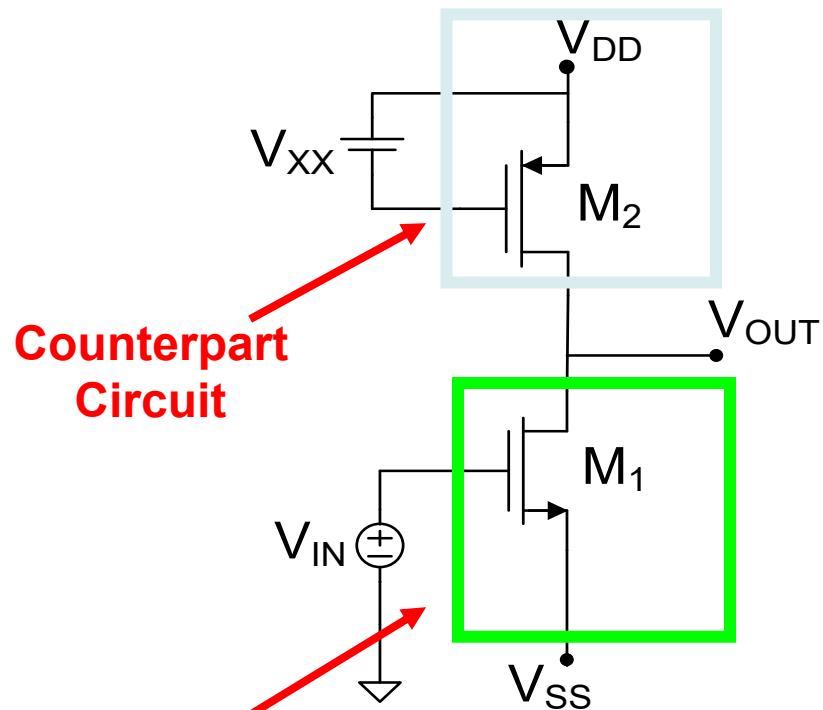

Counterpart Circuit


Practical Implementation

Small signal model of half-circuit

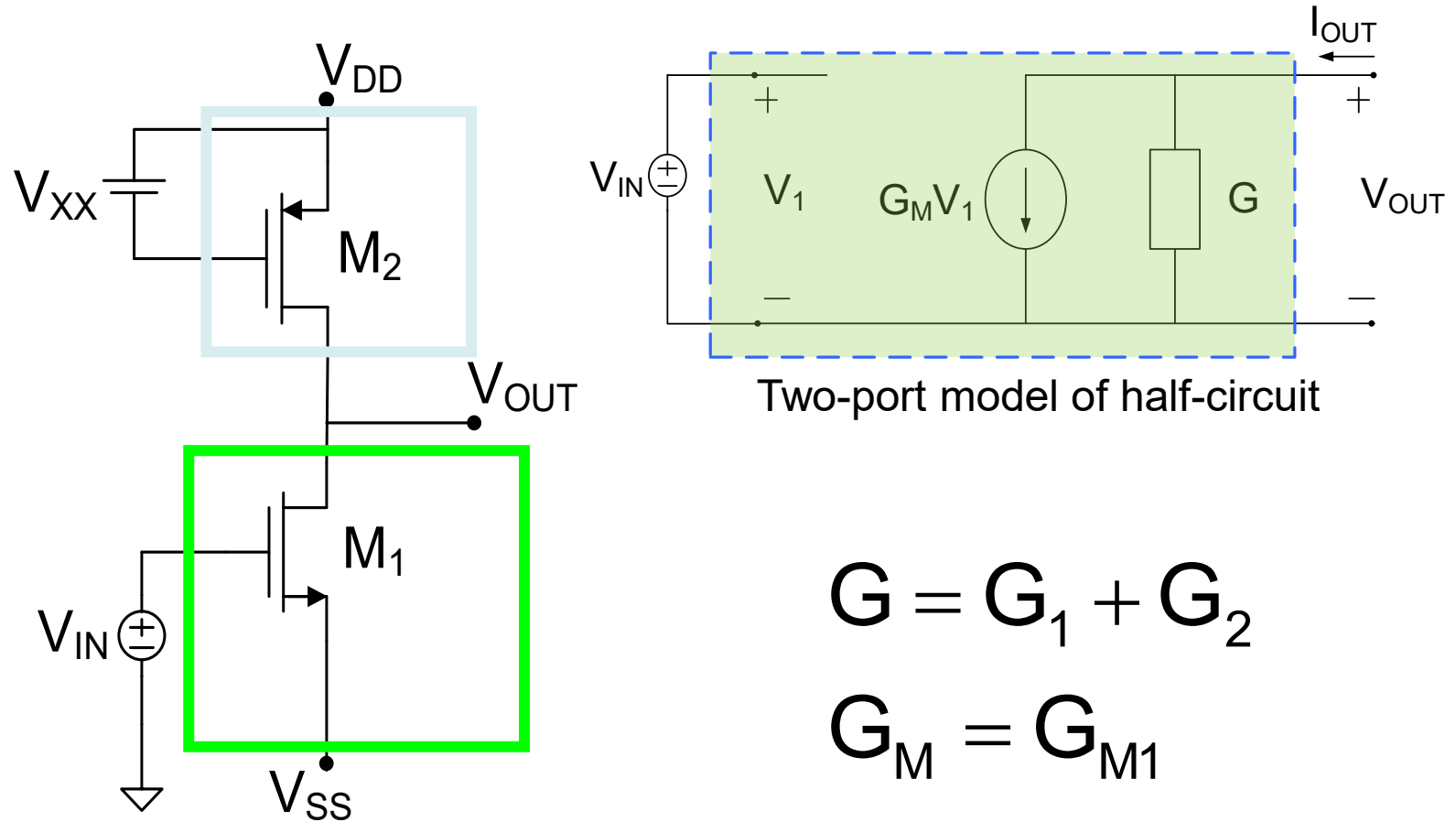


Single-stage low-gain differential op amp

-- The "differential" gain --

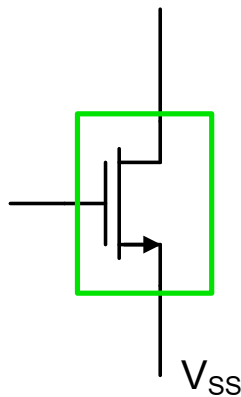

Quarter Circuit

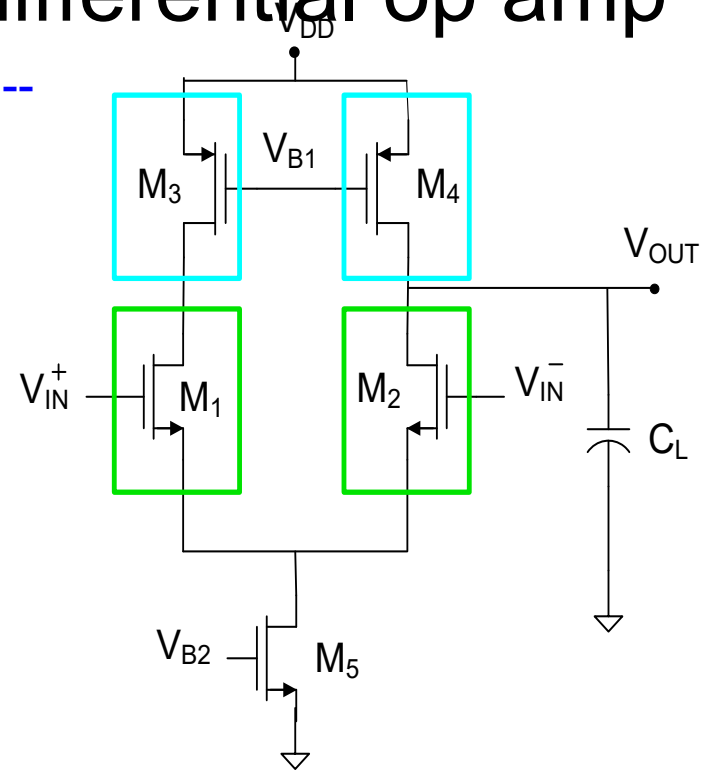

Single-Ended Output : Differential Input Gain

$$A(s) = \frac{v_{OUT}}{v_d} = \frac{-\frac{g_{m1}}{2}}{sC_L + g_{o1} + g_{o3}}$$


$$A_{V0} = \frac{-g_{m1}}{2(g_{o1} + g_{o3})}$$

$$BW = \frac{g_{o1} + g_{o3}}{C_L}$$

$$GB = \frac{g_{m1}}{2C_L}$$


Circuit is Very Sensitive to V_{B1} and V_{B2} !!

- Have synthesized fully differential op amp from quarter circuit !
- Have obtained analysis of fully differential op amp directly from quarter circuit !
- Still need to determine what happens if input is not differential !
- Have almost obtained op amp characteristics by inspection from quarter circuit !!

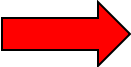- Fully Differential Single-Stage Amplifier
 - General Differential Analysis
 - 5T Op Amp from simple quarter circuit
 -  – Biasing with CMFB circuit
 - Common-mode and differential-mode analysis
 - Common Mode Gain
 - Overall Transfer Characteristics
- Design of 5T Op Amp
- Slew Rate

Single-stage low-gain differential op amp

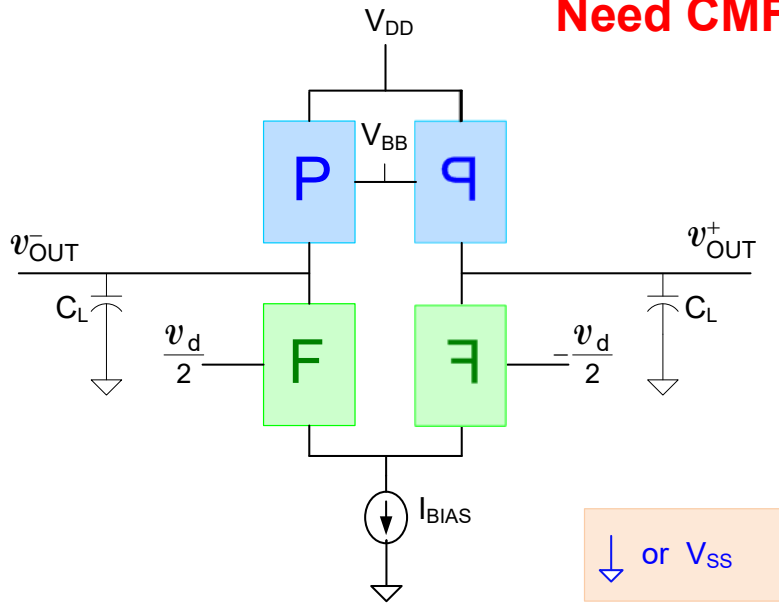-- The "differential" gain --
Need CMFB circuit




$$A(s) = \frac{v_{OUT}^-}{v_d} = \frac{-\frac{G_M}{2}}{sC_L + G_1 + G_2}$$

$$A_{V0} = \frac{-G_{M1}}{2(G_1 + G_2)}$$

$$BW = \frac{G_1 + G_2}{C_L}$$

$$GB = \frac{G_{M1}}{2C_L}$$

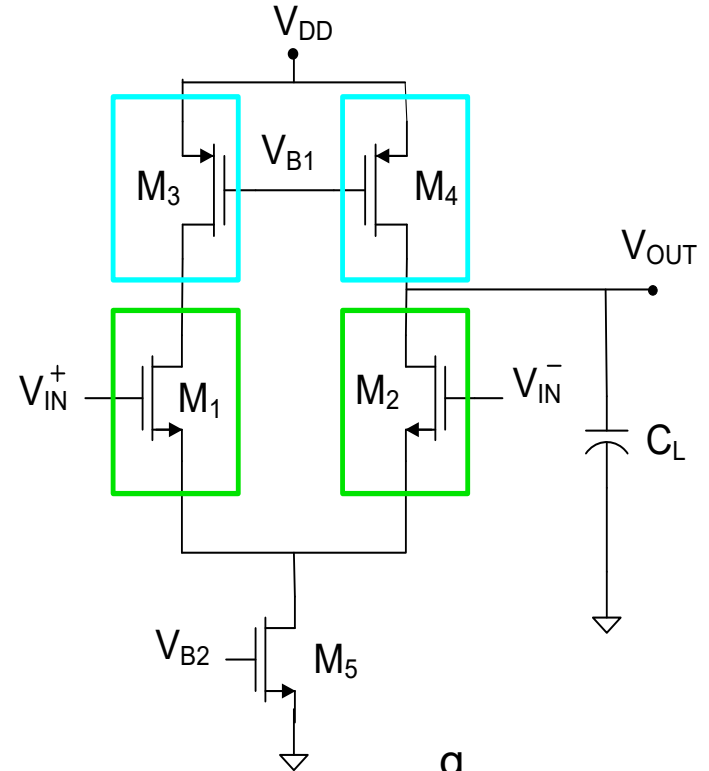


$$A(s) = \frac{-\frac{g_{m1}}{2}}{sC_L + g_{o1} + g_{o3}}$$

$$GB = \frac{g_{m1}}{2C_L}$$

$$A_o = \frac{\frac{g_{m1}}{2}}{g_{o1} + g_{o3}}$$

Have obtained differential gain of 5T Op Amp by inspection from quarter circuit

- Fully Differential Single-Stage Amplifier
 - General Differential Analysis
 - 5T Op Amp from simple quarter circuit
 - Biasing with CMFB circuit
 -  – Common-mode and differential-mode analysis
 - Common Mode Gain
 - Overall Transfer Characteristics
- Design of 5T Op Amp
- Slew Rate



Stay Safe and Stay Healthy !

End of Lecture 3