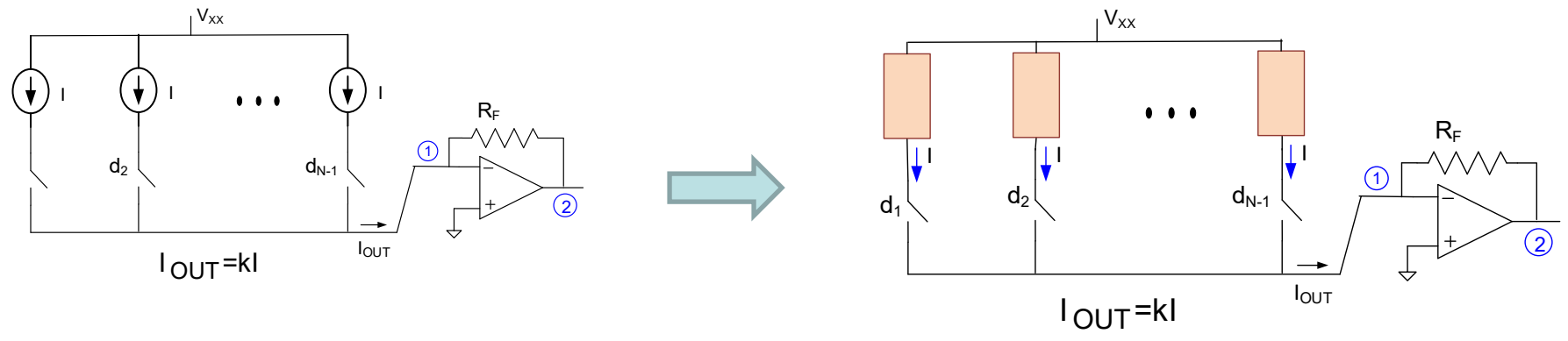


# EE 435


## Lecture 35

- Current Steering DACs
- Charge Redistribution Circuits
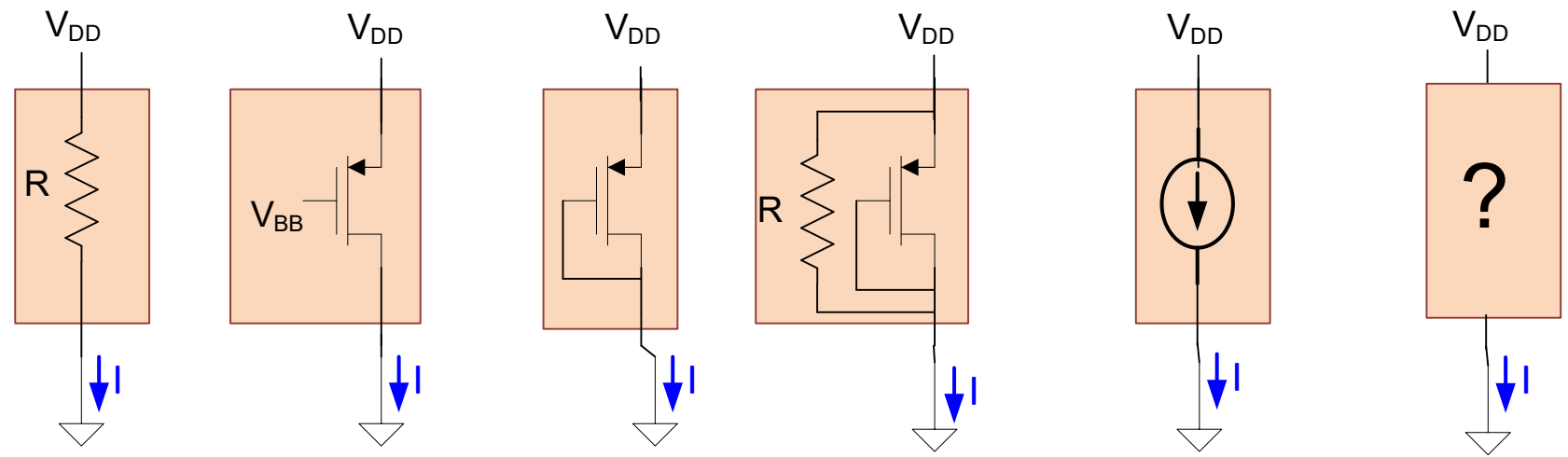
# Current Steering DACs




What is important is the current generated, not whether it comes from a “current source”



Many potential current generator blocks, just require that all be ideally identical

## Another R-2R DAC

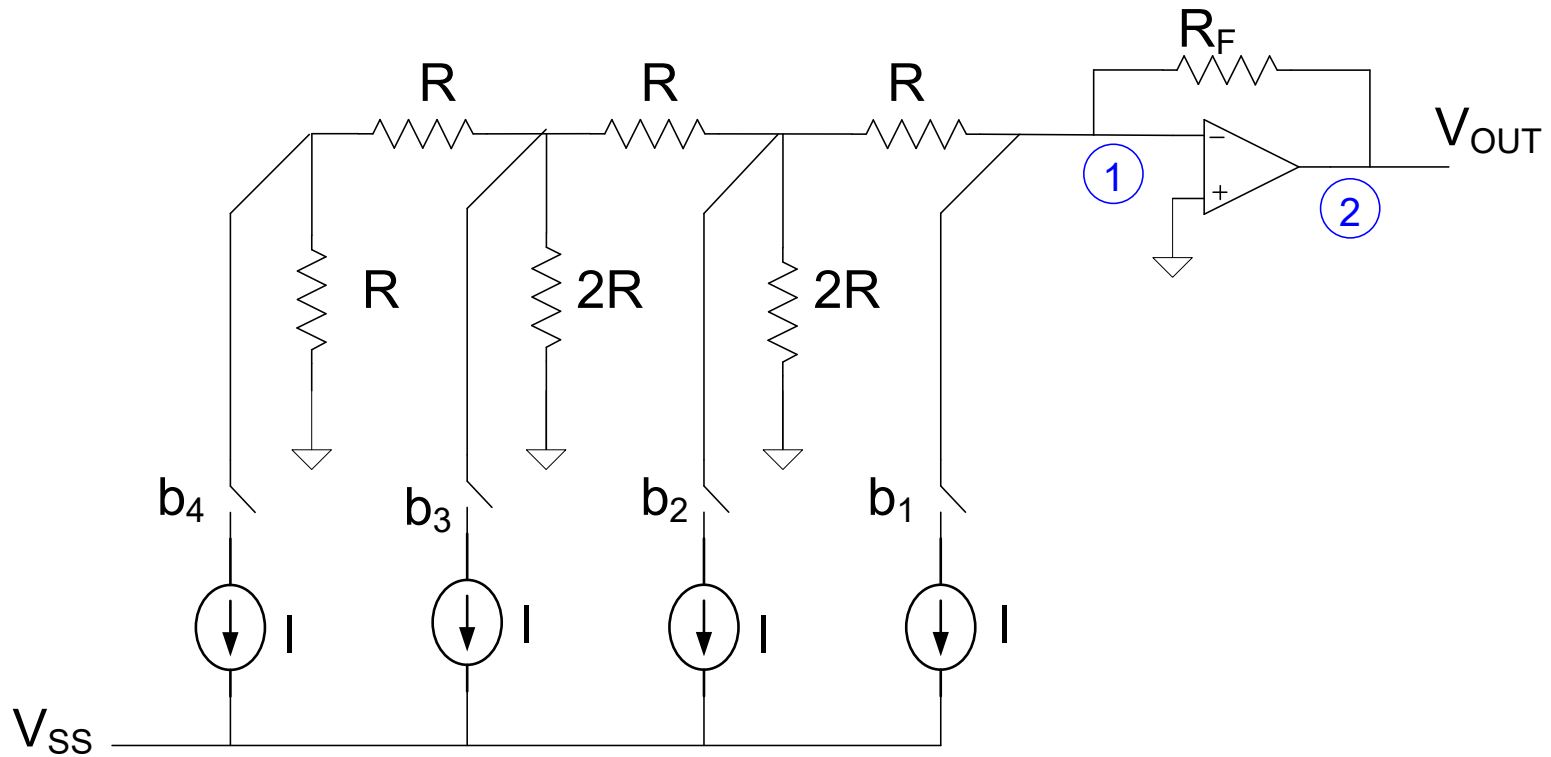

Requires matching both current sources and resistors


But switch impedance does not affect performance

$\beta$  is independent of Boolean code

Node voltages in R/2R block must change for any input transitions

Review from Last Lecture

# Another R-2R DAC

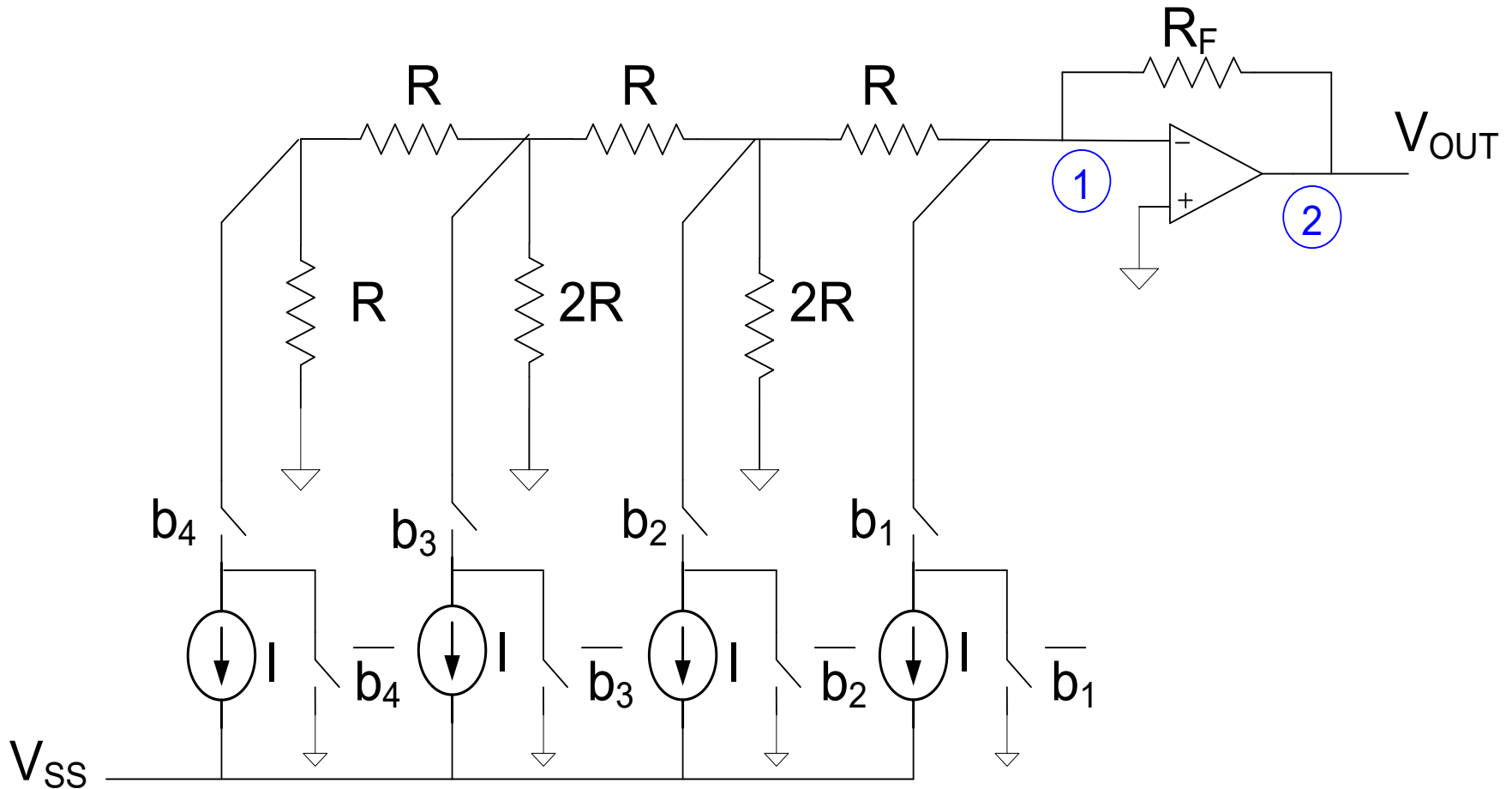


Clocks must be nonoverlapping

Does this offer any benefits over previous approach ?

Offers some compensation for capacitances on current sources

Are there other terminations for the current sources?

# R-2R DACs

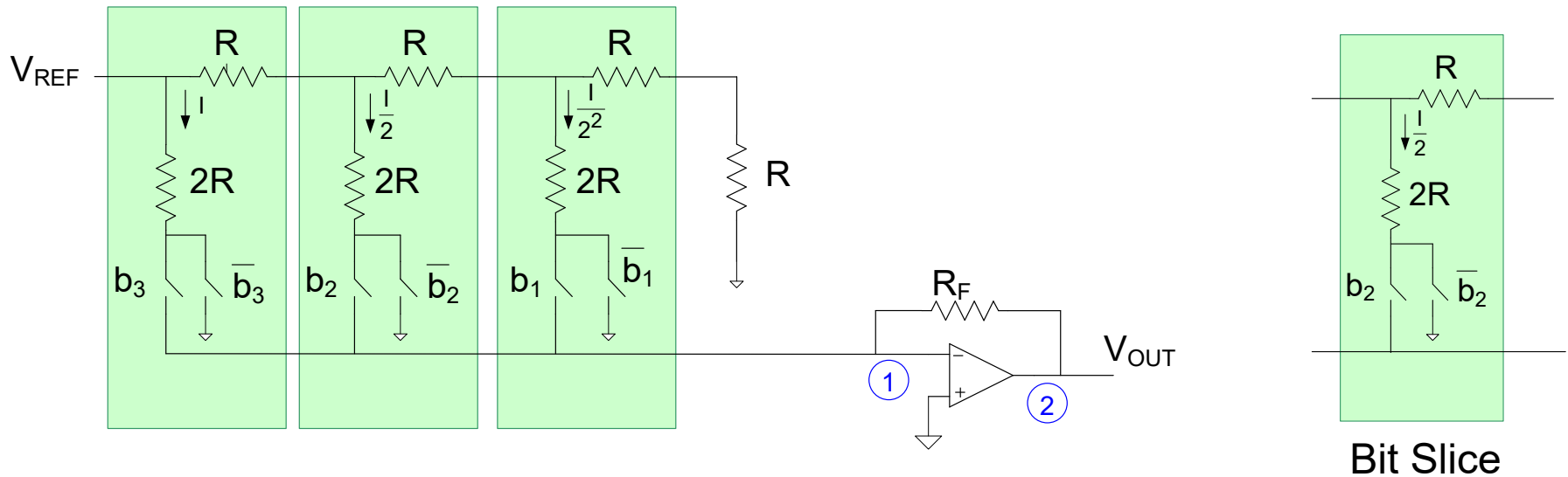



## Key characteristic of R-2R Structures

- Area increases linearly with number of bits of resolution
- Binary to thermometer/bubble converter eliminated
- Simple unary cell can be used for R elements
- Common-centroid layout manageable ??

## Key challenges of R-2R Structures


- Switches directly affect R-2R values and ratios
- Voltage on internal nodes must settle for some structures
- If unary cell used, area not optimally allocated for matching

# Current Steering DAC

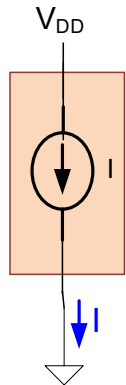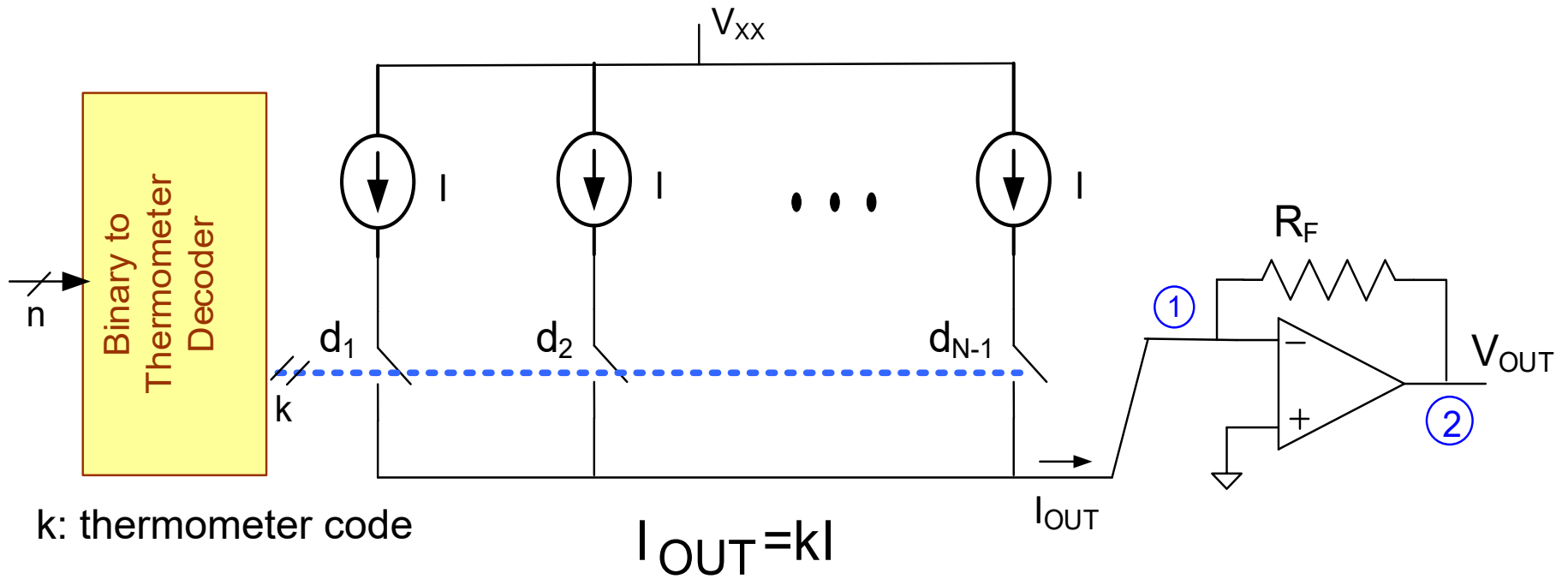


Switch impedance of little concern if current sources ideal

# Current Steering DAC

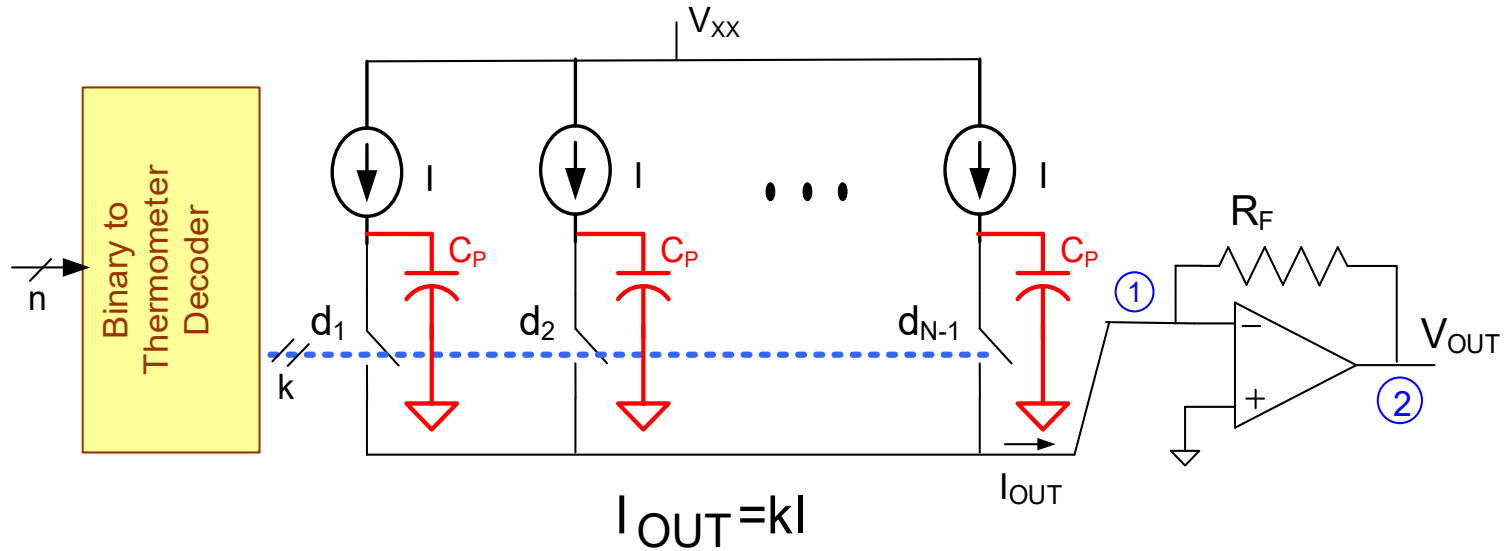

Critical parasitic capacitors in current-steering DAC


# Current Steering DAC

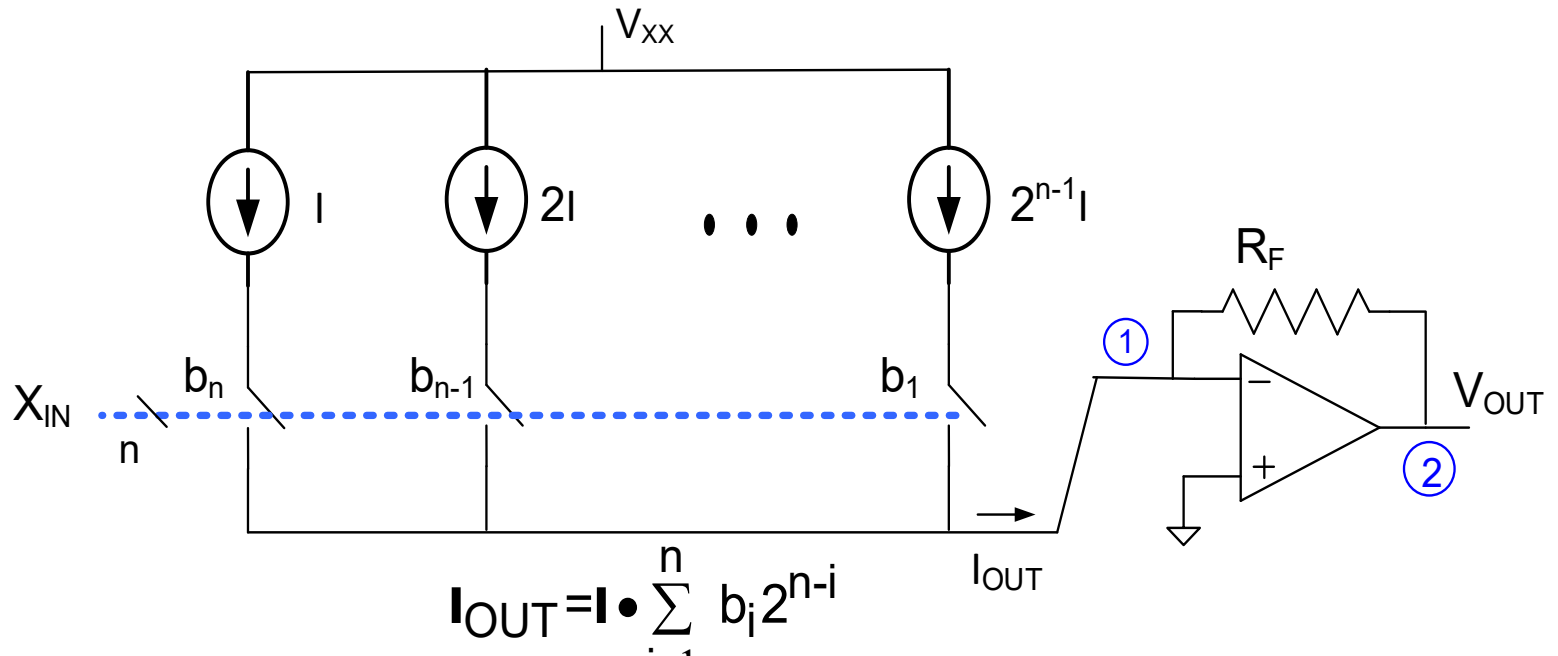

- Binary to thermometer decoder eliminated
- Current sources bundled unary cells
- Bundles large for large  $n$




# Current Steering DAC

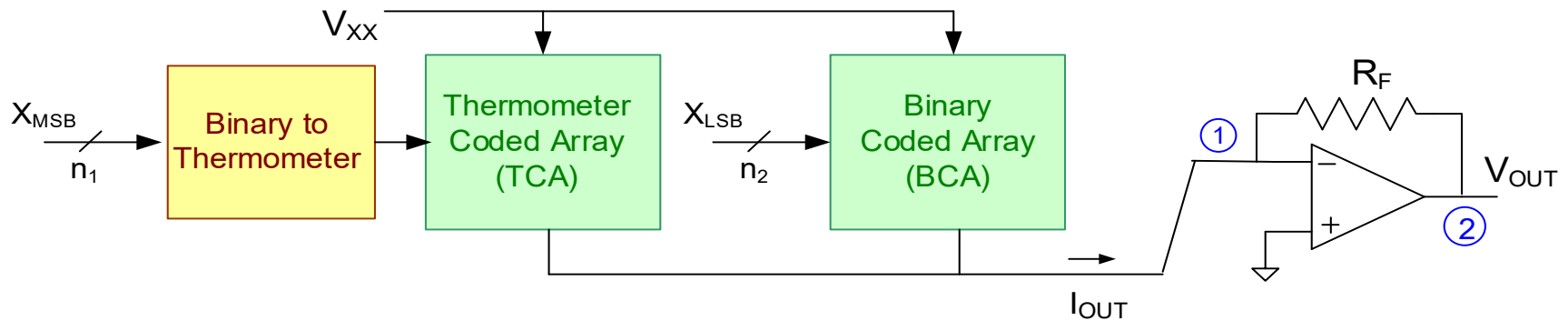



Segmented Structure

- Exploits benefits of both thermometer and binary coded structures
- Common-centroid layout likely only necessary on TCA
- Dramatic reduction in complexity of decoder possible

# Current Steering DAC

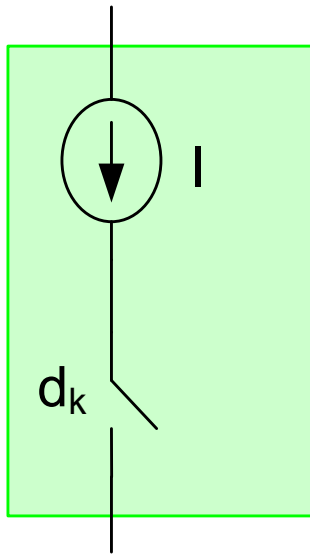




*popular current source* →

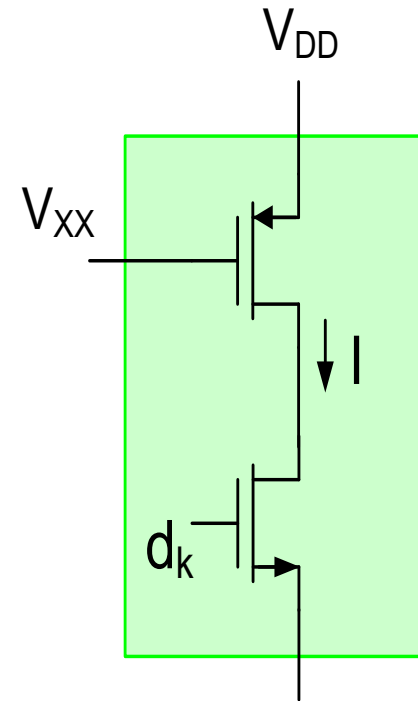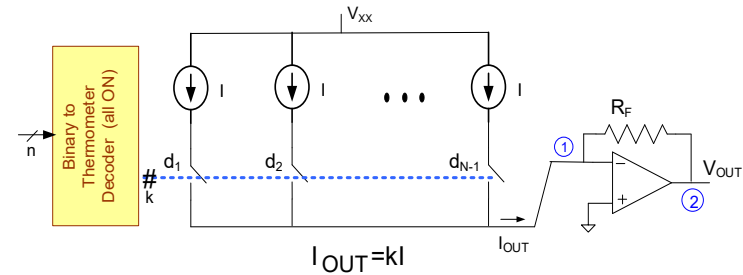

Is linearity or output impedance of current source of concern?



Not if individual slices are matched !

# Current Steering DAC

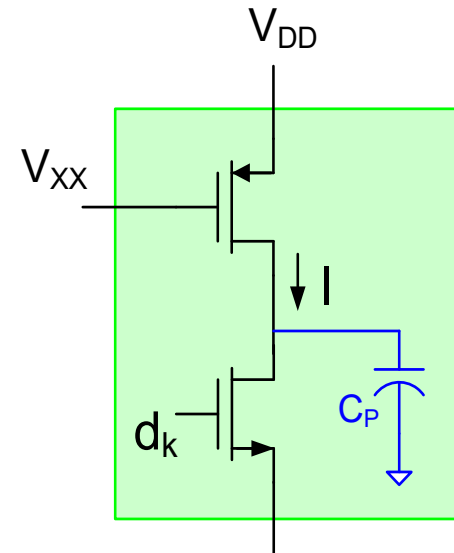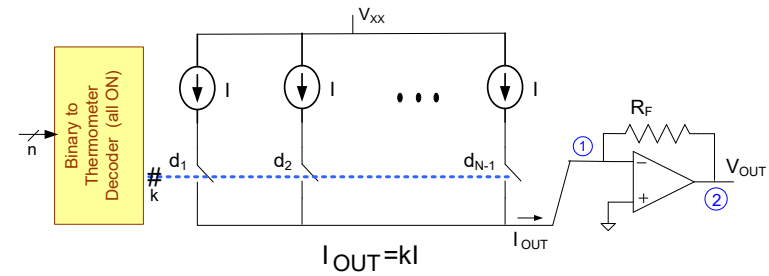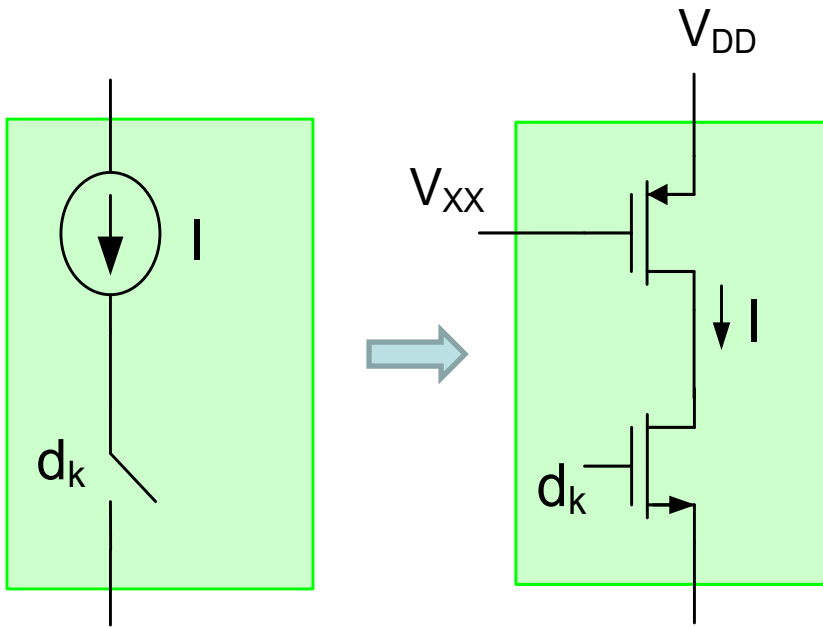


Parasitic capacitance on output of current source problematic

# Current Steering DAC

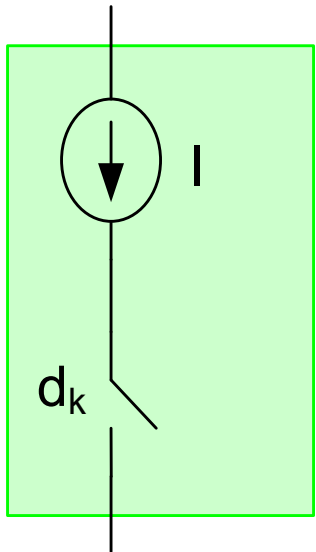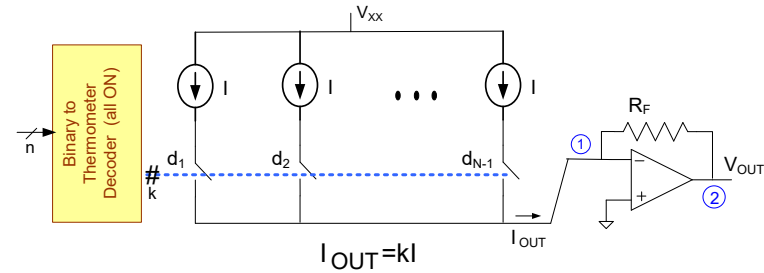



## Alternative current source cells

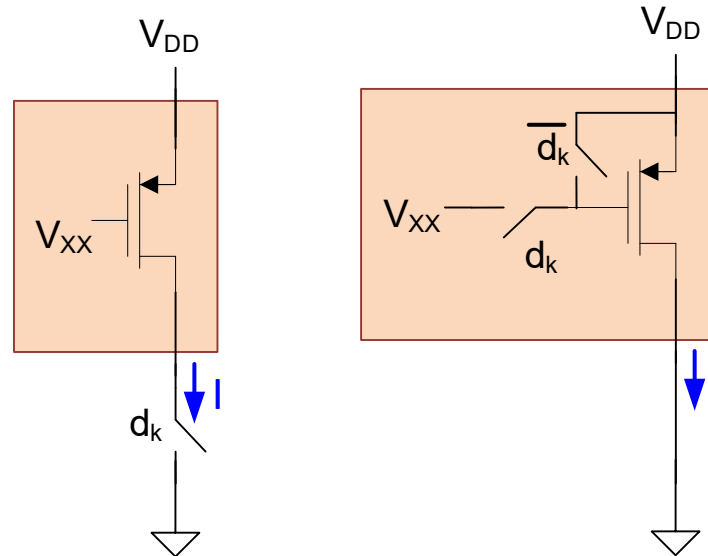

Which is better?

Effects of parasitic diffusion capacitance?  
Effects of gate capacitance?

# Current Steering DAC

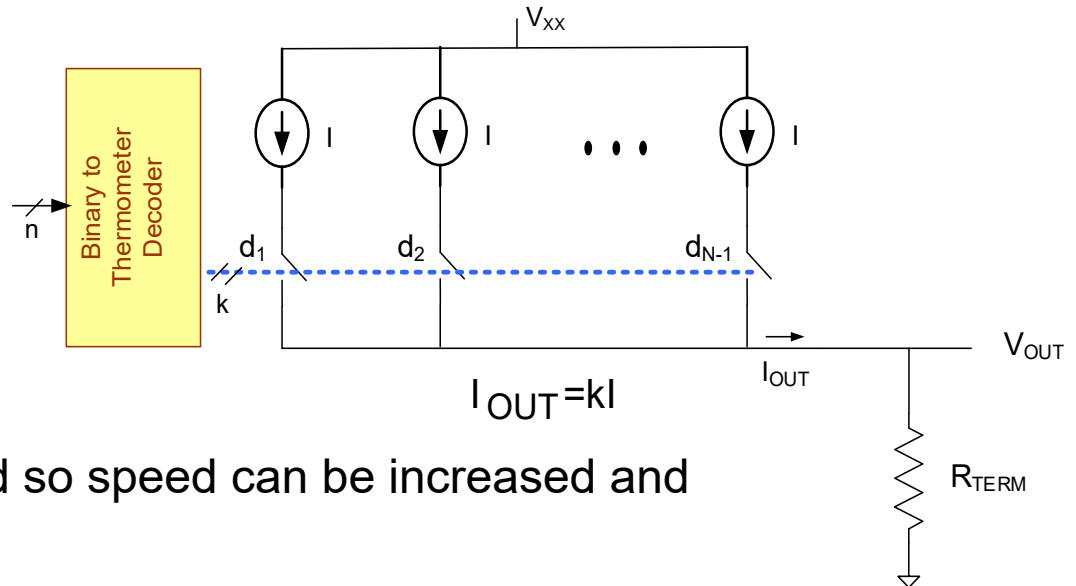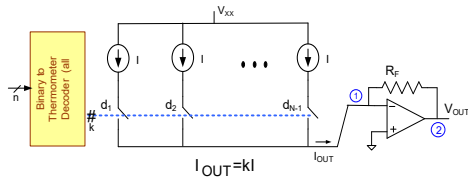

Op Amp can be eliminated so speed can be increased and power reduced





$R_{TERM}$  often 50 $\Omega$  or 100 $\Omega$

$R_{TERM}$  can be internal or external

Switch impedance now of concern





Output impedance of current sources now of concern

# Current Steering DAC

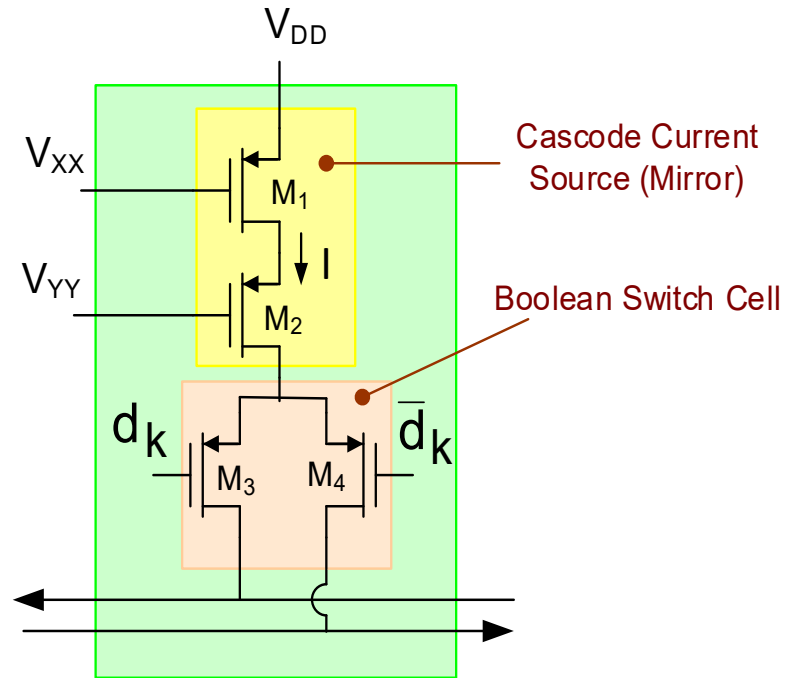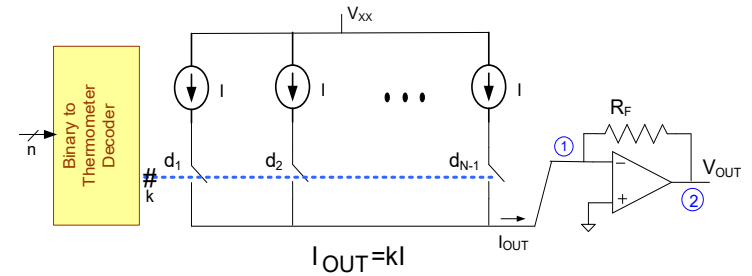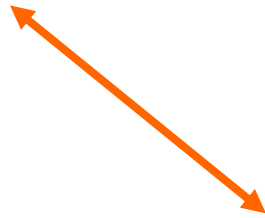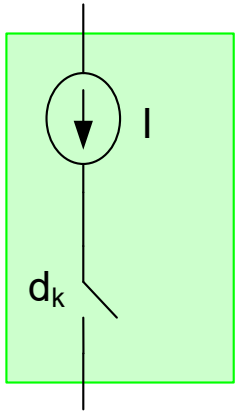






Cascodeing reduces output conductance of current source  
 No power penalty, slight reduction in overhead

# Current Steering DAC

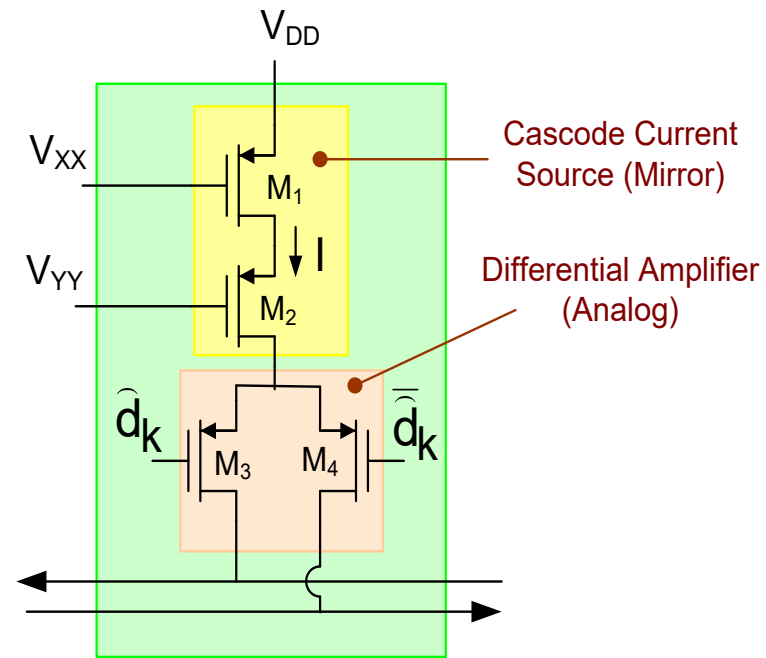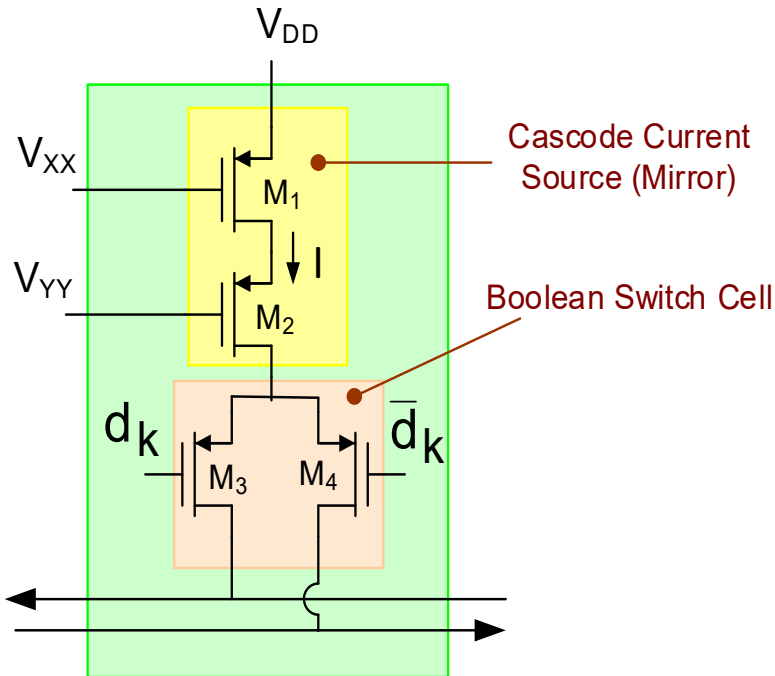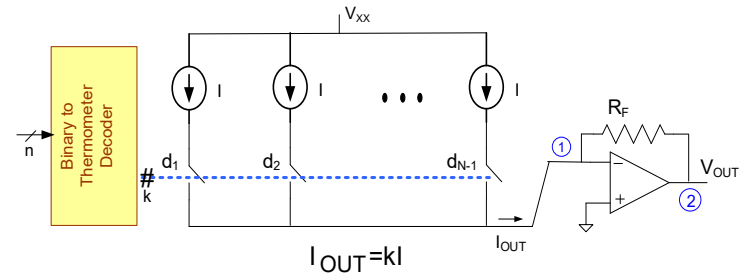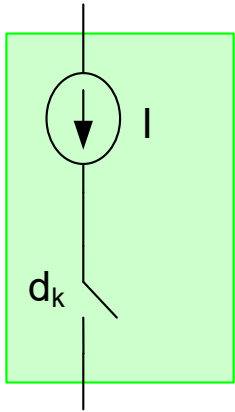





Steer rather than switch current  
Reduced swing on control signals

# Current Steering DAC

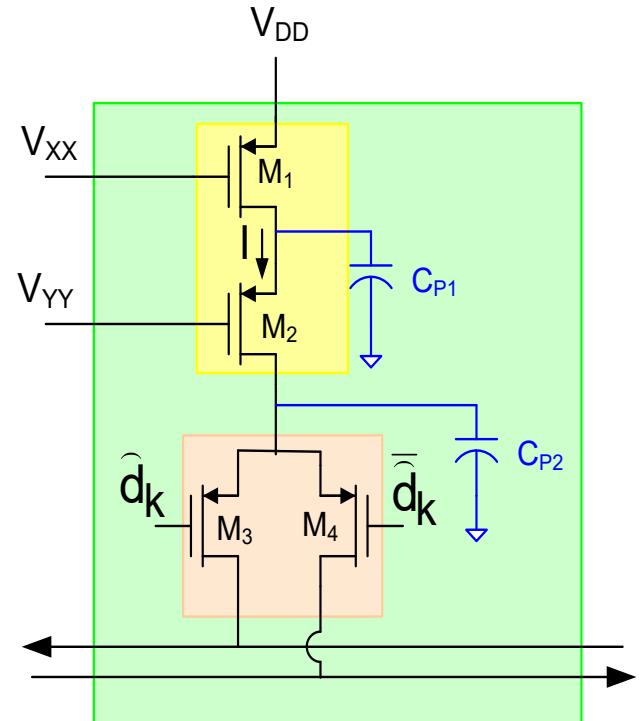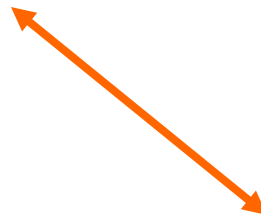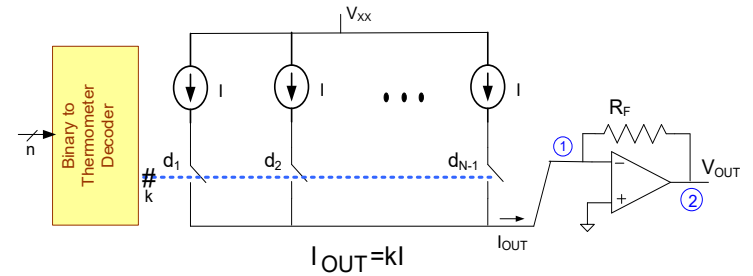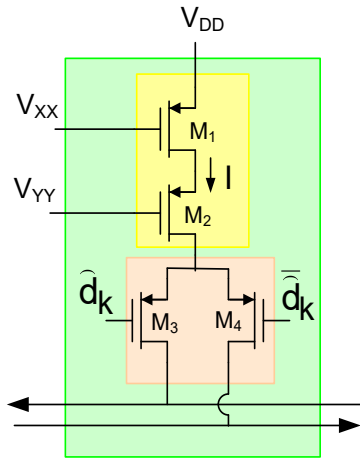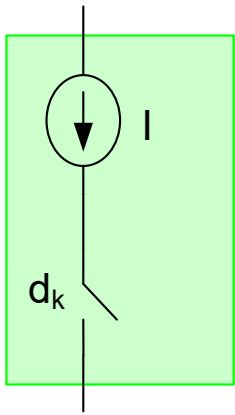





# Current Steering DAC

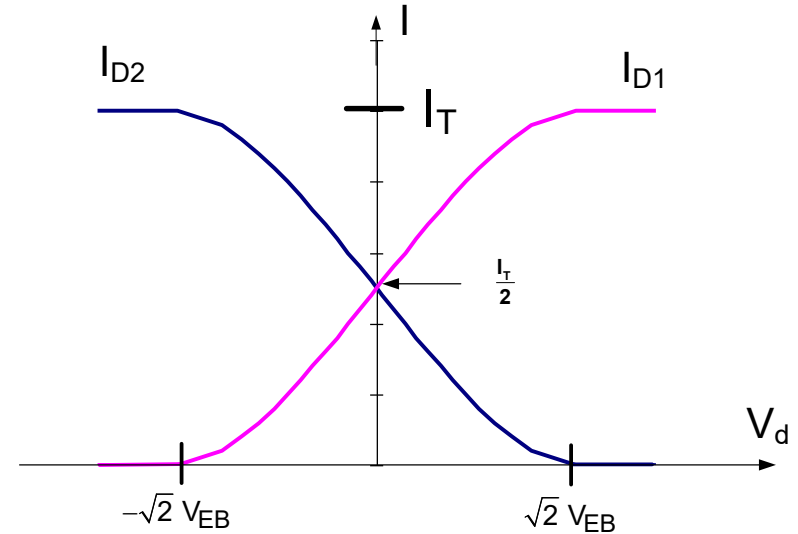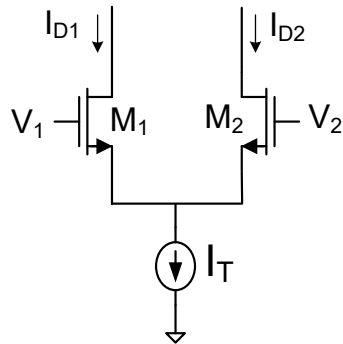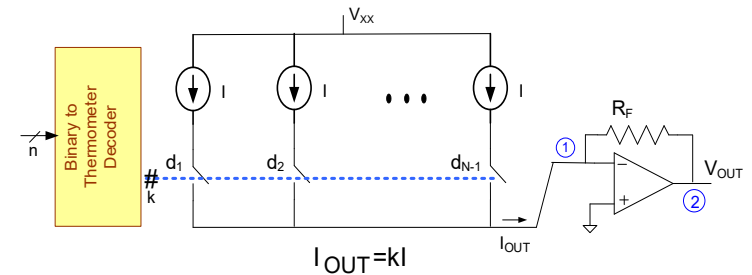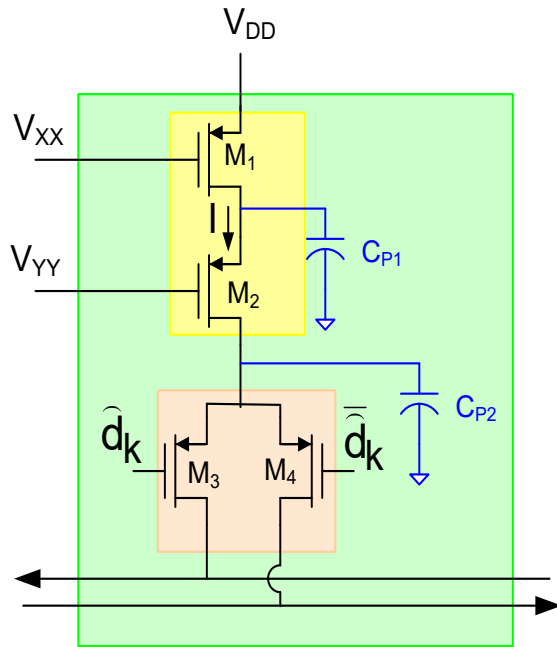


- Need only signal swing of  $2\sqrt{2}V_{EB}$  to steer currents (so can reduce turn-on and turn-off times)
- Steering also results in cascoding with  $M_3$  and  $M_4$  thus increasing output impedance of current source (so can probably eliminate  $M_2$ )


# Current Steering DAC

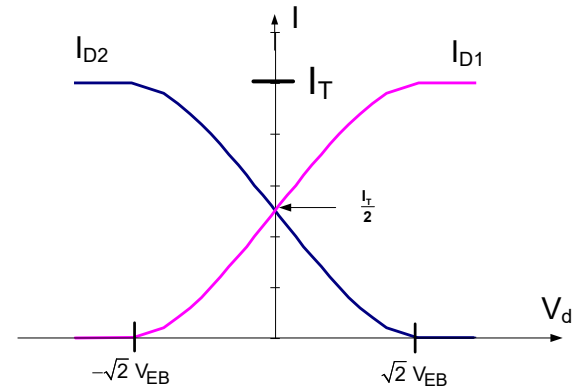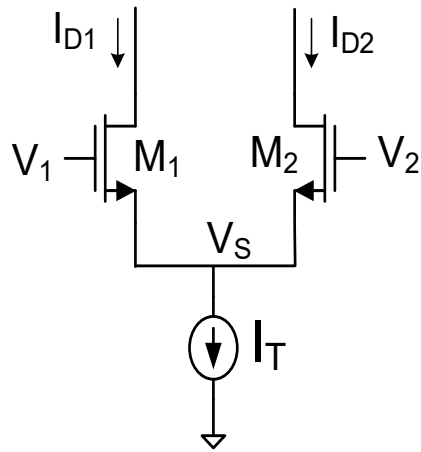

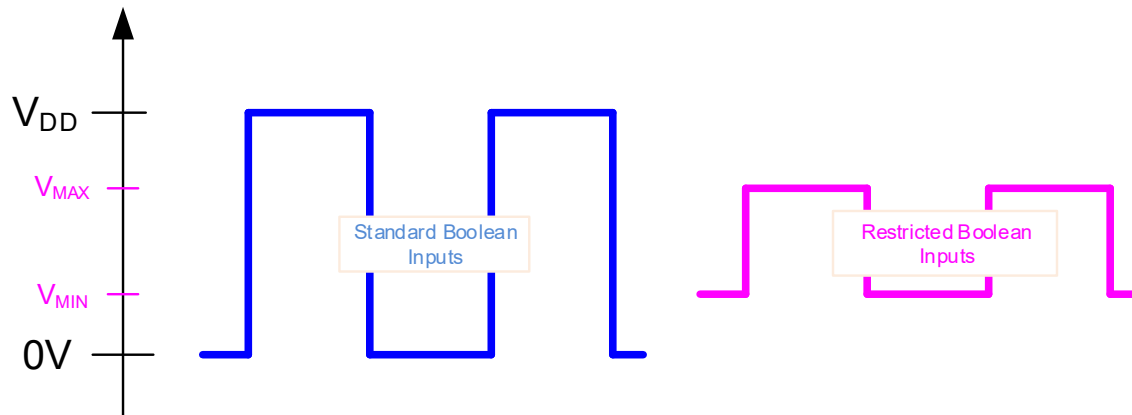
Reduced Signal Swing on  $V_S$  Node with Current Steering





# Current Steering DAC

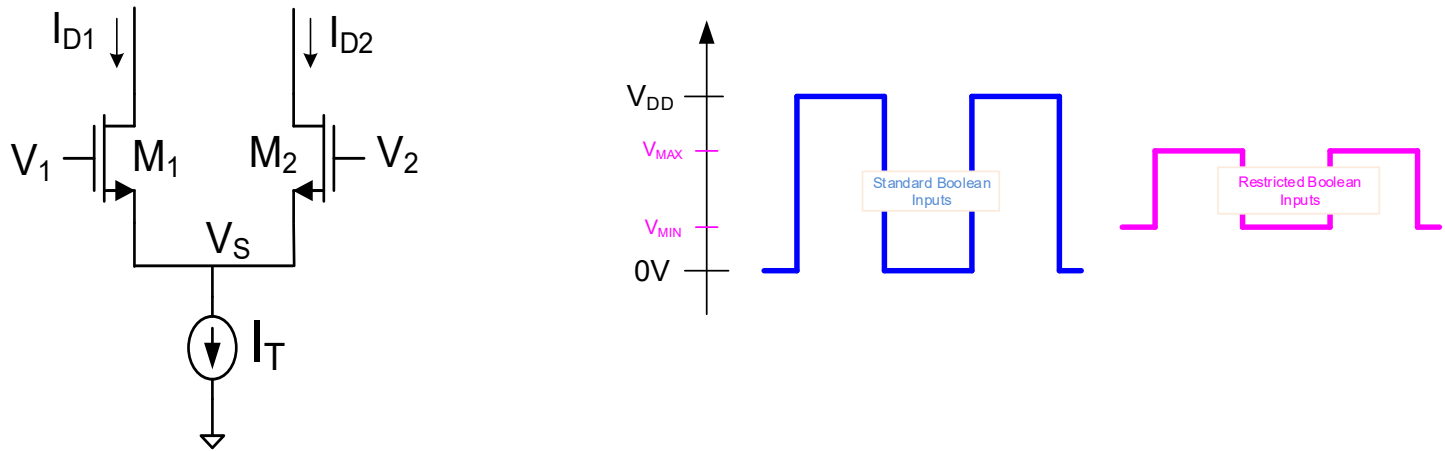

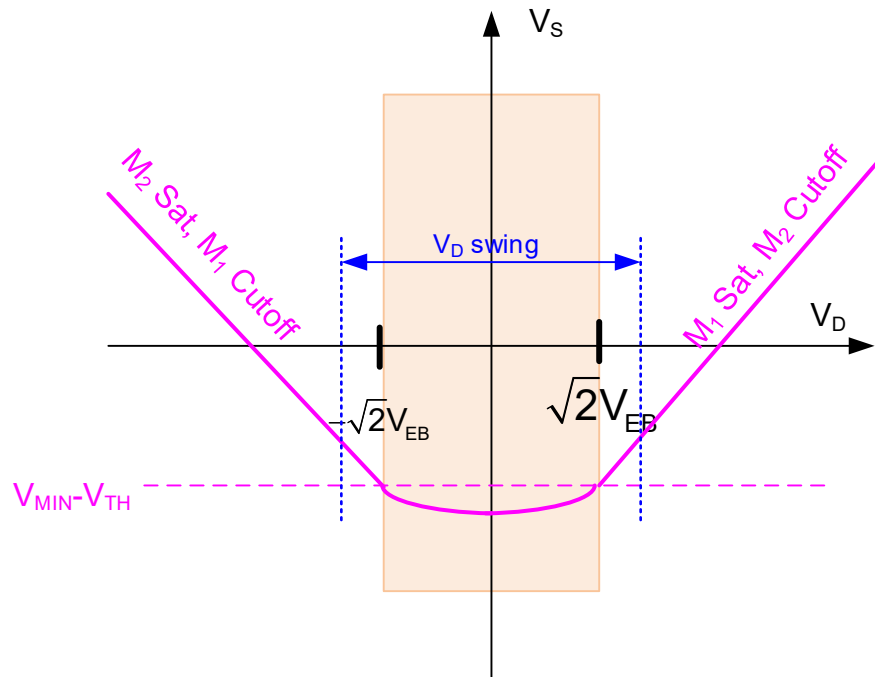Reduced Signal Swing on  $V_S$  Node with Current Steering




# Current Steering DAC

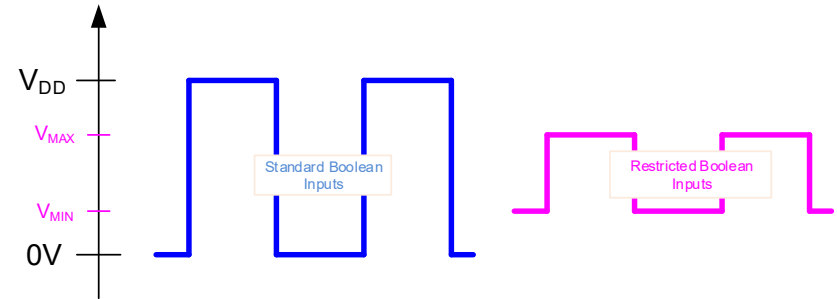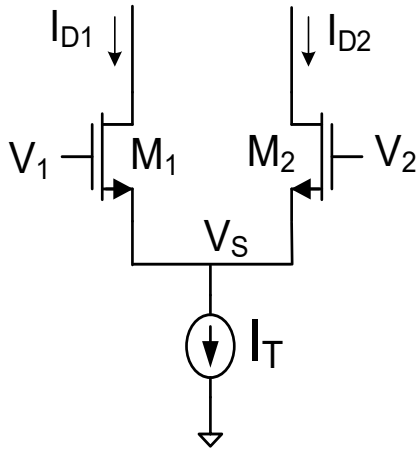


Reduced Signal Swing on  $V_S$  Node with Current Steering

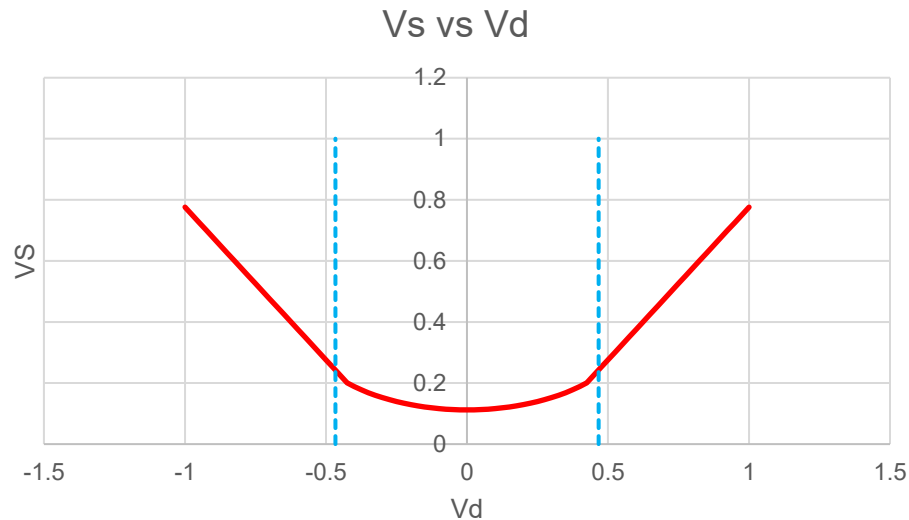Simulation Results:  $V_{TH}=0.4V$ ,  $V_{MIN}=0.6V$ ,  $V_{MAX}=1.07V$ ,  $V_{EB}=0.3V$ ,  $\gamma=1.1$




$V_S$  swing about 100mV
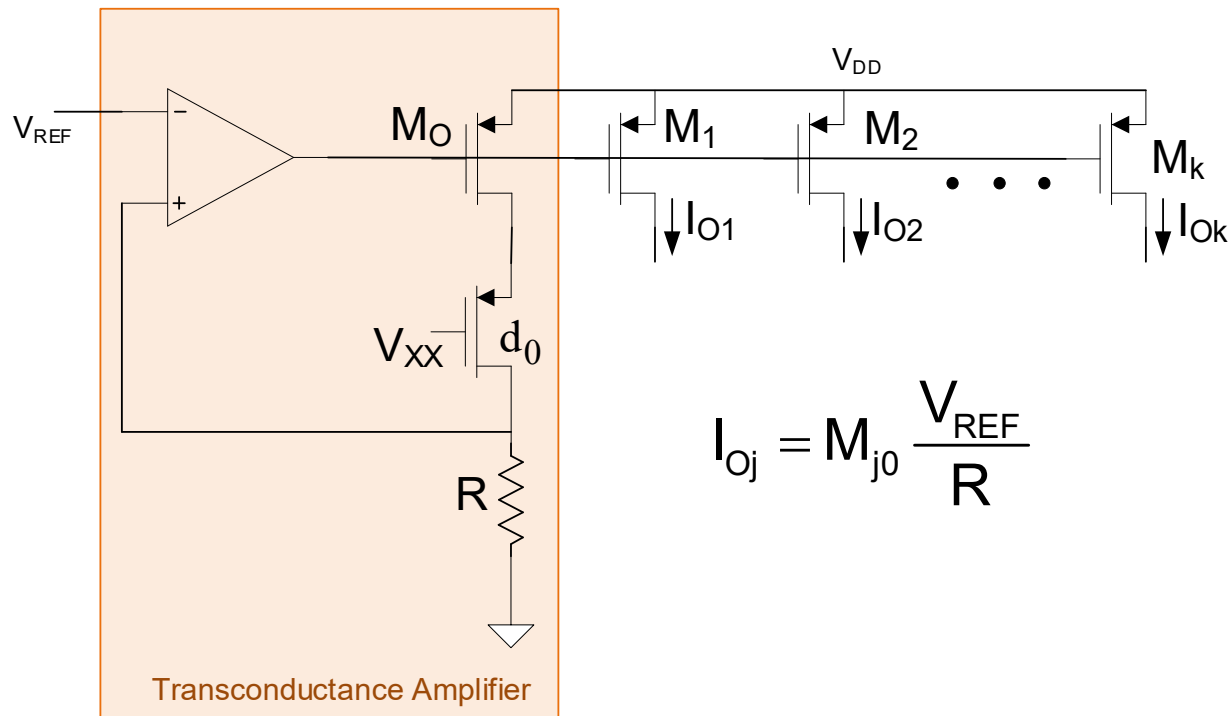
# Multiple-output Transconductance Amplifier



- Good linearity
- Each additional output requires only one additional transistor
- Relevant is MDAC output desired
- Cascoding of output devices useful if driving resistive load
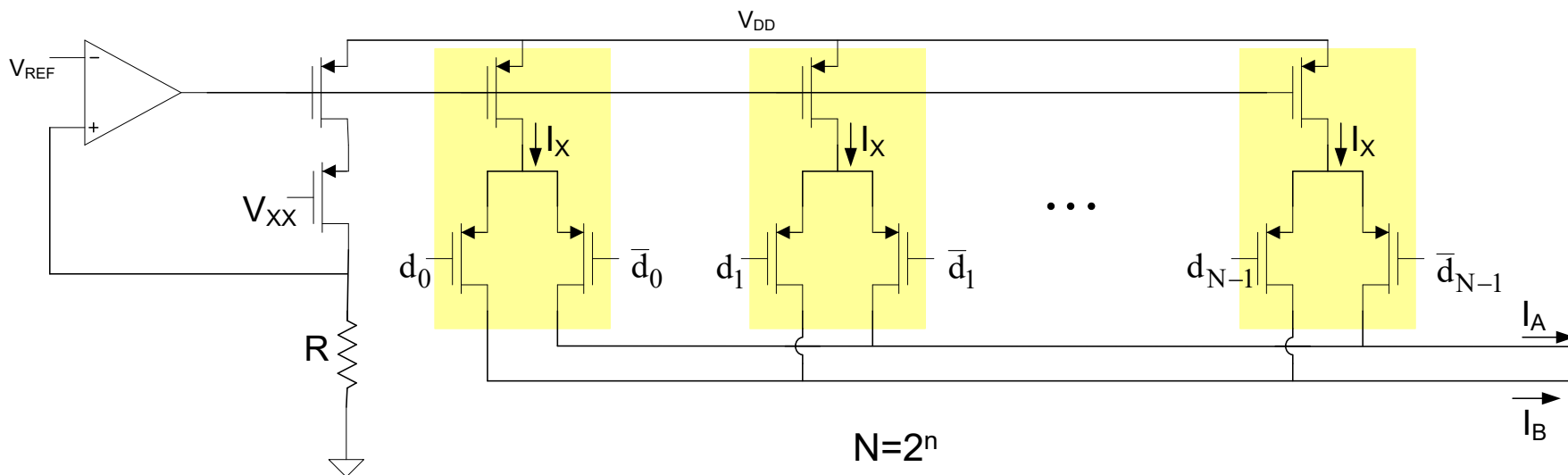
# Current Steering DAC with Supply Independent Biasing




If transistors on top row are all matched,  $I_X = V_{REF}/R$

Thermometer coded structure (requires binary to thermometer decoder)

$$I_A = \left( \frac{V_{REF}}{R} \right) \sum_{i=0}^{N-1} d_i$$

Provides Differential Output Currents
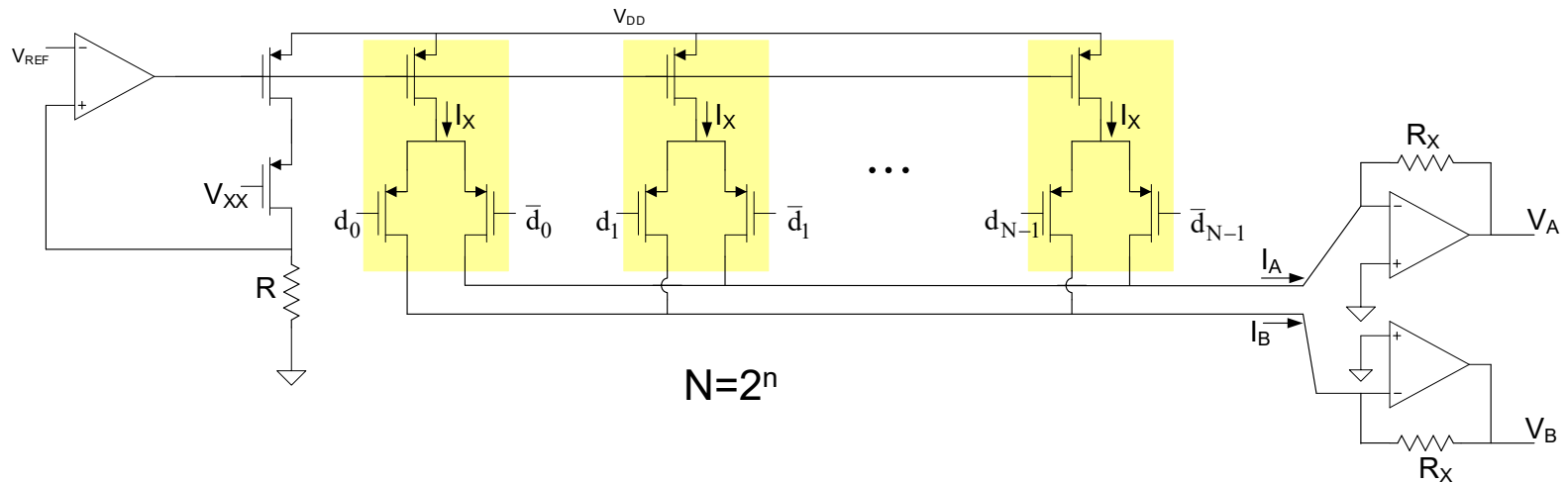
# Current Steering DAC with Supply Independent Biasing




If transistors on top row are all matched,  $I_X = V_{REF}/R$

$$V_A = \left( -V_{REF} \frac{R_A}{R} \right) \sum_{i=0}^{N-1} d_i$$

Provides Differential Output Voltages
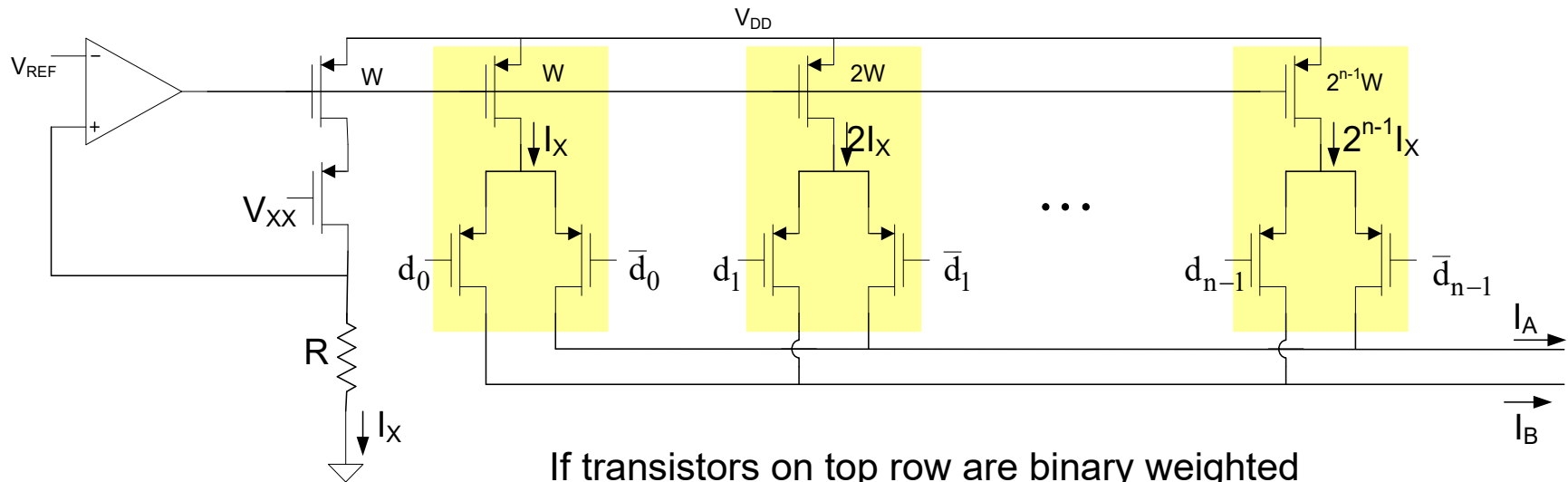
# Current Current Steering DAC with Supply Independent Biasing



If transistors on top row are binary weighted

$$I_A = \left( \frac{V_{REF}}{R} \right) \sum_{i=0}^{n-1} d_i 2^i$$

Provides Differential Output Currents





Usually use bundled unary cells

Can use current steering rather than current switching

(switched LSB:MSB notation)



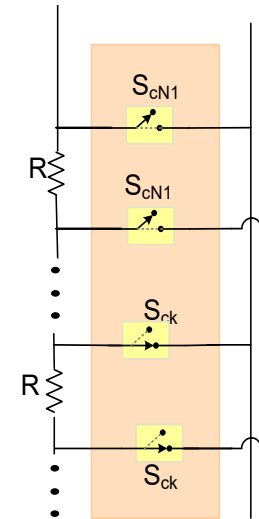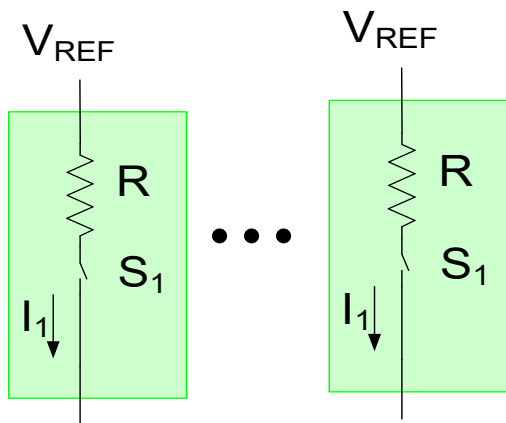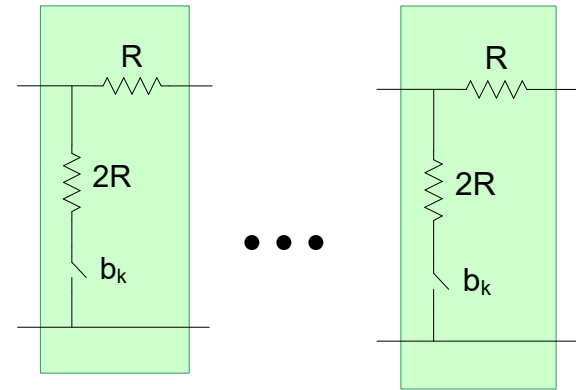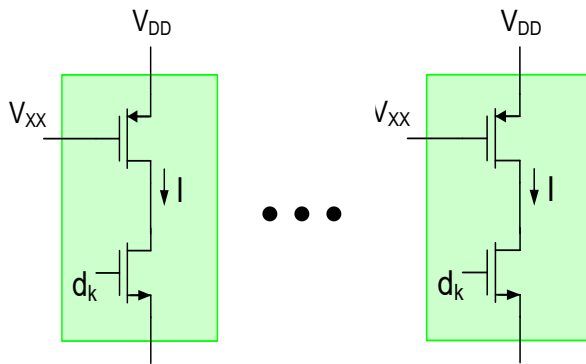
# Matching is Critical in all DAC Considered



Obtaining adequate matching remains one of the major challenges facing the designer!


# Dynamic Current Source Matching

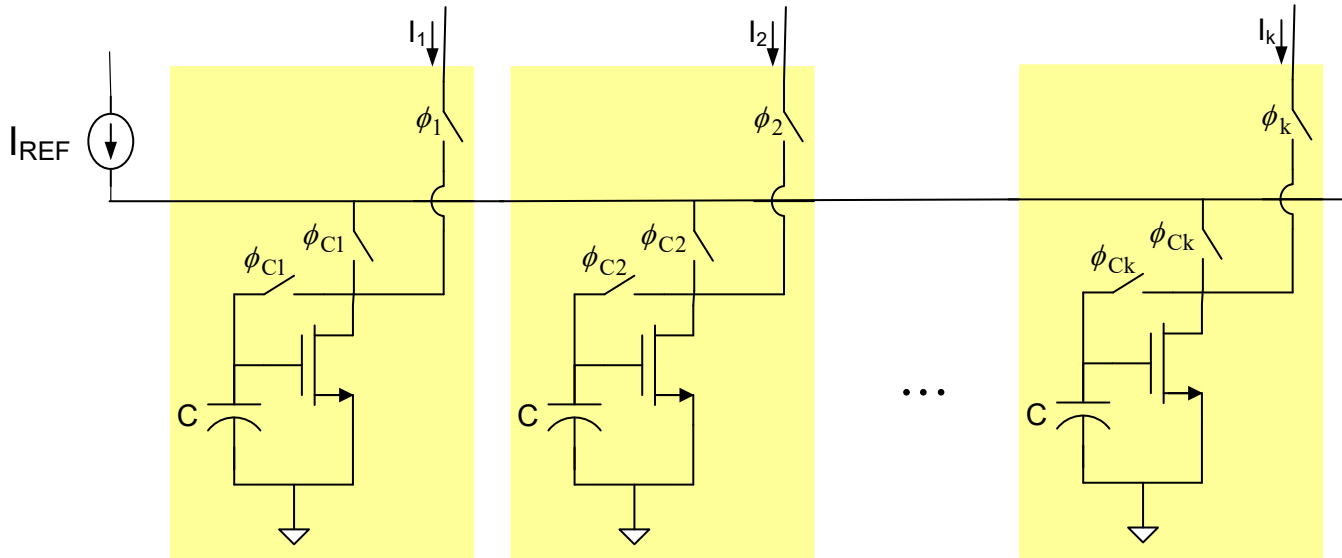

- $\phi_1, \dots, \phi_k, \dots, \phi_n$  distinct from  $d_1, \dots, d_n$  (not shown)
- Correct charge is stored on  $C$  to make all currents equal to  $I_{REF}$
- Does not require matching of transistors or capacitors
- Requires refreshing to keep charge on  $C$
- Form of self-calibration
- Calibrates current sources one at a time
- Current source unavailable for use while calibrating
- Can be directly used in DACs (thermometer or binary coded)

Often termed “Current Copier” or “Current Replication” circuit

# Dynamic Current Source Matching

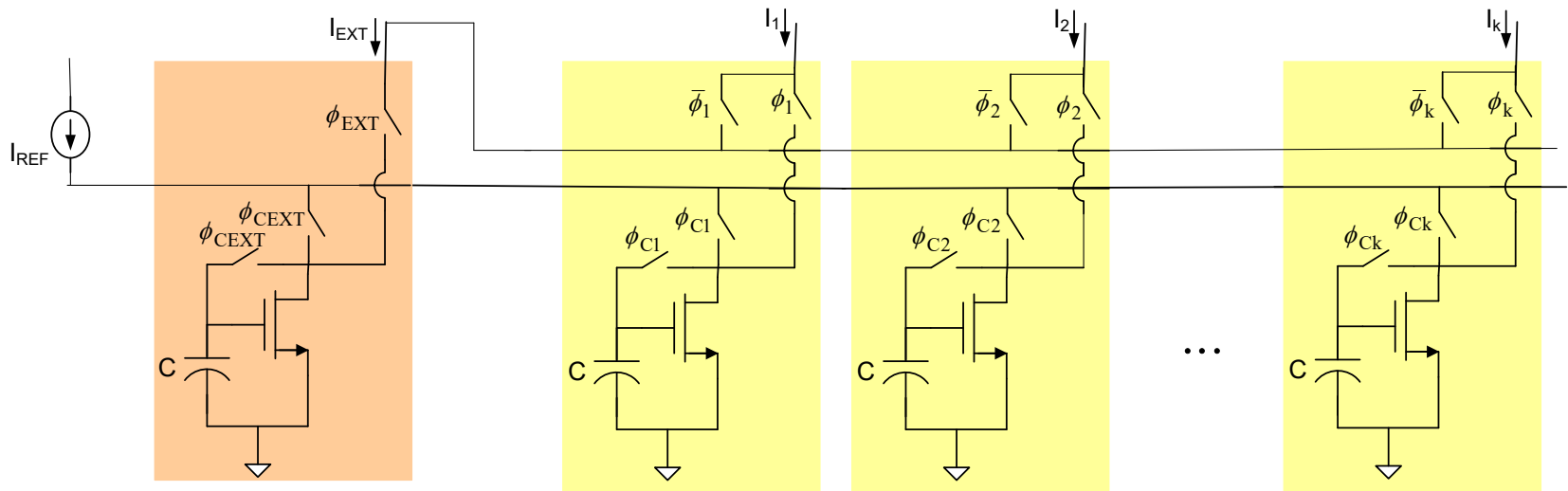

Extra current source can be added to facilitate background calibration



Stay Safe and Stay Healthy !

End of Lecture 35