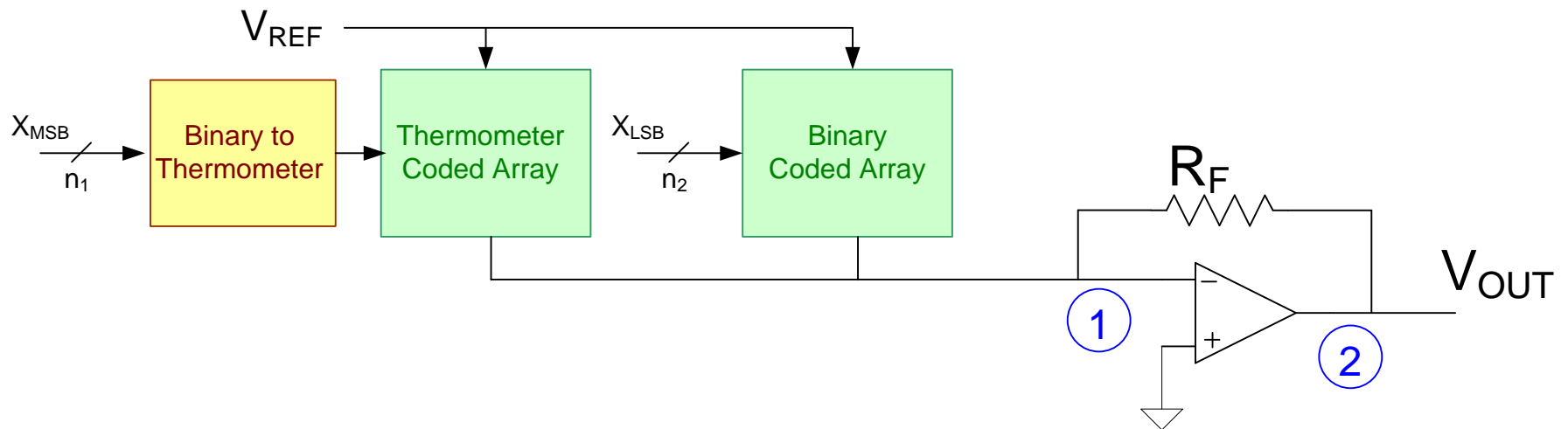


EE 435

Lecture 35

Dynamic Current Source Matching
Charge Redistribution DACs
ADC Design



Current Steering DACs



Segmented Resistor Arrays

- Combines two types of architectures
- Inherits advantages of both thermometer and binary approach
- Minimizes limitations of both thermometer and binary approach

 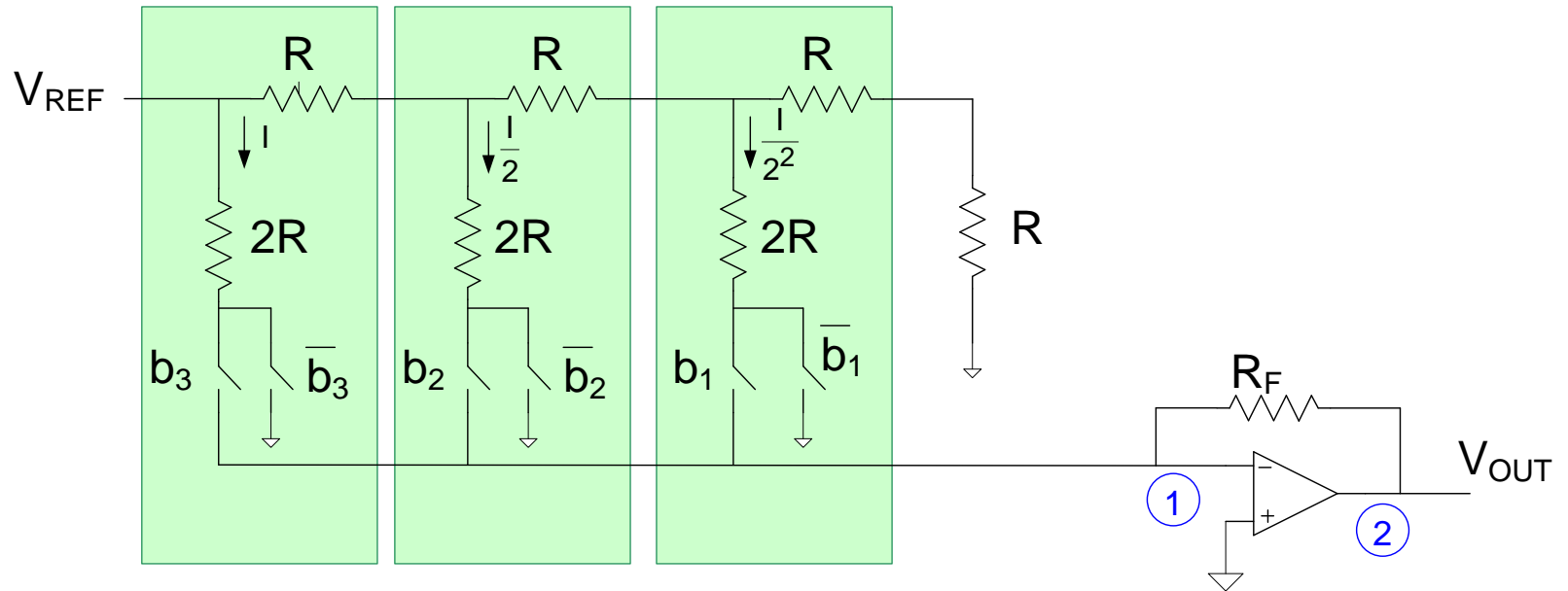
Review from Last Lecture
Current Steering DACs



R-2R Resistor Arrays

Review from Last Lecture



Current Steering DAC

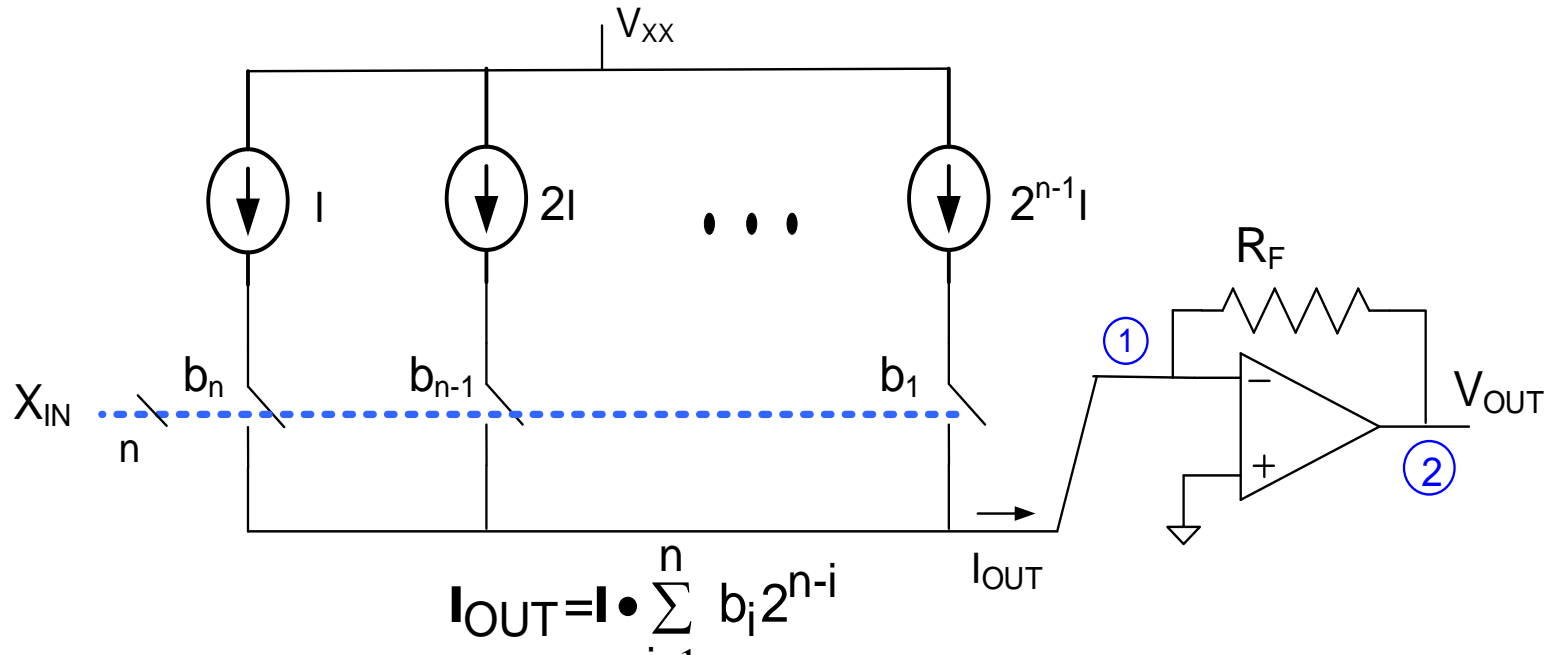

- Binary to thermometer decoder eliminated
- Current sources bundled unary cells
- Bundles large for large n

Review from Last Lecture

Current Steering DAC

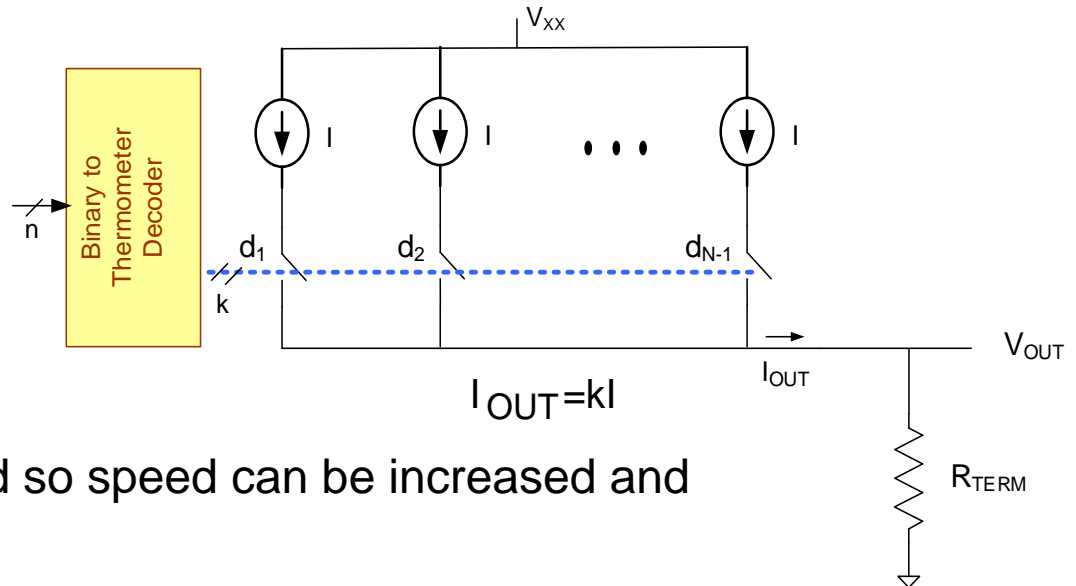 

Op Amp can be eliminated so speed can be increased and power reduced

R_{TERM} often 50 Ω or 100 Ω





R_{TERM} can be internal or external

Switch impedance now of concern

Output impedance of current sources now of concern


Review from Last Lecture

Current Steering DAC

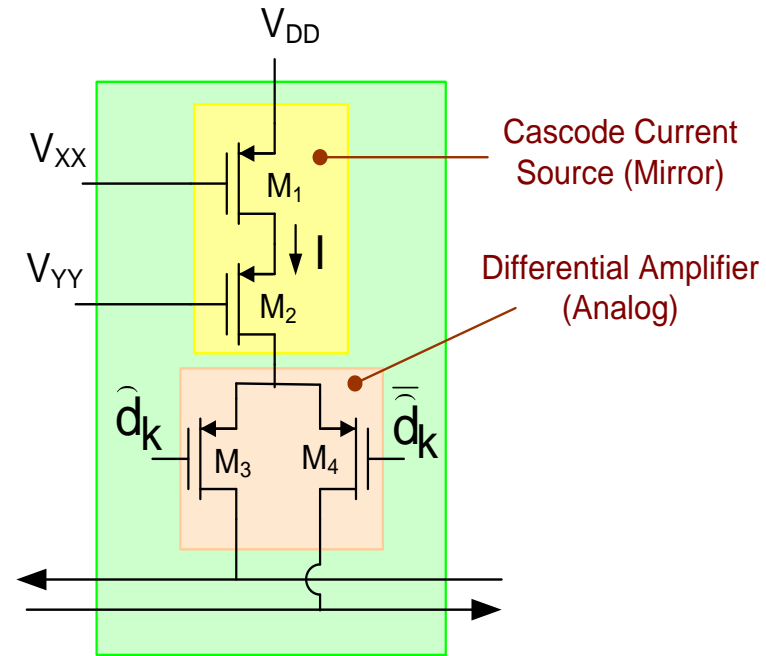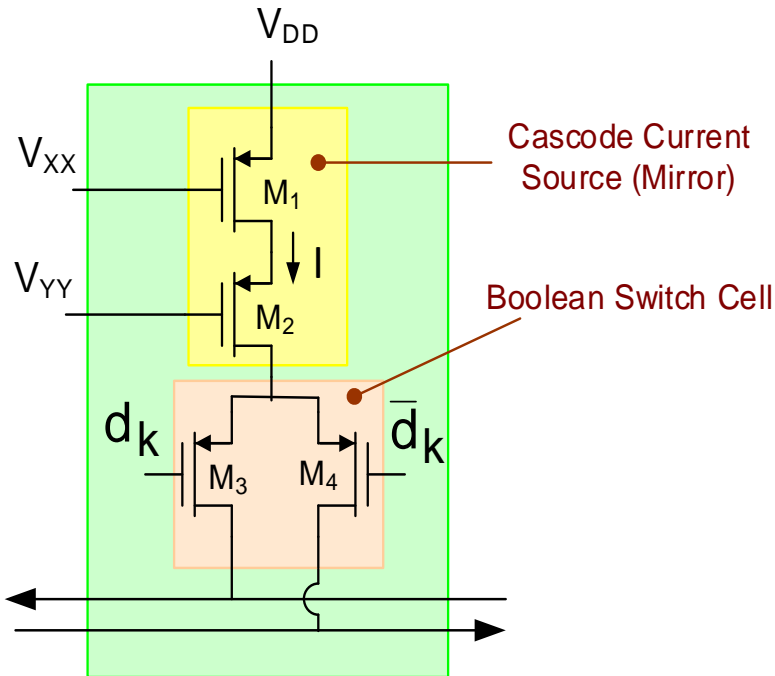  


Steer rather than switch current
Reduced swing on control signals

 Multiple-output Transconductance Amplifier



- Good linearity
- Each additional output requires only one additional transistor
- Relevant if MDAC output desired
- Cascoding of output devices useful if driving resistive load

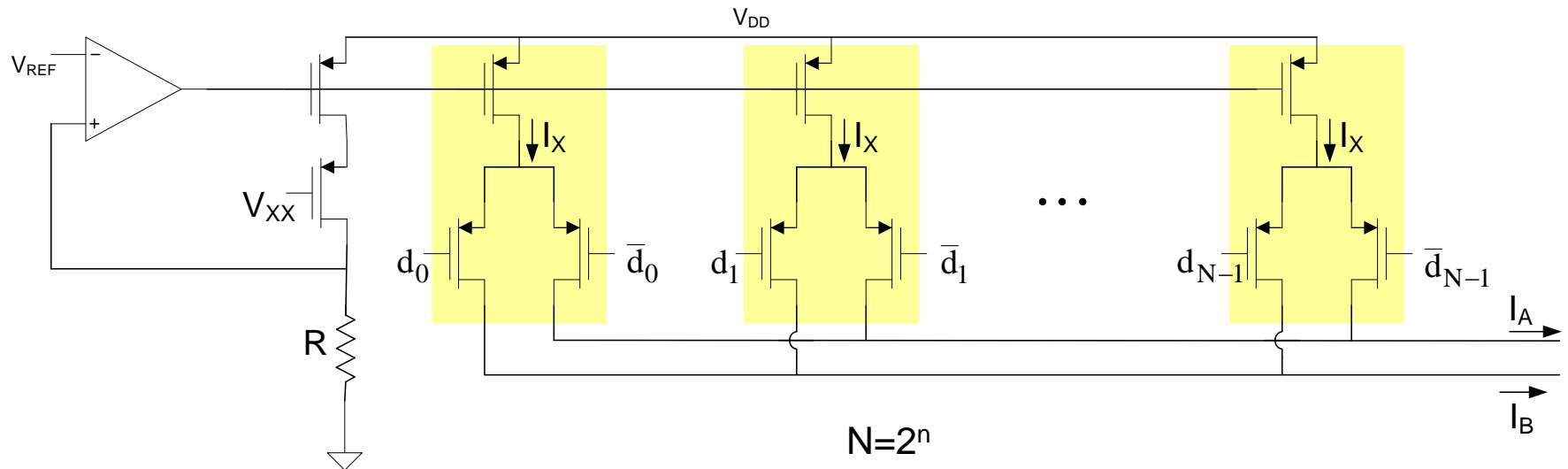Current Steering DAC with Supply Independent Biasing




If transistors on top row are all matched, $I_X = V_{REF}/R$

Thermometer coded structure (requires binary to thermometer decoder)

$$I_A = \left(\frac{V_{REF}}{R} \right) \sum_{i=0}^{N-1} d_i$$

Provides Differential Output Currents

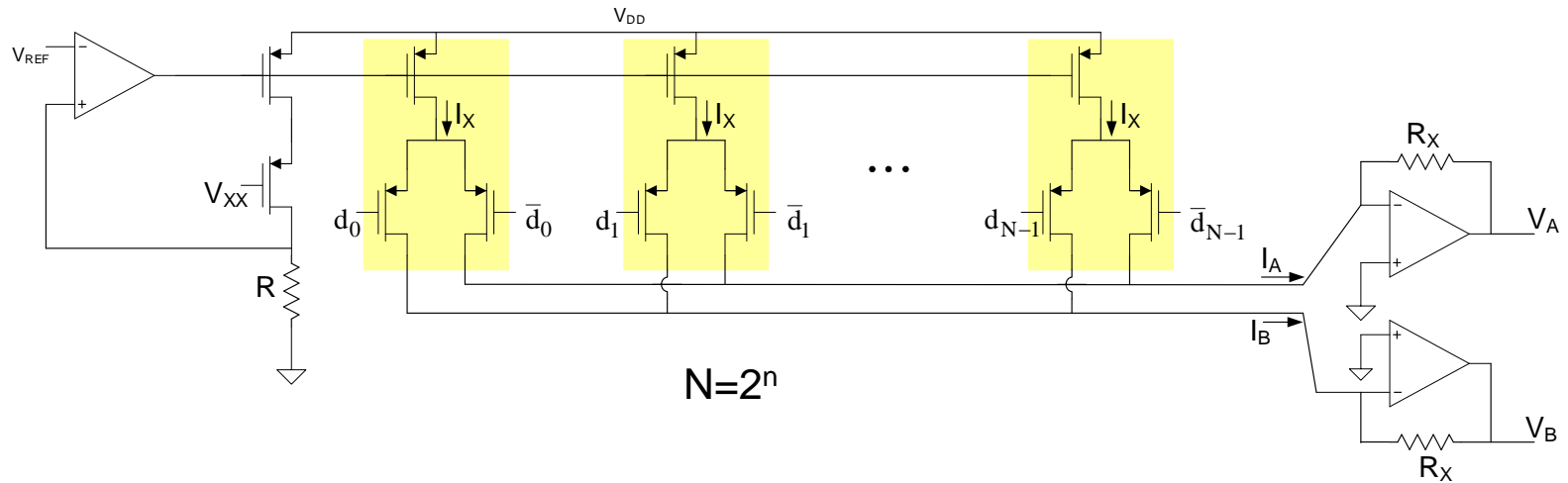Current Steering DAC with Supply Independent Biasing




If transistors on top row are all matched, $I_X = V_{REF}/R$

$$V_A = \left(-V_{REF} \frac{R_A}{R} \right) \sum_{i=0}^{N-1} d_i$$

Provides Differential Output Voltages

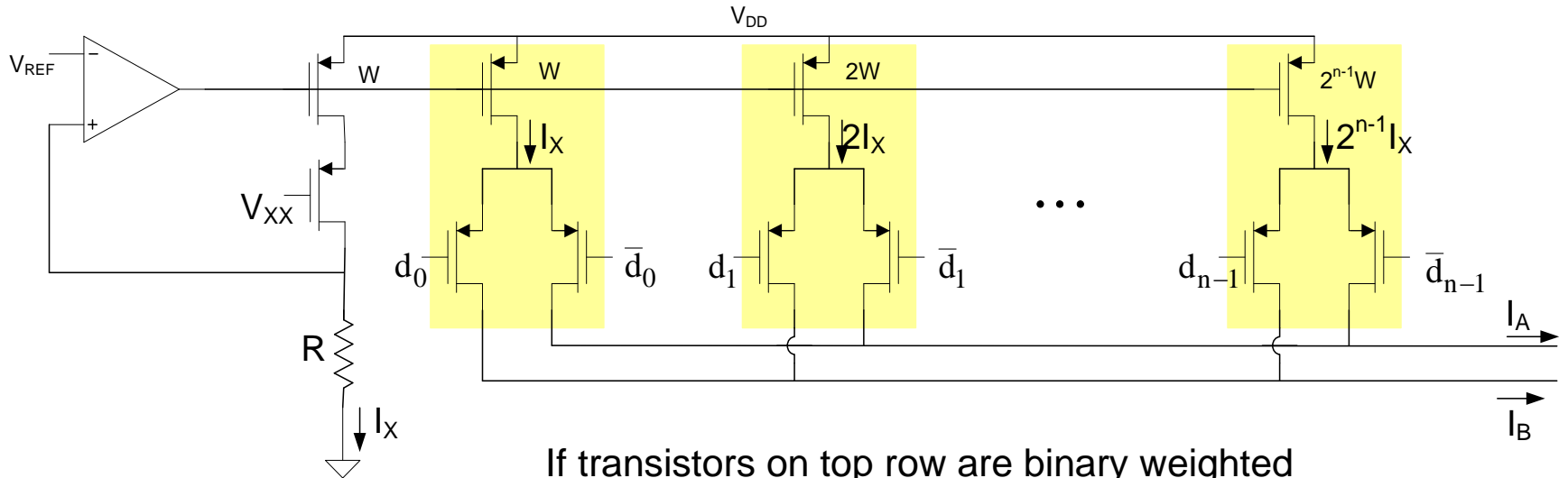Current Steering DAC with Supply Independent Biasing



If transistors on top row are binary weighted

$$I_A = \left(\frac{V_{REF}}{R} \right) \sum_{i=0}^{n-1} d_i 2^i$$





Provides Differential Output Currents

Usually use bundled unary cells

Can use current steering rather than current switching


(switched LSB:MSB notation)

    Matching is Critical in all DAC Considered



Obtaining adequate matching remains one of the major challenges facing the designer!


Dynamic Current Source Matching

 

- $\phi_1, \dots, \phi_k, \dots, \phi_n$ distinct from d_1, \dots, d_n (not shown)
- Correct charge is stored on C to make all currents equal to I_{REF}
- Does not require matching of transistors or capacitors
- Requires refreshing to keep charge on C
- Form of self-calibration
- Calibrates current sources one at a time
- Current source unavailable for use while calibrating
- Can be directly used in DACs (thermometer or binary coded)

Often termed “Current Copier” or “Current Replication” circuit

Dynamic Current Source Matching

 


Extra current source can be added to facilitate background calibration

Charge Redistribution DACs

- Previous DACs based upon matching of resistors or transistors
- Switch impedance was of concern in most of the structures
- Capacitor matching can be very good in most processes and area required for a given level of matching may be smaller for capacitors than for resistors or transistors in some processes
- Capacitor linearity is often excellent



Will now focus on building DACs that take advantage of good capacitor matching and linearity

A charge redistribution circuit

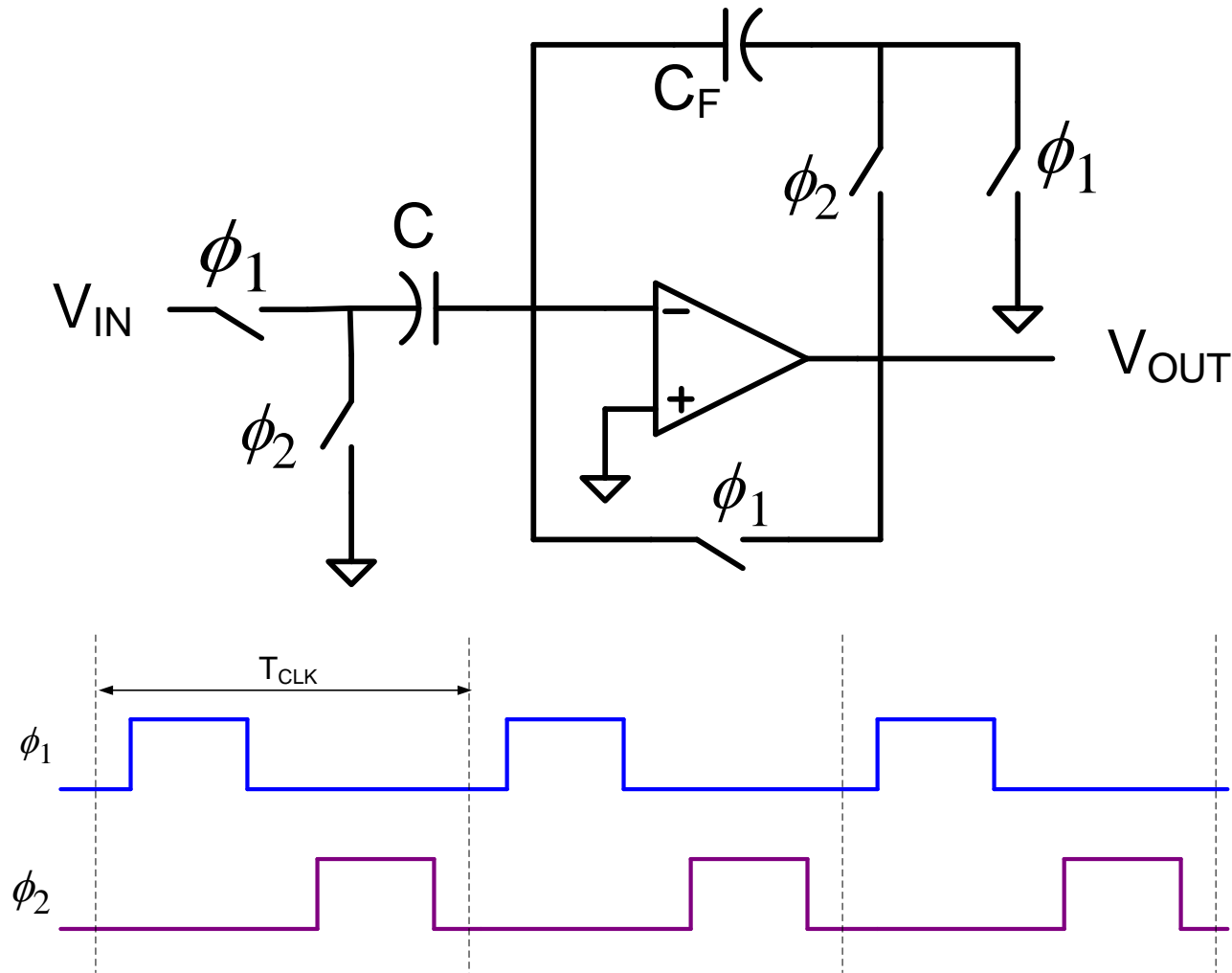

Clocks are complimentary non-overlapping

A charge redistribution circuit

  

During phase ϕ_1

$$Q_{\phi_1} = CV_{IN}$$

$$Q_{CF} = 0$$

During phase ϕ_2



$$\frac{Q_{\phi_1}}{C_F} = V_{OUT}$$

$$\frac{CV_{IN}}{C_F} = V_{OUT}$$



$$\frac{V_{OUT}}{V_{IN}} = \frac{C}{C_F}$$

Serves as a noninverting amplifier
Gain can be very accurate
Output valid only during Φ_2

Another charge redistribution circuit

 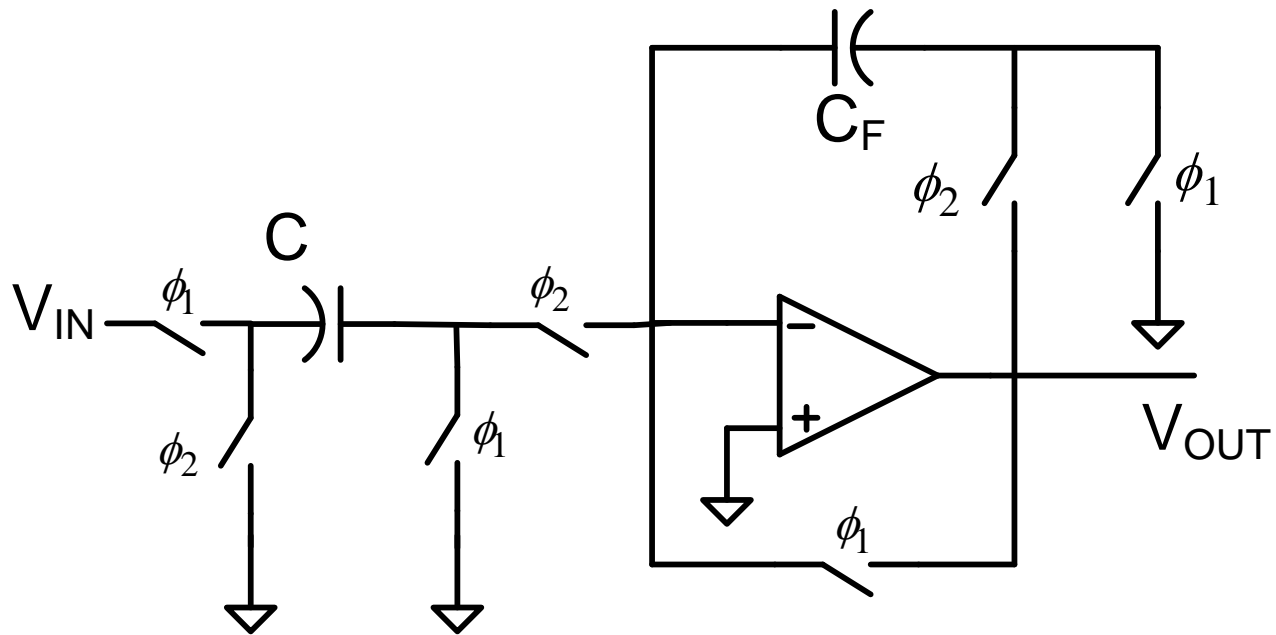

A charge redistribution circuit

  

During phase ϕ_1

$$Q_{\phi_1} = CV_{IN}$$

$$Q_{CF} = 0$$

During phase ϕ_2



$$\frac{-Q_{\phi_1}}{C_F} = V_{OUT}$$

$$\frac{-CV_{IN}}{C_F} = V_{OUT}$$

$$\frac{V_{OUT}}{V_{IN}} = -\frac{C}{C_F}$$

Serves as an inverting amplifier
Gain can be very accurate
Output valid only during Φ_2


A charge redistribution DAC

 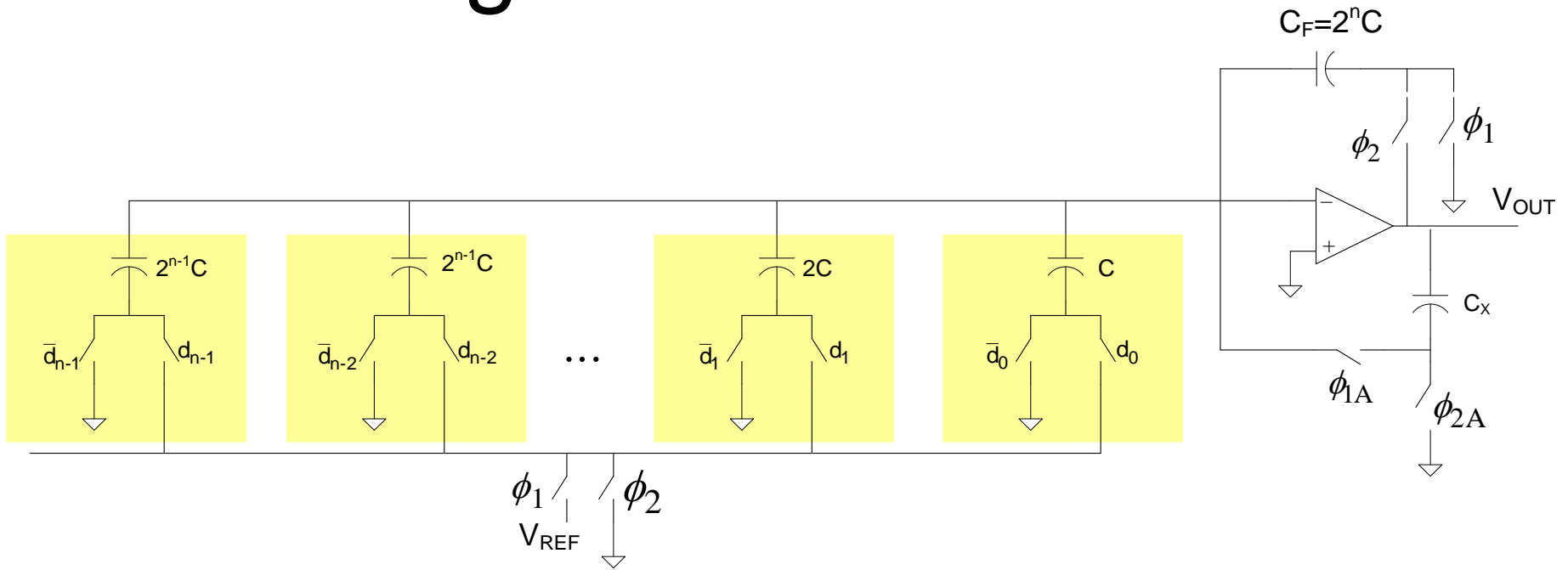

C_X does some good things
 (mitigates V_{OS} , $1/f$ noise and finite gain errors)

Will not consider C_X affects at this time

A charge redistribution DAC

 

During phase ϕ_1

$$Q_{\phi_1} = V_{REF} \sum_{i=0}^{n-1} d_i \cdot 2^i C$$


$$Q_{CF} = 0$$

During phase ϕ_2

$$V_{OUT}(\phi_2) = \frac{1}{C_F} Q_{\phi_1}$$

$$V_{OUT}(\phi_2) = \frac{1}{2^n C} V_{REF} \sum_{i=0}^{n-1} d_i \cdot 2^i C$$
 
$$V_{OUT}(\phi_2) = V_{REF} \sum_{i=0}^{n-1} \frac{d_i}{2^{n-i}}$$




Analog to Digital Converters





Will now focus on design of ADCs

Analog to Digital Converters

 


Analog to Digital Converters

  The conversion from analog to digital in most ADCs is done with comparators





Most ADC design is primarily involved with designing comparators and embedding these into circuits that are robust to nonideal effects

Nyquist Rate

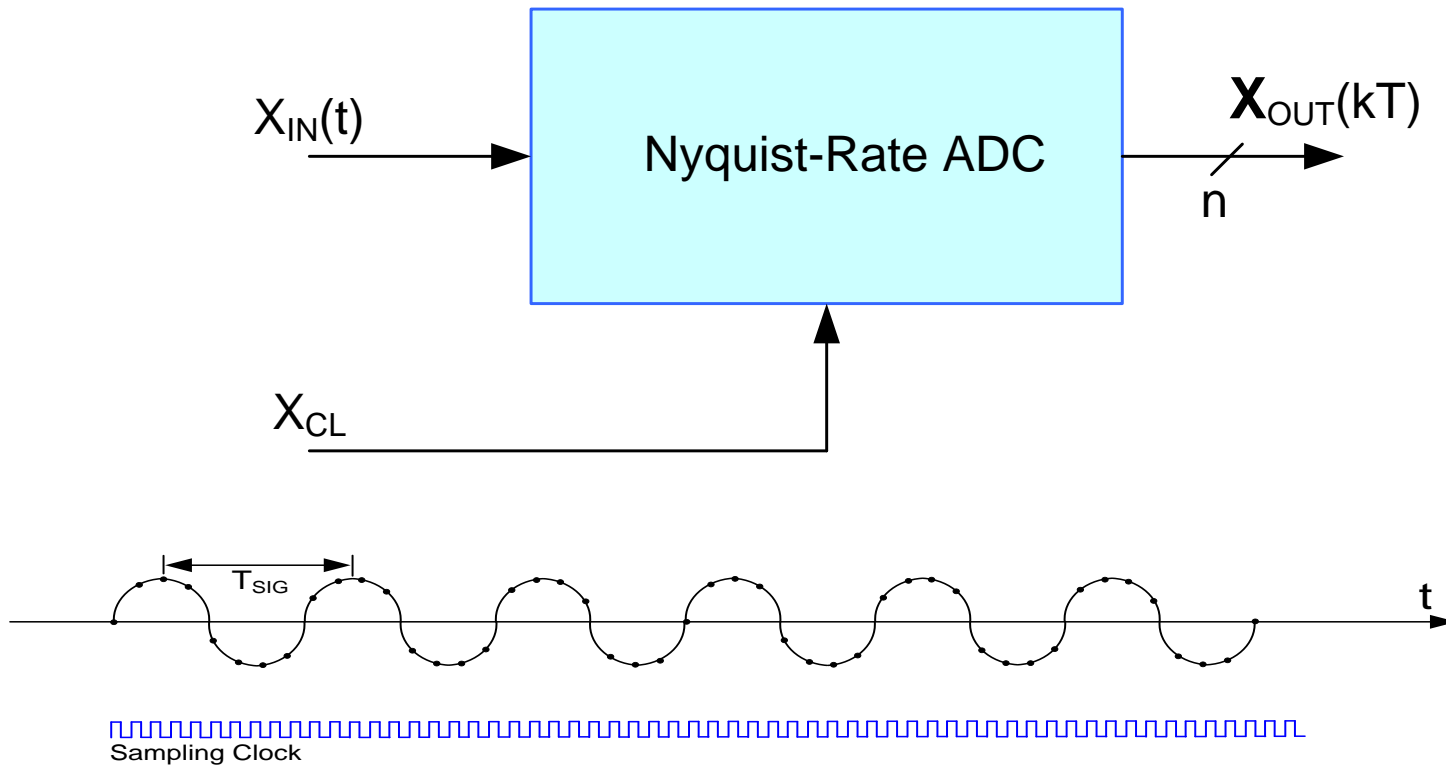


Nyquist Rate Data Converters provide one output for each period of the sampling clock

Nyquist Rate

  


Over-Sampled

 

Over-Sampled Data Converters require multiple sampling clock periods for each output

Over-sampling ratios of 128:1 or 64:1 are common
Dramatic reduction in quantization noise effects
Limited to relatively low effective conversion rates

Data Converter Type Chart

 

ADC Types

Nyquist Rate

- Flash
- Pipeline
- Two-Step Flash
- Multi-Step Flash
- Cyclic (algorithmic)
- Interpolating
- Successive Approximation
- Folded
- Dual Slope

Over-Sampled

- Single-bit
- Multi-bit
- First-order
- Higher-order
- Continuous-time

What Architectures are Actually Used

DACs
Texas Instruments Mar 1, 2023


String	168
R-2R	79
Current Source	52
MDAC	23
Current Sink	17
SAR	9
Pipeline	7
Delta Sigma	4
1-Steering	3
Current Steering	2

ADCs
Texas Instruments April 13 2023

SAR	728
Pipeline	294
Delta Sigma	187
Folding Interpolating Delta Sigma	66
Modulator	9
Two-Step	6
Flash	3
Total	1293

- These are catalog parts
- Specific details about architecture usually absent in data sheets
- Some (many) in list are slight variants and carry different part numbers
- Variety of converters used in ASIC applications will be larger

Nyquist Rate Usage Structures

 

ADC Types

Nyquist Rate

- Flash
- Pipeline
- Two-Step Flash
- Multi-Step Flash
- Cyclic (algorithmic)
- Interpolating
- Successive Approximation
- Folded
- Dual Slope


Over-Sampled

- Single-bit
- Multi-bit
- First-order
- Higher-order
- Continuous-time


All have comparable conversion rates

Basic approach in all is very similar

Flash ADC

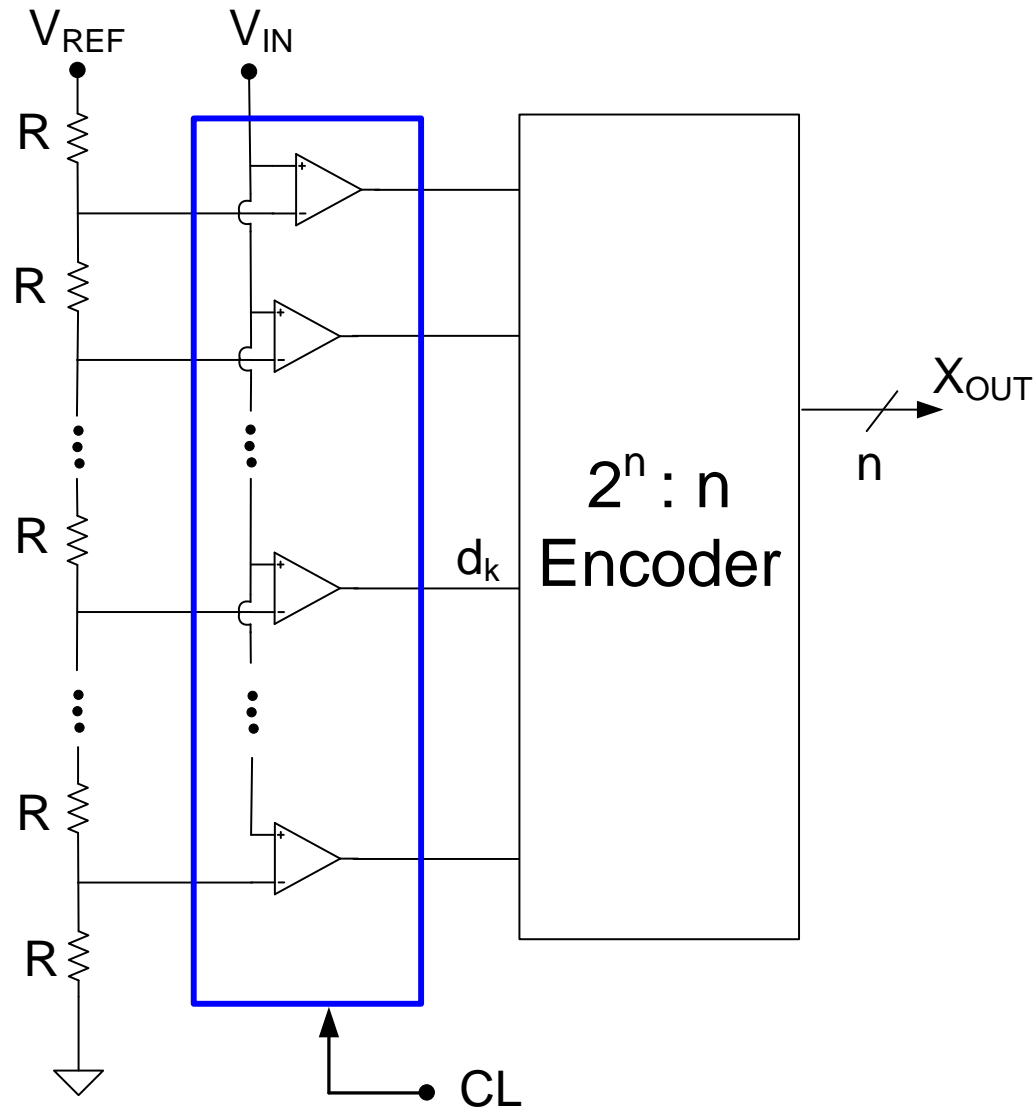

SAR ADC

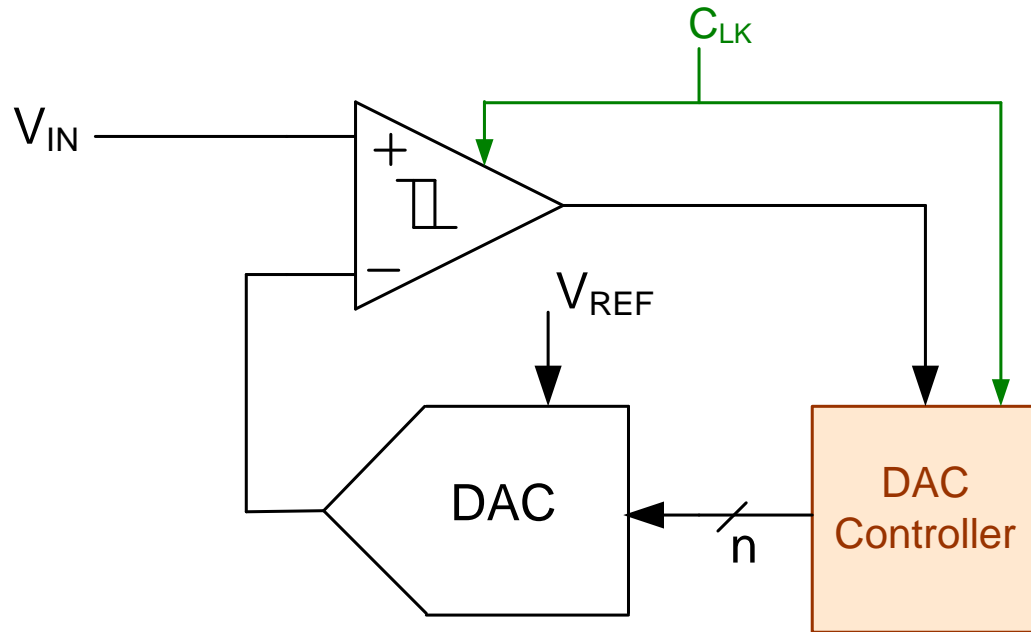

- DAC Controller may be simply U/D counter
- Binary search controlled by Finite State Machine is faster
- SAR ADC will have no missing codes if DAC is monotone
- Not very fast but can be small



Stay Safe and Stay Healthy !

End of Lecture 35