EE 435

Lecture 35

Current Steering DACs

Review from Last Lecture



Basic R-String DAC

For all b_1 and b_2 , $R_U+R_L=R$

- Another Segmented DAC structure
- Can be viewed as a "dither" DAC
- Often n₁ is much smaller than n₂
- Dither can be used in other applications as well

Review from Last Lecture Switches used extensively in data converters ! Switch Implementation Issues



Review from Last Lecture Current Steering DACs

Current will be "steered" to a resistive load (on chip)

Output could be a current (user supplies load)

Basic Concept of Current Steering DACs







What is important is the current generated, not whether it comes from a "current source"



Many potential current generator blocks, just require that all be ideally identical



Inherently Insensitive to Nonlinearities in Switches and Resistors Smaller ON resistance and less phase-shift from clock edges

- Termed "bottom plate switching"
- Thermometer coded

Review from Last Lecture



Transistor Implementation of Switches

Current Steering DACs n V_{REF} **Binary to Thermometer Decoder** (all ON) R R R $N=2^n$. . . S_2 S_{N-1} S₁ R_{F} $|\mathbf{I}_1|$, I₂ ↓I_{N-1} V_{OUT} 1 2

Transistor Implementation of Switches

How should the op amp be compensated?

Assume k switches are on 0<k<N-1

$$\beta = \frac{\frac{R_{CELL}}{k}}{\frac{R_{CELL}}{k} + R_{F}} = \frac{R_{CELL}}{R_{CELL} + kR_{F}}$$
 If $V_{OUTFS} = V_{REF}$ $R_{CELL} = NR_{F}$
 $0.5 < \beta \le 1$

How should the op amp be compensated?









	Problem?
Switch impedance	No
Code-dependent phase margin	Yes
Single-ended output	Yes
C _P	Yes
Binary to Thermometer Decoder	Yes
Op Amp Bandwidth	Yes





Transistors switch between deep cutoff and deep triode



approximately $\sigma = \frac{A_{PEL}}{\sqrt{\Lambda}}$

Consider a k-bit structure that has an acceptable (and desired) yield of Y

Can a k+1 bit structure be easily implemented by simply making 2 copies of the resistor array and adding one bit to the decoder?

The one-afternoon design ?

Current Steering DACs Binary-Weighted Resistor Arrays

 R_{F}

2

Vout



- Need for decoder eliminated !
- Same number of unit resistors as for thermometer coded structure
- DNL may be a major problem
- INL performance about same as thermometer coded if same unit resistors used
- Sizing and layout of switches is critical
- Unary resistor arrays usually used with common-centroid layout(at least for MSB)
- Ratio matching strongly dependent upon area (if common-centroid used to eliminate gradients)
- INL is a random variable with variance approximately proportional to
- Area gets large for good yield with large n

Observe thermometer coding and binary weighted both offer some major advantages and some major limitations

- Thermometer coding (particularly of MSBs) reduces DNL
- Binary coding reduces/eliminates binary:thermometer decoder

Can benefits of thermometer coded and binary weighted structures be obtained?



Binary-Weighted Resistor Arrays

As stated earlier, bundled unary cells are almost always used

Actual layout of resistors is very important

Common centroid layout is desired but may not be practical with a large number of elements



Segmented Resistor Arrays

- Combines two types of architectures
- Inherits advantages of both thermometer and binary approach
- Minimizes limitations of both thermometer and binary approach

R-2R Resistor Arrays



- 4 bit-slices shown
- Can be extended to arbitrary number of bit slices
- Conceptually, area goes up linearly with number of bit slices



Eliminates need for decoder

Node voltages ideally stay constant for any input code

Highly sensitive to nonlinearities in switches

How should switches be sized?





R-2R Resistor Arrays

R-2R Implementation



- Unit cell widely used
- Switch included in cell even if not switched!
- Switches always ON in series elements in R-2R array
- Code dependence of switch impedance of concern How can switch impedances be matched?

Another R-2R DAC



Node voltages change with input code



Switch impedance does not affect performance

Requires matching both current sources and resistors

 β is independent of Boolean code

Node voltages in R/2R block must change for any input transitions Voltages on internal R-2R nodes must settle with input transitions



Clocks must be nonoverlapping

Does this offer any benefits over previous approach ? Offers some compensation for capacitances on current sources Are there other terminations for the current sources? e.g. Dual R-2R?

Data Converter Design Strategies

Remember:

Need to keep nonideal effects below an acceptable performance threshold



R-2R DACs



Key characteristic of R-2R Structures

- Area increases linearly with number of bits of resolution
- Binary to thermometer/bubble converter eliminated
- Simple unary cell can be used for R elements
- Common-centroid layout manageable ??

Key challenges of R-2R Structures

- Switches directly affect R-2R values and ratios
- Voltage on internal nodes must settle for some structures
- If unary cell used, area not optimally allocated for matching





Switch impedance of little concern if current sources ideal Just requires matching of current sources



Critical parasitic capacitors in current-steering DAC



- Binary to thermometer decoder eliminated
- Current sources bundled unary cells
- Bundles large for large n



- Exploits benefits of both thermometer and binary coded structures
- Common-centroid layout likely only necessary on TCA
- Dramatic reduction in complexity of decoder possible



Is linearity or output impedance of current source of concern? Not if individual slices are matched !



Parasitic capacitance on output of current source problematic





Reducing Effects of Parasitic capacitance on output of current source





Which is better?

Effects of parasitic diffusion capacitance? Effects of gate capacitance?



 R_{TERM} often 50Ω or $~100\Omega$

R_{TERM} can be internal or external

Switch impedance now of concern

Output impedance of current sources now of concern



Cascoding reduces output conductance of current source No power penalty, slight reduction in overhead

Current Steering DAC V_{XX} (↓ • () Binary to Thermometer Decoder . . . R_F ∕► n d_1 d_2 d_{N-1} V_{OUT} 2 \boldsymbol{d}_k I_{OUT} I_{OUT}=kI V_{DD} V_{DD} **Cascode Current** V_{XX} **Cascode Current** V_{XX} Source (Mirror) Source (Mirror) M₁ M_1 $V_{\rm YY}$ V_{YY} **Differential Amplifier Boolean Switch Cell** M_2 M_2 (Analog) dk \overline{d}_k $\widehat{\mathbf{d}}_{\mathbf{k}}$ ▲ M₃ M4 M_3

Steer rather than switch current Reduced swing on control signals











- Need only signal swing of $2\sqrt{2}V_{EB}$ to steer currents (so can reduce turn-on and turn-off times) Steering also results in cascoding with M_3 and M_4 thus increasing output impedance of current source (so can probably eliminate M_2)



Reduced Signal Swing on V_S Node with Current Steering



Current Steering DAC I_{D1} ↓ ↓ I_{D2} V_{DD} -M₂ V₁ - M_1 V_{MAX} Standard Boolean Inputs Restricted Boole an Inputs V_{MIN} V_{S} 0V ♥) Ι_T

Reduced Signal Swing on V_S Node with Current Steering





Reduced Signal Swing on V_S Node with Current Steering

Simulation Results: V_{TH} =0.4V, V_{MIN} =0.6V, V_{MAX} =1.07V, V_{EB} =0.3V, γ =1.1



Multiple-output Transconductance Amplifier



- Good linearity
- Each additional output requires only one additional transistor
- Relevant if MDAC output desired
- Cascoding of output devices useful if driving resistive load

Current Steering DAC with Supply Independent Biasing



If transistors on top row are all matched, $I_X = V_{REF}/R$

Thermometer coded structure (requires binary to thermometer decoder)

$$I_{A} = \left(\frac{V_{REF}}{R}\right) \sum_{i=0}^{N-1} d_{i}$$

Provides Differential Output Currents

Current Steering DAC with Supply Independent Biasing



If transistors on top row are all matched, $I_X = V_{REF}/R$

$$V_{A} = \left(-V_{REF} \frac{R_{A}}{R}\right) \sum_{i=0}^{N-1} d_{i}$$

Provides Differential Output Voltages

Current Current Steering DAC with Supply Independent Biasing



$$I_{A} = \left(\frac{V_{REF}}{R}\right)_{i=0}^{n-1} d_{i} 2^{i}$$

Provides Differential Output Currents

Usually use bundled unary cells Can use current steering rather than current switching

(switched LSB:MSB notation)



Stay Safe and Stay Healthy !

End of Lecture 35