



EE 435

Lecture 36

ADC Design

Analog to Digital Converters

 
 
The conversion from analog to digital in ALL ADCs is done with comparators



ADC design is primarily involved with designing comparators and embedding these into circuits that are robust to nonideal effects


Review from Last Lecture

Nyquist Rate

  

Review from Last Lecture

Over-Sampled

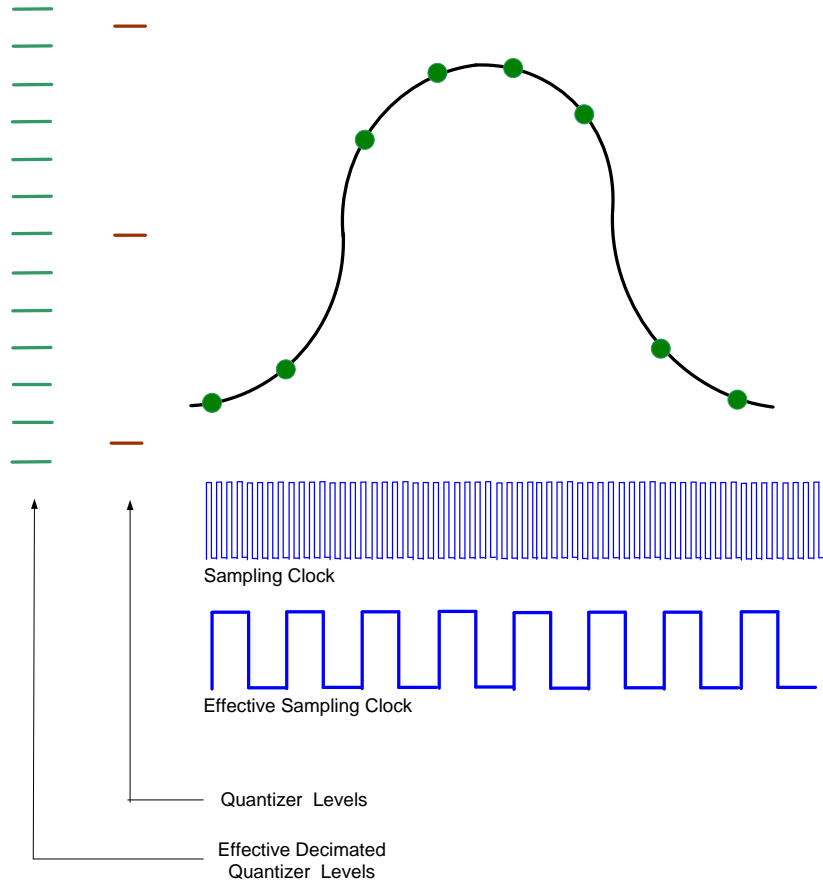

Over-sampling ratios of 128:1 or 64:1 are common
Dramatic reduction in quantization noise effects
Limited to relatively low frequencies

ADC Types

Nyquist Rate

- Flash
- Pipeline
- Two-Step Flash
- Multi-Step Flash
- Cyclic (algorithmic)
- Successive Approximation
- Folded
- Dual Slope

Over-Sampled

- Single-bit
- Multi-bit
- First-order
- Higher-order
- Continuous-time

Review from Last Lecture

ADC Types

Nyquist Rate

- Flash
- Pipeline
- Two-Step Flash
- Multi-Step Flash
- Cyclic (algorithmic)
- Interpolating
- Successive Approximation
- Folded
- Dual Slope

Over-Sampled


- Single-bit
- Multi-bit
- First-order
- Higher-order
- Continuous-time

All have comparable conversion rates

Basic approach in all is very similar



Review from Last Lecture

Flash ADC

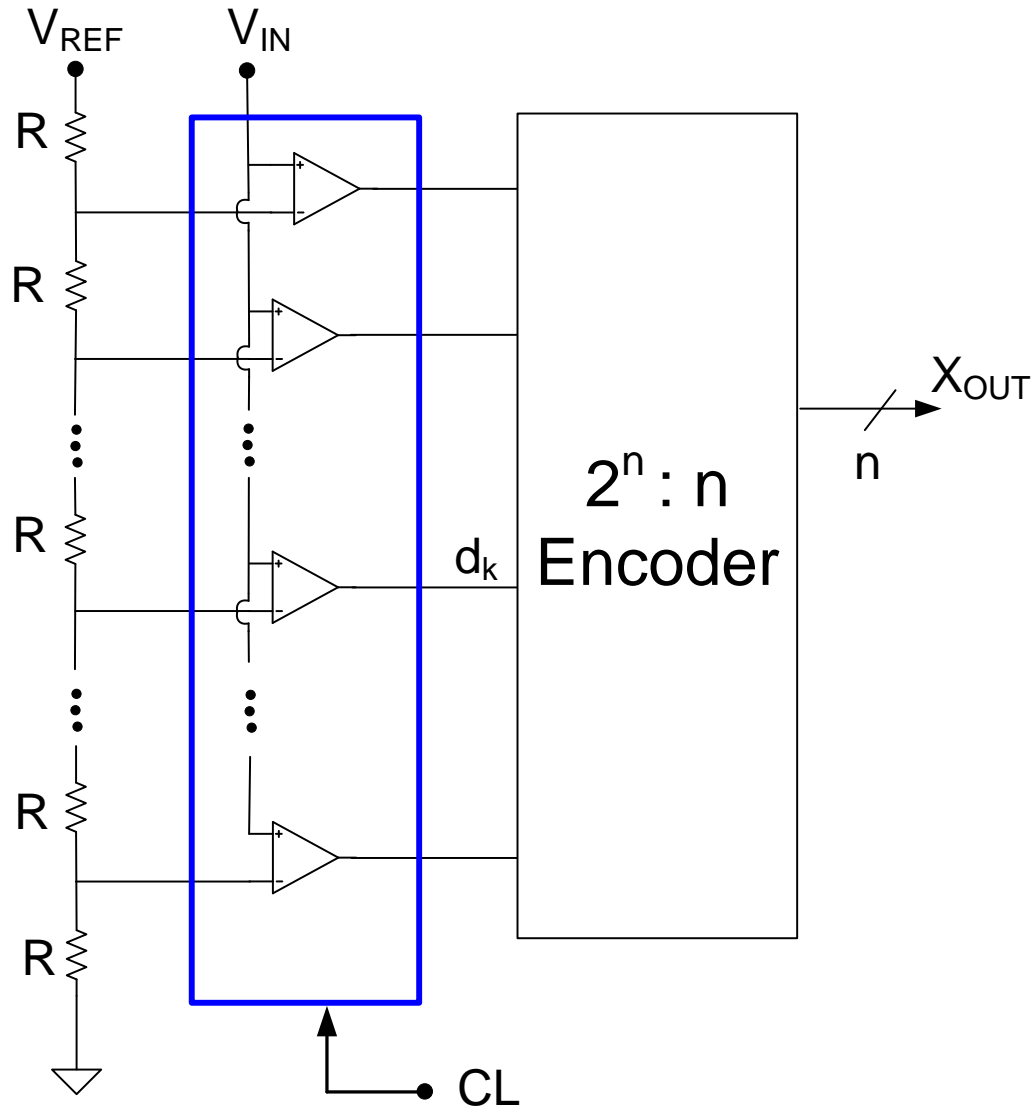

Review from Last Lecture

Clocked Comparator

  

Preamplifier with offset compensation and regenerative latch

Gain of preamplifier may still not be large enough

Flash ADC Summary

Flash ADC

Very fast

Simple structure

Usually Clocked

Bubble Removal Important

Seldom over 6 or 7 bits of resolution

- Flash ADC has some really desirable properties (simple and fast)
- Wouldn't it be nice if we could derive most of the benefits of the FLASH ADC without the major limitations


To be practical at higher resolution, must address the major limitation of the FLASH ADC

Major Limitation of FLASH ADC at higher resolutions?


Number of comparators increases geometrically --- 2^n

Review from Last Lecture

Two-Step Flash ADC with Interstage Gain


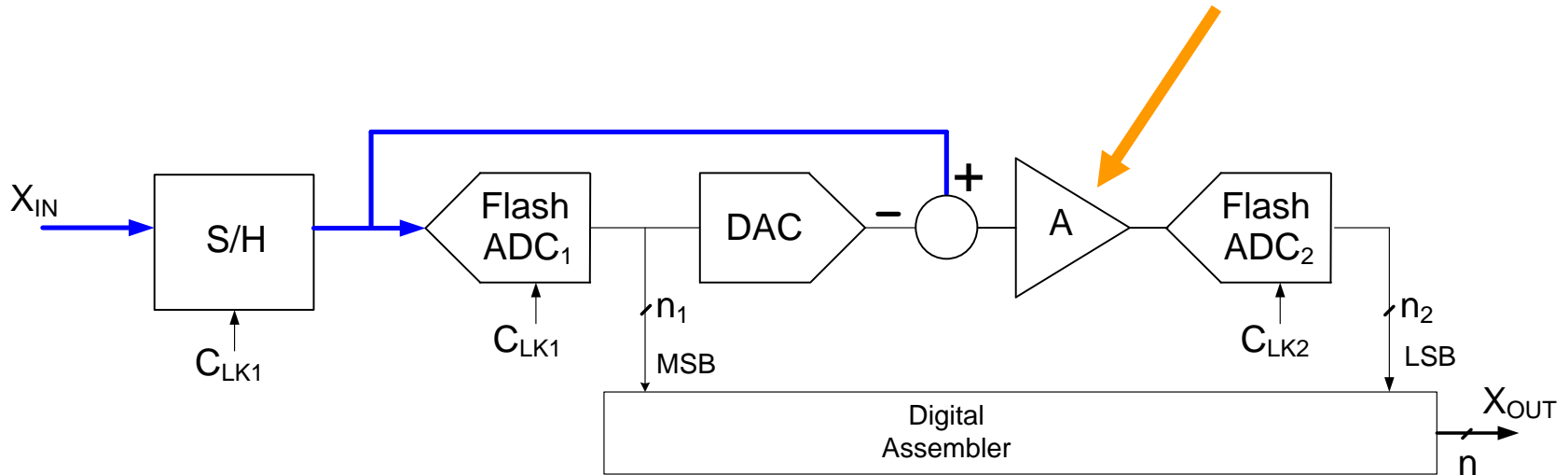


 Three-Step Flash ADC with Interstage Gain and S/H





- S/H frees first stage to take another sample during second stage conversion
- This has a pipelining capability

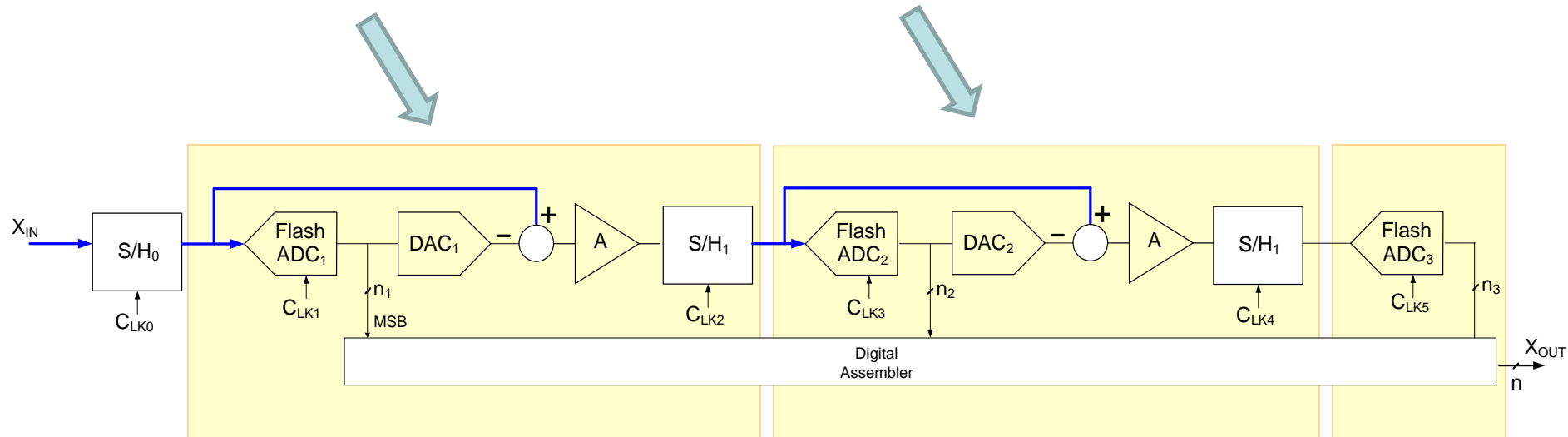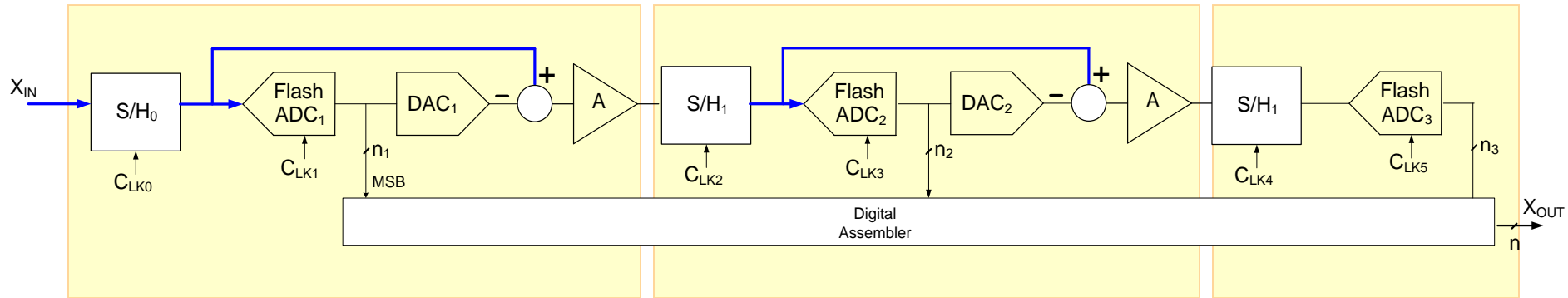Three-Step Flash ADC with Interstage Gain and S/H




Same structure, different grouping!

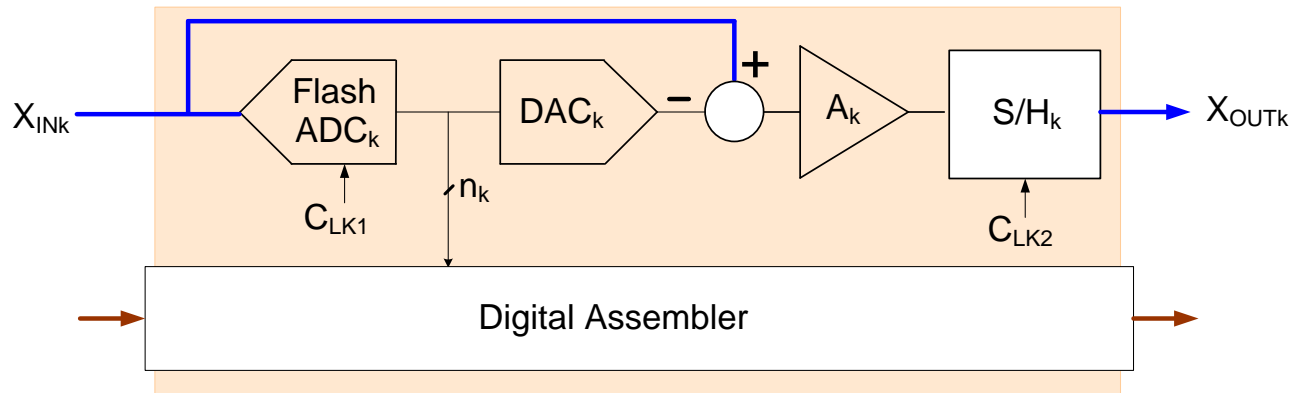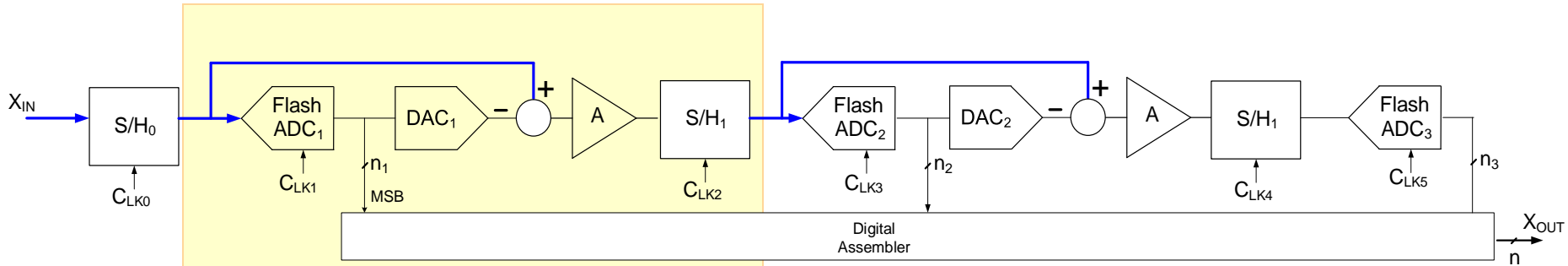
Three-Step Flash ADC with Interstage Gain




Pipelined ADC

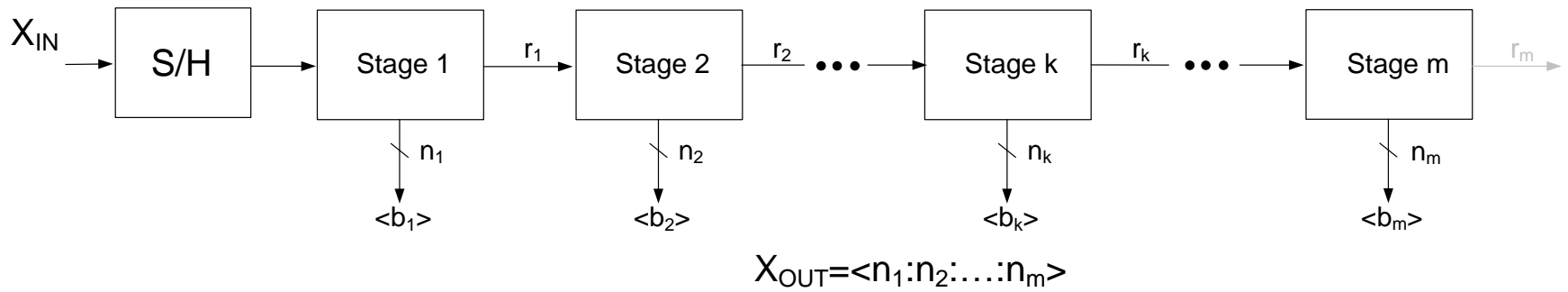


Pipelined ADC

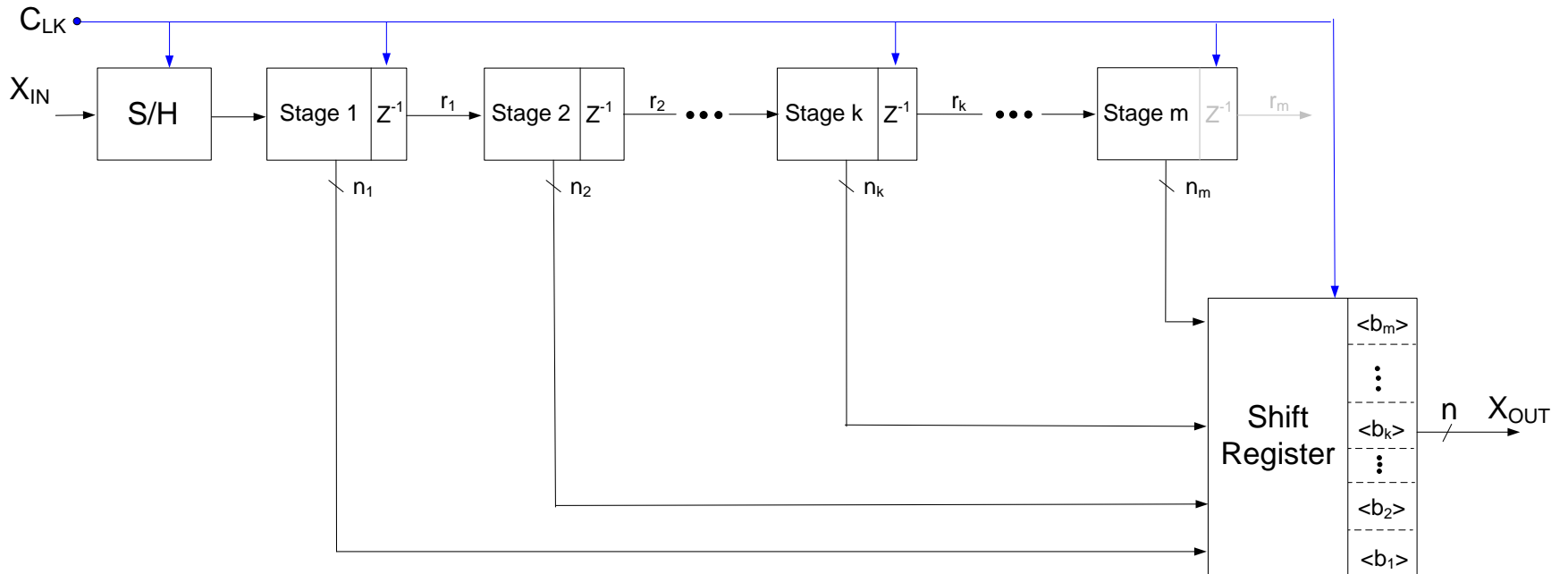

Pipelined ADC Stage k

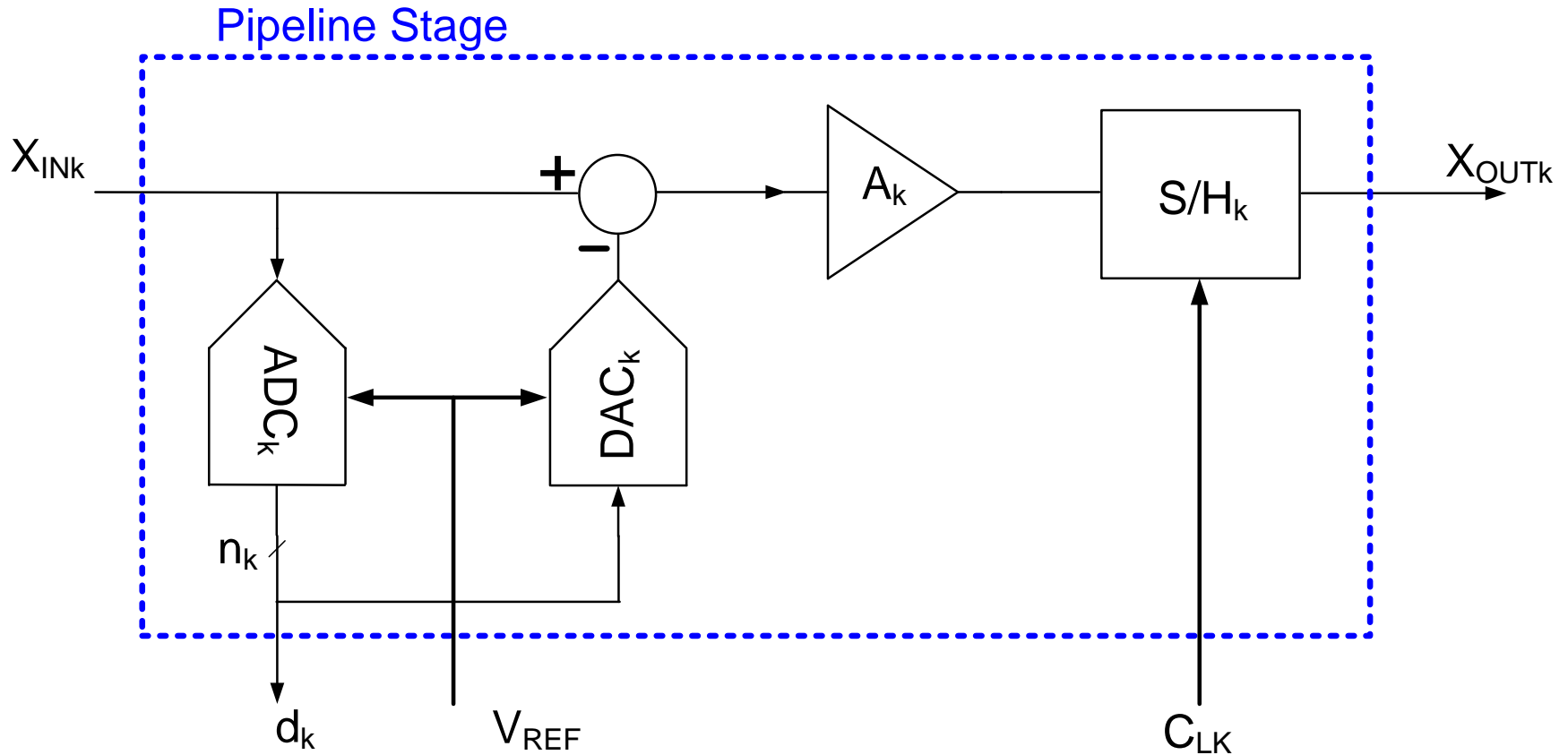


Pipelined ADC Stage k

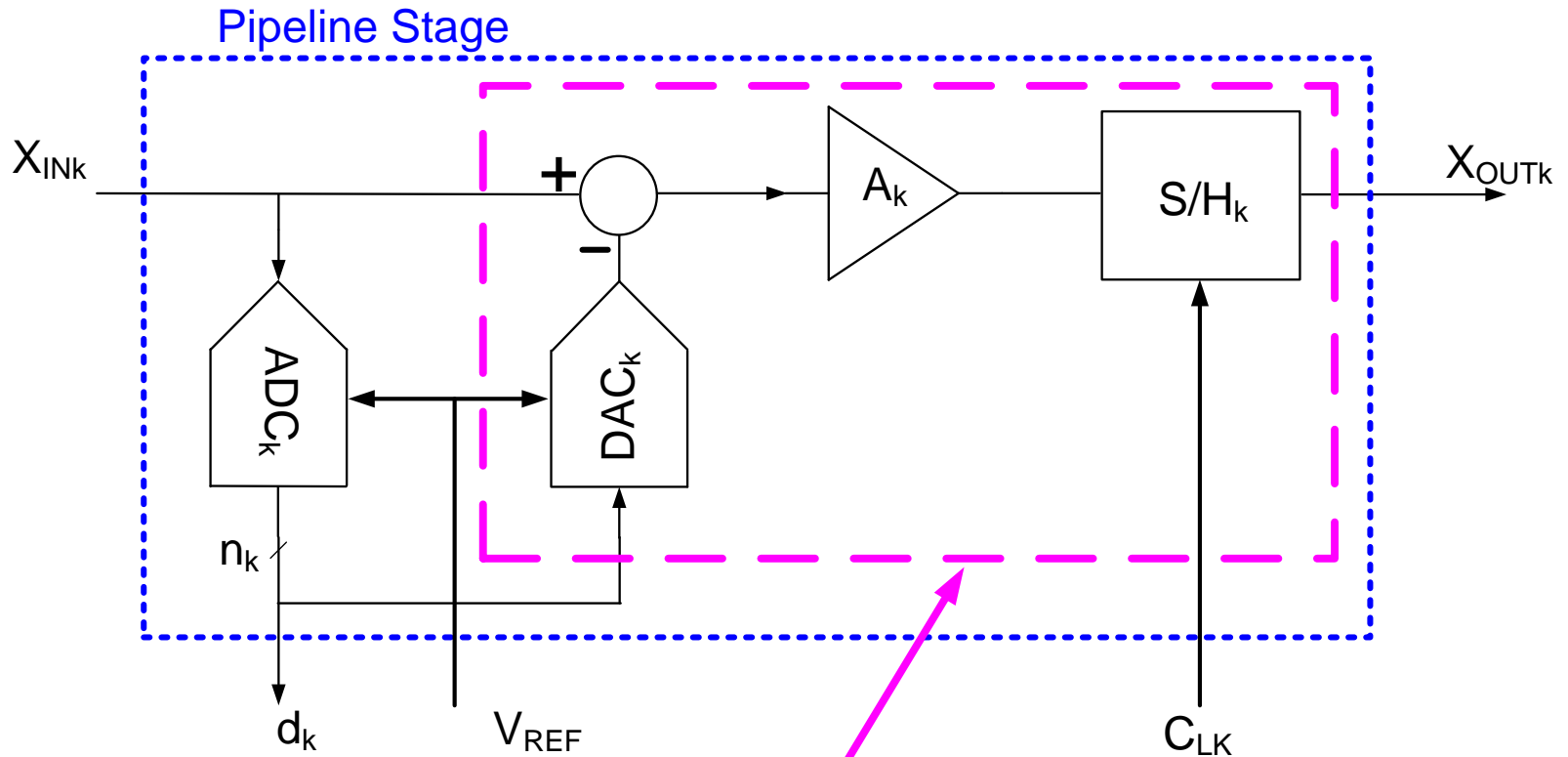


Usually Realized as
Single SC Block

Pipelined ADC Stage k

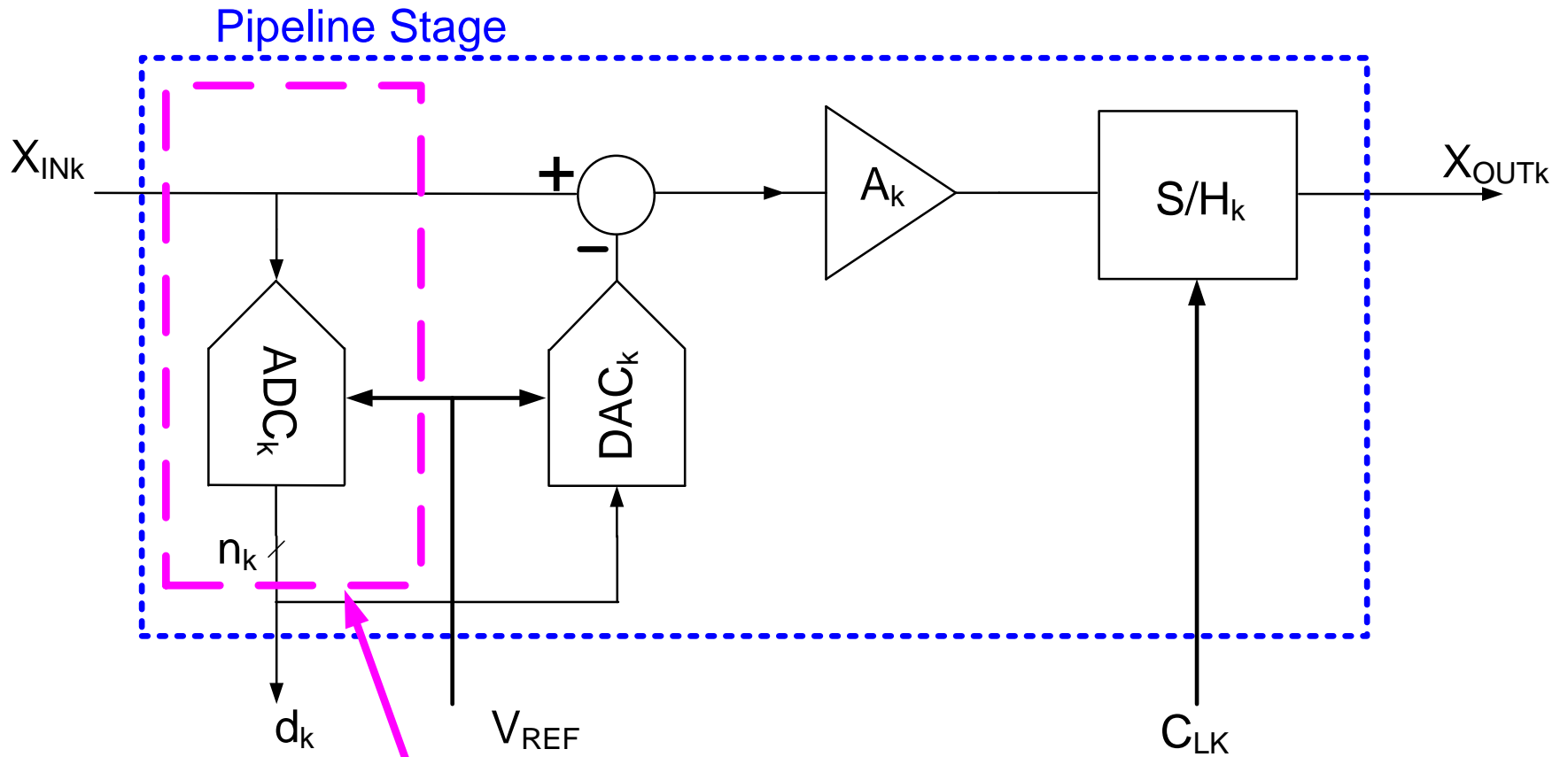

Usually Realized as Flash ADC
(often simple comparator if $n_k=1$)


Pipelined ADC Stage k

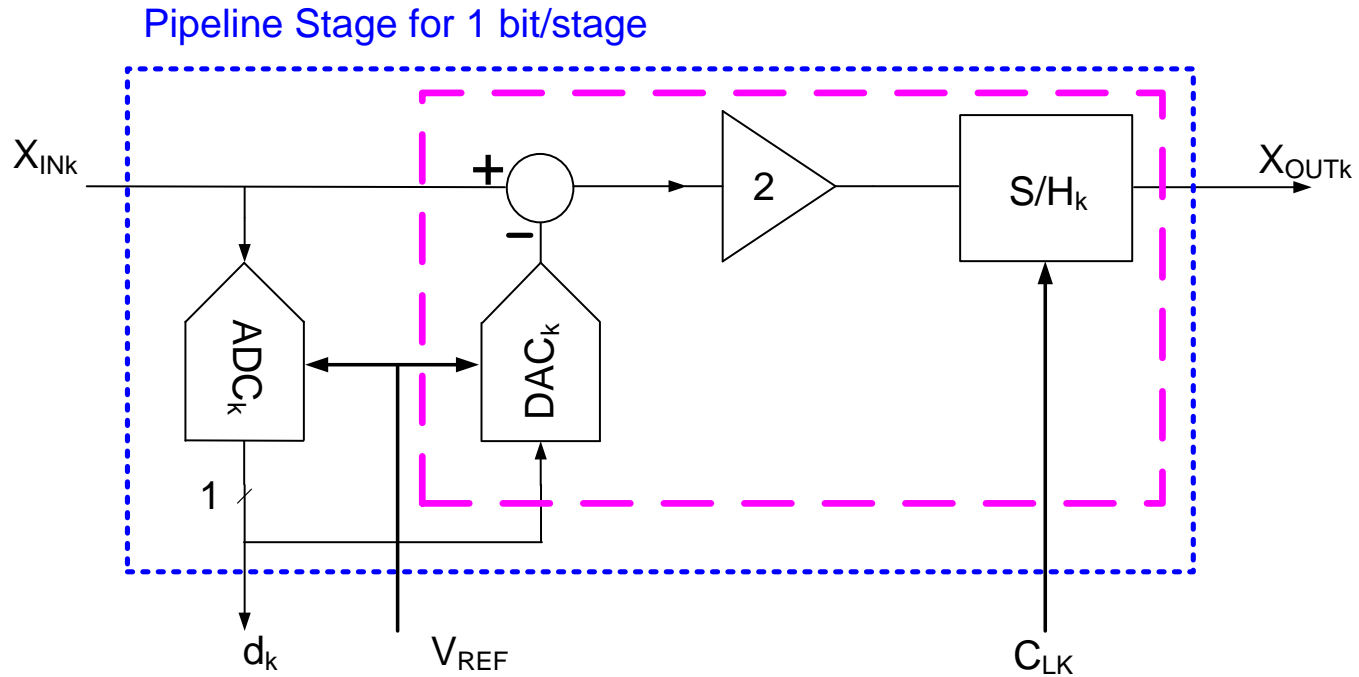



$$V_O = \begin{cases} 2V_{IN} + \frac{V_{REF}}{2} & V_{IN} < 0 \\ 2V_{IN} - \frac{V_{REF}}{2} & V_{IN} > 0 \end{cases}$$

Transfer Characteristics for 1 bit/stage

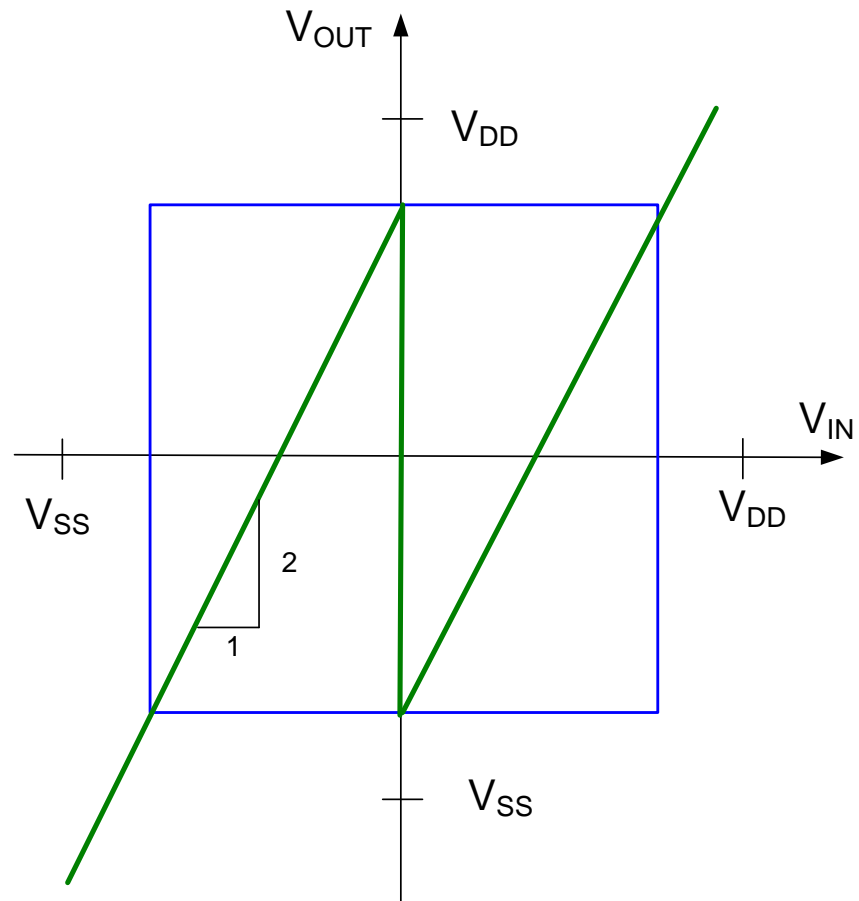
$$V_O = \begin{cases} 2V_{IN} + \frac{V_{REF}}{2} & V_{IN} < 0 \\ 2V_{IN} - \frac{V_{REF}}{2} & V_{IN} > 0 \end{cases}$$




Consider the following circuit

 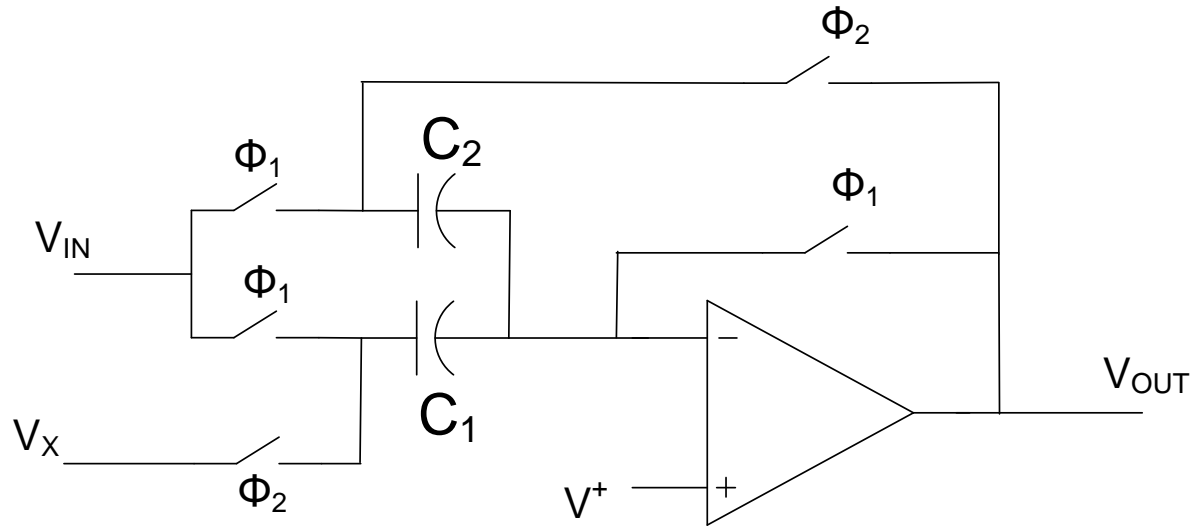

Consider the following circuit

 


During Φ_1

 

Consider the following circuit


During Φ_1

 


$$Q_1 = C_1 (V_{IN} - V^+)$$

$$Q_2 = C_2 (V_{IN} - V^+)$$

Consider the following circuit

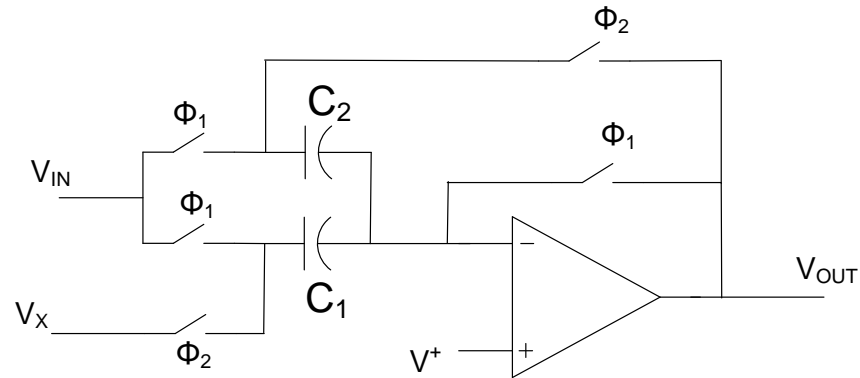

During Φ_2

 


Consider the following circuit

$$Q_1 = C_1 (V_{\text{IN}} - V^+)$$

$$Q_2 = C_2 (V_{\text{IN}} - V^+)$$

During Φ_2

 

Define Q_{1T} to be the charge transferred from C_1 during phase Φ_2


$$Q_{1T} = C_1 (V_{\text{IN}} - V^+) - C_1 (V_X - V^+) = C_1 (V_{\text{IN}} - V_X)$$

Define Q_{2F} to be the total charge on C_2 during phase Φ_2

$$Q_{2F} = Q_2 + Q_{1T} = C_2 (V_{\text{IN}} - V^+) + C_1 (V_{\text{IN}} - V_X) = (C_1 + C_2) V_{\text{IN}} - C_2 V^+ - C_1 V_X$$

Consider the following circuit

During Φ_2

 


$$Q_{2F} = (C_1 + C_2)V_{IN} - C_2V^+ - C_1V_X$$

$$V_{C2F} = \frac{Q_{2F}}{C_2} = \left(1 + \frac{C_1}{C_2}\right)V_{IN} - V^+ - \frac{C_1}{C_2}V_X$$

$$V_{OUTF} = V_{C2F} + V^+ = \left(1 + \frac{C_1}{C_2}\right)V_{IN} - \frac{C_1}{C_2}V_X$$

Consider the following circuit

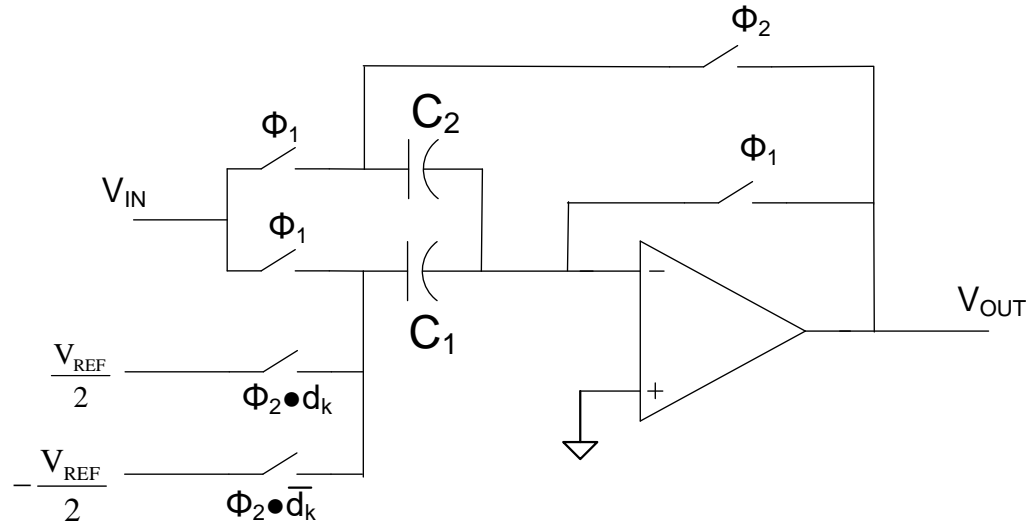


$$V_{OUTF} = \left(1 + \frac{C_1}{C_2}\right) V_{IN} - \frac{C_1}{C_2} V_X$$

If $C_1 = C_2 = C$ and $V_X = -\frac{V_{REF}}{2}$

$$V_{OUTF} = 2V_{IN} + \frac{V_{REF}}{2}$$

Consider the following circuit

 


$$V_{OUTF} = \left(1 + \frac{C_1}{C_2}\right) V_{IN} - \frac{C_1}{C_2} V_X$$

Likewise

$$\text{If } C_1 = C_2 = C \text{ and } V_X = \frac{V_{REF}}{2}$$



$$V_{OUTF} = 2V_{IN} - \frac{V_{REF}}{2}$$

Observe

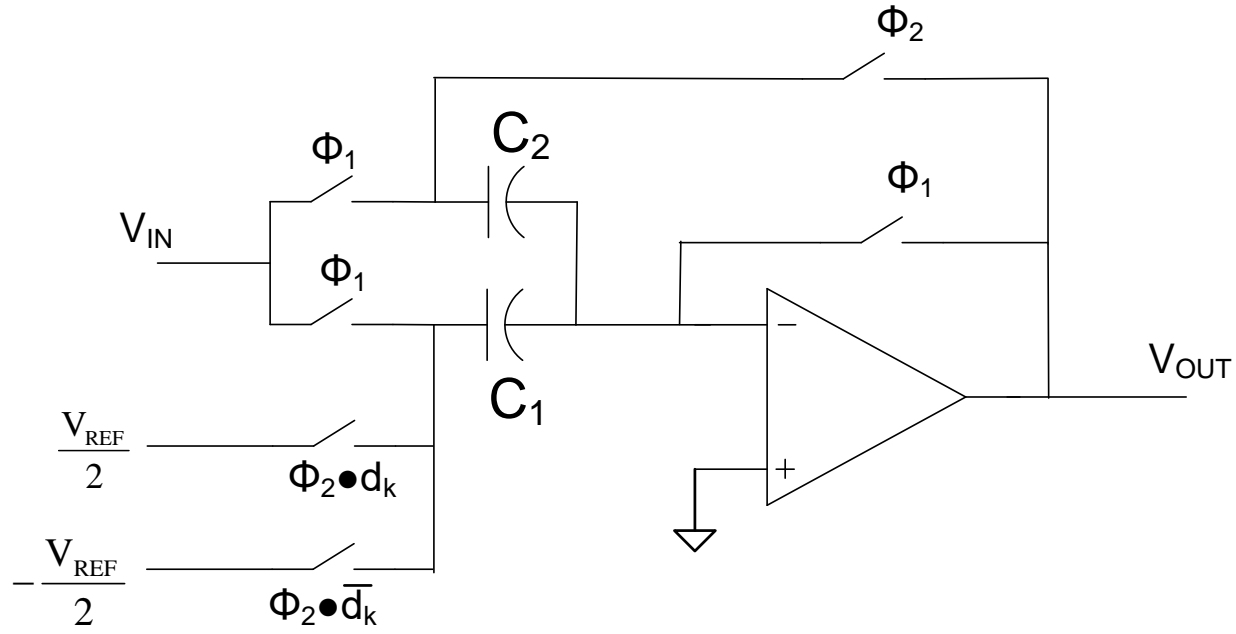


$$V_O = \begin{cases} 2V_{IN} + \frac{V_{REF}}{2} & V_{IN} < 0 \\ 2V_{IN} - \frac{V_{REF}}{2} & V_{IN} > 0 \end{cases}$$

1-bit/Stage Pipeline Implementation

 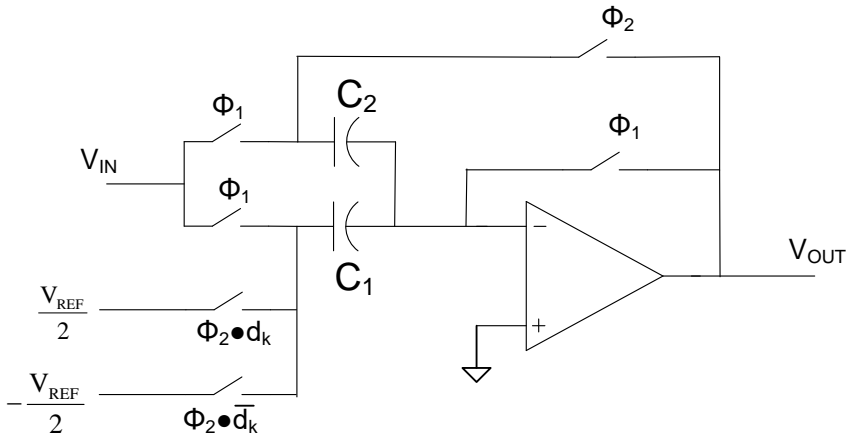


$$V_O = \begin{cases} 2V_{IN} + \frac{V_{REF}}{2} & V_{IN} < 0 \\ 2V_{IN} - \frac{V_{REF}}{2} & V_{IN} > 0 \end{cases}$$

1-bit/Stage Pipeline Implementation

 

ADC Types


Nyquist Rate

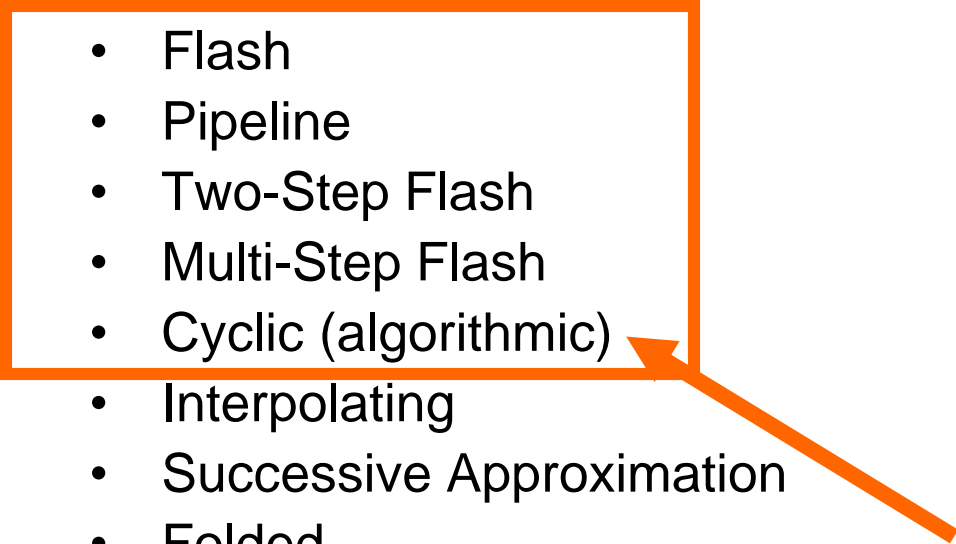- Flash
 - Pipeline
 - Two-Step Flash
 - Multi-Step Flash
 - Cyclic (algorithmic)
 - Interpolating
 - Successive Approximation
 - Folded
 - Dual Slope
- 

Over-Sampled

- Single-bit
- Multi-bit
- First-order
- Higher-order
- Continuous-time

Cyclic (Algorithmic) ADC

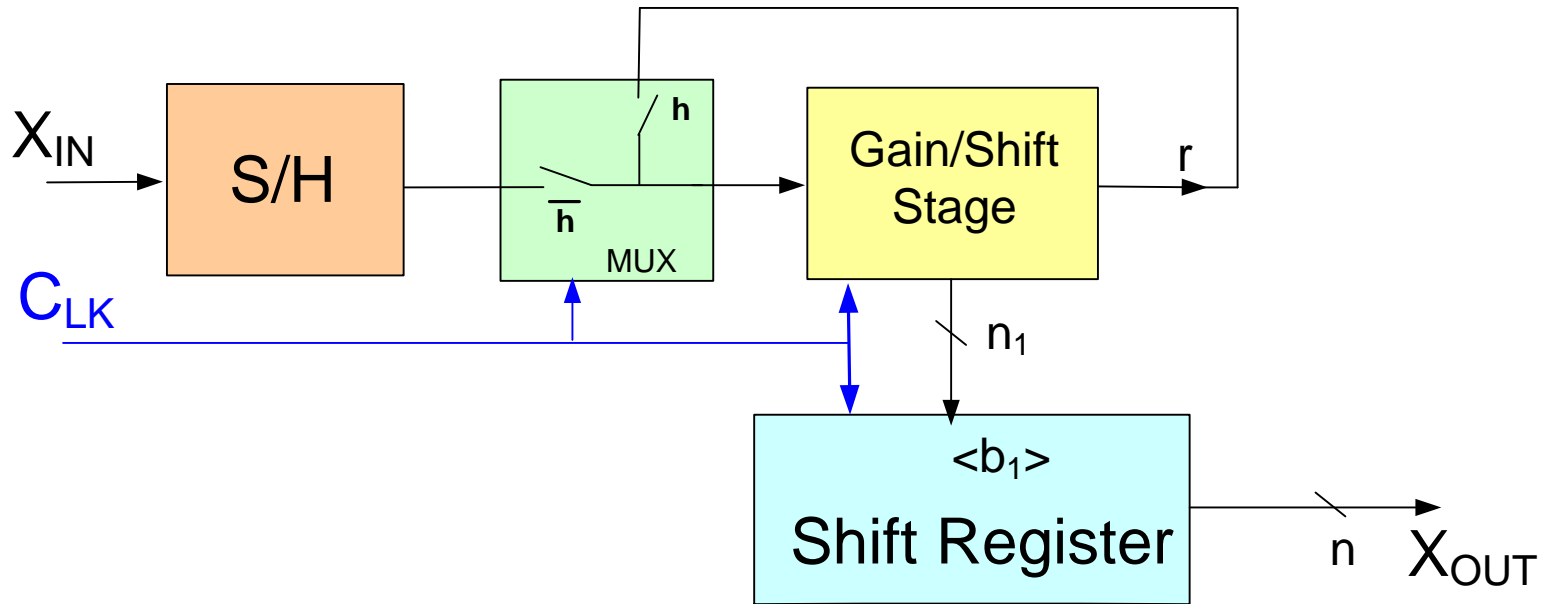

- Re-use Pipelined Stage
- Small amount of hardware
- Effective thru-put decreases

ADC Types

Nyquist Rate


- Flash
- Pipeline
- Two-Step Flash
- Multi-Step Flash
- Cyclic (algorithmic)
- Interpolating
- Successive Approximation
- Folded
- Dual Slope

Over-Sampled


- Single-bit
- Multi-bit
- First-order
- Higher-order
- Continuous-time



Interpolating ADC

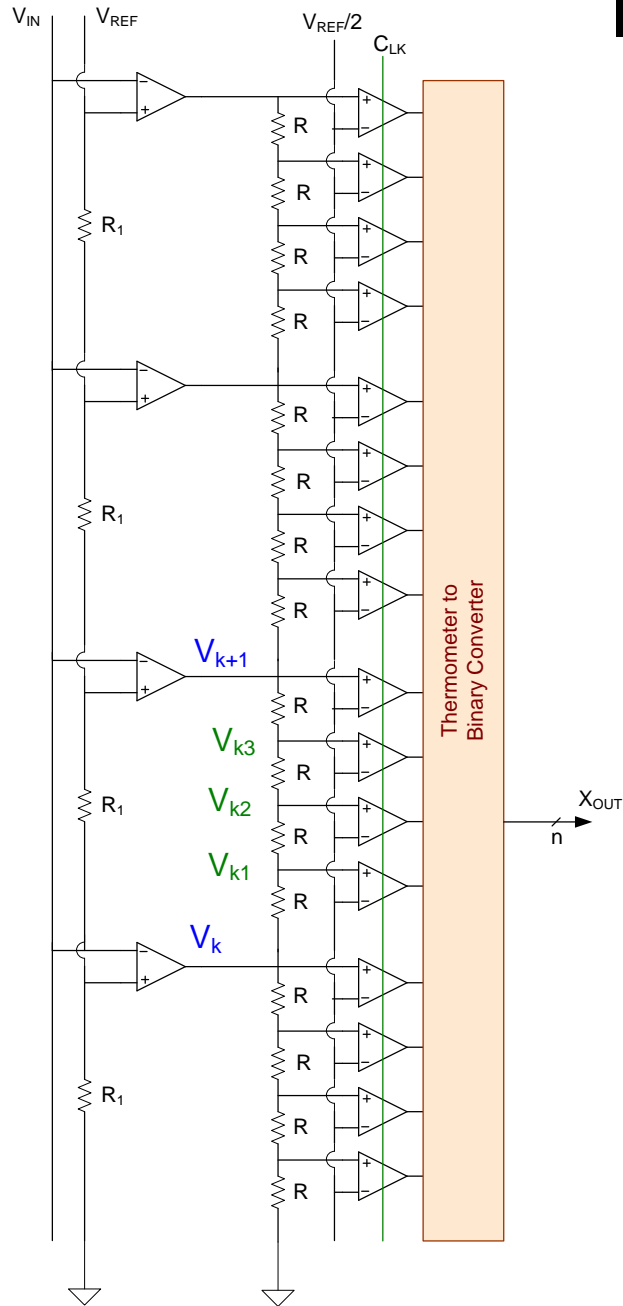

 - Amplifiers are finite-gain saturating
- Shown for 4-bit
- Clocked comparators usually regenerative
- Reduces Offset Requirements for Comparators



ADC Types

Nyquist Rate


- Flash
- Pipeline
- Two-Step Flash
- Multi-Step Flash
- Cyclic (algorithmic)
- Interpolating
- Successive Approximation
- Folded
- Dual Slope

Over-Sampled

- Single-bit
- Multi-bit
- First-order
- Higher-order
- Continuous-time



SAR ADC

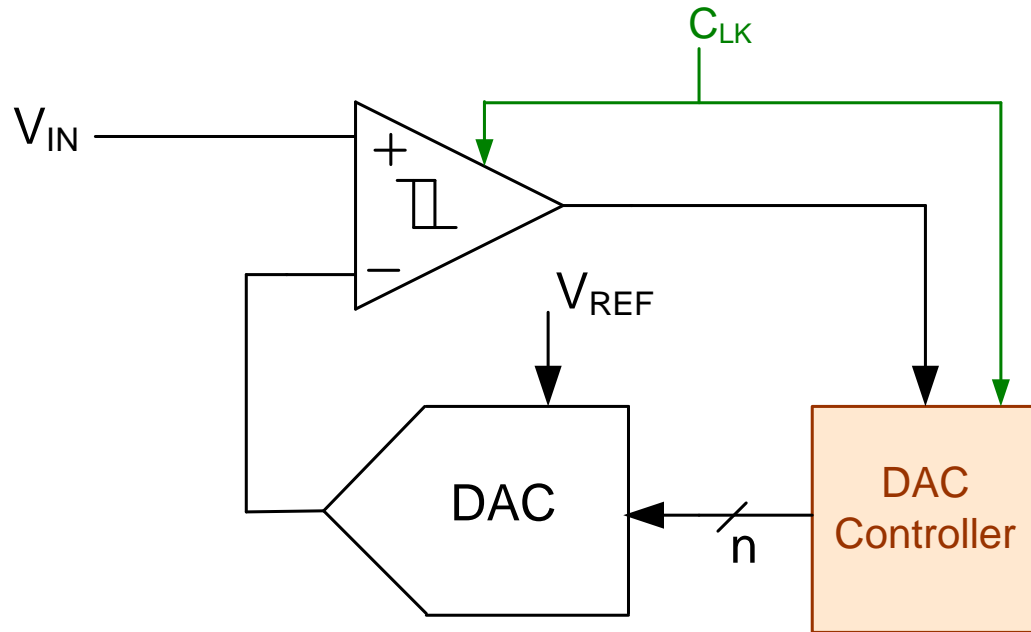

- DAC Controller may be simply U/D counter
- Binary search controlled by Finite State Machine is faster
- SAR ADC will have no missing codes if DAC is monotone
- Not very fast but can be small

ADC Types

Nyquist Rate

- Flash
- Pipeline
- Two-Step Flash
- Multi-Step Flash
- Cyclic (algorithmic)
- Interpolating
- Successive Approximation
- Folded
- Dual Slope

Over-Sampled



- Single-bit
- Multi-bit
- First-order
- Higher-order
- Continuous-time

And Single Slope



Single-Slope ADC

Sometimes Termed Integrating ADC

 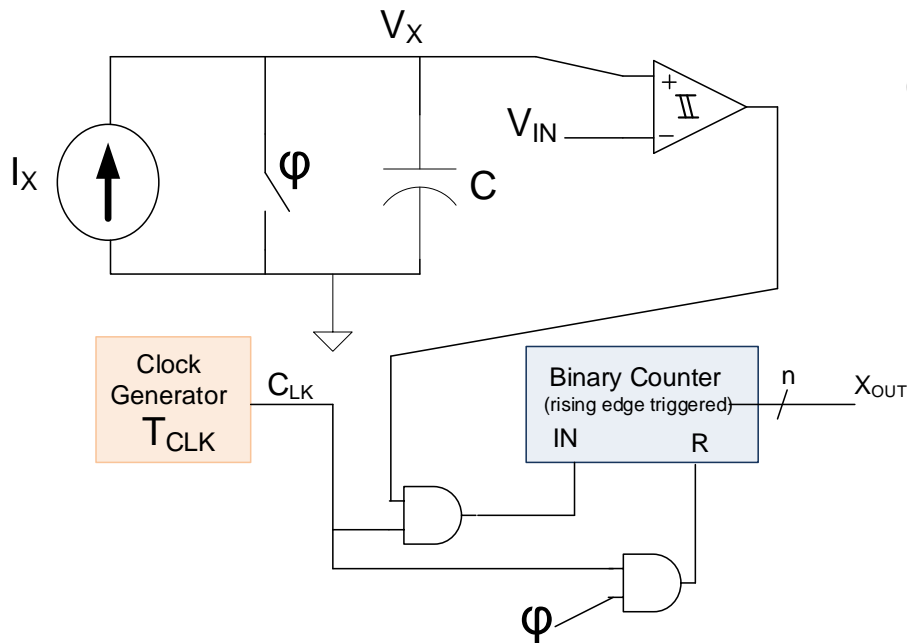

Falling edge of ϕ synchronous with respect to falling edge of C_{CLK}

Can convert asynchronously wrt C_{CLK} or can be a clocked ADC where conversion clock signal is synchronous wrt C_{CLK} .

Output valid when comparator output goes low


Note V_{REF} not explicitly shown in ADC architecture

Single-Slope ADC

Operation:

Assume $V_X(t_{\text{CONV}})=0$
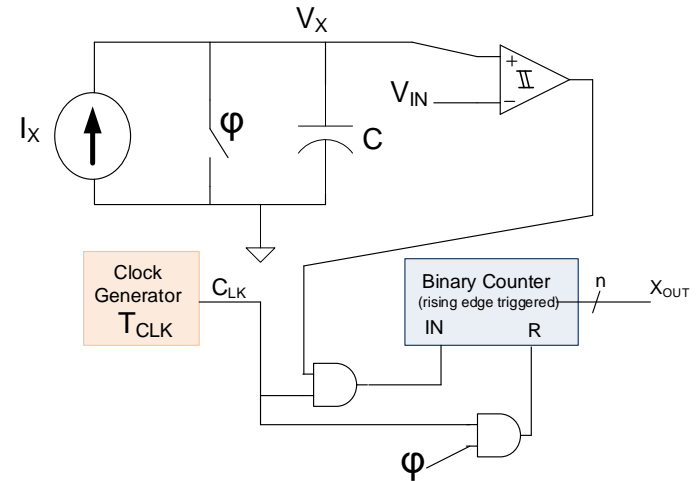
$$V_X(t) = \frac{1}{C} \int_{t_{\text{CONV}}}^t I_X dt = \frac{I_X}{C} (t - t_{\text{CONV}}) \quad (1)$$



Assume $I_X, V_{\text{REF}}, R, C, T_{\text{CLK}}$ are selected to satisfy the relationship

$$V_{\text{REF}} = \frac{1}{C} \int_{t_{\text{CONV}}}^{t_{\text{CONV}} + 2^n T_{\text{CLK}}} I_X dt = \frac{I_X}{C} 2^n T_{\text{CLK}} \quad \text{thus} \quad V_{\text{LSB}} = \frac{V_{\text{REF}}}{2^n} = \frac{I_X}{C} T_{\text{CLK}} \quad (2)$$

Comparator will stop counter when $V_X = V_{\text{IN}}$ and counter output will be $X_{\text{OUT}} = k$

$$\text{thus } V_X(t_{\text{CONV}} + kT_{\text{CLK}}) = V_{\text{IN}} + \varepsilon \quad \text{where } 0 < \varepsilon < V_{\text{LSB}}$$

It follows from (1) that

$$V_X(t_{\text{CONV}} + kT_{\text{CLK}}) = \frac{I_X}{C} kT_{\text{CLK}} = V_{\text{IN}} + \varepsilon \quad (3)$$

And finally from (2) and (3) that


$$V_{\text{IN}} = k \left(\frac{I_X}{C} T_{\text{CLK}} \right) - \varepsilon \cong \frac{k}{2^n} V_{\text{REF}}$$

Single-Slope ADC

$I_X, V_{REF}, R, C, T_{CLK}$ must satisfy the relationship

$$V_{REF} = \frac{I_X}{C} 2^n T_{CLK} \quad (1)$$

$$V_{IN} \cong \frac{k}{2^n} V_{REF}$$

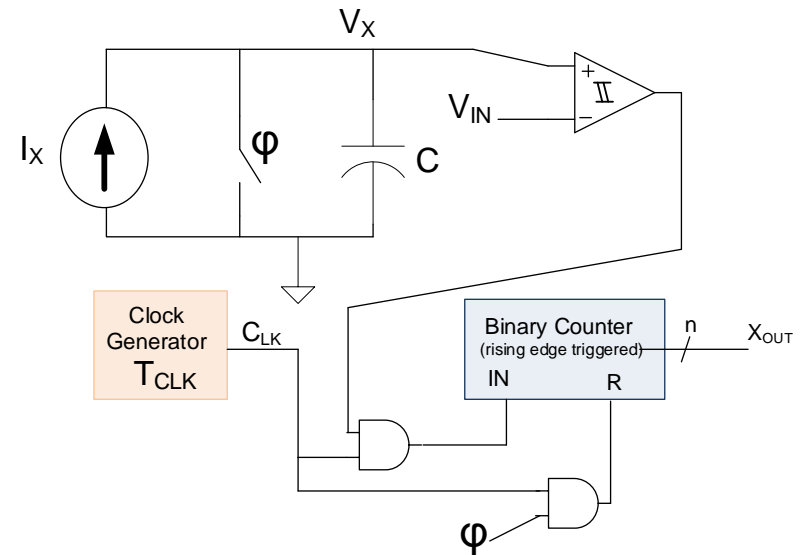

Benefits: Very simple structure and can provide a low-cost easy solution for low speed applications



Limitations:

- Process variations make it difficult to satisfy (1)
- C is large and must be off chip
- Linearity of C important (since off-chip)
- Nonlinearity in I_X degrades performance
- R_{OUT} of I_X degrades performance
- Slow
- Not widely used

Options for improving performance:

- Introduce self-calibration cycle to satisfy (1) by trimming I_X or C
- Use high-impedance current source
- Use OP-Amp Based RC integrator

Dual-Slope ADC

 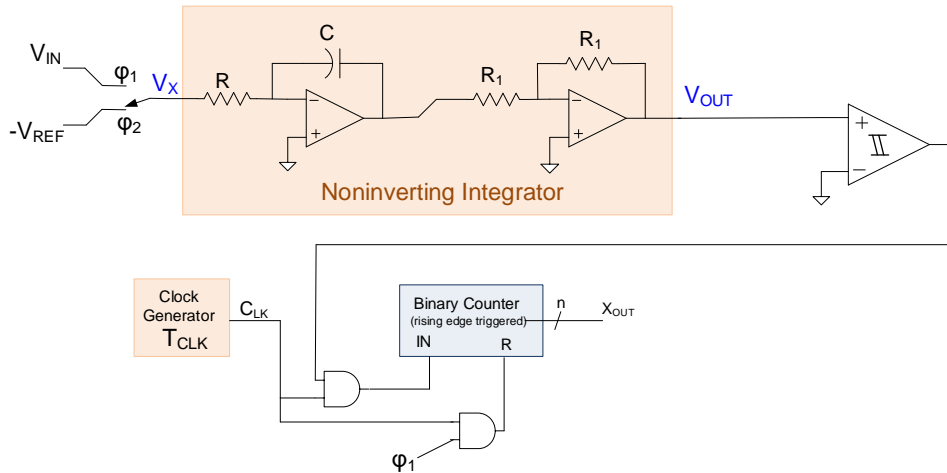

- Output valid when comparator output transitions to Low
- Must set RC time constants and CCLK so output does not saturate
- Shown as noninverting integrator but slight modification will also work with inverting integrator
- Other integrator structures could be used
- Can leave one or more clock cycles between integrate up and integrate down

Dual-Slope ADC

Operation:

$$V_{OUT}(t) = \frac{1}{RC} \int_{t_{CONV}}^t V_X dt$$

During ϕ_1 , integrate V_{IN} for time $2^n T_{CLK}$


At end of integrate up interval, $V_{OUT}(2^n T_{CLK}) = \frac{1}{RC} V_{IN} 2^n T_{CLK}$

Reset counter at time $2^n T_{CLK}$

During ϕ_2 , integrate $-V_{IN}$ until comparator goes low and count clock transitions during down integration interval. At time comparator changes states, $V_{OUT}=0$ and code in counter is k

$$0 = \frac{1}{RC} \int_{t_{CONV}}^{t_{CONV} + 2^n T_{CLK}} V_{IN} dt - \frac{1}{RC} \int_{t_{CONV} + 2^n T_{CLK}}^{t_{CONV} + 2^n T_{CLK} + k T_{CLK}} V_{REF} dt \quad \Rightarrow \quad \frac{1}{RC} V_{IN} 2^n T_{CLK} = \frac{1}{RC} V_{REF} k T_{CLK}$$

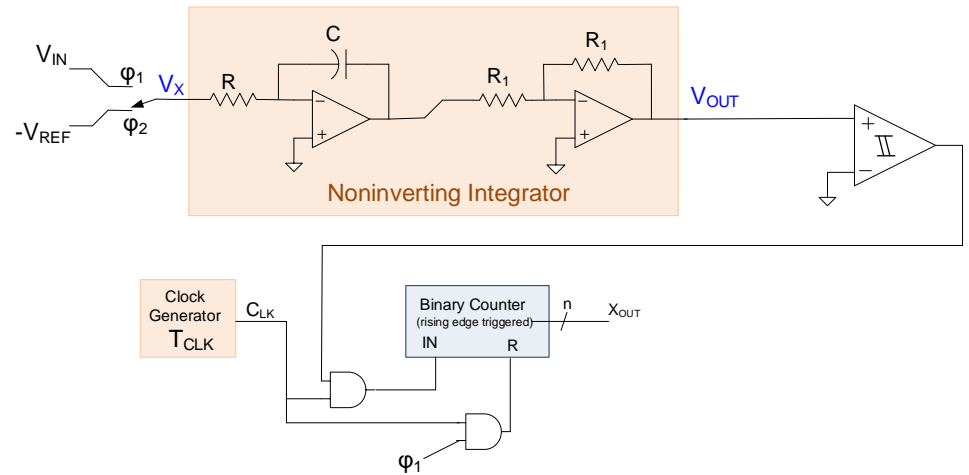Solving, obtain: $V_{IN} = \frac{k}{2^n} V_{REF}$



Dual-Slope ADC

$$V_{IN} = \frac{k}{2^n} V_{REF}$$


Observations:

Benefits

- Not dependent upon R, C, or T_{CLK} (provided integrator does not saturate)
- Very simple structure that can give good results and cost can be low
- Inherently monotone

Limitations:

 - Capacitor large and likely must be off-chip
- Linearity of capacitor is important (particularly of concern when off-chip)
- Slow
- Not widely used





Stay Safe and Stay Healthy !

End of Lecture 36

End of Lecture 40
From Spring 2020