

EE 435



Lecture 36

ADC Design

- Flash Architecture
- Pipelined Architecture

Analog to Digital Converters

 
 
The conversion from analog to digital in most ADCs is done with comparators



ADC design is primarily involved with designing comparators and embedding these into circuits that are robust to nonideal effects


Review from Last Lecture

Nyquist Rate

  

Review from Last Lecture

Over-Sampled

 

Over-sampling ratios of 128:1 or 64:1 are common
Dramatic reduction in quantization noise effects
Limited to relatively low frequencies

ADC Types

Nyquist Rate

- Flash
- Pipeline
- Two-Step Flash
- Multi-Step Flash
- Cyclic (algorithmic)
- Successive Approximation
- Folded
- Dual Slope

Over-Sampled

- Single-bit
- Multi-bit
- First-order
- Higher-order
- Continuous-time

What Architectures are Actually Used

DACs
Texas Instruments Mar 1, 2023

String	168
R-2R	79
Current Source	52
MDAC	23
Current Sink	17
SAR	9
Pipeline	7
Delta Sigma	4
1-Steering	3
Current Steering	2

ADCs
Texas Instruments April 13 2023

SAR	728
Pipeline	294
Delta Sigma	187
Folding Interpolating Delta Sigma	66
Modulator	9
Two-Step	6
Flash	3
Total	1293

- These are catalog parts
- Specific details about architecture usually absent in data sheets
- Some (many) in list are slight variants and carry different part numbers
- Variety of converters used in ASIC applications will be larger

Review from Last Lecture

ADC Types

Nyquist Rate

- Flash
- Pipeline
- Two-Step Flash
- Multi-Step Flash
- Cyclic (algorithmic)
- Interpolating
- Successive Approximation
- Folded
- Dual Slope

Over-Sampled


- Single-bit
- Multi-bit
- First-order
- Higher-order
- Continuous-time

All have comparable conversion rates


Basic approach in all is very similar

Review from Last Lecture

Flash ADC

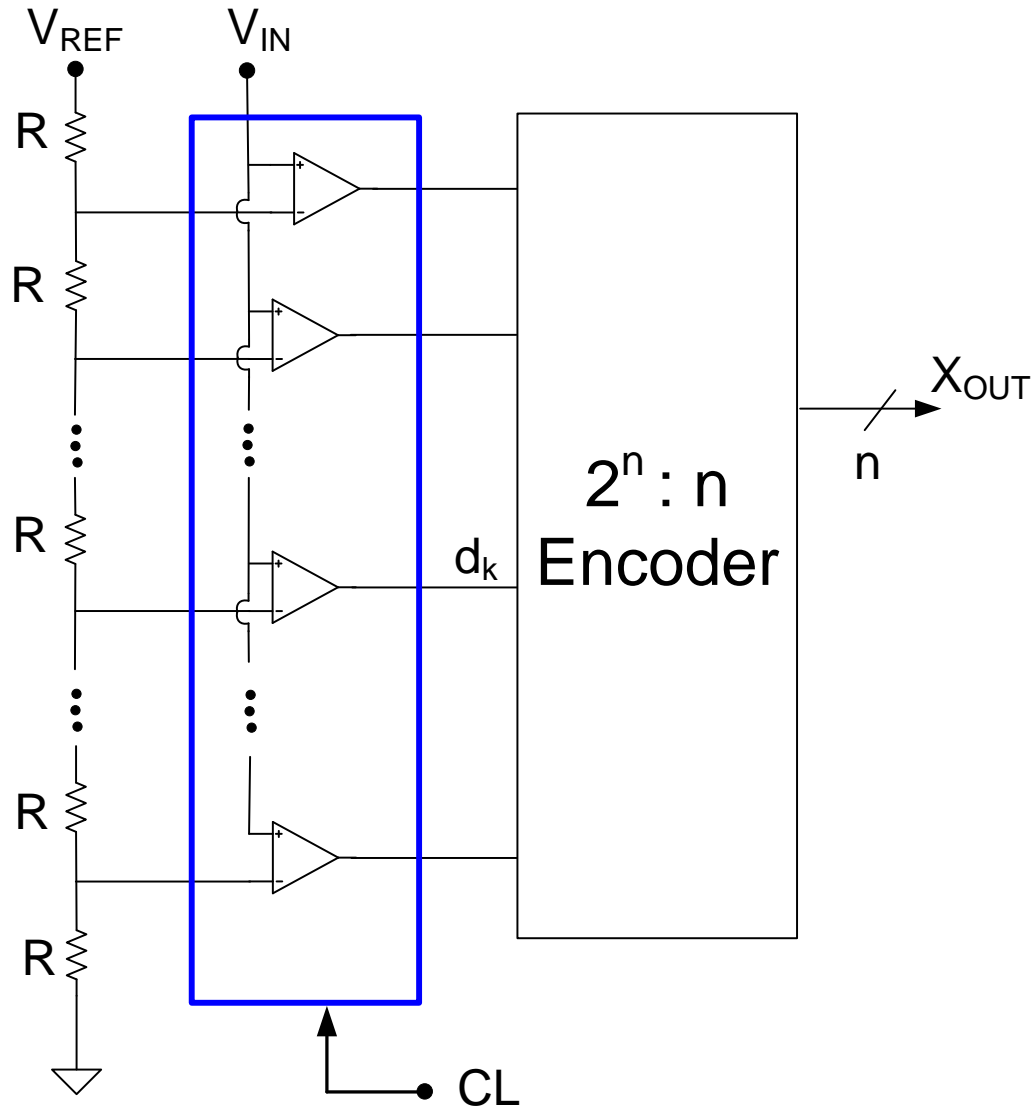


SAR ADC

 

- DAC Controller may be simply U/D counter
- Binary search controlled by Finite State Machine is faster
- SAR ADC will have no missing codes if DAC is monotone
- Not very fast but can be small

Flash ADC

 

Asynchronous operation (benefit or liability?)

Vulnerable to missing codes

High number of comparators needed (for large n)

R-string area requires considerable area and source of INL limitations

Offset voltage of comparators of concern

Simultaneous switching of large number of comparators can cause supply glitches


Large parasitic capacitance on V_{IN} pin

Bubbles in output can occur

Metastability an issue

Power dissipation can be large

Flash ADC with Front-End S/H

 


Prevents input to ADC from changing during sampling (Synchronous instead of Asynchronous)

Performance of ADC can be no better than that of the S/H

Significant amount of effort and power may go into the S/H

Comparators


High-Gain Saturating Amplifier

 

Clocked Comparator



Linear High-gain Amplifier

Regenerative Feedback Amplifier

 


Clocked Comparator

Regenerative Comparators

  

Differential

 

Single-Ended

Regenerative Feedback



Large offset voltage (100mV or more)

Previous-decision affects offset

Clocked Comparator

(Single-ended input)

Recall:

  

Forcing $V_{OUT}=V_{IN}$ (by closing switch ϕ) forces the amplifier to operate at the trip point



Concept applicable irrespective of how large the gain of the amplifier is

But power dissipation may be high when ϕ is activated


How can this property be exploited to form clocked comparator?

Clocked Comparator


(Single-ended input)

  

Low Gain Comparator

 

High Gain Comparator

 

High Gain Comparator with hysteresis (regenerative)


If goal is to compare V_{IN} with V_{TRIP} , have clocked comparator

But comparison point highly process dependent thus limiting this approach

Clocked Comparator

(Single-ended input)

Comparison now with V_{DACK}


 


Amplifier may be viewed as a preamplifier with offset compensation

- Ideally removes all offset effects
- May not have a large enough gain
- Regenerative latch often used (either for gain block or following)

Clocked Comparator

(Single-ended input)

  


Preamplifier with offset compensation and regenerative latch

Gain of preamplifier may still not be large enough


Can use two pre-amp stages and/or offset compensation on latch

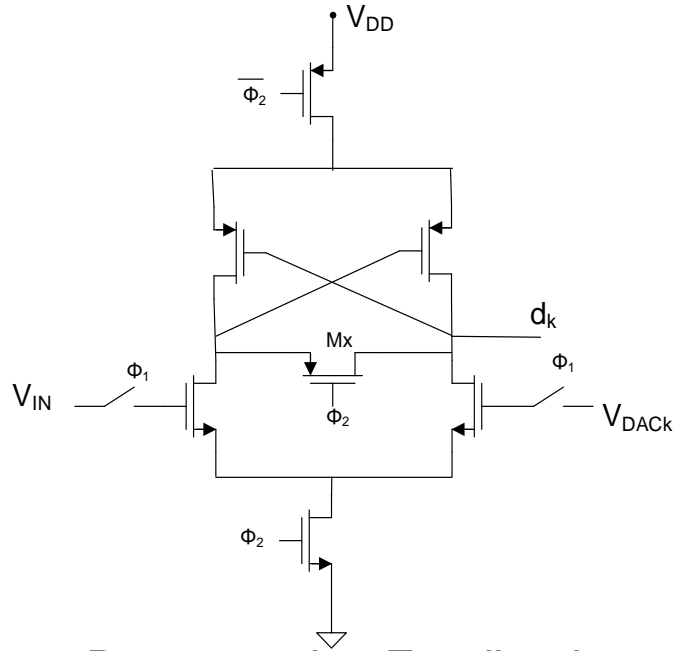Clocked Comparator with Regenerative Feedback




Regenerative Feedback

Regenerative Comparators

 





Differential

 

Single-Ended

- Mx used to reduce (eliminate) previous code dependence on comparator decision
- Regenerative feedback often used to force decision when differential inputs are small
- Several variants of clocked comparators are available
- Important to not have trip point dependent upon previous comparison results
- Often one or more linear gain stages precede the regenerative stage
- Power dissipation can be small in regenerative feedback comparators
- Large offset voltage (100mV or more) common for regenerative feedback comparators

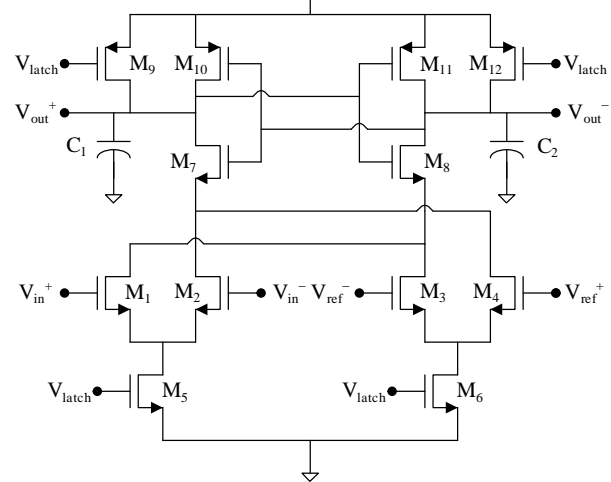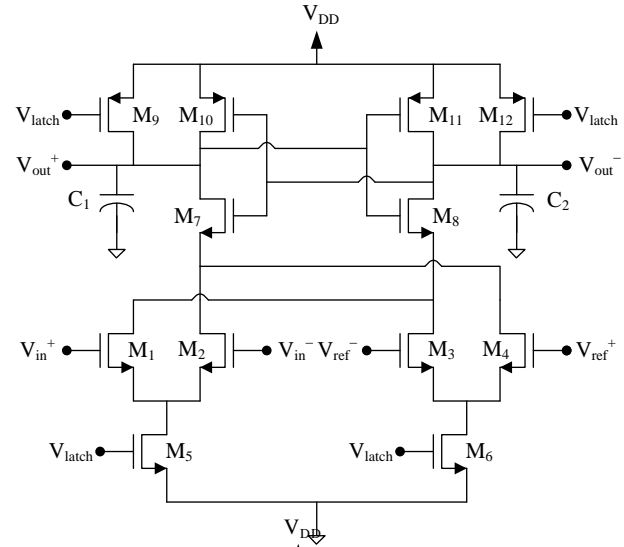  Clocked Comparator with Regenerative Feedback



V_{REF} denotes V_{DACK} in these figures

Flash ADC Summary

Flash ADC

Very fast

Simple structure

Usually Clocked

Bubble Removal Important

Seldom over 6 or 7 bits of resolution


- Flash ADC has some really desirable properties (simple and fast)
- Wouldn't it be nice if we could derive most of the benefits of the FLASH ADC without the major limitations

To be practical at higher resolution, must address the major limitation of the FLASH ADC

Major Limitation of FLASH ADC at higher resolutions?

Number of comparators increases geometrically --- 2^n

Two-Step Flash ADC

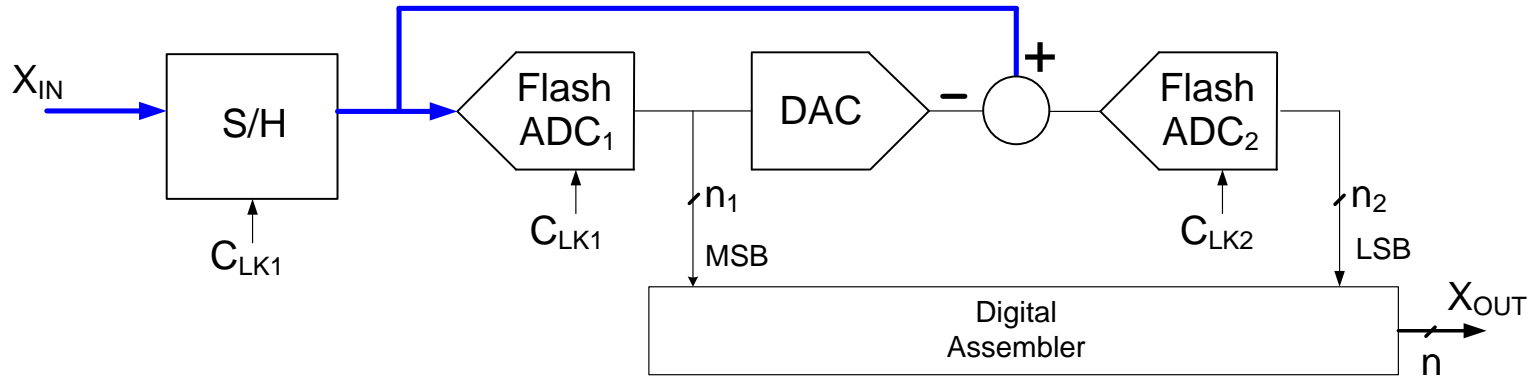

Can operate asynchronously (either after first S/H or even w/o S/H)

Reduces the number of comparators significantly

Reduces complexity of thermometer to binary converter

Residue signal at input to second Flash ADC is small


Difference block is a linear module that must be accurate

Have added a DAC that must have accuracy at the overall ADC resolution level

Speed of difference amplifier and DAC limit speed of ADC


Sequential clocking of ADC₁ and ADC₂ limits speed of ADC

Two-Step Flash ADC with Interstage Gain

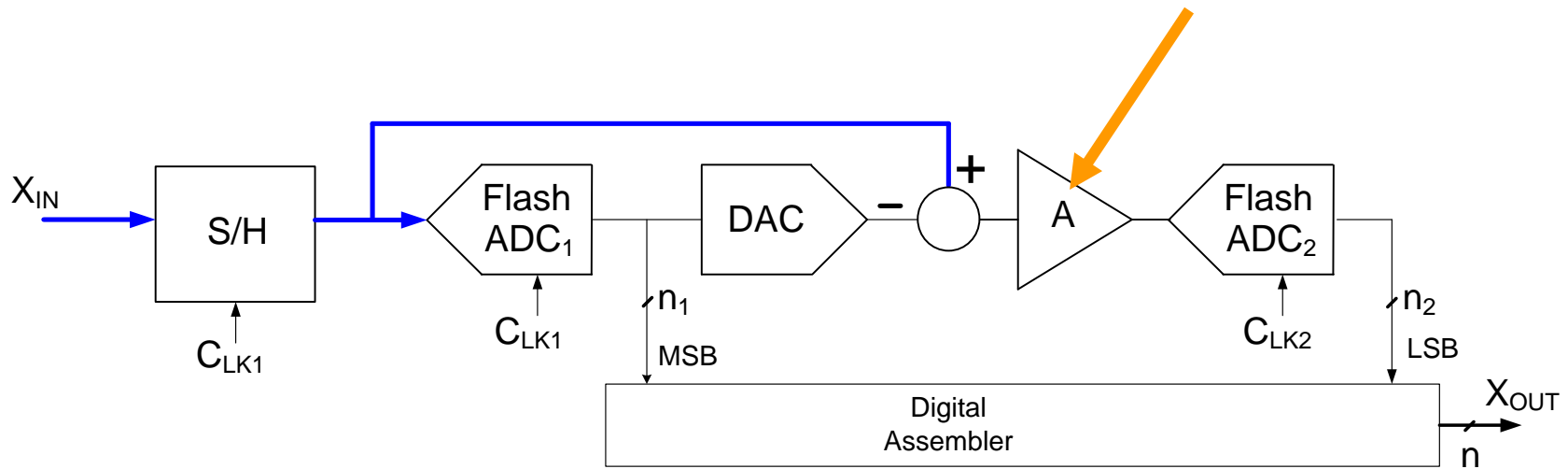



- Increases level of signals into second Flash ADC
(reducing offset concerns by a factor of A)
- Speed of A of concern
- Considerable power dissipation in A amplifier
- Complexity is increasing significantly !

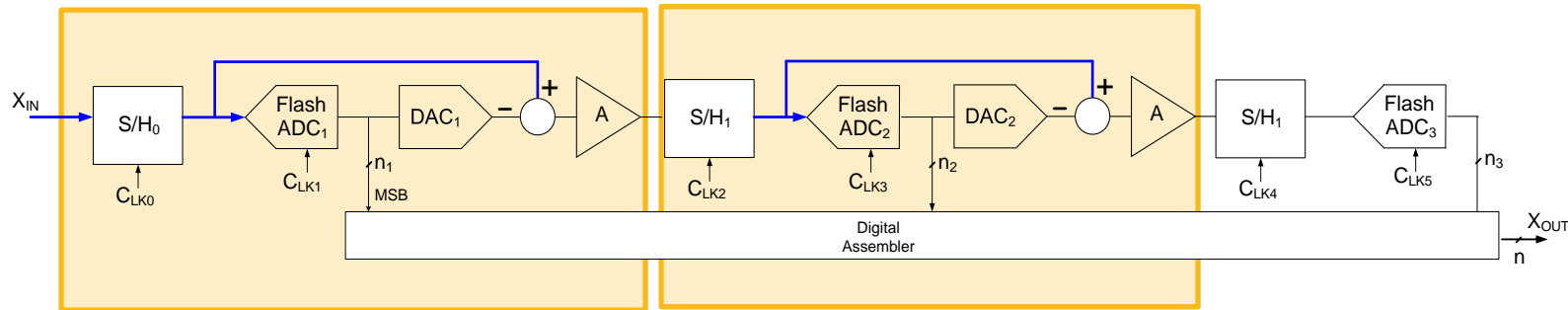Three-Step Flash ADC with Interstage Gain and S/H





- Further reduces number of comparators needed!
- Even more complexity!
- But appears first two stages perform identical operations (if $n_1=n_2$)
- S/H_1 frees first stage to take another sample during second stage conversion
- S/H_2 frees second stage to take another sample during third stage conversion
- **This has a pipelining capability !**

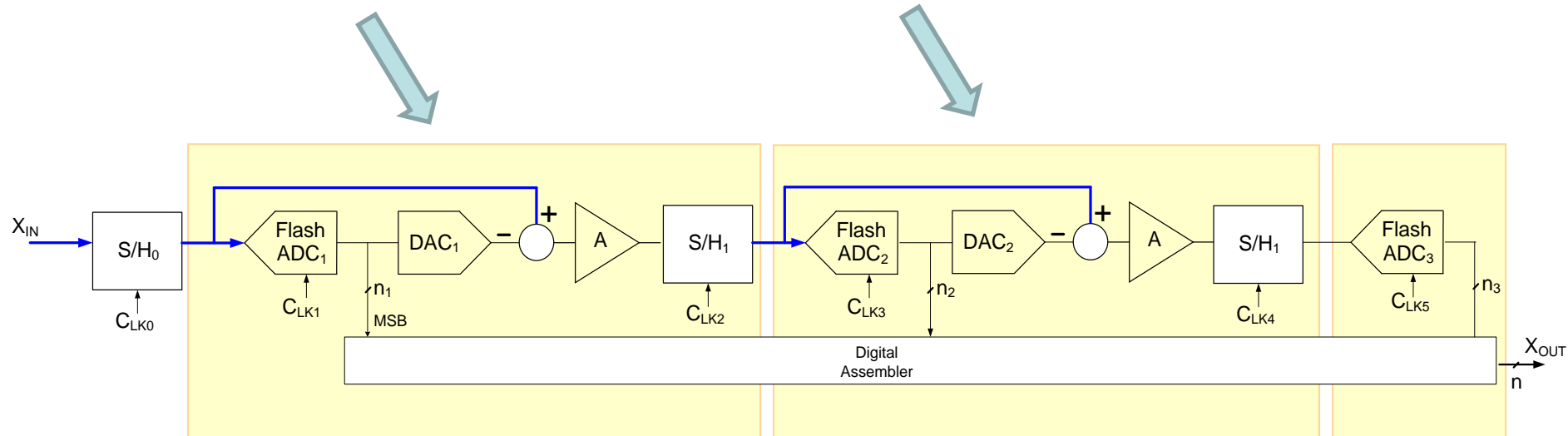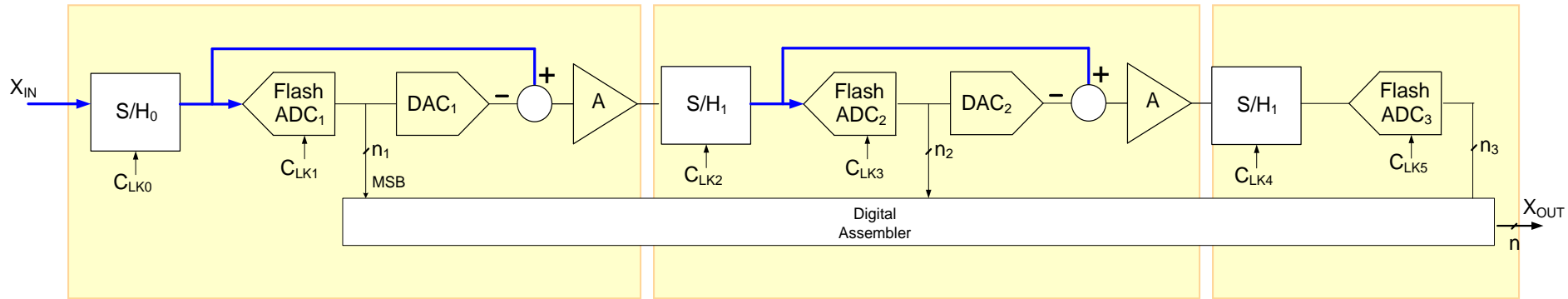Three-Step Flash ADC with Interstage Gain and S/H




Same structure, different grouping!

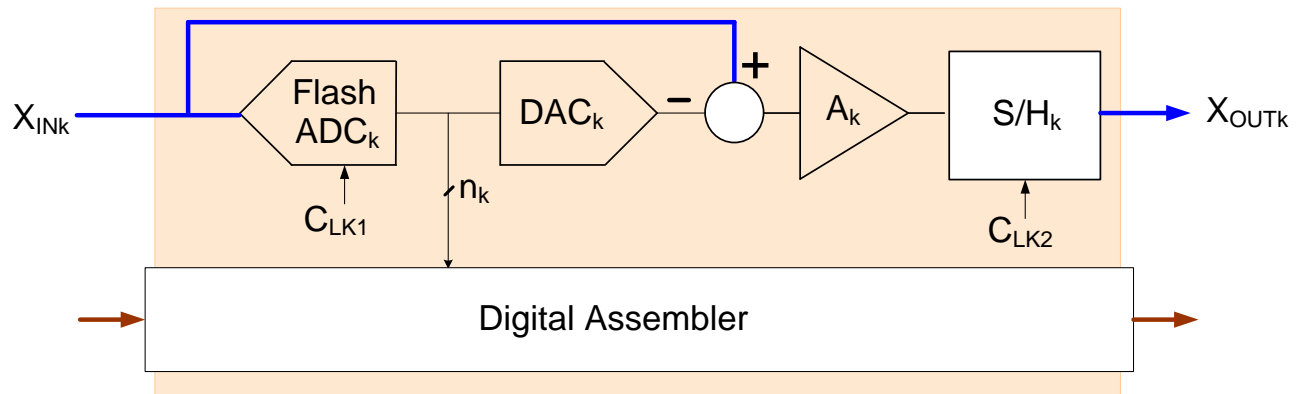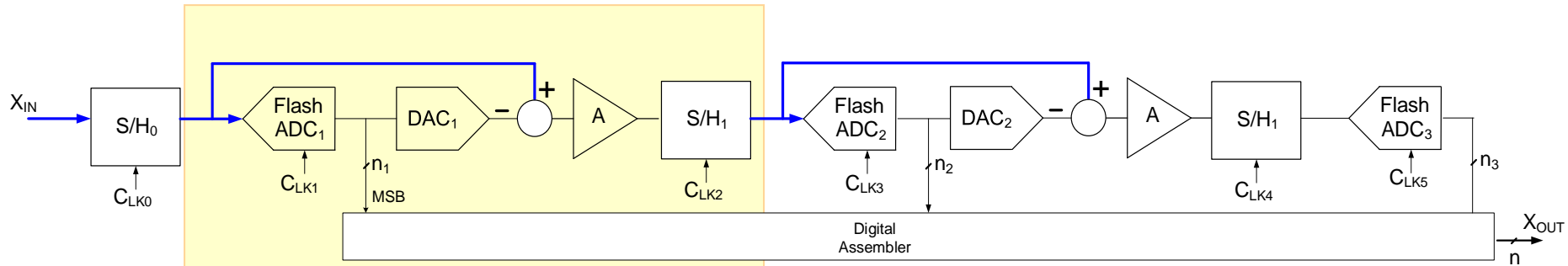
Three-Step Flash ADC with Interstage Gain




Pipelined ADC

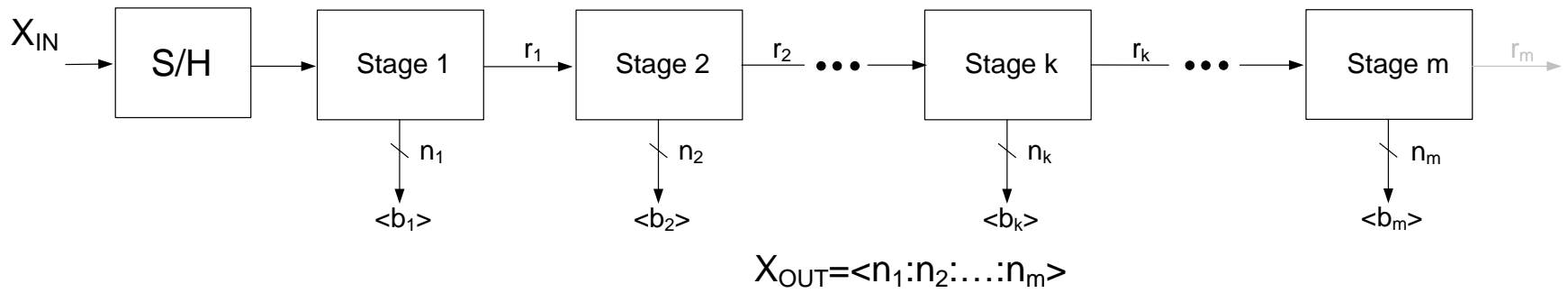


Pipelined ADC

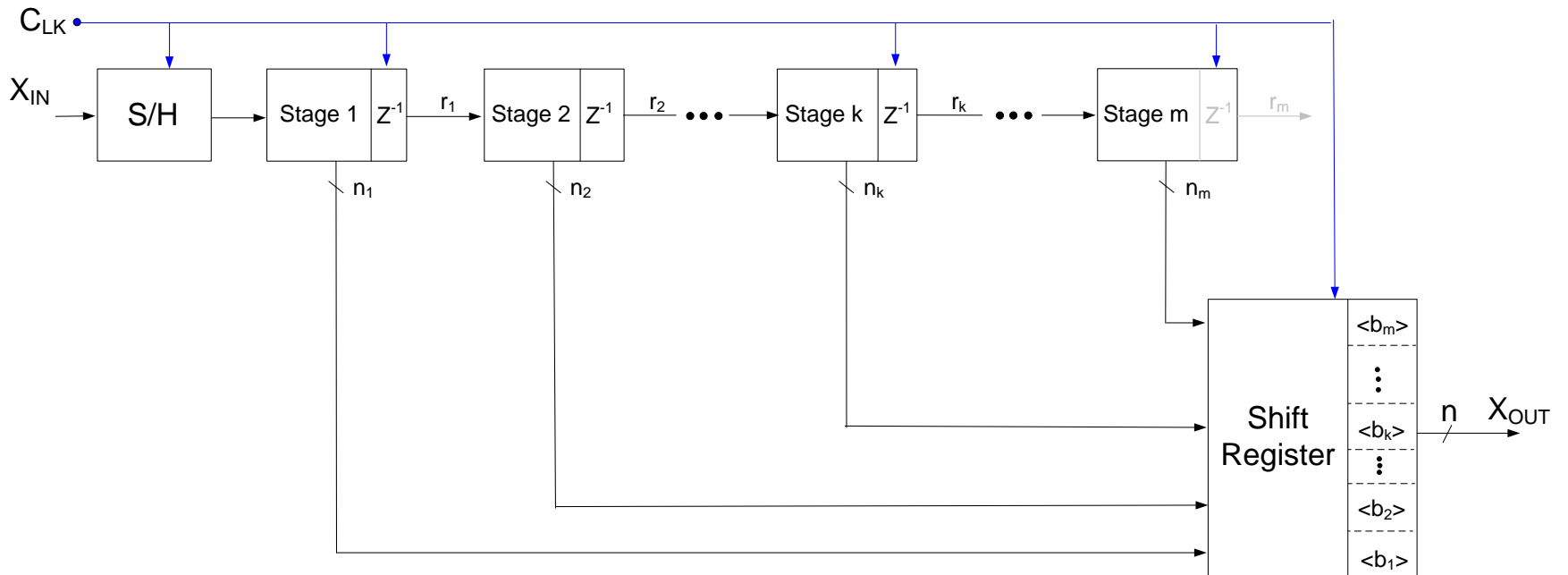

Pipelined ADC Stage k

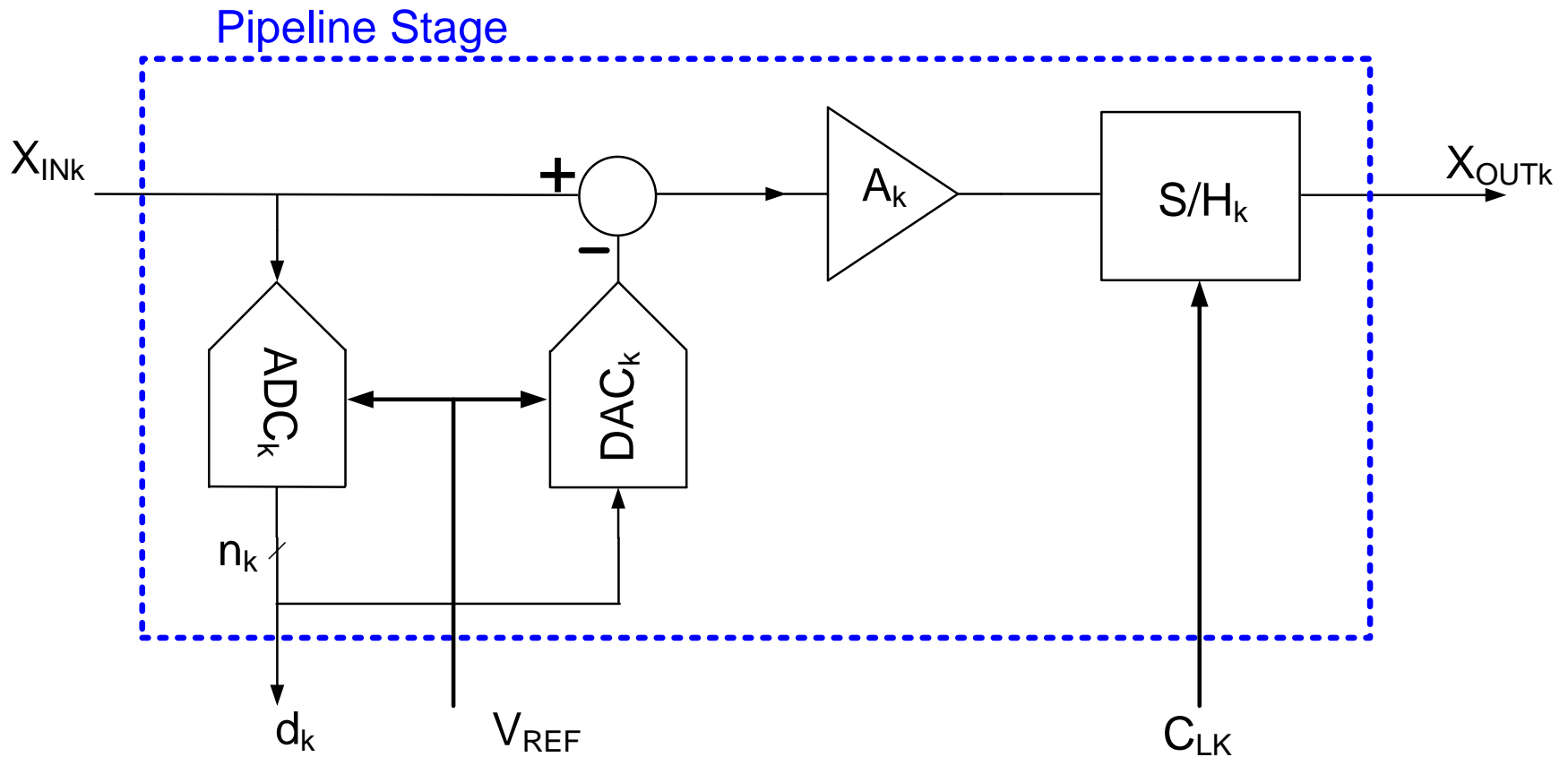


Pipelined ADC Stage k

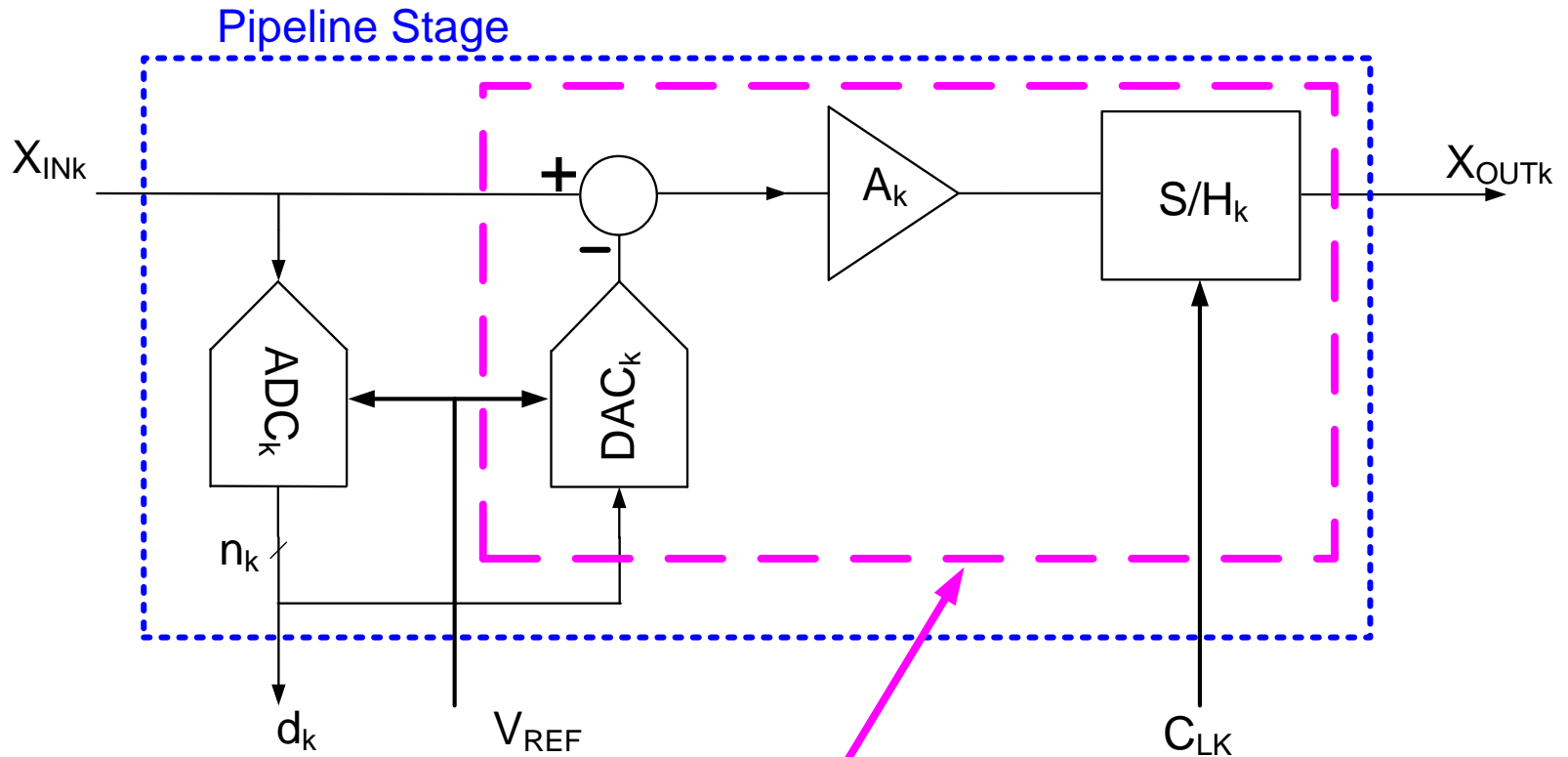

Usually Realized as
Single SC Block


Pipelined ADC Stage k

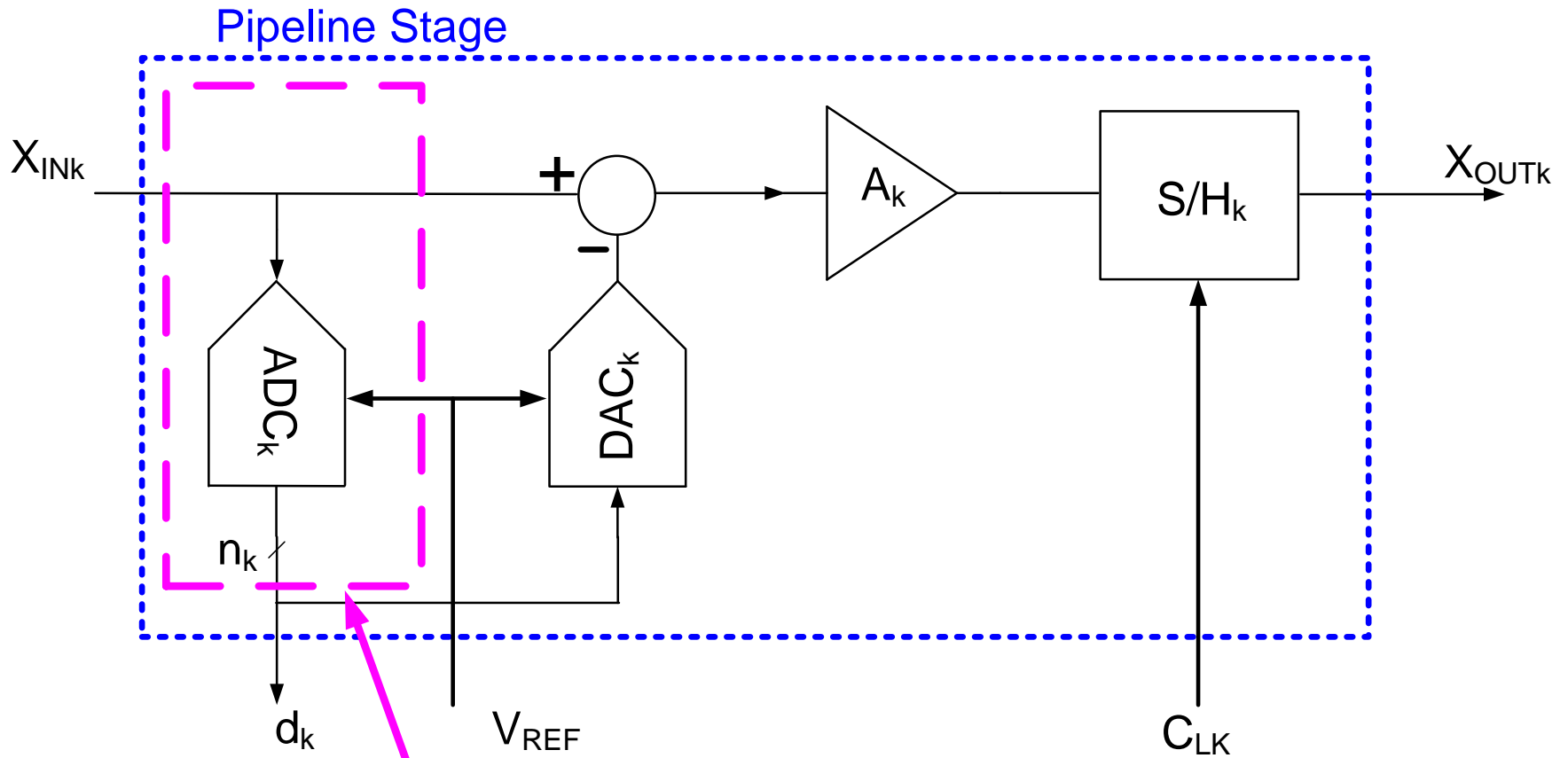

Usually Realized as Flash ADC
(often simple comparator if $n_k=1$)

Pipelined ADC Stage k

Pipeline Stage for 1 bit/stage

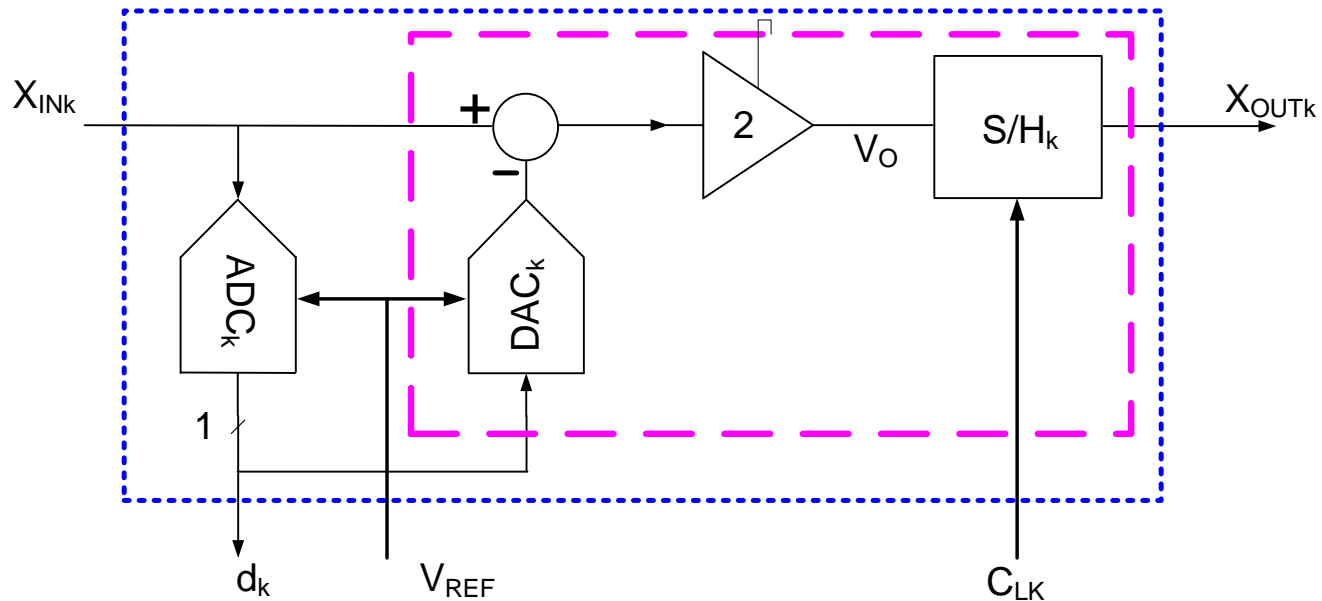


Assuming $-\frac{V_{REF}}{2} < V_{IN} < \frac{V_{REF}}{2}$



$$V_O = \begin{cases} 2V_{IN} + \frac{V_{REF}}{2} & V_{IN} < 0 \\ 2V_{IN} - \frac{V_{REF}}{2} & V_{IN} > 0 \end{cases}$$

Transfer Characteristics for 1 bit/stage

 
$$V_O = \begin{cases} 2V_{IN} + \frac{V_{REF}}{2} & V_{IN} < 0 \\ 2V_{IN} - \frac{V_{REF}}{2} & V_{IN} > 0 \end{cases}$$




Consider the following circuit

 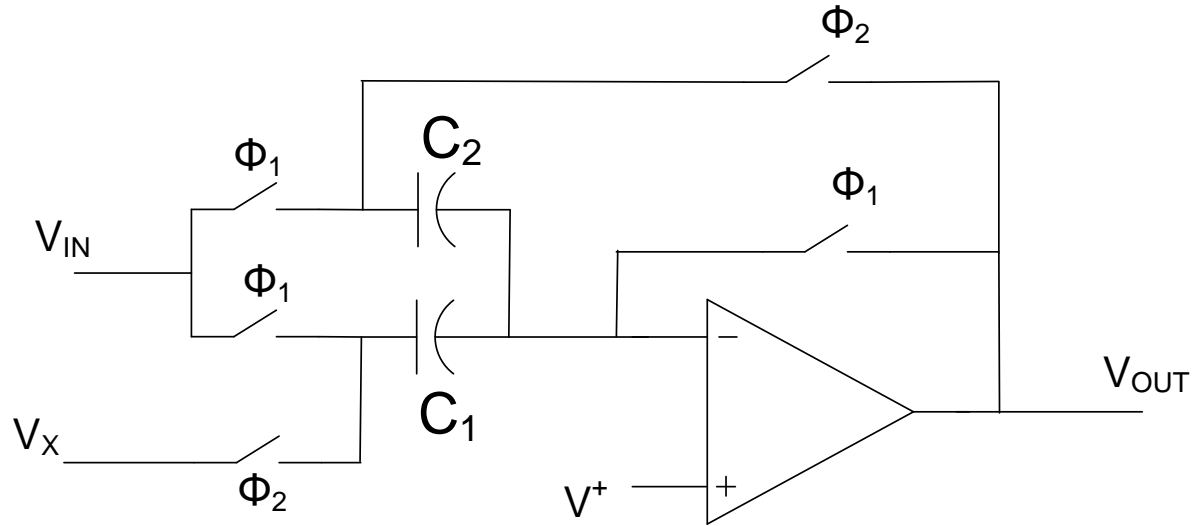

Consider the following circuit

 


During Φ_1

 

Consider the following circuit


During Φ_1

 


$$Q_1 = C_1 (V_{IN} - V^+)$$

$$Q_2 = C_2 (V_{IN} - V^+)$$

Consider the following circuit

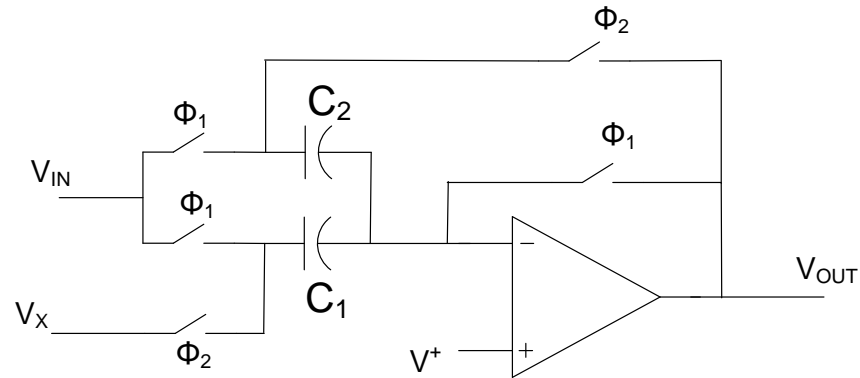


During Φ_2

 

Consider the following circuit

During Φ_2

 

$$Q_1 = C_1 (V_{\text{IN}} - V^+)$$

$$Q_2 = C_2 (V_{\text{IN}} - V^+)$$

Define Q_{1T} to be the charge transferred from C_1 during phase Φ_2


$$Q_{1T} = C_1 (V_{\text{IN}} - V^+) - C_1 (V_X - V^+) = C_1 (V_{\text{IN}} - V_X)$$

Define Q_{2F} to be the total charge on C_2 during phase Φ_2

$$Q_{2F} = Q_2 + Q_{1T} = C_2 (V_{\text{IN}} - V^+) + C_1 (V_{\text{IN}} - V_X) = (C_1 + C_2) V_{\text{IN}} - C_2 V^+ - C_1 V_X$$

Consider the following circuit

During Φ_2

 


$$Q_{2F} = (C_1 + C_2)V_{IN} - C_2V^+ - C_1V_X$$

$$V_{C2F} = \frac{Q_{2F}}{C_2} = \left(1 + \frac{C_1}{C_2}\right)V_{IN} - V^+ - \frac{C_1}{C_2}V_X$$

$$V_{OUTF} = V_{C2F} + V^+ = \left(1 + \frac{C_1}{C_2}\right)V_{IN} - \frac{C_1}{C_2}V_X$$

Consider the following circuit

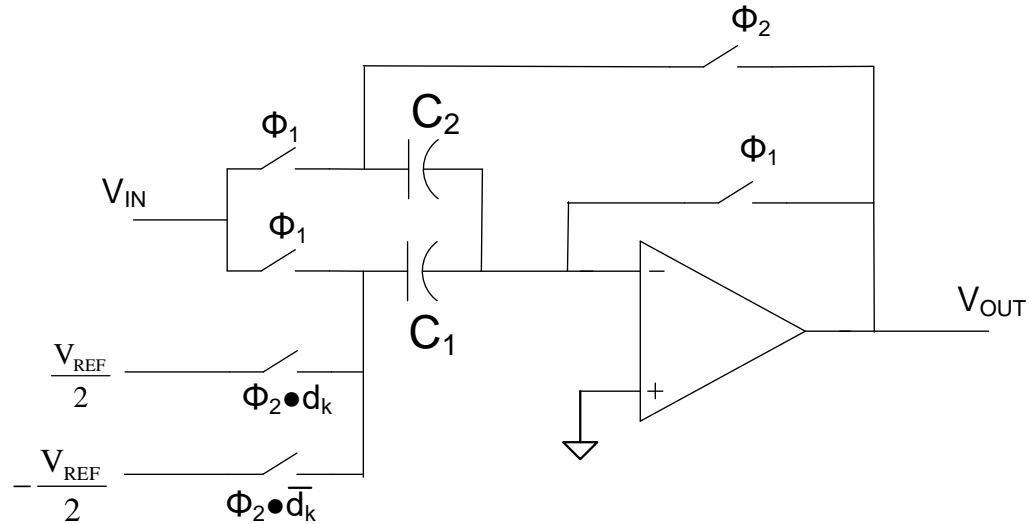


$$V_{OUTF} = \left(1 + \frac{C_1}{C_2}\right) V_{IN} - \frac{C_1}{C_2} V_X$$

If $C_1=C_2=C$ and $V_X = -\frac{V_{REF}}{2}$

$$V_{OUTF} = 2V_{IN} + \frac{V_{REF}}{2}$$

Consider the following circuit

 


$$V_{OUTF} = \left(1 + \frac{C_1}{C_2}\right) V_{IN} - \frac{C_1}{C_2} V_X$$

Likewise

$$\text{If } C_1 = C_2 = C \text{ and } V_X = \frac{V_{REF}}{2}$$



$$V_{OUTF} = 2V_{IN} - \frac{V_{REF}}{2}$$

Observe

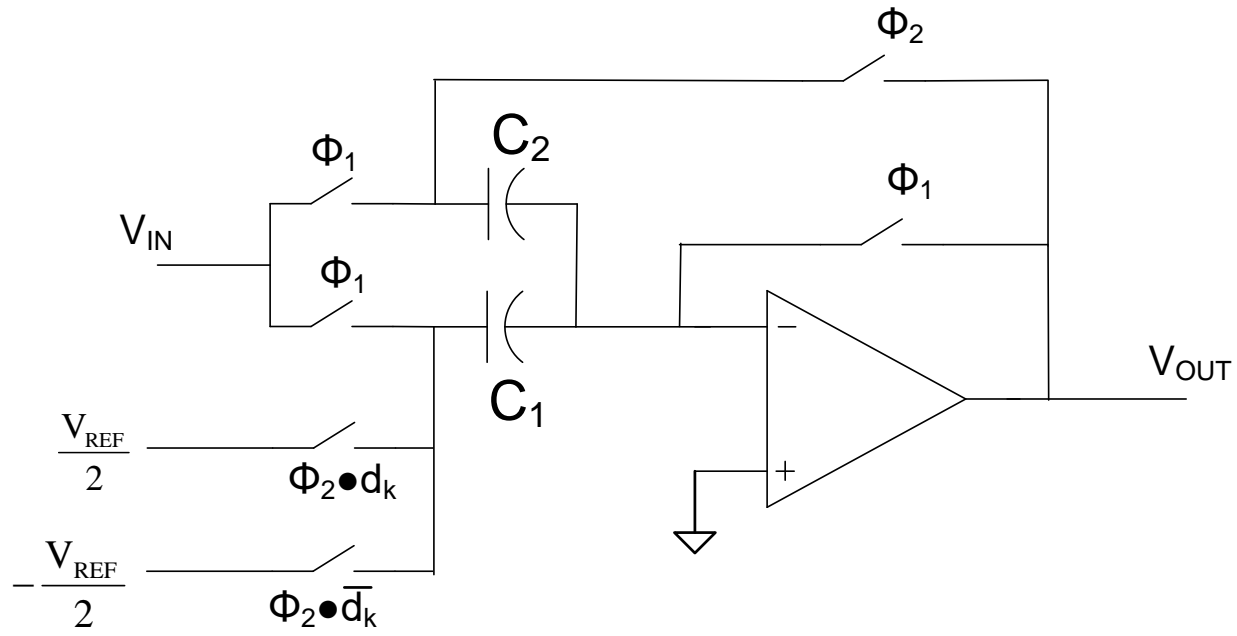



$$V_O = \begin{cases} 2V_{IN} + \frac{V_{REF}}{2} & V_{IN} < 0 \\ 2V_{IN} - \frac{V_{REF}}{2} & V_{IN} > 0 \end{cases}$$

1-bit/Stage Pipeline Implementation

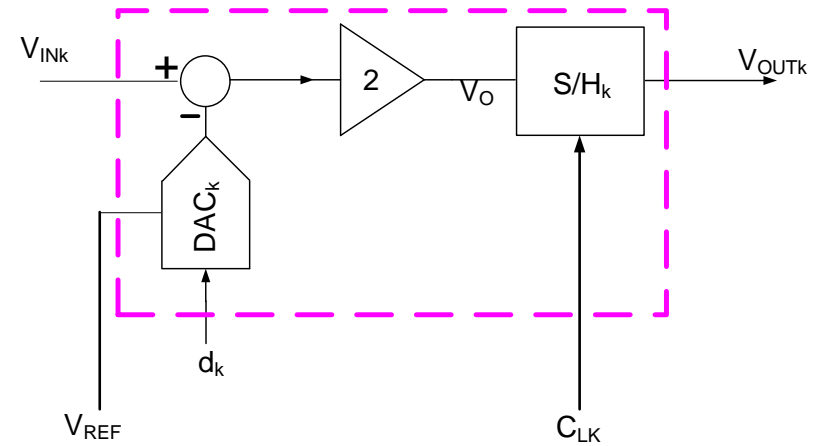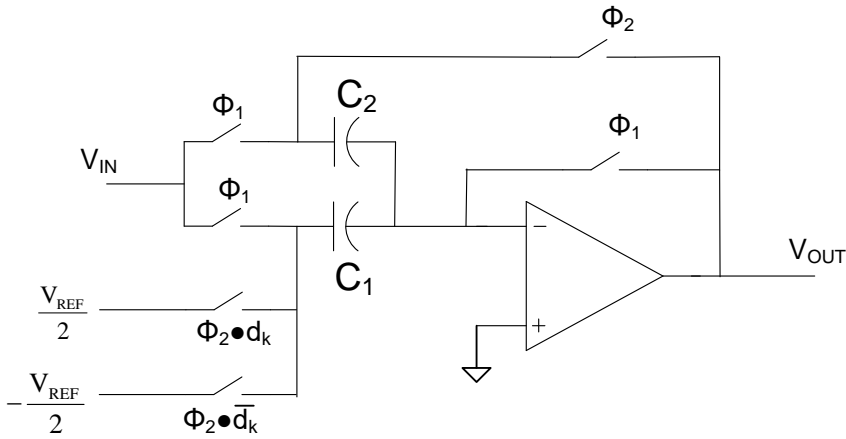


$$V_O = \begin{cases} 2V_{IN} + \frac{V_{REF}}{2} & V_{IN} < 0 \\ 2V_{IN} - \frac{V_{REF}}{2} & V_{IN} > 0 \end{cases}$$

1-bit/Stage Pipeline Implementation

  

Pipelined ADC Stage k

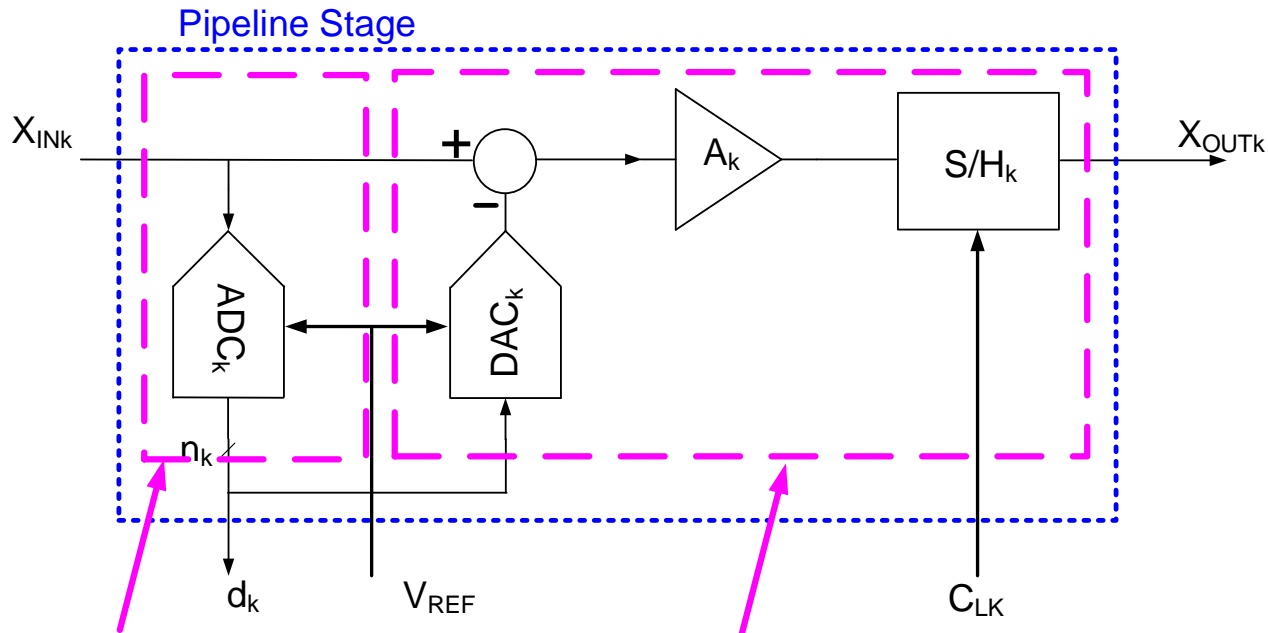

Have implementation
with simple comparator



Have implementation
with Single SC Block

- Have shown simple implementation with 1-bit/stage structure
- Implementations with 2-bits/stage or 3-bits/stage also straightforward

Typical SC Pipeline Stage

For 2 bits/stage (Digital Assembler not shown)

Assuming $0 < V_{IN} < V_{REF}$

 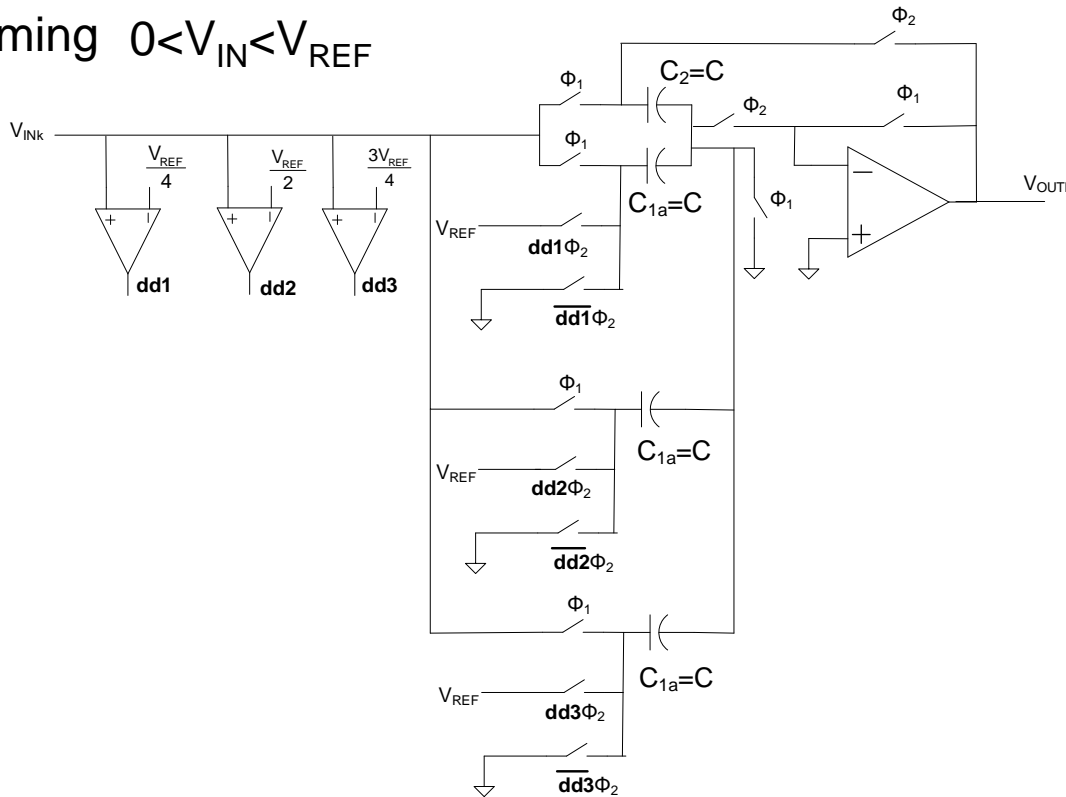


Gain = 4

$$V_{OUT} = V_{IN} \left(1 + \frac{C_{1a} + C_{1b} + C_{1c}}{C_2} \right) - \left(d_{d1} \left(\frac{C_{1a}}{C_2} \right) + d_{d2} \left(\frac{C_{1b}}{C_2} \right) + d_{d3} \left(\frac{C_{1c}}{C_2} \right) \right) V_{REF} \implies V_{OUTk} = 4 V_{INk} - (d_{dd1} + d_{dd2} + d_{dd3}) V_{REF}$$

- Directly use thermometer code outputs
- Can be extended to more bits/stage
- Accurate gain possible with good layout

Pipelined ADC

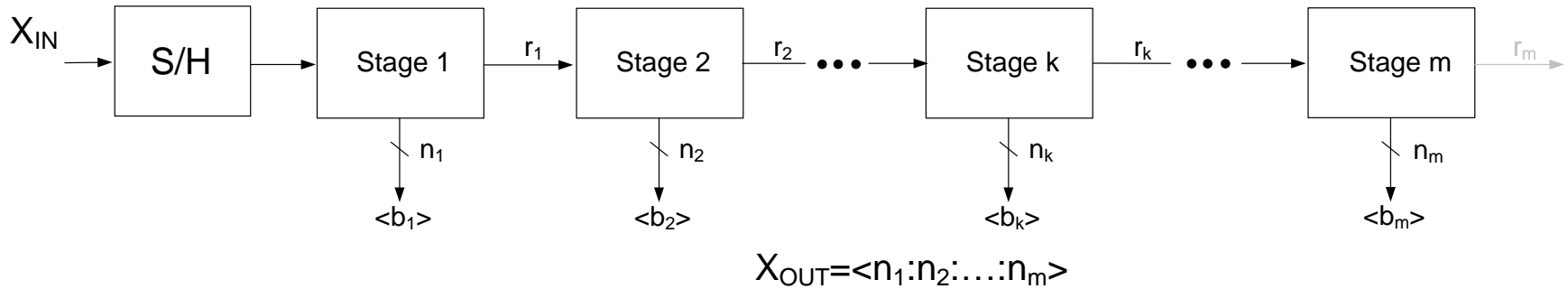

- Pipelined structure is widely used
- More than one bit/stage is often used
- Optimal number of bits/stage still an area of debate
- Conceptually can simply design one stage and then copy/paste to increase resolution
- Accuracy (and correspondingly power) in latter stages can be dramatically reduced
- Most power consumed in op amps
- Power dominantly allocated to S/H and MSB stages



Stay Safe and Stay Healthy !

End of Lecture 36