


EE 435

Lecture 39

ADC Design


Review from Last Lecture

Data Converter Type Chart

 


Review from Last Lecture

Nyquist Rate Usage Structures

 

Flash ADC

 

Asynchronous operation (benefit or liability?)

Vulnerable to missing codes

High number of comparators needed (for large n)

R-string area requires considerable area and source of INL limitations

Offset voltage of comparators of concern

Simultaneous switching of large number of comparators can cause supply glitches

Large parasitic capacitance on V_{IN} pin

Bubbles in output can occur

Metastability an issue

Power dissipation can be large

Flash ADC Summary

Flash ADC

Very fast

Simple structure

Usually Clocked

Bubble Removal Important

Seldom over 6 or 7 bits of resolution

- Flash ADC has some really desirable properties (simple and fast)
- Wouldn't it be nice if we could derive most of the benefits of the FLASH ADC without the major limitations


To be practical at higher resolution, must address the major limitation of the FLASH ADC

Major Limitation of FLASH ADC at higher resolutions?

Number of comparators increases geometrically --- 2^n

Review from Last Lecture


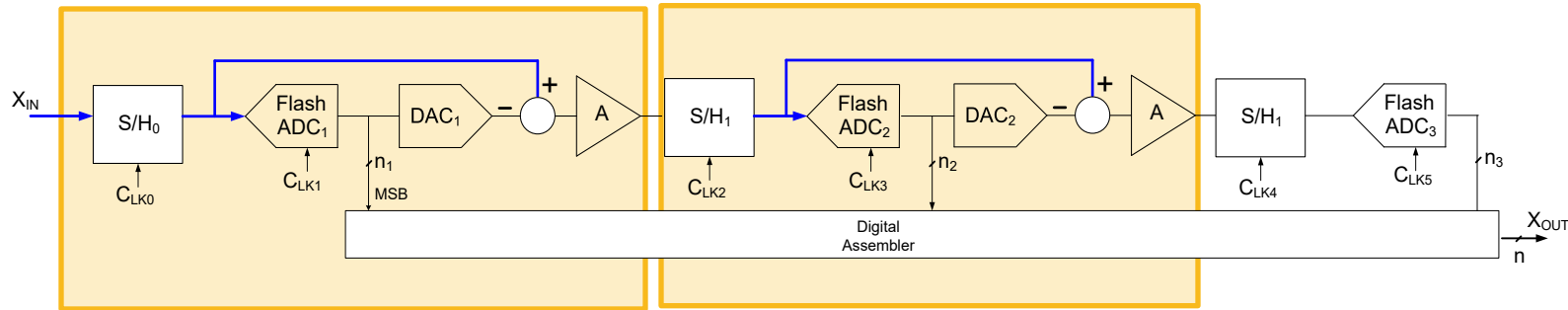
Three-Step Flash ADC with Interstage Gain and S/H



- Further reduces number of comparators needed!
- Even more complexity!
- But appears first two stages perform identical operations (if $n_1 = n_2$)
- S/H_1 frees first stage to take another sample during second stage conversion
- S/H_2 frees second stage to take another sample during third stage conversion
- **This has a pipelining capability !**


Review from Last Lecture

 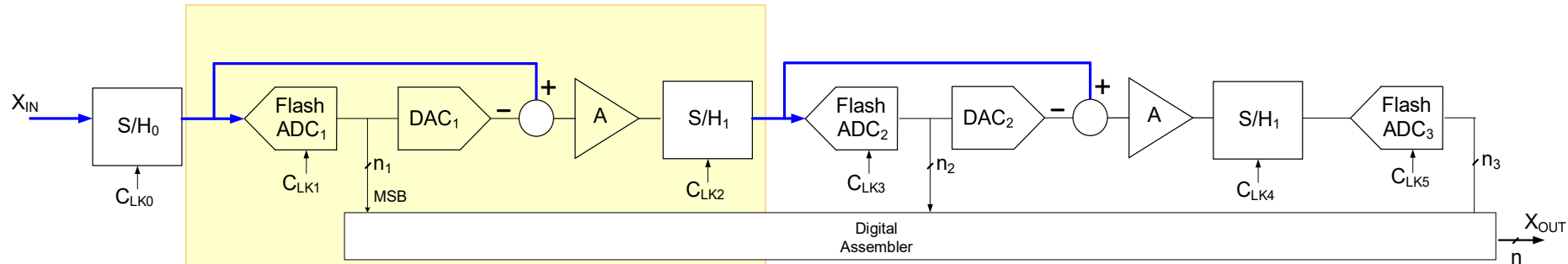Three-Step Flash ADC with Interstage Gain




Review from Last Lecture


Pipelined ADC

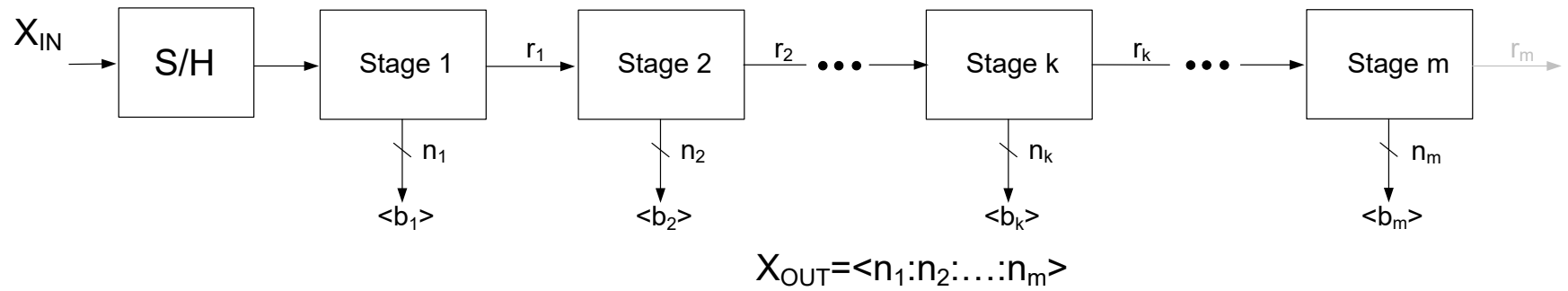


Pipelined ADC

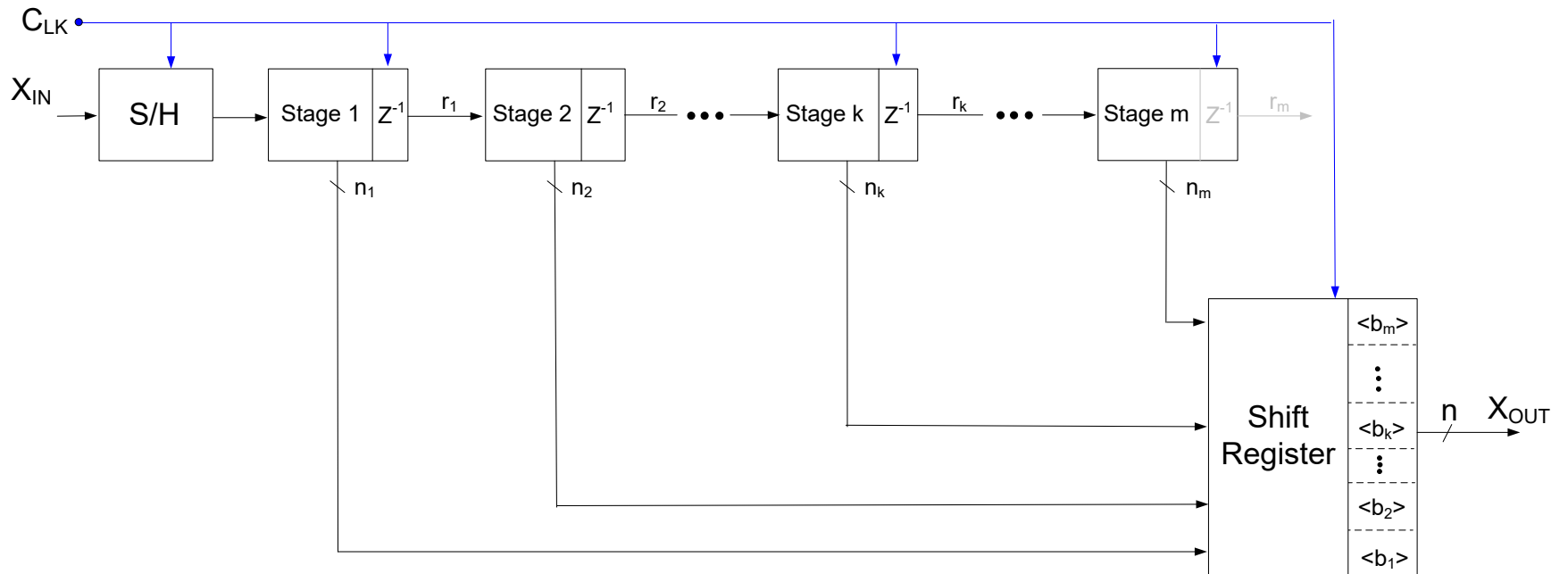

Pipelined ADC Stage k

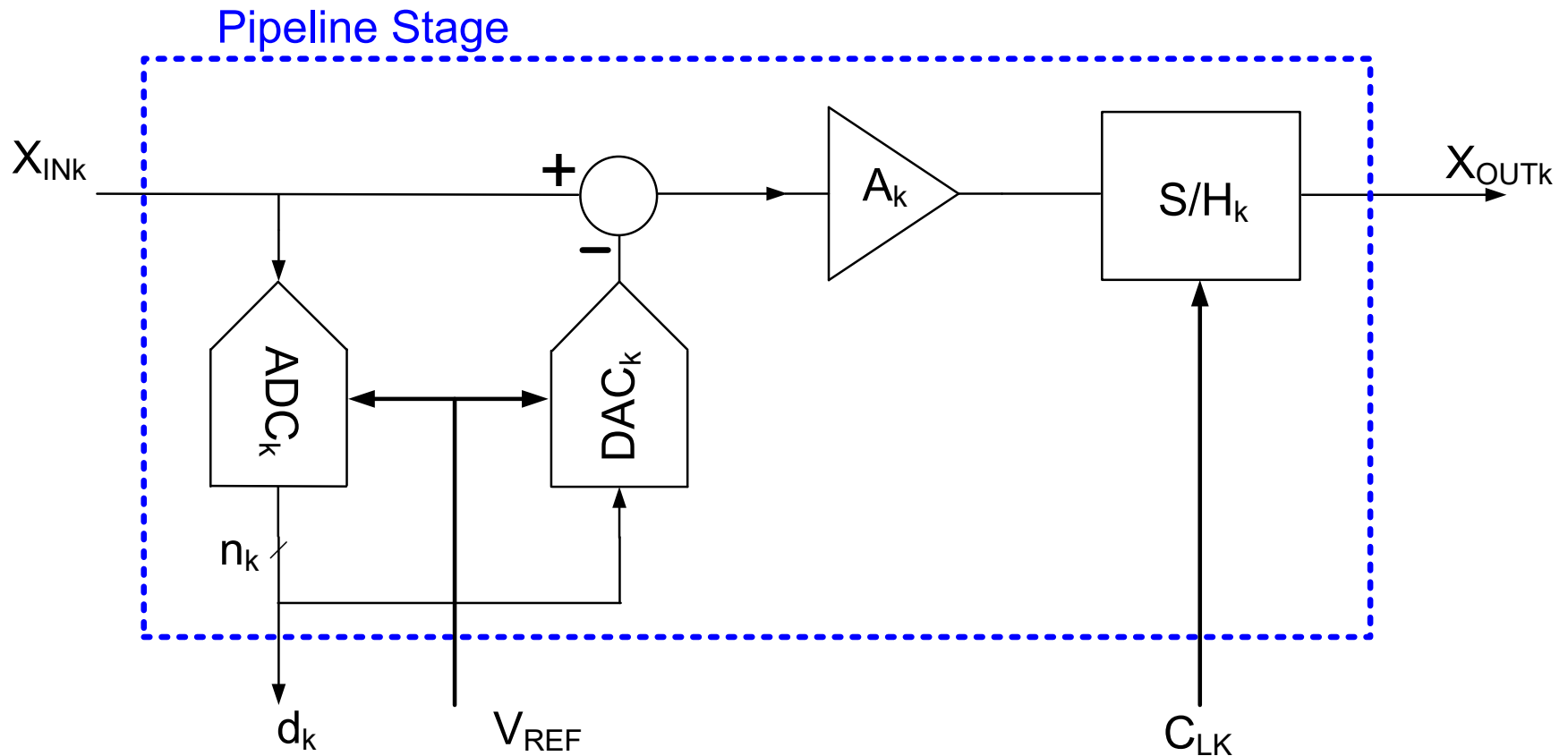


Pipelined ADC Stage k

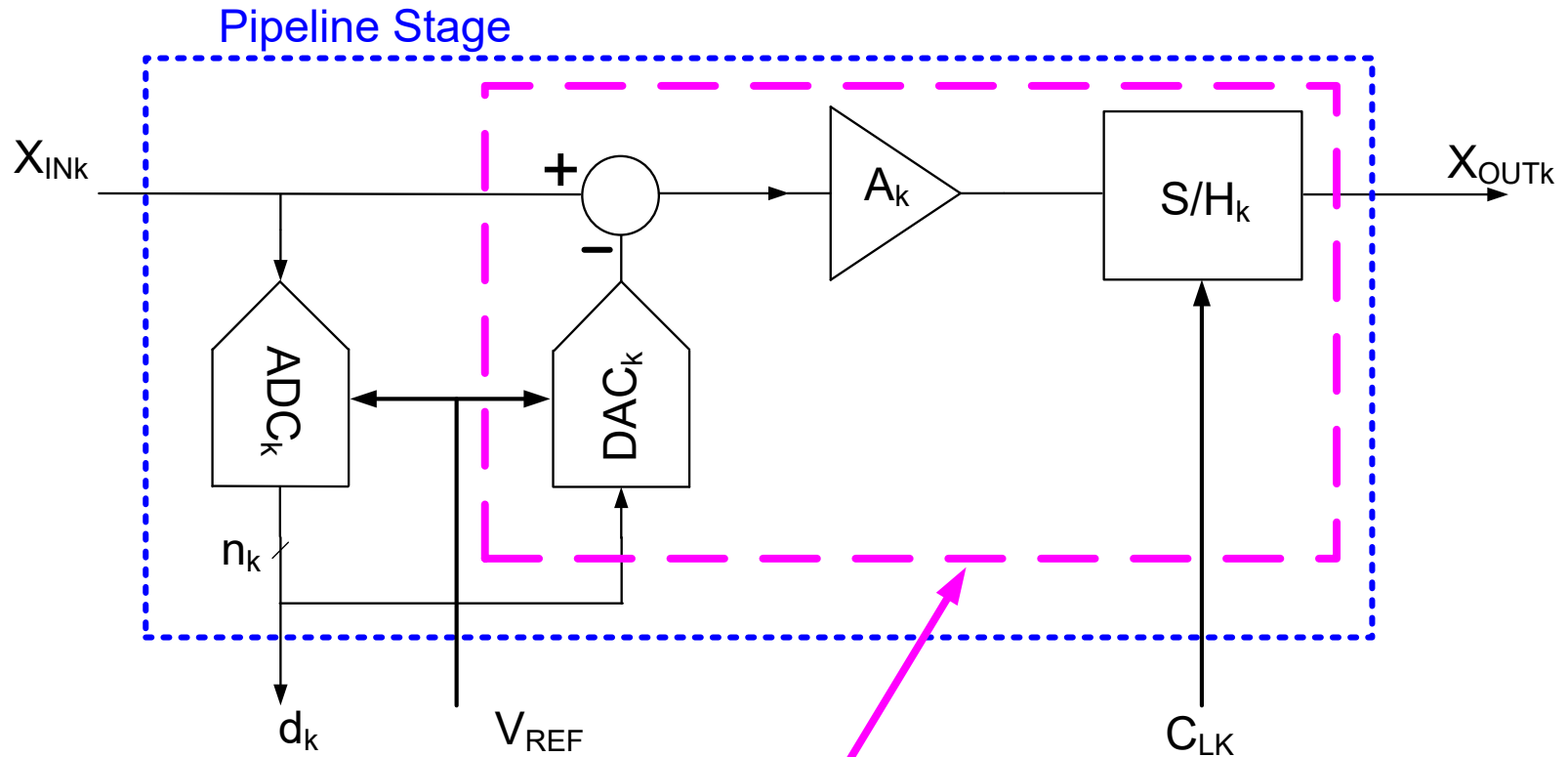

Usually Realized as
Single SC Block


Pipelined ADC Stage k

 

Usually Realized as Flash ADC
(often simple comparator if $n_k=1$)

Pipelined ADC Stage k

Pipeline Stage for 1 bit/stage

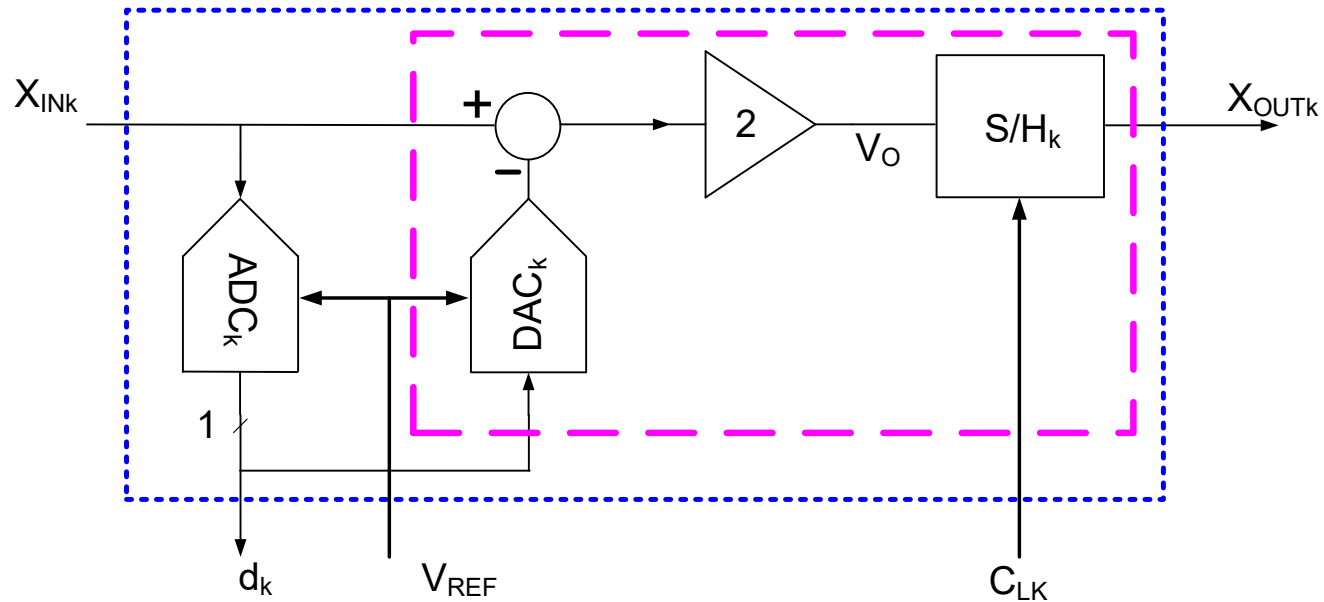


Assuming $-\frac{V_{REF}}{2} < V_{IN_k} < \frac{V_{REF}}{2}$



$$V_{Ok} = \begin{cases} 2V_{IN_k} + \frac{V_{REF}}{2} & V_{IN_k} < 0 \\ 2V_{IN_k} - \frac{V_{REF}}{2} & V_{IN_k} > 0 \end{cases}$$

Transfer Characteristics for 1 bit/stage

 
$$V_{O_k} = \begin{cases} 2V_{IN_k} + \frac{V_{REF}}{2} & V_{IN_k} < 0 \\ 2V_{IN_k} - \frac{V_{REF}}{2} & V_{IN_k} > 0 \end{cases}$$




Consider the following circuit

  

Consider the following circuit

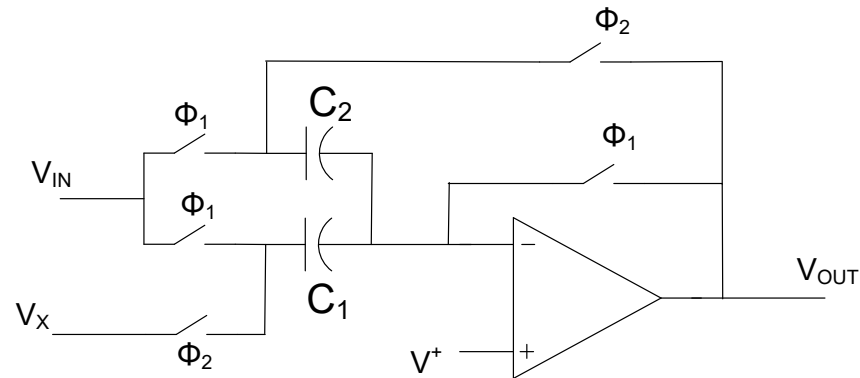


During Φ_1

 

Consider the following circuit


During Φ_1

 


$$Q_1 = C_1 (V_{IN} - V^+)$$

$$Q_2 = C_2 (V_{IN} - V^+)$$

Consider the following circuit

 


During Φ_2

 

Consider the following circuit

During Φ_2

 

$$Q_1 = C_1 (V_{IN} - V^+)$$

$$Q_2 = C_2 (V_{IN} - V^+)$$

Define Q_{1T} to be the charge transferred from C_1 during phase Φ_2


$$Q_{1T} = C_1 (V_{IN} - V^+) - C_1 (V_X - V^+) = C_1 (V_{IN} - V_X)$$

Define Q_{2F} to be the total charge on C_2 during phase Φ_2

$$Q_{2F} = Q_2 + Q_{1T} = C_2 (V_{IN} - V^+) + C_1 (V_{IN} - V_X) = (C_1 + C_2) V_{IN} - C_2 V^+ - C_1 V_X$$

Consider the following circuit

During Φ_2

 


$$Q_{2F} = (C_1 + C_2)V_{IN} - C_2V^+ - C_1V_X$$

$$V_{C2F} = \frac{Q_{2F}}{C_2} = \left(1 + \frac{C_1}{C_2}\right)V_{IN} - V^+ - \frac{C_1}{C_2}V_X$$

$$V_{OUTF} = V_{C2F} + V^+ = \left(1 + \frac{C_1}{C_2}\right)V_{IN} - \frac{C_1}{C_2}V_X$$

Consider the following circuit

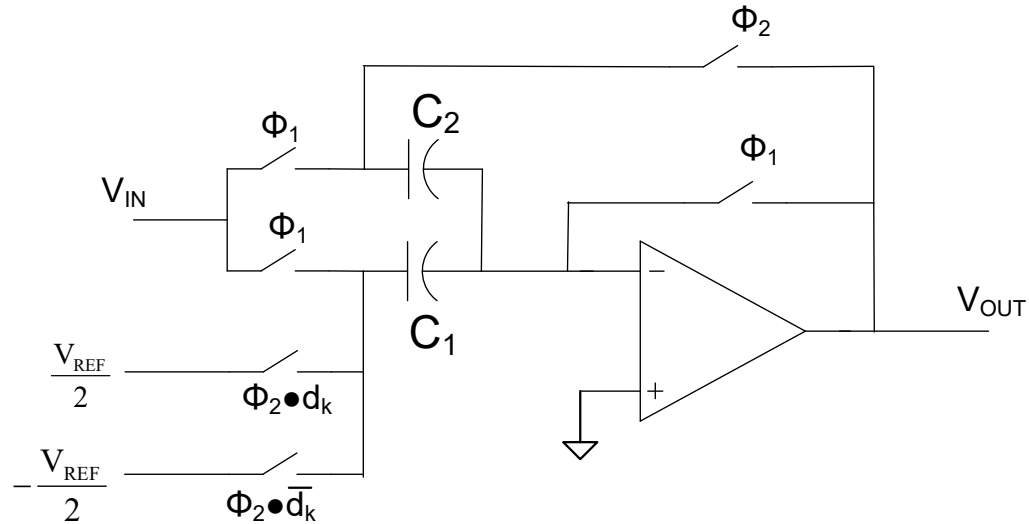


$$V_{OUTF} = \left(1 + \frac{C_1}{C_2}\right) V_{IN} - \frac{C_1}{C_2} V_X$$

If $C_1=C_2=C$ and $V_X = -\frac{V_{REF}}{2}$

$$V_{OUTF} = 2V_{IN} + \frac{V_{REF}}{2}$$

Consider the following circuit

 


$$V_{OUTF} = \left(1 + \frac{C_1}{C_2}\right) V_{IN} - \frac{C_1}{C_2} V_X$$

Likewise

$$\text{If } C_1 = C_2 = C \text{ and } V_X = \frac{V_{REF}}{2}$$

$$V_{OUTF} = 2V_{IN} - \frac{V_{REF}}{2}$$




Observe

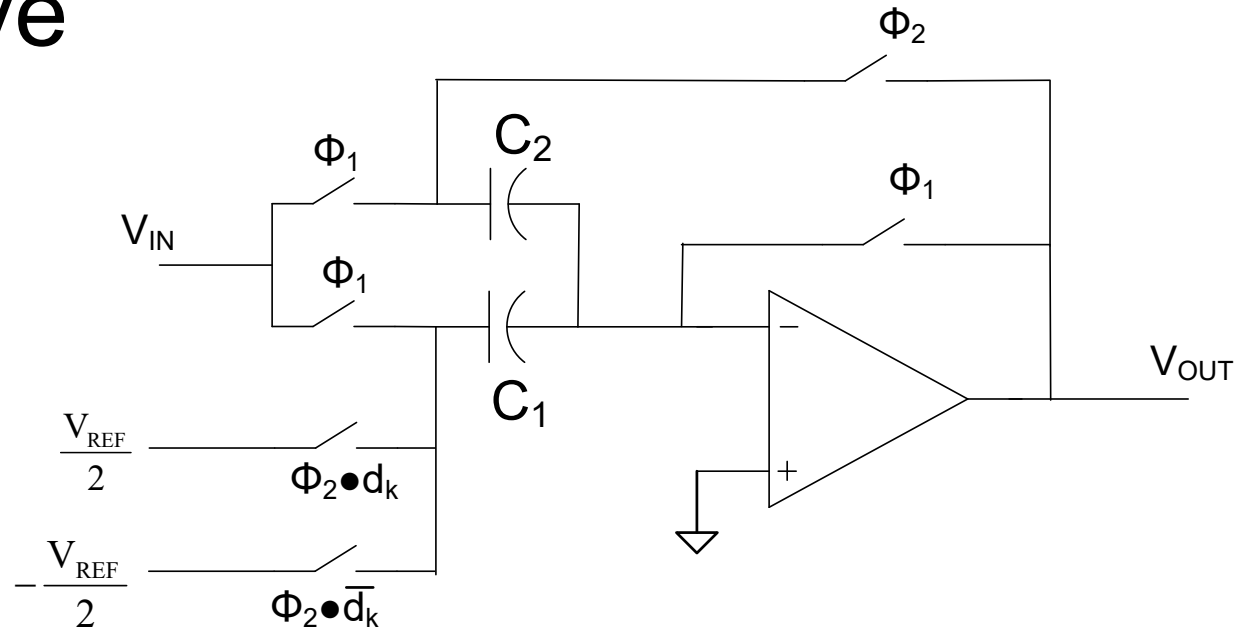

$$V_O = \begin{cases} 2V_{IN} + \frac{V_{REF}}{2} & V_{IN} < 0 \\ 2V_{IN} - \frac{V_{REF}}{2} & V_{IN} > 0 \end{cases}$$


This is exactly what is needed for the transfer characteristics needed for each stage in a 1 bit/stage pipelined ADC

1-bit/Stage Pipeline Implementation

  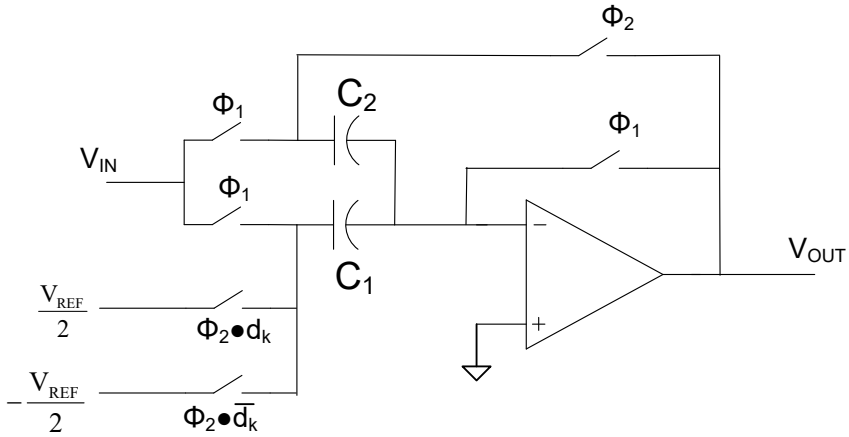


$$V_O = \begin{cases} 2V_{IN} + \frac{V_{REF}}{2} & V_{IN} < 0 \\ 2V_{IN} - \frac{V_{REF}}{2} & V_{IN} > 0 \end{cases}$$

1-bit/Stage Pipeline Implementation

 

Pipelined ADC Stage k

 

Have implementation
with simple comparator



Have implementation
with Single SC Block

- Have shown simple implementation with 1-bit/stage structure
- Implementations with 2-bits/stage or 3-bits/stage also straightforward

Typical SC Pipeline Stage

For 2 bits/stage (Digital Assembler not shown)

Assuming $0 < V_{IN} < V_{REF}$

  


Gain = 4

$$V_{OUT} = V_{IN} \left(1 + \frac{C_{1a} + C_{1b} + C_{1c}}{C_2} \right) - \left(d_{d1} \left(\frac{C_{1a}}{C_2} \right) + d_{d2} \left(\frac{C_{1b}}{C_2} \right) + d_{d3} \left(\frac{C_{1c}}{C_2} \right) \right) V_{REF} \longrightarrow V_{OUTk} = 4 V_{INk} - (d_{dd1} + d_{dd2} + d_{dd3}) V_{REF}$$

- Directly use thermometer code outputs
- Can be extended to more bits/stage
- Accurate gain possible with good layout


Pipelined ADC

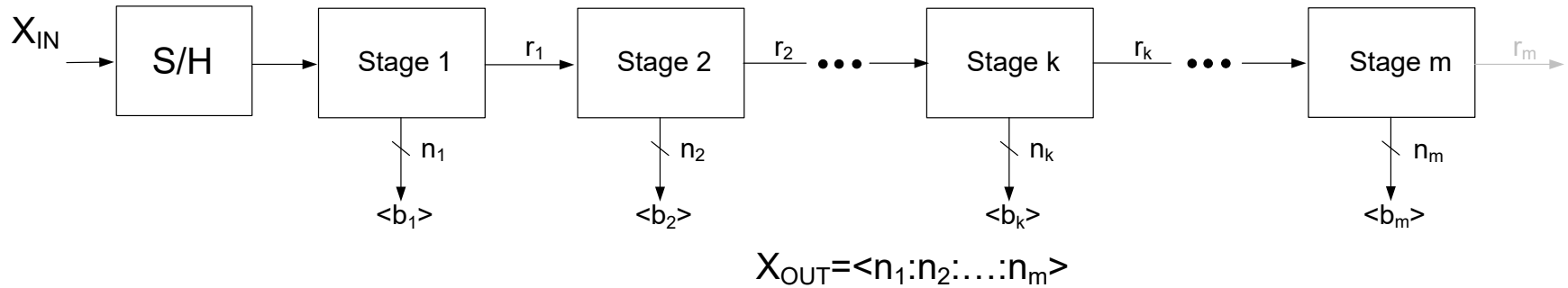

- Pipelined structure is widely used
- More than one bit/stage is often used
- Optimal number of bits/stage still an area of debate
- Conceptually can simply design one stage and then copy/paste to increase resolution
- Accuracy (and correspondingly power) in latter stages can be dramatically reduced
- Most power consumed in op amps
- Power dominantly allocated to S/H and MSB stages

ADC Types



Nyquist Rate

- Flash
 - Pipeline
 - Two-Step Flash
 - Multi-Step Flash
 - Cyclic (algorithmic)
 - Interpolating
 - Successive Approximation
 - Folded
 - Dual Slope
- 

Over-Sampled

- Single-bit
- Multi-bit
- First-order
- Higher-order
- Continuous-time

Cyclic (Algorithmic) ADC

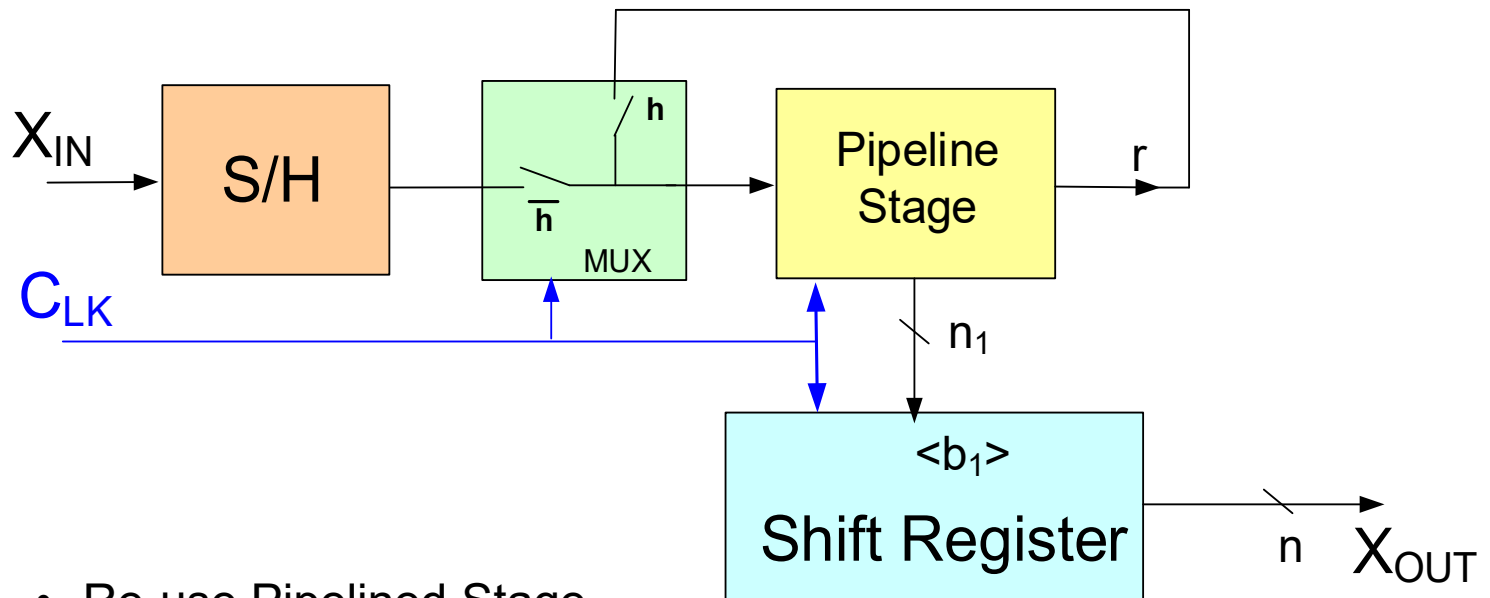 

- Re-use Pipelined Stage
- Small amount of hardware
- Effective thru-put decreases

ADC Types

Nyquist Rate


- Flash
- Pipeline
- Two-Step Flash
- Multi-Step Flash
- Cyclic (algorithmic)
- Interpolating
- Successive Approximation
- Folded
- Dual Slope

Over-Sampled

- Single-bit
- Multi-bit
- First-order
- Higher-order
- Continuous-time



Interpolating ADC

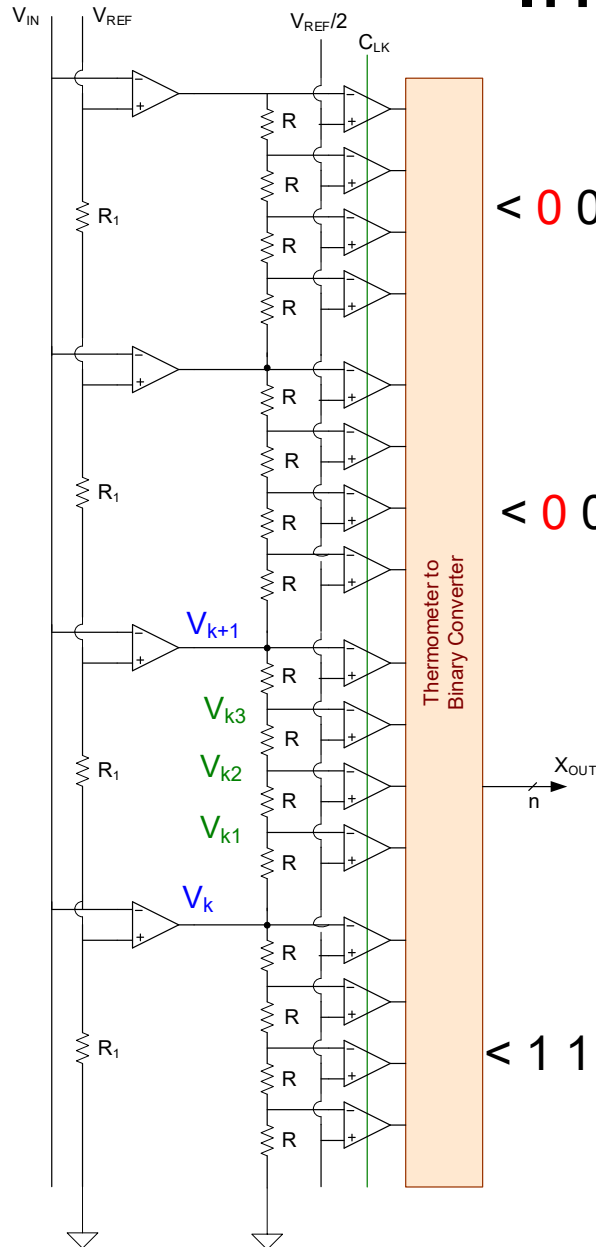


< 0 0 0 0 0 >

< 0 0 0 0 0 >

< 1 1 1 1 1 >

< 1 1 0 0 0 >

 - Amplifiers are finite-gain saturating
- Amplifiers need not be accurate or linear
- Shown for 4-bit
- Same common-mode input on comparators
- Clocked comparators usually regenerative
- Reduces Offset Requirements for Comparators



Colored bits are shared

ADC Types

Nyquist Rate


- Flash
- Pipeline
- Two-Step Flash
- Multi-Step Flash
- Cyclic (algorithmic)
- Interpolating
- Successive Approximation
- Folded
- Dual Slope

Over-Sampled

- Single-bit
- Multi-bit
- First-order
- Higher-order
- Continuous-time




SAR ADC

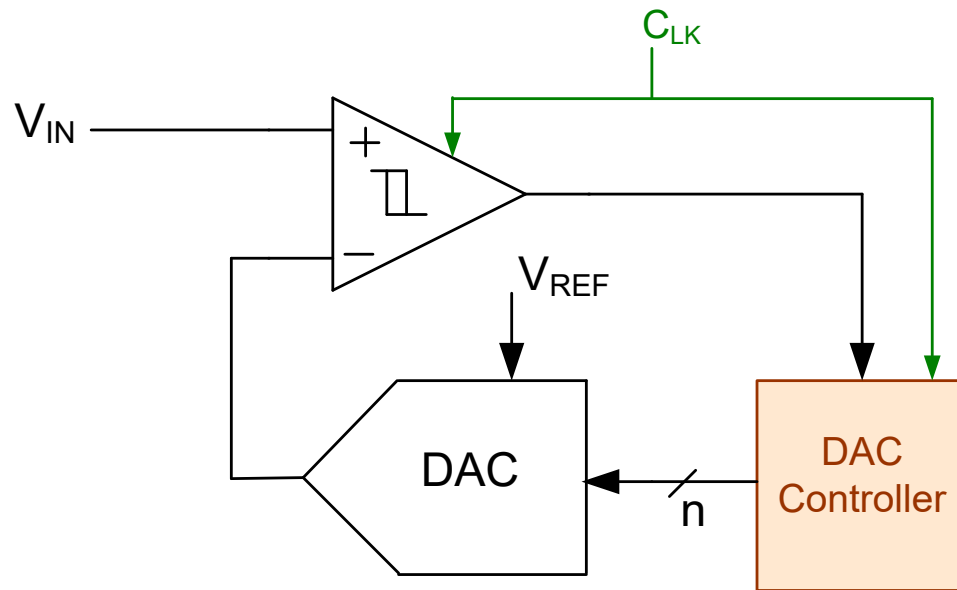

ADCs Texas Instruments


SAR		728
Pipeline		294
Delta Sigma		187
Folding Interpolating		66
Delta Sigma		
Modulator		9
Two-Step		6
Flash		3
Total		1293

SAR ADC

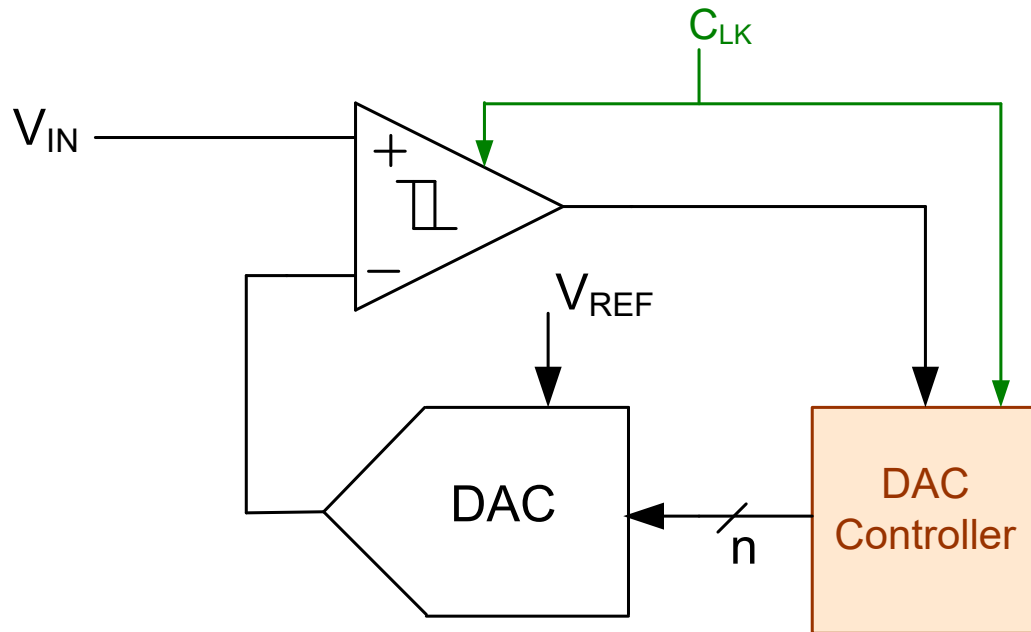


- DAC Controller may be simply U/D counter
- Binary search controlled by Finite State Machine is faster
- SAR ADC will have no missing codes if DAC is monotone
- Not very fast but can be small
- Any DAC can be used
- Single comparator !


Time Interleaved SAR ADC

 

 Time interleaving increases effective conversion rate by factor of m



Time Interleaved SAR ADC

 

- Provides high-speed solution when single SAR can not operate fast enough
- May be more energy efficient even if single SAR can work
- May provide better performance than pipelined structure
- Matching between stages is critical
- Clock phasing is critical
- Idea is 40+ years old but only recently has become popular
- Calibration is essential to provide matching and phasing

ADC Types

Nyquist Rate

- Flash
- Pipeline
- Two-Step Flash
- Multi-Step Flash
- Cyclic (algorithmic)
- Interpolating
- Successive Approximation
- Folded
- Dual Slope

Over-Sampled



- Single-bit
- Multi-bit
- First-order
- Higher-order
- Continuous-time



And Single Slope

Single-Slope ADC

Sometimes Termed Integrating ADC

 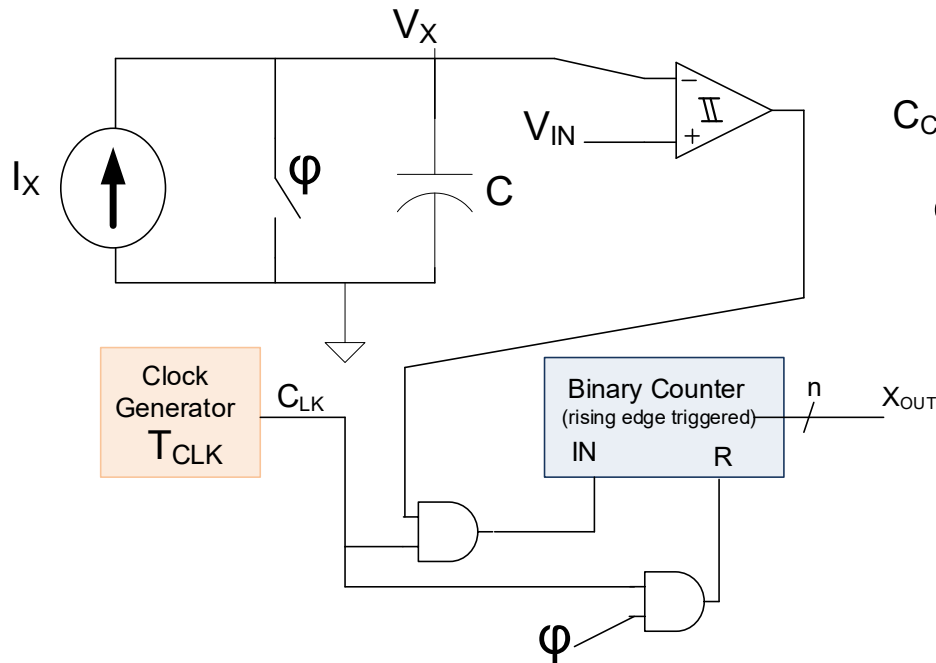

- Falling edge of ϕ synchronous with respect to falling edge of C_{CLK}
- Can convert asynchronously wrt C_{CLK} or can be a clocked ADC where conversion clock signal is synchronous wrt C_{CLK} .
- Output valid when comparator output goes low
- Note V_{REF} not explicitly shown in ADC architecture
- Very simple structure if C is off-chip

Single-Slope ADC

Operation:

Assume $V_X(t_{\text{CONV}})=0$

$$V_X(t) = \frac{1}{C} \int_{t_{\text{CONV}}}^t I_X dt = \frac{I_X}{C} (t - t_{\text{CONV}}) \quad (1)$$

Assume $I_X, V_{\text{REF}}, R, C, T_{\text{CLK}}$ are selected to satisfy the relationship

$$V_{\text{REF}} = \frac{1}{C} \int_{t_{\text{CONV}}}^{t_{\text{CONV}} + 2^n T_{\text{CLK}}} I_X dt = \frac{I_X}{C} 2^n T_{\text{CLK}} \quad \text{thus} \quad V_{\text{LSB}} = \frac{V_{\text{REF}}}{2^n} = \frac{I_X}{C} T_{\text{CLK}} \quad (2)$$

Comparator will stop counter when $V_X = V_{\text{IN}}$ and counter output will be $X_{\text{OUT}} = k$


$$\text{thus } V_X(t_{\text{CONV}} + kT_{\text{CLK}}) = V_{\text{IN}} + \varepsilon \quad \text{where } 0 < \varepsilon < V_{\text{LSB}}$$

It follows from (1) that

$$V_X(t_{\text{CONV}} + kT_{\text{CLK}}) = \frac{I_X}{C} kT_{\text{CLK}} = V_{\text{IN}} + \varepsilon \quad (3)$$

And finally from (2) and (3) that
 
$$V_{\text{IN}} = k \left(\frac{I_X}{C} T_{\text{CLK}} \right) - \varepsilon \cong \frac{k}{2^n} V_{\text{REF}}$$




Single-Slope ADC

$I_X, V_{REF}, R, C, T_{CLK}$ must satisfy the relationship

$$V_{REF} = \frac{I_X}{C} 2^n T_{CLK} \quad (1)$$

$$V_{IN} \cong \frac{k}{2^n} V_{REF}$$

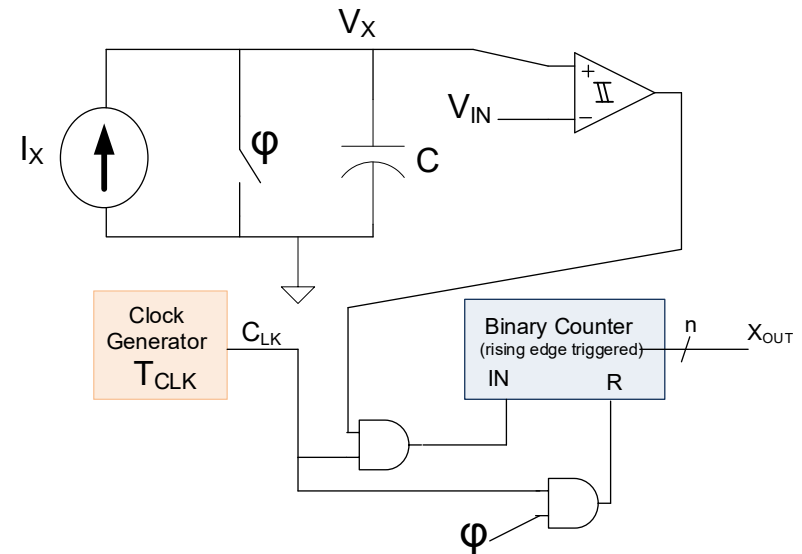

Benefits: Very simple structure and can provide a low-cost easy solution for low speed applications



Limitations:

- Process variations make it difficult to satisfy (1)
- C is usually large and thus off chip is often most practical
- Linearity of C important (since often off-chip)
- Nonlinearity in I_X degrades performance
- R_{OUT} of I_X degrades performance
- Slow
- Not widely used

Options for improving performance:

- Introduce self-calibration cycle to satisfy (1) by trimming I_X or C
- Use high-impedance current source
- Use OP-Amp Based RC integrator

Dual-Slope ADC

 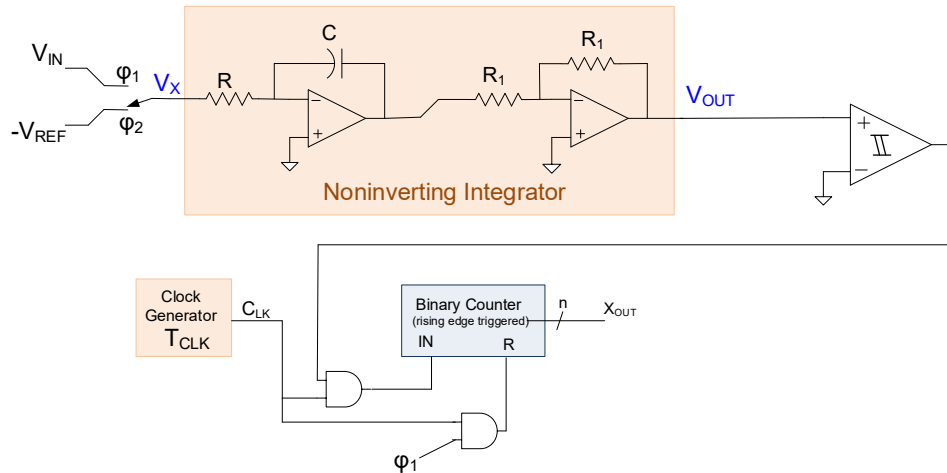

- Output valid when comparator output transitions to Low
- Must set RC time constants and T_{CLK} so output does not saturate
- Shown as noninverting integrator but slight modification will also work with inverting integrator
- Other integrator structures could be used
- Can leave one or more clock cycles between integrate up and integrate down

Dual-Slope ADC

Operation:

$$V_{OUT}(t) = \frac{1}{RC} \int_{t_{CONV}}^t V_X dt$$

During ϕ_1 , integrate V_{IN} for time $2^n T_{CLK}$


At end of integrate up interval, $V_{OUT}(2^n T_{CLK}) = \frac{1}{RC} V_{IN} 2^n T_{CLK}$

Reset counter at time $2^n T_{CLK}$

During ϕ_2 , integrate $-V_{REF}$ until comparator goes low and count clock transitions during down integration interval. At time comparator changes states, $V_{OUT}=0$ and code in counter is k

$$0 = \frac{1}{RC} \int_{t_{CONV}}^{t_{CONV} + 2^n T_{CLK}} V_{IN} dt - \frac{1}{RC} \int_{t_{CONV} + 2^n T_{CLK}}^{t_{CONV} + 2^n T_{CLK} + k T_{CLK}} V_{REF} dt \quad \Rightarrow \quad \frac{1}{RC} V_{IN} 2^n T_{CLK} = \frac{1}{RC} V_{REF} k T_{CLK}$$

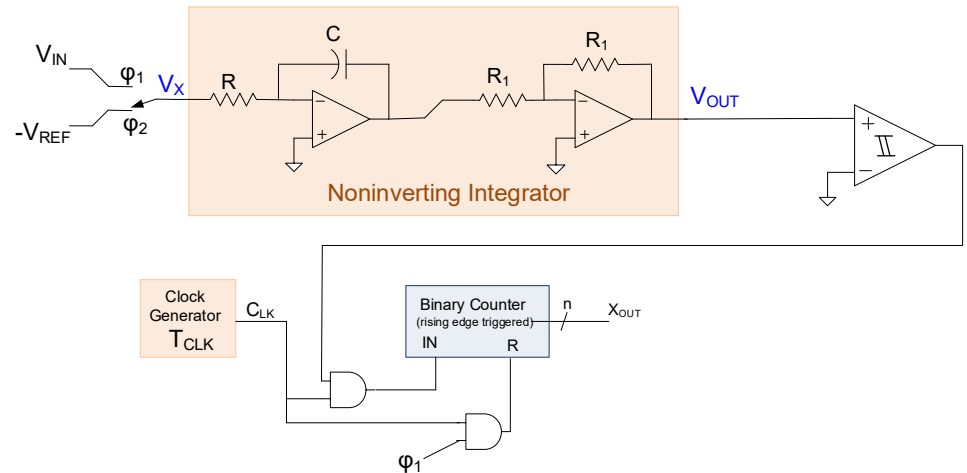Solving, obtain: $V_{IN} = \frac{k}{2^n} V_{REF}$



Dual-Slope ADC

$$V_{IN} = \frac{k}{2^n} V_{REF}$$


Observations:

Benefits

- Not dependent upon R, C, or T_{CLK} (provided integrator does not saturate)
- Very simple structure that can give good results and cost can be low
- Inherently monotone

Limitations:

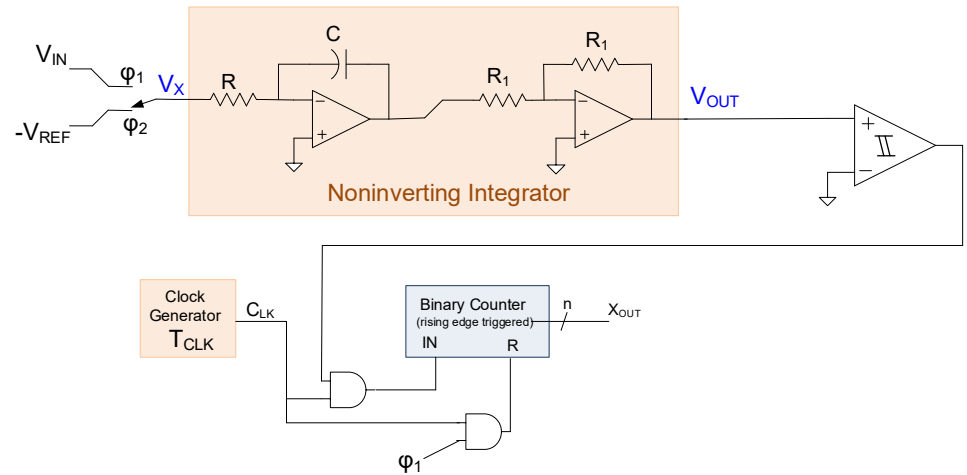- Capacitor large and likely must be off-chip
- Linearity of capacitor is important (particularly of concern when off-chip)
- Slow
- Not widely used





Stay Safe and Stay Healthy !

End of Lecture 39