

EE 435

Lecture 43

Phased Locked Loops and VCOs  
Over Sampled Data Converters

# Final Exam:

Scheduled on Final Exam Schedule:


Wednesday May 10 7:30 – 9:30 a.m.

Revised Final Exam:

- Take-home format – open book and open notes
- Will be posted on course WEB site by Tues morning May 9
- Due at 11:59 p.m. on Wednesday May 10: (Hard copy under office door of instructor)

If anyone would prefer an in-class closed-notes exam during the 2-hour scheduled period, arrangements will be made to accommodate those preferences. Such preferences must be conveyed to the instructor by class on Friday May 5

# Injection Locking

 

<https://www.youtube.com/watch?v=W1TMZASCR-I>

# Phase Locked Loops

Special case of injection-locked systems

In 1600's pendulums and organ pipes were occasionally injection locked

In 1919 electronic oscillators were observed that lock or synchronize

For the subsequent several decades, a form of PLLs was used to build radio and television receivers

In 1969 Signetics introduced the first integrated PLLs (NE 565 and NE 567)

In 1970's RCA introduced the 4046 PLL



# Phase Locked Loops

PLLs widely used throughout industry today


Easy to establish basic operation of a PLL

Highly nonlinear systems with seemingly simple operation but high-end designs can become quite complicated and mathematical rigor is often cumbersome and only approximate

Performance potential of most wireless communication systems and serial data transmission networks strongly dependent upon the performance characteristics of multiple embedded PLLs

Concepts of DLL and PLL are closely related

# Basic PLL Architecture

 

Applications include:

Frequency Demodulation

Frequency Synthesis


Clock Synchronization

Noise filtering (extreme)


Tracking and calibrated filters

- **One of the most widely used analog blocks**
- **Many SoC systems include multiple PLLs**
- **Closely related to Delay Locked Loop (DLL)**

# Basic PLL Architecture

 


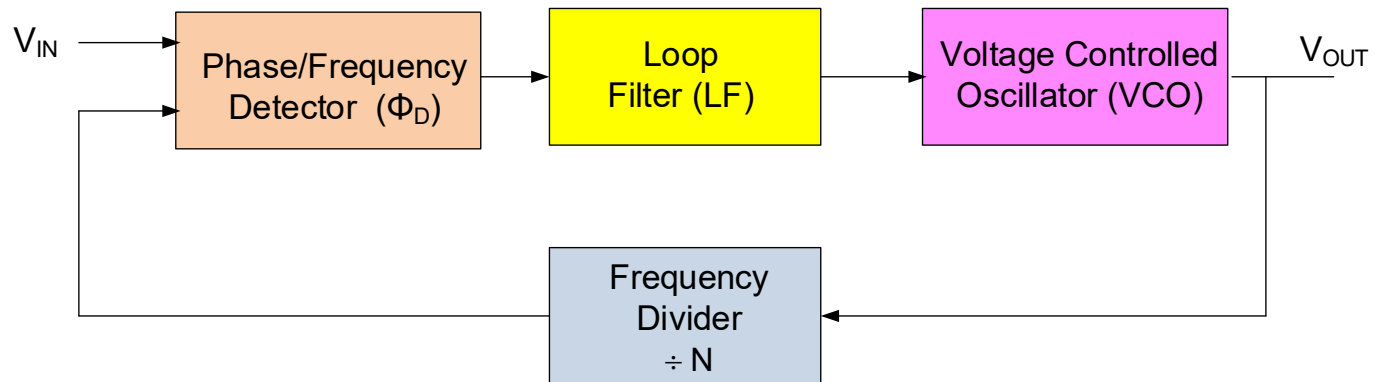Most basic structure actually uses phase/frequency detector but still termed PLL<sup>1</sup>



<sup>1</sup>Ian Collins, "Phase-Locked Loop (PLL) Fundamentals", Analog Dialogue, July 2018.

# Basis PLL Architecture

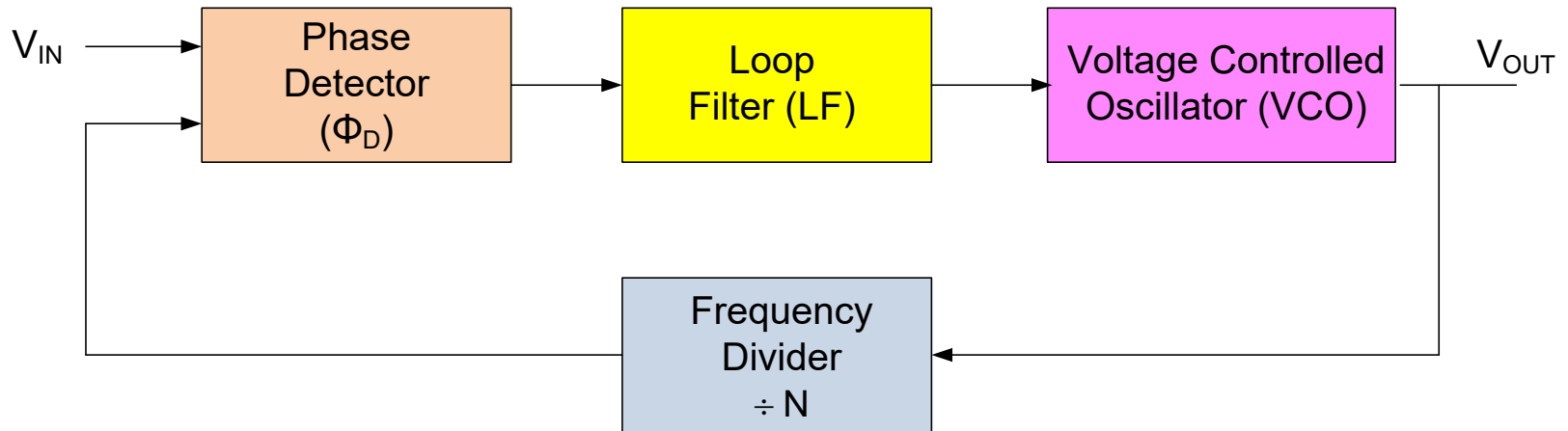

Applications by subcategory:


Clock and Data Recovery

Recovering signals when  $SNR \ll \ll 1$

Timing generators in digital systems



# Desired Operation of PLL

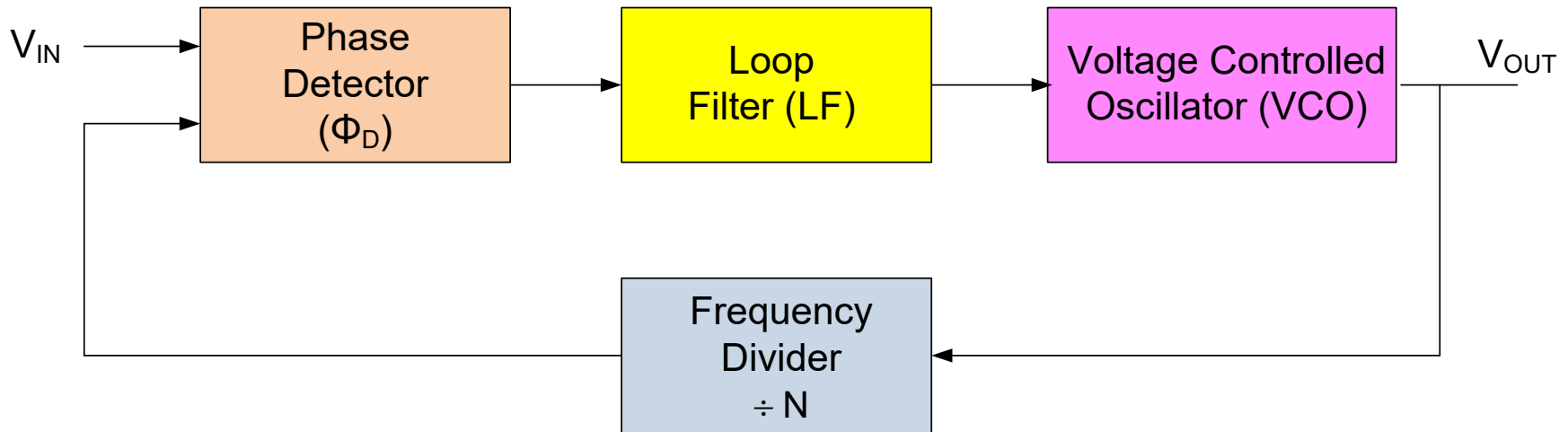


$$V_{IN} = V_M \sin(\omega_{IN} t + \phi_{IN})$$

Desired output when locked:

$$V_{OUT} = V_X \sin(N\omega_{IN} t + \phi_{OUT})$$

- Relationship between  $V_M$  and  $V_X$  is of little concern
- Frequency relationship is critical
- $\phi_{OUT}$  is often critical too
- Waveshape of  $V_{IN}$  and  $V_{OUT}$  is often of little concern  
May be highly distorted or even square waves

# Desired Operation of PLL

 

$$V_{IN} = V_M \sin(\omega_{IN} t + \phi_{IN})$$

Desired output when locked:

$$V_{OUT} = V_X \sin(N\omega_{IN} t + \phi_{OUT})$$

## Some Terminology of PLLs

Locked / Unlocked

Locked when  $V_{OUT}$  assumes desired value

Lock Range

$f_{LOW} < f_{IN} < f_{HIGH}$  If locked, will remain locked for  $f_{IN}$  in lock range

Capture Range


$f_{CLOW} < f_{IN} < f_{CHIGH}$  If unlocked, will lock for  $f_{IN}$  in capture range

Free-running frequency


frequency of VCO when not locked

Harmonic/Subharmonic Lock

# Desired Operation of PLL

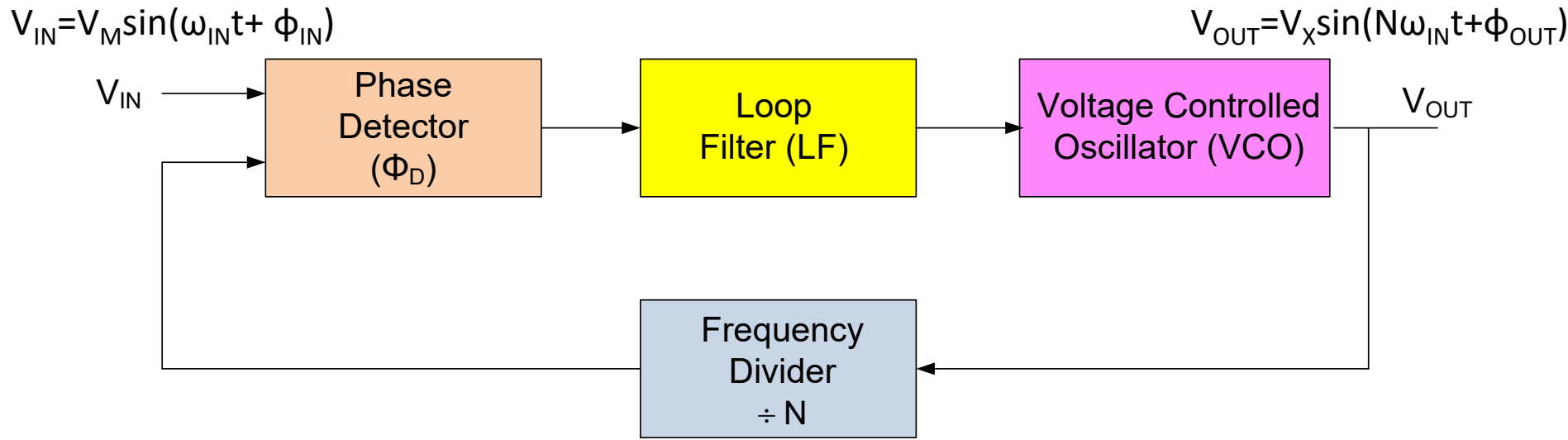

 Capture range always less than lock range  $f_{LLOW} < f_{CLOW} < f_{CHIGH} < f_{LHIGH}$



Loop filter controls capture and lock range


Jitter in VCO output strongly dependent upon lock range

(large lock range results in high jitter, low lock range in low jitter)

Loop filter is often dynamic with wide bandwidth prior to lock and narrow BW after lock

 
# Desired Operation of PLL

$$V_{IN} = V_M \sin(\omega_{IN} t + \phi_{IN})$$




$$V_{OUT} = V_X \sin(N\omega_{IN} t + \phi_{OUT})$$

Before Lock

 

After Lock

 

Loop filter is often dynamic with wide bandwidth prior to lock and narrow BW after lock

# Conceptual Operation of PLL

Consider a signal defined for  $-\infty < t < \infty$  expressed as

$$V(t) = V_M \sin(\phi(t))$$

If the signal is sinusoidal with frequency  $\omega$ , the argument  $\phi$  can be expressed as

$$\phi(t) = \omega t + \theta$$

where  $\phi$  is defined to be the phase of the signal and  $\theta$  is the phase offset on the time axis from the time reference  $t=0$

Taking the time derivative of  $\phi(t)$ , we obtain

$$\frac{d\phi}{dt} = \omega$$

Taking the Laplace Transform, we have

$$\phi_s = \frac{\omega}{s}$$

Is the second statement “If the signal is sinusoidal ....” redundant ?

## Is the second statement “If the signal is sinusoidal ....” redundant ?

Consider a signal defined for  $-\infty < t < \infty$  expressed as

$$V(t) = V_M \sin(\phi)$$

If the signal is sinusoidal with frequency  $\omega$ , the argument  $\phi$  can be expressed as

$$\phi = \omega t + \theta$$

---

Consider any signal  $f(t)$  defined for all time (not necessarily periodic but could be)


Define  $\phi(t)$  by the expression  $\phi(t) = \sin^{-1}\left(\frac{f(t)}{V_M}\right)$

It follows that  $V(t) = V_M \sin(\phi(t)) = V_M \sin\left(\sin^{-1}\left(\frac{f(t)}{V_M}\right)\right) = f(t)$

**Thus, the first statement gives NO information about the signal  $V(t)$**
 
# Consider a VCO where the output is sinusoidal

Assume the output of interest is the phase  $\phi$




$$V_{OUT} = V_m \sin(\omega t + \theta)$$

$$\omega = V_{LF} \bullet K_{VCO}$$


$$\frac{d\phi}{dt} = \omega = V_{LF} K_{VCO}$$

 Taking Laplace Transform:  $s\phi_S = V_{LFS} K_{VCO} \quad \longrightarrow \quad \phi_S = V_{LFS} \frac{K_{VCO}}{s}$


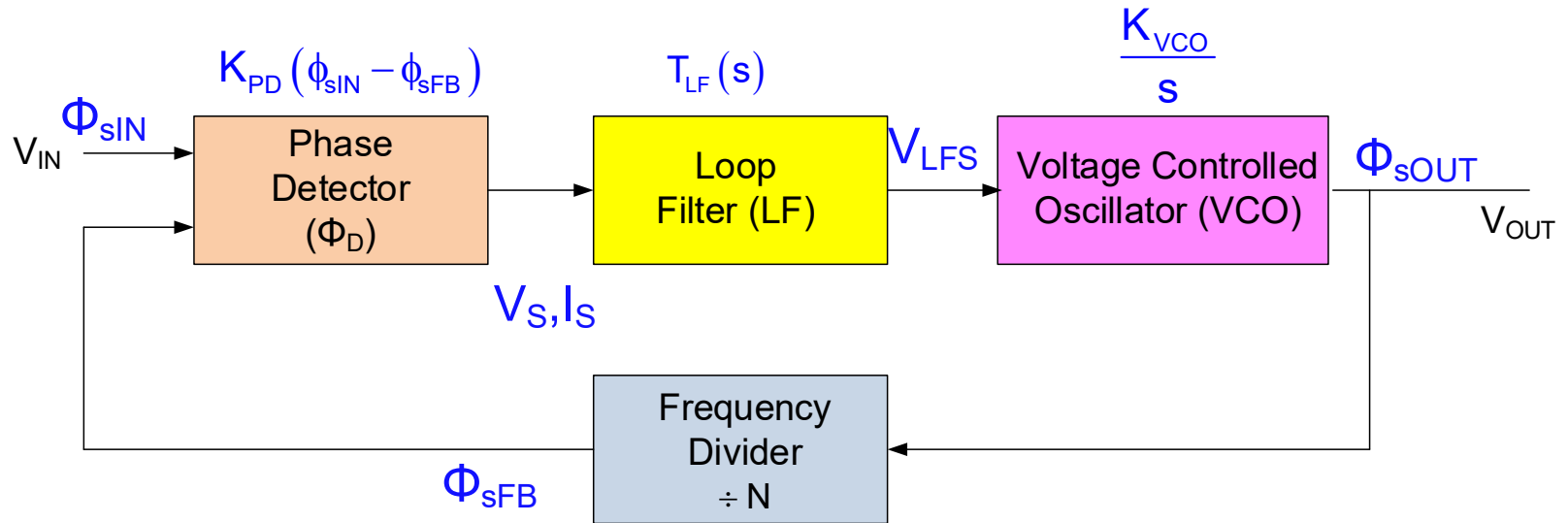
# Conceptual Operation of PLL

- When locked, PLL can be modeled as a linear system
- Small-signal s-domain analysis when PLL is locked



Note: Dimensions of variables in loop are not the same

$$V_S = K_{PD} (\phi_{sIN} - \phi_{sFB})$$

$$V_{LFS} = T_{LF}(s) V_S$$

$$\phi_{sOUT} = V_{LFS} \frac{K_{VCO}}{s}$$

$$\phi_{sFB} = \frac{\phi_{sOUT}}{N}$$


Solving, we obtain

$$T_{PLL}(s) = \frac{\phi_{sOUT}}{\phi_{sIN}} = \frac{T_{LF}(s) K_{PD} K_{VCO}}{s + T_{LF}(s) \frac{K_{VCO} K_{PD}}{N}}$$



# Often the LF is low order

 Example: Assume  $N=1$  and  $T_{LF}(s) = \frac{1}{1+RCs}$




$$T_{PLL}(s) = \frac{T_{LF}(s)K_{PD}K_{VCO}}{s + T_{LF}(s)K_{VCO}K_{PD}} = \frac{K_{PD}K_{VCO}}{s(1+RCs) + K_{VCO}K_{PD}}$$

$$T_{PLL}(s) = \frac{\frac{K_{PD}K_{VCO}}{RC}}{s^2 + s\frac{1}{RC} + \frac{K_{VCO}K_{PD}}{RC}}$$

# Often the LF is low order

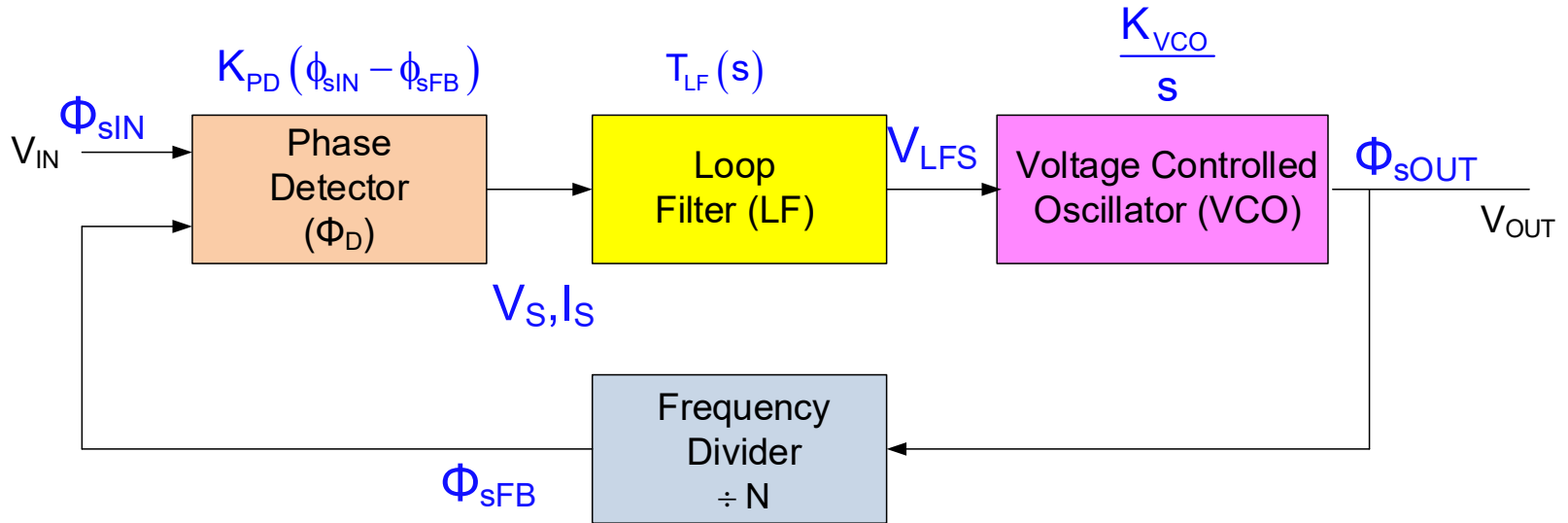Example: Assume  $N=1$  and  $T_{LF}(s) = \frac{1}{1+RCs}$



$$T_{PLL}(s) = \frac{K_{PD}K_{VCO}}{s^2 + s \frac{1}{RC} + \frac{K_{VCO}K_{PD}}{RC}}$$

$$s^2 + s \frac{1}{RC} + \frac{K_{VCO}K_{PD}}{RC} = s^2 + s \frac{\omega_0}{Q} + \omega_0^2$$

$$\omega_0 = \sqrt{\frac{K_{VCO}K_{PD}}{RC}}$$


$$Q = \sqrt{RC K_{VCO}K_{PD}}$$

# Voltage Controlled Oscillators


Many different VCOs can be used

Voltage Controlled Oscillator (VCO)


 
Assume  $I_0$  is determined by a controlling voltage



Integrator-Based VCO

 


Lossy Integrator-Based VCO

  

# Voltage Controlled Oscillators


## Voltage Controlled Oscillator (VCO)

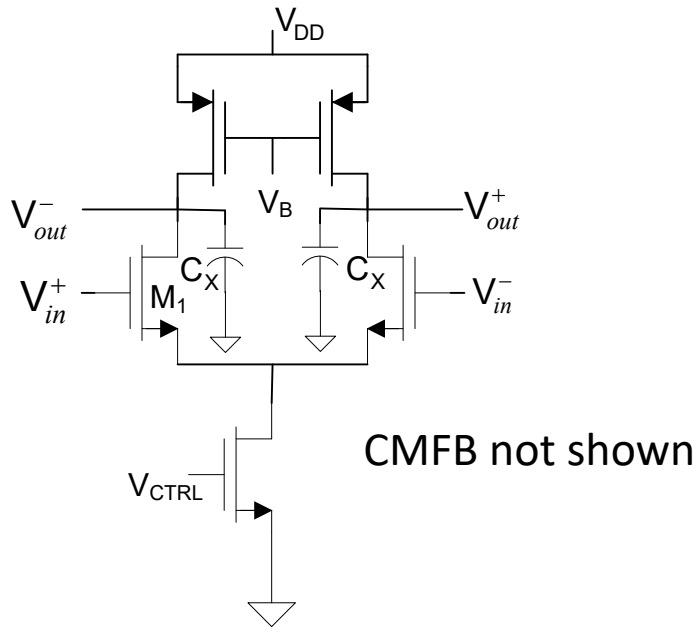

$$I_{0d}(s) = \frac{g_{m1}}{sC_X}$$

$$I_0 = \frac{g_{m1}}{C_X}$$

Integrator for: Integrator-based VCO

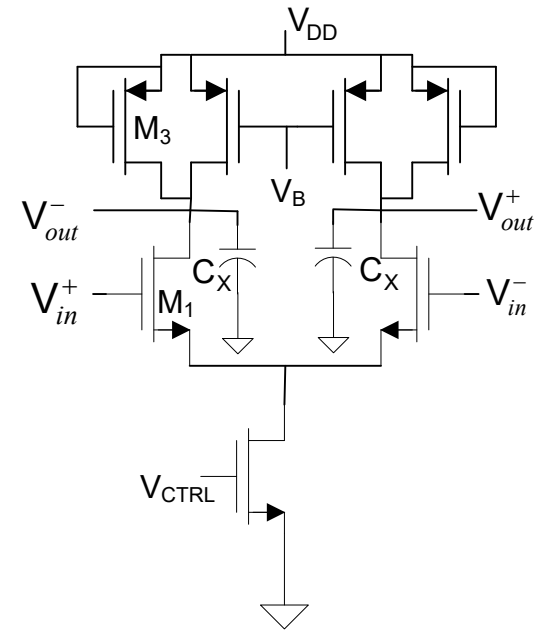

$$I_{0d}(s) = \frac{g_{m1}}{sC_X + g_{m3}}$$




$$I_0 = \frac{g_{m1}}{C_X} \quad \alpha = \frac{g_{m3}}{C_X}$$

Integrator for: Lossy Integrator-based VCO
   
# Voltage Controlled Oscillators

Voltage Controlled Oscillator (VCO)

Relaxation Oscillator Derived VCO (comparator not Op Amp)




$V_Z$  is approximately triangle wave,  $V_{OUT}$  is square wave

Can have either triangle wave or square wave outputs

 
# Phase Detectors

Many different Phase Detectors can be used



Some Popular Phase Detector Circuits

 - Analog Multiplier
- Exclusive OR Gate
- Sample and Hold
- Charge Pump



Charge-pump based Phase Detector


Average  $I_{OUT}$  is the average phase

# Phase Detectors






Many different Phase Detectors can be used

Desired phase difference often  $0^\circ$  or  $90^\circ$

Could be simply

 


$90^\circ$  nominal phase diff

  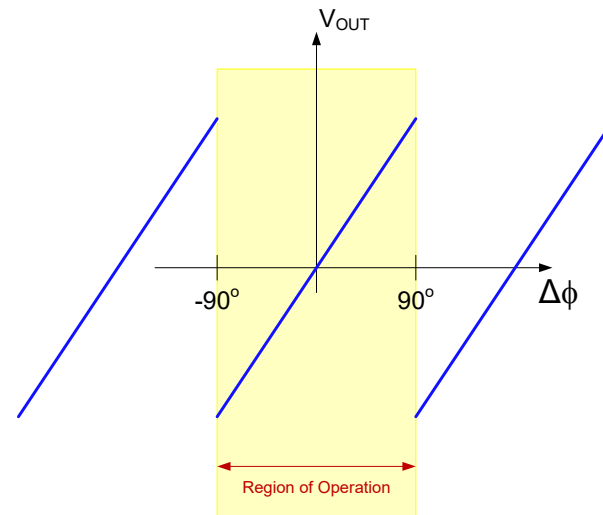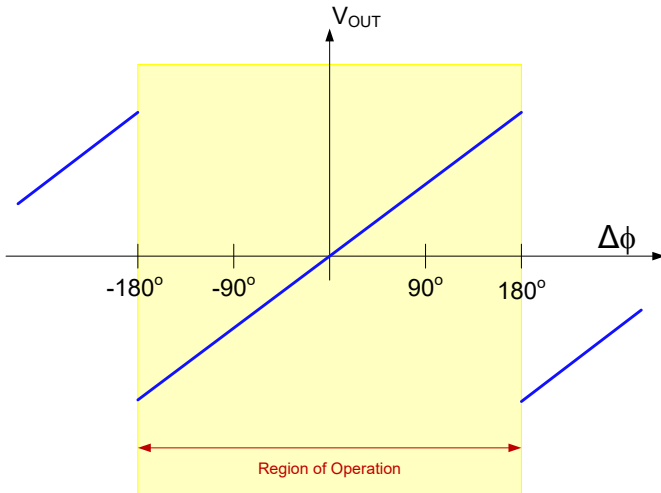 


Average  $I_{OUT}$  is the average phase

# Phase Detectors



Phase Detector ( $\Phi_D$ )

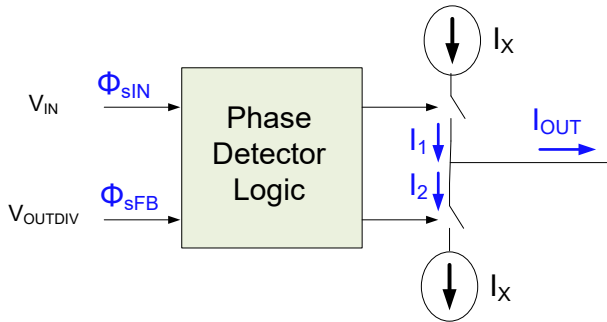



Average  $I_{OUT}$  is the average phase

 


$\Delta\phi=0$

  

$\Delta\phi>0$

 
 


$\Delta\phi<0$

 




# Phase Detectors

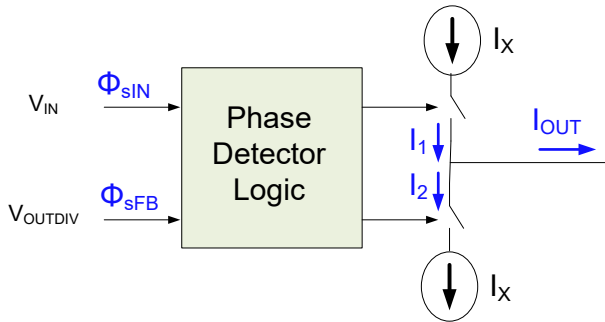 

Average  $I_{OUT}$  is the average phase

 


Vulnerable to dead zone problem

# Loop Filters

Many different Phase Detectors can be used  
Often the loop filter is first or second order  
Usually the loop filter circuit is very simple

$T_{LF}(s)$


Loop  
Filter (LF)

 

$$\frac{V_{OUT}}{I_{INAVG}} = T_{LF}(s) = \frac{R}{1+RCs}$$

Basic first-order LF with average current difference as input

# What is the phase of a signal?

 


Assume  $\omega_1 = \omega_2 = \omega$

If  $V_1$  can be expressed as  $V_1 = V_{M1} \sin(\omega t + \phi_1)$  the phase is  $\phi_1$

But what is the phase if  $\omega$  is time varying? Or what is the “phase” if this functional form does not really characterize  $V(t)$ ? Or what if  $\omega_1 \neq \omega_2$ ?

What does a phase detector do if the two inputs are not at the same frequency?


# What is the phase of a signal?

 

Most Phase Detectors are actually Phase/Frequency Detectors

- Large output when frequency difference exists
- Also provides output when phase difference exists after frequencies are matched

# Data Converter Type Chart


 


# Over-Sampled Data Converters


## General Classes

- Single-bit
- Multi-bit
- First-order
- Higher-order
- Continuous-time

# Nyquist Rate

  

# Over-Sampled

 

Over-sampling ratios of 128:1 or 64:1 are common  
Dramatic reduction in quantization noise effects  
Limited to relatively low frequencies




Recall:

$$f_{\text{SIG}}=50\text{Hz}$$

$$f_{\text{NYQ}}=100\text{Hz}$$

$$f_{\text{SAMP}}=2.3\text{KHz}$$


Oversampled: 23:1

 

MatLab Results

Recall:

# Quantization Effects

 


**Simulation environment:**

$$N_p = 23$$
$$f_{\text{SIG}} = 50\text{Hz}$$

Recall:

# Quantization Effects

Res = 4 bits

 

$f_{\text{SIG}}=50\text{Hz}$   
 $f_{\text{NYQ}}=100\text{Hz}$   
 $f_{\text{SAMP}}=1113\text{KHz}$   
Oversampled: 11:1

RMS Quantization Noise:


$$E_{\text{RMS}} = \frac{x_{\text{LSB}}}{\sqrt{12}}$$

Lets now increase resolution

Recall:

# Quantization Effects

Res = 10 bits

 

$f_{\text{SIG}}=50\text{Hz}$   
 $f_{\text{NYQ}}=100\text{Hz}$   
 $f_{\text{SAMP}}=1113\text{KHz}$   
Oversampled: 11:1

$$E_{\text{RMS}} = \frac{x_{\text{LSB}}}{\sqrt{12}}$$


Quantization noise is much lower but still significant

Lets now increase oversampling ratio (i.e. number of samples)

Recall:

# Quantization Effects

Res = 10 bits

 

$f_{\text{SIG}} = 50\text{Hz}$   
 $f_{\text{NYQ}} = 100\text{Hz}$   
 $f_{\text{SAMP}} = 8904\text{KHz}$   
Oversampled: 89:1

$$E_{\text{RMS}} = \frac{x_{\text{LSB}}}{\sqrt{12}}$$


Compared to the previous slide, it appears that the quantization noise has gone down

But has it? Magnitude of quantization DFT terms decreased but  $E_{\text{RMS}}$  unchanged

Recall:

# Quantization Effects

Res = 10 bits

 


$f_{\text{SIG}} = 50\text{Hz}$   
 $f_{\text{NYQ}} = 100\text{Hz}$   
 $f_{\text{SAMP}} = 8904\text{KHz}$   
Oversampled: 89:1

$$E_{\text{RMS}} = \frac{x_{\text{LSB}}}{\sqrt{12}}$$

Can any additional useful information about the input be obtained since we have many more samples than are needed?

# Over-Sampling

 


Res = 10 bits

$$f_{\text{SIG}} = 50\text{Hz}$$


$$f_{\text{NYQ}} = 100\text{Hz}$$

$$f_{\text{SAMP}} = 8904\text{KHz}$$

Oversampled: 89:1

 

 What would happen if we break the 4096 samples into groups of 20 samples and form?




$$E_{\text{RMS}} = ?$$

$$\hat{X}_{\text{OUT}}(k \cdot 20T_{\text{SAMP}}) = \frac{1}{20} \sum_{j=1}^{20} x_{\text{OUT}}(jT_{\text{SAMP}} + 20kT_{\text{SAMP}})$$

- Though the individual samples have been quantized to 10 bits, the arithmetic operations will have many more bits
- The effective sampling rate has been reduced by a factor of 20 but is still over 4 times the Nyquist rate
- Has the quantization noise been reduced (or equivalently has the resolution of the ADC been improved?)
- Is there more information available about the signal?

# Over-Sampling

 

Res = 10 bits

$$f_{\text{SIG}} = 50\text{Hz}$$

$$f_{\text{NYQ}} = 100\text{Hz}$$


$$f_{\text{SAMP}} = 8904\text{KHz}$$

Oversampled: 89:1



$$E_{\text{RMS}} = \frac{x_{\text{LSB}}}{\sqrt{12}}$$

 Since the quantization noise is at high frequencies, what would happen if filtered the Boolean output signal?




$$E_{\text{RMS}} = ?$$

$$Y_{\text{OUT}}(kT_{\text{SAMP}}) = \sum_{j=0}^m a_j x_{\text{OUT}}(k - jT_{\text{SAMP}})$$

Or 
$$Y_{\text{OUT}}(kT_{\text{SAMP}}) = \sum_{j=0}^m a_j x_{\text{OUT}}(k - jT_{\text{SAMP}}) + \sum_{j=1}^h b_j Y_{\text{OUT}}(k - jT_{\text{SAMP}})$$



# Over-Sampling

 

Res = 10 bits

$$f_{\text{SIG}} = 50\text{Hz}$$

$$f_{\text{NYQ}} = 100\text{Hz}$$

$$f_{\text{SAMP}} = 8904\text{KHz}$$

Oversampled: 89:1

$$E_{\text{RMS}} = \frac{x_{\text{LSB}}}{\sqrt{12}}$$

What does this difference equation represent?

$$Y_{\text{OUT}}(kT_{\text{SAMP}}) = \sum_{j=0}^m a_j x_{\text{OUT}}(k - jT_{\text{SAMP}})$$


- Moving Average (MA) Digital Filter
- Filter shape (e.g. low-pass, band-pass, high-pass, ... dependent upon  $\langle a_i \rangle$  coefficients)

What does this difference equation represent?

$$Y_{\text{OUT}}(kT_{\text{SAMP}}) = \sum_{j=0}^m a_j x_{\text{OUT}}(k - jT_{\text{SAMP}}) + \sum_{j=1}^h b_j Y_{\text{OUT}}(k - jT_{\text{SAMP}})$$

- Auto Regressive Moving Average (ARMA) Digital Filter
- Filter shape (e.g. low-pass, band-pass, high-pass, ... dependent upon  $\langle a_i \rangle$  and  $\langle b_j \rangle$  coefficients)

# Over-Sampling

 

Res = 10 bits

$$f_{\text{SIG}} = 50\text{Hz}$$

$$f_{\text{NYQ}} = 100\text{Hz}$$

$$f_{\text{SAMP}} = 8904\text{KHz}$$

Oversampled: 89:1



$$E_{\text{RMS}} = \frac{x_{\text{LSB}}}{\sqrt{12}}$$

Since the quantization noise is at high frequencies, what would happen if filtered and decimated the Boolean output signal?


$$Y_{\text{OUT}}(kT_{\text{SAMP}}) = \sum_{j=0}^m a_j x_{\text{OUT}}(k - jT_{\text{SAMP}})$$

$$Y_{\text{OUT}}(kT_{\text{SAMP}}) = \sum_{j=0}^m a_j x_{\text{OUT}}(k - jT_{\text{SAMP}}) + \sum_{j=1}^h b_j Y_{\text{OUT}}(k - jT_{\text{SAMP}})$$




$$E_{\text{RMS}} = ?$$


# Over-Sampling

 

$$E_{RMS} = \frac{x_{LSB}}{\sqrt{12}}$$

 


$$E_{RMS} = ?$$

 

$$E_{RMS} = ?$$


- What is the overhead?
- What is the performance potential?
- How can these or related over-sampling approaches be designed?
- Though this approach may help quantization noise, will not improve ADC linearity
 
# Over-Sampled Spectrum showing quantization noise with digital lowpass filter




Residual Quantization Noise if Filter Band-edge at  $f_x$

# Over-Sampling

 


$$f_s = f_{\text{SAMP}}$$

$$OSR = \frac{f_s}{2 f_0}$$

 

With ideal lowpass filter with band-edge at  $f_0$

 
$$V_{\text{Rms}} = \frac{V_{\text{LSB}}}{\sqrt{12}} \frac{1}{\sqrt{OSR}}$$



For sinusoidal input with p-p value  $V_{\text{REF}}$


$$SNR = 6.02n + 1.76 + 10\log(OSR)$$

 Improvement of 3dB/octave or 0.5bits/octave



Oversampling increases resolution and if followed by LP filter Reduces Quantization Noise!

# Over-sampled ADC

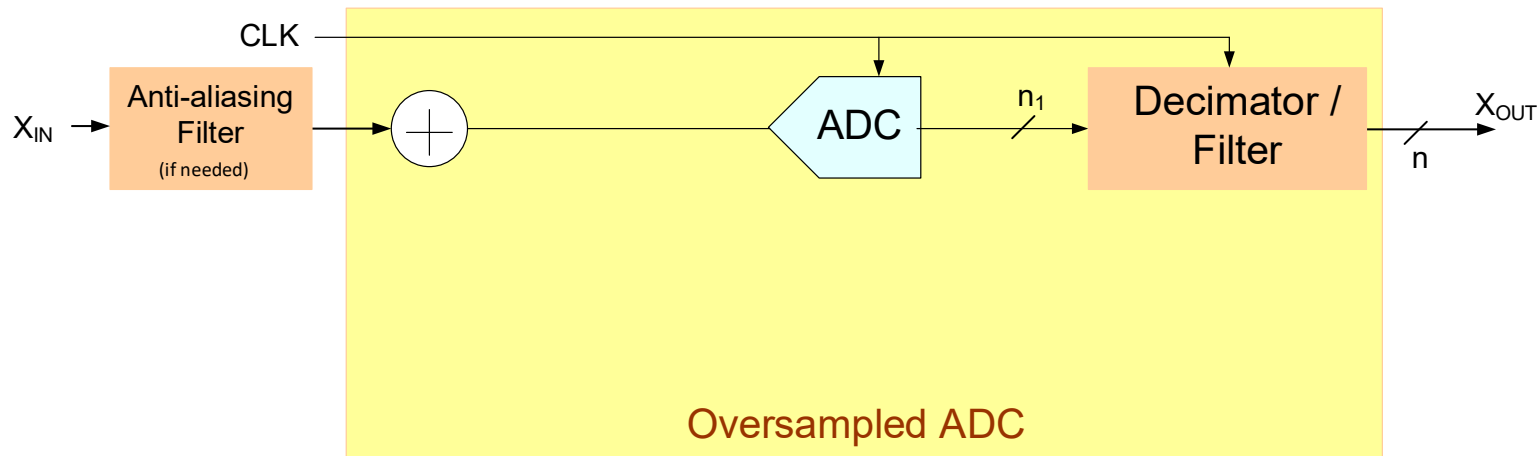

- Anti-aliasing filter at the input (if needed) to limit bandwidth of input signal
- ADC is often simply a comparator
- CLK is much higher in frequency than effective sampling rate (maybe 128:1 though lower OSR also widely used)
- Can obtain very high resolution but effective sampling rate is small
- **With clever design, this approach can reduce quantization effects and improve linearity**



Stay Safe and Stay Healthy !

End of Lecture 43