

EE 435

Lecture 43

Phased Locked Loops and VCOs
Over Sampled Data Converters

Final Exam:

Scheduled on Final Exam Schedule:


Wednesday May 8 7:30 – 9:30 a.m.

Revised Final Exam:

- Take-home format – open book and open notes
- Will be posted on course WEB site by Tues morning May 7
- Due at 11:59 p.m. on Wednesday May 8: (Hard copy under office door of instructor)

If anyone would prefer an in-class closed-notes exam during the 2-hour scheduled period, arrangements will be made to accommodate those preferences. Such preferences must be conveyed to the instructor by class on Friday May 3

Injection Locking

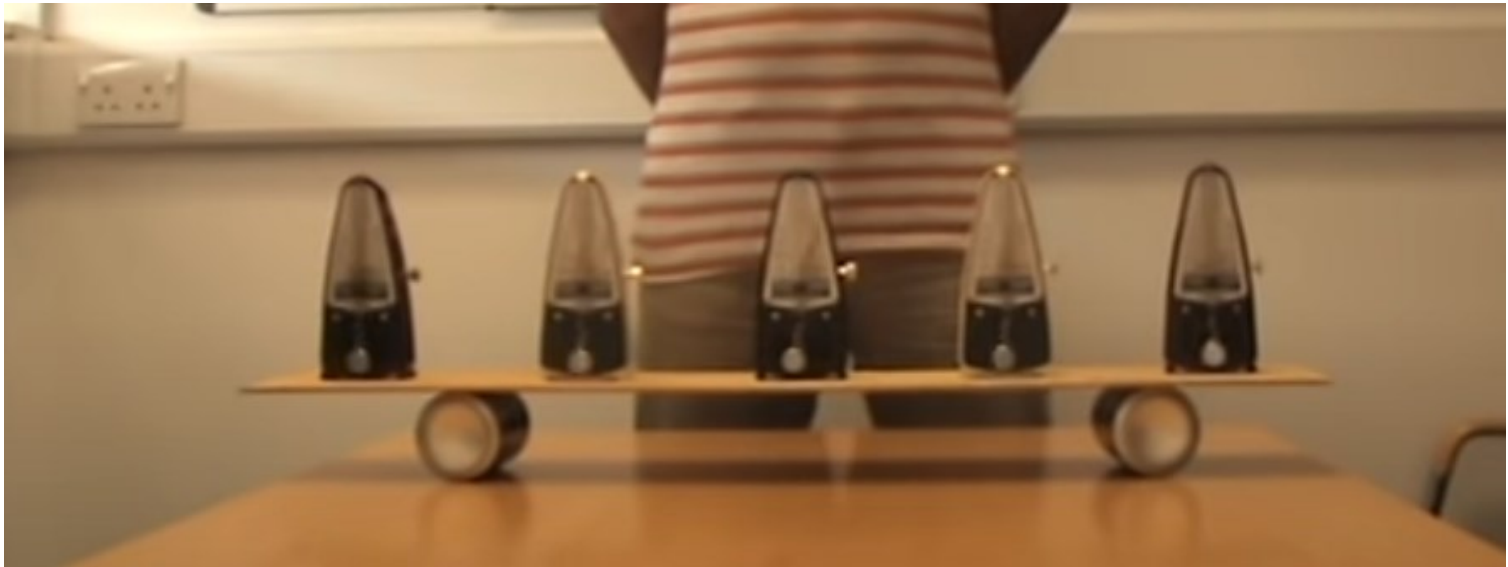

<https://www.youtube.com/watch?v=W1TMZASCR-I>

Phase Locked Loops

Special case of injection-locked systems

In 1600's pendulums and organ pipes were occasionally injection locked

In 1919 electronic oscillators were observed that lock or synchronize

For the subsequent several decades, a form of PLLs was used to build radio and television receivers

In 1969 Signetics introduced the first integrated PLLs (NE 565 and NE 567)

In 1970's RCA introduced the 4046 PLL



Phase Locked Loops

PLLs widely used throughout industry today


Easy to establish basic operation of a PLL

Highly nonlinear systems with seemingly simple operation but high-end designs can become quite complicated and mathematical rigor is often cumbersome and only approximate

Performance potential of most wireless communication systems and serial data transmission networks strongly dependent upon the performance characteristics of multiple embedded PLLs

Concepts of DLL and PLL are closely related

Basic PLL Architecture

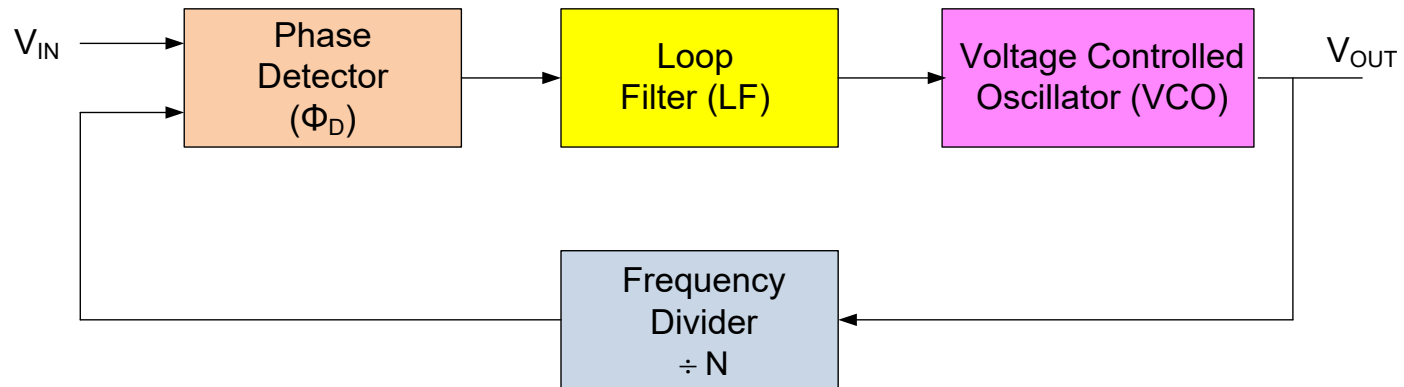

Applications include:

Frequency Demodulation

Frequency Synthesis


Clock Synchronization

Noise filtering (extreme)


Tracking and calibrated filters

- **One of the most widely used analog blocks**
- **Many SoC systems include multiple PLLs**
- **Closely related to Delay Locked Loop (DLL)**

Basic PLL Architecture

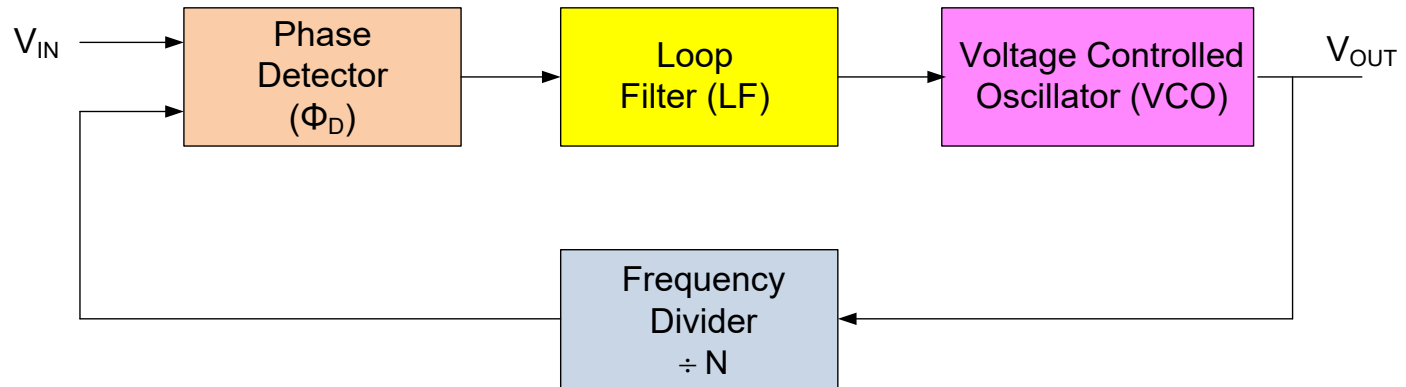


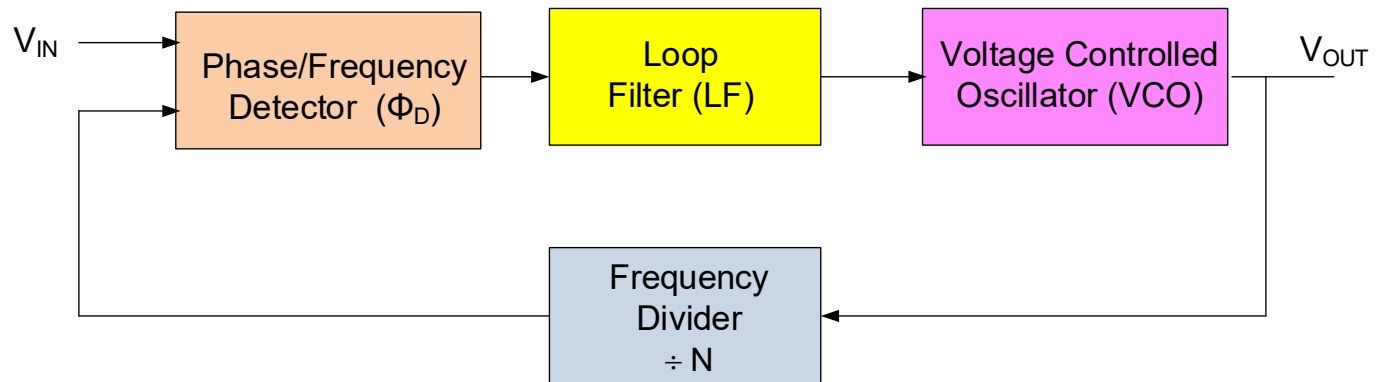Most basic structure actually uses phase/frequency detector but still termed PLL¹



¹Ian Collins, "Phase-Locked Loop (PLL) Fundamentals", Analog Dialogue, July 2018.

Basis PLL Architecture

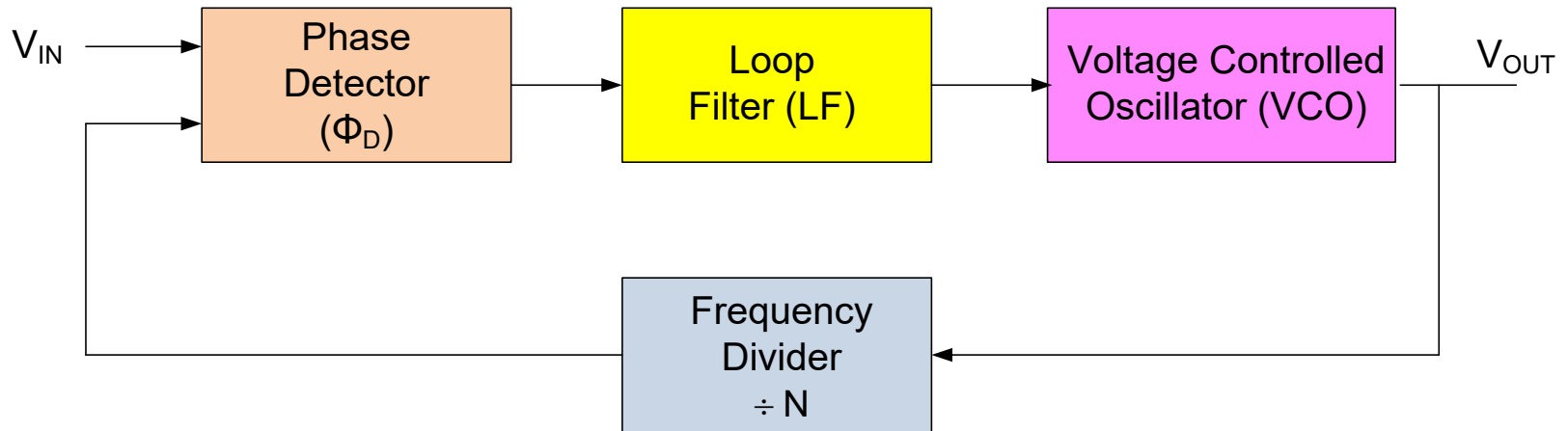


Applications by subcategory:

Clock and Data Recovery

Recovering signals when $SNR \ll \ll 1$

Timing generators in digital systems

Desired Operation of PLL

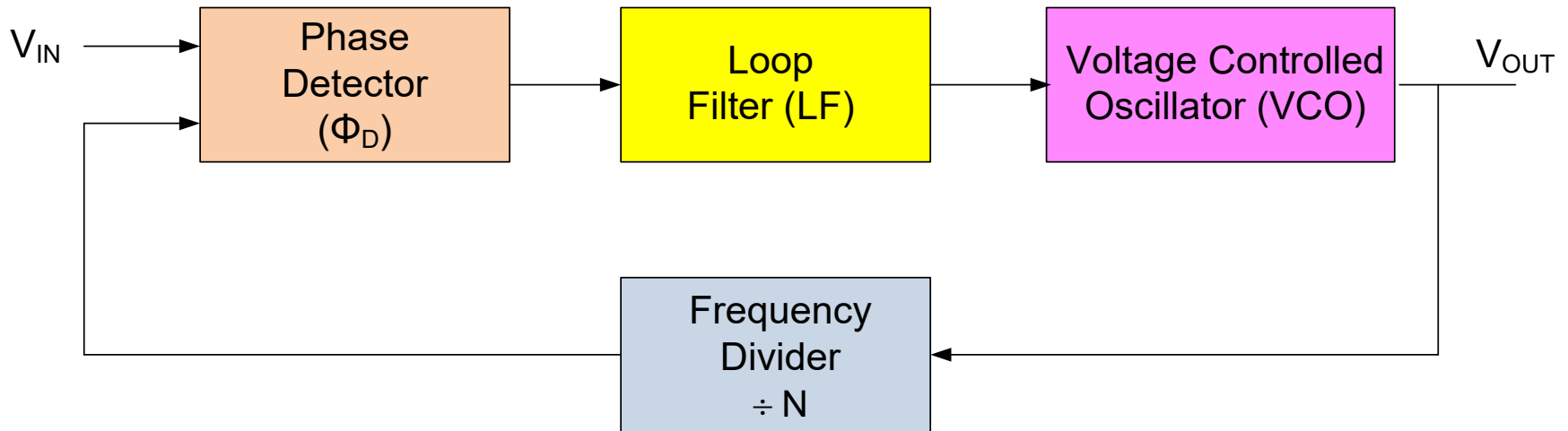


$$V_{IN} = V_M \sin(\omega_{IN} t + \phi_{IN})$$

Desired output when locked:

$$V_{OUT} = V_X \sin(N\omega_{IN} t + \phi_{OUT})$$

- Relationship between V_M and V_X is of little concern
- Frequency relationship is critical
- ϕ_{OUT} is often critical too
- Waveshape of V_{IN} and V_{OUT} is often of little concern
May be highly distorted or even square waves

Desired Operation of PLL

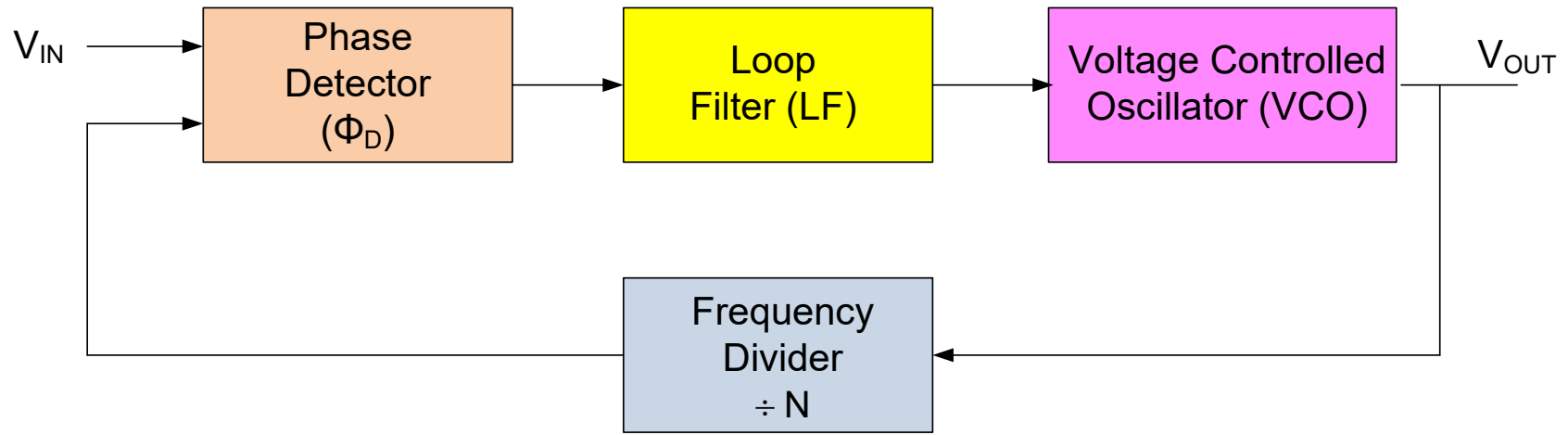

$$V_{IN} = V_M \sin(\omega_{IN} t + \phi_{IN})$$

Desired output when locked:

$$V_{OUT} = V_X \sin(N\omega_{IN} t + \phi_{OUT})$$

Some Terminology of PLLs

Locked / Unlocked

Locked when V_{OUT} assumes desired value

Lock Range

$f_{LOW} < f_{IN} < f_{HIGH}$ If locked, will remain locked for f_{IN} in lock range

Capture Range


$f_{CLOW} < f_{IN} < f_{CHIGH}$ If unlocked, will lock for f_{IN} in capture range

Free-running frequency


frequency of VCO when not locked

Harmonic/Subharmonic Lock

Desired Operation of PLL

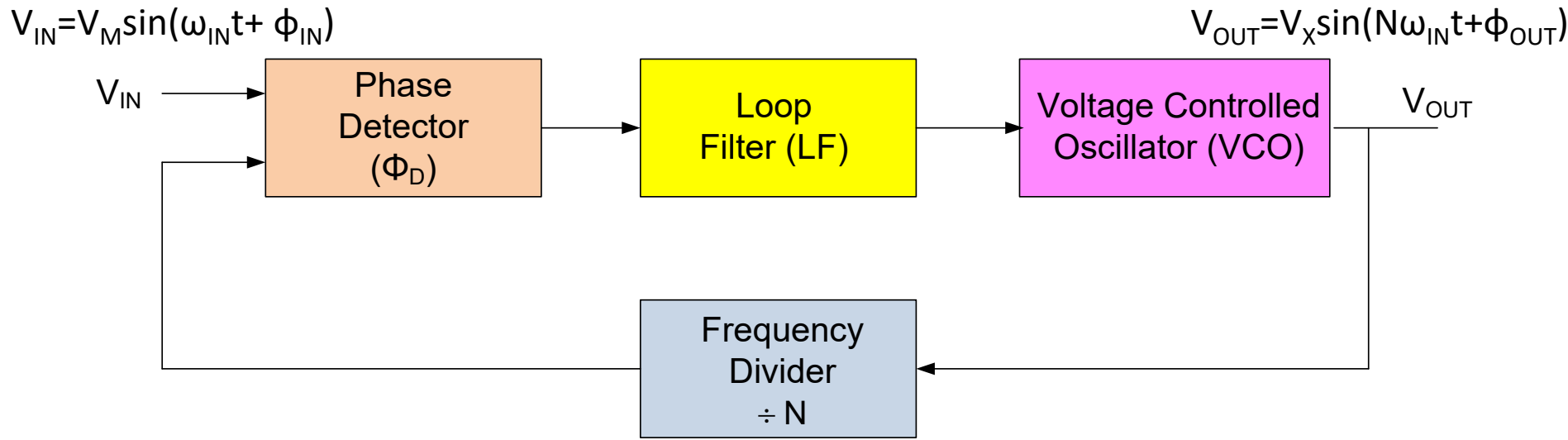

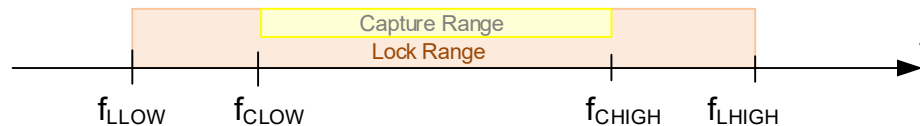Capture range always less than lock range $f_{LLOW} < f_{CLOW} < f_{CHIGH} < f_{LHIGH}$



Loop filter controls capture and lock range


Jitter in VCO output strongly dependent upon lock range

(large lock range results in high jitter, low lock range in low jitter)

Loop filter is often dynamic with wide bandwidth prior to lock and narrow BW after lock


Desired Operation of PLL
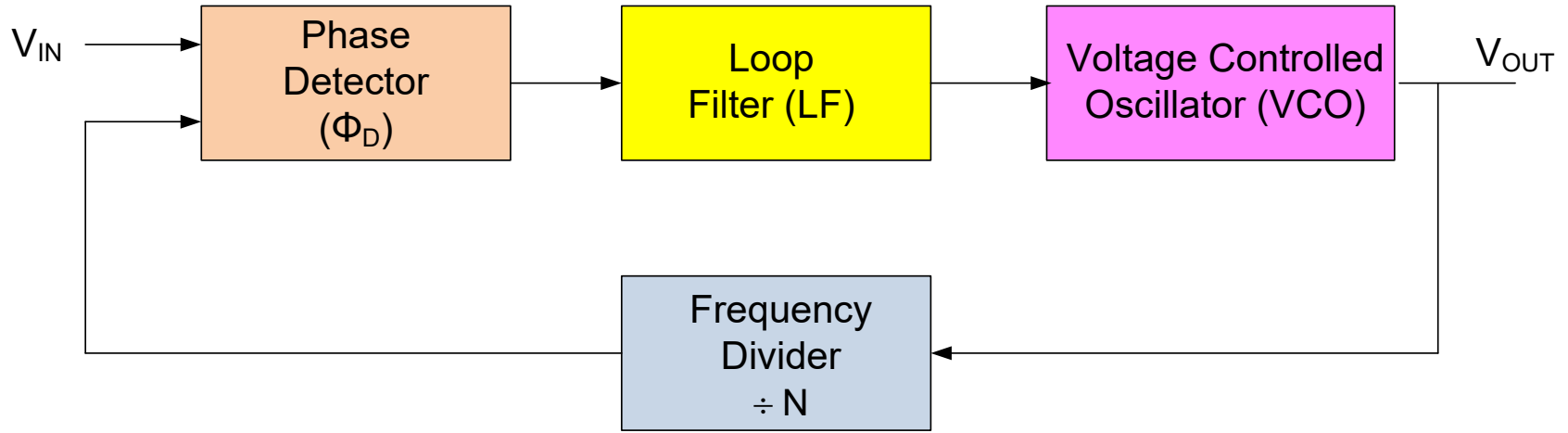
$$V_{IN} = V_M \sin(\omega_{IN} t + \phi_{IN})$$




$$V_{OUT} = V_X \sin(N\omega_{IN} t + \phi_{OUT})$$

Before Lock

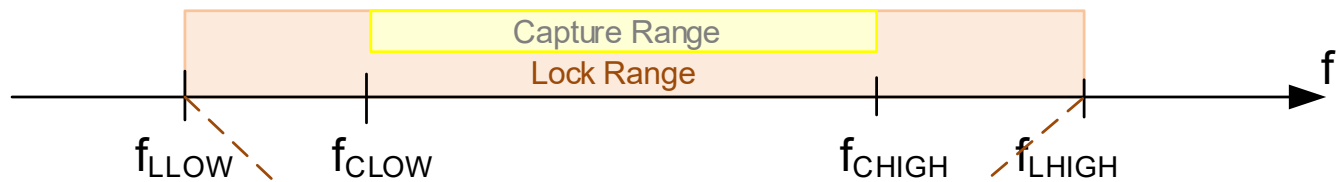

After Lock

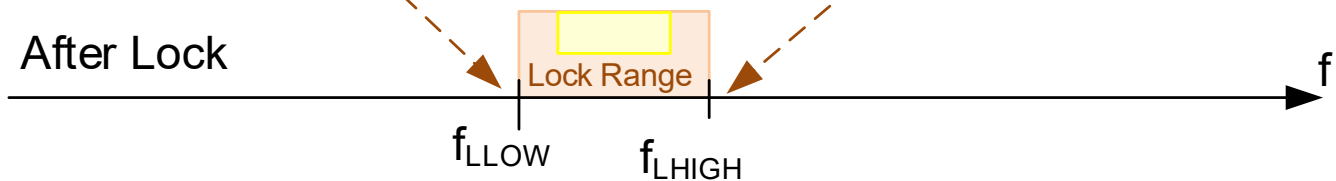

Loop filter is often dynamic with wide bandwidth prior to lock and narrow BW after lock

Conceptual Operation of PLL

Consider a signal defined for $-\infty < t < \infty$ expressed as

$$V(t) = V_M \sin(\phi(t))$$

If the signal is sinusoidal with frequency ω , the argument ϕ can be expressed as

$$\phi(t) = \omega t + \theta$$

where ϕ is defined to be the phase of the signal and θ is the phase offset on the time axis from the time reference $t=0$

Taking the time derivative of $\phi(t)$, we obtain

$$\frac{d\phi}{dt} = \omega$$

Taking the Laplace Transform, we have

$$\phi_s = \frac{\omega}{s}$$

Is the second statement “If the signal is sinusoidal” redundant ?

Is the second statement “If the signal is sinusoidal” redundant ?

Consider a signal defined for $-\infty < t < \infty$ expressed as

$$V(t) = V_M \sin(\phi)$$

If the signal is sinusoidal with frequency ω , the argument ϕ can be expressed as

$$\phi = \omega t + \theta$$

Consider any signal $f(t)$ defined for all time (not necessarily periodic but could be)


Define $\phi(t)$ by the expression $\phi(t) = \sin^{-1}\left(\frac{f(t)}{V_M}\right)$

It follows that $V(t) = V_M \sin(\phi(t)) = V_M \sin\left(\sin^{-1}\left(\frac{f(t)}{V_M}\right)\right) = f(t)$

Thus, the first statement gives NO information about the signal $V(t)$

Consider a VCO where the output is sinusoidal

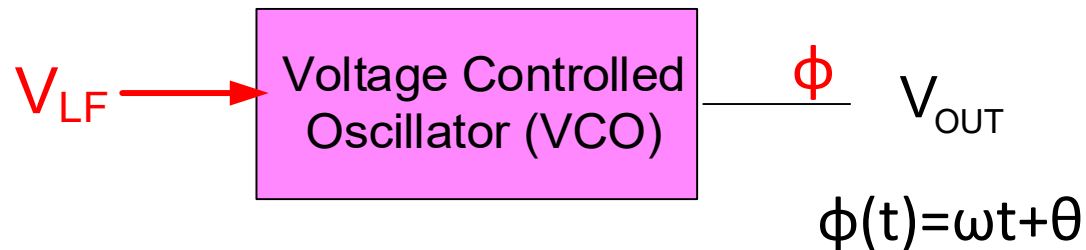Assume the output of interest is the phase ϕ




$$V_{OUT} = V_m \sin(\omega t + \theta)$$

$$\omega = V_{LF} \cdot K_{VCO}$$


$$\frac{d\phi}{dt} = \omega = V_{LF} K_{VCO}$$

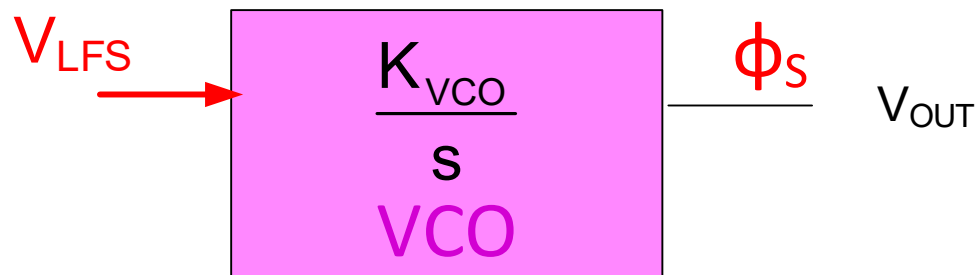Taking Laplace Transform: $s\phi_S = V_{LFS} K_{VCO} \longrightarrow \phi_S = V_{LFS} \frac{K_{VCO}}{s}$



Conceptual Operation of PLL

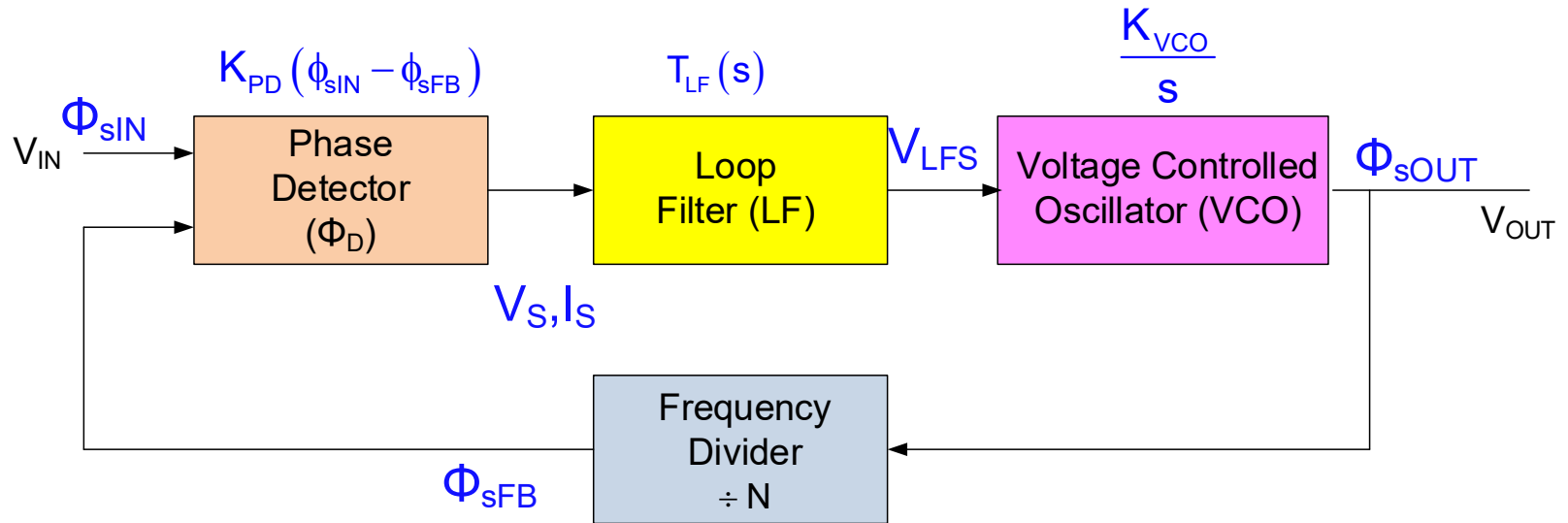- When locked, PLL can be modeled as a linear system
- Small-signal s-domain analysis when PLL is locked



Note: Dimensions of variables in loop are not the same

$$V_S = K_{PD} (\phi_{sIN} - \phi_{sFB})$$

$$V_{LFS} = T_{LF}(s) V_S$$

$$\phi_{sOUT} = V_{LFS} \frac{K_{VCO}}{s}$$


$$\phi_{sFB} = \frac{\phi_{sOUT}}{N}$$

Solving, we obtain

$$T_{PLL}(s) = \frac{\phi_{sOUT}}{\phi_{sIN}} = \frac{T_{LF}(s) K_{PD} K_{VCO}}{s + T_{LF}(s) \frac{K_{VCO} K_{PD}}{N}}$$

Often the LF is low order

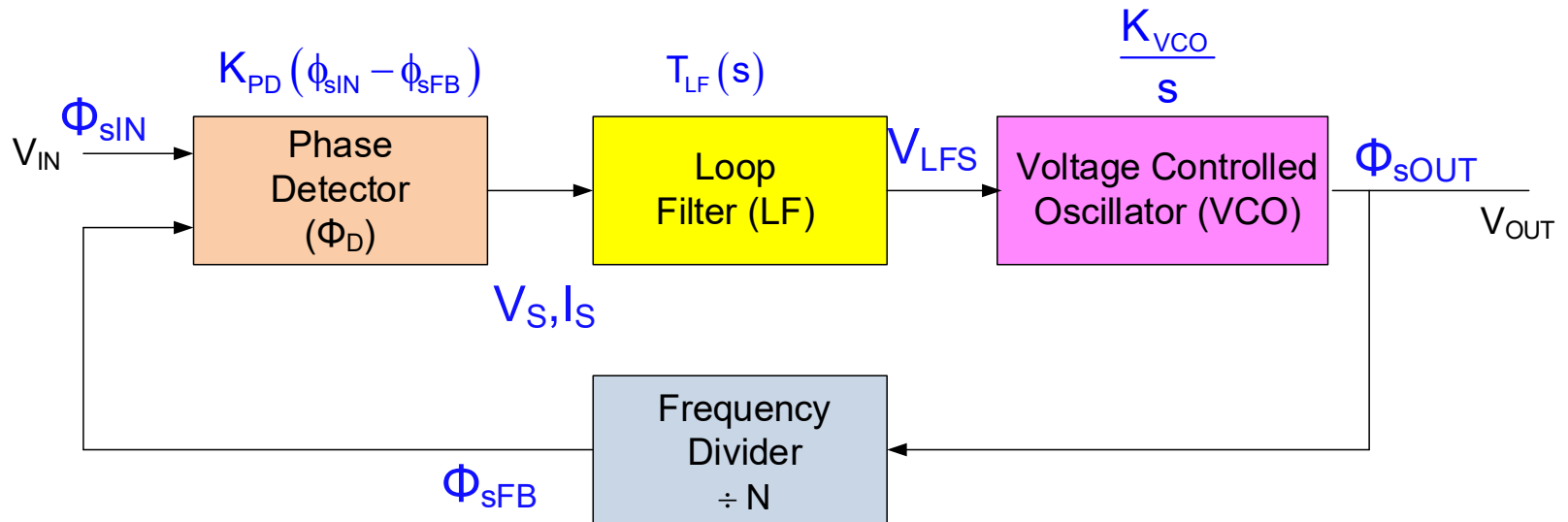Example: Assume $N=1$ and $T_{LF}(s) = \frac{1}{1+RCs}$




$$T_{PLL}(s) = \frac{T_{LF}(s)K_{PD}K_{VCO}}{s + T_{LF}(s)K_{VCO}K_{PD}} = \frac{K_{PD}K_{VCO}}{s(1+RCs) + K_{VCO}K_{PD}}$$

$$T_{PLL}(s) = \frac{\frac{K_{PD}K_{VCO}}{RC}}{s^2 + s\frac{1}{RC} + \frac{K_{VCO}K_{PD}}{RC}}$$

Often the LF is low order

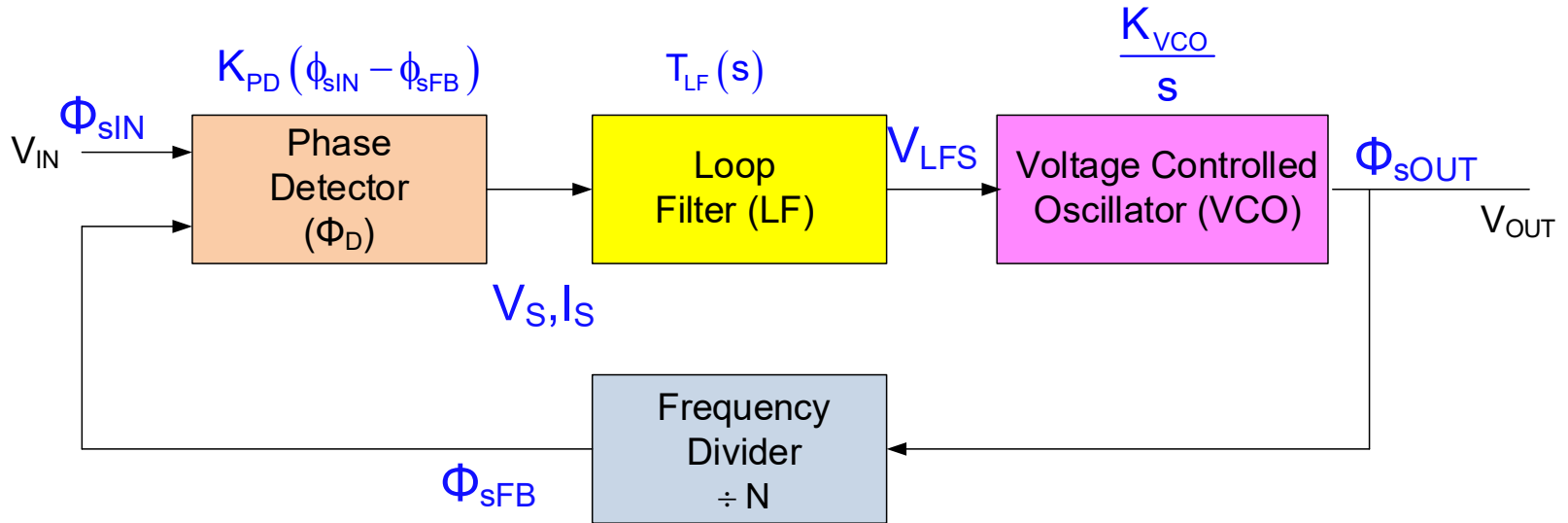Example: Assume $N=1$ and $T_{LF}(s) = \frac{1}{1+RCs}$



$$T_{PLL}(s) = \frac{K_{PD}K_{VCO}}{s^2 + s\frac{1}{RC} + \frac{K_{VCO}K_{PD}}{RC}}$$

$$s^2 + s\frac{1}{RC} + \frac{K_{VCO}K_{PD}}{RC} = s^2 + s\frac{\omega_0}{Q} + \omega_0^2$$

$$\omega_0 = \sqrt{\frac{K_{VCO}K_{PD}}{RC}}$$


$$Q = \sqrt{RC K_{VCO}K_{PD}}$$

Voltage Controlled Oscillators


Many different VCOs can be used

Voltage Controlled Oscillator (VCO)


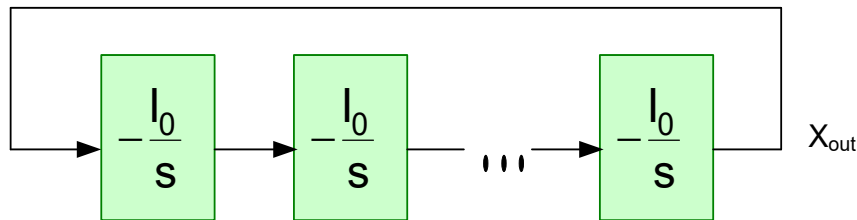
Assume I_0 is determined by a controlling voltage



Integrator-Based VCO

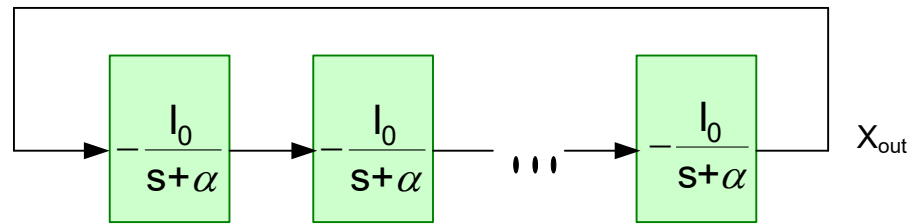


Lossy Integrator-Based VCO

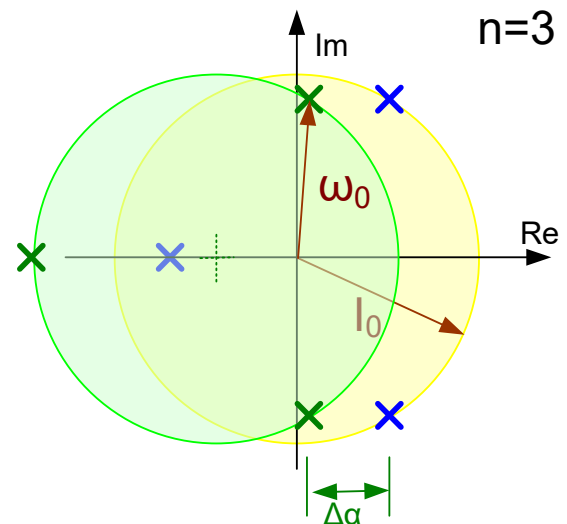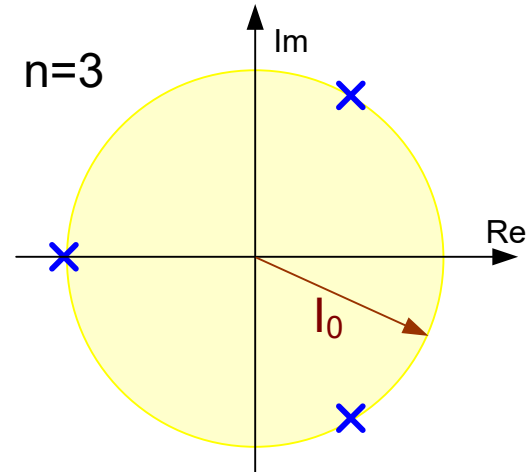

Voltage Controlled Oscillators


Voltage Controlled Oscillator (VCO)

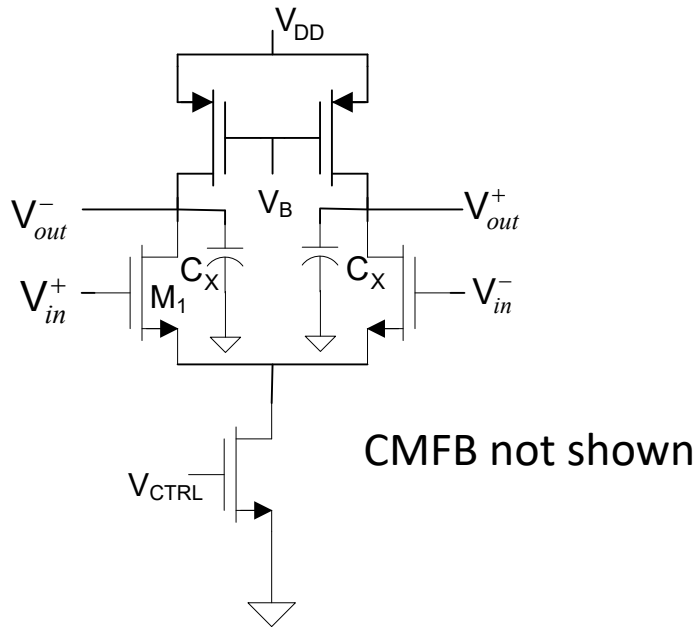

$$I_{0d}(s) = \frac{g_{m1}}{sC_X}$$

$$I_0 = \frac{g_{m1}}{C_X}$$

Integrator for: Integrator-based VCO

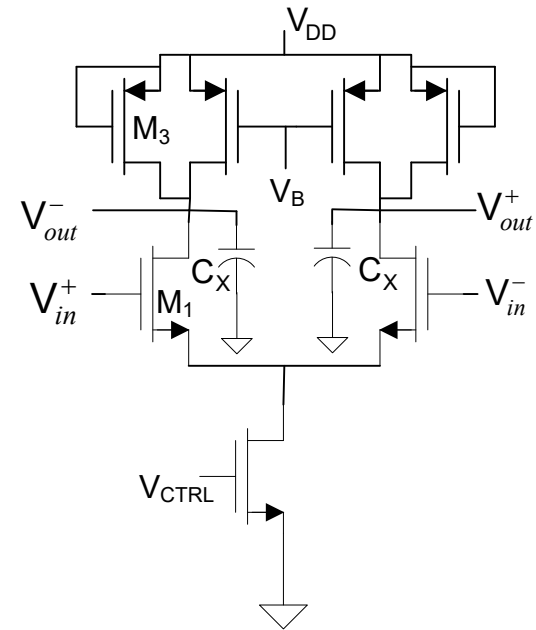

$$I_{0d}(s) = \frac{g_{m1}}{sC_X + g_{m3}}$$




$$I_0 = \frac{g_{m1}}{C_X} \quad \alpha = \frac{g_{m3}}{C_X}$$

Integrator for: Lossy Integrator-based VCO

Voltage Controlled Oscillators

Voltage Controlled Oscillator (VCO)

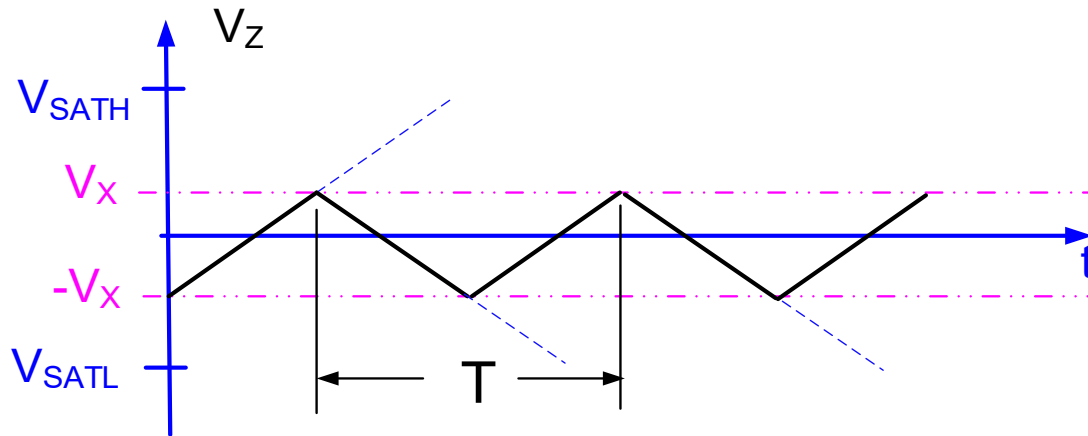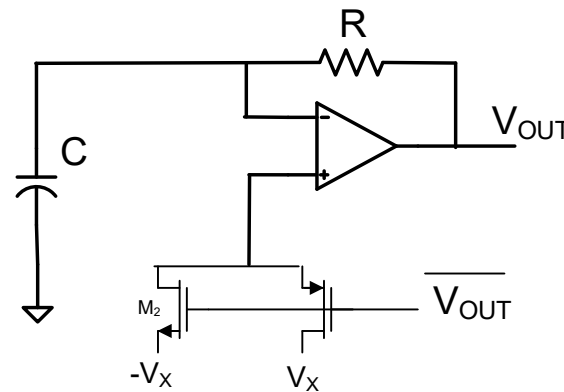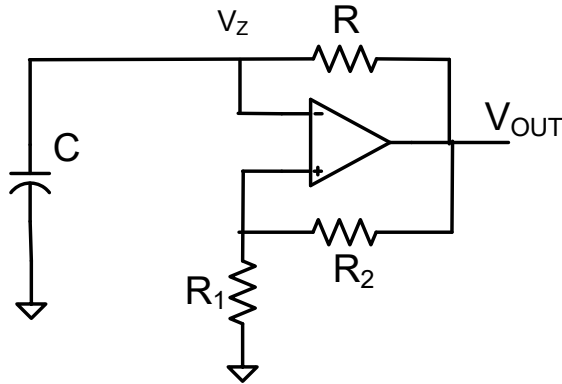Relaxation Oscillator Derived VCO (comparator not Op Amp)




V_Z is approximately triangle wave, V_{OUT} is square wave

Can have either triangle wave or square wave outputs


Phase Detectors

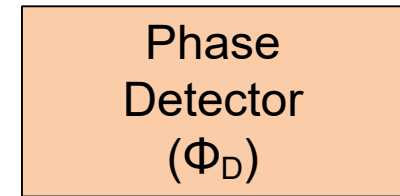Many different Phase Detectors can be used



Some Popular Phase Detector Circuits

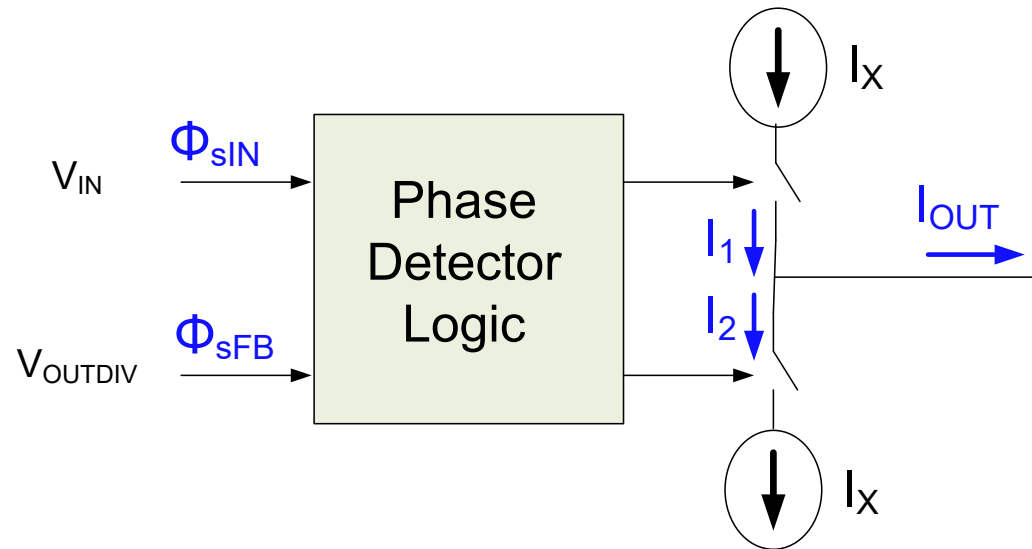- Analog Multiplier
- Exclusive OR Gate
- Sample and Hold
- Charge Pump



Charge-pump based Phase Detector


Average I_{OUT} is the average phase

Phase Detectors






Many different Phase Detectors can be used

Desired phase difference often 0° or 90°

Could be simply

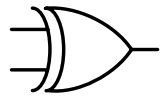


90° nominal phase diff

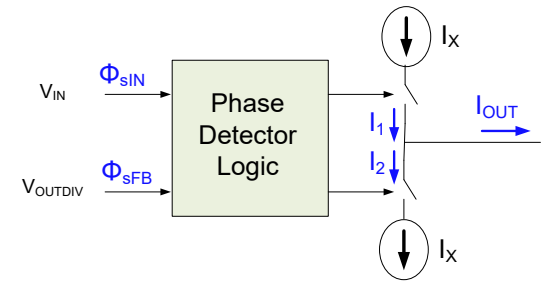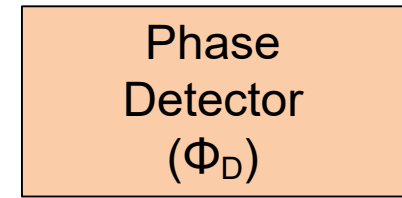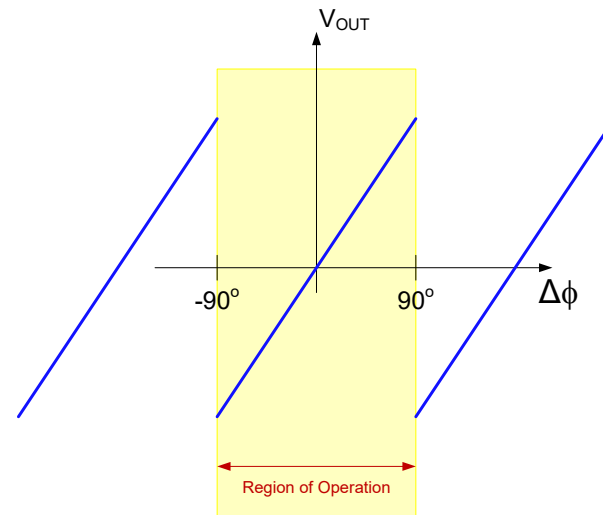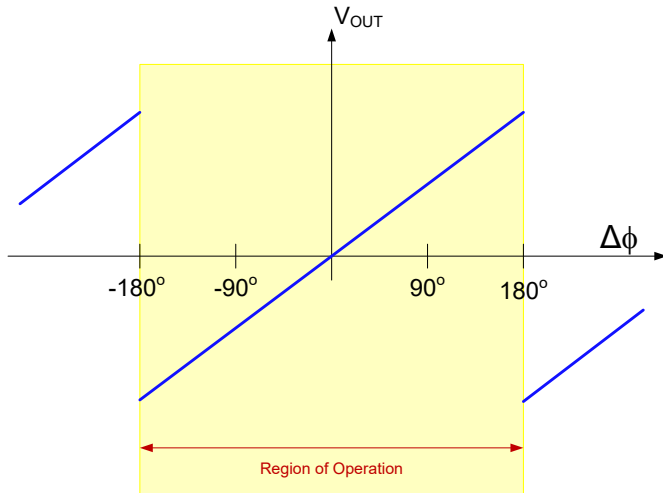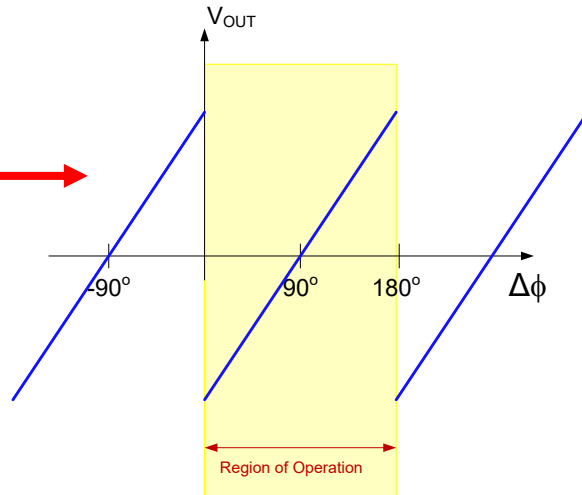


Average I_{OUT} is the average phase

Phase Detectors



Phase Detector (Φ_D)

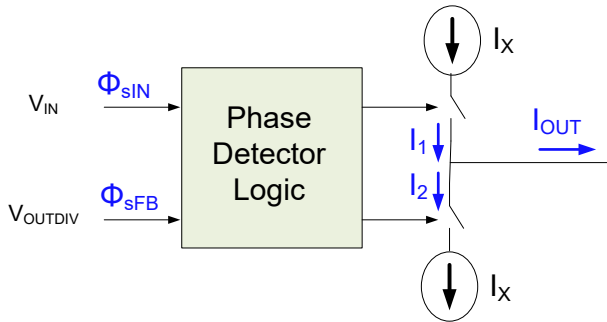



Average I_{OUT} is the average phase

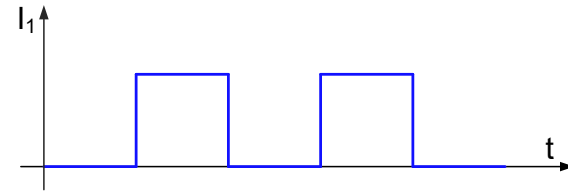


$\Delta\phi=0$

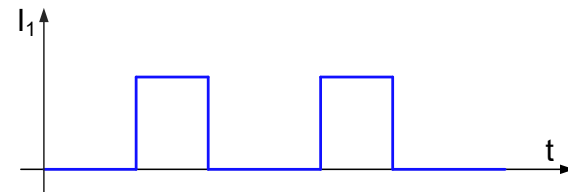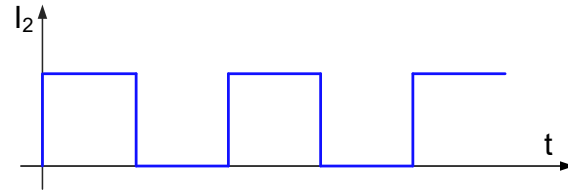

$\Delta\phi>0$

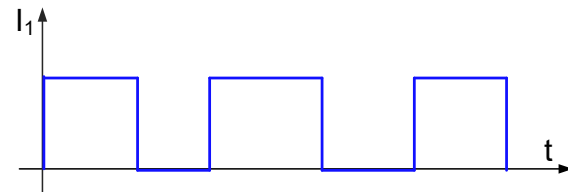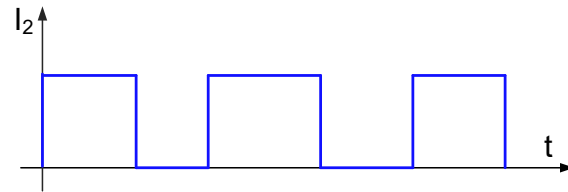


$\Delta\phi<0$

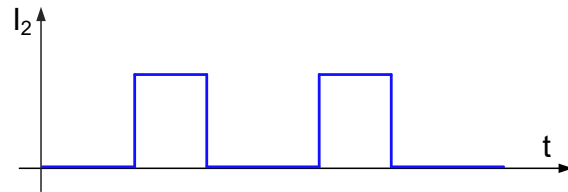


Phase Detectors

Phase Detector (Φ_D)

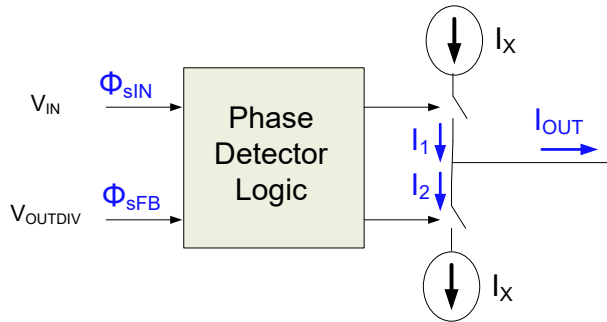

Average I_{OUT} is the average phase

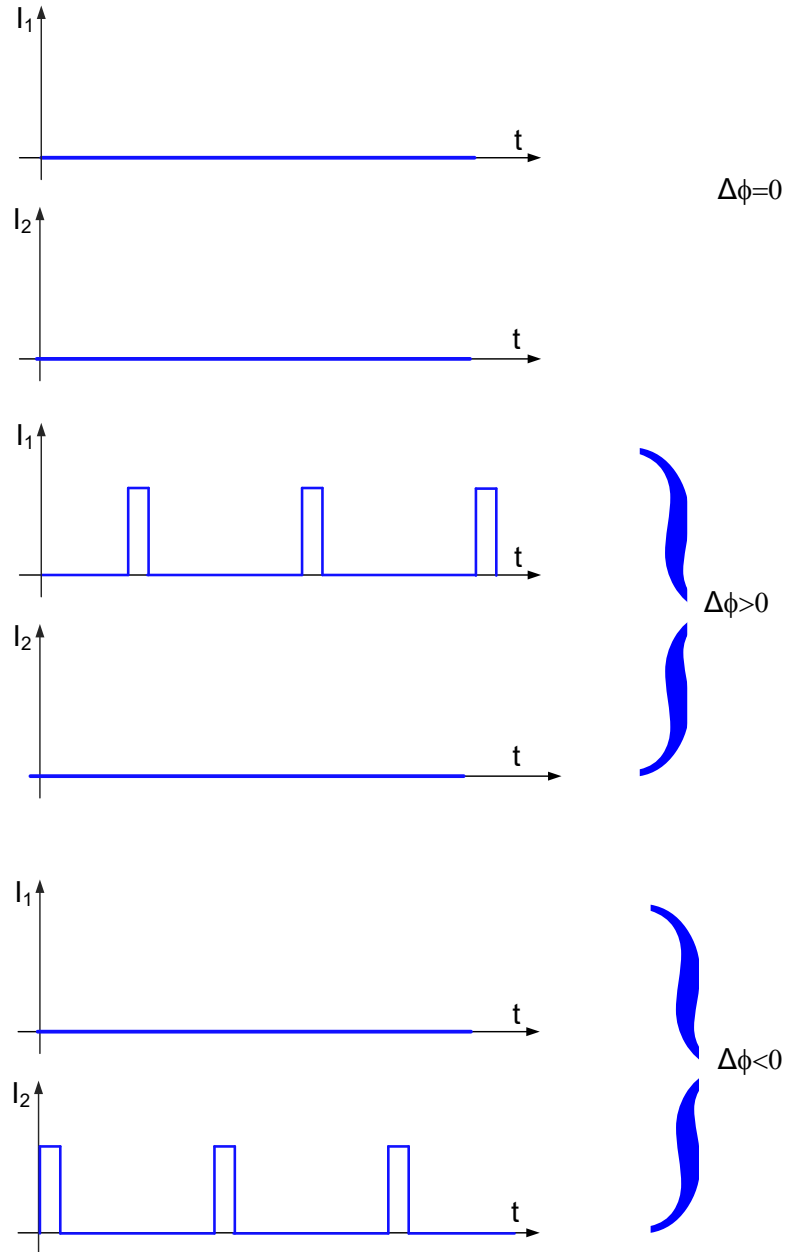


Vulnerable to dead zone problem

Loop Filters

Many different Phase Detectors can be used
Often the loop filter is first or second order
Usually the loop filter circuit is very simple

$T_{LF}(s)$


Loop
Filter (LF)

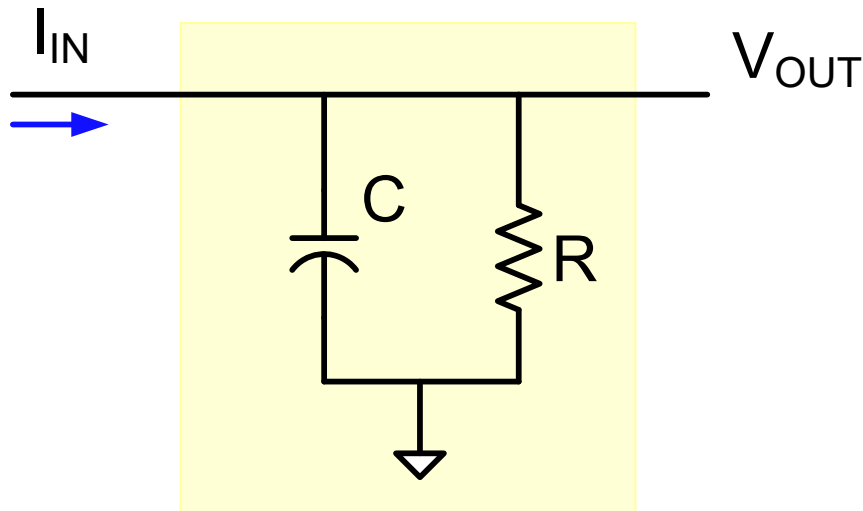

$$\frac{V_{OUT}}{I_{INAVG}} = T_{LF}(s) = \frac{R}{1+RCs}$$

Basic first-order LF with average current difference as input

What is the phase of a signal?

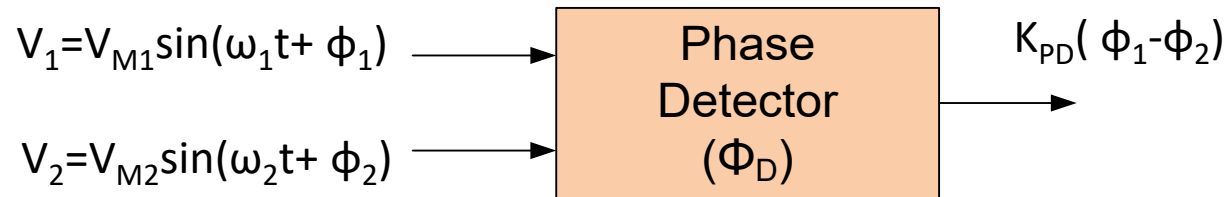


Assume $\omega_1 = \omega_2 = \omega$

If V_1 can be expressed as $V_1 = V_{M1} \sin(\omega t + \phi_1)$ the phase is ϕ_1

But what is the phase if ω is time varying? Or what is the “phase” if this functional form does not really characterize $V(t)$? Or what if $\omega_1 \neq \omega_2$?

What does a phase detector do if the two inputs are not at the same frequency?

What is the phase of a signal?

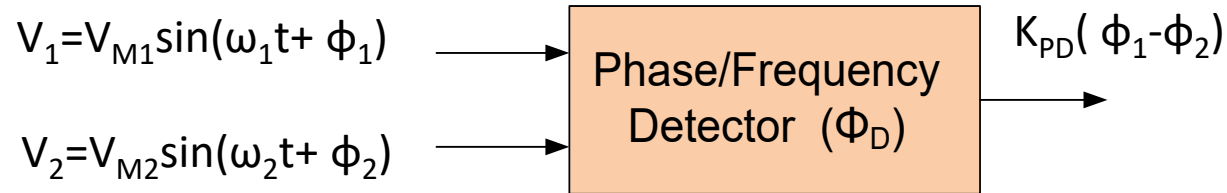

Most Phase Detectors are actually Phase/Frequency Detectors

- Large output when frequency difference exists
- Also provides output when phase difference exists after frequencies are matched



Stay Safe and Stay Healthy !

End of Lecture 43