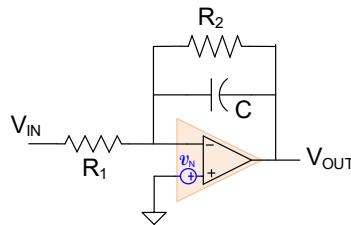


## Noise Analysis of Filter Structures

**Purpose:** The purpose of this experiment is to develop familiarity with methods for predicting the effects of noise on filter structures. This topic will be investigated both analytically and by computer simulations with a comparison of the results obtained by both methods. The computer simulations will be based upon both a time-domain and a frequency-domain noise analysis. To keep the analysis analytically tractable, a lossy integrator structure will be used as a test vehicle.

**Test Vehicle:** A lossy integrator is shown below. Assume the input-referred spectral density of the op amp is  $S_{INV} = 8\text{nV} / \sqrt{\text{Hz}}$  ( $S_{IN} = S_{INV}^2$ ). In this circuit assume  $R_1=1\text{K}$ ,  $R_2=100\text{K}$  and  $C=100\text{nF}$ .



**Part 1** Derive an expression for the noise spectral density of the output voltage of the lossy integrator in terms of  $R_1$ ,  $R_2$ ,  $C$ , and  $v_N$ . From the results of this derivation, plot the output noise spectral density with the values of  $R_1$ ,  $R_2$ ,  $C$ , and  $v_N$  specified above.

**Part 2** Do a frequency-domain spectral analysis of this integrator in Spectre and compare the results with those obtained in Part 1.

**Part 3** Do a time-domain noise analysis of this integrator in Spectre and compare the results with those obtained in Part 1.

**Part 4** Repeat Part 2 if the operational amplifier has a GB of 1MHz and compare the results with those obtained in Part 2.

**Part 5** Determine the input-referred noise spectral density of this lossy integrator.

**Part 6** Determine the signal to noise ratio at  $V_{OUT}$  if  $V_{IN}=5\sin(2\pi\cdot 10^4t)$

**Part 7** Which noise source is the dominant contributor to the noise in this circuit? What errors would be introduced in the noise analysis if only the noise in the dominant source is included in the noise analysis?